

**Texas A&M University
Department of Electrical and Computer Engineering**

ECEN 474/704 – (Analog) VLSI Circuit Design

Spring 2016

Exam #2

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are **5** pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		30
2		30
3		40
Total		100

Name: SAM PALERMO

UIN: _____


Problem 1 (30 points)

For the circuit shown below, assume that all transistors are operating in the saturation region. Calculate the following using these transistor parameters.

$$K_{PN} = \mu_n C_{ox} = 200 \mu A/V^2, V_{TH,N} = 0.4V, \lambda = 0.1V^{-1}$$

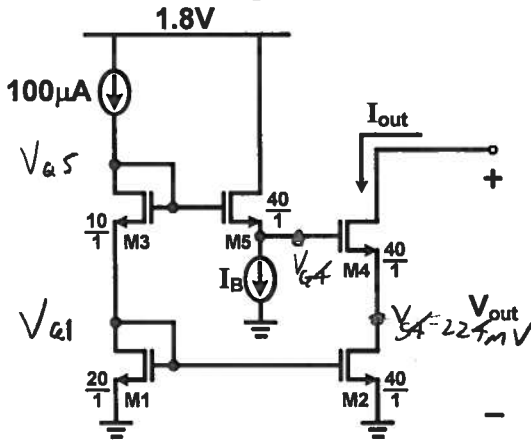- a) Output current, I_{out}
- b) Minimum output compliance voltage, such that all transistors remain in saturation, $V_{out,min}$. What is the value of I_B to achieve this?
- c) Output resistance, R_{out}

Note, for parts (a) and (b) you can neglect λ effects in the DC calculations, but you need to include λ effects for part (c).



$$I_{out} = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} I_{REF} = \frac{\left(\frac{40}{1}\right)}{\left(\frac{10}{1}\right)} 100 \mu A = 200 \mu A$$

$$V_{out,min} = V_{SAT2} + V_{SAT4} = 448 mV$$

$$V_{SAT2} = \sqrt{\frac{2(200 \mu A)}{(200 \mu A)(40/1)}} = 224 mV = V_{SAT4}$$

For minimum compliance voltage $\Rightarrow V_{S4} = 224 mV$

$$V_{G4} = V_{S4} + V_T + V_{OV4} = 224 mV + 0.4V + 0.224 mV = 0.848 V$$

$$V_{G1} = 0.4V + \sqrt{\frac{2(100 \mu A)}{200 \mu A (10/1)}} = 0.624 V$$

$$V_{G5} = 0.624 + 0.4 + \sqrt{\frac{2(100 \mu A)}{200 \mu A (40/1)}} = 1.34 V$$

$$I_B = \frac{\mu_n C_{ox}}{2} \left(\frac{W}{L}\right)_5 (V_{G5} - V_T)^2 = \frac{200 \mu A}{2} \left(\frac{40}{1}\right) (1.34 - 0.848 - 0.4)^2 = 33.9 \mu A$$

$$R_{out} = r_{o2} + r_{o4} + g_{m4} r_{o4} r_{o2}$$

$$r_{o2} = r_{o4} = \frac{1}{\lambda I_D} = \frac{1}{(0.1)(200 \mu A)} = 50 k \Omega$$

$$g_{m4} = \sqrt{2(200 \mu A) \left(\frac{40}{1}\right) (2)(200 \mu A)} = 1.79 mA/V$$

$$R_{out} = 50 k \Omega + 50 k \Omega + (1.79 mA/V)(50 k \Omega)^2 = 4.58 M \Omega$$

$$I_{out} = 200 \mu A$$

$$V_{out,min} = 0.448 V$$


$$I_B = 33.9 \mu A$$

$$R_{out} = 4.58 M \Omega$$

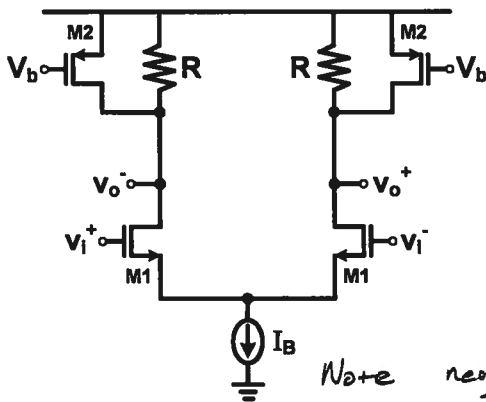Problem 2 (30 points)

For the fully differential amplifier below obtain the following:

- Give an expression for the differential gain, $A_{vd} = (v_o^+ - v_o^-) / (v_i^+ - v_i^-)$. **Do NOT neglect the transistors' r_o .** Assume all transistors are operating in saturation and that you can neglect body effect.
- Give an expression for the dominant pole of the amplifier. This expression should include all the appropriate transistor capacitances and include the Miller effect when appropriate.




a. $A_{vd} = \frac{g_{m1}}{g_{o1} + g_{o2} + G}$ where $G = \frac{1}{R}$

b. $\omega_p = \frac{g_{o1} + g_{o2} + G}{C_{oB1} + C_{eO1} + C_{oB2} + C_{eO2}}$

Note neglecting Miller in C_{eO1} because $1 - A_{vB} = 1 - \left(\frac{1}{A_{vD}}\right)$
 this is generally very small

- Now a more complete schematic is shown with biasing and transistor sizes. Assuming that the input common-mode can be as high as 1.3V, select R to achieve the maximum gain, while allowing all transistors to remain in saturation. What is the maximum gain, $A_{v,max}$? Use the following transistor parameters.

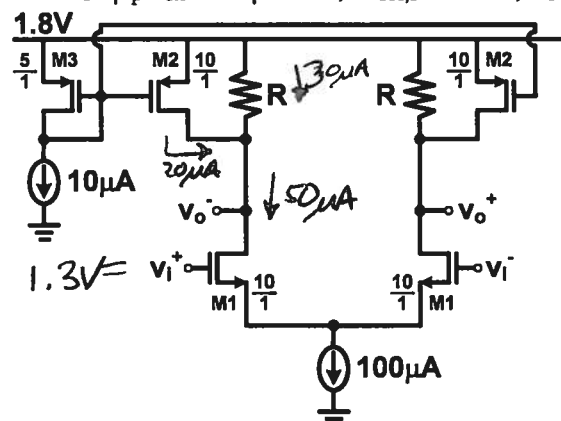$K_{PN} = \mu_n C_{ox} = 200 \mu A/V^2$, $V_{TH,N} = 0.4V$, $\lambda_N = 0.1V^{-1}$
 $K_{PP} = \mu_p C_{ox} = 100 \mu A/V^2$, $V_{TH,P} = -0.4V$, $\lambda_P = 0.1V^{-1}$



If $V_{i,cm} = 1.3V \Rightarrow$ Min $V_o = 0.9V$

Max $R = \frac{1.8V - 0.9V}{30\mu A} = 30k\Omega$

$g_{m1} = \sqrt{200\mu (10)(2)(50\mu)} = 447\mu A/V$

$g_{o1} = (0.1)(50\mu) = 5\mu A/V$

$g_{o2} = (0.1)(20\mu) = 2\mu A/V$

$A_{v,max} = \frac{447\mu}{5\mu + 2\mu + \frac{1}{30k}} = 11.1$


$R_{max} = 30k\Omega$

$A_{v,max} = 11.1 V/V$

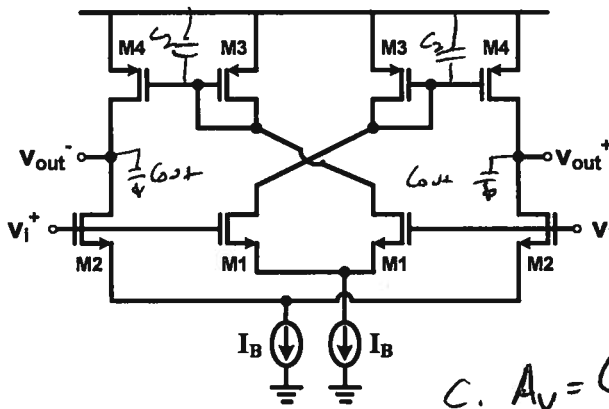Problem 3 (40 points)

For the amplifier below, assume all transistors are operating in saturation and that you can neglect body effect. Obtain expressions for the following:

- Small-signal transconductance.
- Output resistance.
- DC gain.
- The amplifier's two poles. Note, it's OK here to state this as a function of an effective capacitance at a certain node, but make sure to appropriately label the nodes.
- Output referred noise current power spectral density. Consider only thermal noise and include all important noise sources.
- Input referred noise voltage power spectral density. Consider only thermal noise and include all important noise sources.



a.
$$\frac{g_{m1}g_{m4}}{g_{o1} + g_{o3} + g_{m3}} + g_{m2}$$

b.
$$R_{out} = \frac{1}{g_{o2} + g_{o4}}$$

c.
$$A_v = G_m R_{out} = \frac{\frac{g_{m1}g_{m4}}{g_{o1} + g_{o3} + g_{m3}} + g_{m2}}{g_{o2} + g_{o4}}$$

d.
$$\omega_{p1} = \frac{g_{o2} + g_{o4}}{C_{out}} \quad \omega_{p2} = \frac{g_{o1} + g_{o3} + g_{m3}}{C_2}$$

e.
$$\frac{i_{o,n}^2}{\Delta f} = (i_{o1}^2 + i_{o2}^2 + i_{o3}^2 + i_{o4}^2) \cdot 2 = \frac{16}{3} kT \left[g_{m1} \left(\frac{1}{g_{o1} + g_{o3} + g_{m3}} \right)^2 g_{m4}^2 + g_{m2} + g_{m3} \left(\frac{1}{g_{o1} + g_{o3} + g_{m3}} \right)^2 g_{m4}^2 + g_{m4} \right]$$

f.
$$\frac{v_{in}^2}{\Delta f} = \frac{i_{o,n}^2}{\Delta f} \left(\frac{1}{G_m} \right)^2$$

Scratch Paper