

**Texas A&M University
Department of Electrical and Computer Engineering**

ECEN 474 – (Analog) VLSI Circuit Design

Fall 2012

Exam #3

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are **5** pages (1 blank) in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		35
2		30
3		35
Total		100


Name: SAM PALERMO

UIN: _____

Problem 1 (35 points)

For the fully-differential amplifier below, assume all transistors are operating in saturation, the internal amplifier blocks have finite gain A and infinite bandwidth, and obtain expressions for the following:

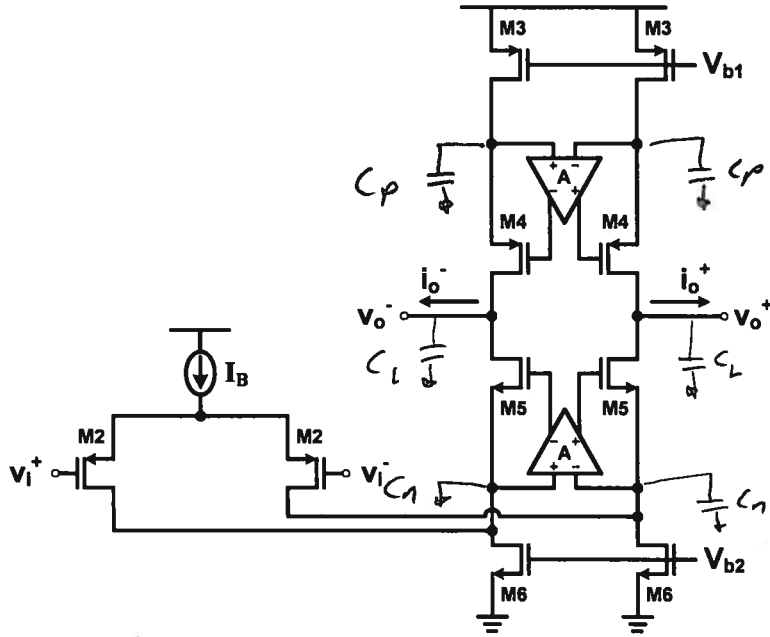- a) Small-signal differential transconductance, $(i_o^+ - i_o^-)/(v_i^+ - v_i^-)$.
- b) Fully differential amplifier DC gain, $A_{vd} = (v_o^+ - v_o^-)/(v_i^+ - v_i^-)$.
- c) The amplifier's ~~two~~ main poles. Note, it's OK here to state this as a function of an effective capacitance at a certain node, but make sure to appropriately label the nodes.



a. $G_m = g_{m2}$

$R_{out} = \left[r_{o5} g_{m5} (1+A) (r_{o6} \parallel r_{o2}) \right] \parallel \left[r_{o4} g_{m4} (1+A) r_{o3} \right]$

b. $A_v = g_{m2} \left[r_{o5} g_{m5} (1+A) (r_{o6} \parallel r_{o2}) \right] \parallel \left[r_{o4} g_{m4} (1+A) r_{o3} \right]$


c. $p_1 = -\frac{1}{R_{out} + C_L}, p_2 = -\frac{g_{m4} (1+A)}{C_P}, p_3 = -\frac{g_{m5} (1+A)}{C_n}$

Problem 2 (30 points)

For the amplifier below, assume all transistors are operating in saturation **except for M5, which is in triode**, and obtain expressions for the following:

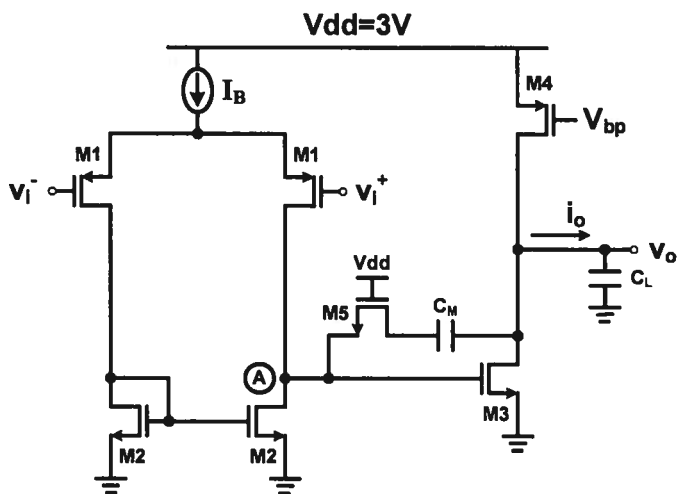- a) Small-signal transconductance.
- b) The amplifier's two main poles. Note, it's OK to neglect the transistor capacitors here.
- c) What is the value of $(W/L)_5$ that sets the main compensation zero to infinity? For this calculation, use the following:

$(W/L)_3 = (6\mu/0.6\mu)$, $V_{T0} = 1V$, $\gamma = 0V^{1/2}$, $\mu C_{ox} = 100\mu A/V^2$, $V_{dd} = 3V$, Node A DC operating point = 1.5V



$$a. G_m = \left(-\frac{g_{m1}}{g_{o1} + g_{o2}} \right) (-g_{m3}) = \frac{g_{m1} g_{m3}}{g_{o1} + g_{o2}}$$

$$b. P_1 \approx -\frac{(g_{o1} + g_{o2})(g_{o3} + g_{o4})}{C_M g_{m3}}$$

$$P_2 \approx -\frac{g_{m3}}{C_L}$$

$$\left(\frac{W}{L}\right)_5 = \frac{6\mu}{0.6\mu}$$

$$c. \omega_z = \left(\frac{1}{g_{m3}} - R_z\right) C_M$$

For $\omega_z \Rightarrow \infty$, need $R_z = \frac{1}{g_{m3}}$

$$R_z = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_5 (V_{GS5} - V_T)} \quad , \quad g_{m3} = \mu_n C_{ox} \left(\frac{W}{L}\right)_3 (V_{GS3} - V_T)$$

$$\frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_5 (V_{GS5} - V_T)} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_3 (V_{GS3} - V_T)}$$


3

$$\left(\frac{W}{L}\right)_5 = \left(\frac{W}{L}\right)_3 \left(\frac{V_{GS3} - V_T}{V_{GS5} - V_T}\right) = \left(\frac{6}{0.6}\right) \left(\frac{1.5 - 1}{1.5 - 1}\right)$$

Problem 3 (35 points)

For the fully differential amplifier with common-mode feedback (CMFB) below, assume all transistors are operating in saturation, and obtain the following:

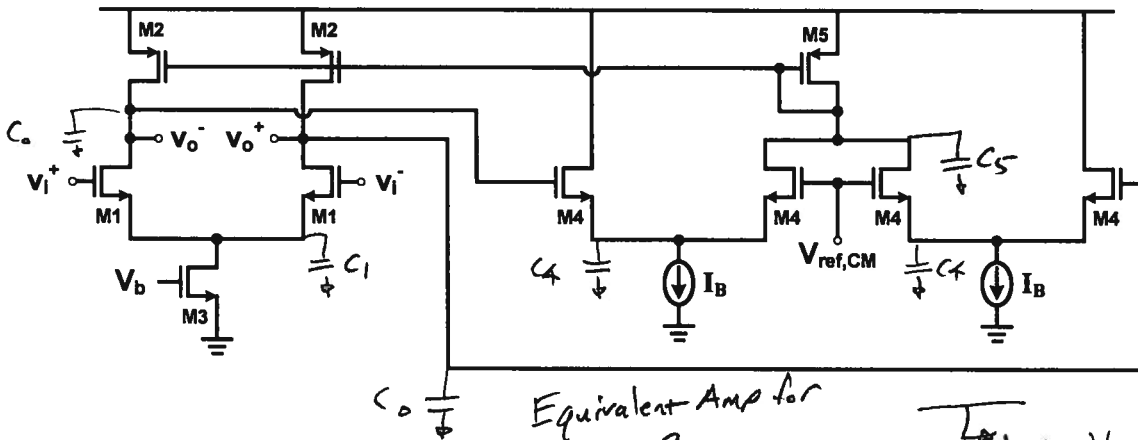
- a) Neglecting the CMFB network, give an expression for the fully differential amplifier DC gain, $A_{vd} = (v_{o+} - v_{o-}) / (v_{i+} - v_{i-})$.
- b) Give an expression for the CMFB loop DC gain.
- c) Give expressions for the poles of the CMFB loop. Note, it's OK here to state this as a function of an effective capacitance at a certain node, but make sure to appropriately label the nodes.



a.
$$A_{VD} = \frac{g_{m1}}{g_{o1} + g_{o2}}$$

Equivalent Amp for CMFB

AC and

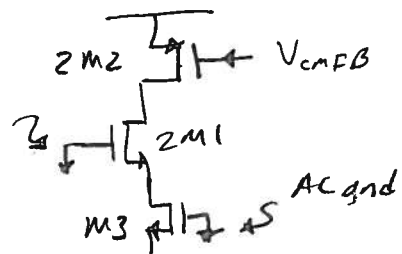

b.
$$\text{CMFB Loop Gain} = \left(\frac{g_{m4}}{g_{m5}} \right) (-2g_{m2}) \left(\frac{r_{o1}}{2} (2g_{m1} r_{o2}) \parallel \frac{r_{o2}}{2} \right)$$

$$\approx - \frac{g_{m4} g_{m2} r_{o2}}{g_{m5}}$$

c.
$$P_1 = - \frac{g_{o2}}{C_0} \quad , \quad P_2 = - \frac{2g_{m4}}{C_4} \quad , \quad P_3 = - \frac{g_{m5}}{C_5}$$

⇒ There is also a pole at $- \frac{2g_{m1}}{C_1}$ which will reduce

the "bottom" output impedance $\frac{r_{o1}}{2} (2g_{m1} r_{o2})$

However, the above 3 poles are enough for full credit

Scratch Paper