

# ECEN474/704: (Analog) VLSI Circuit Design Spring 2018

---

## Lecture 7: Table-Based ( $g_m/I_D$ ) Design



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

# Announcements & Agenda

---

- Reading
  - $g_m/I_D$  paper and book reference on website
    - Material is only supplementary reference
- Technology characterization for design
- Table-based ( $g_m/I_D$ ) design example
- Adapted from Prof. B. Murmann (Stanford) notes


# How to Design with Modern Sub-Micron (Nanometer) Transistors?

---

- Hand calculations with square-law model can deviate significantly from actual device performance
  - However, advanced model equations are too tedious for design
- Tempts designers to dive straight to simulation with little understanding on circuit performance trade-offs
  - “Spice Monkey” approach
- How can we accurately design when hand analysis models are way off?
- Employ a design methodology which leverages characterization data from BSIM simulations

# The Problem


---

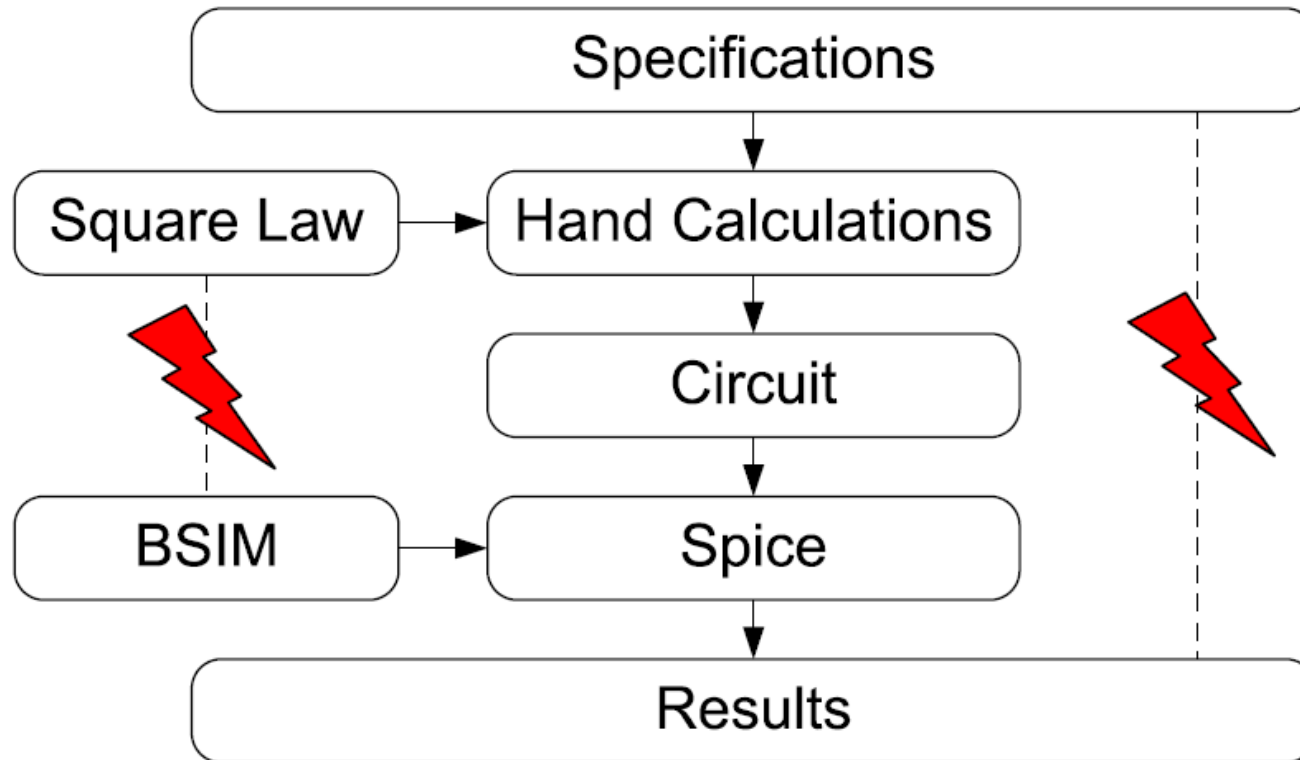

[Murmman]

# The Solution

---

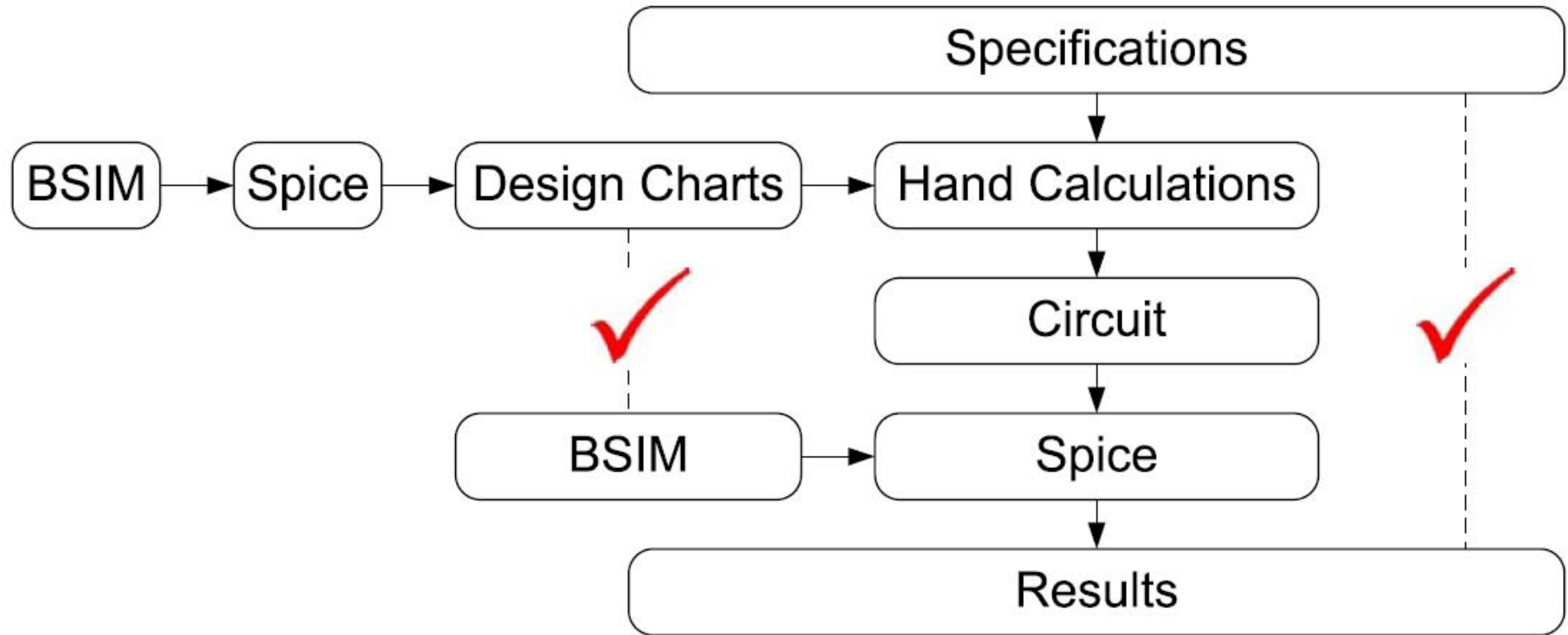


[Murmman]

# Technology Characterization for Design

---

- Generate data for the following over a reasonable range of  $g_m/I_D$  and channel lengths
  - Transit frequency ( $f_T$ )
  - Intrinsic gain ( $g_m/g_{ds}$ )
  - Current density ( $I_D/W$ )
- Also useful is extrinsic capacitor ratios
  - $C_{gd}/C_{gg}$  and  $C_{dd}/C_{gg}$
- Parameters are (to first order) independent of transistor width, which enables “normalized design”
- Do design hand calculations using the generated technology data
- Still need to understand how the circuit operates for an efficient design!!!


# $g_m/I_D$

 


- These plots tell us how much transconductance ( $g_m$ ) we can get for a given current ( $I_D$ )
- The transistor is a more efficient transconductor at low overdrive voltages
- A main trade-off will be the transistor frequency response ( $f_T$ )
- We will use  $g_m/I_D$  as the reference axis to compare other transistor parameters
 
# Intrinsic Transistor Gain ( $g_m/g_o$ )

NMOS Gain ( $g_m/g_o$ ) vs  $V_{ov}$ ,  $W=6\mu\text{m}$ ,  $V_{DS}=1.5\text{V}$




 
NMOS Gain ( $g_m/g_o$ ) vs  $g_m/I_D$ ,  $W=6\mu\text{m}$ ,  $V_{DS}=1.5\text{V}$



- These plots tell us how much intrinsic transistor gain we have
- The transistor has higher intrinsic gain at lower overdrive values due to the output resistance decreasing faster than the transconductance increases at higher current levels
- Plotted vs  $g_m/I_D$  shows that after a certain minimum level, the transistor gain is somewhat flat





# Transit Frequency, $f_T$

  

$$f_T = \frac{g_m}{2\pi(C_{GS} + C_{GD})} = \frac{g_m}{2\pi C_{gg}}$$

- The transit frequency is defined as the frequency when the transistor small-signal current gain goes to unity with the source and drain at AC grounds
- Overall, the ratio of  $g_m$  to  $C_{gg}$  comes up often in analog circuits, and is a good metric to compare the device frequency response (speed)
- Transistor  $f_T$  increases with overdrive voltage and high  $f_T$  values demand a low  $g_m/I_D$
- If you need high bandwidth, you have to operate the device at low efficiency


# Current Density, $I_D/W$

 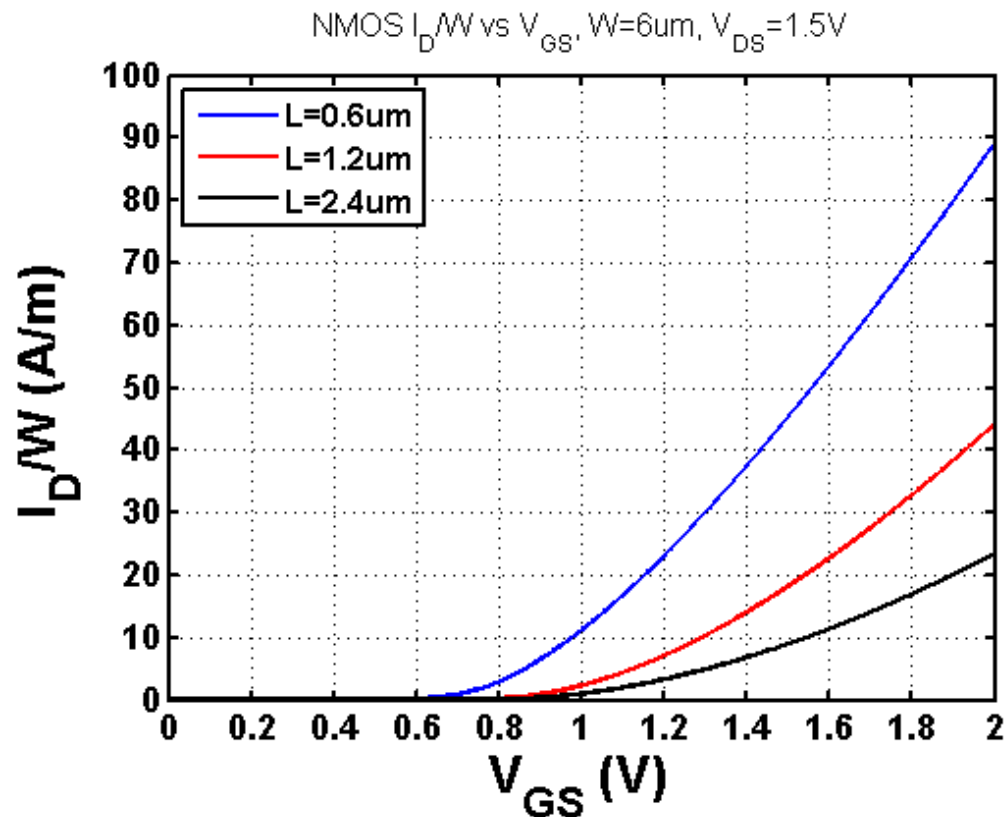

- Ultimately, we need to know how to size our devices to get a certain current
- The current density of a transistor increases with increased  $V_{GS}$  or overdrive voltage
- High  $g_m/I_D$  requires low current density, which implies bigger devices for a given current


# CS Amplifier Design Example

---

 

- Specifications
  - $0.6\mu\text{m}$  technology
  - $|A_v| \geq 4\text{V/V}$
  - $f_u \geq 100\text{MHz}$
  - $C_L = 5\text{pF}$
  - $V_{dd} = 3\text{V}$
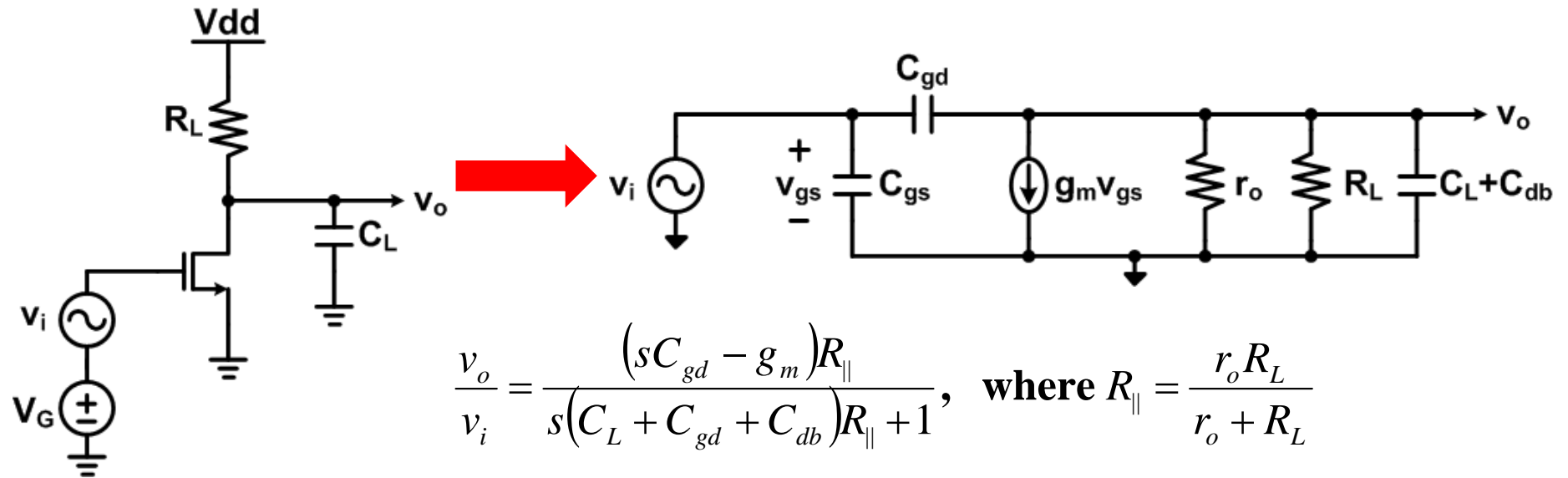
# CS Amplifier Small-Signal Model (No $R_S$ )



$$\frac{v_o}{v_i} = \frac{(sC_{gd} - g_m)R_{\parallel}}{s(C_L + C_{gd} + C_{db})R_{\parallel} + 1}, \quad \text{where } R_{\parallel} = \frac{r_o R_L}{r_o + R_L}$$

$$\omega_z = \frac{g_m}{C_{gd}} \quad (\text{located at very high frequency, } > \omega_T)$$

$$\omega_p = -\frac{1}{R_{\parallel}(C_L + C_{gd} + C_{db})} \approx -\frac{1}{R_L C_L}$$

$$A_v = -g_m R_{\parallel} \approx -g_m R_L$$

$$\omega_u = A_v \omega_p \approx \frac{g_m}{C_L}$$

# Design Procedure

---

1. Determine  $g_m$  from design specifications
    - a.  $\omega_u$  in this example
  2. Pick transistor L
    - a. Short channel  $\rightarrow$  high  $f_T$  (high bandwidth)
    - b. Long channel  $\rightarrow$  high  $r_o$  (high gain)
  3. Pick  $g_m/I_D$  (or  $f_T$ )
    - a. Large  $g_m/I_D \rightarrow$  low power, large signal swing (low  $V_{ov}$ )
    - b. Small  $g_m/I_D \rightarrow$  high  $f_T$  (high speed)
    - c. May also be set by common-mode considerations
  4. Determine  $I_D/W$  from  $I_D/W$  vs  $g_m/I_D$  chart
  5. Determine  $W$  from  $I_D/W$
- Other approaches exist

# 1. Determine $g_m$ (& $R_L$ )

---

- From  $\omega_u$  and DC gain specification

$$\omega_u = A_v \omega_p \approx \frac{g_m}{C_L}$$

$$g_m = \omega_u C_L = 2\pi(100\text{MHz})(5\text{pF}) = 3.14\text{mA/V}$$

**Note, this may be slightly low due to neglecting  $C_{gd}$  and  $C_{db}$**

$$A_v = -g_m R_{||} \approx -g_m R_L$$

$$R_L = \frac{A_v}{g_m}$$


**Adding 20% margin to compensate for  $r_o$  effects**

$$R_L = \frac{A_v}{g_m} = \frac{4.8}{3.14\text{mA/V}} = 1.5\text{k}\Omega$$

 
# 2. Pick Transistor L

- Need to look at gain and  $f_T$  plots

NMOS Gain ( $g_m/g_o$ ) vs  $g_m/I_D$ ,  $W=6\mu\text{m}$ ,  $V_{DS}=1.5\text{V}$



 NMOS  $f_T$  ( $g_m/C_{gg'}$ ) vs  $g_m/I_D$ ,  $W=6\mu\text{m}$ ,  $V_{DS}=1.5\text{V}$




- Since amplifier  $A_v \geq 4$ , min channel length ( $L=0.6\mu\text{m}$ ) will work with  $g_m/I_D \sim > 2$ 
  - Min channel length provides highest  $f_T$  at this  $g_m/I_D$  setting
 
### 3. Pick $g_m/I_D$ (or $f_T$ )

---

- Setting  $I_D$  for  $V_O=1.5V$  for large output swing range




$$\frac{g_m}{I_D} = \frac{3.14mA/V}{1mA} = 3.14V^{-1}$$



 
# Verify Transistor Gain & $f_T$ at $g_m/I_D$ Setting

NMOS Gain ( $g_m/g_o$ ) vs  $g_m/I_D$ ,  $W=6\mu\text{m}$ ,  $V_{DS}=1.5\text{V}$





 NMOS  $f_T$  ( $g_m/C_{gg}$ ) vs  $g_m/I_D$ ,  $W=6\mu\text{m}$ ,  $V_{DS}=1.5\text{V}$



- Transistor gain=30.6  $\gg$  amplifier  $A_V \geq 4$
- Transistor  $f_T=6.7\text{GHz}$   $\gg$  amplifier  $f_u=100\text{MHz}$
- $g_m/I_D$  setting is acceptable
 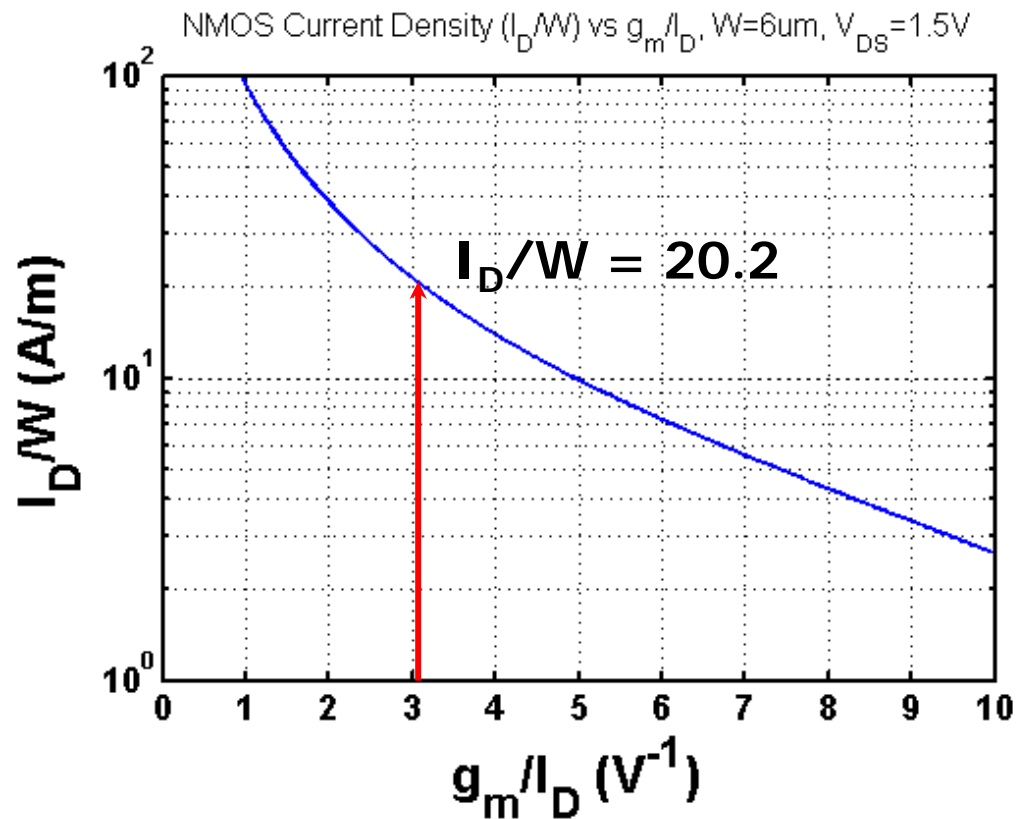
# 4. Determine Current Density ( $I_D/W$ )



- $g_m/I_D = 3.14\text{V}^{-1}$  maps to a current density of  $20.2\mu\text{A}/\mu\text{m}$

- Verify current density is achievable at a reasonable  $V_{GS}$
- $V_{GS} = 1.15\text{V}$  is reasonable with  $V_{DD} = 3\text{V}$  &  $V_{DS} = 1.5\text{V}$

## 5. Determine Transistor W from $I_D/W$


---

- From Step 3, we determined that  $I_D = 1\text{mA}$

$$W = \frac{I_D}{(I_D/W)} = \frac{1\text{mA}}{20.2\mu\text{A}/\mu\text{m}} = 49.5\mu\text{m}$$

- For layout considerations and to comply with the technology design rules
  - Adjust  $49.5\mu\text{m}$  to  $49.2\mu\text{m}$  and realize with 8 fingers of  $6.15\mu\text{m}$
  - This should match our predictions well, as the charts are extracted with a  $6\mu\text{m}$  device
    - Although it shouldn't be too sensitive to exact finger width

# Simulation Circuit

 

# Operating Point Information

## Design Value

N0:betaeff	9.97E-03	N0:csg	-3.68E-14	N0:qb	-5.03E-14
N0:cbb	2.48E-14	N0:css	4.32E-14	N0:qbd	-9.46E-14
N0:cbd	-1.28E-17	N0:cssbi	3.07E-14	N0:qbi	-5.03E-14
N0:cdbi	5.56E-14	N0:gbd	0	N0:qbs	0
N0:cbg	-8.56E-15	N0:gbs	1.03E-10	N0:qd	-3.72E-15
N0:cbs	-1.63E-14	N0:gds	1.02E-04	N0:qdi	-8.10E-15
N0:cbsbi	-1.63E-14	N0:gm	3.13E-03	N0:qg	8.07E-14
N0:cdb	-4.26E-15	N0:gms	7.64E-04	N0:qgi	7.06E-14
N0:cdd	1.25E-14	N0:gmoveryid	3.131	N0:qinv	4.20E-03
N0:cddb	-5.56E-14	N0:i1	9.99E-04	N0:qsi	-1.21E-14
N0:cdg	-2.87E-14	N0:i3	-9.99E-04	N0:qsrco	-2.66E-14
N0:cds	2.05E-14	N0:i4	-8.00E-14	N0:region	2
N0:cgb	-1.42E-14	N0:ibd	-8.00E-14	N0:reversed	0
N0:cgbovl	0	N0:ibs	0	N0:ron	1.50E+03
N0:cgd	-1.25E-14	N0:ibulk	-8.00E-14	N0:type	0
N0:cgdbi	5.07E-17	N0:id	9.99E-04	N0:vbs	0
N0:cgdovl	1.26E-14	N0:ids	9.99E-04	N0:vdb	1.502
N0:cgg	7.41E-14	N0:igb	0	N0:vds	1.502
N0:cggi	4.90E-14	N0:igcd	0	N0:vdsat	3.91E-01
N0:cgs	-4.74E-14	N0:igcs	0	N0:vfbeff	-9.65E-01
N0:cgsbi	-3.49E-14	N0:igd	0	N0:vgb	1.153
N0:cgsovl	1.26E-14	N0:igidl	0	N0:vgd	-3.49E-01
N0:cjd	5.56E-14	N0:igisl	0	N0:vgs	1.153
N0:cjs	0	N0:igs	0	N0:vgsteff	5.00E-01
N0:csb	-6.39E-15	N0:is	-9.99E-04	N0:vth	6.53E-01
N0:csd	-2.60E-17	N0:isub	0		
		N0:pwr	1.50E-03		

3.14mA/V

3.14V<sup>-1</sup>


1mA

$$\text{Total } C_{\text{gate}} = C_{\text{gg}} = 74.1\text{fF}$$

$$\text{Total } C_{\text{drain}} = C_{\text{dd}} + C_{\text{jd}} = 12.5\text{fF} + 55.6\text{fF} = 68.1\text{fF}$$

$$\text{Total } C_{\text{source}} = C_{\text{ss}} + C_{\text{js}} = 43.2\text{fF} + 0\text{fF} = 43.2\text{fF}$$

# AC Response

 

- Design is very close to specs
- Discrepancies come from neglecting  $r_o$  and  $C_{\text{drain}}$
- With design table information we can include estimates of these in our original procedure for more accurate results

# Next Time

---

- Single-Stage Amplifiers Frequency Response