

# ECEN474/704: (Analog) VLSI Circuit Design

## Fall 2018

---

### Lecture 10: Simple OTA



Sam Palermo  
Analog & Mixed-Signal Center  
Texas A&M University

# Announcements

---

- HW2 is due today
- No class on Thursday Mar 8

# Announcements & Agenda



---

- Simple OTA Parameters
- OTA w/ Cascode Load & Tail Current Source
  
- References
  - Razavi Chapters 4, 6, 9.8-9.11
  - Sedra/Smith Section 9.5.5

# OpAmps and OTAs



---

**OpAmp**

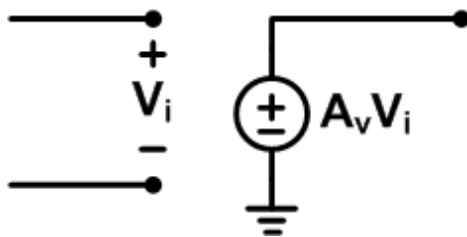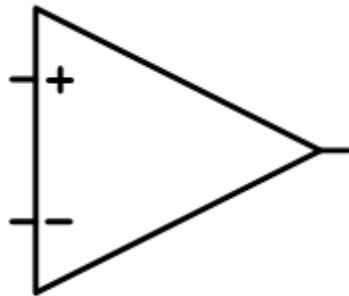


- High voltage gain
- High input impedance
- Voltage source output (low impedance)

**OTA**

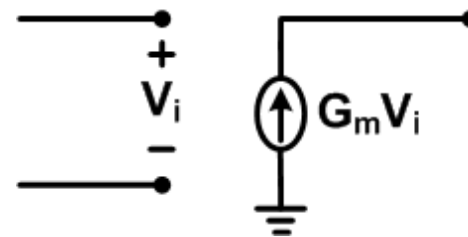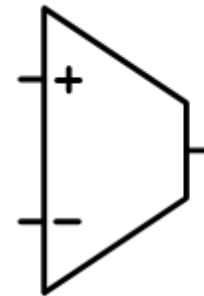


- High “voltage” gain
- High input impedance
- Current source output (high impedance)

# Operational Transconductance Amplifier

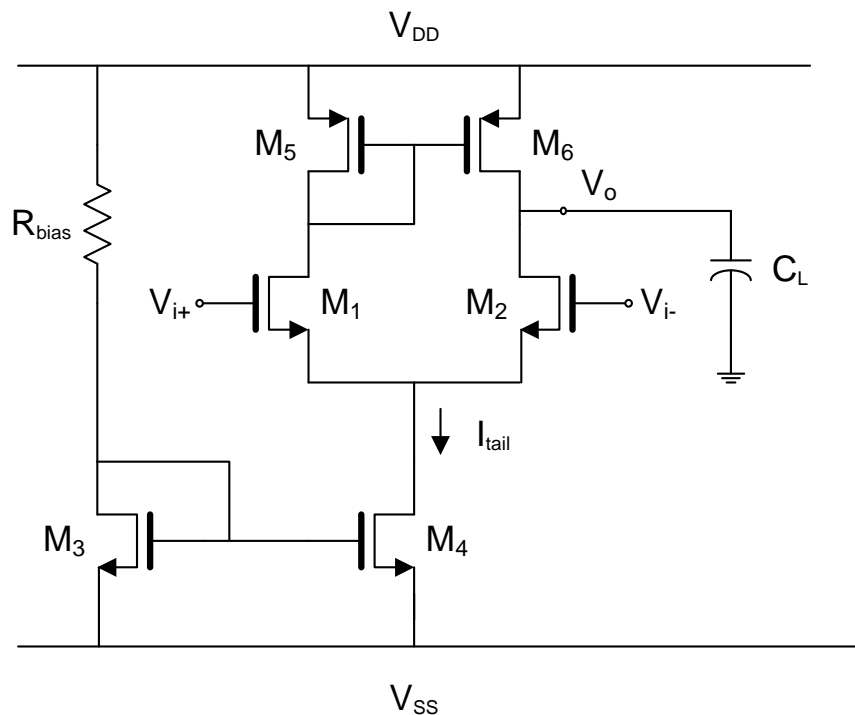

- Important Parameters
  - Differential Gain
  - Gain-Bandwidth Product
  - Common-Mode Input Range
  - Common-Mode Gain
  - Common-Mode Rejection Ratio (CMRR)
  - Power-Supply Rejection Ratio (PSRR)
  - Slew Rate

# OTA Differential Gain

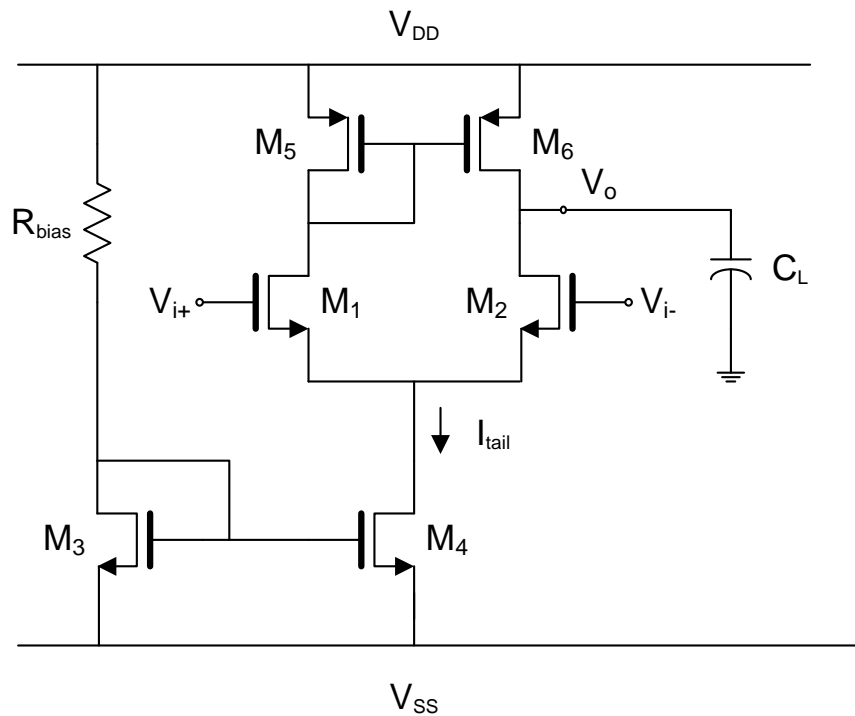

$$\text{Let } V_{i+} = \frac{v_{id}}{2} \text{ and } V_{i-} = -\frac{v_{id}}{2}$$


$$v_o = -g_{m2}r_{out} \left( -\frac{v_{id}}{2} \right) - \frac{g_{m1}}{g_{m5}} \left( -g_{m6}r_{out} \right) \left( \frac{v_{id}}{2} \right)$$

$$\text{By design } g_{m1} = g_{m2} \text{ and } g_{m5} = g_{m6}$$



$$v_o = g_{m1}r_{out}v_{id}$$

$$A_{DM} = \frac{v_o}{v_{id}} = g_{m1}r_{out} = \frac{g_{m1}}{g_{o6} + g_{o2}}$$

# Frequency Response

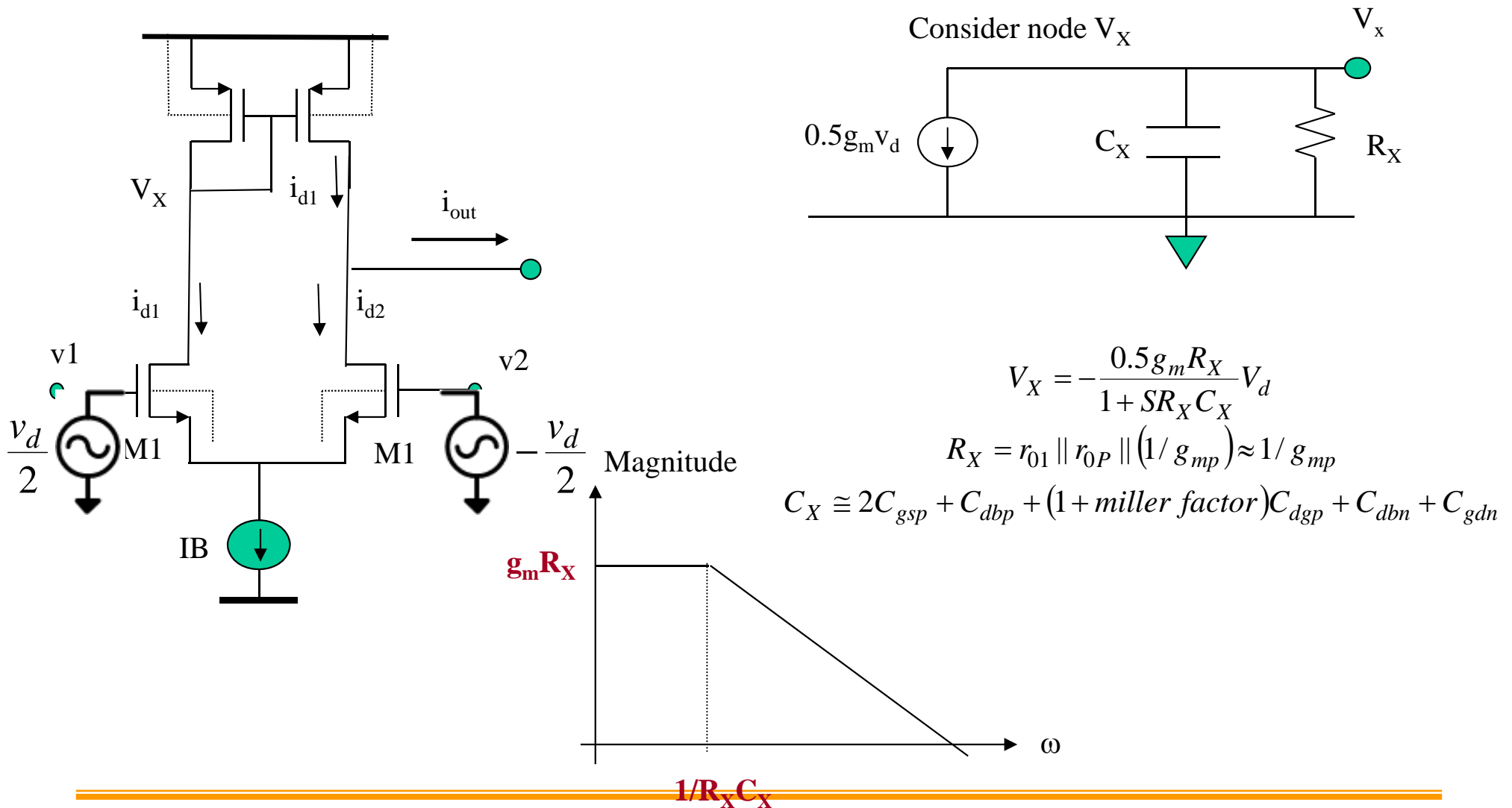

# Low Frequency Response

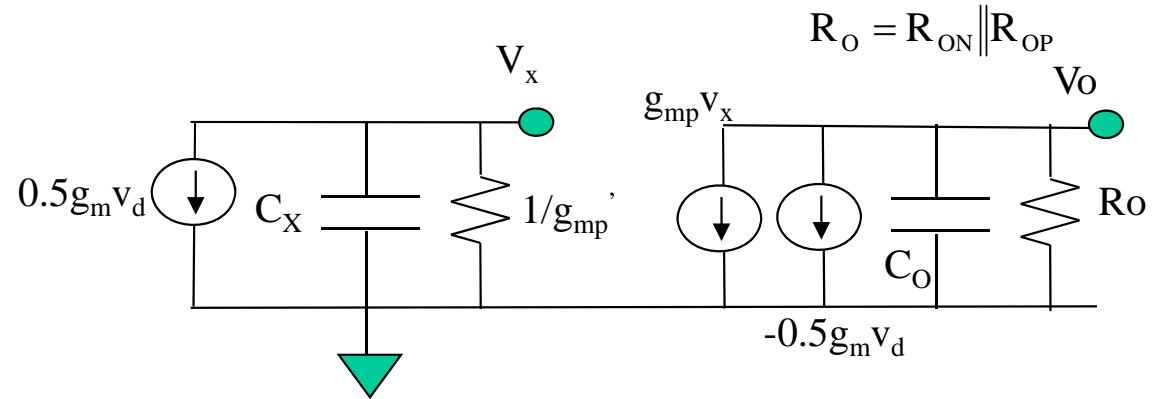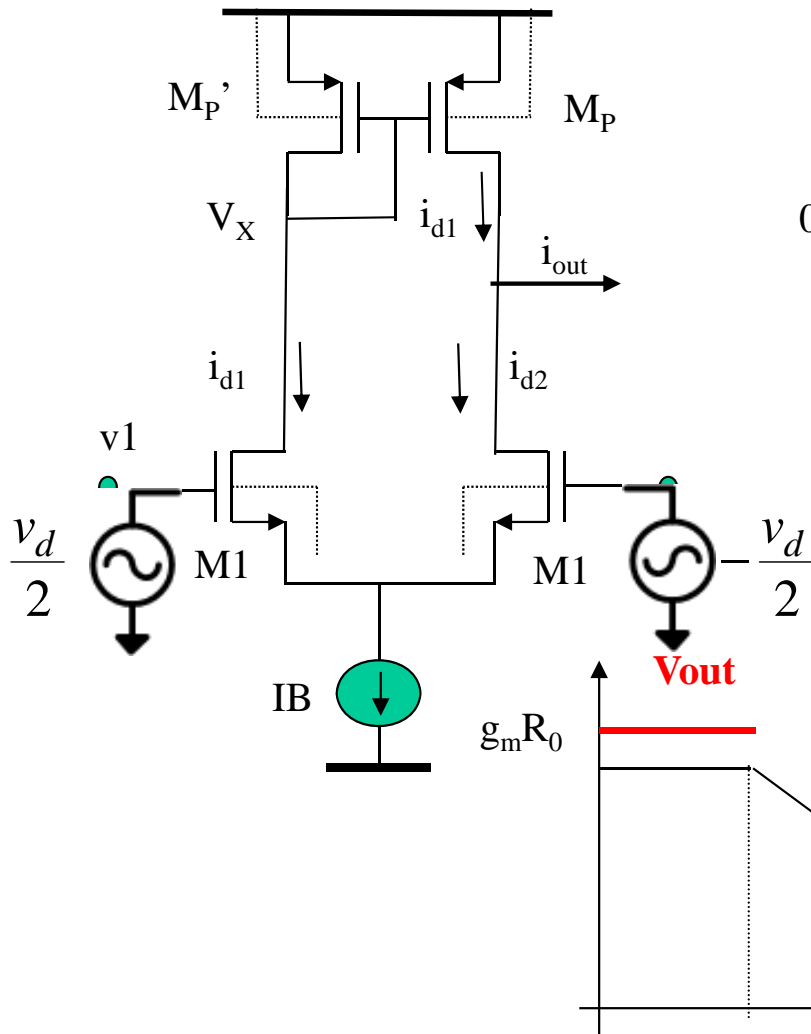

$$R_o = R_{ON} \parallel R_{OP}$$



$$v_o = -g_m \left( -\frac{v_d}{2} \right) R_o - g_m \left( \frac{v_d}{2} \right) R_x \left( -g_{mp} R_o \right)$$

$$R_x \approx \frac{1}{g_{mp}}$$


$$v_o = g_m v_d R_o$$



# Frequency Response

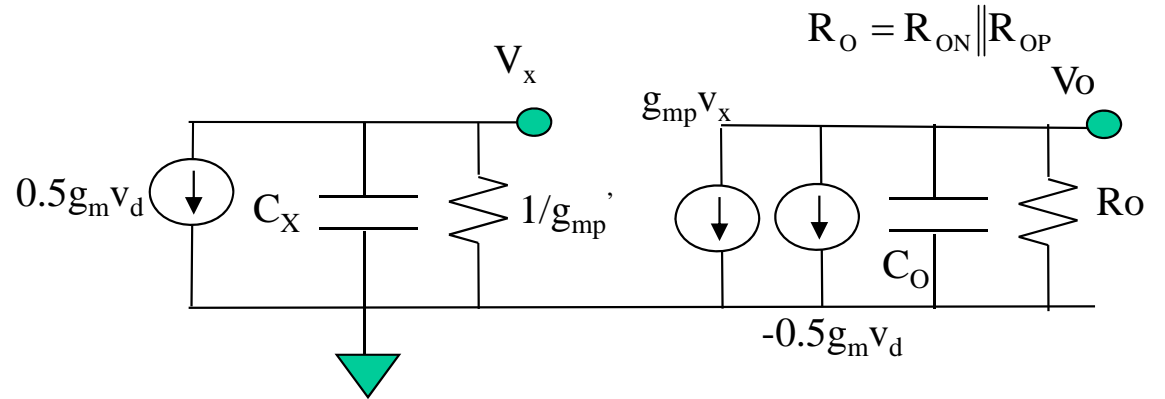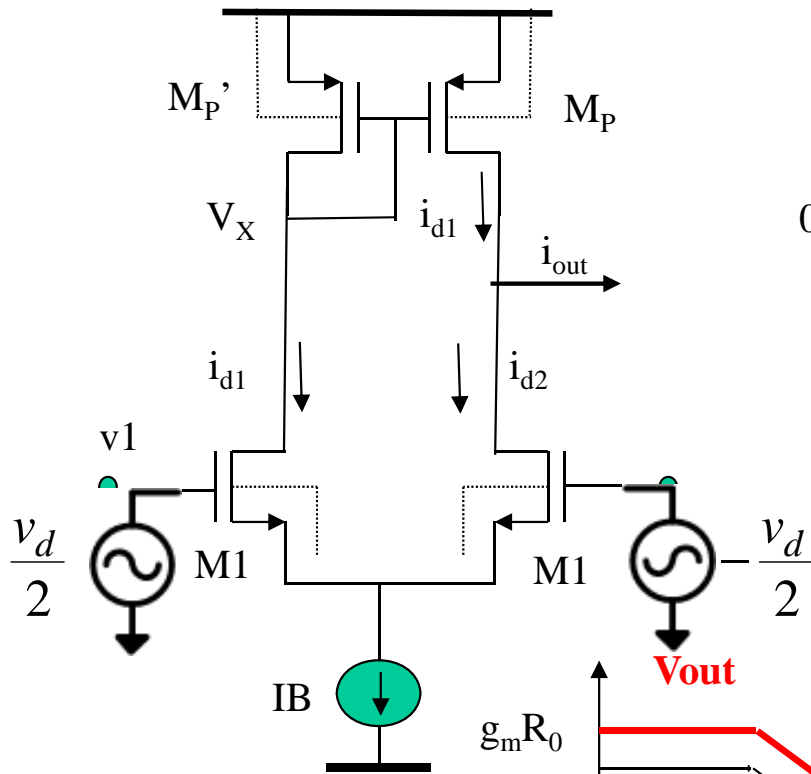

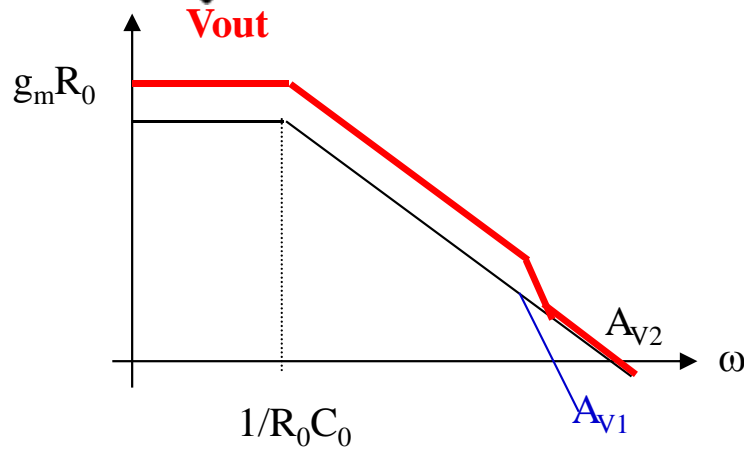
$$v_o = -g_m \left( -\frac{v_d}{2} \right) \frac{R_o}{1 + sR_o C_o} - g_m \left( \frac{v_d}{2} \right) \left( \frac{1/g_{mp}}{1 + s \frac{C_x}{g_{mp}}} \right) \left( -\frac{g_{mp} R_o}{1 + sR_o C_o} \right)$$



$$v_o = g_m R_o \left( \frac{v_d}{2} \right) \frac{1}{1 + sR_o C_o} \left[ 1 + \frac{1}{1 + s \frac{C_x}{g_{mp}}} \right]$$

$$v_o = g_m R_o \left( \frac{v_d}{2} \right) \frac{1}{1 + sR_o C_o} \left[ \frac{2 + s \frac{C_x}{g_{mp}}}{1 + s \frac{C_x}{g_{mp}}} \right]$$

# OTA Gain-Bandwidth Product (GBW)

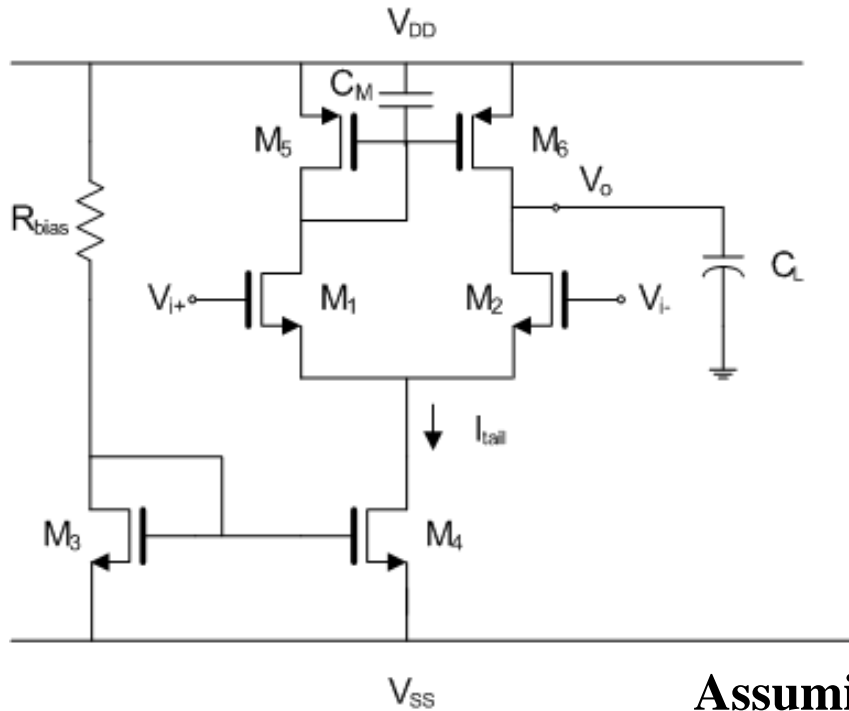


$$A_{DM} = \frac{g_{m1}}{g_{o6} + g_{o2}}$$

The circuit will have 2 poles

$\omega_{po}$  at the output node and  $\omega_{pm}$  at the "mirror" node


$$\omega_{po} \approx \frac{g_{o6} + g_{o2}}{C_L}, \quad \omega_{pm} \approx \frac{g_{m5}}{C_M}$$

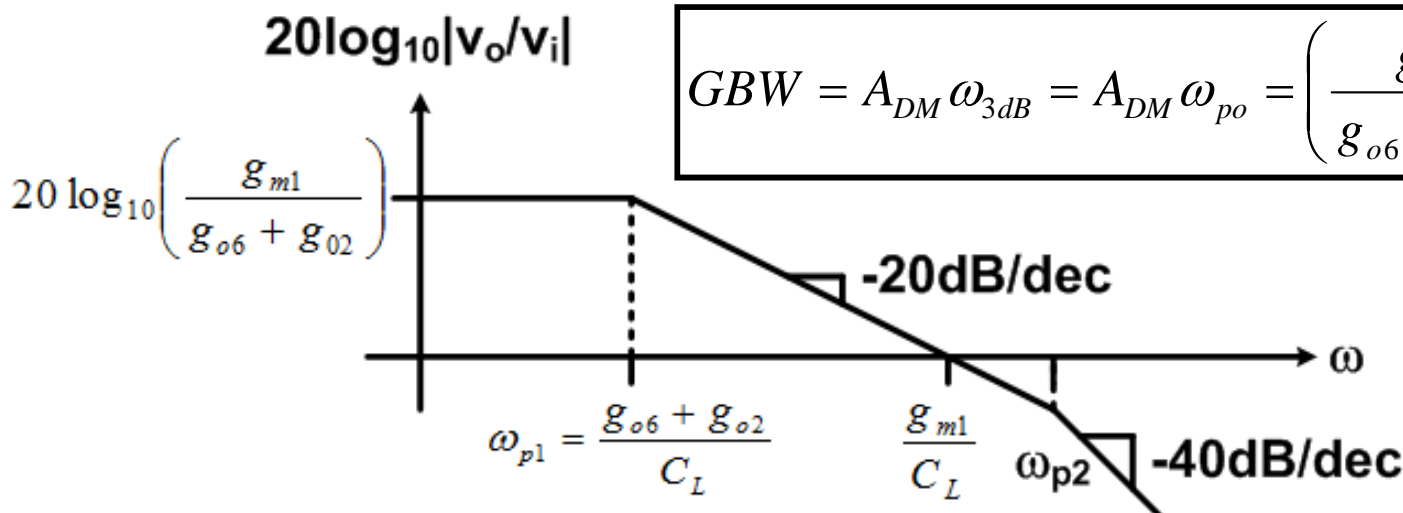Assuming the poles are widely spaced and  $\omega_{po}$  dominates



$$GBW = A_{DM} \omega_{3dB} = A_{DM} \omega_{po} = \left( \frac{g_{m1}}{g_{o6} + g_{o2}} \right) \left( \frac{g_{o6} + g_{o2}}{C_L} \right) = \frac{g_{m1}}{C_L}$$

# OTA Common-Mode Input Range

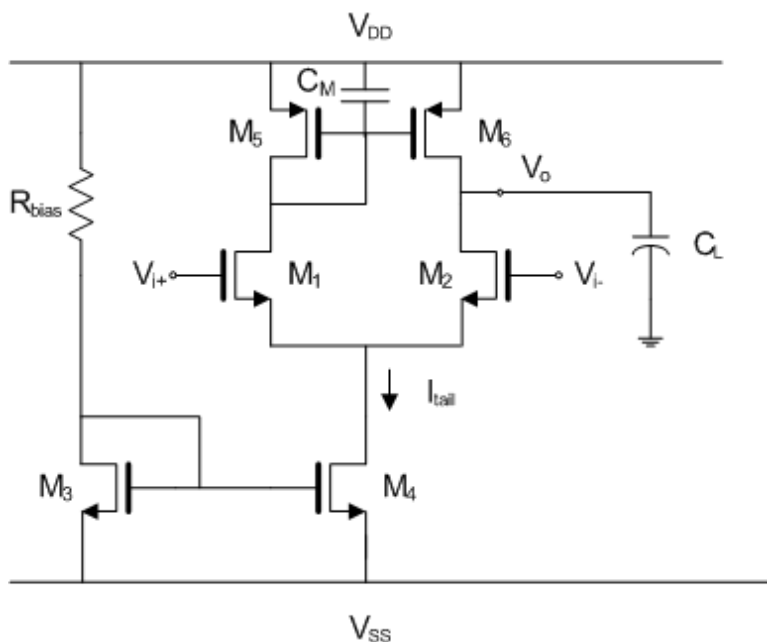

- Common-mode input range set by transistor saturation conditions

- Low-end set by tail current source saturation

$$V_{icm} \geq V_{SS} + V_{DSAT4} + V_{GS1} = V_{SS} + \sqrt{\frac{2I_{tail}}{\mu_n C_{ox} \frac{W}{L_4}}} + \sqrt{\frac{I_{tail}}{\mu_n C_{ox} \frac{W}{L_1}}} + V_{Tn1}$$


- High-end set by differential pair saturation

$$V_{icm} \leq V_{ocm} + V_{T1} = V_{DD} - V_{GS5} + V_{T1} = V_{DD} - \left( \sqrt{\frac{I_{tail}}{\mu_p C_{ox} \frac{W}{L_5}}} + |V_{Tp5}| \right) + V_{Tn1}$$

$$V_{SS} + \sqrt{\frac{2I_{tail}}{\mu_n C_{ox} \frac{W}{L_4}}} + \sqrt{\frac{I_{tail}}{\mu_n C_{ox} \frac{W}{L_1}}} + V_{Tn1} \leq V_{icm} \leq V_{DD} - \left( \sqrt{\frac{I_{tail}}{\mu_p C_{ox} \frac{W}{L_5}}} + |V_{Tp5}| \right) + V_{Tn1}$$

# OTA Common-Mode Gain


[Sedra]

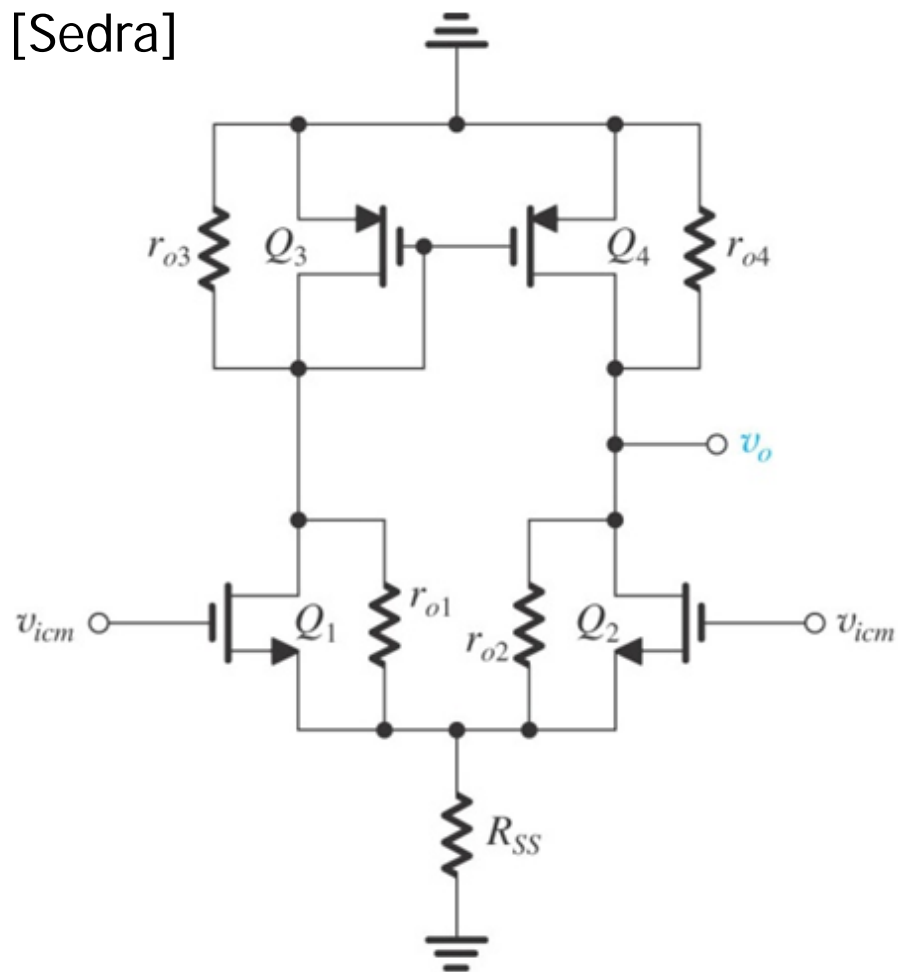

- Ideally, common-mode perturbations are suppressed by the differential amplifier, i.e.  $A_{cm} = 0$
- Finite common-mode gain exists due to amplifier asymmetries and finite tail current source impedance
- Note transistor numbers are different from previous slides, as I borrow figures from Sedra/Smith text

# OTA Common-Mode Gain

[Sedra]

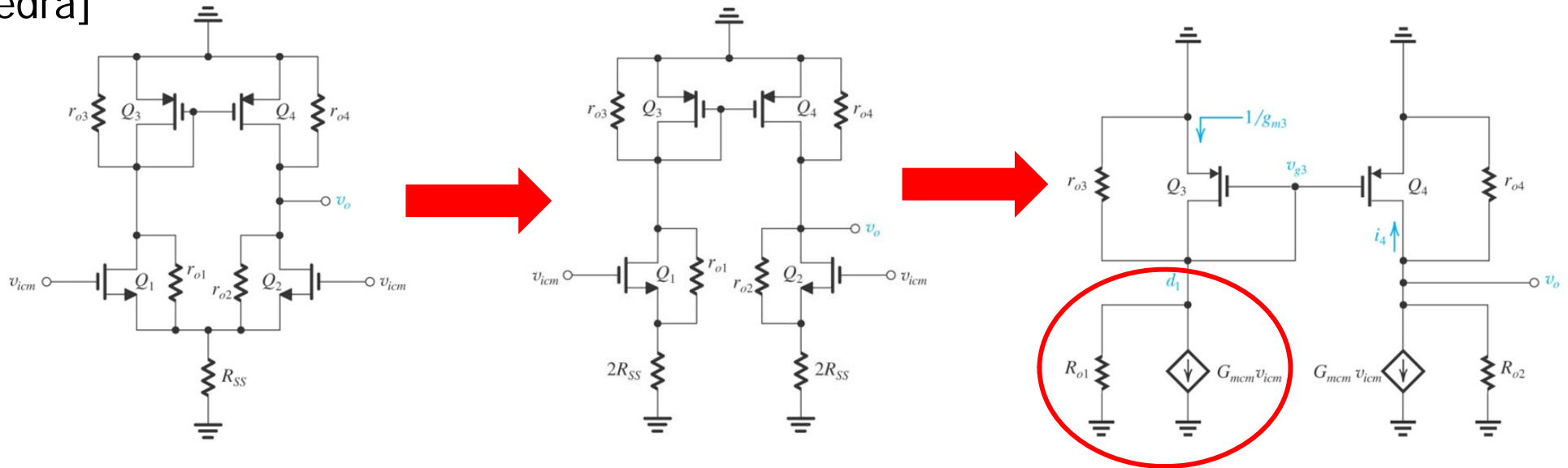


- Modeling the input transistors as a transconductance current source with a parallel output resistance

$$v_s = v_{icm} \frac{(2R_{SS} \parallel r_{o1})}{(2R_{SS} \parallel r_{o1}) + \frac{1}{g_{m1}}} \approx v_{icm}$$


$$i_o = \frac{v_{icm}}{2R_{SS}}$$
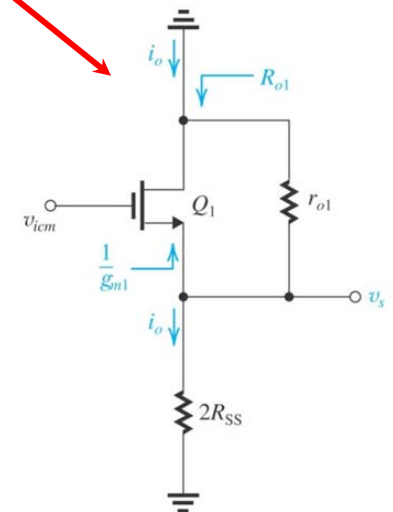
$$G_{mcm} = \frac{i_o}{v_{icm}} = \frac{1}{2R_{SS}}$$



# OTA Common-Mode Gain

[Sedra]

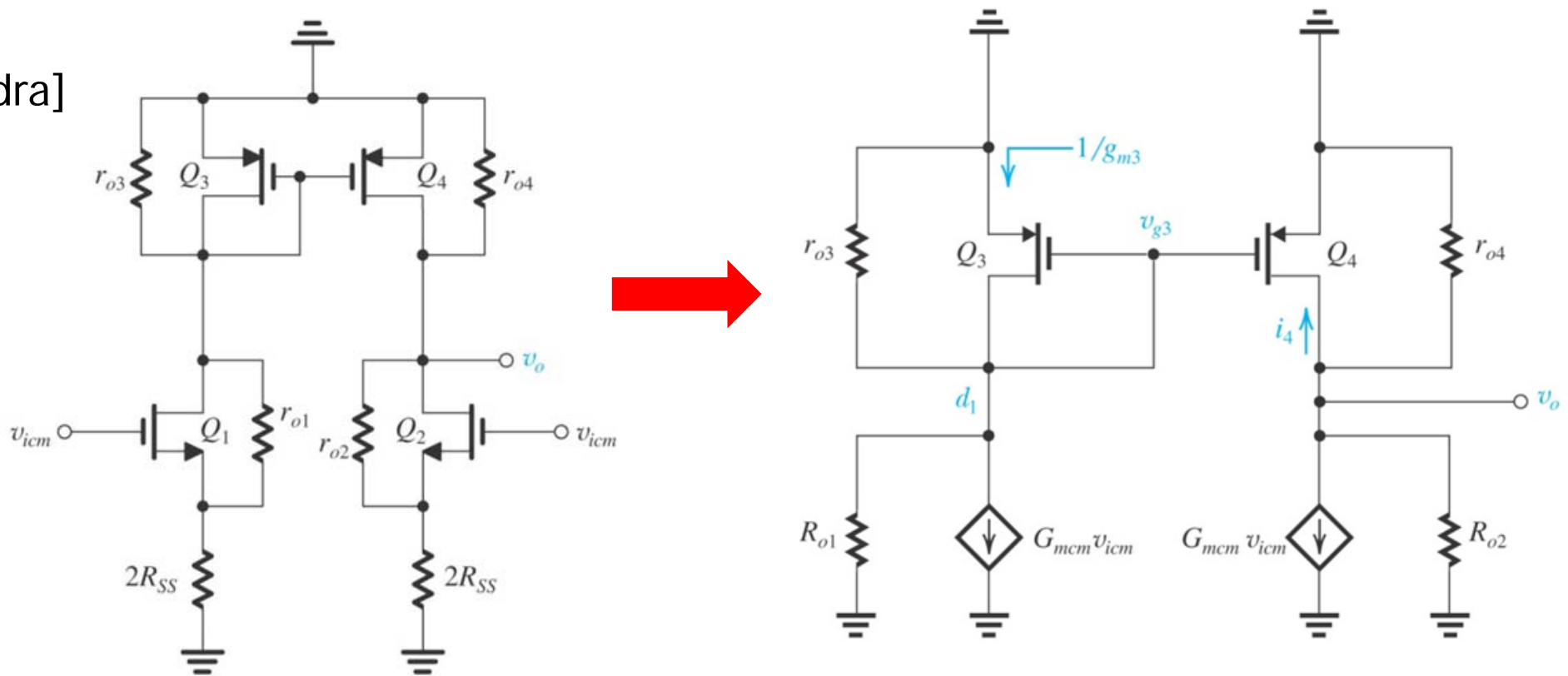

$$G_{mcm} = \frac{i_o}{v_{icm}} = \frac{1}{2R_{SS}}$$

$$R_{o1} = 2R_{SS} + r_{o1} + g_{m1}(2R_{SS})r_{o1}$$


$$R_{o2} = 2R_{SS} + r_{o2} + g_{m2}(2R_{SS})r_{o2}$$

$$v_{g3} = -G_{mcm} v_{icm} \left( R_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}} \right)$$

$$i_4 = -g_{m4} G_{mcm} v_{icm} \left( R_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}} \right)$$

# OTA Common-Mode Gain

[Sedra]

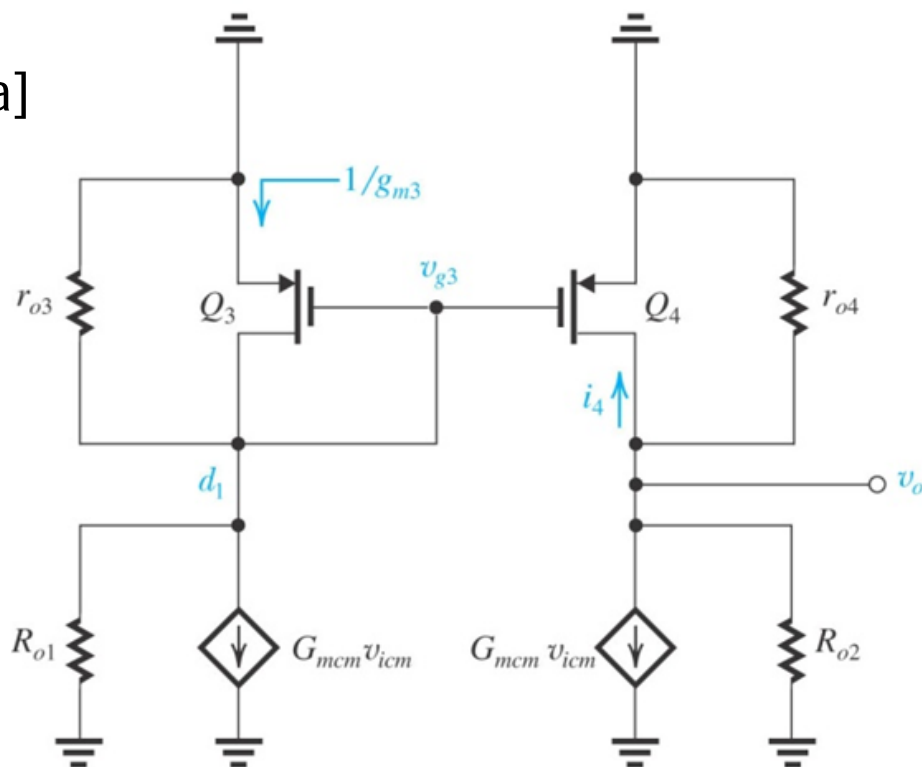

$$i_4 = -g_{m4} G_{mcm} v_{icm} \left( R_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}} \right)$$

KCL at  $v_o$

$$G_{mcm} v_{icm} + i_4 + \frac{v_o}{R_{o2}} + \frac{v_o}{r_{o2}} = 0$$


$$v_o = -v_{icm} \frac{r_{o4} \parallel R_{o2}}{2R_{SS}} \left[ 1 - g_{m4} \left( R_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}} \right) \right]$$

Since  $R_{o2} \gg r_{o4}$  and  $R_{o1} \gg r_{o3}$  and  $g_{m3} = g_{m4}$

$$A_{CM} = \frac{v_o}{v_{icm}} \approx -\frac{r_{o4}}{2R_{SS}} \frac{1}{1 + g_{m3} r_{o3}}$$

$$A_{CM} \approx -\frac{1}{2g_{m3} R_{SS}}$$
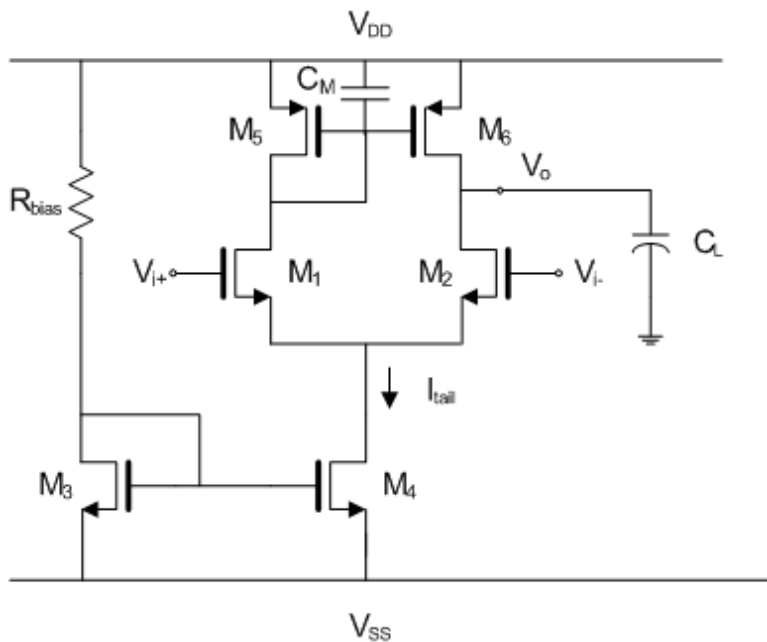
# OTA Common-Mode Gain & Rejection Ratio (CMRR)



$$A_{cm} = \frac{v_o}{v_{CM}} \approx -\frac{1}{2g_{m6}r_{o4}}$$

- To improve (lower) common-mode gain, we need a high tail current impedance

- An amplifier figure-of-merit is the common-mode rejection ratio (CMRR)


$$CMRR = 20\log_{10} \left| \frac{A_{dm}}{A_{cm}} \right|$$

$$CMRR = 20\log_{10} \left| \frac{A_{dm}}{A_{cm}} \right| = 20\log_{10} \left| \left( \frac{g_{m1}}{g_{o6} + g_{o2}} \right) (-2g_{m6}r_{o4}) \right|$$



# OTA Power-Supply Rejection Ratio (PSRR)

[Razavi]

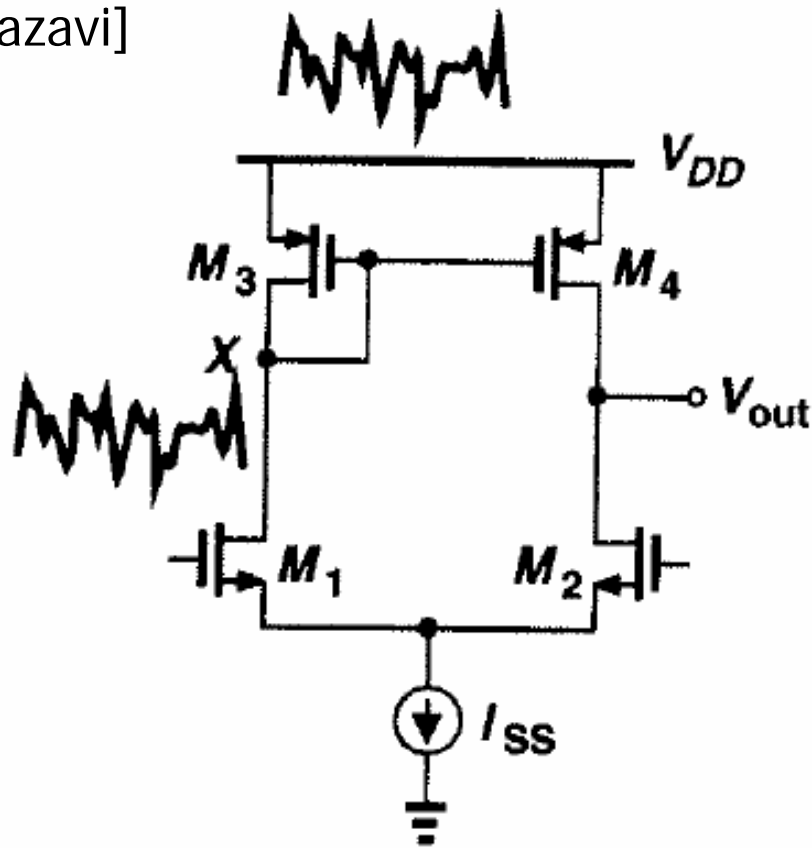

$$PSRR^+ = 20 \cdot \log_{10} \left( \left| \frac{A_{dm}}{v_o / v_{DD}} \right| \right)$$
$$PSRR^- = 20 \cdot \log_{10} \left( \left| \frac{A_{dm}}{v_o / v_{SS}} \right| \right)$$



$$A_{dm} = \frac{g_{m1}}{g_{o2} + g_{o4}}$$

$$A_{vdd} \approx 1$$

$$PSRR^+ \approx \frac{g_{m1}}{g_{o2} + g_{o4}}$$


# OTA Slew Rate

[Razavi]

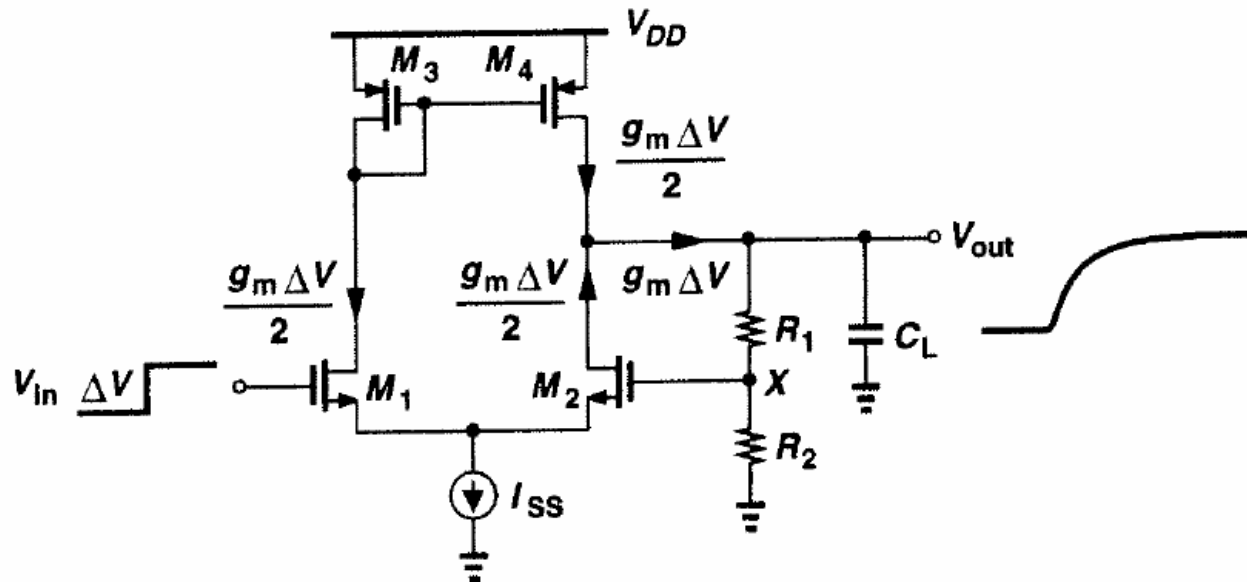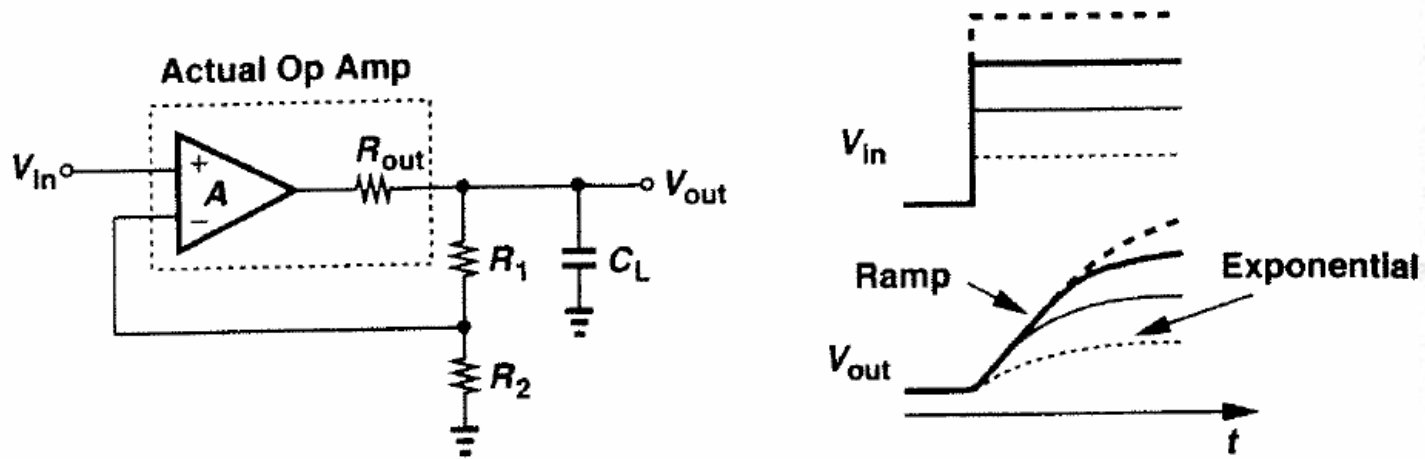


# OTA Slew Rate


[Razavi]

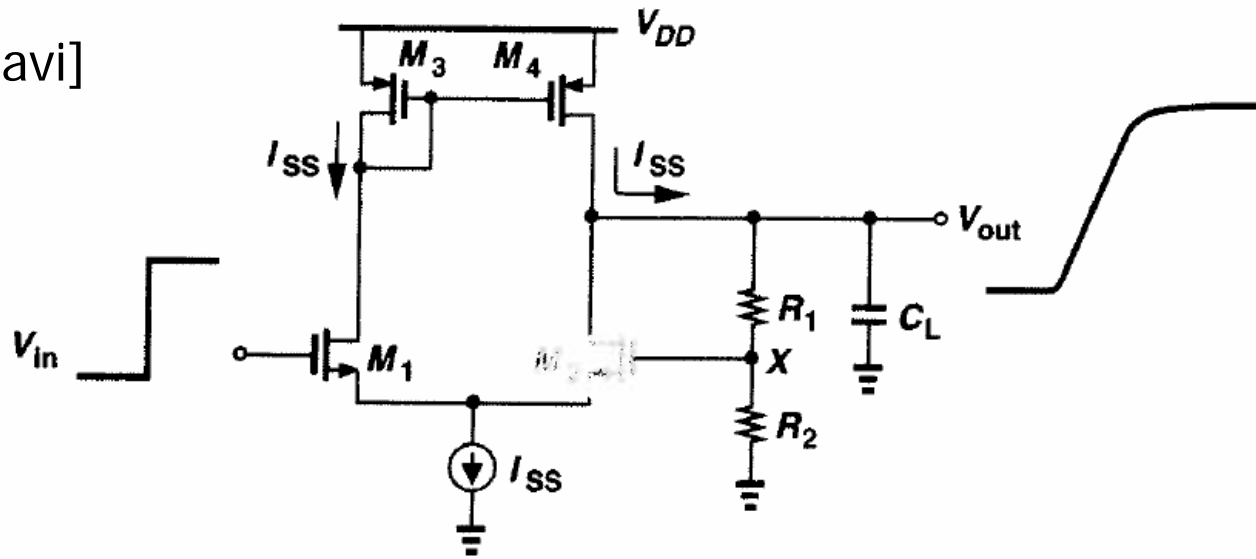
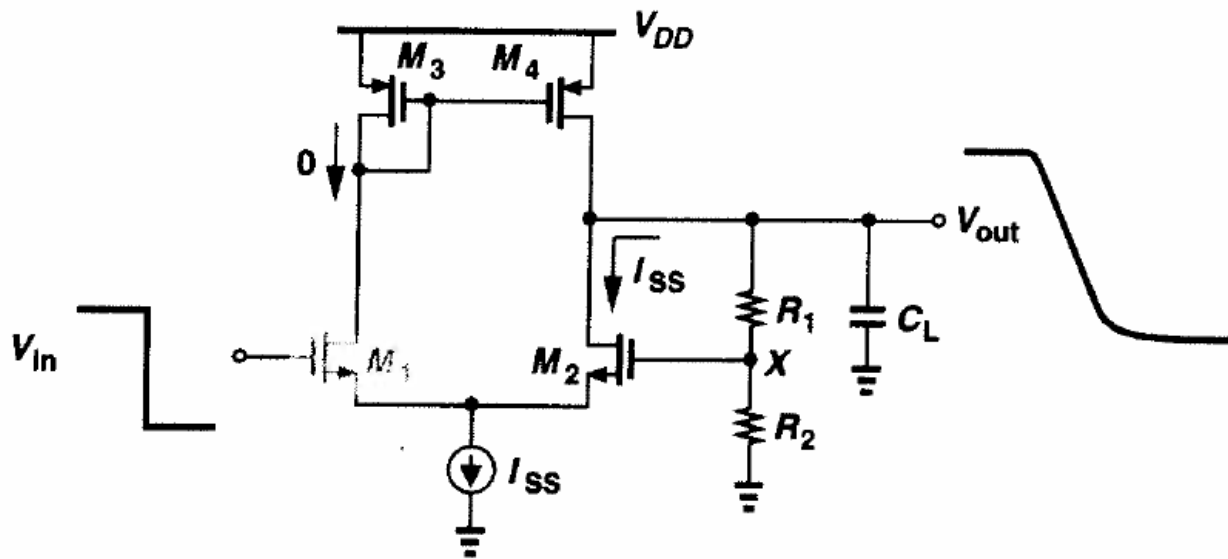
$$\text{Slew Rate} = \frac{I_{SS}}{C_L}$$



# Simple OTA Summary

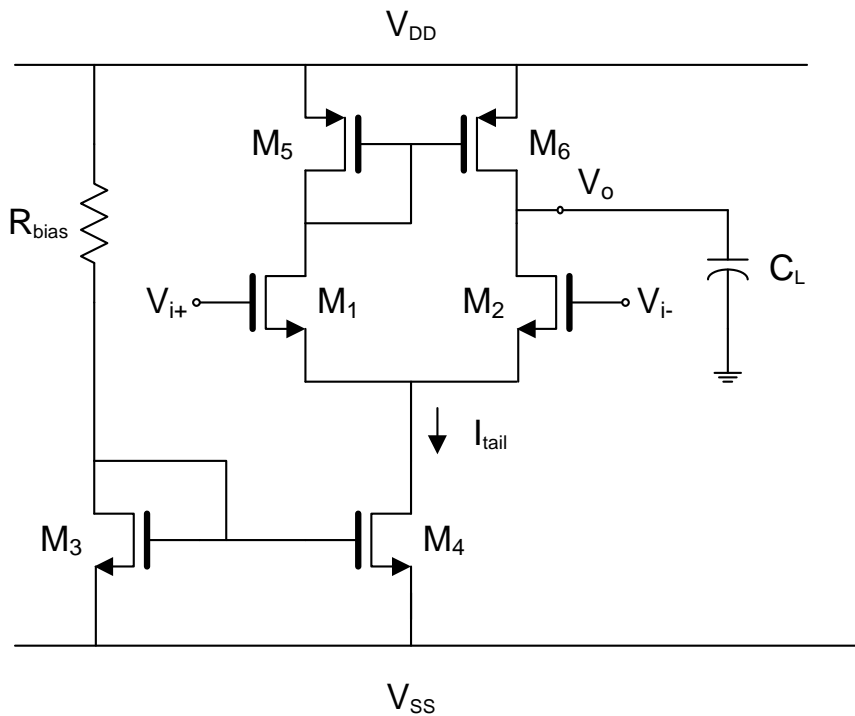

$$\text{Transconductance } G_m = g_{m1} = \sqrt{KP_n \frac{W}{L_1} I_{TAIL}}$$

$$\text{Output Conductance } g_{out} = g_{o2} + g_{o6} = \frac{I_{TAIL}}{2} (\lambda_n + \lambda_p)$$

$$\text{DC Gain } A_v = G_m R_{out} = \frac{g_{m1}}{g_{o2} + g_{o6}} = \frac{2 \sqrt{KP_n \frac{W}{L_1} I_{TAIL}}}{\lambda_n + \lambda_p}$$

$$\text{Dominant Pole } \omega_{p1} = \frac{g_{o2} + g_{o6}}{C_L}$$

$$\text{Non-Dominant Pole } \omega_{p2} = \frac{g_{m6}}{C_M} \approx \frac{g_{mg}}{2C_{gs6}}$$


$$\text{Output Noise Current } i_{on}^2 = 2 \left( \frac{8}{3} kT \right) (g_{m1} + g_{m6})$$

$$\text{Input Noise Voltage } v_{in}^2 = 2 \left( \frac{8}{3} kT \right) \left( \frac{1}{g_{m1}} \right) \left( 1 + \frac{g_{m6}}{g_{m1}} \right)$$

$$GBW = \frac{G_m}{C_L} = \frac{\sqrt{KP_n \frac{W}{L_1} I_{TAIL}}}{C_L}$$

$$\text{Slew Rate } SR = \frac{I_{tail}}{C_L}$$
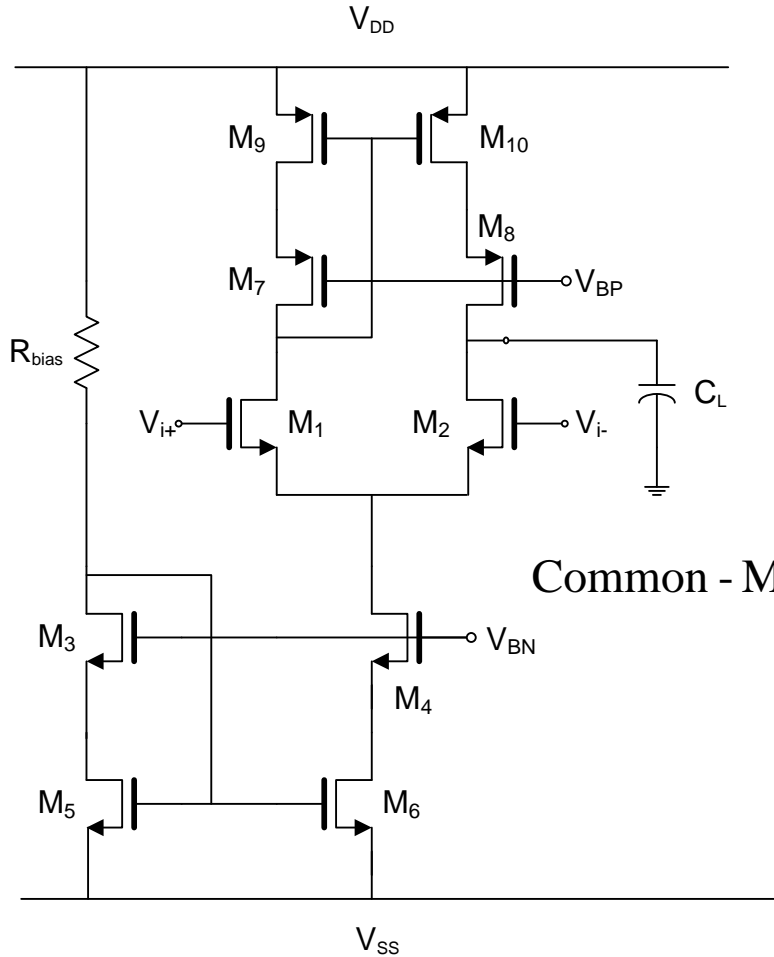
# OTA w/ Cascode Load and Tail Current Source



$$\text{DC Gain } A_{DM} = g_{m1} (r_{o2} \parallel (r_{o8} + r_{o10} + g_{m8} r_{o10} r_{o8})) \approx g_{m1} r_{o2}$$

$$\text{Dominant Pole } \omega_{p1} = \frac{1}{(r_{o2} \parallel (r_{o8} + r_{o10} + g_{m8} r_{o10} r_{o8})) C_L} \approx \frac{1}{r_{o2} C_L}$$

$$GBW = \frac{g_{m1} r_{o2}}{r_{o2} C_L} = \frac{g_{m1}}{C_L}$$

$$\text{Slew Rate } SR = \frac{I_{tail}}{C_L}$$

$$\text{Common - Mode Gain } A_{CM} \approx -\frac{1}{2g_{m9} R_{SS}} \quad \text{where } R_{SS} = r_{o4} + r_{o6} + g_{m4} r_{o6} r_{o4}$$

$$A_{CM} \approx -\frac{1}{2g_{m9} g_{m4} r_{o6} r_{o4}}$$

$$CMRR = -2g_{m1} r_{o2} g_{m9} g_{m4} r_{o6} r_{o4}$$

Input Common - Mode Range

$$V_{SS} + \sqrt{\frac{2I_{tail}}{\mu_n C_{ox} \frac{W}{L_6}}} + \sqrt{\frac{2I_{tail}}{\mu_n C_{ox} \frac{W}{L_4}}} + \sqrt{\frac{I_{tail}}{\mu_n C_{ox} \frac{W}{L_1}}} + V_{Tn1} \leq V_{icm} \leq V_{DD} - \left( \sqrt{\frac{I_{tail}}{\mu_p C_{ox} \frac{W}{L_9}}} + |V_{Tp9}| \right) + V_{Tn1}$$

# Next Time

---

- Noise