

# ECEN474: (Analog) VLSI Circuit Design

## Fall 2012

---

### Lecture 17: Fully Differential Amplifiers & CMFB



Sam Palermo

Analog & Mixed-Signal Center


Texas A&M University

# Announcements & Agenda


---

- Preliminary report due 11/19
- Fully differential circuits
- Common-mode feedback circuits
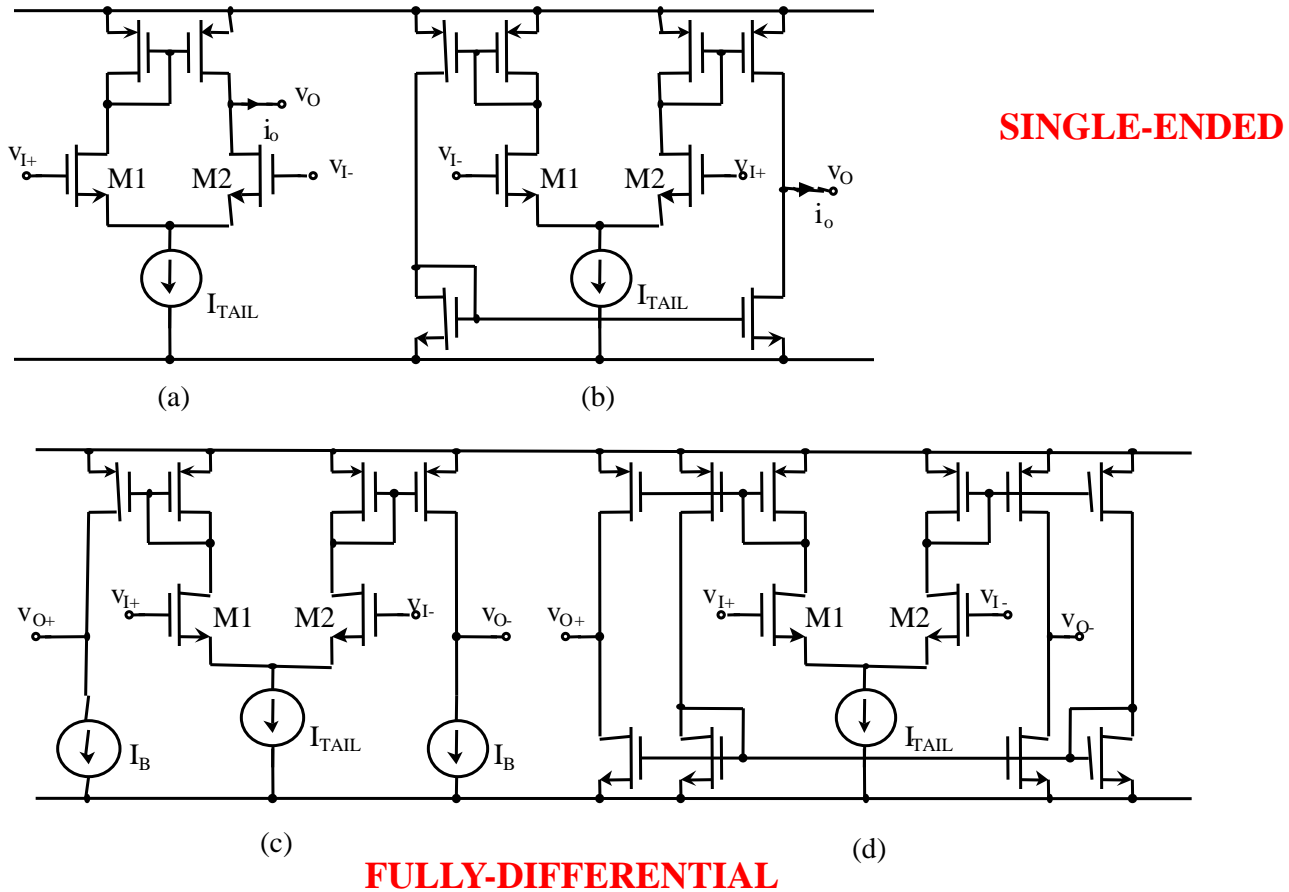
## Basic Operational Transconductance Amplifier Topologies



# Fully-Differential Circuits

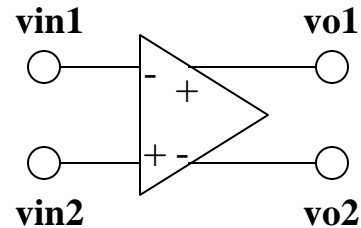

In general:

$$v_{o1} = \frac{v_{o1} - v_{o2}}{2} + \frac{v_{o1} + v_{o2}}{2} = \frac{v_{od}}{2} + v_{oc}$$

$$v_{o2} = \frac{v_{o2} - v_{o1}}{2} + \frac{v_{o1} + v_{o2}}{2} = -\frac{v_{od}}{2} + v_{oc}$$

➤ Hence

$$\begin{bmatrix} v_{od} \\ v_{oc} \end{bmatrix} = \begin{bmatrix} A_{dd} & A_{dc} \\ A_{cd} & A_{cc} \end{bmatrix} \begin{bmatrix} v_{id} \\ v_{ic} \end{bmatrix}$$


**Differential-mode output**

$$A_{dd} = \left. \frac{v_{od}}{v_{id}} \right|_{v_{ic}=0} \quad A_{dc} = \left. \frac{v_{od}}{v_{ic}} \right|_{v_{id}=0}$$

**Common-mode output**

$$A_{cd} = \left. \frac{v_{oc}}{v_{id}} \right|_{v_{ic}=0} \quad A_{cc} = \left. \frac{v_{oc}}{v_{ic}} \right|_{v_{id}=0}$$
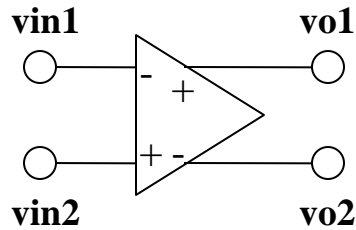
# Fully-Differential Filters: Effects of current source impedance and mismatches




A very important parameter:

$$CMRR = \frac{A_{dd}}{A_{dc}}$$

w/  $v_{id} = v_{i2} - v_{i1}$  and  $v_{ic} = \frac{v_{i2} + v_{i1}}{2}$

Solving the circuit:

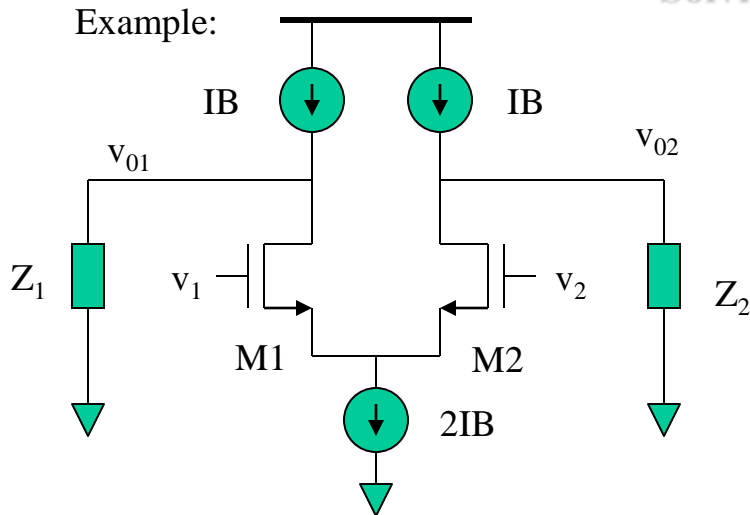


$$v_{01} = \frac{g_{m1}g_{m2}Z_1}{g_{m1} + g_{m2} + Y_s} \left[ \left( 1 + \frac{Y_s}{2g_{m2}} \right) v_{id} - \left( \frac{Y_s}{g_{m2}} \right) v_{ic} \right]$$

$$v_{02} = \frac{g_{m1}g_{m2}Z_2}{g_{m1} + g_{m2} + Y_s} \left[ - \left( 1 + \frac{Y_s}{2g_{m1}} \right) v_{id} - \left( \frac{Y_s}{g_{m1}} \right) v_{ic} \right]$$

$Y_s$  is the admittance associated with the current source  $2IB$

# Fully-Differential Filters: Non-idealities

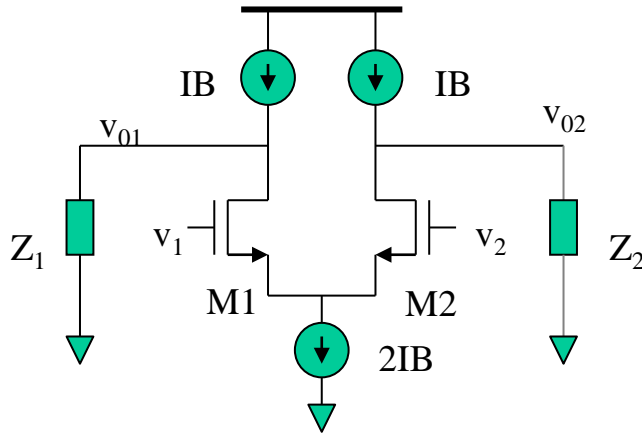**Voltage gain: Note the effects of the mismatches, especially in  $A_{dc}$  and  $A_{cd}$**



$$CMRR = \frac{A_{dd}}{A_{dc}} \cong \frac{g_{m1} \left( 1 + \frac{Z_1}{Z_2} \right)}{Y_s \left( 1 - \frac{g_{m1} Z_1}{g_{m2} Z_2} \right)}$$


$$A_{dd} = \left. \frac{v_{o1} - v_{o2}}{v_{i2} - v_{i1}} \right|_{v_{ic}=0} = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2} + Y_s} \left[ Z_1 + Z_2 + \frac{Y_s}{2} \left( \frac{Z_1}{g_{m2}} + \frac{Z_2}{g_{m1}} \right) \right]$$

$$A_{dc} = \left. \frac{v_{o1} - v_{o2}}{(v_{i2} + v_{i1})/2} \right|_{v_{id}=0} = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2} + Y_s} \left[ Y_s \left( \frac{Z_2}{g_{m1}} - \frac{Z_1}{g_{m2}} \right) \right]$$

$$A_{cd} = \left. \frac{(v_{o2} + v_{o1})/2}{v_{i2} - v_{i1}} \right|_{v_{ic}=0} = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2} + Y_s} \left( \frac{1}{2} \right) \left[ Z_1 - Z_2 + \frac{Y_s}{2} \left( \frac{Z_1}{g_{m2}} - \frac{Z_2}{g_{m1}} \right) \right]$$

$$A_{cc} = \left. \frac{(v_{o2} + v_{o1})/2}{(v_{i2} + v_{i1})/2} \right|_{v_{id}=0} = - \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2} + Y_s} \left( \frac{1}{2} \right) \left[ Y_s \left( \frac{Z_2}{g_{m1}} + \frac{Z_1}{g_{m2}} \right) \right]$$

# Fully-Differential Circuits

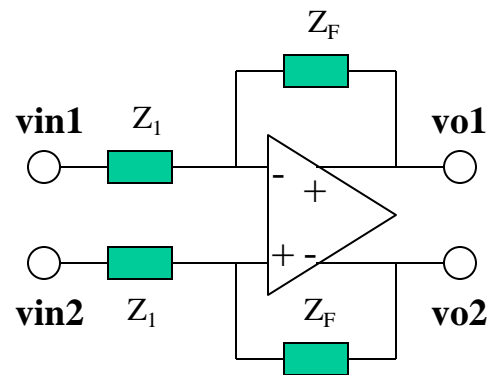

➤ **Ideal voltage gain**


$$A_{dd} = \frac{v_{o1} - v_{o2}}{v_{in2} - v_{in1}} = \frac{Z_f}{Z_1}$$

➤ **Ideally even-order distortions are cancelled**

➤ **Ideally common-mode signals are rejected**

➤ **What sets the output common-mode of these circuits?**

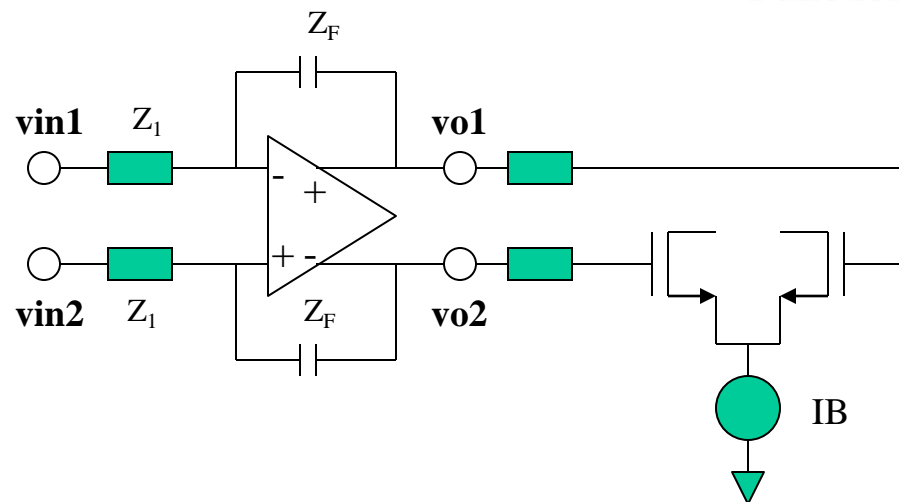
➤ **Function of the amplifier output resistance**



**Common-mode offsets can impact the performance of the following stages**

- **Can exceed the common-mode input range of preceding stages**
- **With finite  $A_{cc}$  can accumulate in a multi-stage amplifier circuit**
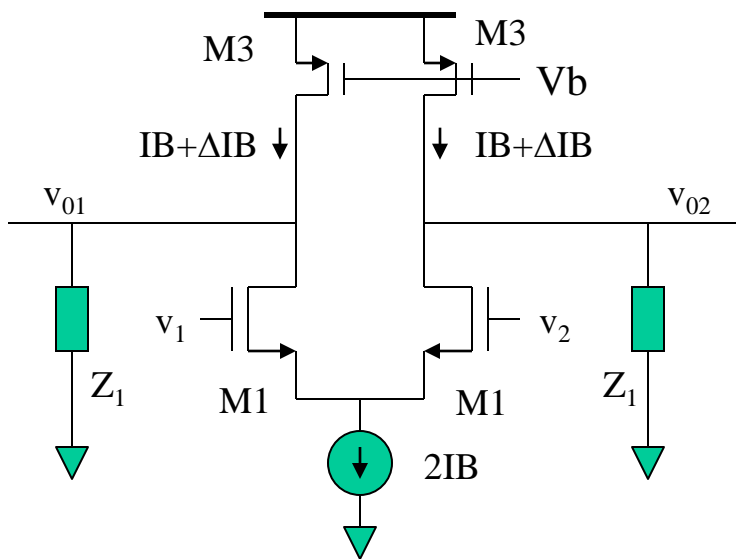
## Fully-Differential Amplifiers: COMMON-MODE DC offset



✓ If  $\Delta I_B$  is positive transistors M3 eventually will be biased in triode region (small resistance)

✓ dc gain reduces drastically

✓ Linear range is further minimized

✓ THD increases

✓ The common-mode output impedance is the parallel of the equivalent output resistance (M1 and M3) and the parasitic capacitors.


✓ For large dc gain, the output impedance at nodes  $v_{01}$  and  $v_{02}$  are further increased and  $\Delta I_B$  produces a dc offset =  $R_{out}\Delta I_B$ .

**Large common-mode offsets!**

✓ How can this issue be fixed?


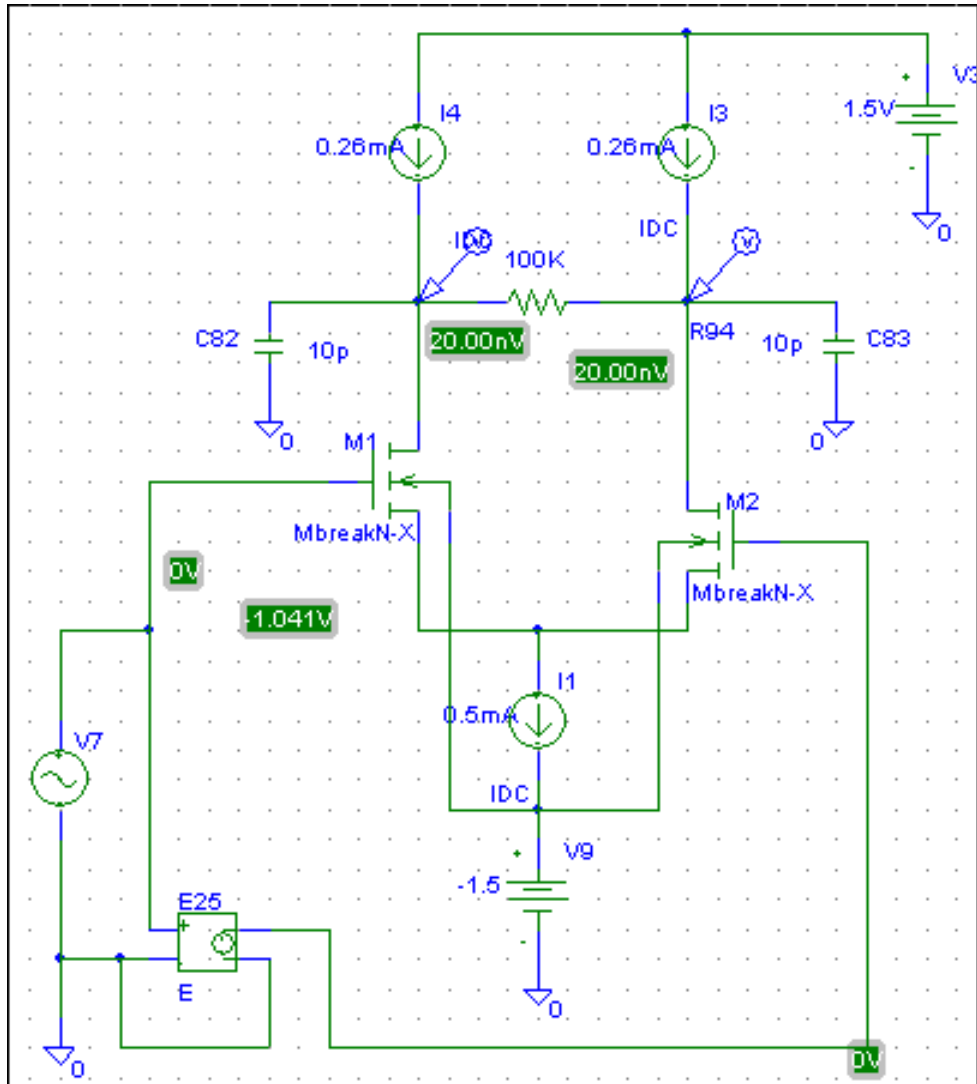
# Fully-Differential Amplifiers: Characterization





✓ Common-mode current offset of 0.01 mA per side is added on purpose

Tail current is 0.5 mA while the current sources on top are 0.26 mA!

✓ Differential input voltage is set at 0

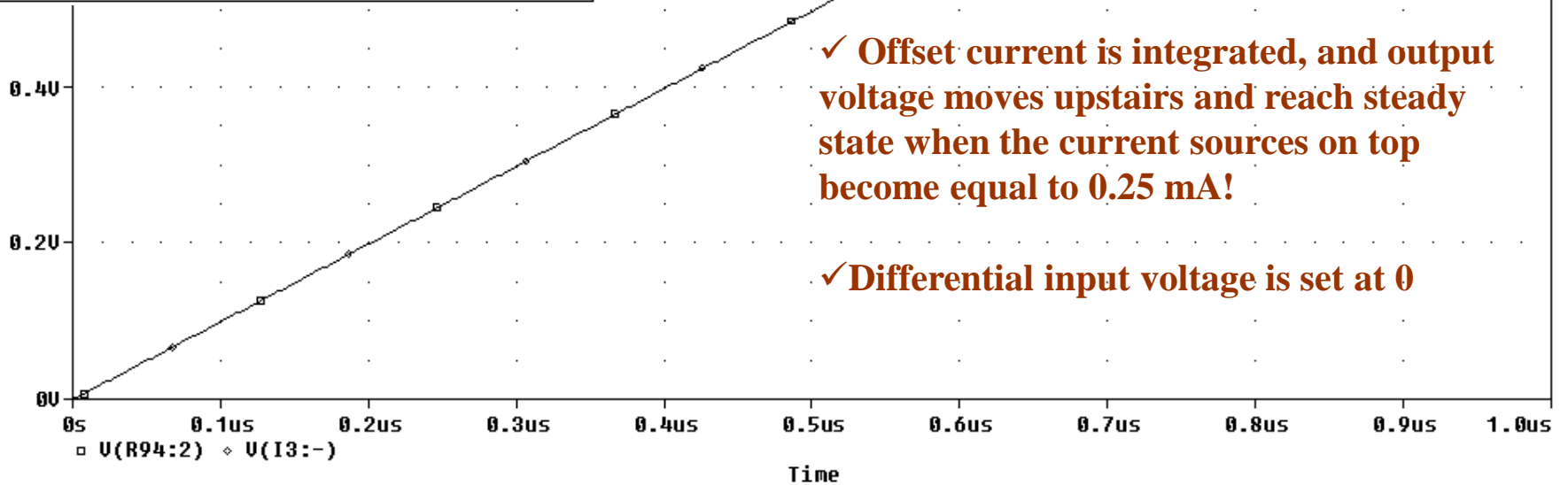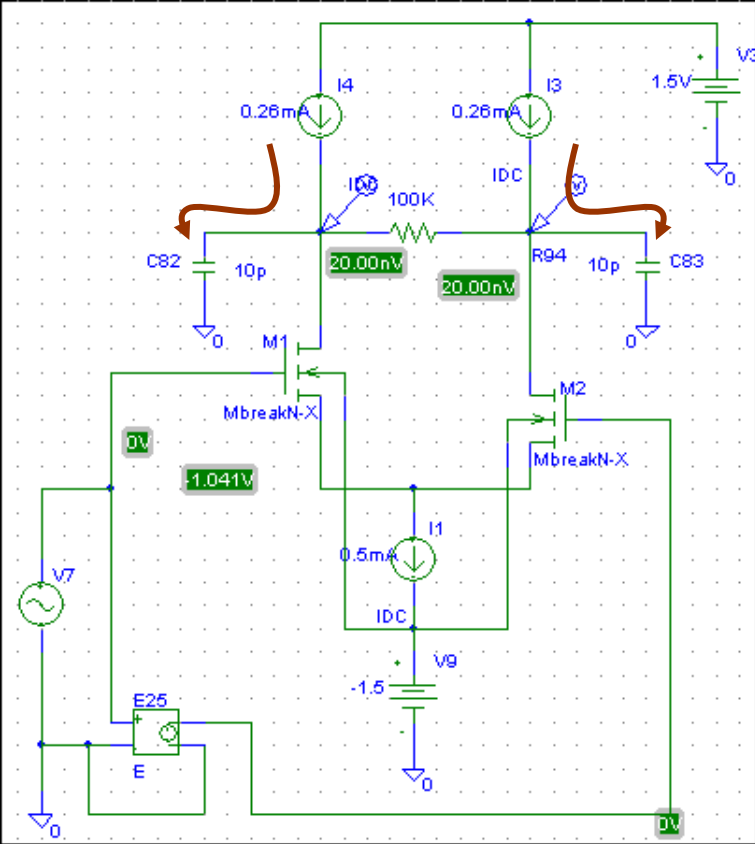
# Differential Amplifiers: Characterization



✓ Offset current is integrated, and output voltage moves upstairs and reach steady state when the current sources on top become equal to 0.25 mA!

✓ Differential input voltage is set at 0
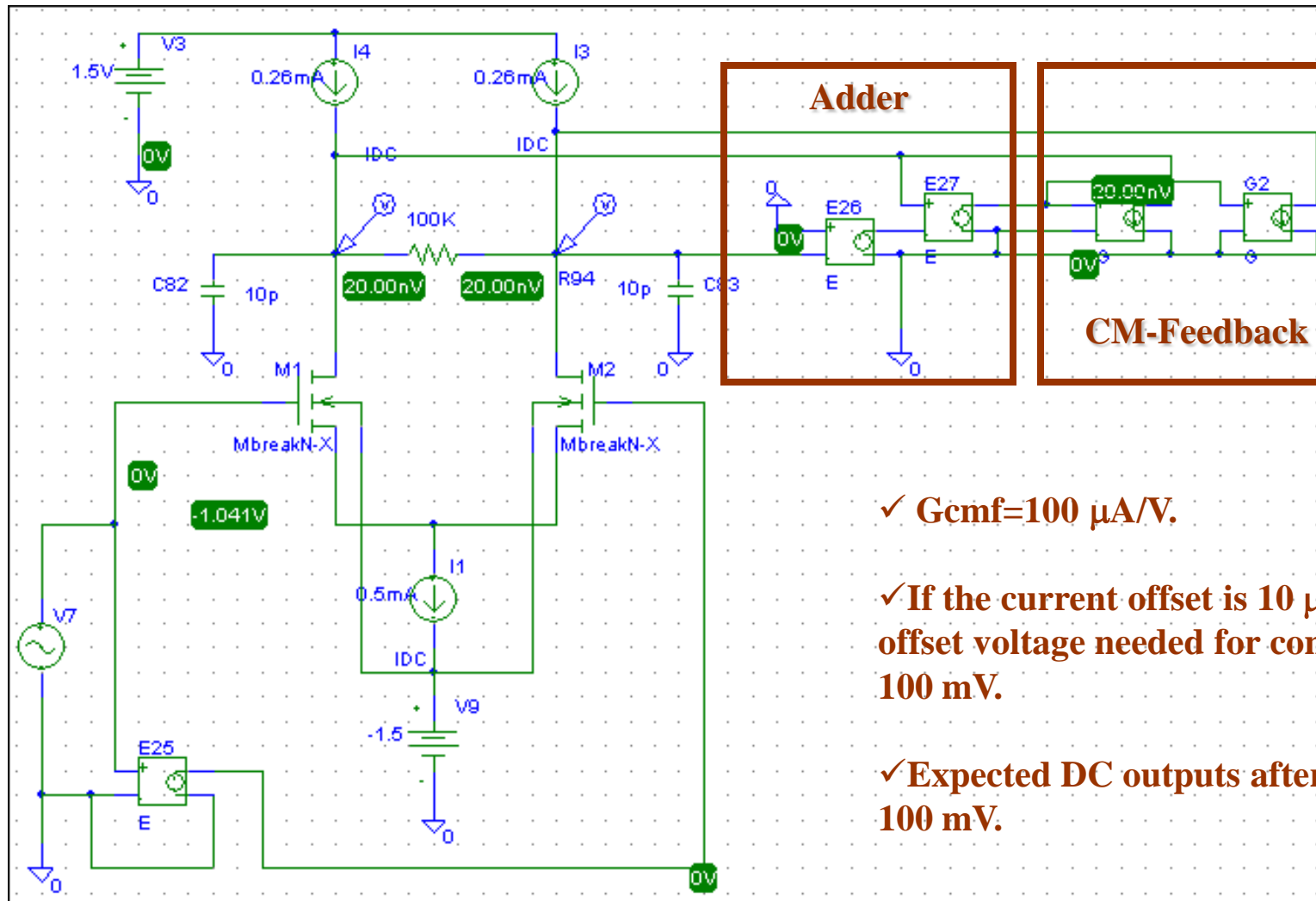
# Fully-Differential Amplifiers: Common-mode Feedback




✓  $G_{cmf} = 100 \mu\text{A/V}$ .

✓ If the current offset is  $10 \mu\text{A}$ , then the offset voltage needed for compensation is 100 mV.

✓ Expected DC outputs after settling are 100 mV.

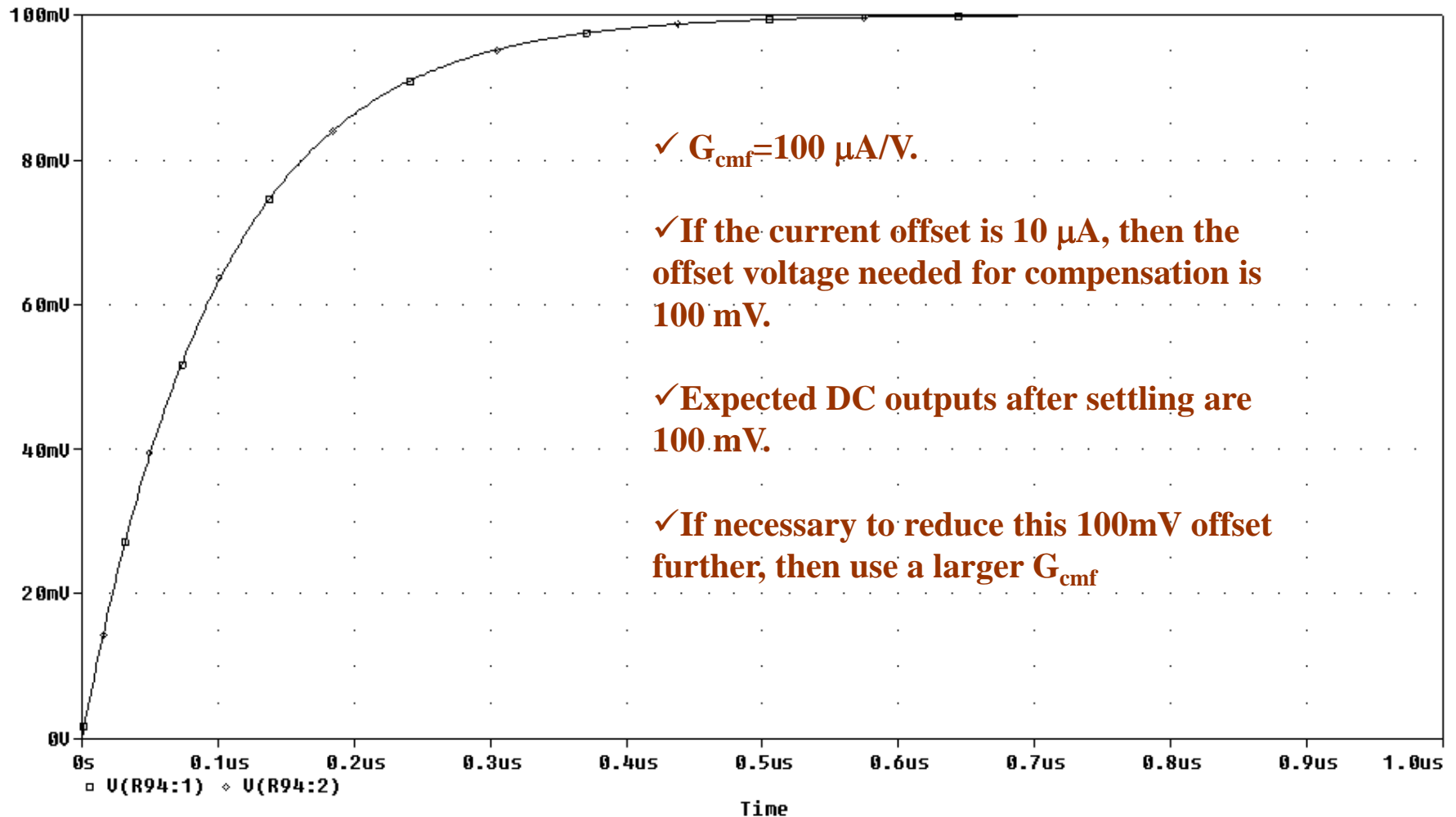
## Fully-Differential Amplifiers: Common-mode Feedback




## What is a common-mode feed-back correction circuit ?

A common mode **feed-back** circuit is a circuit sensing the common-mode voltage, comparing it with a proper reference, and feeding back the correcting common-mode signal (both nodes of the fully-differential circuit) with the purpose to cancel the output common-mode current component, and to fix the dc outputs to the desired level.
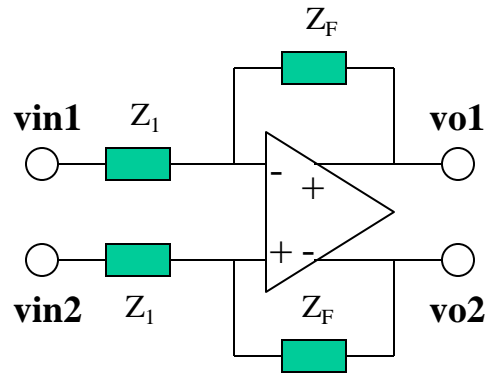
## Fully-Differential Filters: CMFB Principle




### Simplest common-mode detector

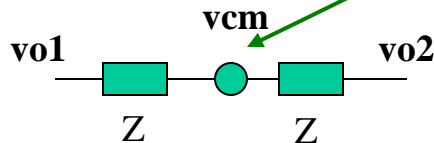

$$v_{cm} = \frac{v_{o1} + v_{o2}}{2}$$

- A common-mode feedback loop must be used: Circuit must operate on the common-mode signals only!
- BASIC IDEA: CMFB is a circuit with very small impedance for the common-mode signals but transparent for the differential signals.
- Use a common-mode detector (eliminates the effect of differential signals and detect common-mode signals)
- Analyze the common-mode feedback loop: Large transconductance gain and enough phase margin
- Minimum power consumption
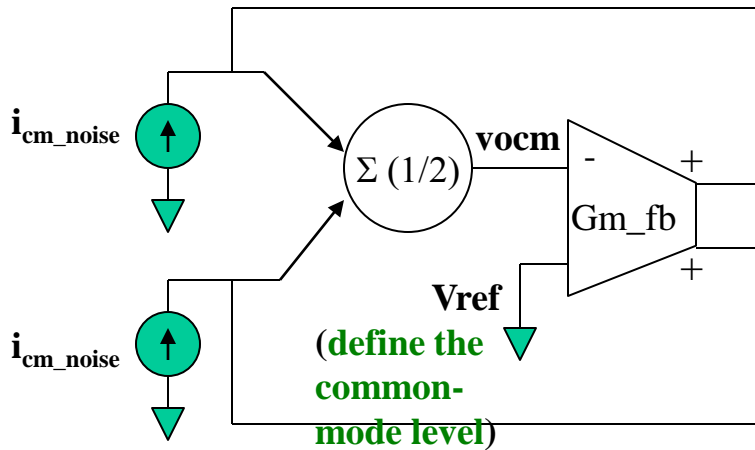
# CMFB Principles: Analysis of the loop for common-mode signals only



- Analysis for common-mode noise; for instance noise due to power supplies:
- $i_{o1} = i_{o2} = i_{cm\_noise}$

➤ **The two outputs can be connected together for the analysis of the CMFB loop!**

### ➤ BASIC CONCEPTS:


- The common-mode input noise is converted into a common-mode voltage (common-mode voltage noise) by the common-mode transconductance of the CMFB  $= 1/G_{m\_fb}$ .

### ➤ common-mode voltage variations


$$v_{cm\_noise} = i_{cm\_noise} / G_{m\_fb} !!$$

- **The larger  $G_{m\_fb}$  the smaller the effects of the common-mode noise!**

## ↓ Effect of common-mode noise:

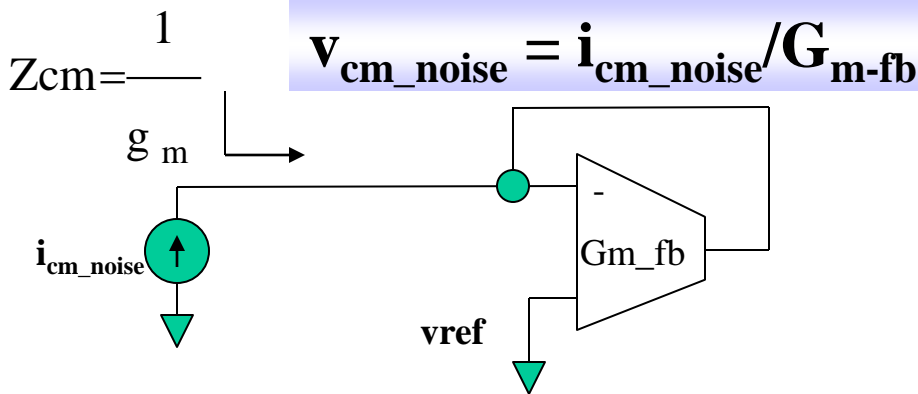

## Fully-Differential Filters: CMFB

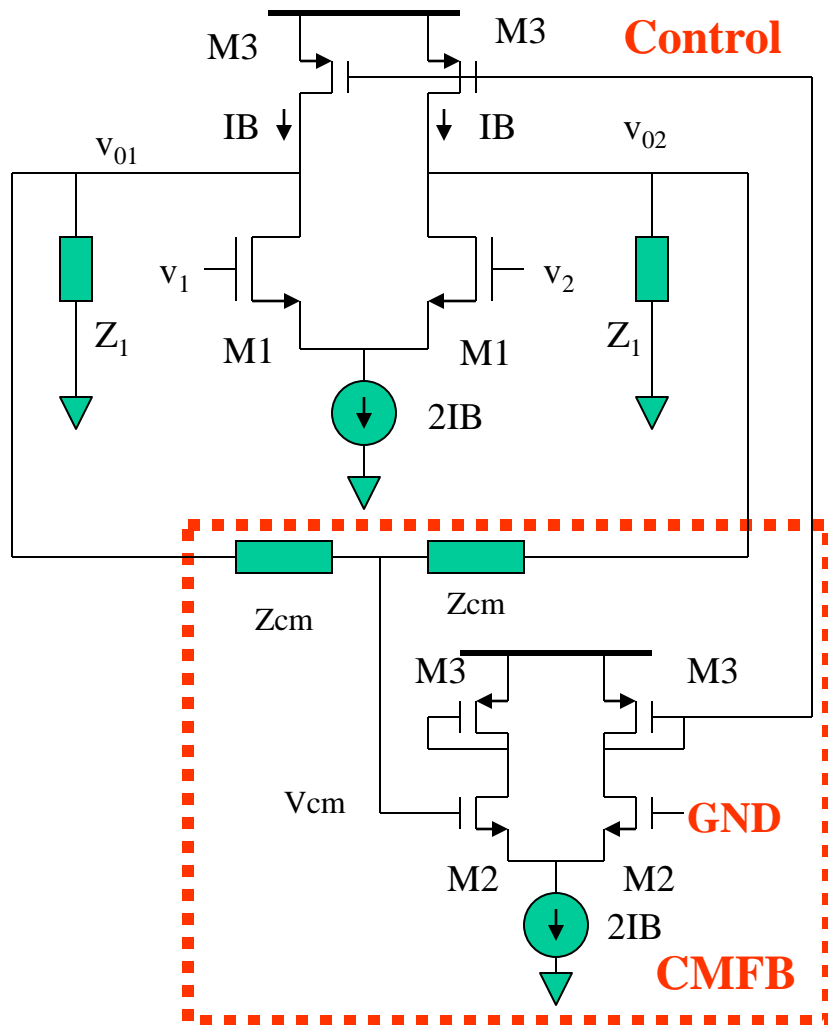

### ➤ CMFB Characteristics:

➤ Transconductance gain =  $g_{m2}/2$  (no PMOS mirror in CMFB OTA)

➤ dominant pole at the output

➤ At least 2 additional poles in the loop


➤  $Z_{cm}$  reduces the OTA dc gain, affecting the differential gain

➤ NOTE THAT  $V_{cm}$  IS FORCED TO BE AROUND THE GROUND LEVEL.

➤ DC OFFSET VOLTAGE IS AROUND  $2 \cdot I_{off}/g_{m2}$



# Fully-Differential Filters: CMFB

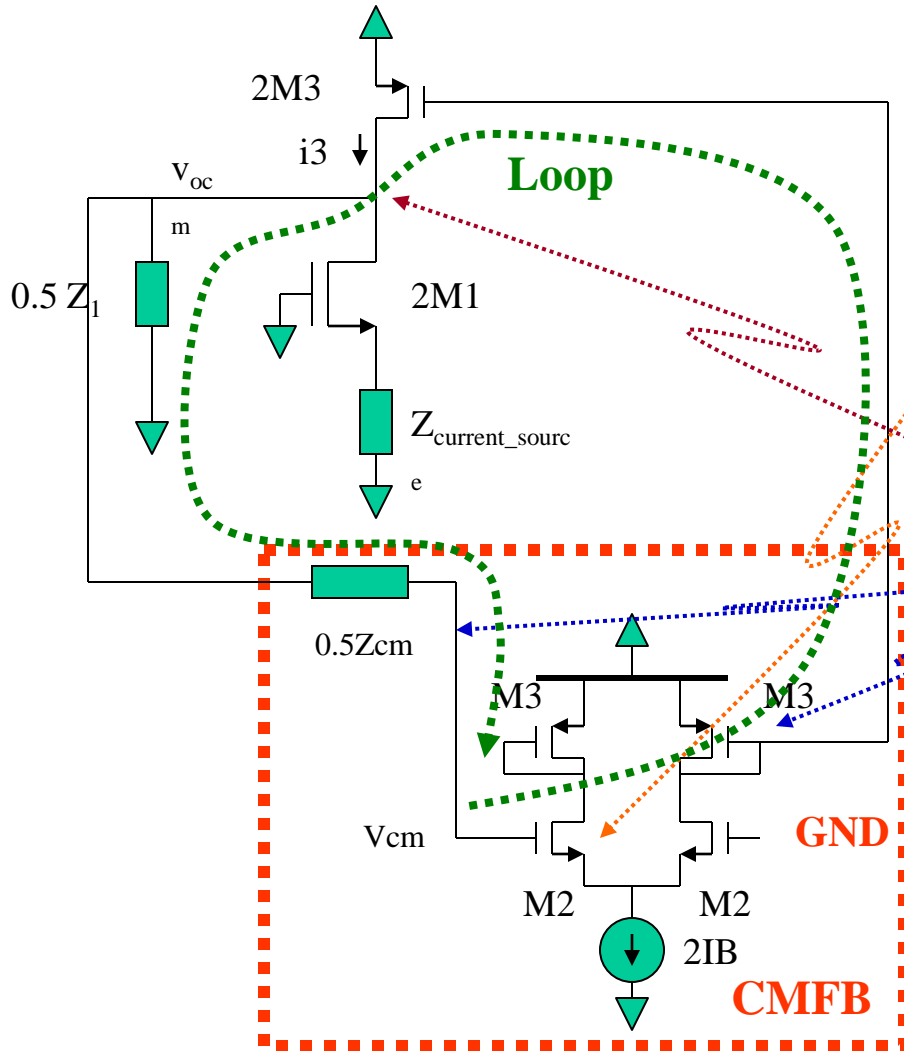

➤ **CMFB Characteristics:**

➤ DC Transconductance gain =  $g_{m2}/2$

➤ Loop gain (ignoring poles)

$$\approx \left( \frac{g_{m2}}{2} \right) \left( \frac{1}{g_{m3}} \right) (-2g_{m3}) \left( \frac{Z_1}{2} \right) = -\frac{g_{m2}Z_1}{2}$$


➤ dominant pole at the output

➤ At least 2 additional poles in the loop

➤ **DC OFFSET IS AROUND  $2I_{off}/g_{m2}$**

# Fully-Differential Filters: CMFB Principles


Can be removed  
for CMFB  
analysis

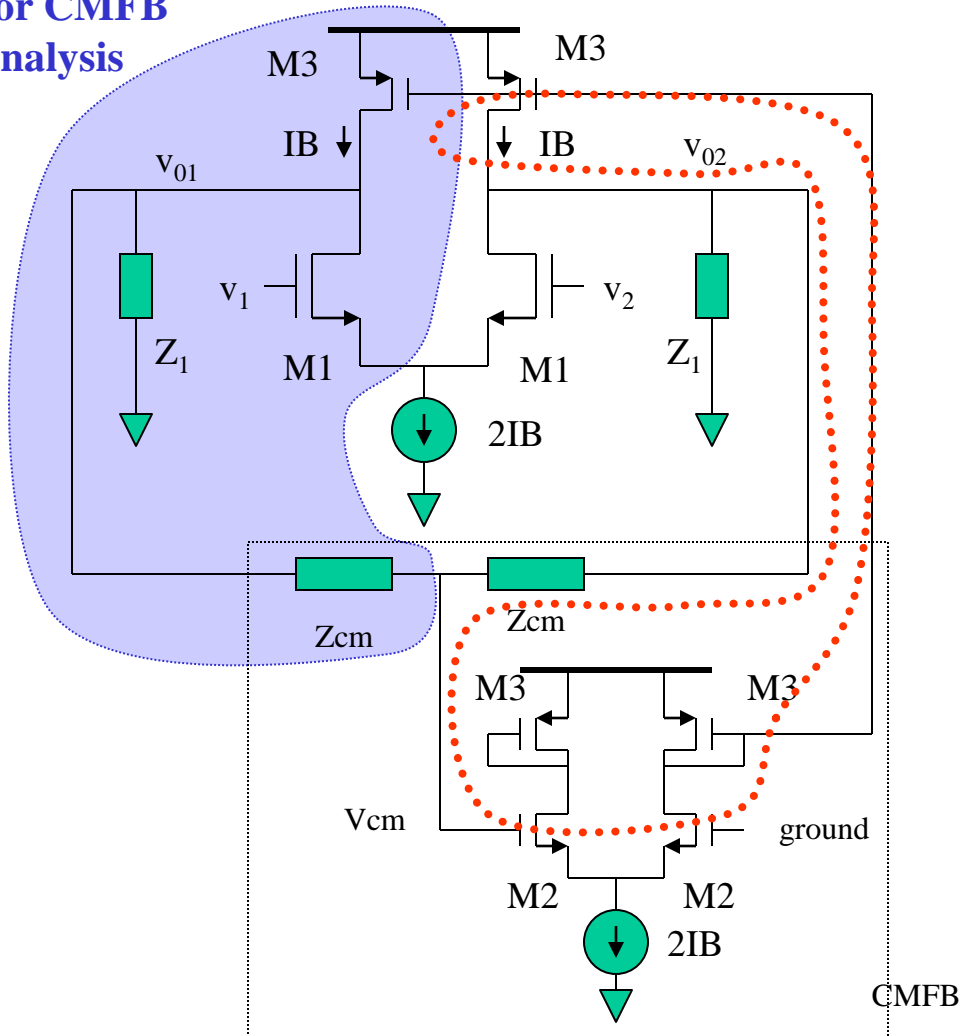


➤ Common-mode stability: DC gain and most relevant poles

- 1 pole at vcm ( $1/RC$ )
- 1 pole at gate of M3 ( $g_{m3}/C_{P3}$ )
- 1 pole at the output ( $g_{o1}/C_1$ )

➤ dc gain =  $0.5 g_{m2}R_{o1}$

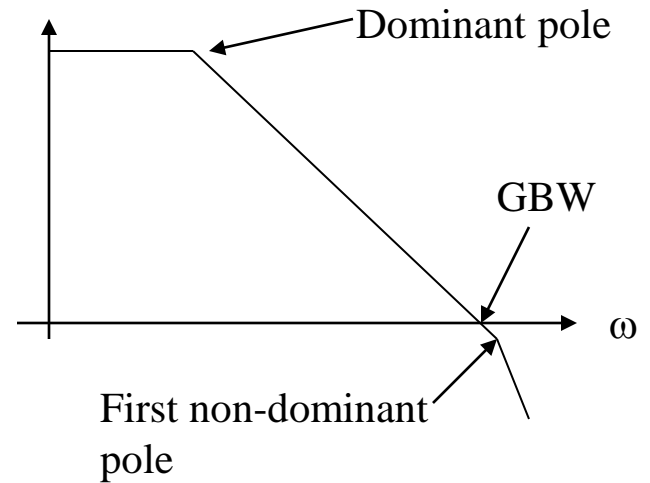


**Be sure phase margin > 45°**

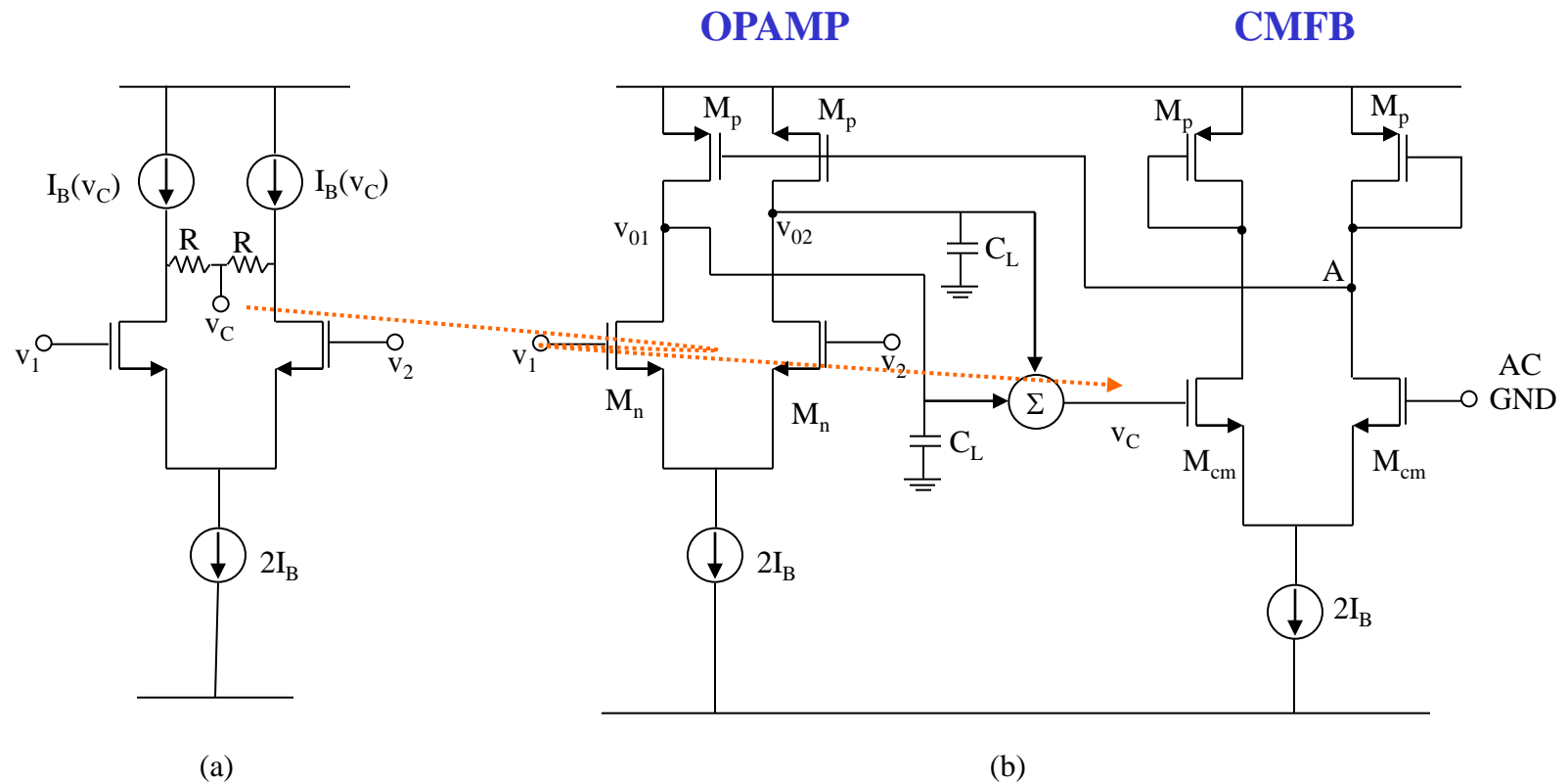

**Fig. 3 Common-mode feedback basic circuit concept. (a) Basic common-mode detector, (b) A CMOS CMFB Implementation.**

**Notice that the resistors  $R$  reduce the differential gain!**
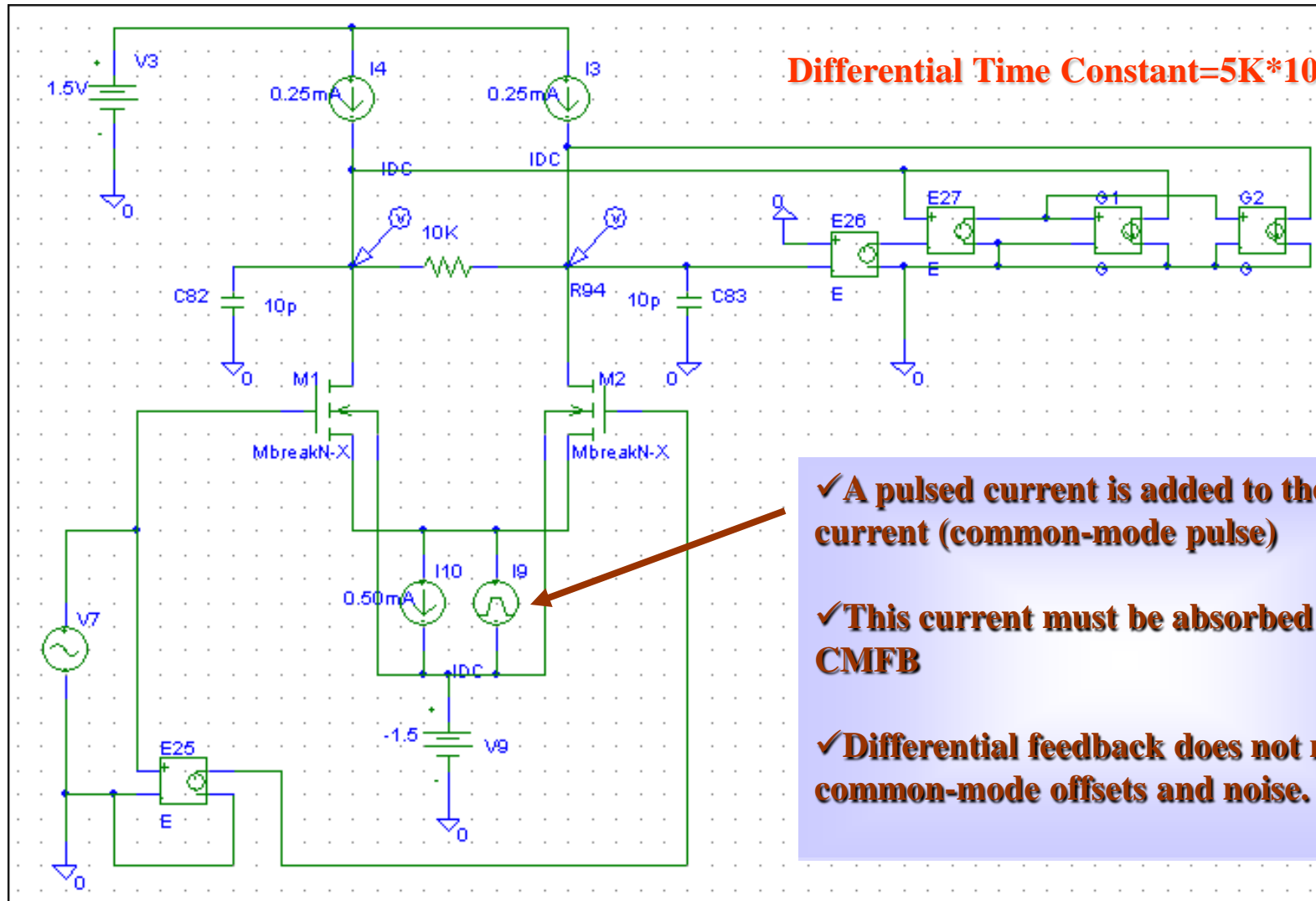
## Fully-Differential Amplifiers: Common-mode pulse



**Differential Time Constant =  $5K * 10P = 50nsecs$**


✓ **A pulsed current is added to the tail current (common-mode pulse)**

✓ **This current must be absorbed by the CMFB**

✓ **Differential feedback does not reduce common-mode offsets and noise.**

## Fully-Differential Amplifiers with CMFB


### Differential input signals only

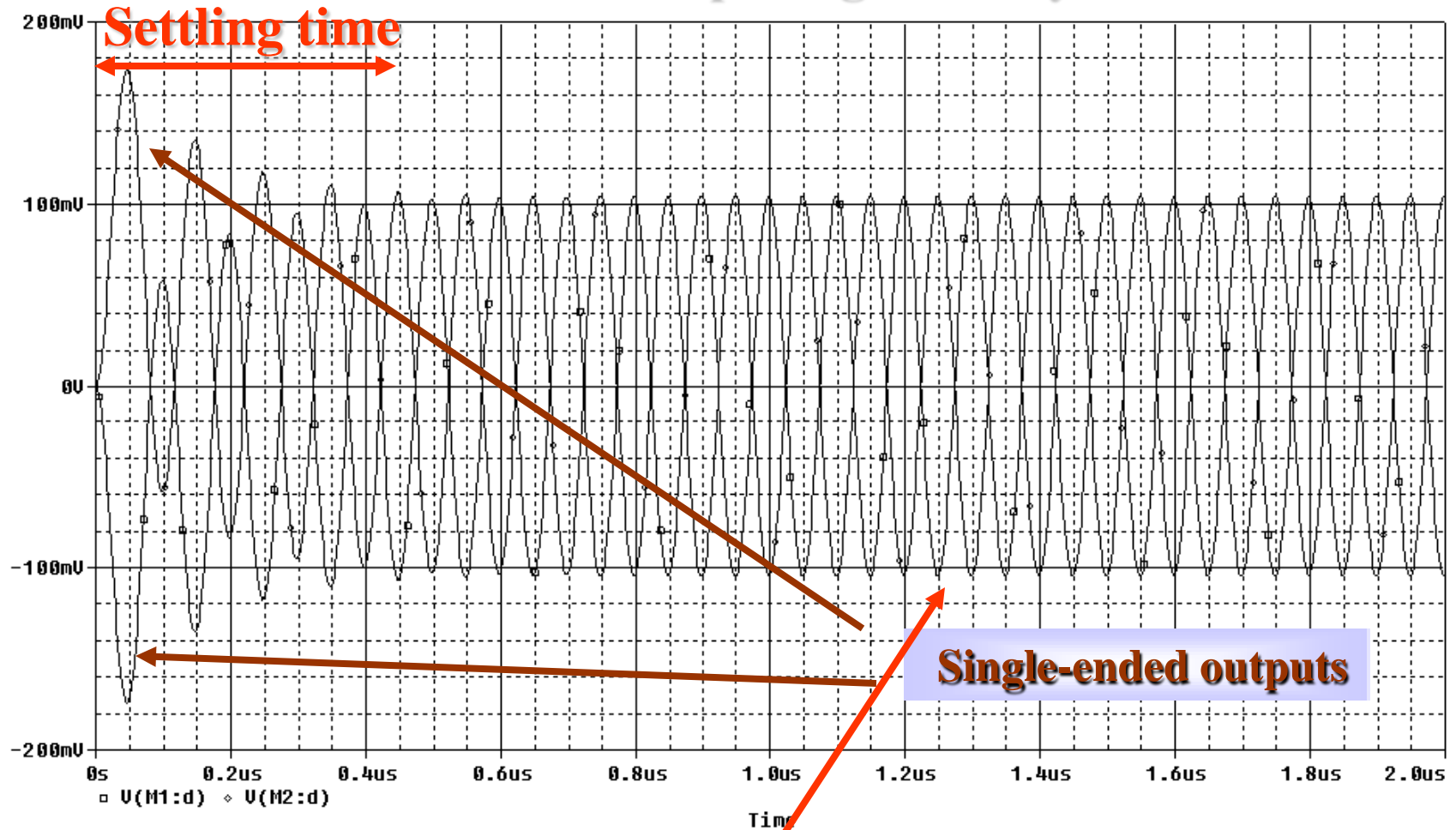

**Seems to be that the system is working fine, isn't it?**

# Fully-Differential Amplifiers with CMFB
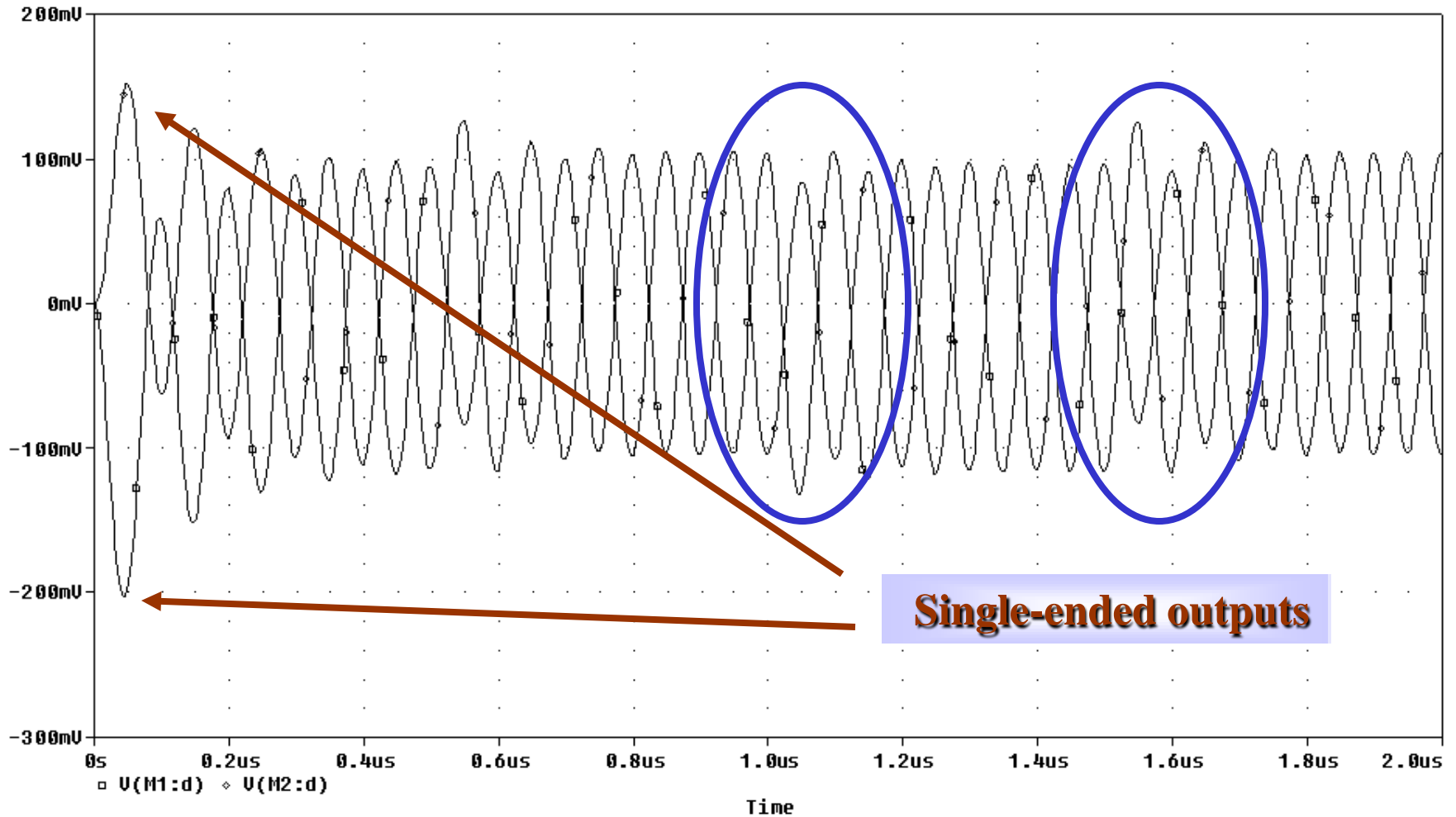
## Differential input signals + common-mode pulses




# Fully-Differential Amplifiers with CMFB


## Differential input signals + common-mode pulses
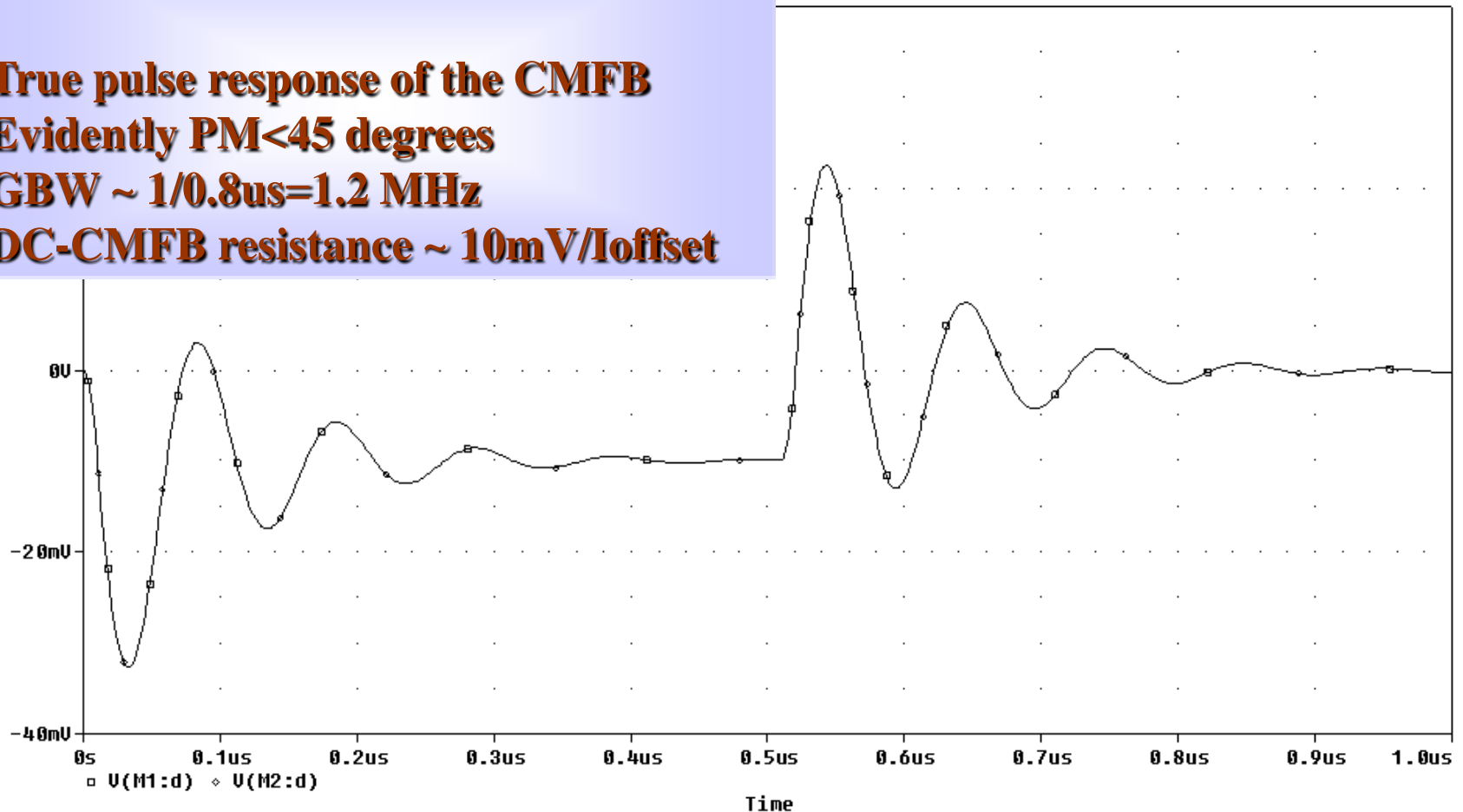
### Common-mode output

**True pulse response of the CMFB**  
**Evidently  $PM < 45$  degrees**  
 **$GBW \sim 1/0.8\mu s = 1.2$  MHz**  
**DC-CMFB resistance  $\sim 10$  mV/I<sub>offset</sub>**



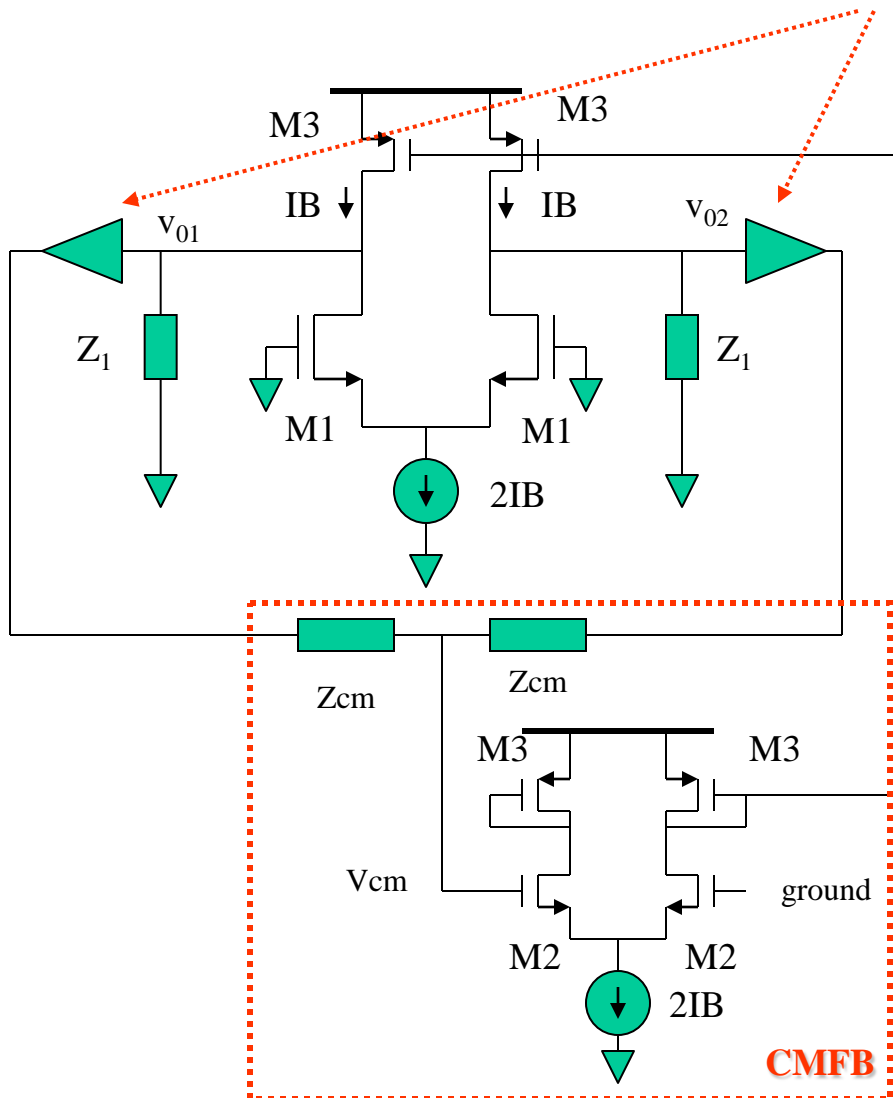
## Fully-Differential Filters: Adding buffers to handle the resistive CM-detector




➤ The stability conditions are exactly the same for OTA's and OPAMP's:

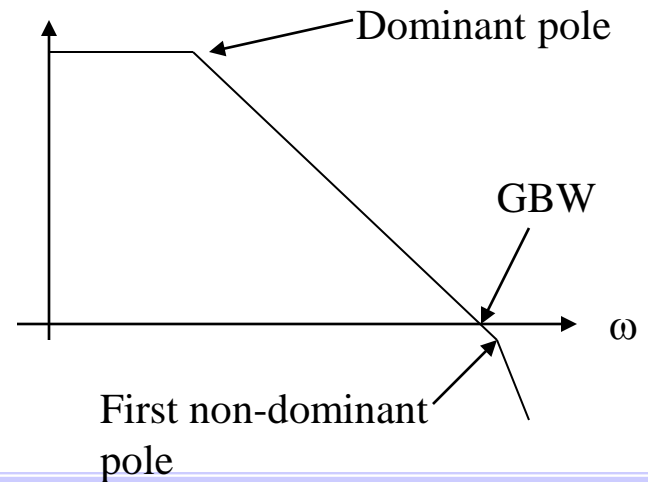- 1 pole at vcm ( $1/RC$ )
- 1 pole at gate of M3 ( $g_{m3}/C_{P3}$ )
- 1 pole at the output ( $g_{o1}/C_1$ )
- In OPAMP's you can use resistors as common-mode detector due to the presence of the output buffers
- dc gain =  $0.5g_{m2}R_{o1}$






# Isolated Common-Mode Sensing

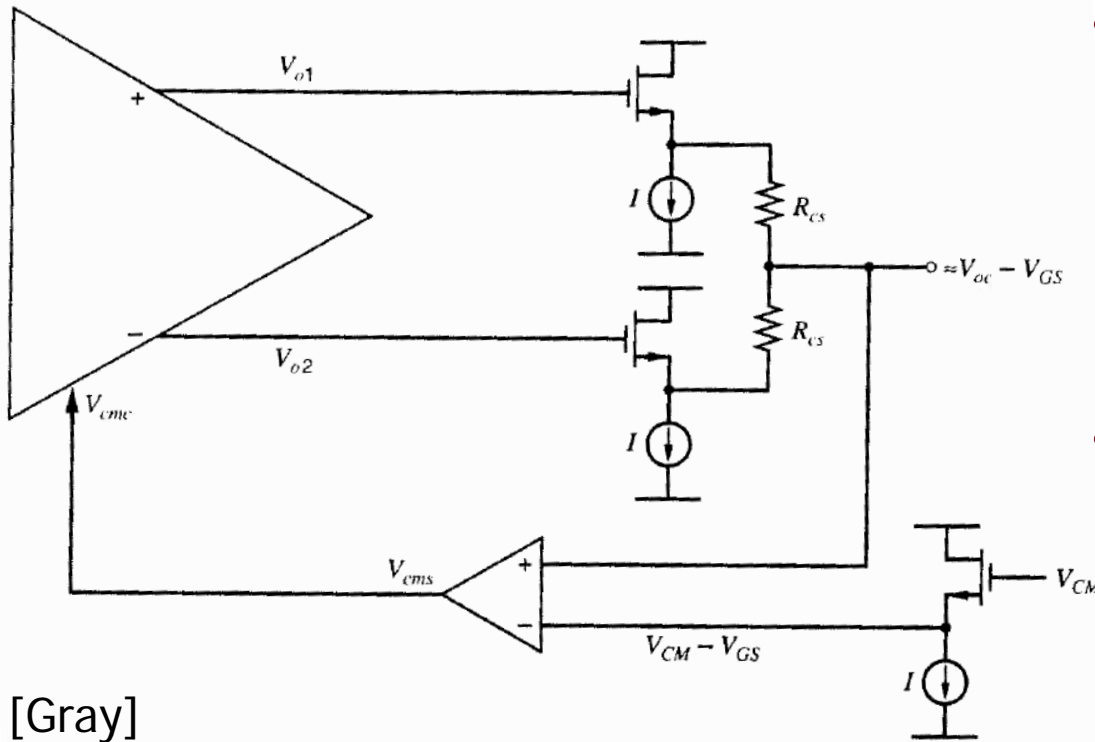

- Source-Followers isolate the loading of the common-mode sensor resistors
- Need to have a replica source follower to set the appropriate reference level for the CMFB amplifier

# Two Differential Pair CM Sensor

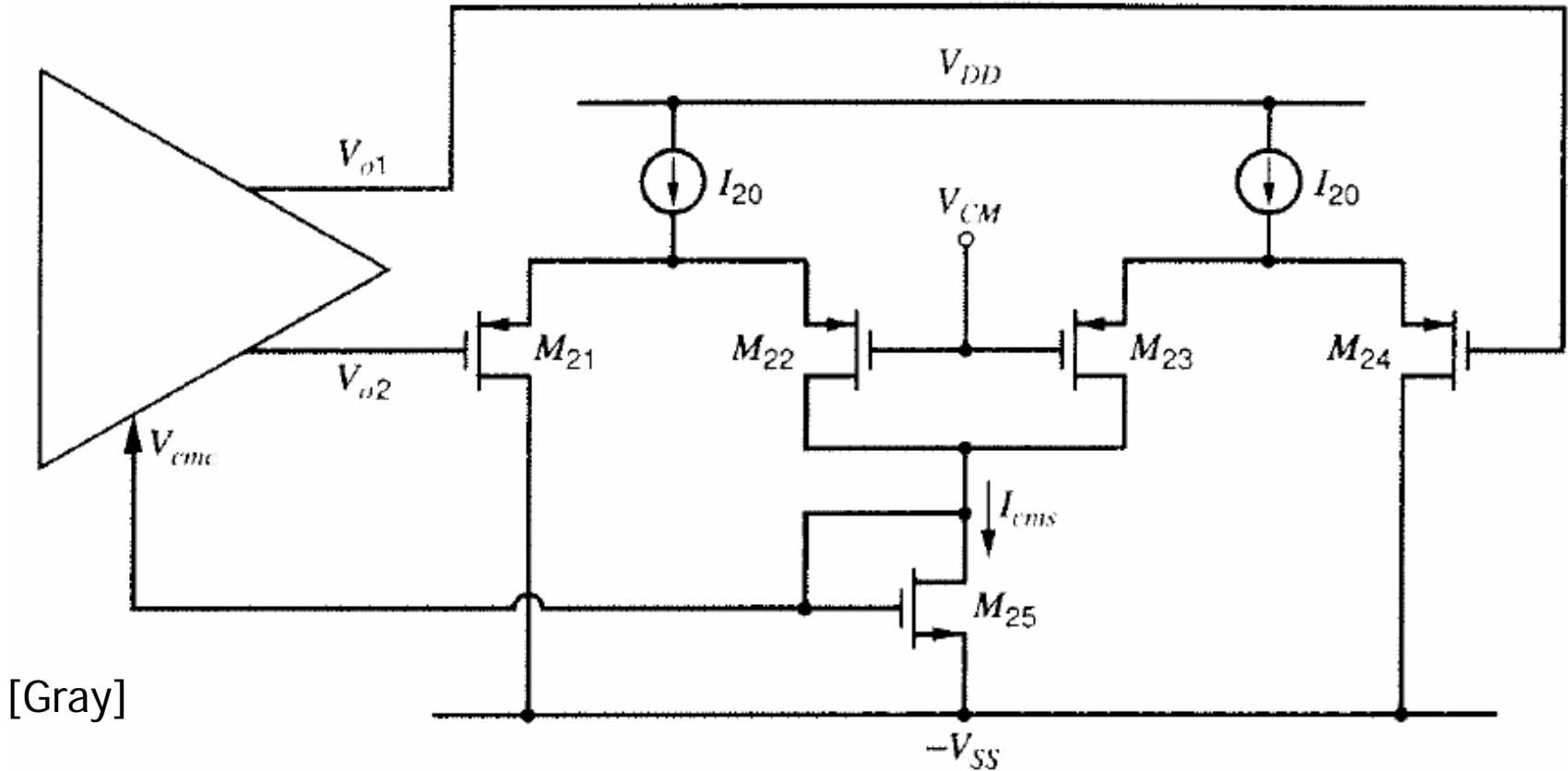


[Gray]

$$I_{cms} = I_{20} + g_{m22}(V_{oc} - V_{CM})$$

$$G_{cmf} = g_{m22}$$

# CMFB w/ Triode Devices in Tail Current Source

[Razavi]

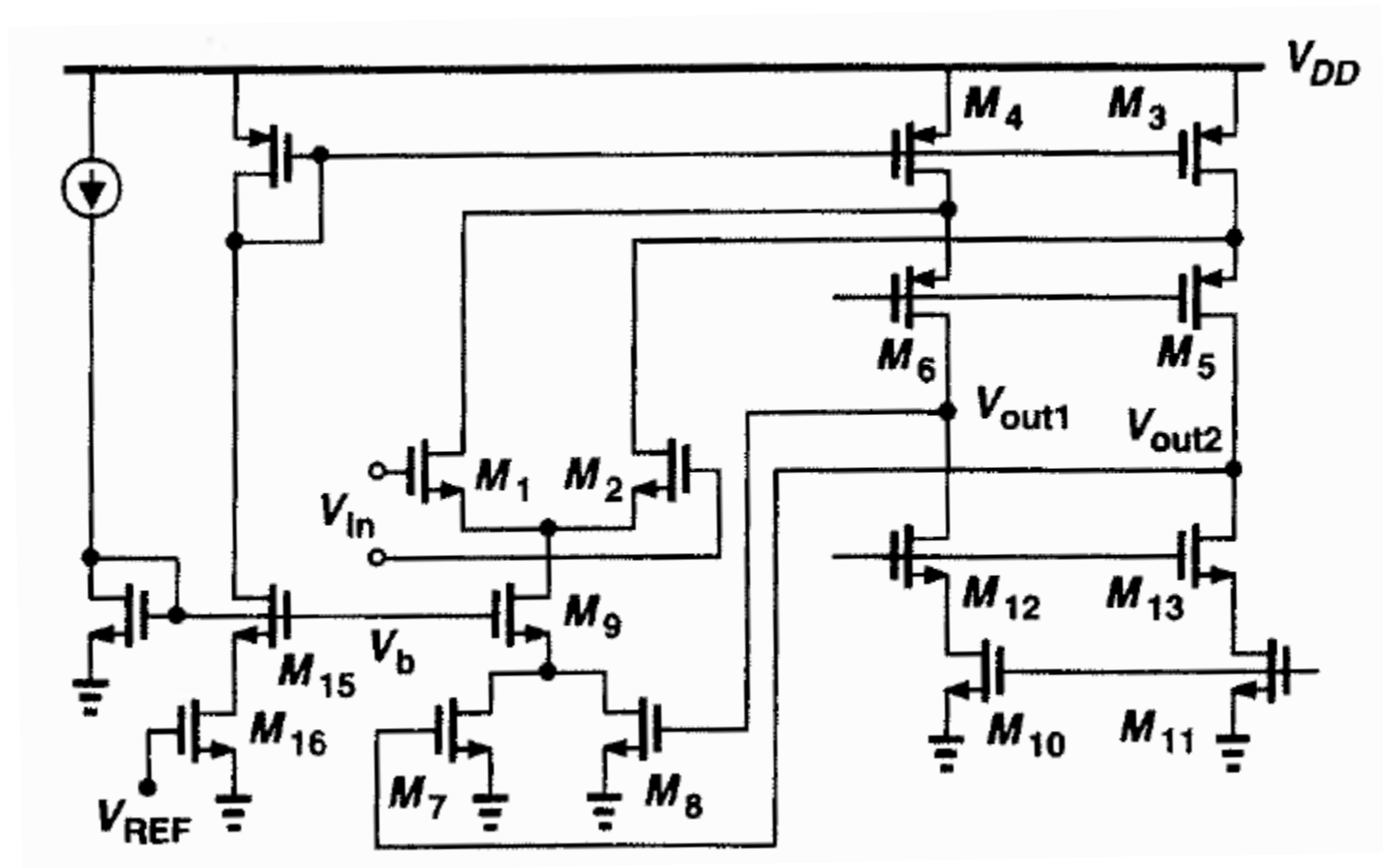

# Next Time

---

- OTA CMFB Examples
- Output Stages