

# ECEN474: (Analog) VLSI Circuit Design

## Fall 2012

---

### Lecture 18: OTA CMFB Examples



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

# Announcements

---

- No class on Monday
- Preliminary report still due Monday (11/19)
  - If you are doing anything not on the list, give me a brief description as soon as possible
- We will have class on Wednesday (11/21)
- Project Extra Credit
  - Potential for 20% extra credit if you layout a key block
  - Report on Dec. 4 doesn't have to have layout
  - For extra credit, an updated report can be turned in during the presentation time (Dec. 10) with layout results
    - The post-layout performance is the only thing that will be considered relative to the original report, i.e. no major circuit changes from the original report


# Agenda

---


- Multi-OTA stages CMFB
- OTA-C filter w/ CMFB example
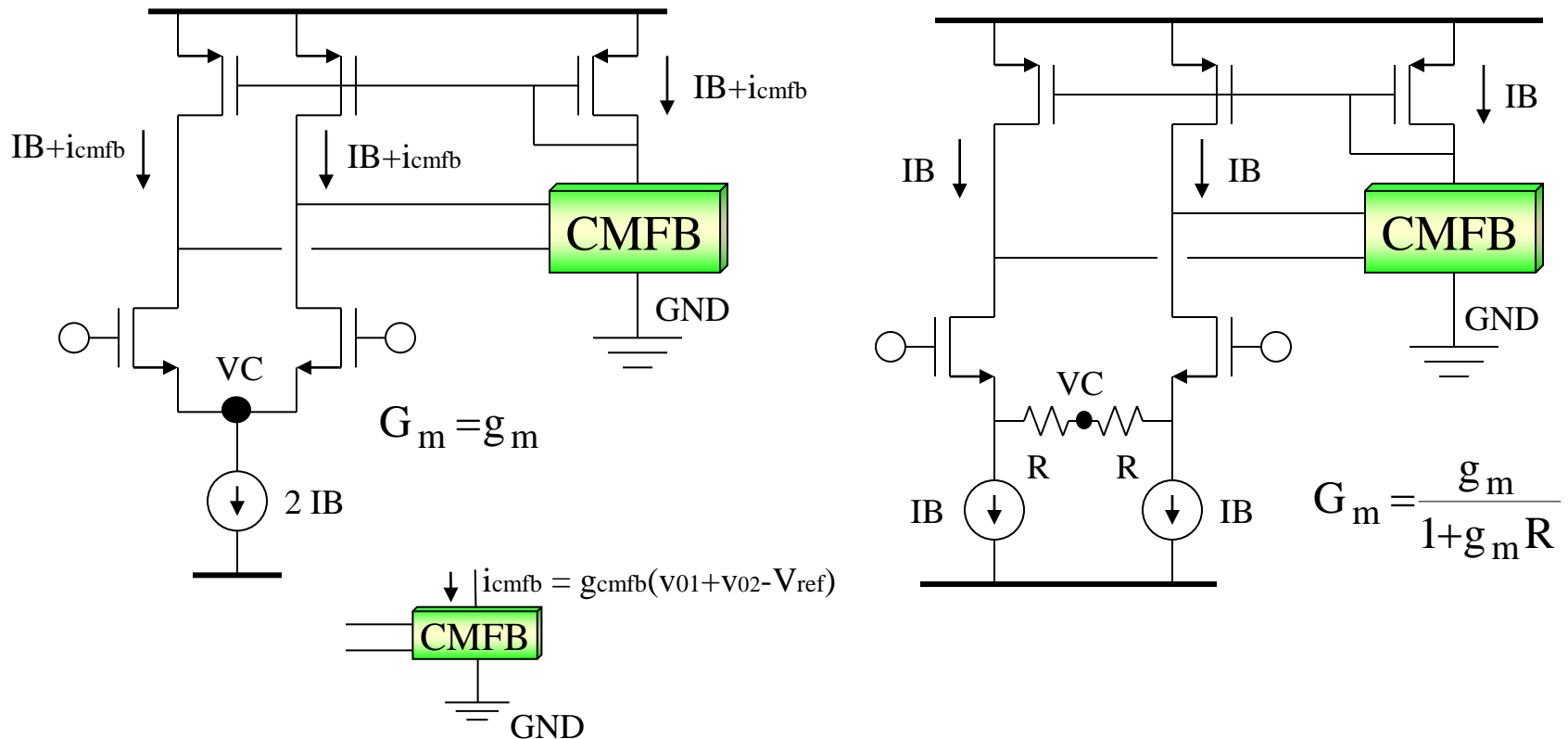
## CMFB is required for Differential Structures

CMFB Requirements: Fixes the OTA output (low offset) ==> High dc loop gain  
Reduction of common-mode noise ==> Large Bandwidth



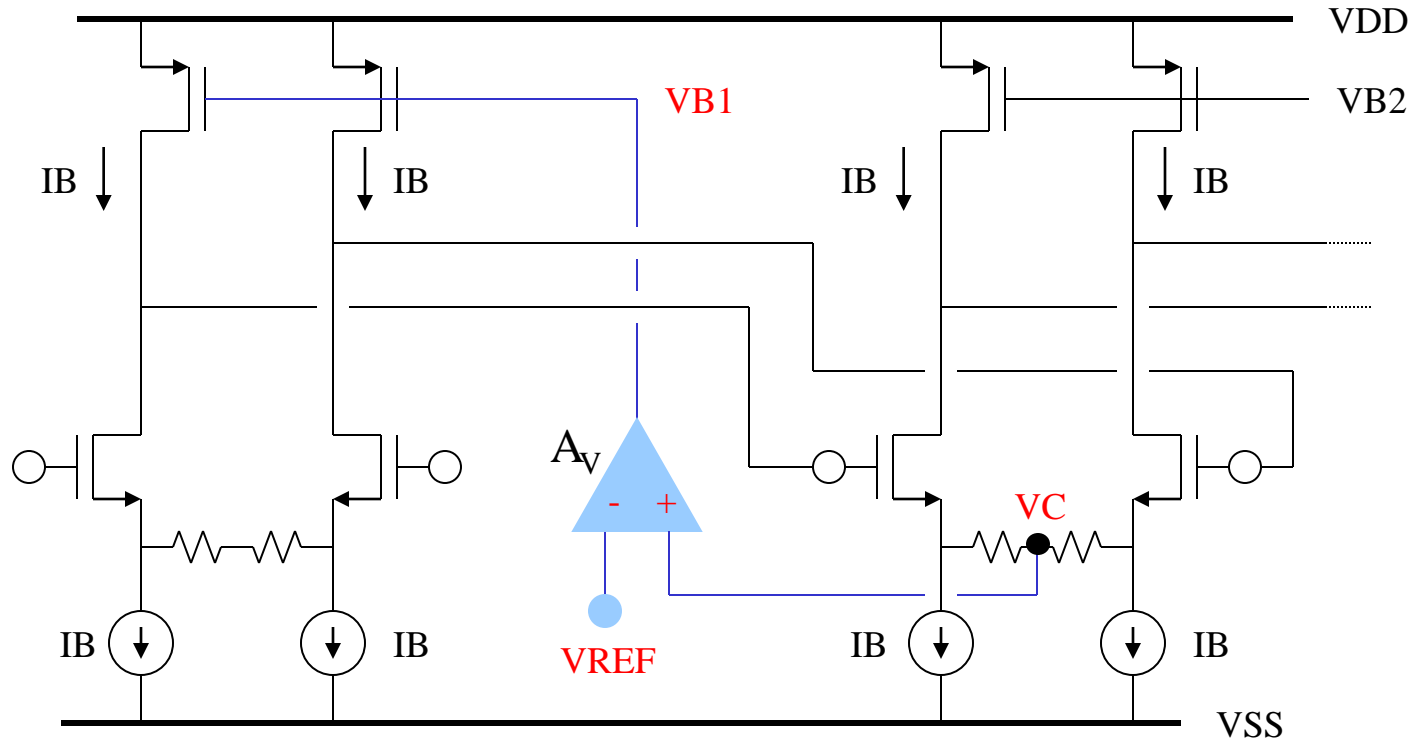
## Efficient CMFB for Differential Pair Based OTAs




**Common-mode loop gain =  $A_V G_{m_p} R_L$**

**3 poles in the CMFB loop. Loop stability requires  $A_V G_{m_p} / C_L < \omega_{p2} @ VC, \omega_{p3} @ VB1$**
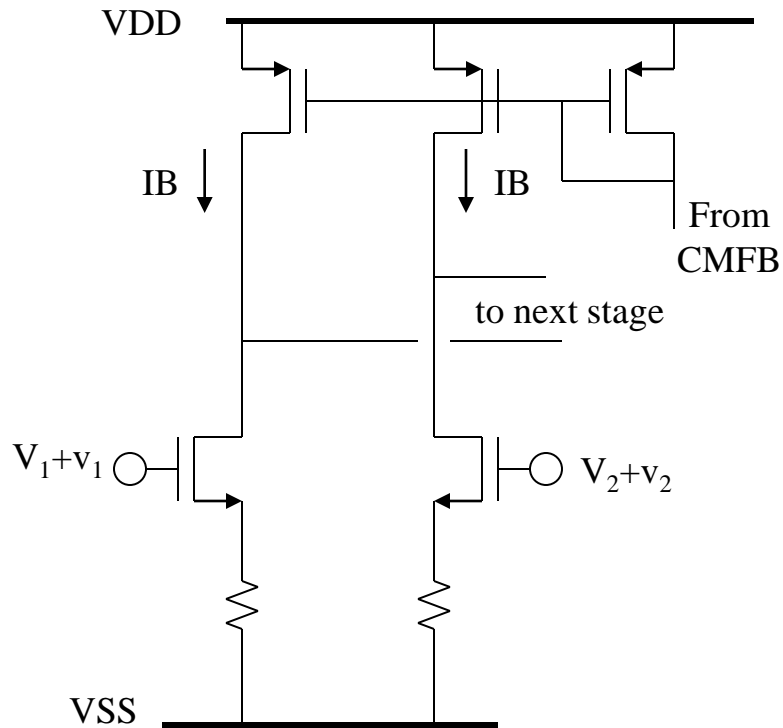
## Pseudo-Differential OTAs with Source Degeneration




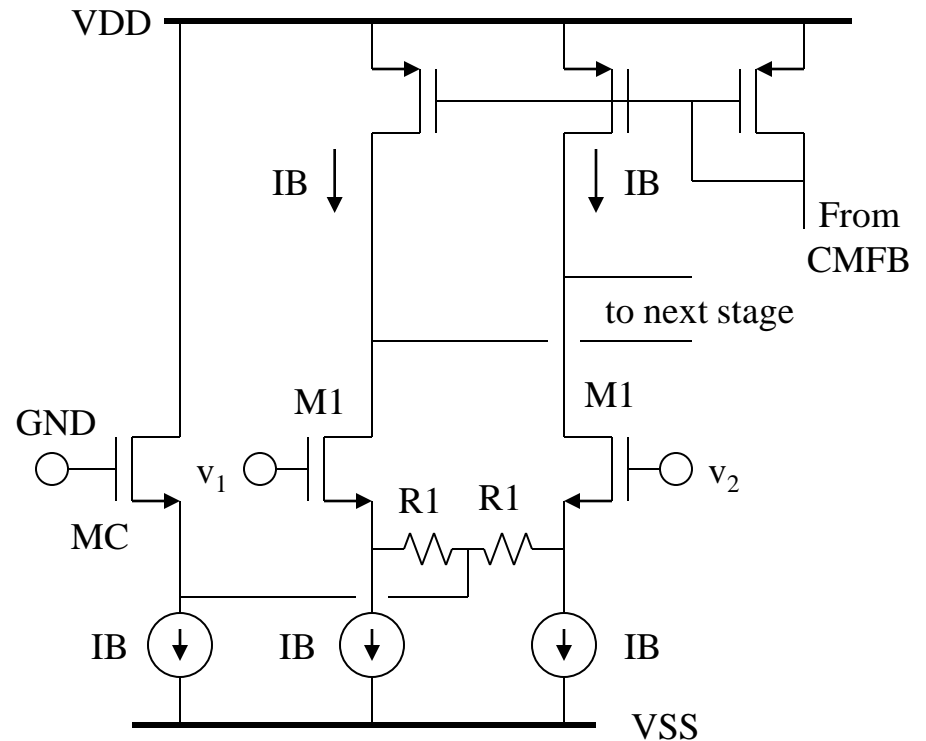**Sensitive to supply noise and common-mode input signals**




**Little sensitive to supply noise and Common-mode noise**
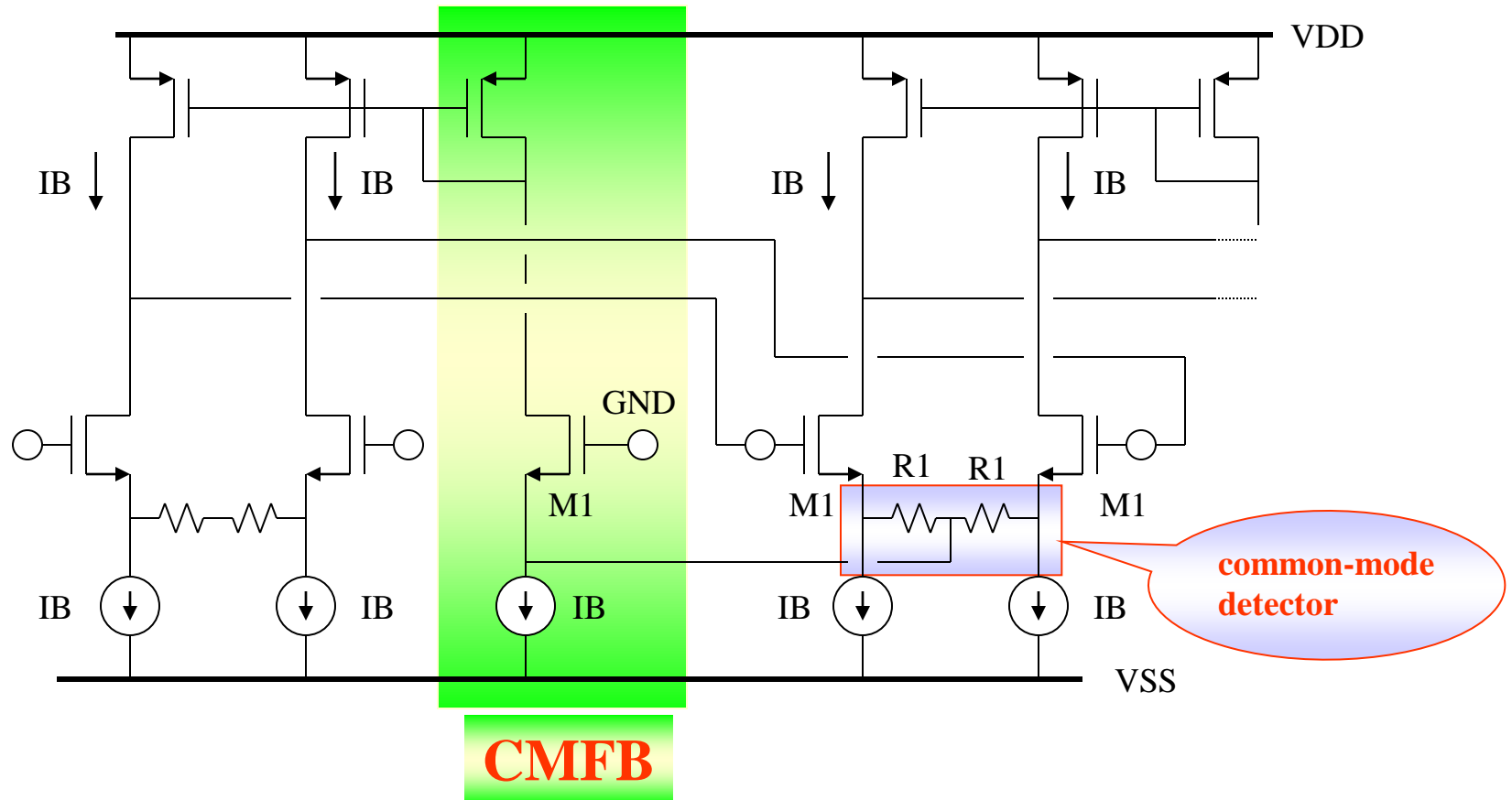
## Efficient CMFB for Pseudo-Differential OTAs


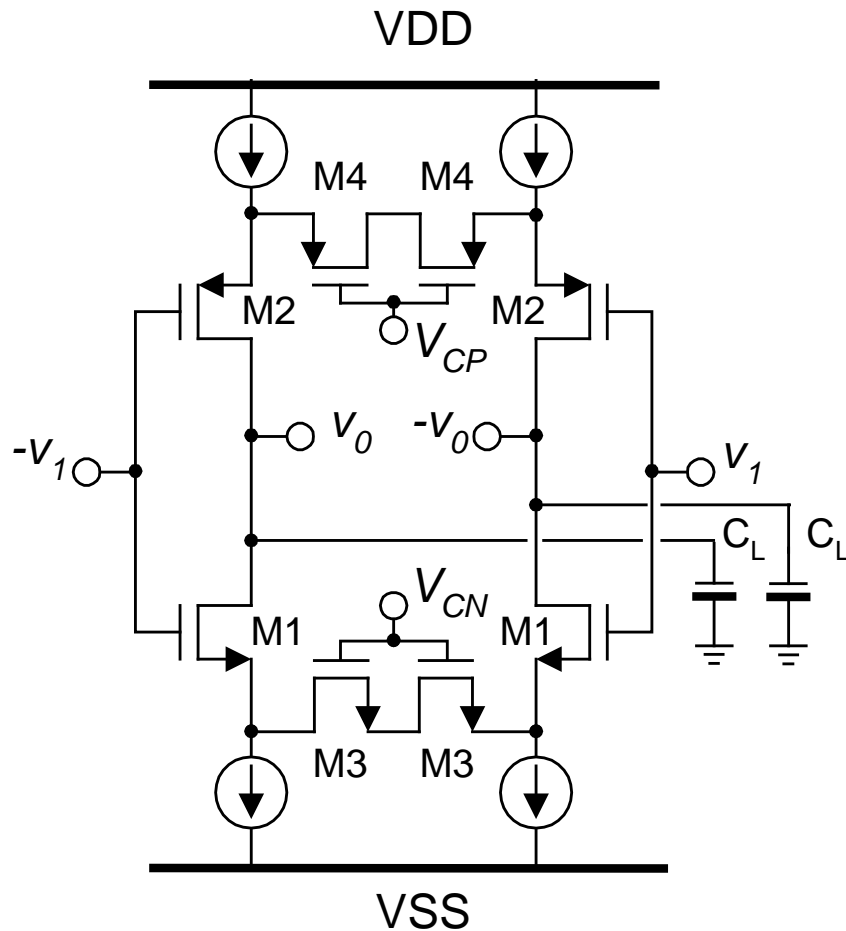
# OTA based on complementary differential pairs




- **Efficient OTA based on linear complementary differential pairs**

$$G_m = \frac{g_{m1}}{g_{m1}R_{M3} + 1} + \frac{g_{m2}}{g_{m2}R_{M2} + 1}$$

- **Linear circuit due to source degeneration M3 and M4**
- **Suitable for fast applications**



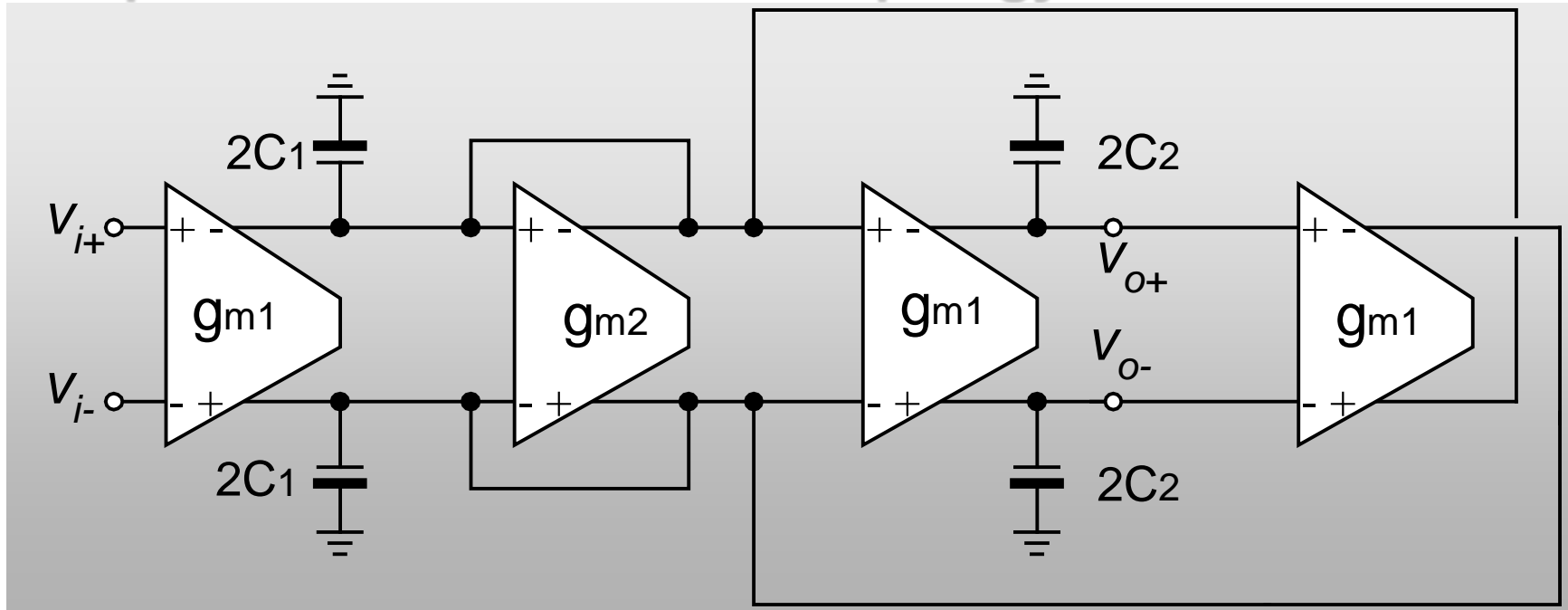
# Filter is based on Biquadratic Cells: Biquad Realization in Gm-C topology



	$f_0$ (MHz)	$G_{m1}$ (mA/V)	$G_{m2}$ (mA/V)
Biquad 1	537.6	5.4	9.6
Biquad 2	793.2	5.4	5.07


**!!! Fast CMFB  
is required**
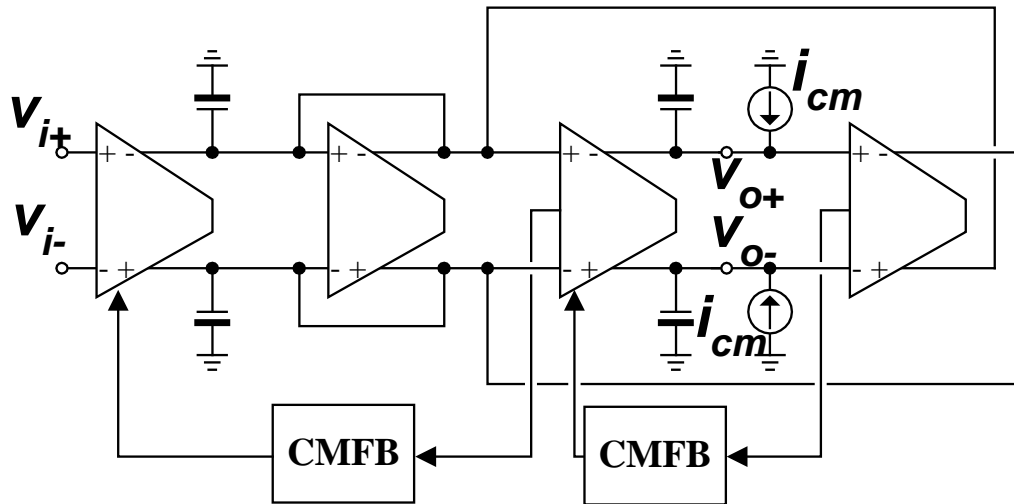
# Time Domain characterization of the CMFB




- Common-mode characterization using common-mode current pulses
- One CMFB circuit per pole

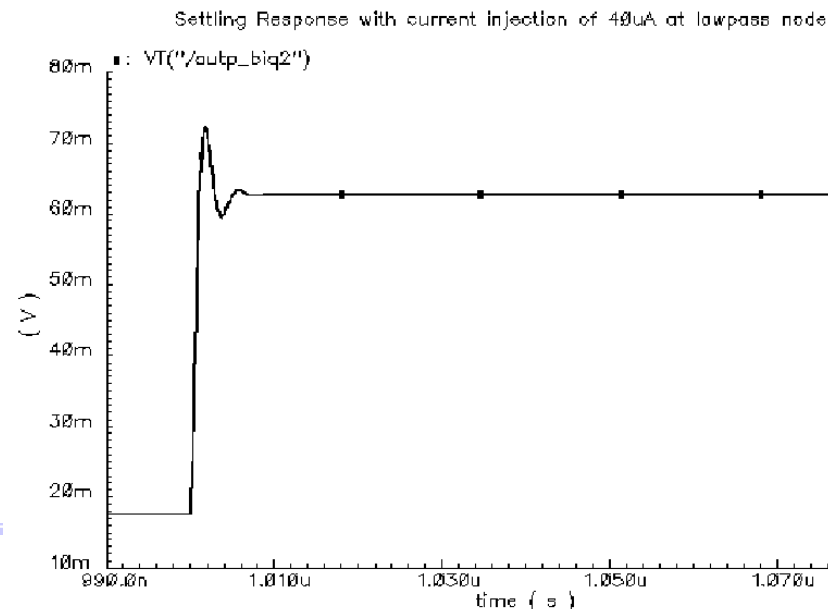- Pulse response of the CMFB
- Phase margin is better than 45 degrees




# OTA with Class AB Common-mode Feedback

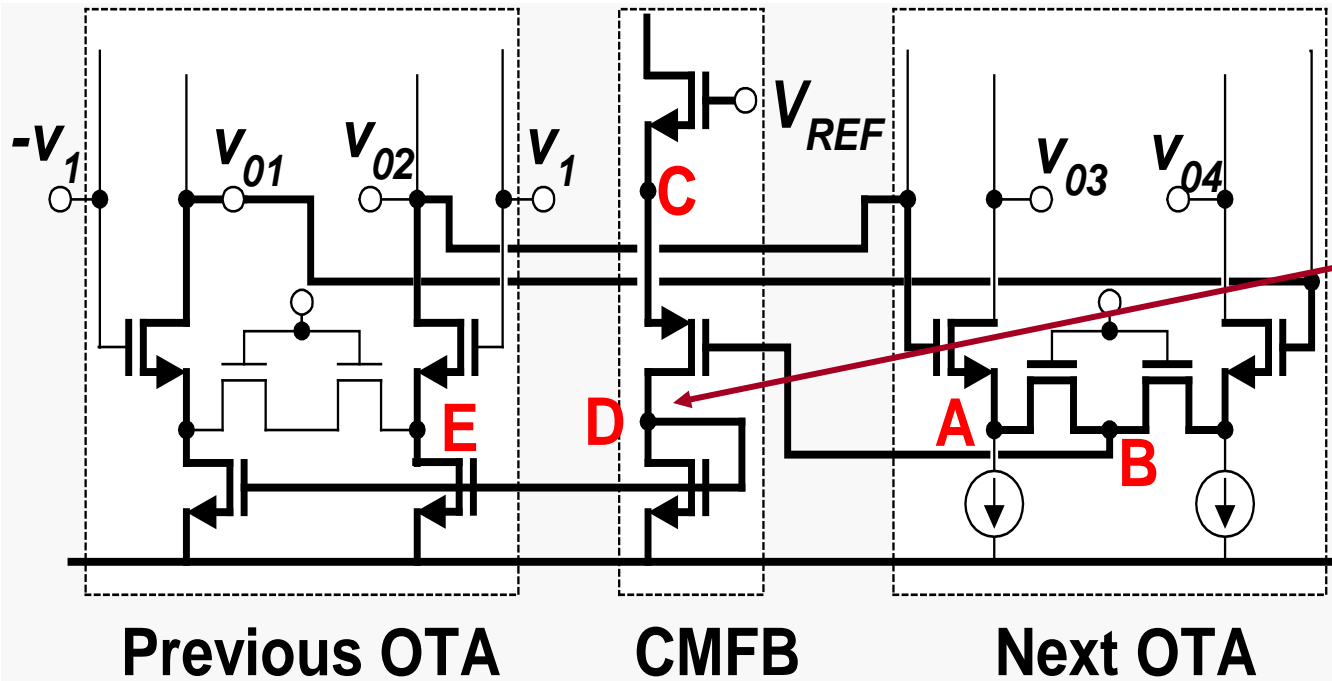

• Most important non-dominant pole at D


- Common-mode signal is detected at next stage
- Class AB error amplifier is used
- 5 non-dominant poles at A~E
- 2 LHP zeros at A and C (Helpful in BW extension)
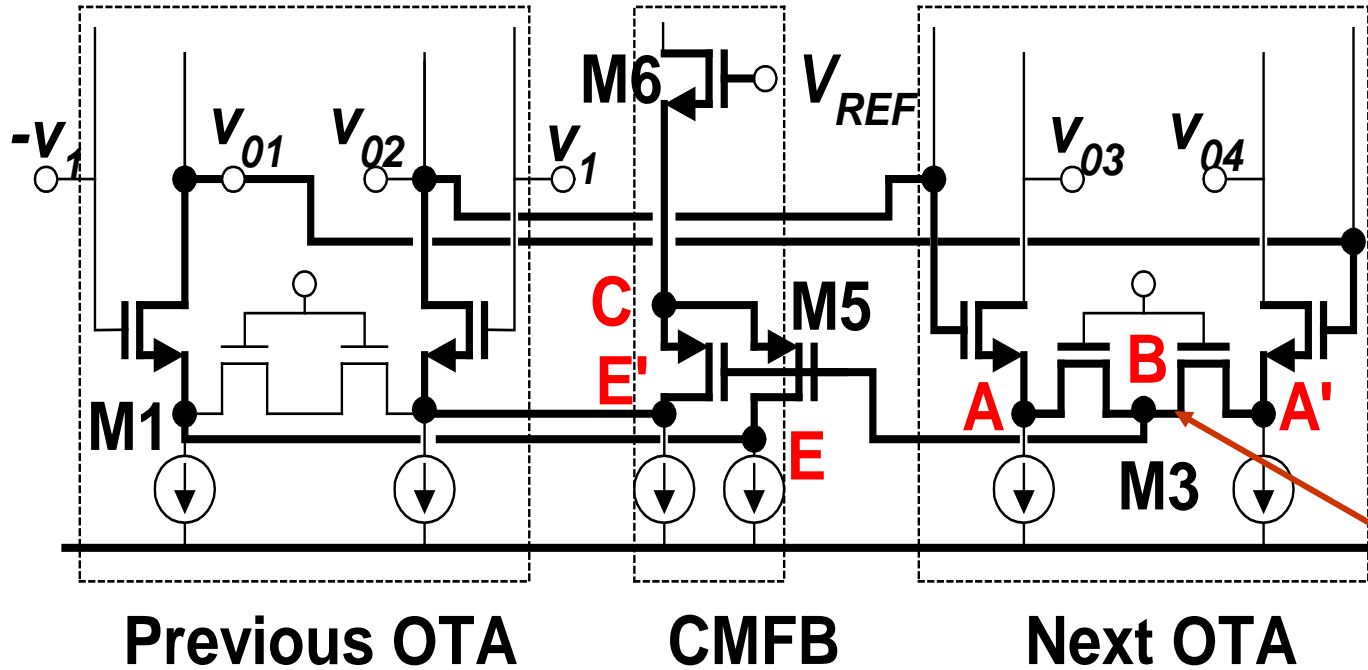
# Optimized Class AB Common-mode Feedback




- **Class AB error amplifier is used**
  - **4 non-dominant poles at A~E**
  - **2 LHP zeros at A and C (Helpful in BW extension)**
  - **Node D was eliminated**
- **Most important non-dominant pole at B**

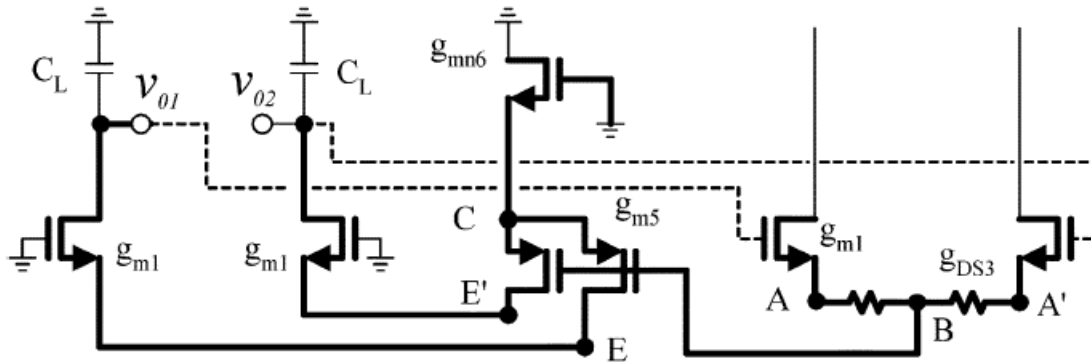
# Analysis of Class AB Common-mode Feedback


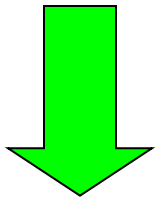
$$A_{VCMFB} \cong \frac{\frac{g_{m5}}{\left(1 + \frac{2g_{m5}}{g_{m6}}\right)g_L}}{\left(1 + \frac{sC_L}{g_L}\right)\left(1 + \frac{sC_B}{g_{03}}\right)\left(1 + \frac{sC_D}{g_{m1}}\right)}$$



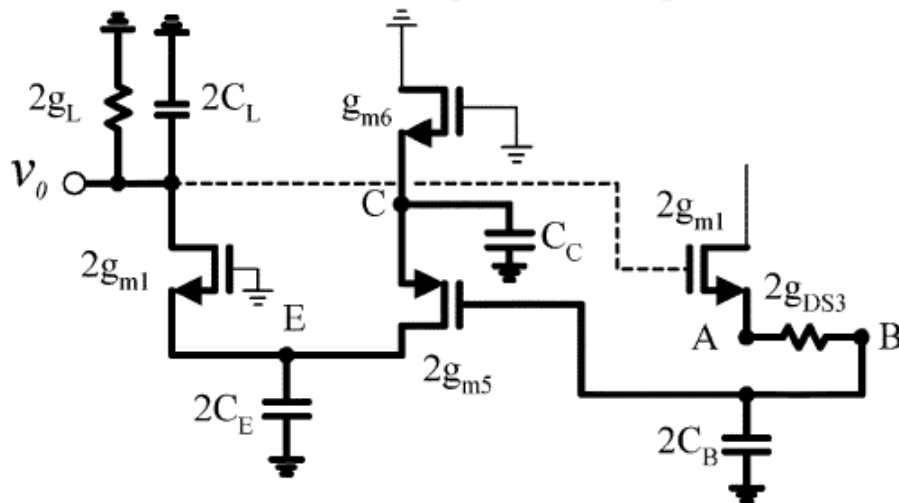**CMFB can be simplified taking advantage of circuit's symmetry**



- 2 pole-zero pairs (A and C) are very close to each other

- More stable CMFB

---

## Remarks

- **DC operating points for high impedances are difficult to fix**
- **Fully differential amplifiers with high output impedance nodes must use common-mode feedback circuits .**
- **Common mode circuits can fix the DC operating points as well as minimize the common mode output components.**
- **Low voltage constraints impose optimal bias conditions at both the input and output ports of an amplifier.**
- **Common mode circuits for LV should be used both at the input and output**

# Next Time

---

- Analog Applications
  - OTA-C Filters
  - Variable-Gain Amplifiers
  - Switch-Cap Filters, Broadband Amplifiers
- Output Stages
- Bandgap Reference Circuits
- Distortion