

# ECEN474: (Analog) VLSI Circuit Design

## Fall 2010

---

### Lecture 28: Feedback TIAs



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

# Announcements

---

- Project
  - Preliminary report will be handed back on Wednesday with feedback
  - Final report due Dec 7
    - **Only one ideal current source for biasing allowed (not tail current source)**
    - **Cadence schematic of key circuits**
- Exam 3 on Dec 3
  - Reference exams posted today


# Agenda

---

- Feedback TIAs
- Material is related primarily to Project #6

# Common-Gate TIA

[Razavi]

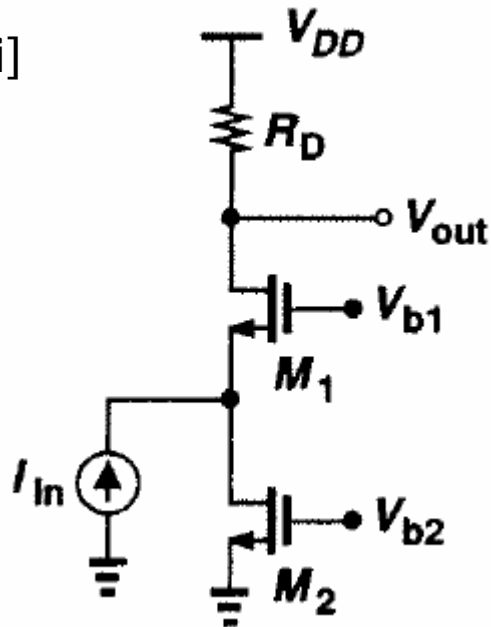

$$R_T = R_D$$


$$R_{in} \approx \frac{1}{g_{m1}}$$

$$\overline{I_{n,in}^2} = 4kT \left( \frac{2}{3} g_{m2} + \frac{1}{R_D} \right) \left( \frac{\text{A}^2}{\text{Hz}} \right)$$

- Input resistance (input bandwidth) and transimpedance are decoupled
- Both the bias current source and  $R_D$  contribute to the input noise current
- $R_D$  can be increased to reduce noise, but voltage headroom can limit this
- Common-gate TIAs are generally not for low-noise applications
- However, they are relatively simple to design with high stability

# Feedback TIA w/ Ideal Amplifier

[Sackinger]

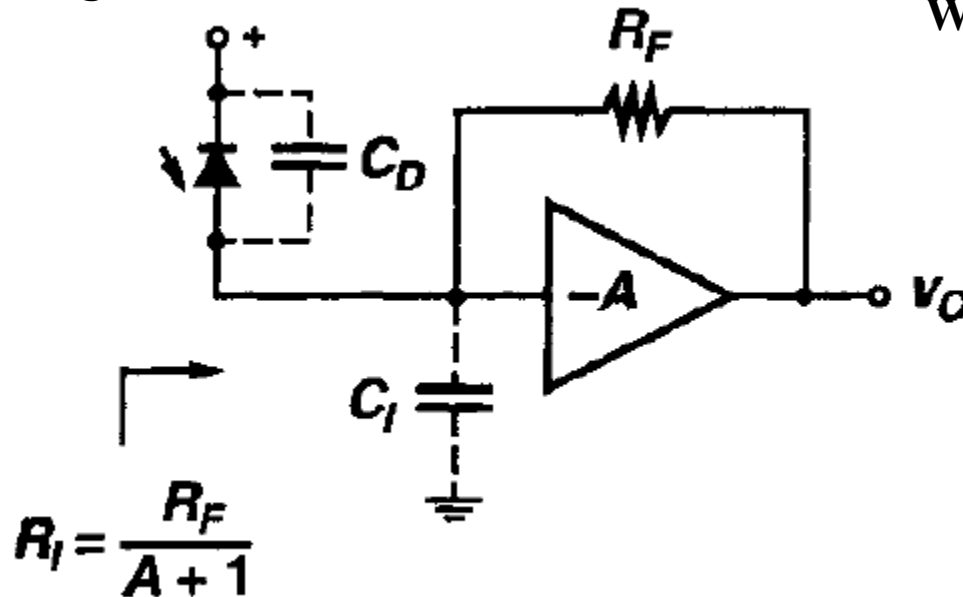

With Infinite Bandwidth Amplifier :

$$Z_T(s) = -R_T \left( \frac{1}{1 + s/\omega_p} \right)$$

$$R_T = \frac{A}{A + 1} R_F$$


$$R_{in} = \frac{R_F}{A + 1}$$

$$\omega_p = \frac{1}{R_{in} C_T} = \frac{A + 1}{R_F (C_D + C_I)}$$

- Input bandwidth is extended by the factor  $A + 1$
- Transimpedance is approximately  $R_F$
- Can make  $R_F$  large without worrying about voltage headroom considerations

# Feedback TIA w/ Finite Amplifier Bandwidth

[Sackinger]

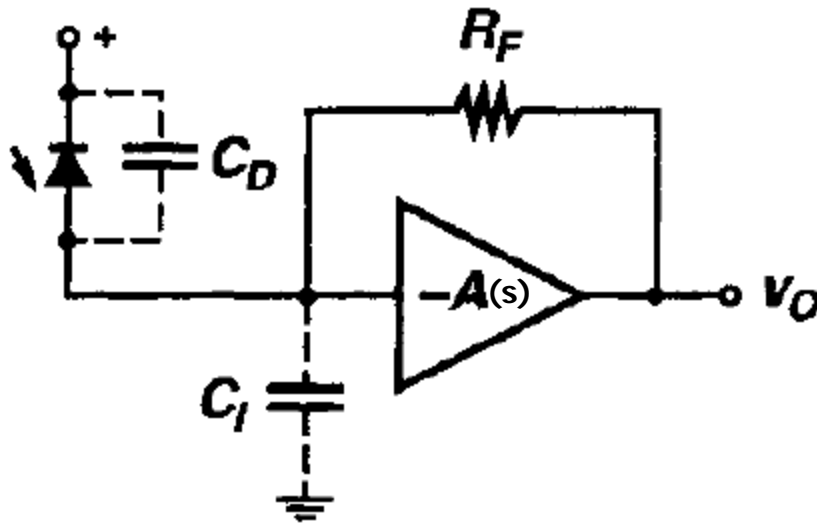

With Finite Bandwidth Amplifier :

$$A(s) = \frac{A}{1 + \frac{s}{\omega_A}} = \frac{A}{1 + sT_A}$$

$$Z_T(s) = -R_T \left( \frac{1}{1 + s/(\omega_o Q) + s^2/\omega_o^2} \right)$$

$$R_T = \frac{A}{A+1} R_F$$



$$\omega_o = \sqrt{\frac{A+1}{R_F C_T T_A}}$$

$$Q = \frac{\sqrt{(A+1)R_F C_T T_A}}{R_F C_T + T_A}$$

$$R_{in} = \frac{R_F}{A+1}$$
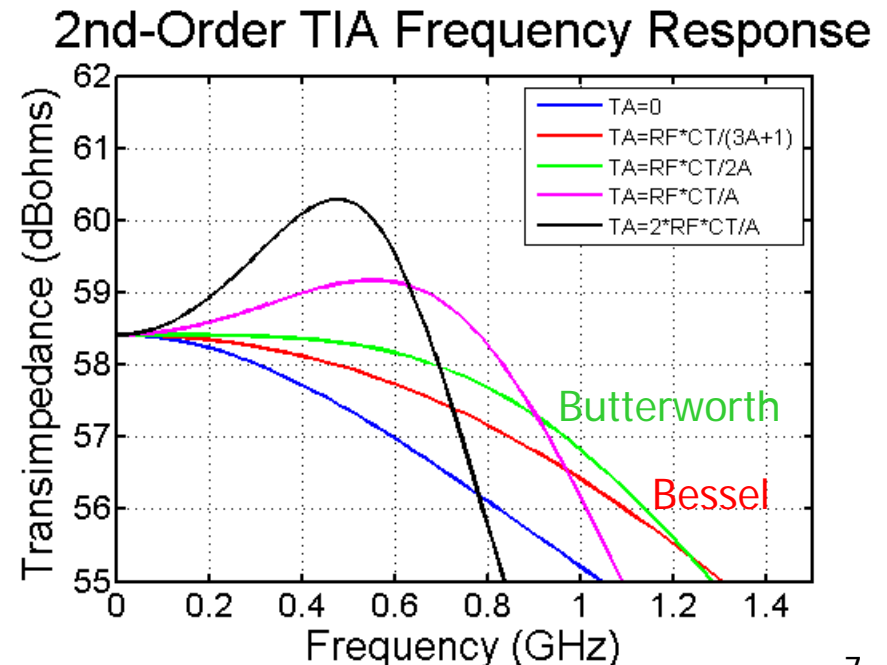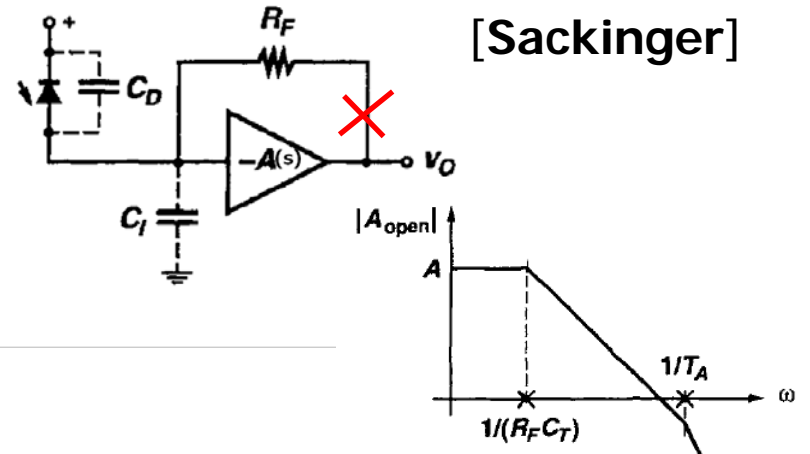
# Feedback TIA w/ Finite Amplifier Bandwidth

- Non-zero amplifier time constant can actually increase TIA bandwidth!!
- However, can result in peaking in frequency domain and overshoot/ringing in time domain
- Often either a Butterworth ( $Q=1/\sqrt{2}$ ) or Bessel response ( $Q=1/\sqrt{3}$ ) is used
  - Butterworth gives maximally flat frequency response
  - Bessel gives maximally flat group-delay



# Feedback TIA Transimpedance Limit

If we assume a Butterworth response for maximally flat frequency response :

$$Q = \frac{1}{\sqrt{2}} \quad \omega_A = \frac{1}{T_A} = \frac{2A}{R_F C_T}$$

For a Butterworth response :

$$\omega_{3dB} = \omega_0 = \sqrt{\frac{(A+1)\omega_A}{R_F C_T}} = \frac{\sqrt{(A+1)2A}}{R_F C_T} \approx \sqrt{2} \text{ times larger than } T_A = 0 \text{ case of } \frac{A+1}{R_F C_T}$$

Plugging  $R_T = \frac{A}{A+1} R_F$  into above expression yields the maximum possible  $R_T$  for a given bandwidth

$$\sqrt{\frac{(A+1)\omega_A}{\left(\frac{A+1}{A}\right)R_T C_T}} \geq \omega_{3dB}$$


$$\text{Maximum } R_T \leq \frac{A \omega_A}{C_T \omega_{3dB}^2}$$

- Maximum  $R_T$  proportional to amp gain-bandwidth product
- If amp GBW is limited by technology  $f_T$ , then in order to increase bandwidth,  $R_T$  must decrease quadratically!



# Feedback TIA

[Razavi]

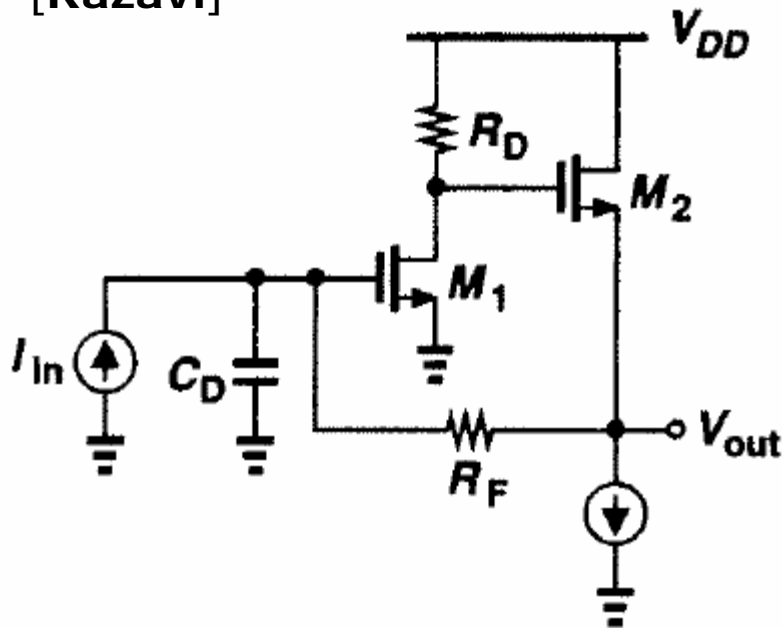

Assuming that the source follower has an ideal gain of 1

$$A = g_{m1} R_D$$



$$R_T = \frac{g_{m1} R_D}{1 + g_{m1} R_D} R_F$$

$$R_{in} = \frac{R_F}{1 + g_{m1} R_D}$$

$$R_{out} = \frac{1}{g_{m2} (1 + g_{m1} R_D)}$$

# Common-Gate & Feedback TIA

[Sackinger]

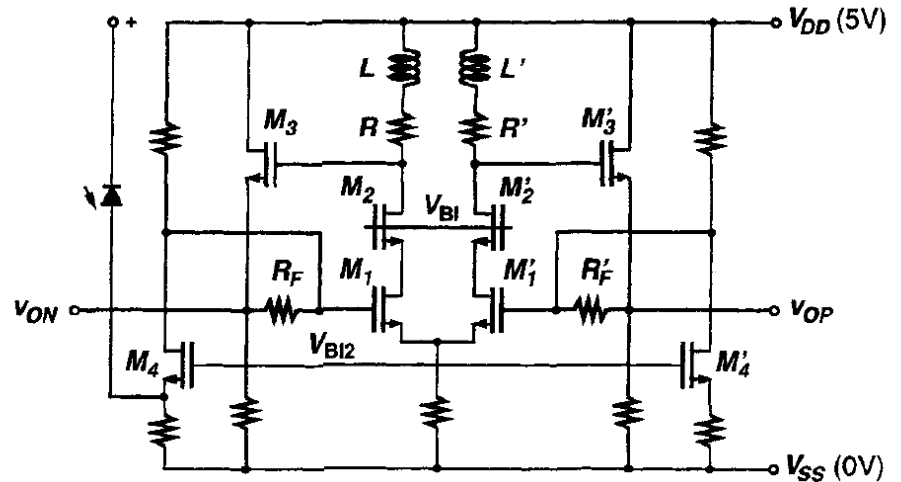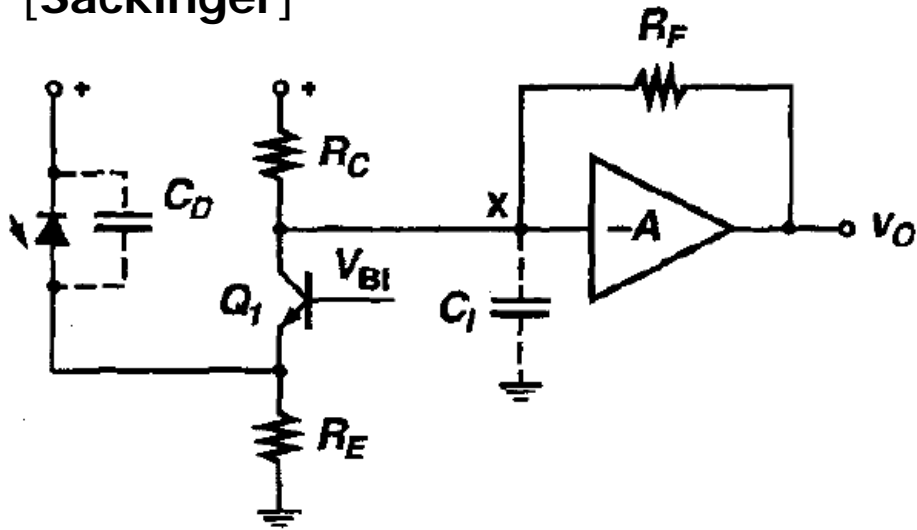


- Common-gate input stage isolates  $C_D$  from input amplifier capacitance, allowing for a stable response with a variety of different photodetectors
- Transimpedance is still approximately  $R_F A / (1 + A)$

# CMOS Inverter-Based Feedback TIA

---

[Sackinger]

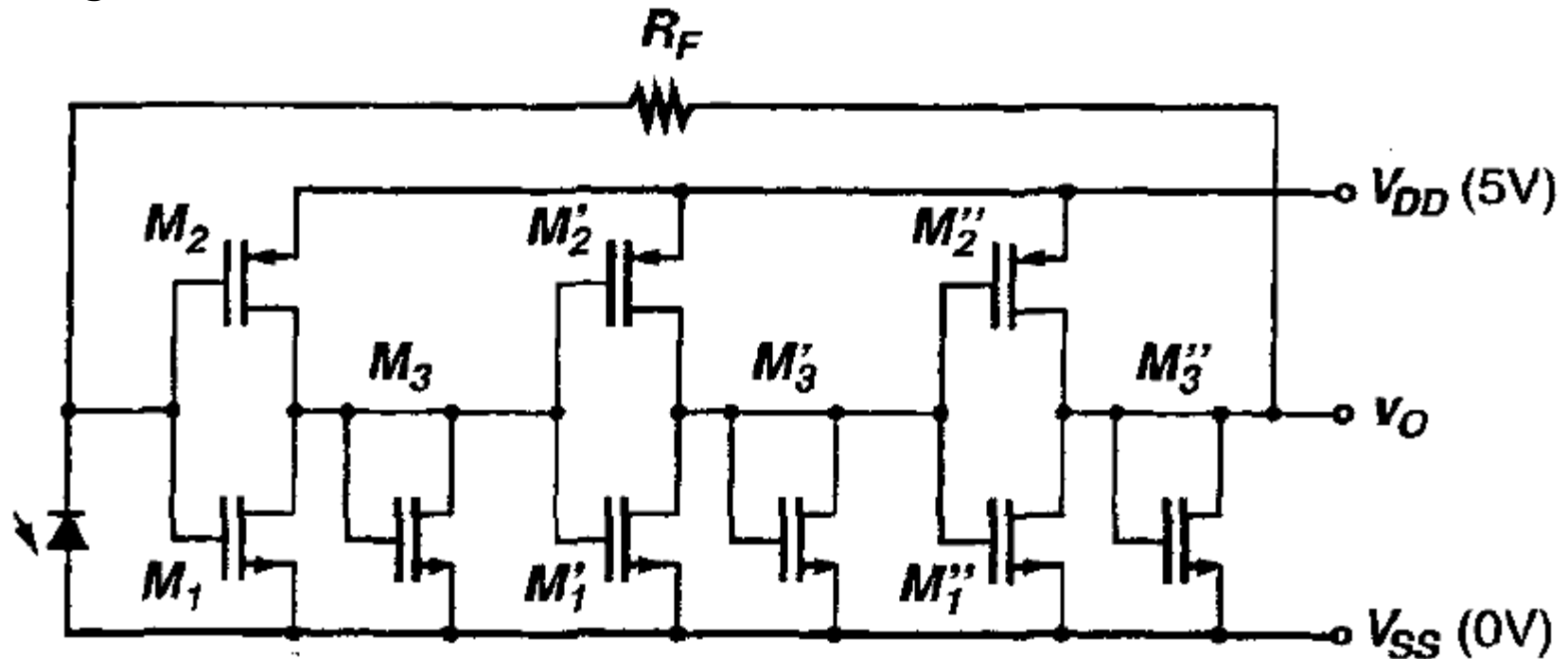

# Next Time

---

- Bandgap References
- Distortion