

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 620 – Network Theory (Broadband Circuit Design)

Fall 2020

Exam #2

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are 4 pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!


Problem	Score	Max Score
1		50
2		50
Total		100

Name: SAM PALERMO

UIN: _____

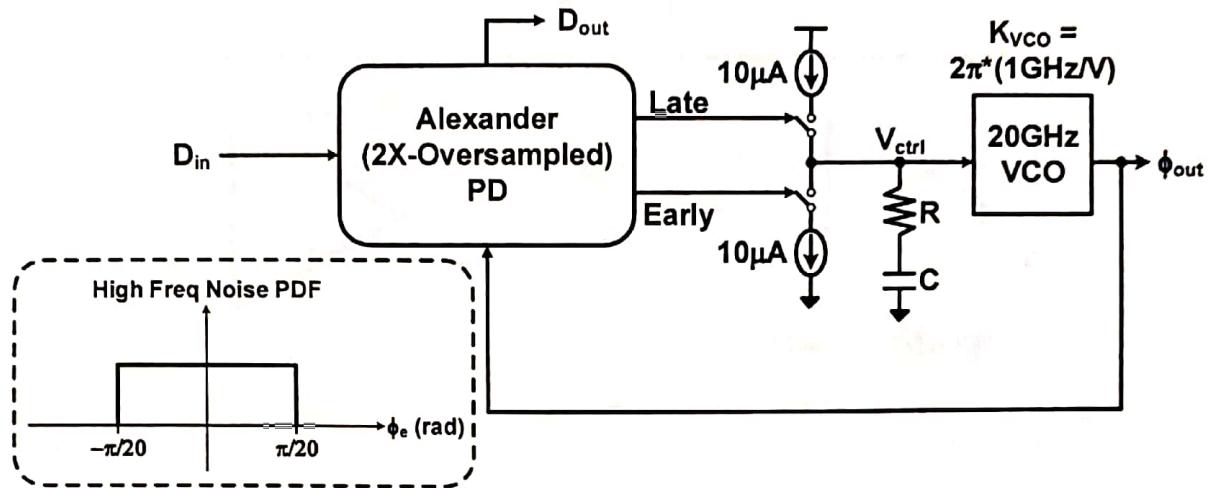Problem 1 (50 points)

For the CDR shown below, assume that the incoming data has a **transition density** $TD = 0.7$. Assume that high-frequency phase noise, given by the uniform PDF below, is present and linearizes the system. Design the loop filter components to yield $\zeta = 1$ and $\omega_{3dB} = 2\pi \cdot (20\text{MHz})$. Note, for $\zeta = 2$, $\omega_{3dB} = 2.48 \cdot \omega_n$.



Closed-loop CDR transfer function

$$H(s) = \frac{2\beta \omega_n (s + \frac{\omega_n}{2\beta})}{s^2 + 2\beta \omega_n s + \omega_n^2}$$

where $\omega_n = \sqrt{\frac{K_{PD} I_{CP} K_{VCO}}{C}}$ and K_{PD} is the linearized

$$K_{PD} = \frac{2}{5_{PP}} (TD) = \frac{2}{\pi/10} (0.7) = \frac{14}{\pi}$$

$$\beta = \frac{\omega_n}{2} RC$$

$$C = \frac{K_{PD} I_{CP} K_{VCO}}{\omega_n^2} = \frac{K_{PD} I_{CP} K_{VCO} (2.48)^2}{\omega_{3dB}^2} = \frac{(\frac{14}{\pi})(10_{\mu A})(2\pi 1642/V)(2.48)^2}{(2\pi 20\text{MHz})^2}$$

$$C = 109\text{pF}$$


$$R = \frac{2\beta}{\omega_n C} = \frac{2\beta (2.48)}{\omega_{3dB} C} = \frac{2(1)(2.48)}{(2\pi 20\text{MHz})(109\text{pF})} = 362\Omega$$

$$R = 362\Omega$$

$$C = 109\text{pF}$$

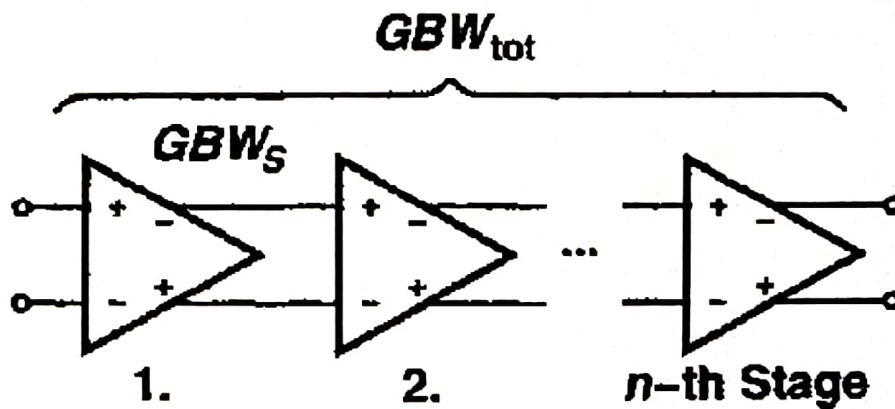Problem 2 (50 points)

Assume that the limiting amplifier below consists of cascaded identical single-pole amplifier stages, with gain A_{vs} and bandwidth ω_{3dBs} .



- a) Design the limiting amplifier to achieve a 26dB total gain and 25GHz total bandwidth with the minimum per-stage gain-bandwidth product. Give the stage number and the per-stage gain and bandwidth. Also compute the per-stage gain-bandwidth product.

$$n_{opt} = 2 \ln(A_{tot}) = 2 \ln(20) = 5.94 \Rightarrow 6 \text{ stages}$$

$$A_{vs} = \sqrt[n]{A_{tot}} = \sqrt[6]{20} = 1.65$$

$$\omega_{3dB_{tot}} = \omega_{3dBs} \sqrt{2^{1/n} - 1} \Rightarrow \omega_{3dBs} = \frac{\omega_{3dB_{tot}}}{\sqrt{2^{1/n} - 1}}$$

$$\omega_{3dBs} = \frac{2\pi(25 \text{ GHz})}{\sqrt{2^{1/6} - 1}} = 449 \text{ Grad/s}$$

$$n = 6$$

$$A_{vs} = 1.65$$

$$\omega_{3dBs} = 449 \text{ Grad/s} \quad (715 \text{ Hz})$$

$$GBW_s = 7416 \text{ Grad/s} \quad (1186 \text{ Hz})$$

- b) Now let's use a more reasonable stage number. With $n=4$ and for the same 26dB total gain and 25GHz total bandwidth, compute the per-stage gain and bandwidth. Also compute the per-stage gain-bandwidth product.

$$A_{vs} = \sqrt[4]{20} = 2.11$$

$$\omega_{3dBs} = \frac{2\pi(25 \text{ GHz})}{\sqrt{2^{1/4} - 1}} = 3616 \text{ Grad/s}$$

$$A_{vs} = 2.11$$

$$\omega_{3dBs} = 3616 \text{ Grad/s} \quad (57.56 \text{ Hz})$$

$$GBW_s = 7626 \text{ Grad/s}$$

$$(1216 \text{ Hz})$$

Scratch Paper