

ECEN620: Network Theory Broadband Circuit Design Fall 2012

Lecture 10: Phase Detector Circuits



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University


Announcements & Agenda

- Exam 1 is on Wed. Oct 3
 - One double-sided 8.5x11 notes page allowed
 - Bring your calculator
- Phase Detector Circuits
 - Mixer PD
 - XOR PD
 - J-K Flip-Flop PD
 - Phase-Frequency Detector (PFD)


References

- *RF Microelectronics*, B. Razavi, Prentice Hall, 1998.
- *Design of Integrated Circuits for Optical Communications*, B. Razavi, McGraw-Hill, 2003.
- *Monolithic Phase-Locked Loops and Clock Recovery Circuits*, B. Razavi, Wiley, 1996.
- M. Perrott, *High Speed Communication Circuits and Systems Course*, MIT Open Courseware

Phase Detector

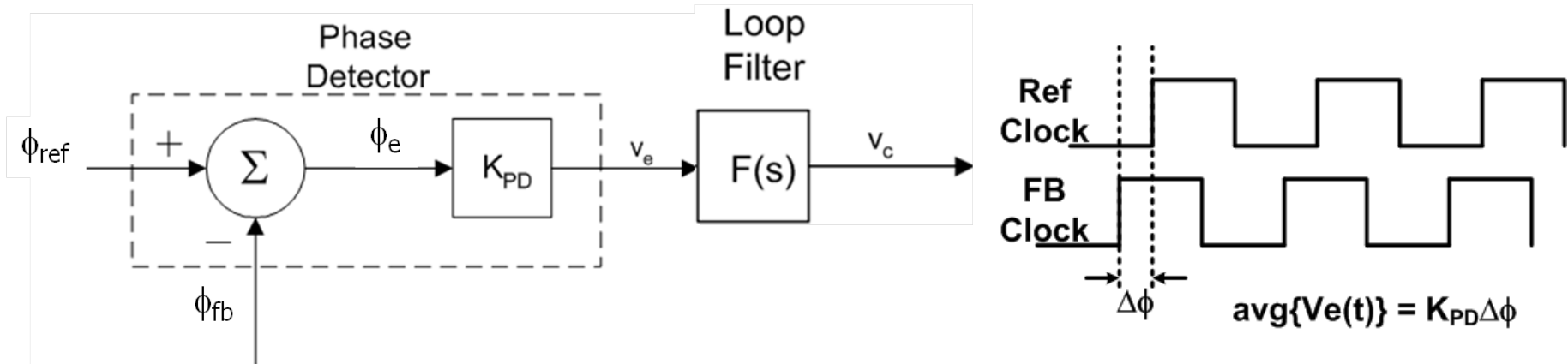

 - Detects phase difference between feedback clock and reference clock
- The loop filter will filter the phase detector output, thus to characterize phase detector gain, extract average output voltage
- The K_{PD} factor can change depending on the specific phase detector circuit




K_{PD} units are V/rad when used with a dimension - less filter

K_{PD} units are rad^{-1} (averaged) or A/rad when combined with the charge - pump

when used with a impedance filter


Analog Multiplier Phase Detector

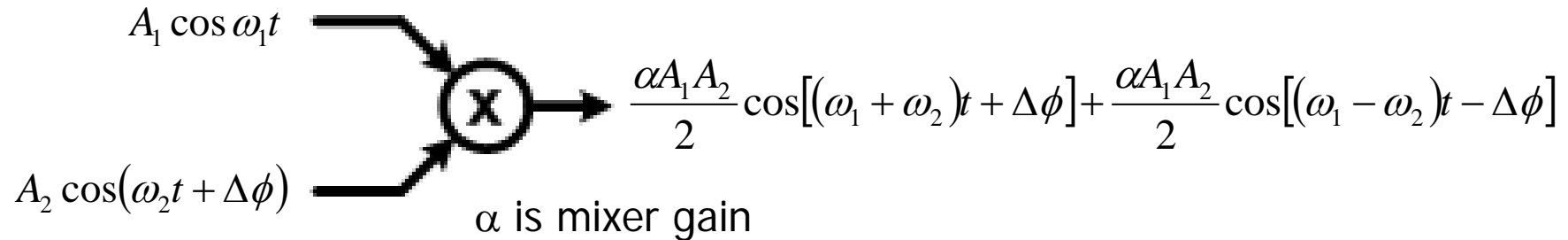

- If $\omega_1 = \omega_2$ and filtering out high-frequency term

$$\overline{y(t)} = \frac{\alpha A_1 A_2}{2} \cos \Delta\phi$$

 - Near $\Delta\phi$ lock region of $\pi/2$: $\overline{y(t)} \approx \frac{\alpha A_1 A_2}{2} \left(\frac{\pi}{2} - \Delta\phi \right)$



[Razavi]

Analog Mixer PD Properties

- The nominal lock point (zero frequency offset or Type-2) with a mixer PD is a 90° static phase shift
 - For many applications this is unimportant or can be cancelled elsewhere
- The mixer cannot serve as a frequency detector, as on average the output will be zero for a frequency difference
- K_{PD} is a function of the input amplitude, which is not desired

Mixer Circuits

Active Mixers



 


Figure 6.19 (a) Single-balanced mixer, (b) double-balanced mixer.

Passive Mixer

 


XOR Phase Detector

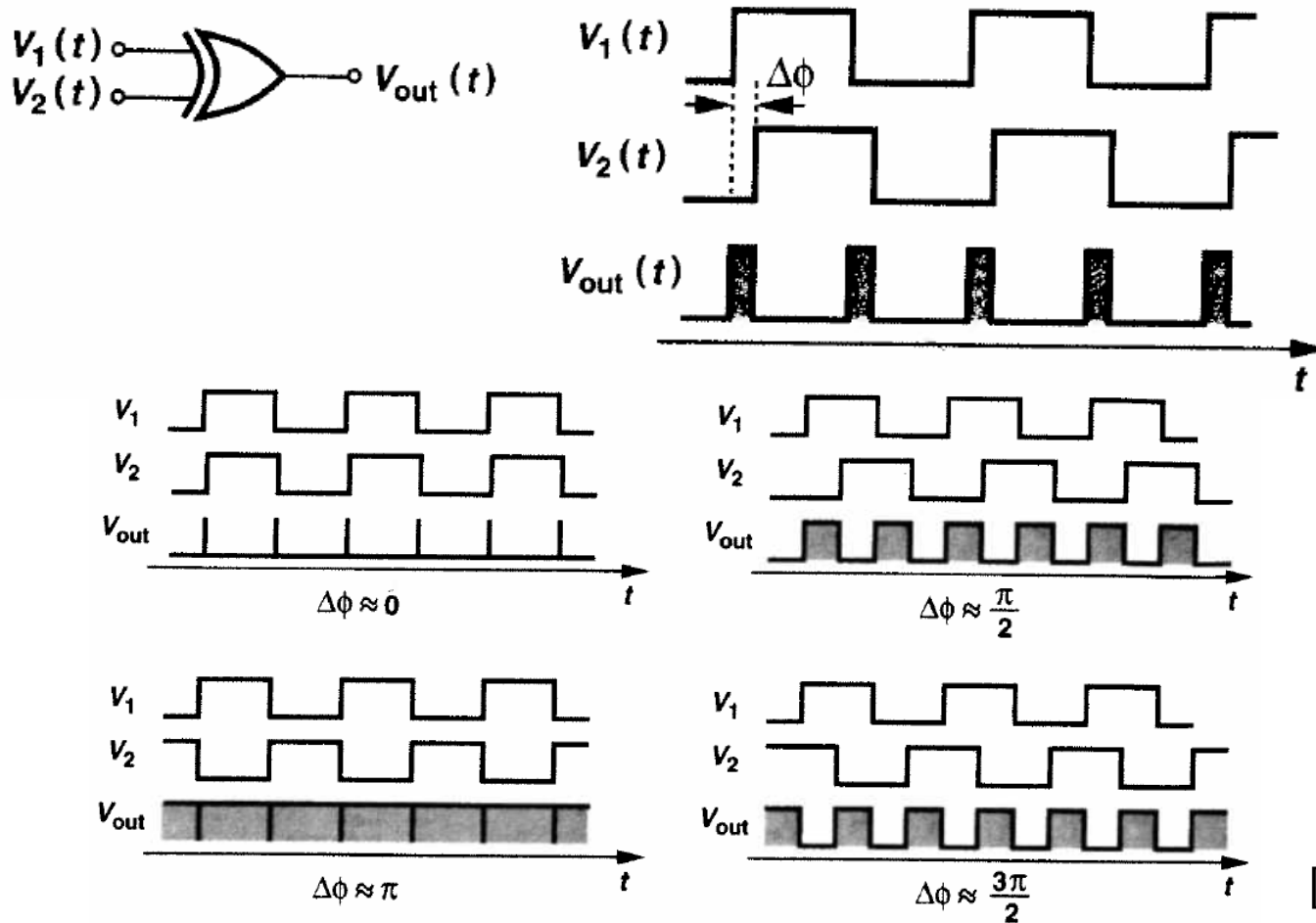


- Sensitive to clock duty cycle

XOR Phase Detector

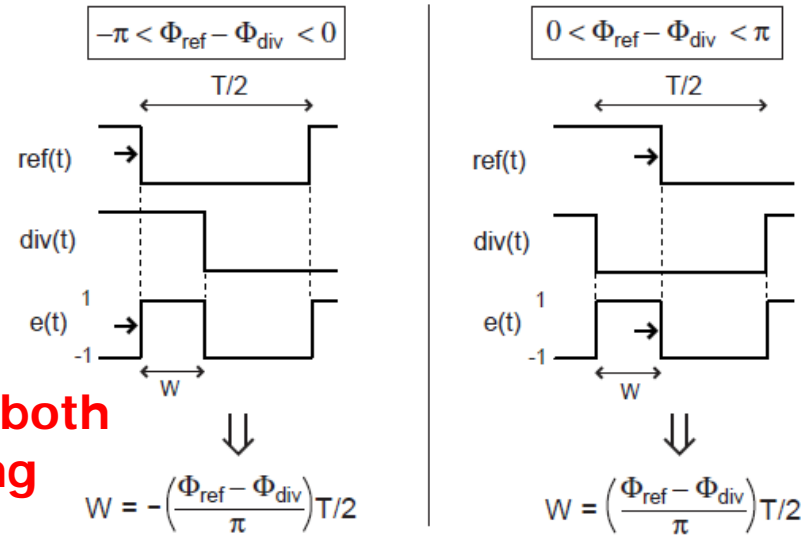


Width is same for both
leading and lagging
phase difference!

[Perrott]

 


Cycle Slipping

 - If there is a frequency difference between the input reference and PLL feedback signals the phase detector can jump between regions of different gain
 - PLL is no longer acting as a linear system



Cycle Slipping

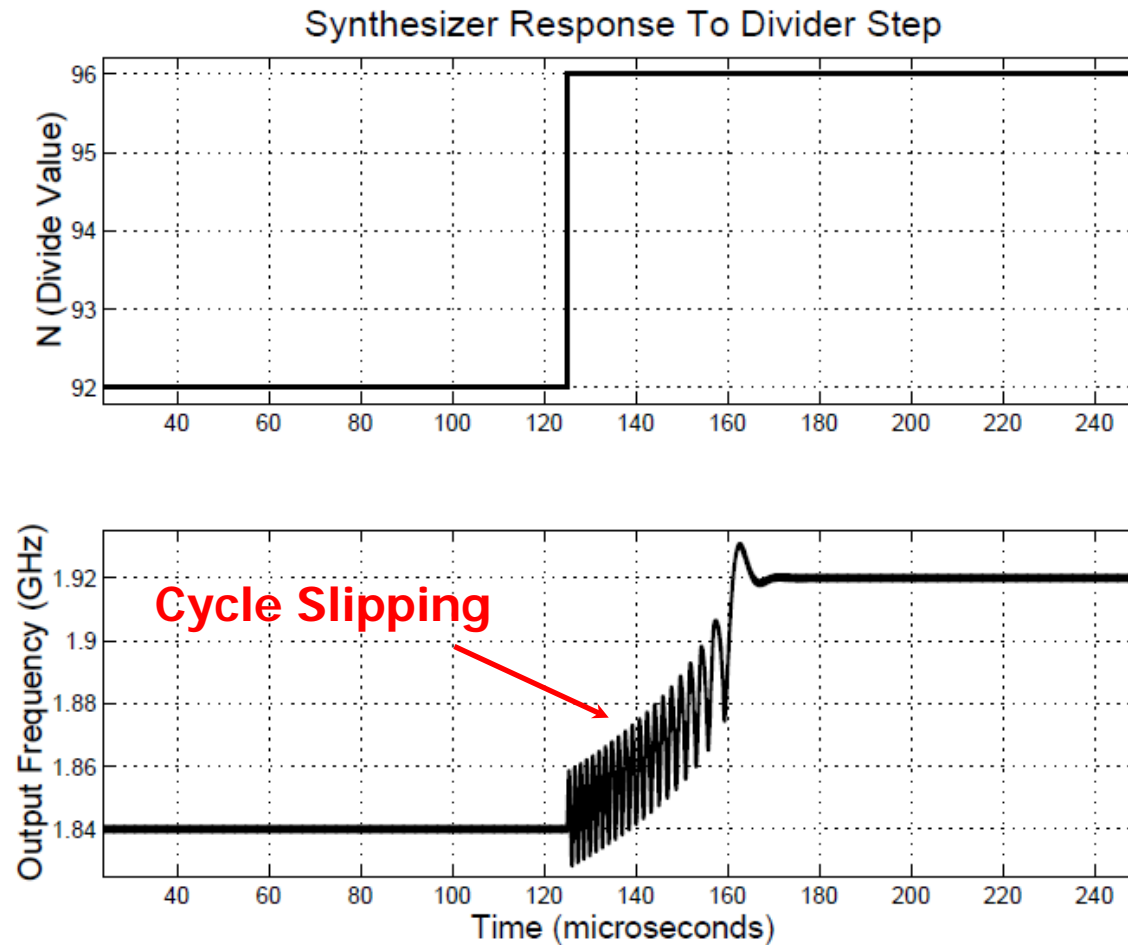


[Perrott]

- If frequency difference is too large the PLL may not lock


XOR PD Properties

- The nominal lock point with an XOR PD is also a 90° static phase shift
- Unlike the analog mixer, K_{PD} is independent of input amplitude and constant over a π phase range
- The XOR PD is sensitive to input duty cycle, and will lock with a phase error if the input duty cycles are not 50%


J-K Flip-Flop Phase Detector

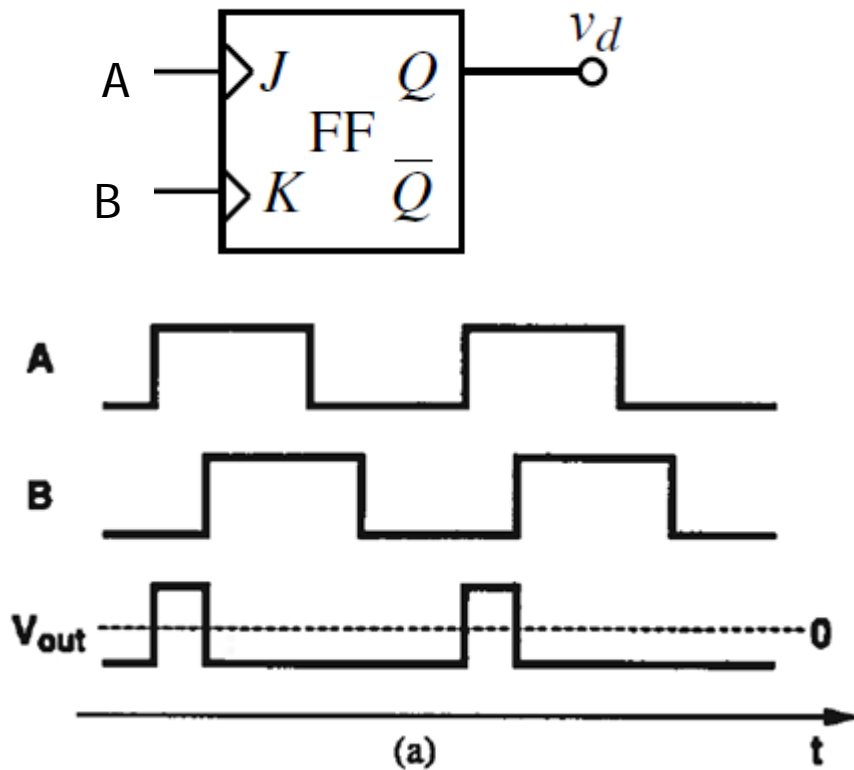


J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$

 


J-K Flip-Flop Details

 

J	K	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	$\overline{Q_n}$

 

 J-K Flip-Flop Phase Detector Harmonic Locking





- Harmonic signals can display the same DC output, leading to potential locking to harmonics

J-K Flip-Flop PD Properties


- The nominal lock point with an J-K Flip-Flop PD is a 180° static phase shift
- The J-K Flip-Flop PD is not sensitive to input duty cycle
- The J-K Flip-Flop displays a constant KPD over a 2π range
- There is the potential to lock to harmonics of the reference clock

Phase Frequency Detector (PFD)

  - Phase Frequency Detector allows for wide frequency locking range, potentially entire VCO tuning range
- 3-stage operation with UP and DOWN outputs
- Edge-triggered results in duty cycle insensitivity





PFD Transfer Characteristic

 


- Constant slope and polarity asymmetry about zero phase allows for wide frequency range operation

PFD Deadzone

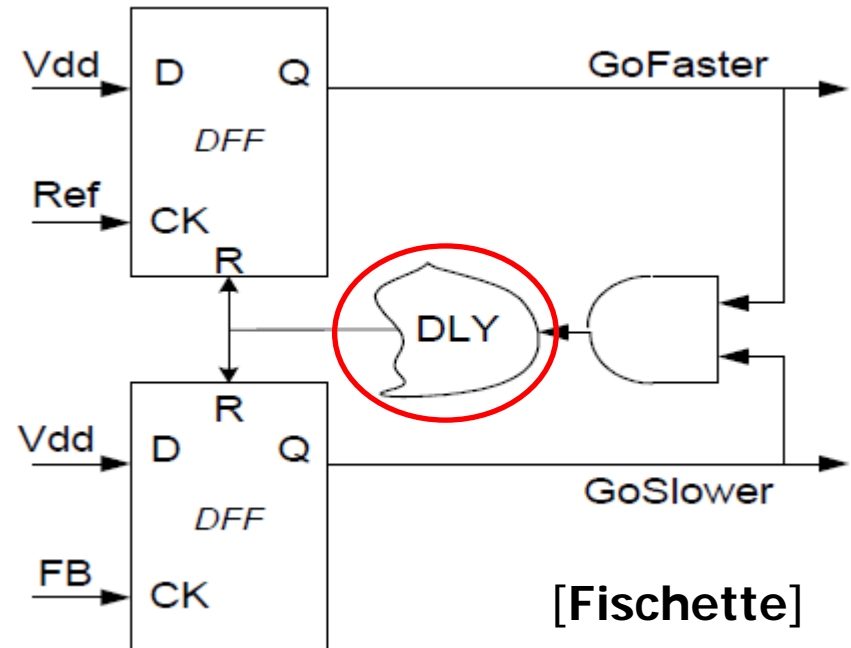 - If phase error is small, then short output pulses are produced by PFD
- Cannot effectively propagate these pulses to switch charge pump
- Results in phase detector “dead zone” which causes low loop gain and increased jitter
- Solution is to add delay in PFD reset path to force a minimum UP and DOWN pulse length



PFD Operation


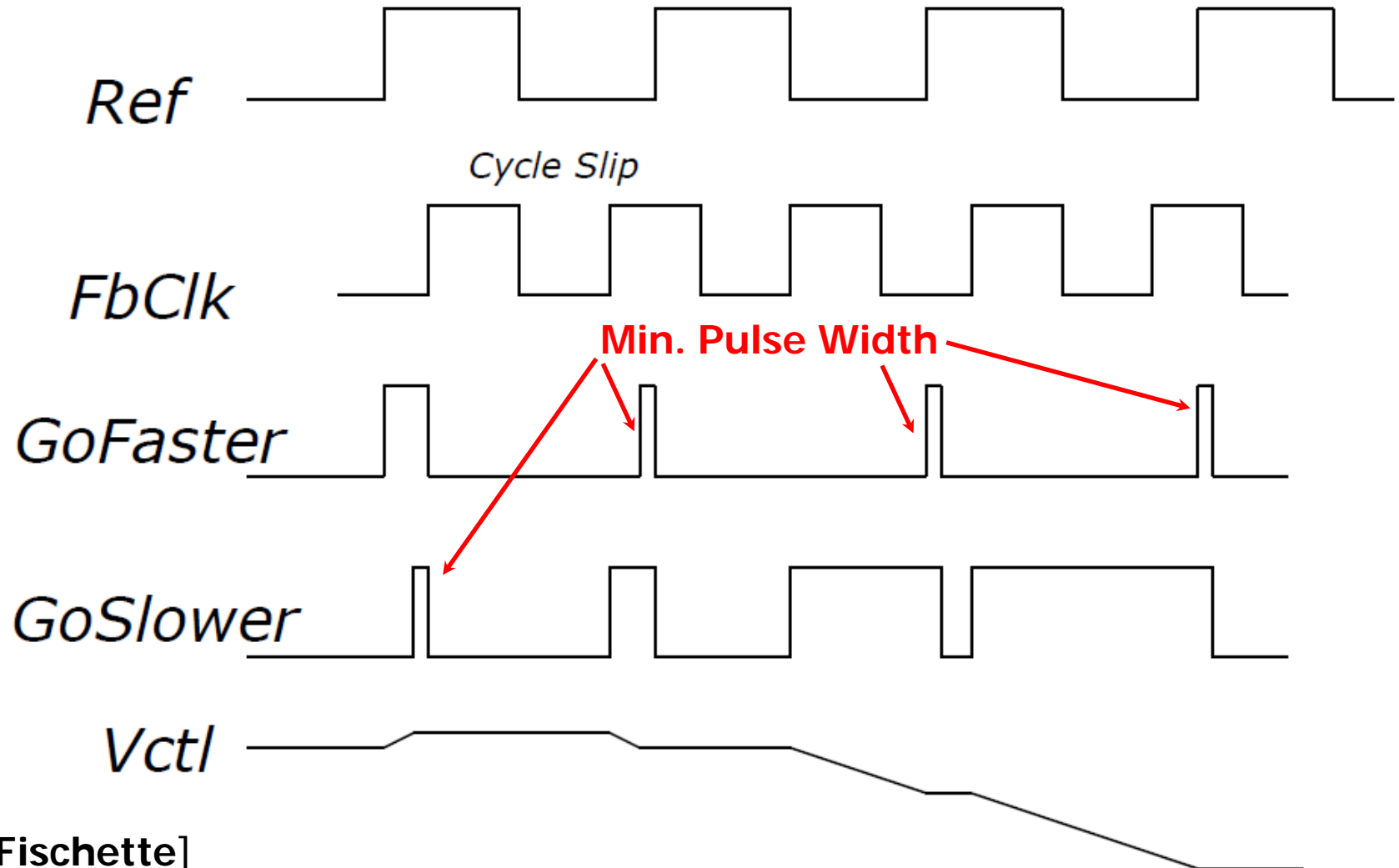


[Fischette]

PFD Properties

- The nominal lock point with a PFD is 0°
- The PFD is not sensitive to input duty cycle
- The PFD outputs "UP" and "DN" are not complementary and stay high until reset by the other, allowing for efficient frequency detection
- Near lock, the propagation of narrow pulses to switch the charge pump can cause a phase detector "dead zone"
 - To prevent this, extra delay is generally inserted in the PFD reset path

Detailed Optimized PFD Schematic

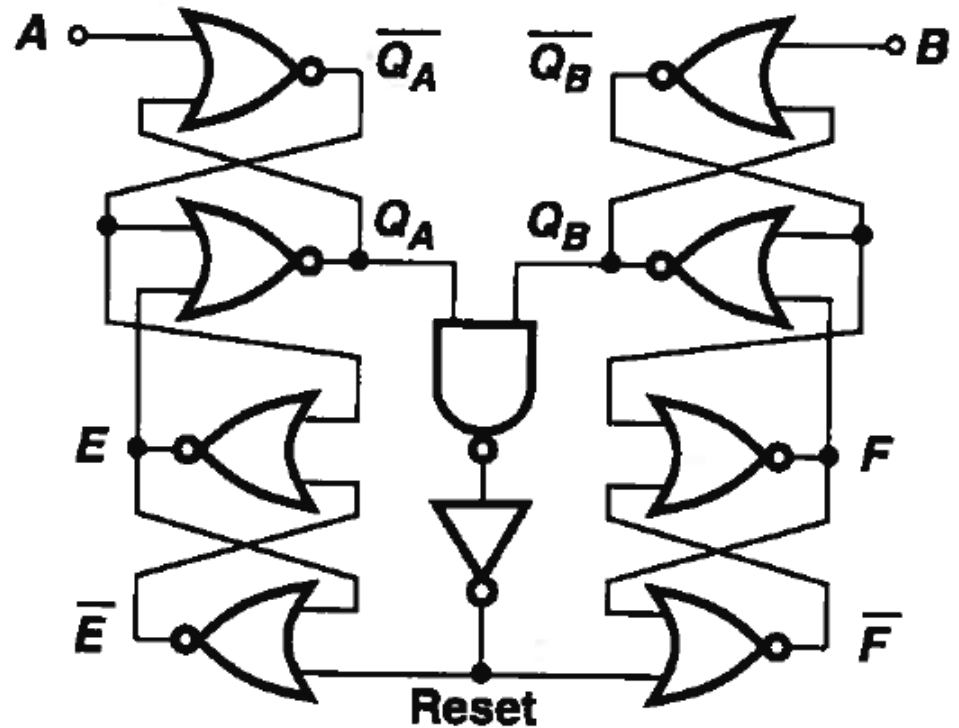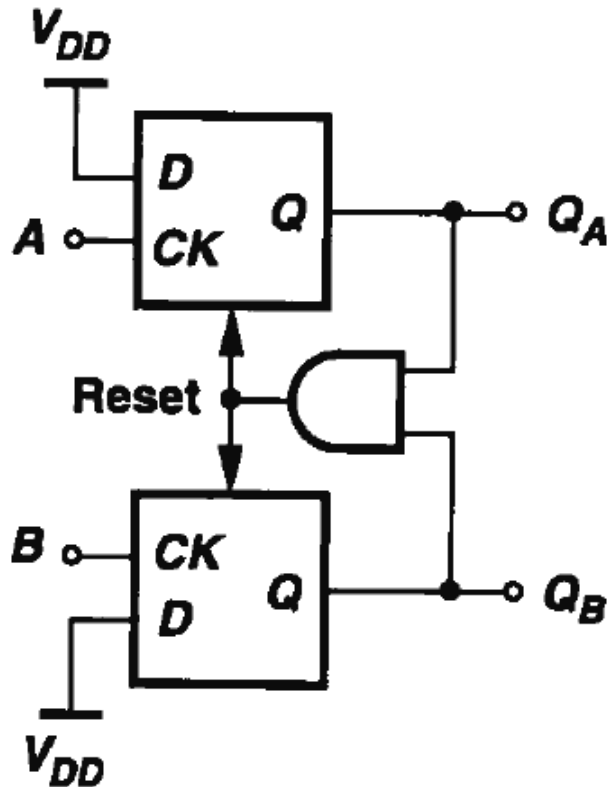

- Because the flip-flop data input is always "1", the logic can be optimized for higher speed operation

Next Time

- Charge Pump Circuits