

# ECEN620: Network Theory Broadband Circuit Design Fall 2014

---

## Lecture 12: Divider Circuits



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University


# Announcements & Agenda

---


- Divider Basics
- Dynamic CMOS Divider
- CML Divider
- Divider Circuit Style Partitioning
- Asynchronous vs Synchronous Dividers
- Dual-Modulus Prescalers
- Injection-Locked Dividers
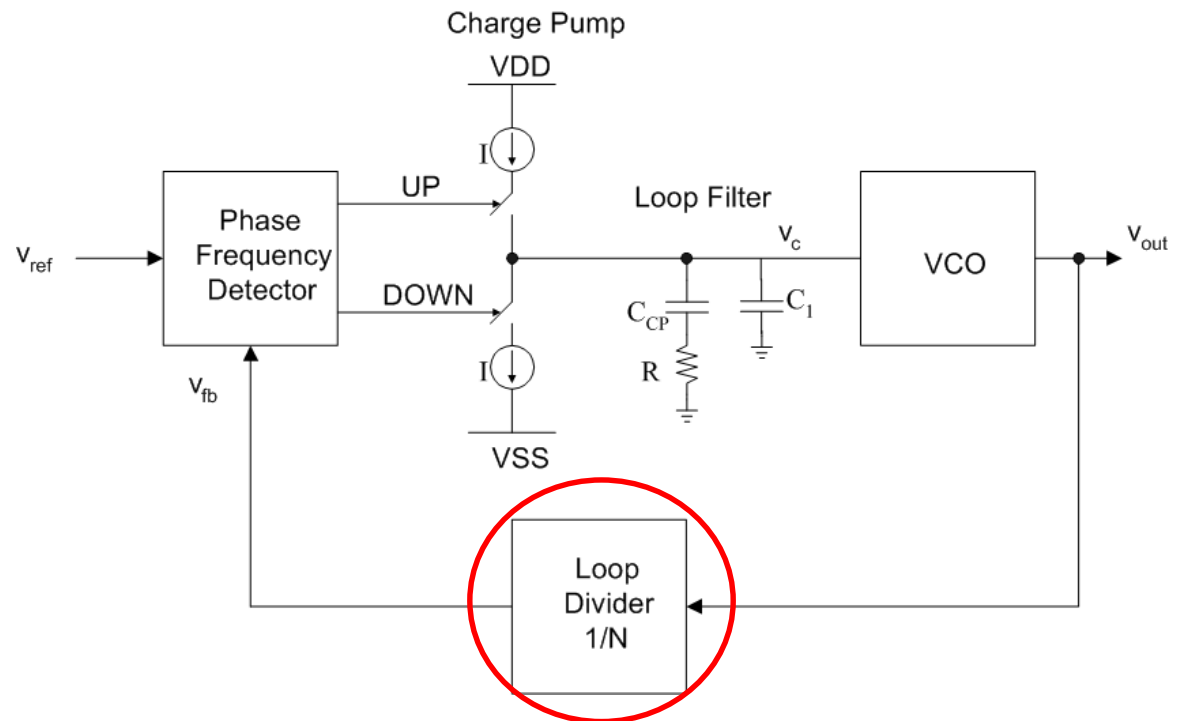
# Charge-Pump PLL Circuits

- Phase Detector
- Charge-Pump
- Loop Filter
- VCO
- Divider



# Loop Divider


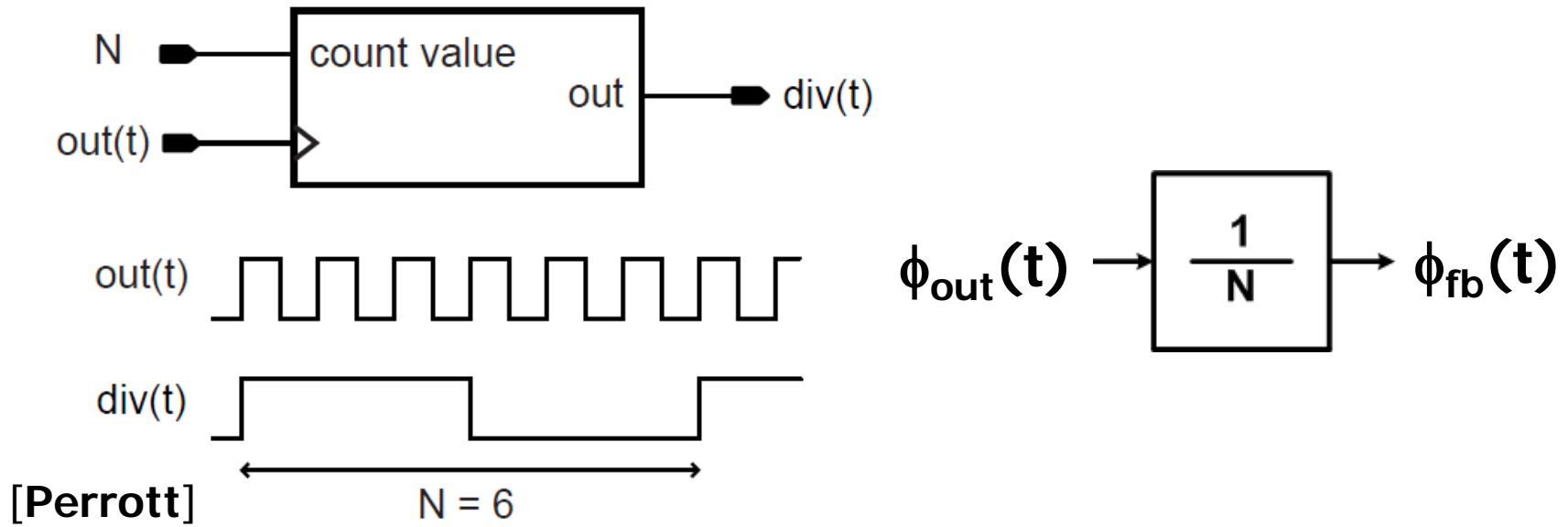


- Time-domain model


$$\omega_{fb}(t) = \frac{1}{N} \omega_{out}(t)$$

$$\phi_{fb}(t) = \int \frac{1}{N} \omega_{out}(t) dt = \frac{1}{N} \phi_{out}(t)$$

# Basic Divide-by-2

 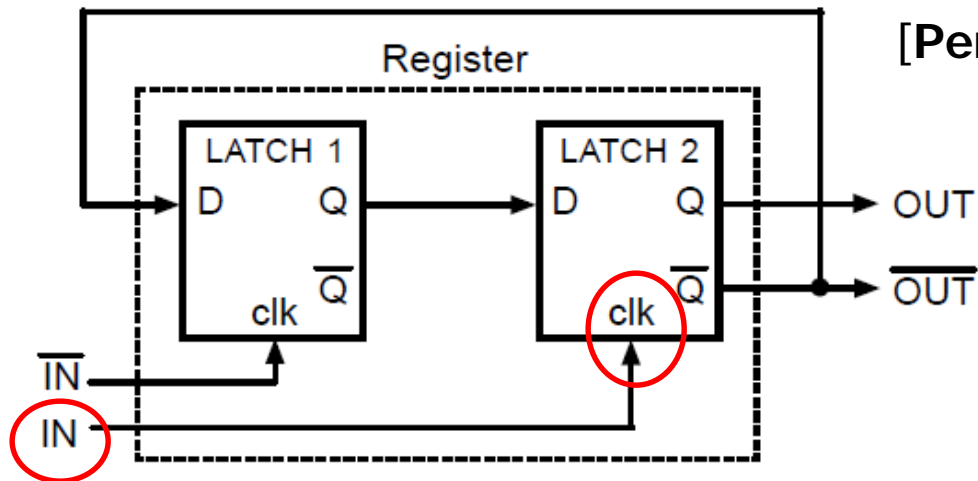

 
- Divide-by-2 can be realized by a flip-flop in "negative feedback"
- Divider should operate correctly up to the maximum output clock frequency of interest **PLUS** some margin



[Fischette]

# Divide-by-2 with TSPC FF


## True Single Phase Clock Flip-Flop

 


- Advantages
  - Reasonably fast, compact size, and no static power
  - Requires only one phase of the clock
- Disadvantages
  - Signal needs to propagate through three gates per input cycle
  - Need full swing CMOS inputs
  - Dynamic flip-flop can fail at low frequency (test mode) due to leakage, as various nodes are floating during different CLK phases & output states
    - Ex: Q\_bar is floating during when CLK is low
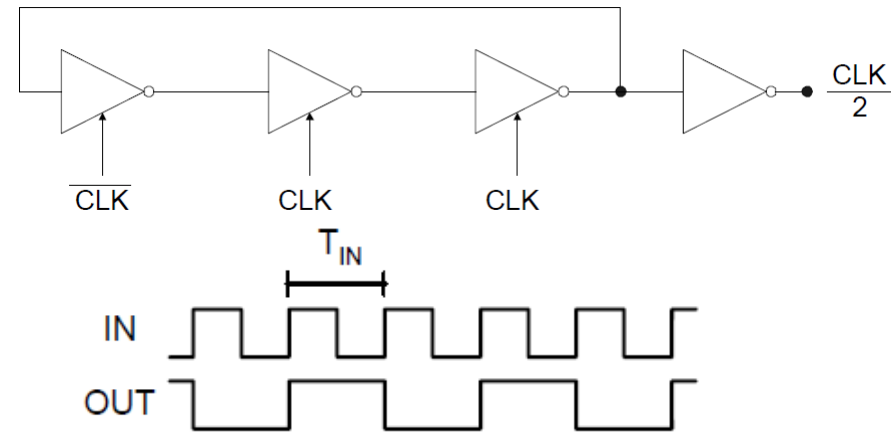
## Divider Equivalent Circuit

Note: output inverter not in left schematic




# Divide-by-2 with CML FF

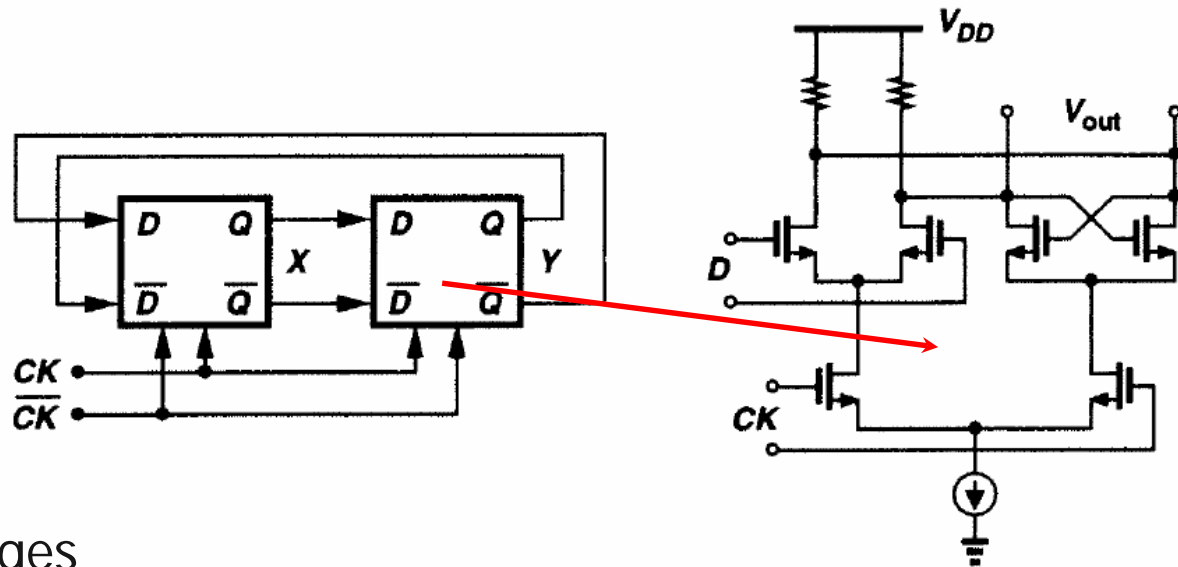


[Razavi]

- Advantages
  - Signal only propagates through two CML gates per input cycle
  - Accepts CML input levels
- Disadvantages
  - Larger size and dissipates static power
  - Requires differential input
  - Need tail current biasing
- Additional speedup (>50%) can be achieved with shunt peaking inductors

# CML Latch

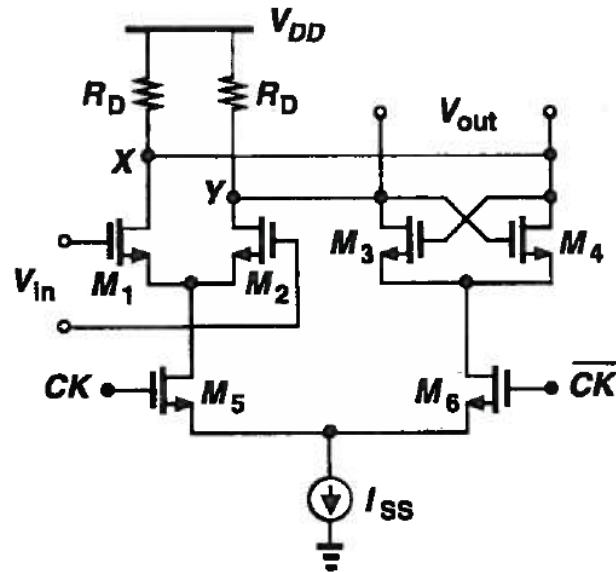


## Low-Frequency Operation

 


- When the clock is high (M5 on), the input pair (M1 & M2) tracks (linearly amplifies) the input
- When the clock is low (M6 on), the regenerative pair (M3 & M4) latches (with positive feedback) the state



# CML Latch

 


## High-Frequency Operation

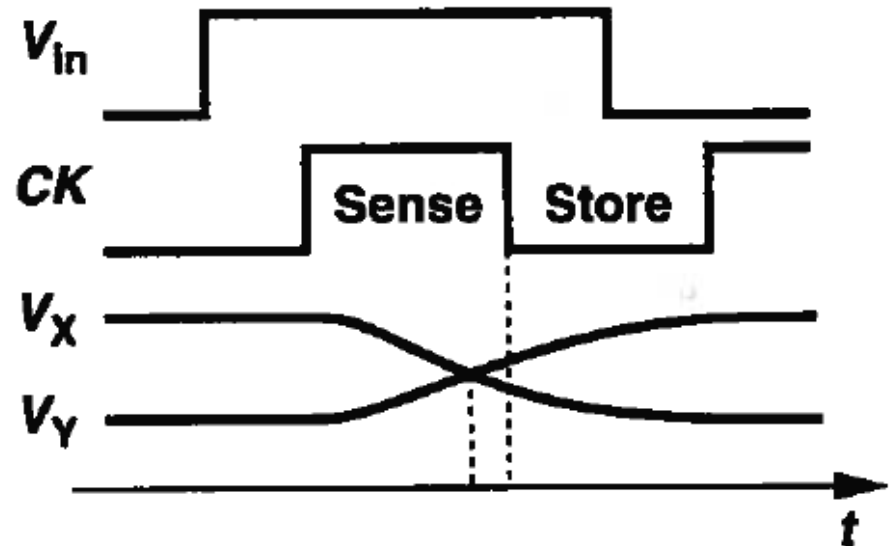



- When the clock is high (M5 on), the input pair (M1 & M2) tracks (linearly amplifies) the input
- When the clock is low (M6 on), the regenerative pair (M3 & M4) latches (with positive feedback) the state
- This regenerative pair continues to provide gain in the store mode, allowing for short cycle operation
- The minimum cross-coupled pair gain to hold the state is  $g_{m3,4}R_D > 1$
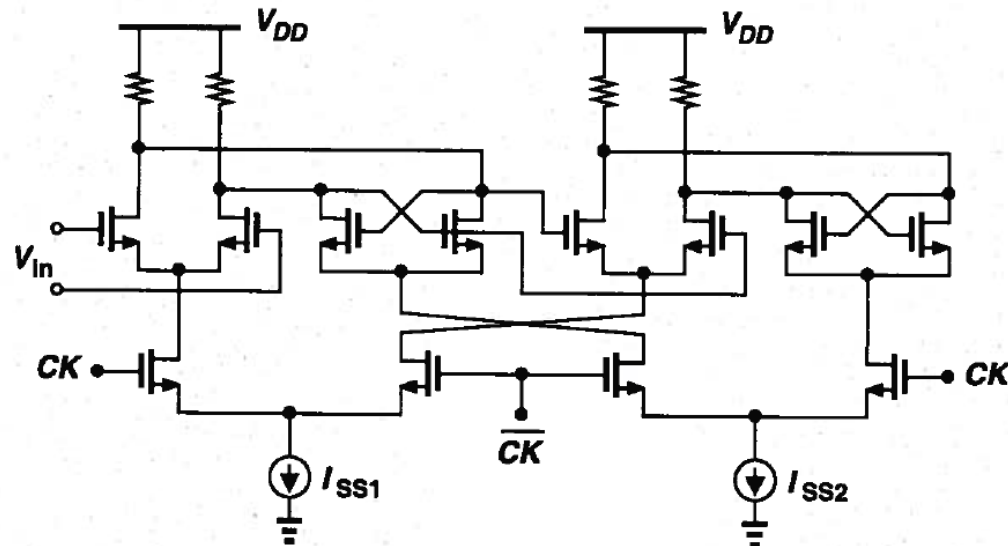
# Optimized CML FF for High-Speed Dividers





- The cross-coupled pair gate and drain capacitances slow down the latch/flip-flop
- If the flip-flop is switching at high-speed, the regenerative pair gain can actually have a loop gain less than unity due to the short hold state
- One way to achieve this is by using a different current in the track state ( $I_{SS1}$ ) and the hold state ( $I_{SS2}$ ), allowing for smaller regeneration transistors when  $I_{SS2} < I_{SS1}$

# CML Latch Swing Control

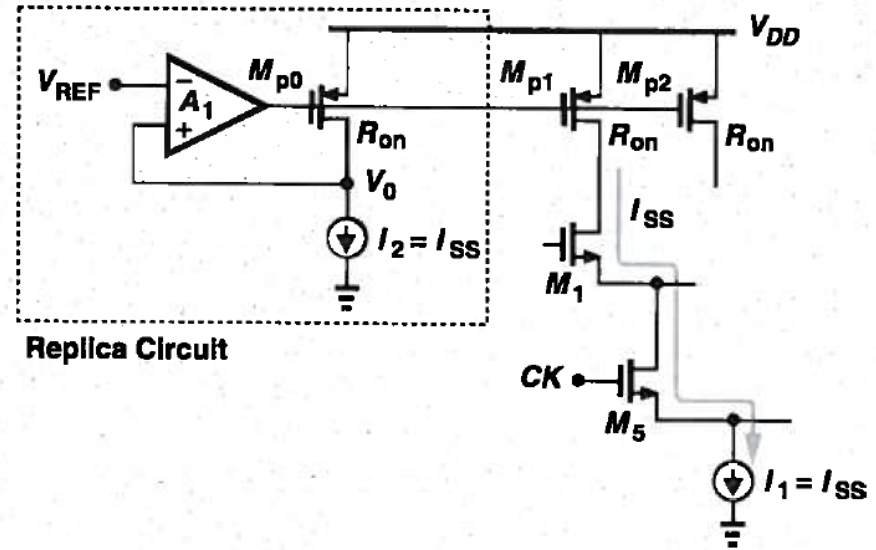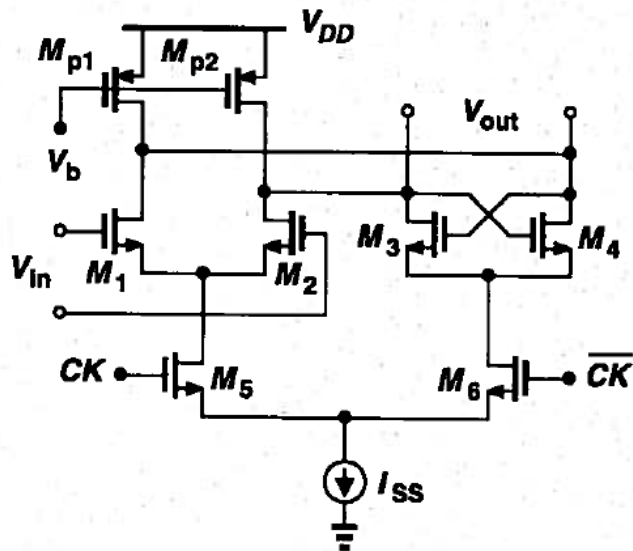


- If suitable resistors are not available in a certain process, the PMOS triode-region loads can be used
- Due to PVT variations, feedback control is generally required to maintain the desired CML logic swing level
- A replica circuit produces the required PMOS gate bias to insure the desired CML logic swing for a given  $I_{SS}$
- Note, triode PMOS loads will generally have more parasitic capacitance than linear resistors, resulting in a slower circuit

# CML Latch with PMOS Diode Loads

 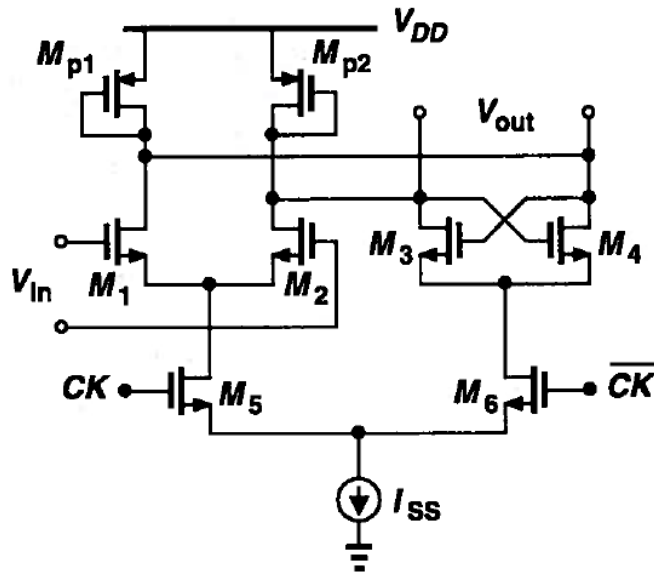



- PMOS diode loads may allow for simpler biasing over PVT variations
- One issue with this is the large headroom ( $|V_{TP}| + V_{OD}$ ) required to turn-on the PMOS diode
  - NMOS source followers can allow for similar headroom as with triode loads

# CML Latch with PMOS Diode Loads

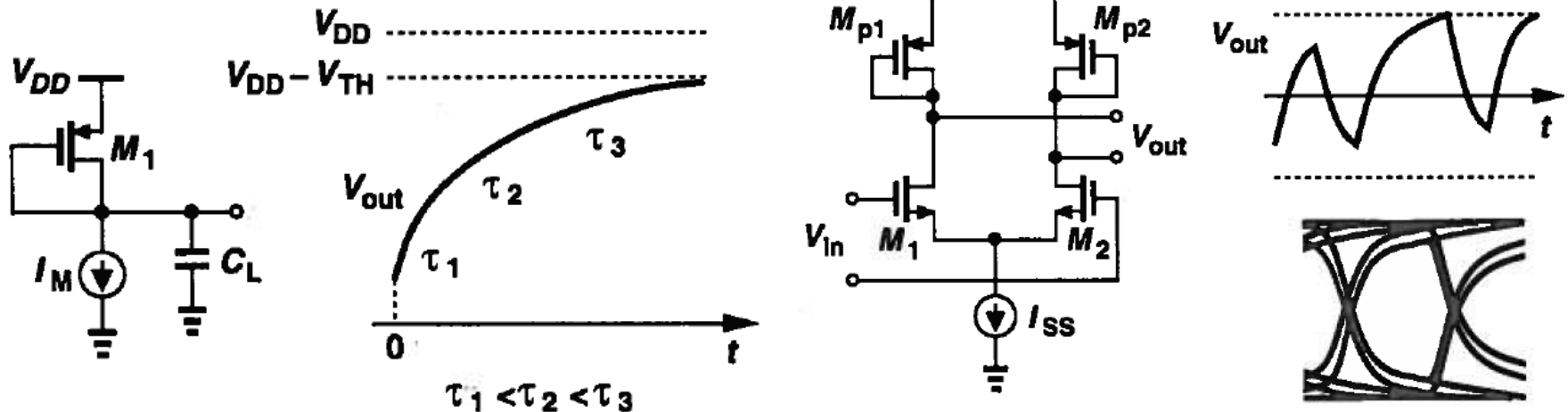

- PMOS diode loads may allow for simpler biasing over PVT variations
- One issue with this is the large headroom ( $|V_{TP}| + V_{OD}$ ) required to turn-on the PMOS diode
  - NMOS source followers can allow for similar headroom as with triode loads
- Another issue stems from the highly non-linear effective resistance which can introduce inter-symbol interference for random data
  - Note, this is not an issue for periodic switching divider applications


# CML Divider Clock Swing vs Frequency

 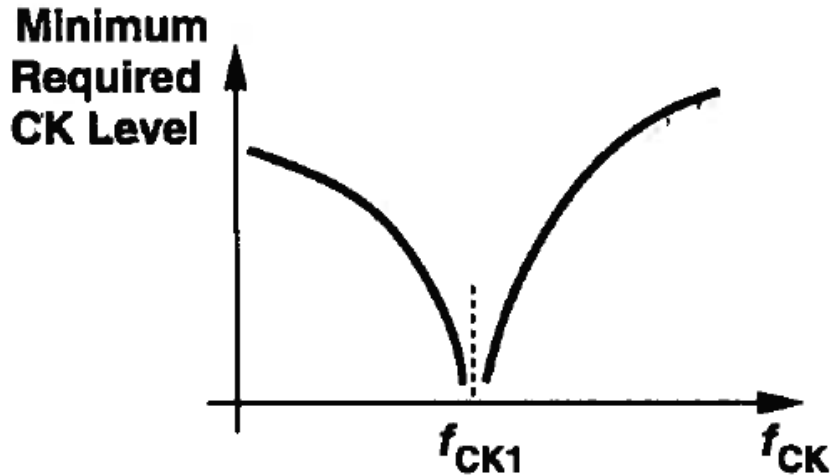

- Interestingly, the divider minimum required clock swing can actually decrease with frequency
- This is due to the feedback configuration of the divider yielding an effective ring oscillator topology that will naturally oscillate at certain frequency
- Near this frequency, the input clock amplitude can be very low
- For frequencies above this natural oscillation frequency, the minimum clock input amplitude increases

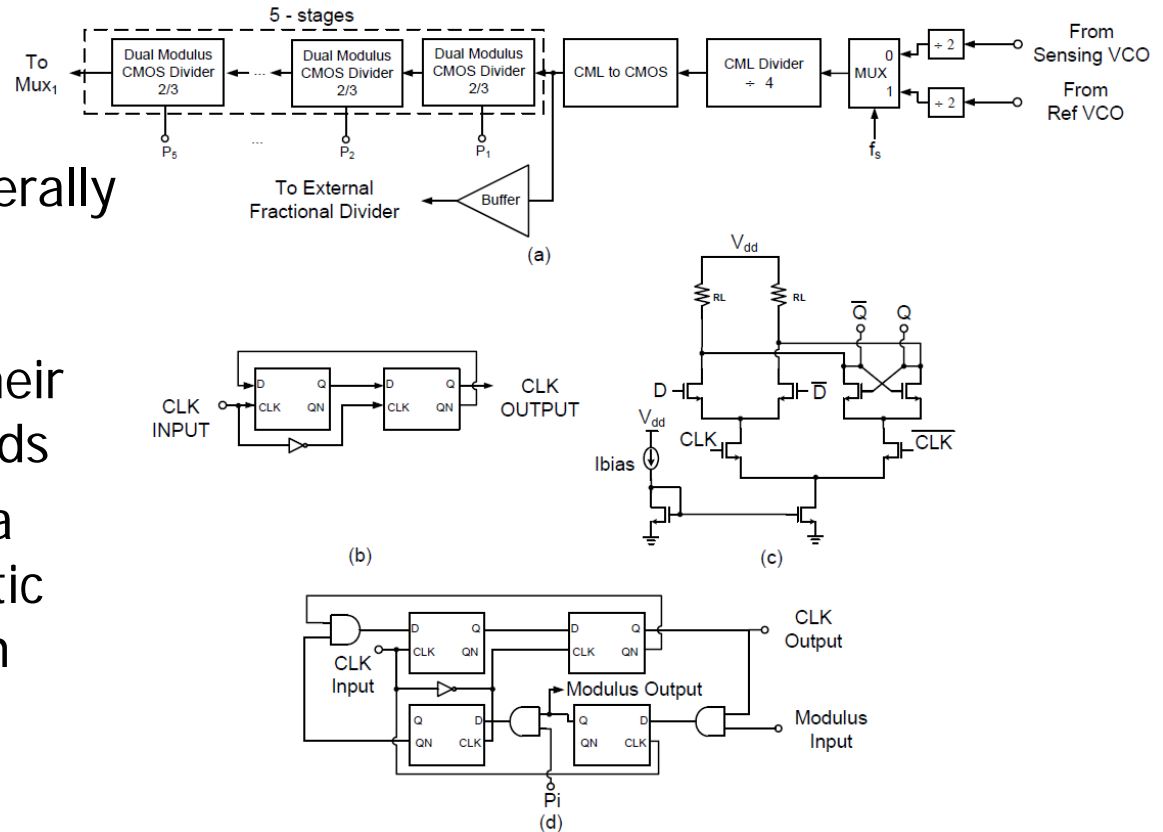
# Divider Circuit Style Partitioning

- While CML dividers generally operate at the highest speed, the static power consumption reduces their efficiency at lower speeds
- For large divide ratios, a mixture of CML and static CMOS dividers are often used
- The first fastest fixed dividers (prescalers) are CML, while the following lower frequency dividers are static CMOS




# Binary Dividers: Asynchronous vs Synchronous

## Asynchronous Divider

 

- Advantages
  - Each stage runs at lower frequency, resulting in reduced power
  - Reduced high frequency clock loading
- Disadvantage
  - Jitter accumulation

## Synchronous Divider

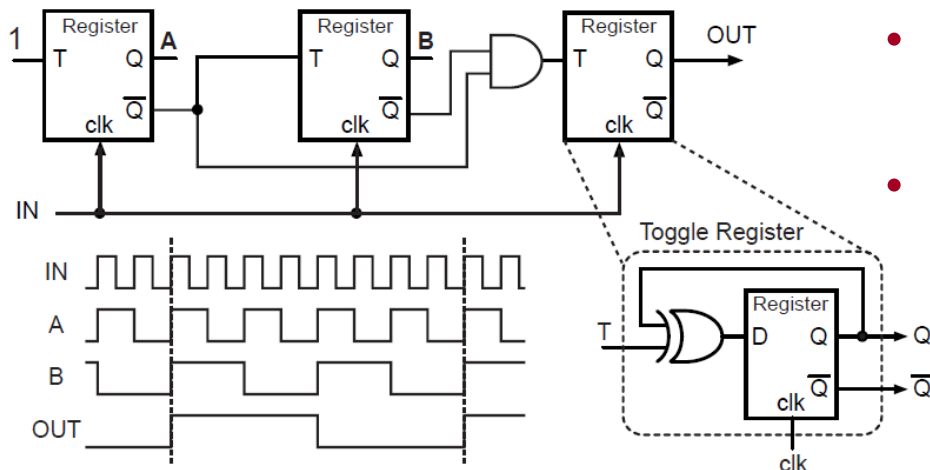


- Advantage
  - Reduced jitter
- Disadvantage
  - All flip-flops work at maximum frequency, resulting in high power
  - Large loading on high frequency clock




# Jitter in Asynchronous vs Synchronous Dividers

## Asynchronous

 

- Jitter accumulates with the clock-to-Q delays through the divider
- Extra divider delay can also degrade PLL phase margin


## Synchronous

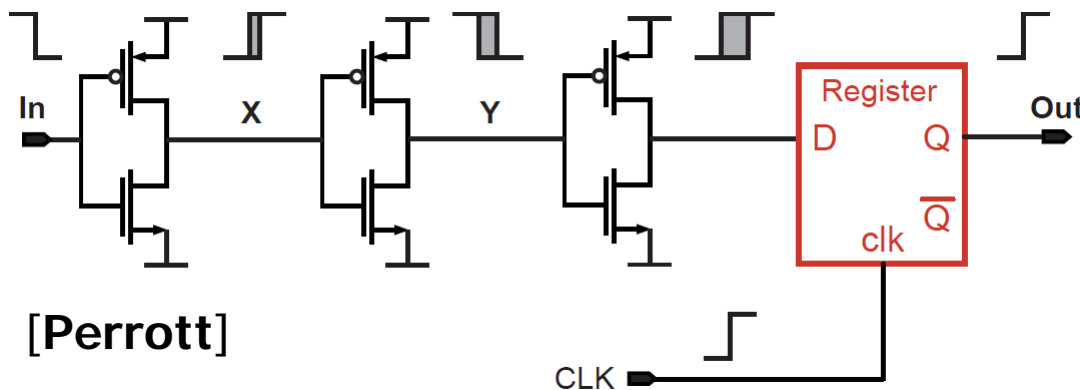

[Perrott]

- Divider output is "sampled" with high frequency clock
- Jitter on divider clock is similar to VCO output
- Minimal divider delay


# Dual Modulus Prescalers

 

MC=0  $\rightarrow$   $\div 3$   
 MC=1  $\rightarrow$   $\div 2$

$\div 15/16$

[Razavi]

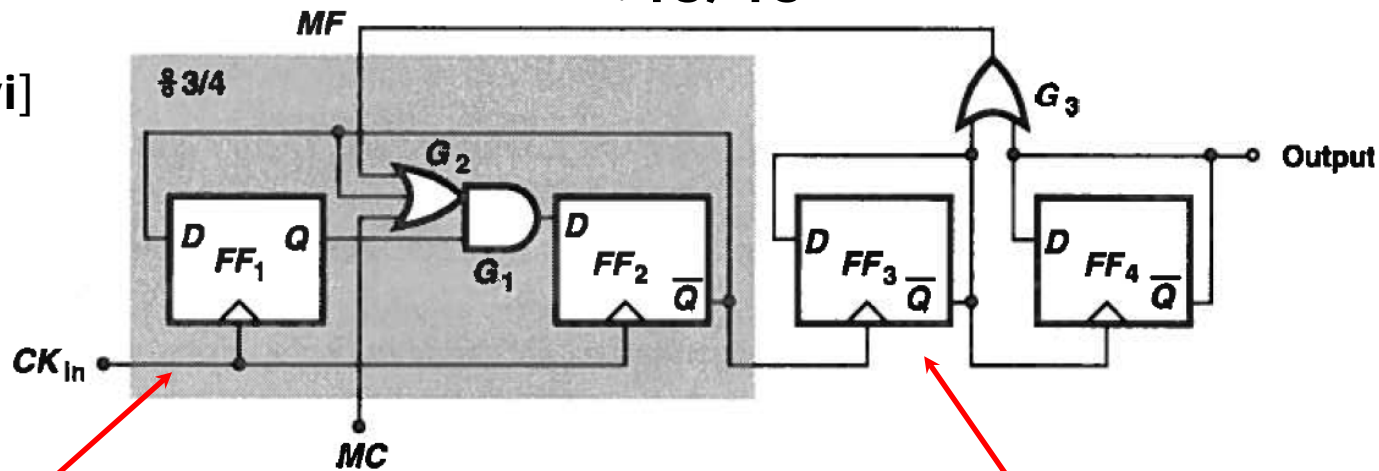

**Synchronous  $\div 3/4$**


**Asynchronous  $\div 4$**

- For /15, first prescaler circuit divides by 3 once and 4 three times during the 15 cycles

# ÷128/129 Dual-Modulus Prescaler

Synchronous ÷4/5

[Craninckx JSSC 1996]

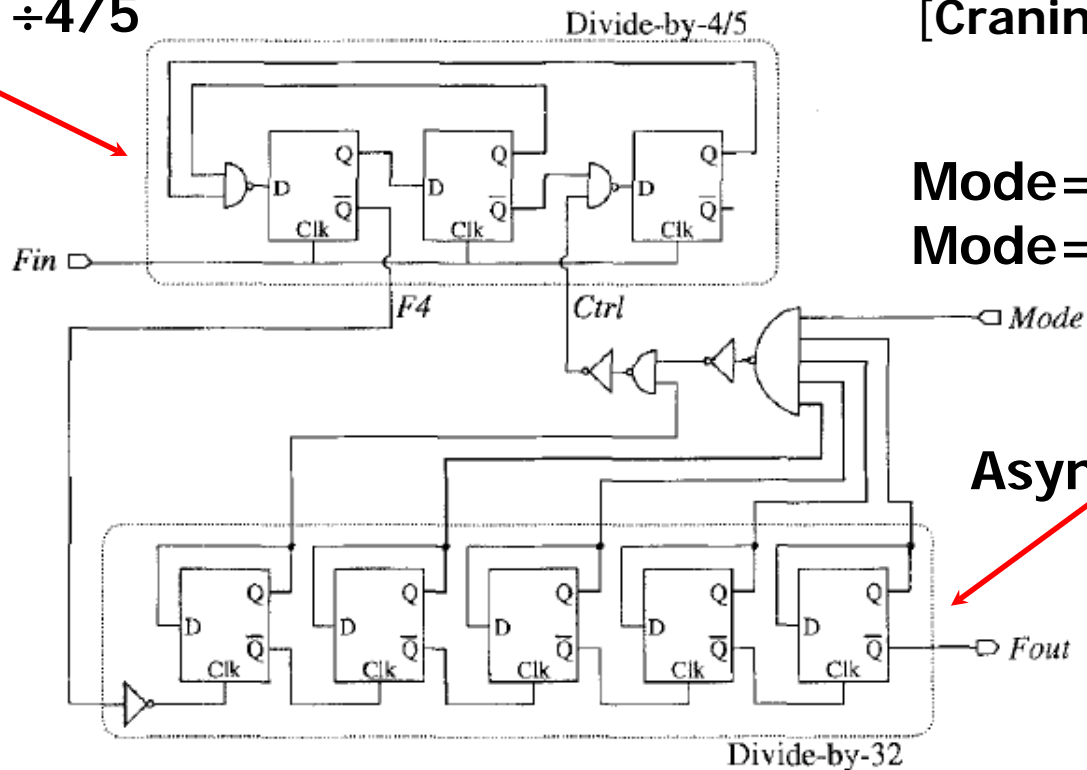


Mode=0 → ÷128  
Mode=1 → ÷129

Asynchronous ÷32

- For /129, first prescaler circuit divides by 5 once and 4 thirty-one times during the 129 cycles
- The synchronous ÷4/5 block with the extra NAND logic limits the maximum operating frequency and has 3 flip-flops operating at the maximum speed

# Phase-Switching Dual-Modulus Prescaler


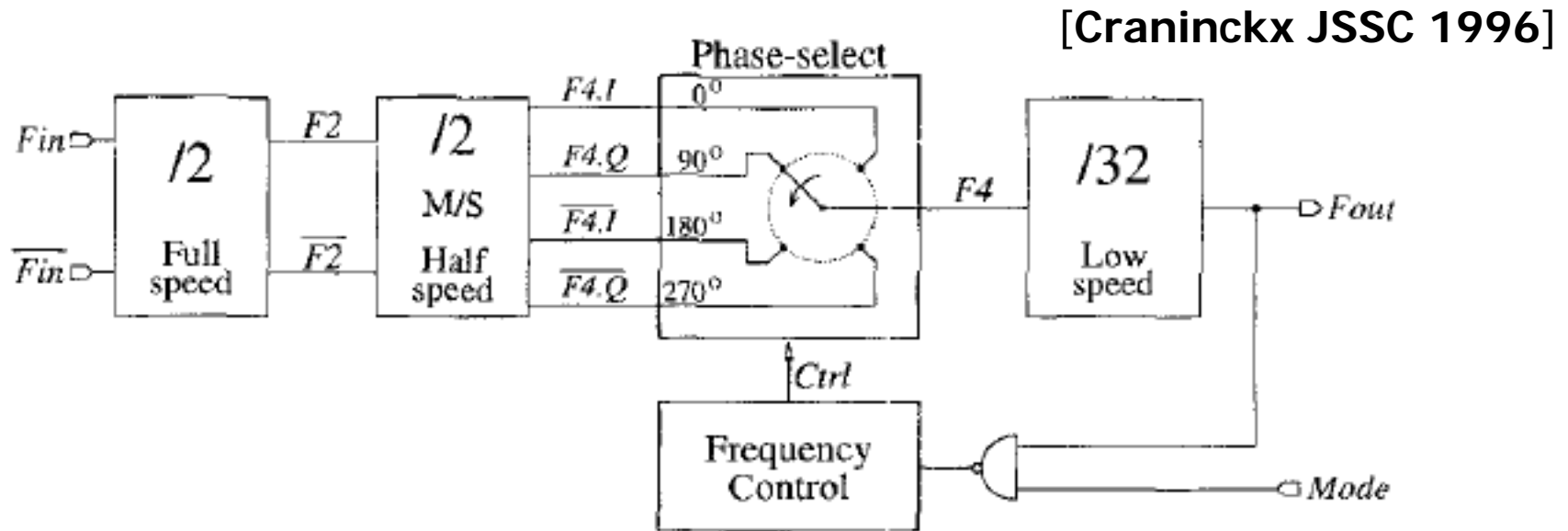


- In order to  $\div 129$ , instead of adding an extra high-frequency cycle in a  $\div 4/5$  block, simply delay the phase of the  $\div 4$  signal by  $90^\circ$
- Allows for a fully-asynchronous design with only 1 flip-flop operating at the maximum speed
- Needs quadrature phase outputs at the  $\div 4$  outputs

# Adding an Extra Cycle with a 90° Shift

- A differential Master/Slave flip-flop provides quadrature signals at the latch outputs
- Every 128 cycles, delay the  $\div 4$  signal by 90° to yield a divide by 129 output

[Craninckx JSSC 1996]

 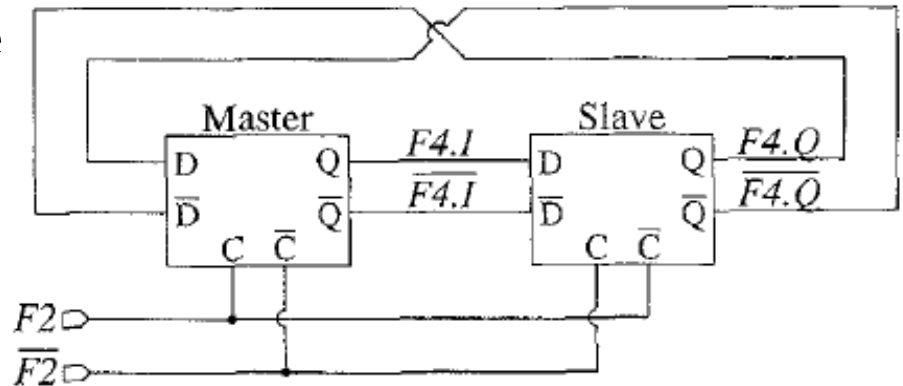

# Watch Out For Glitches!

- There is the potential for glitches at the output of the phase selector during low-frequency operation, causing the divider to fail
- This is solved by insuring a minimum rise time (slowing down C0), such that the block selects a signal when it has a sufficient high value


 




Fig. 7. Phase-selection circuitry.

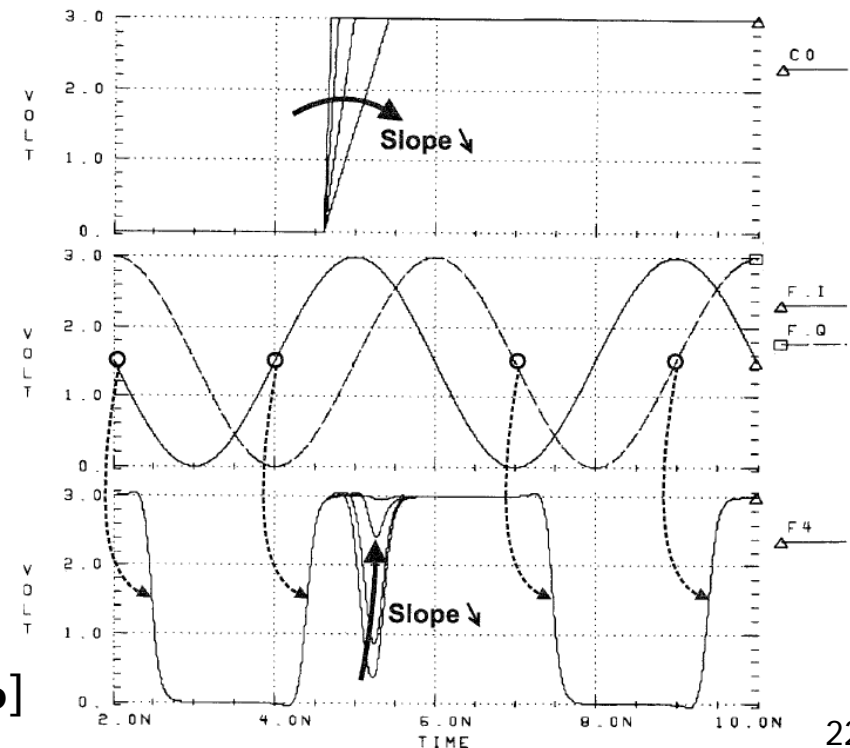

[Craninckx JSSC 1996]


# ÷128/129 Phase-Switching Dual-Modulus Prescaler

[Craninckx JSSC 1996]

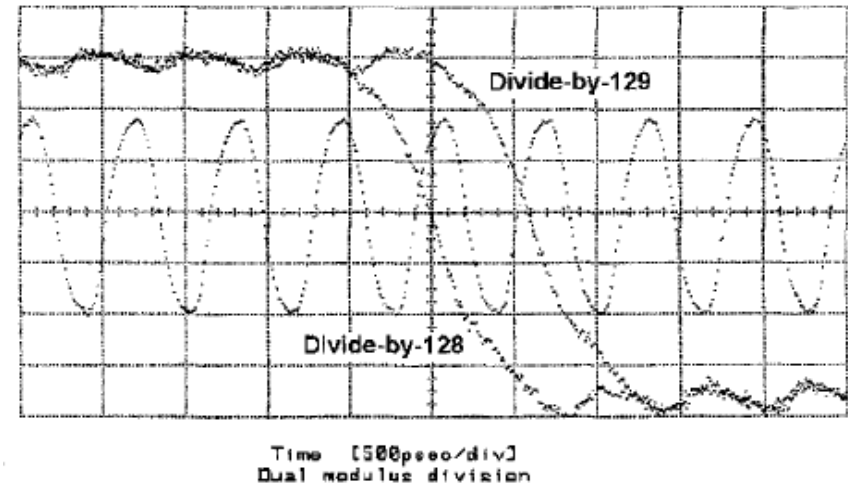 


- In a 0.7 $\mu$ m CMOS process achieved
  - 2.65GHz operation with 5V power supply
  - 1.75GHz operation with 3V power supply
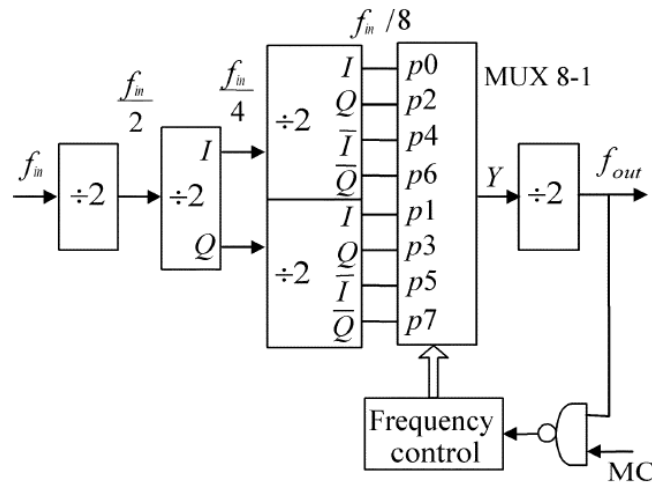
# Improved Glitch Robustness Using $\div 8$ Signals



 - Using  $\div 8$  signals and switching  $45^\circ$  allows for improved glitch robustness
- Requires two parallel  $\div 2$  blocks
- Careful! These two  $\div 2$  blocks have two possible phase relationships
- Need to detect this relationship to determine the appropriate phase switching order




[Shu JSSC 2003]




# Injection-Locked Frequency Dividers

## LC-oscillator type (/2)

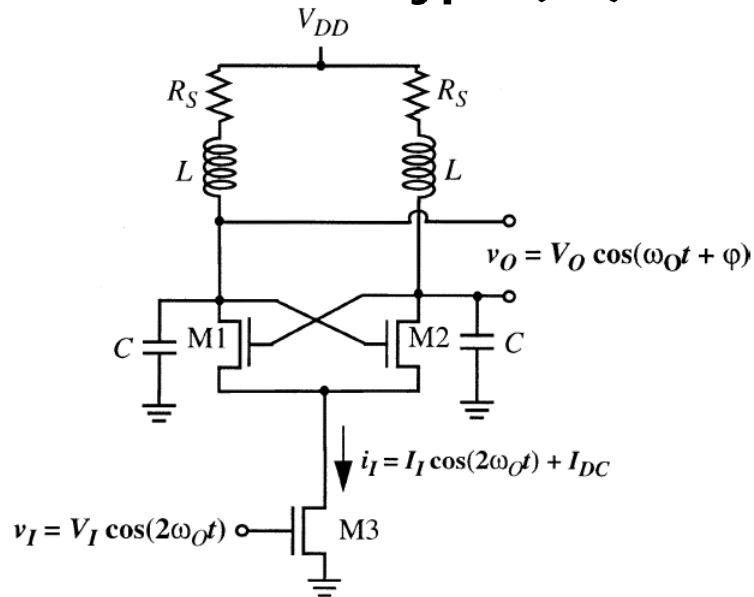

## Ring-oscillator type (/3)

 

[Verma JSSC 2003, Rategh JSSC 1999]

[Lo CICC 2009]

- Superharmonic injection-locked oscillators (ILOs) can realize frequency dividers
- Faster and lower power than flip-flop based dividers
- Injection locking range can be limited

# LC INFDs

## □ Advantage:

- Better noise performance (LC filtering)
- Low power consumption
- Very high operation frequency ( $\sim f_{\max}$ )

## □ Disadvantage:

- Smaller locking range (LC limited)
- Unwanted harmonics
- Large silicon area due to L and C
- Very difficult to provide multiple phases or large divisor number in one LC oscillator stage (area penalty)
- Difficult to find an excellent source to inject signal

# Ring-Oscillator-Based ILFDs

## □ Advantage:

- **Smaller area**
- **Wide locking range**
- **Small power consumption**


## □ Disadvantage:

- **Inferior phase noise to LC ILFDs (Still decent)**
- **Worse unwanted harmonics (No LC resonant filtering)**
- **False locking**

# Complementary Injection-Locked Frequency Divider (CILFD)

- ❑ Large odd-modulus
- ❑ Only dynamic power consumption
- ❑ 100% frequency locking range
- ❑ Differential input/output
- ❑ 50% duty cycle
- ❑ Small area


$/3, 5, 7, \dots$

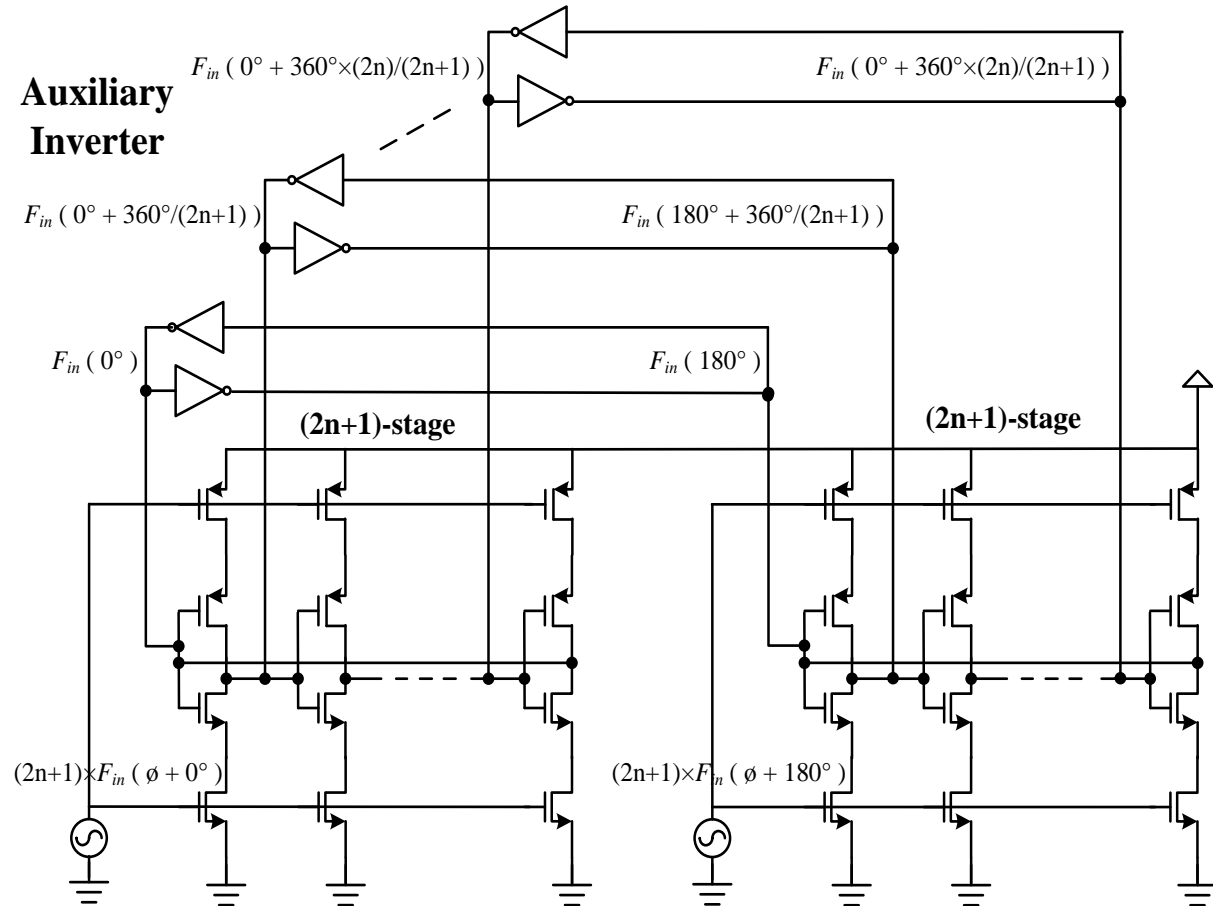


# Complementary Injection Scheme

- Complementary injection reinforces the injection strength to widen the frequency locking range.
- Only when the inverter transits state the tail transistors inject current.
- Independent tail injection to each stage avoids the interference between each stage


Injection Signal

 


Ring-oscillator output

 

Tail NMOS injection current

 


Tail PMOS injection current

 


# Locking Range (Input Sensitivity)

- Over 100% locking range (Post-layout simulation in TSMC 0.18  $\mu\text{m}$  technology)

Divided-by-3 operation

 

Divided-by-15 operation

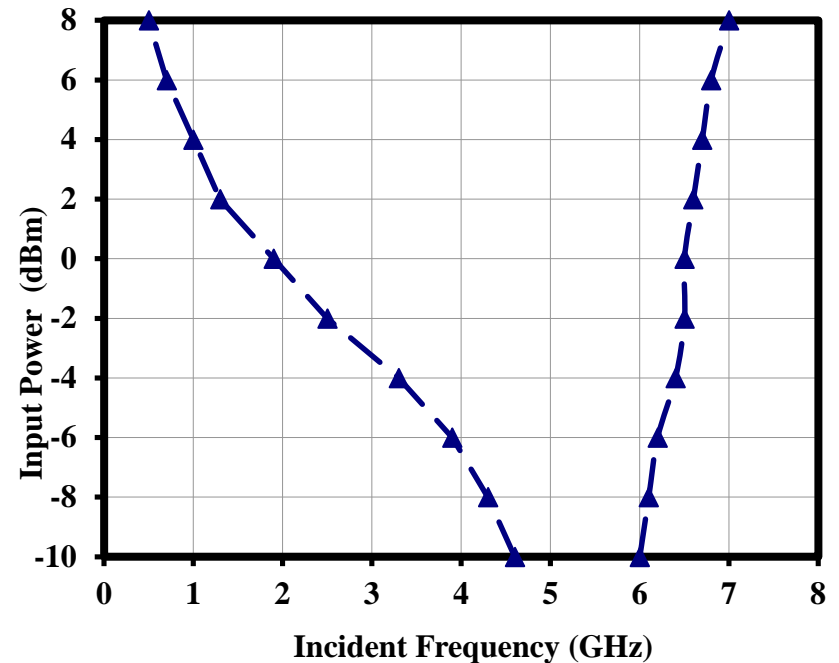

# Power Consumption and Phase Noise

## □ Power consumption:


One ring-oscillator stage:  $P_{Stage} \cong CV_{DD}^2 f_{Inj} \left( \frac{1}{2n+1} \right)$

CILFD:  $P_{Total} \cong 2CV_{DD}^2 f_{Inj}$

The power consumption is independent to the division modulus (# of ring-oscillator stage).
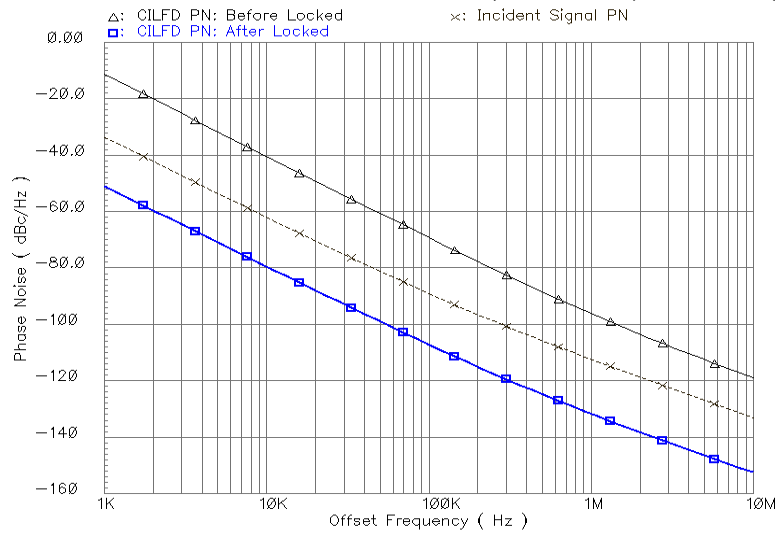
## □ Phase noise:

The phase noise of CILFD is mainly determined by the phase noise of injection signal.  $PN(CILFD) \cong PN(Incident) - 10\log(\text{Modulus No.})^2$



From top to bottom (1) free running CILFD, (2) incident signal, and (3) locked CILFD

# Next Time

---

- Frequency Synthesizer Examples