

ECEN620: Network Theory Broadband Circuit Design Fall 2014

Lecture 13: Frequency Synthesizer Examples



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

Agenda


- Frequency Synthesizer Examples
 - Design of Frequency Synthesizers for Short Range Wireless Transceivers
 - A Multi-Standard Frequency Synthesizer

Design of Frequency Synthesizers for Short Range Wireless Transceivers

Ari Y. Valero - López



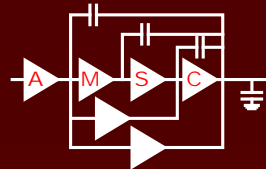Department of Electrical Engineering
Analog & Mixed-Signal Center
Texas A&M University
February 23th, 2004



Most Popular Wireless Standards

WirelessLAN 802.11

11a (5.25GHz, 54Mbps, 50m)

11b (2.45GHz, 11Mbps, 100m)

11g (2.45GHz, 24Mbps, 100m)

Short
Range
Wireless


UWB

(3.1-10.9GHz, 110Mbps, 10m)

Bluetooth

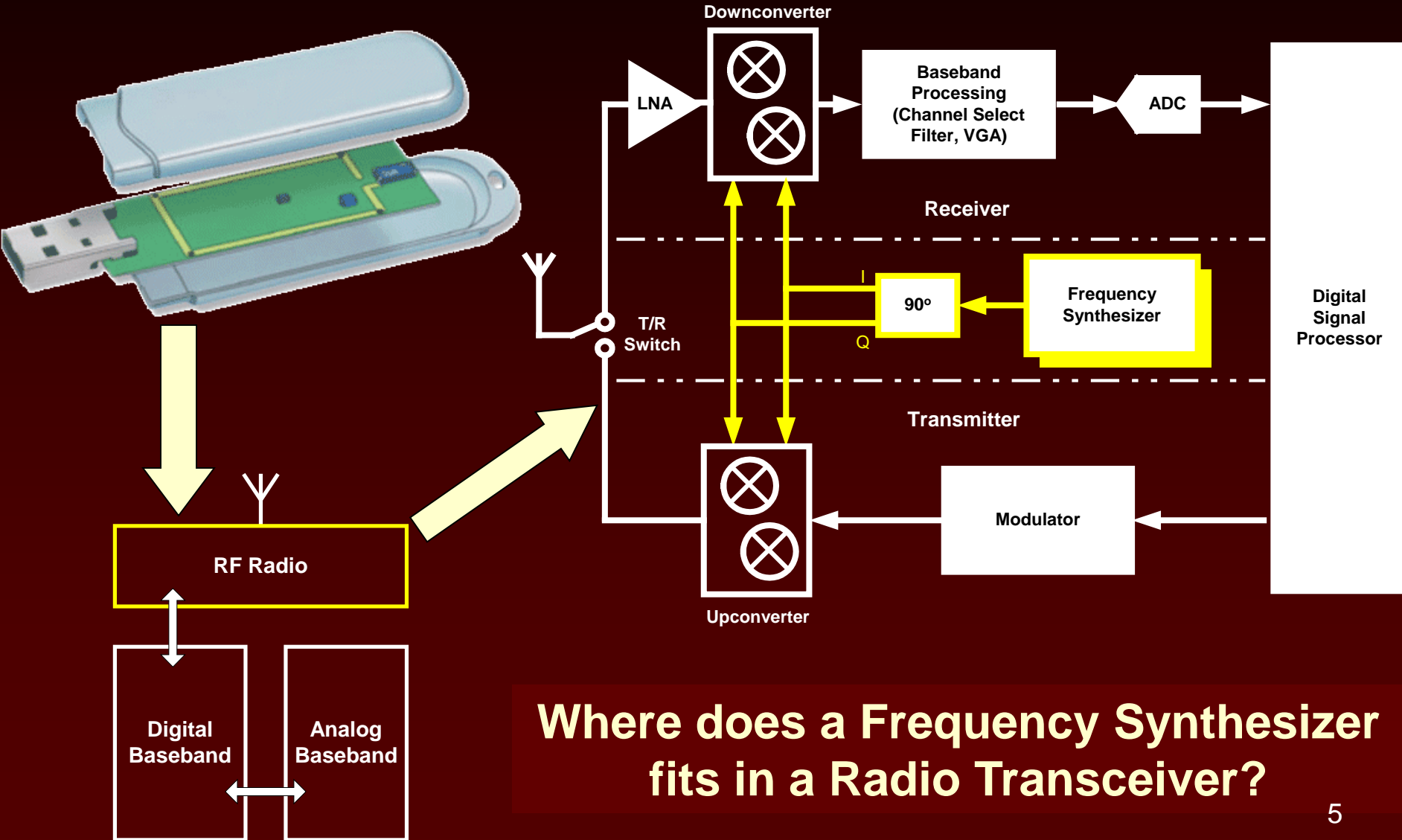
(2.45GHz, 1Mbps, 10m)

Frequency Synthesizer in a Wireless Communication System



Where does a Frequency Synthesizer fit in a Radio Transceiver?

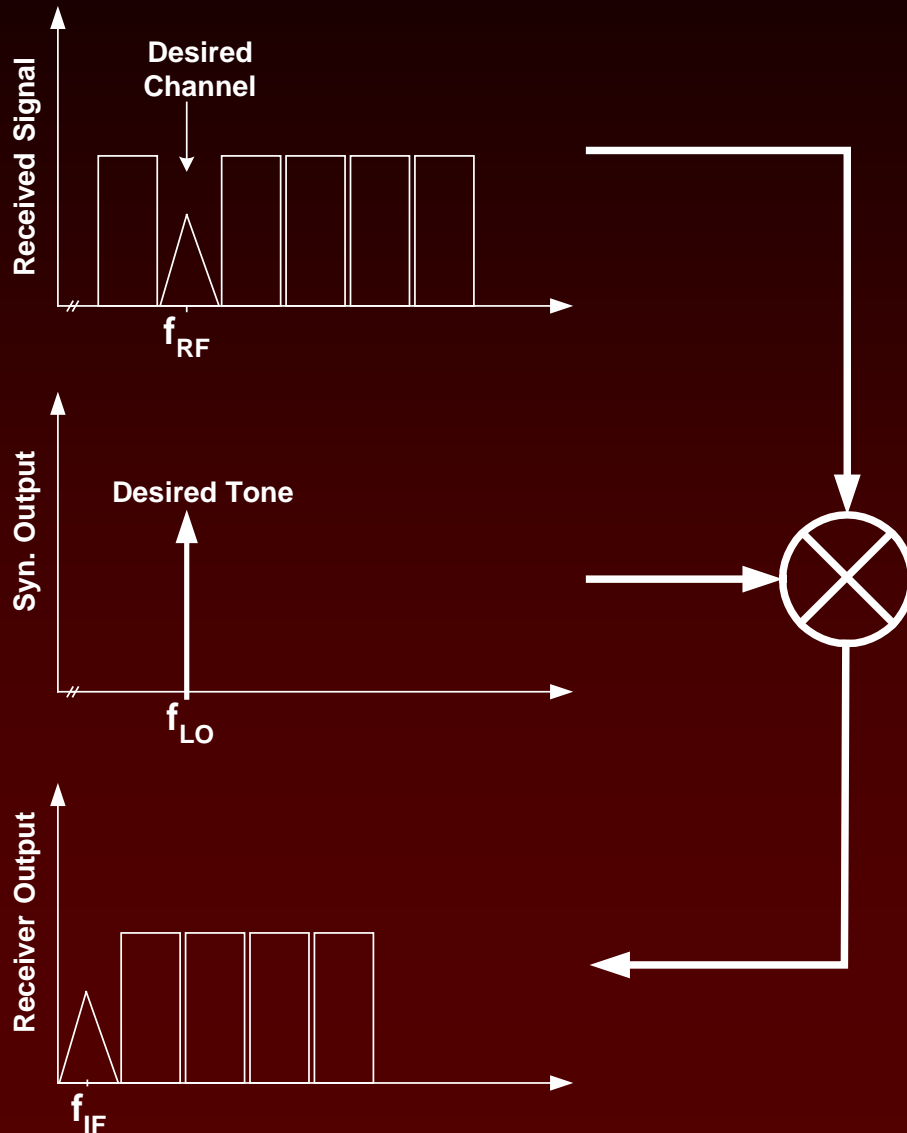Function of a Frequency Synthesizer in a Radio




The Frequency Synthesizer generates the required frequency reference for selection of a communication channel

The desired channel is downconverted to a frequency corresponding to: $f_{IF} = f_{RF} - f_{LO}$


Frequency Synthesizer Building Blocks

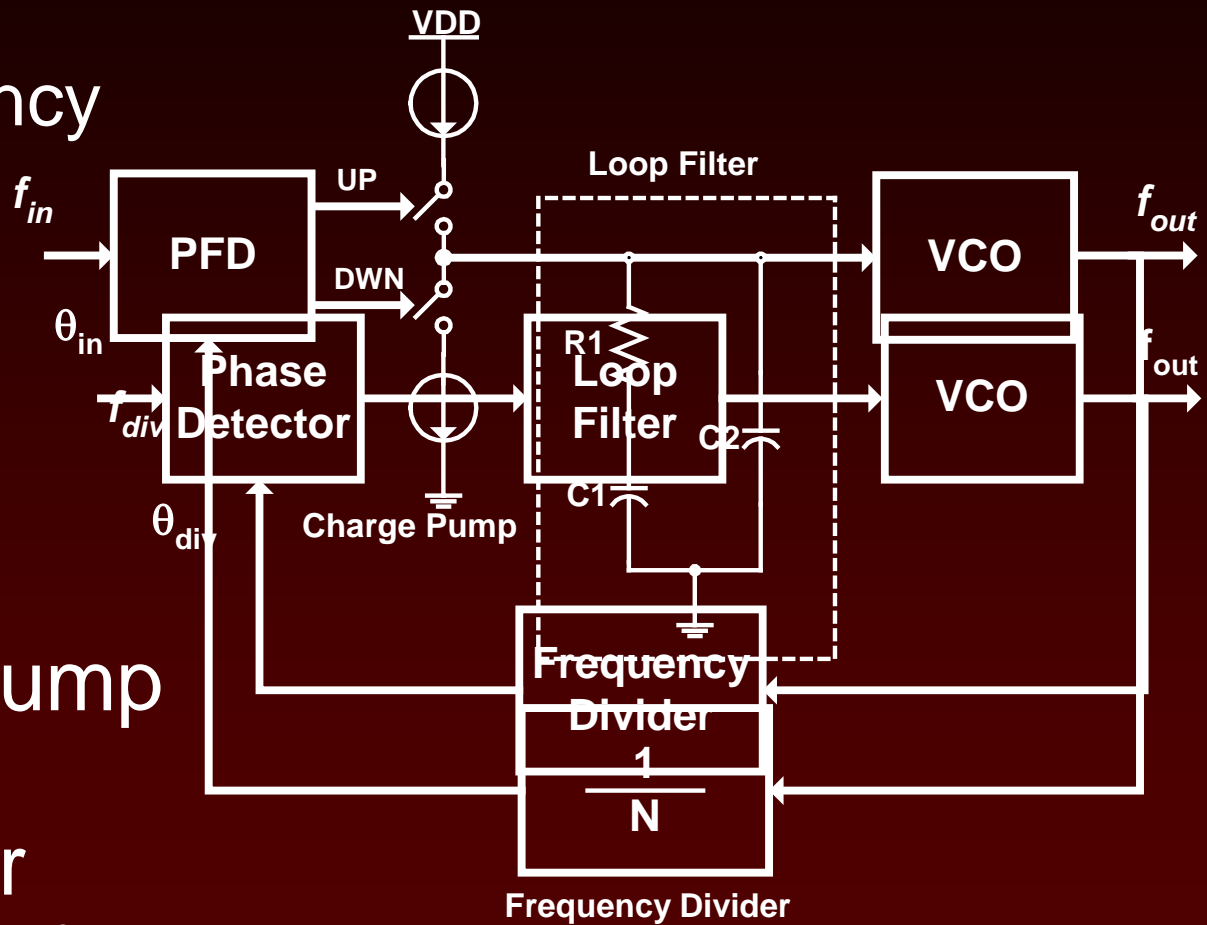- VCO and Frequency Divider operate at high frequency
- PFD, Charge Pump and LPF generate proper control voltage of VCO





$$\theta_{in} = \theta_{div} \Rightarrow f_{in} = f_{div} = f_{out}/N \quad 7$$

FS for Bluetooth Receiver

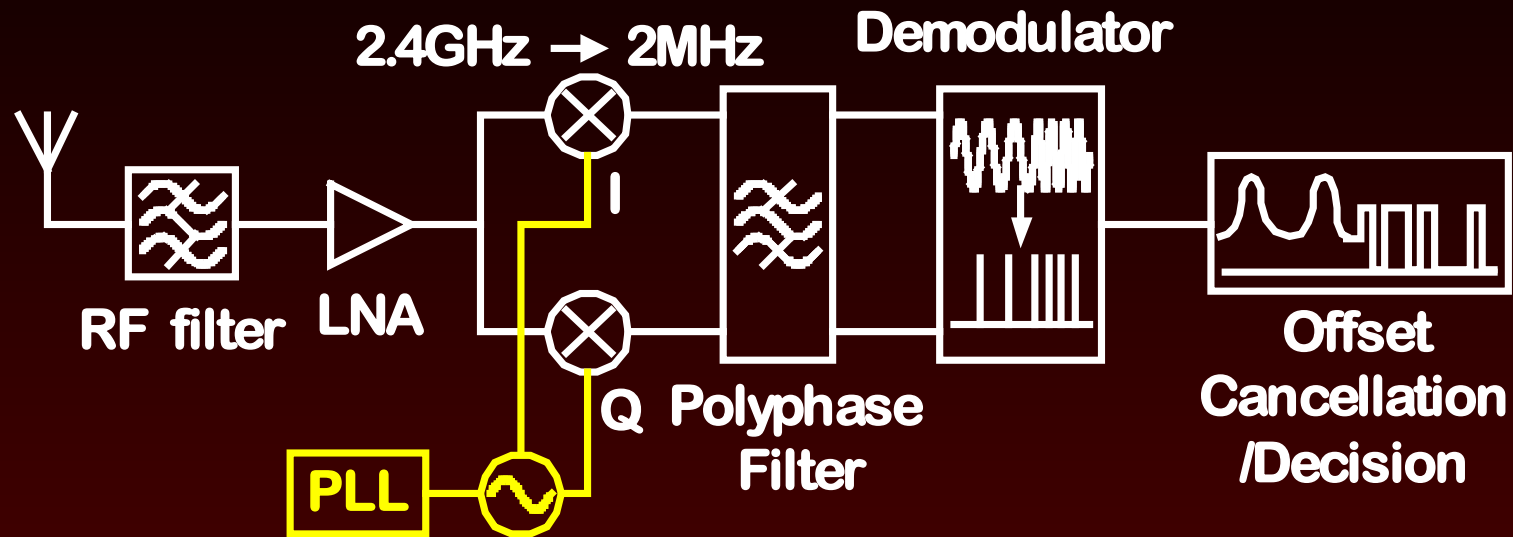


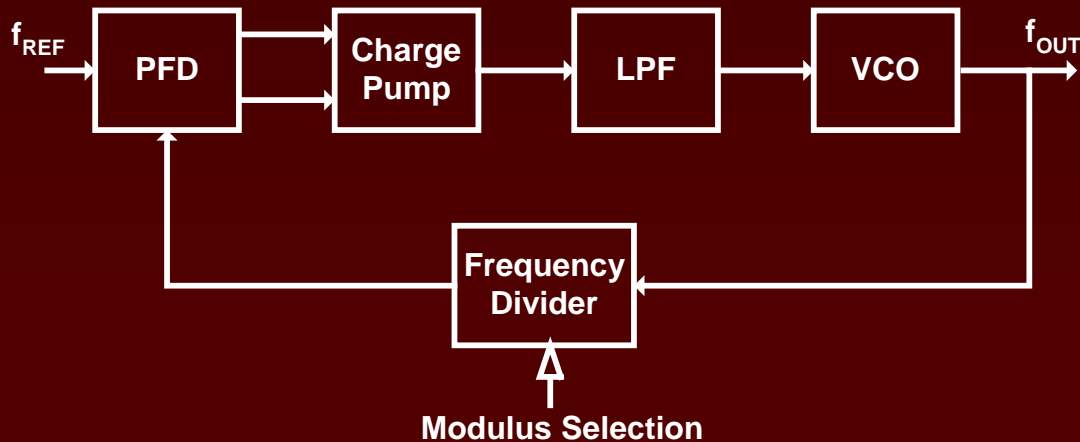Bluetooth Low IF Receiver in 0.35 μm CMOS



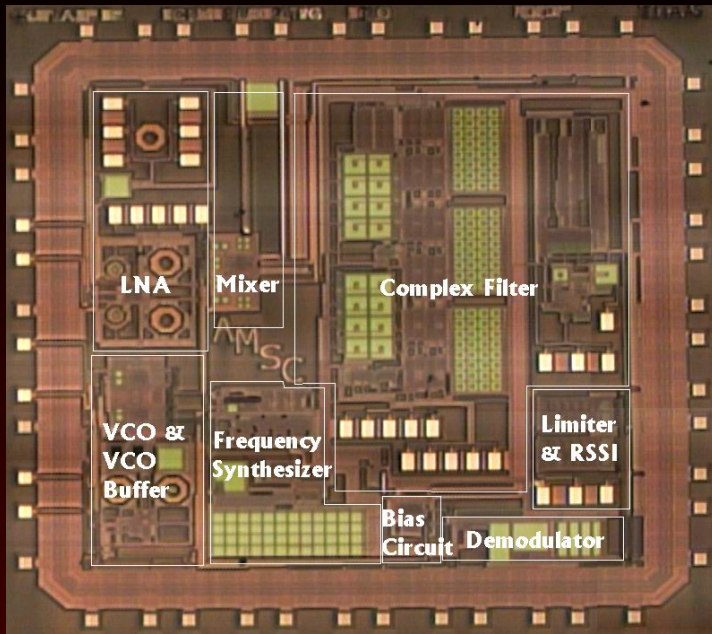


Micrograph

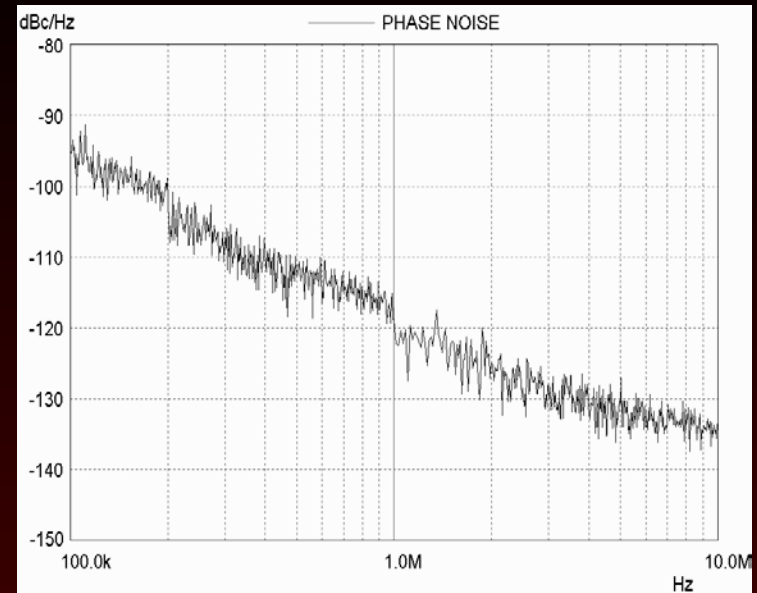

Phase Noise Measurement

- Results
 - Tuning Range: 2.388 - 2.550 GHz
 - PN: -120dBc / Hz @ 1MHz
 - Frequency Step 1MHz
 - Power: 12 mA

Dual Mode Receiver

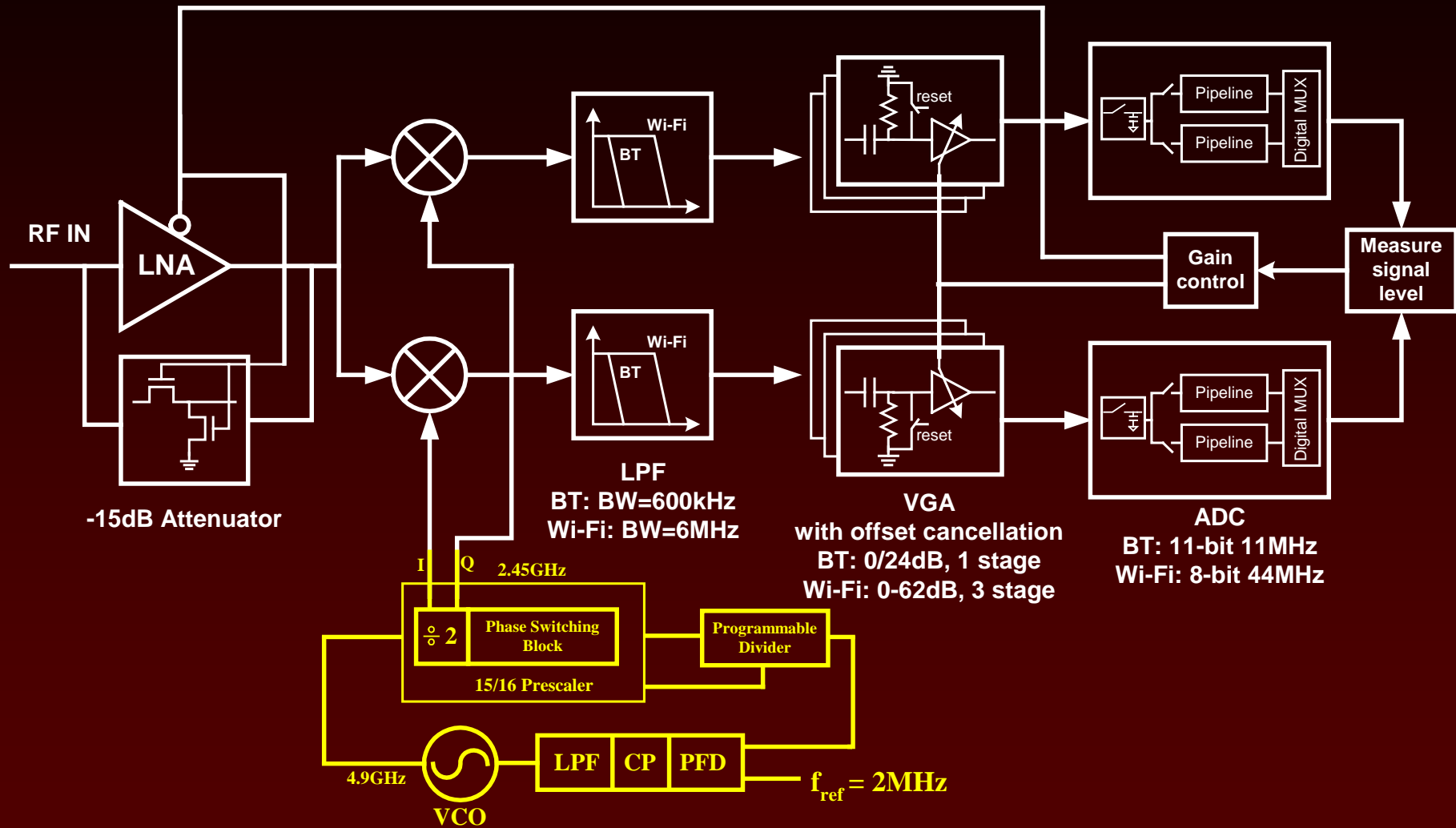

Direct Conversion Bluetooth/Wi-Fi Receiver


Frequency Synthesizer Specifications

	Bluetooth	IEEE 802.11b
Frequency Range	2401 – 2480 GHz	2401 – 2480 GHz
Channel Spacing	1 MHz	5 MHz
Settling time (max)	220 μ s	224 μ s
Phase Noise	-124 dBc/Hz @ 3 MHz	-125 dBc/Hz @ 25 MHz
Center frequency accuracy	\pm 75 kHz	\pm 60 kHz

- Bluetooth specifications are more stringent
- Complying with Bluetooth specs covers WiFi

Frequency Synthesizer Architecture

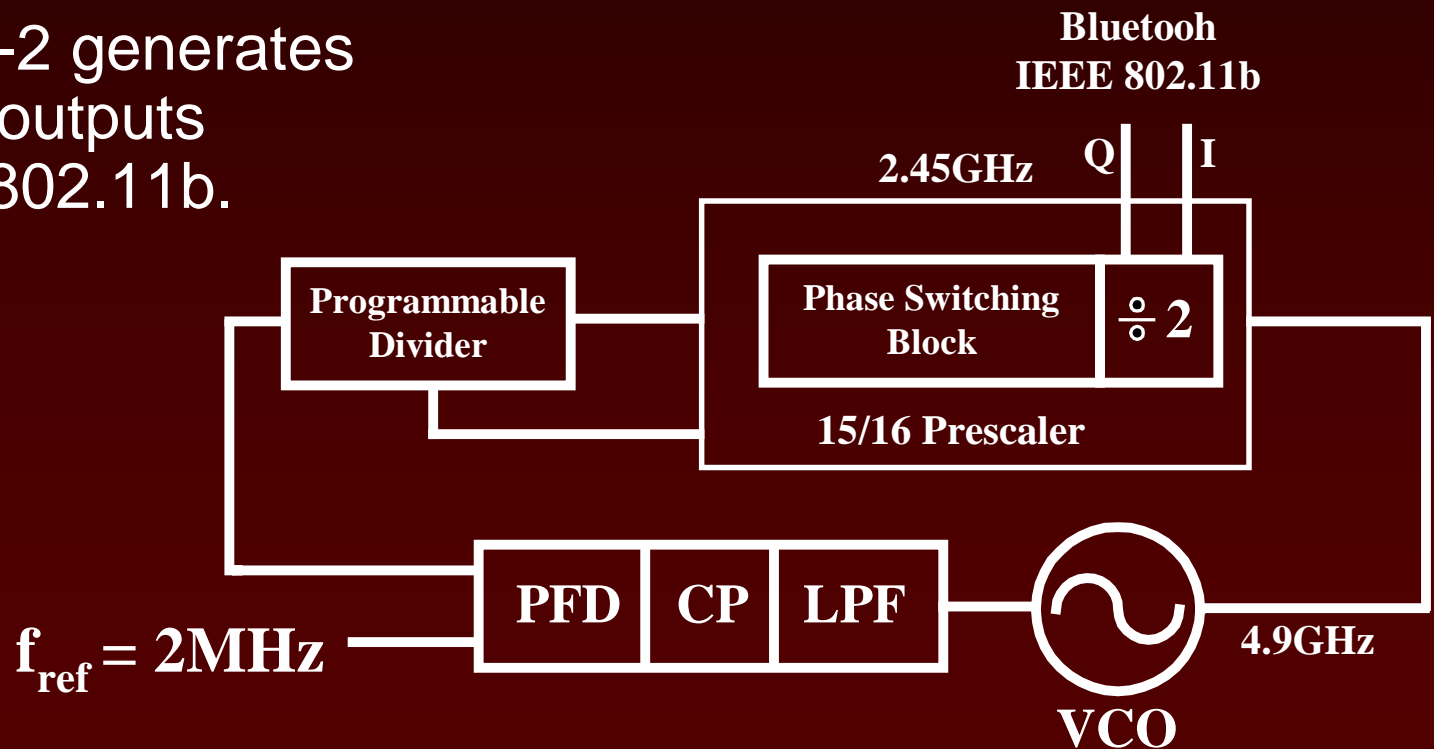- An Integer N Frequency Synthesizer architecture is used.
- The VCO oscillates at 5 GHz to accommodate all the standards (requires 10% tuning range).
- A Divide-by-2 generates quadrature outputs for BT and 802.11b.





Design Considerations

- Phase Margin

$$\phi_m = \tan^{-1}\left(\sqrt{\frac{\omega_{p2}}{\omega_z}}\right) - \tan^{-1}\left(\sqrt{\frac{\omega_z}{\omega_{p2}}}\right)$$
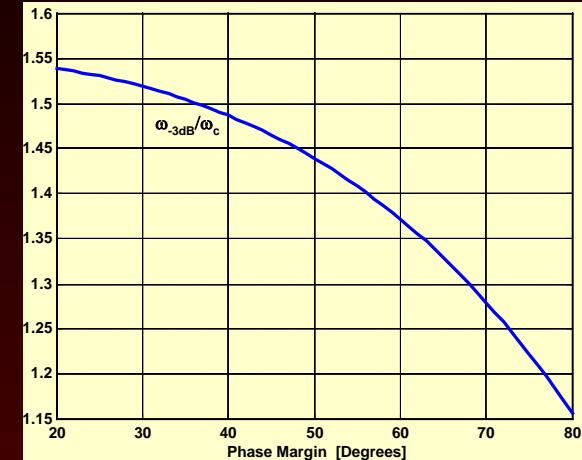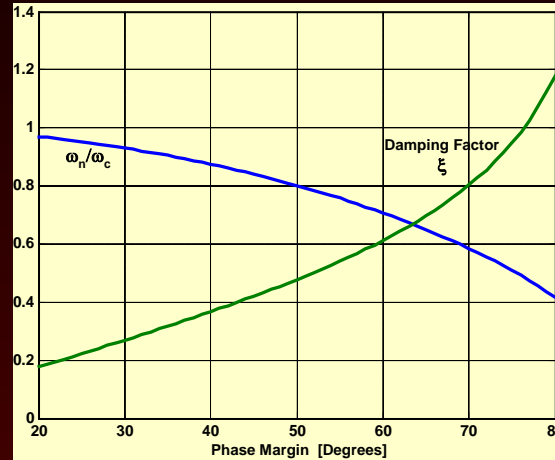
$$\phi_m = \tan^{-1}\left(\sqrt{\frac{C_1}{C_2} + 1}\right) - \tan^{-1}\left(\frac{1}{\sqrt{\frac{C_1}{C_2} + 1}}\right)$$



$$\zeta = \frac{\tau}{2} \sqrt{\frac{K_{pd} K_f K_{vco}}{N}} = \frac{\sin(\phi_m)}{2\sqrt{\cos(\phi_m)}}$$

$$\omega_{-3dB} = \omega_n \sqrt{(2\zeta^2 + 1) + \sqrt{(2\zeta^2 + 1)^2 + 1}}$$


- Settling Time

$$t_{lock} = \begin{cases} \frac{\ln\left(\frac{\Delta N f_{ref}}{\varepsilon \sqrt{1 - \zeta^2}}\right)}{\omega_n \zeta} & \zeta < 1 \\ \frac{1}{(\zeta - \sqrt{\zeta^2 - 1}) \omega_n} \ln\left(\frac{\Delta N f_{ref} \sqrt{\zeta^2 - 1} + \zeta}{\varepsilon 2 \sqrt{1 - \zeta^2}}\right) & \zeta > 1 \end{cases}$$

- Design Parameters

- Loop Bandwidth
- VCO Gain
- Charge Pump Current
- Loop Filter Components

Loop Filter

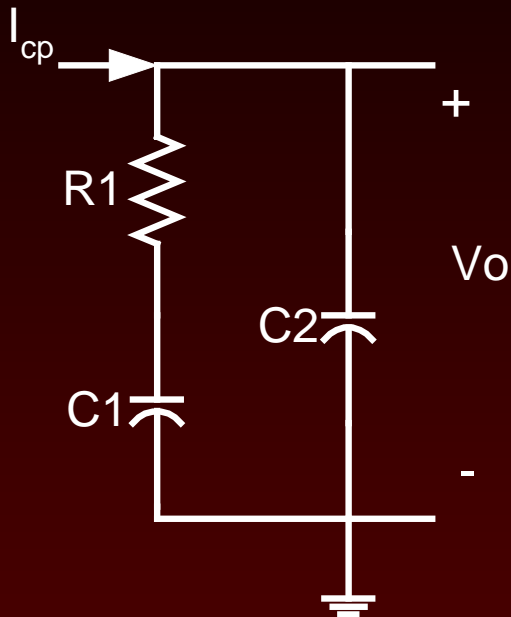

$$K_{vco} = 300\text{MHz/V}$$

$$I_{cp} = 35\ \mu\text{A}$$

$$N = 2450$$

$$C_1 = 340\ \text{pF}$$

$$C_2 = 26.15\ \text{pF}$$

$$R_1 = 52.6\ \text{k}\Omega$$


- Trade offs
 - Settling Time
 - Close-in Phase Noise
 - Total Capacitance
 - Charge Pump Current

Loop Bandwidth = 35 kHz


Phase Margin = 60°

Capacitance Multiplier

- Schematic

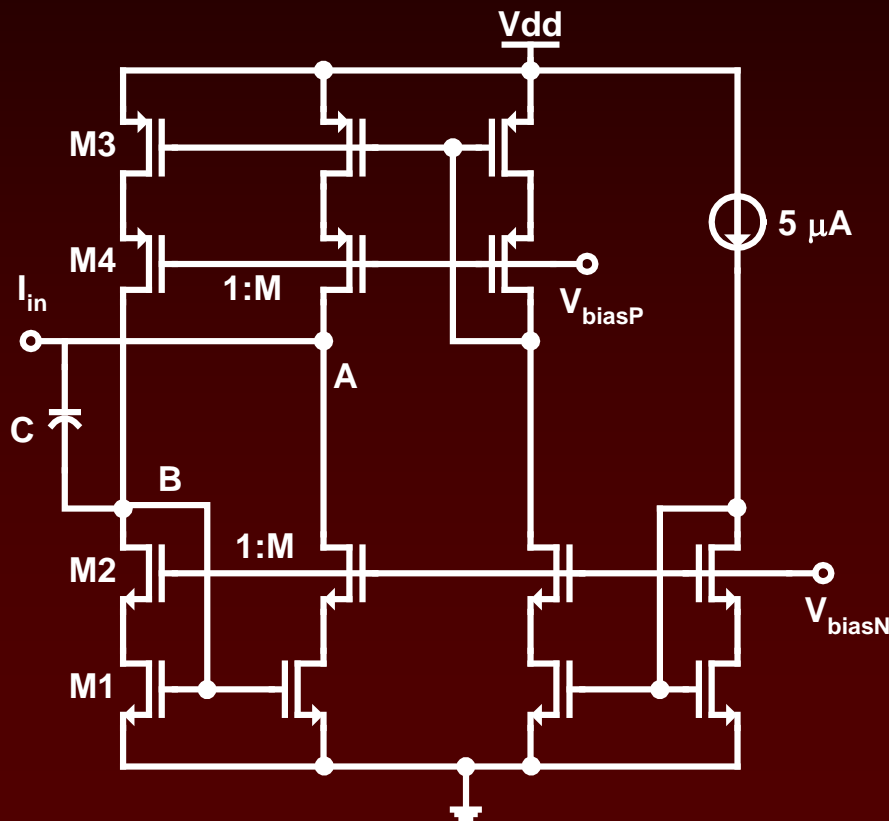


- Model

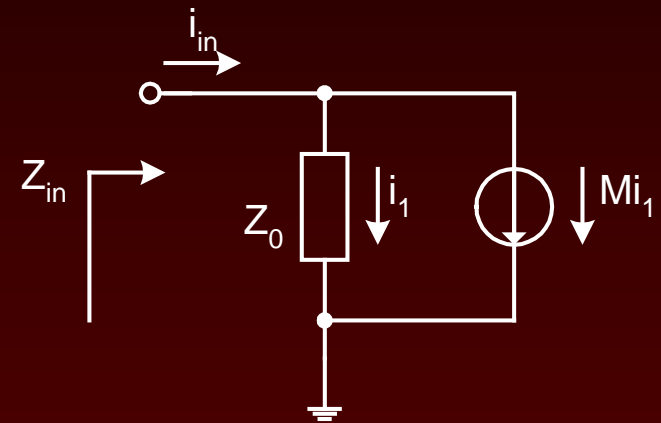

$$Z_{in} = \frac{Z_0}{M + 1}$$

Loop Filter Layout

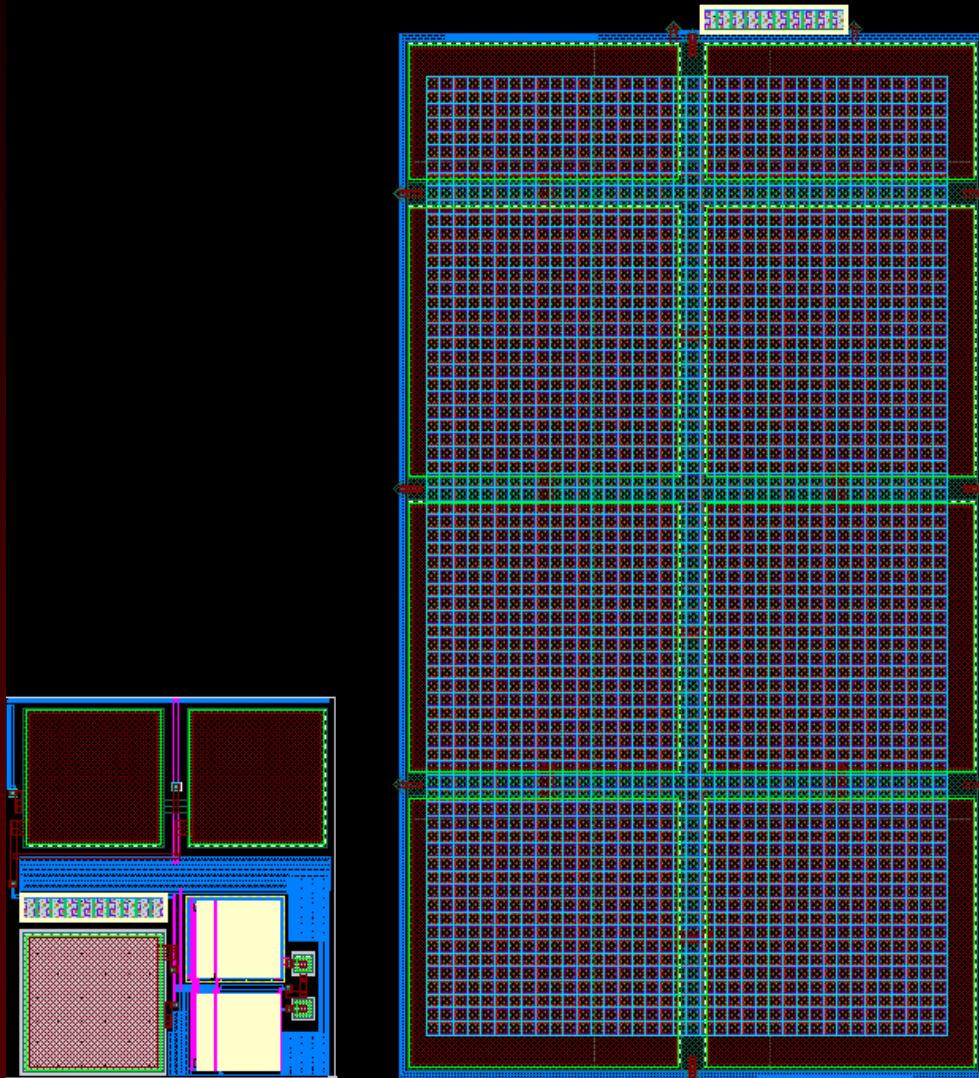


- Active Filter.
 - Reduced area
 - 240µm x 280µm
- Passive Filter.
 - Reduced spurs
 - 430µm x 780µm

Active vs. Passive

Phase Switching Prescaler

- Architecture

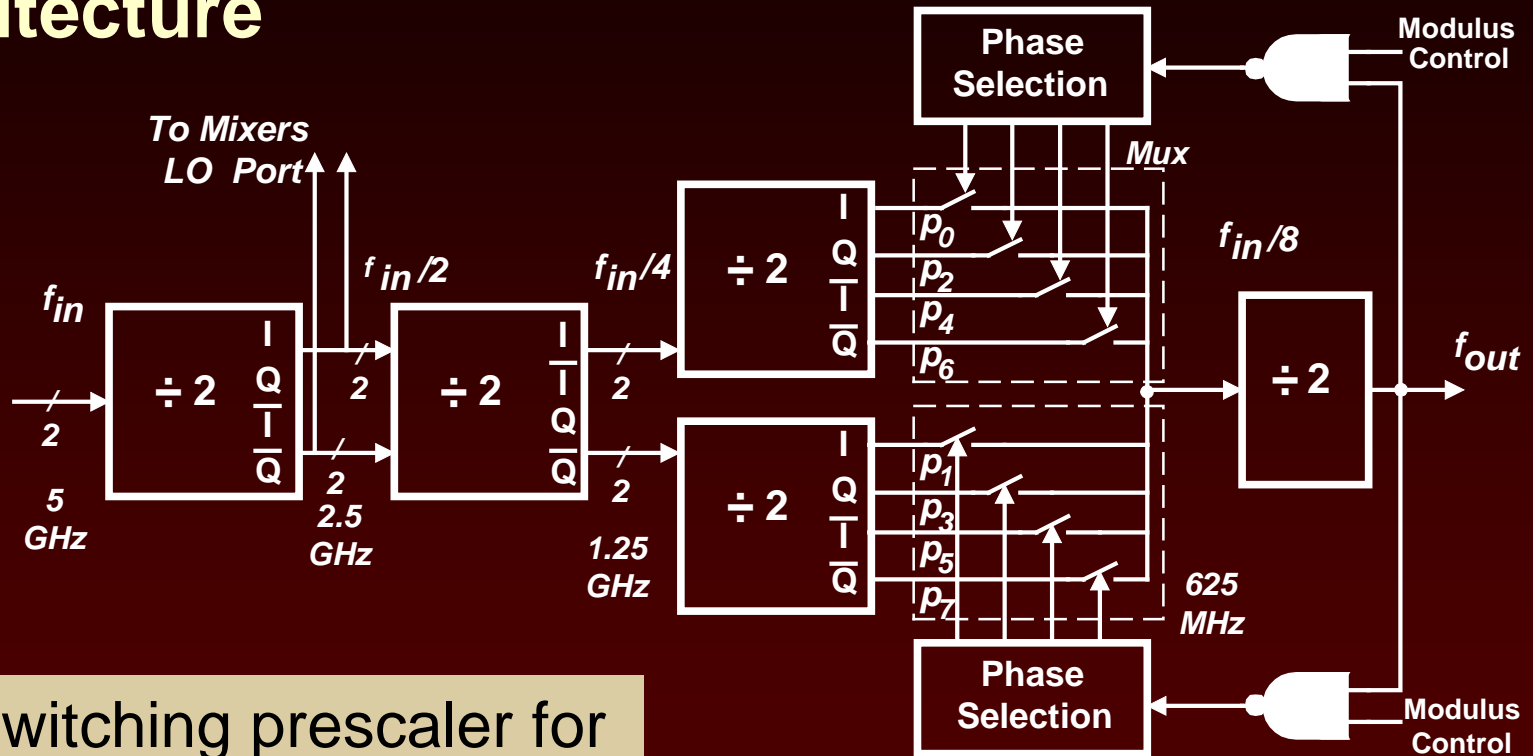



Phase switching prescaler for reduced power consumption compared with traditional architectures.

Total Current: 4 mA

15/16 Dual Modulus





Phase Switching Prescaler

- Circuit Operation**

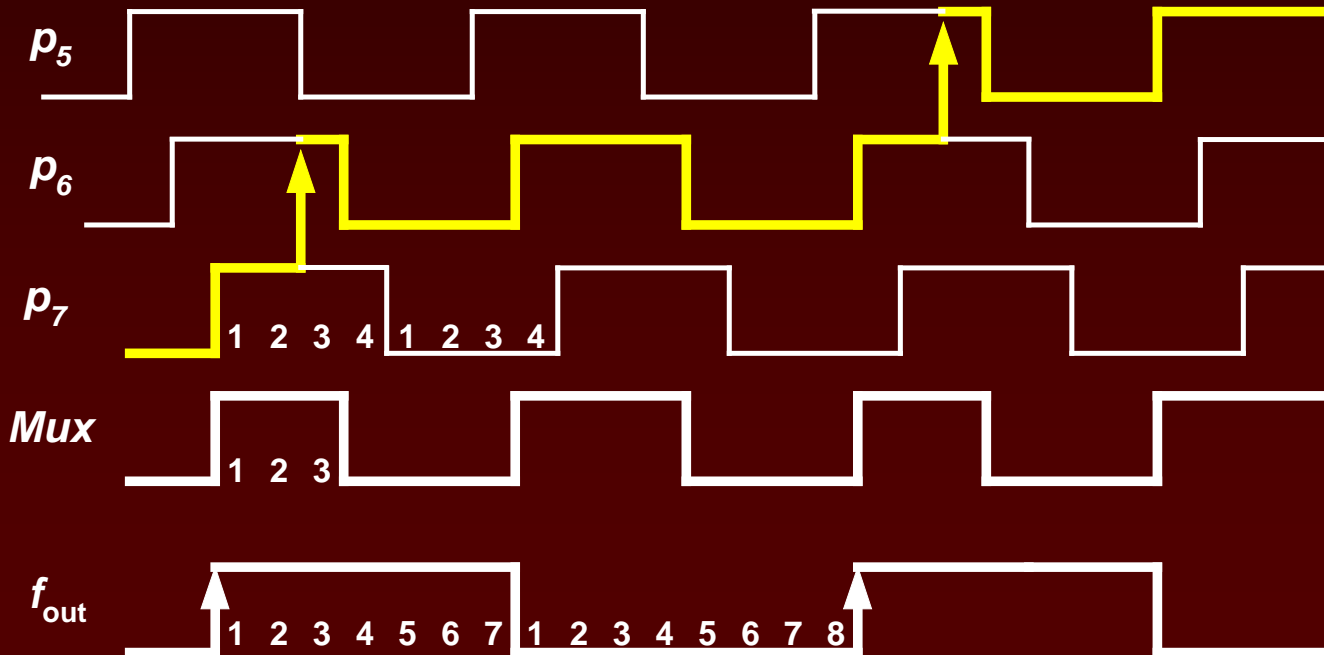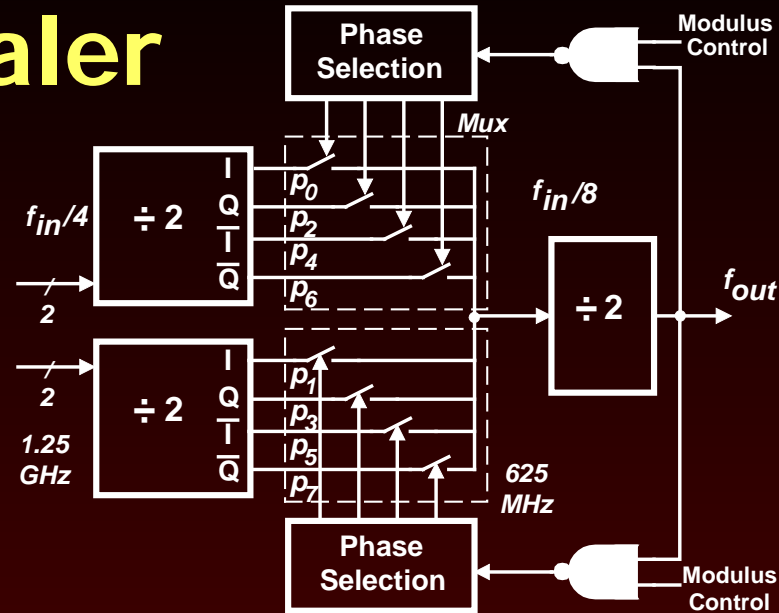

Phase Switching Prescaler

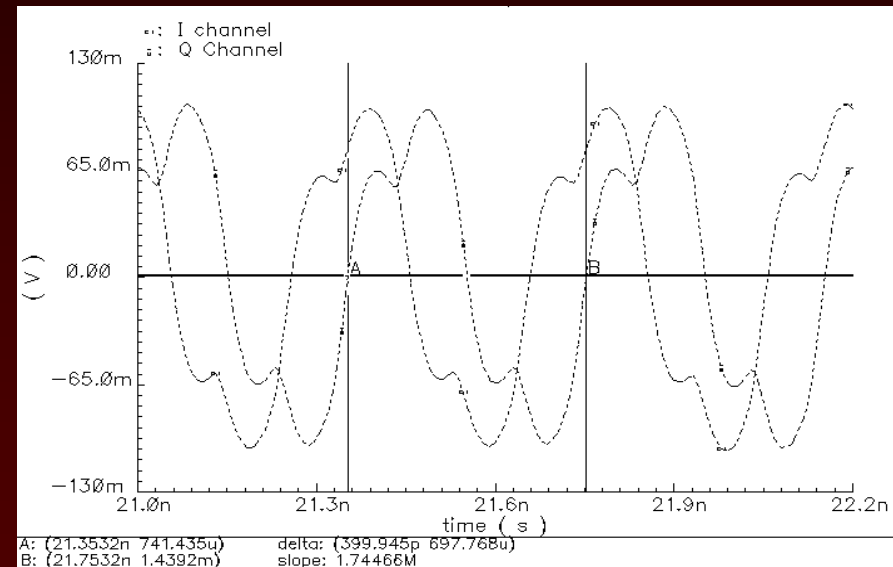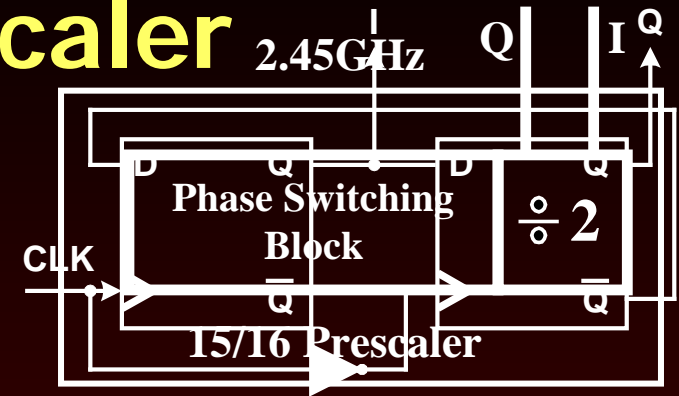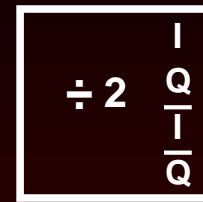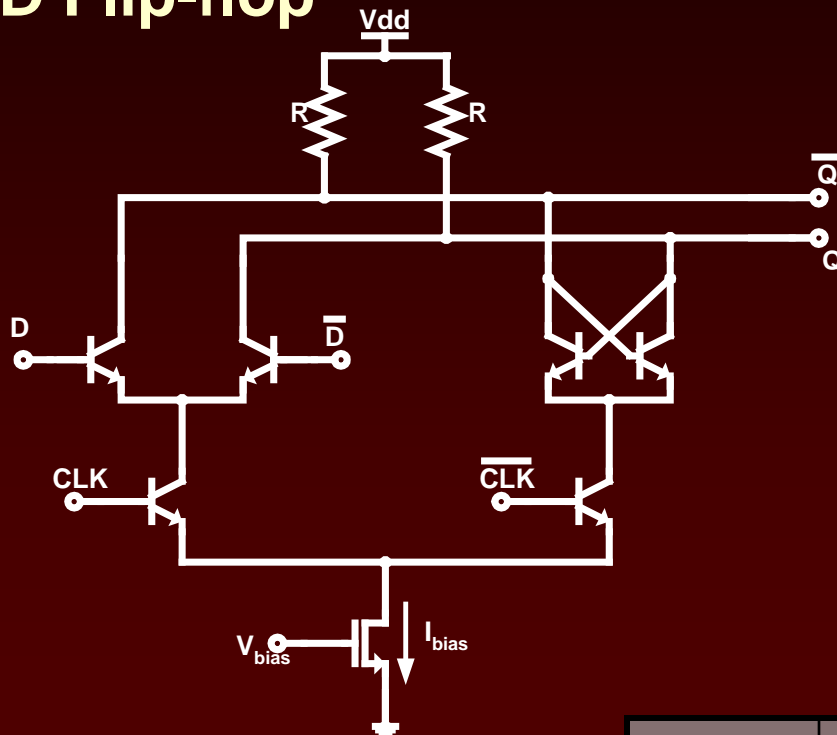
- Implementation: High Frequency D Flip-flop



	1 st stage	2 nd stage	3 rd stage
I_{bias}	500 μA	375 μA	250 μA
R	1 k Ω	1.3 k Ω	2 k Ω


Measurement Results

- Phase Noise

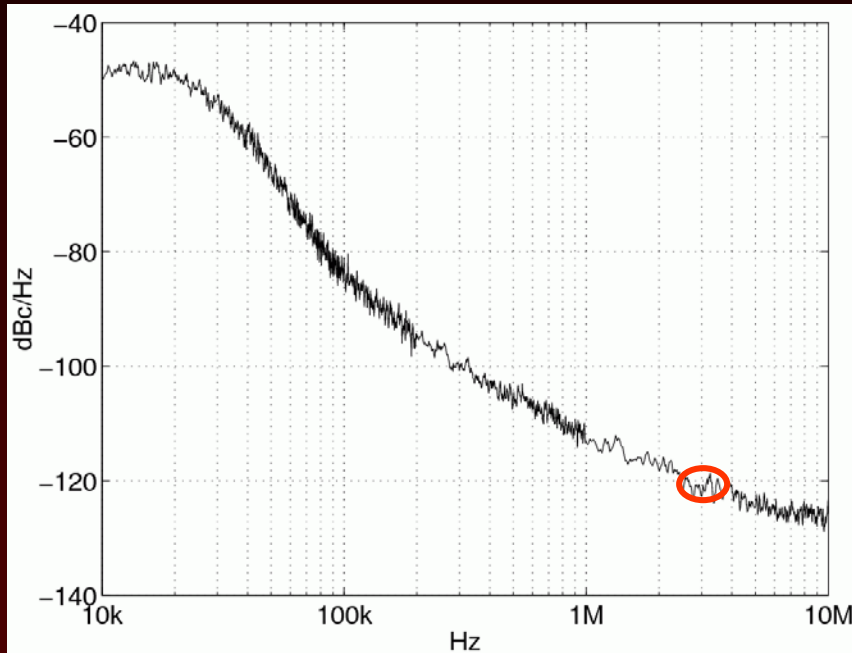

Phase Noise:
-124 dBc/Hz @ 3MHz


- Settling Time

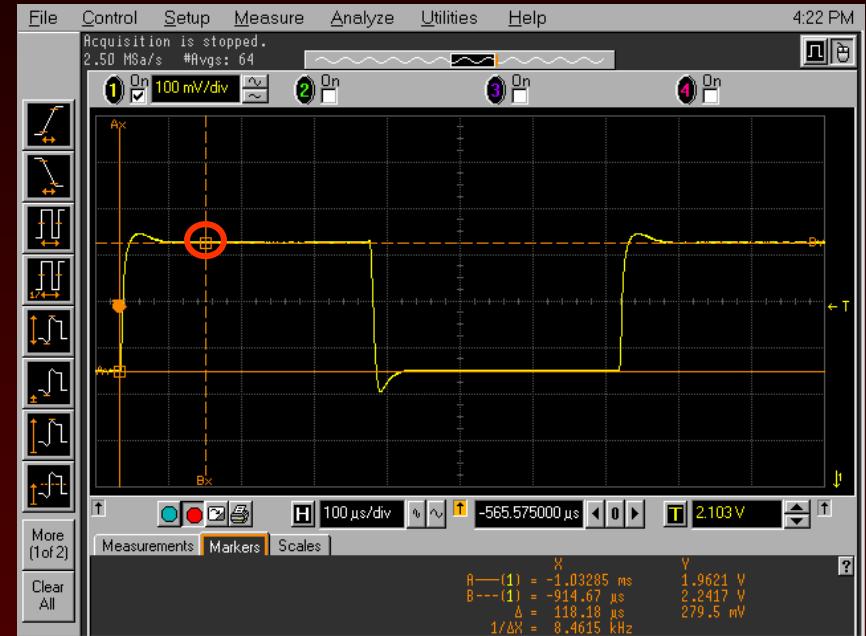


Settling time :
150 μs (220 μs spec)

Measurement Results

- Output Spectrum

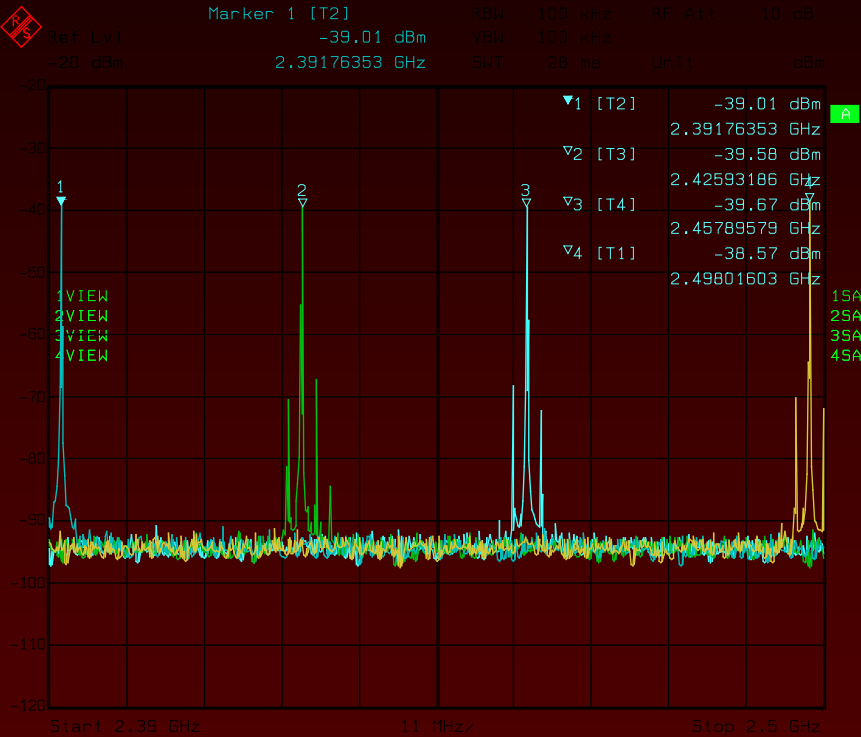

- I/Q Mismatch

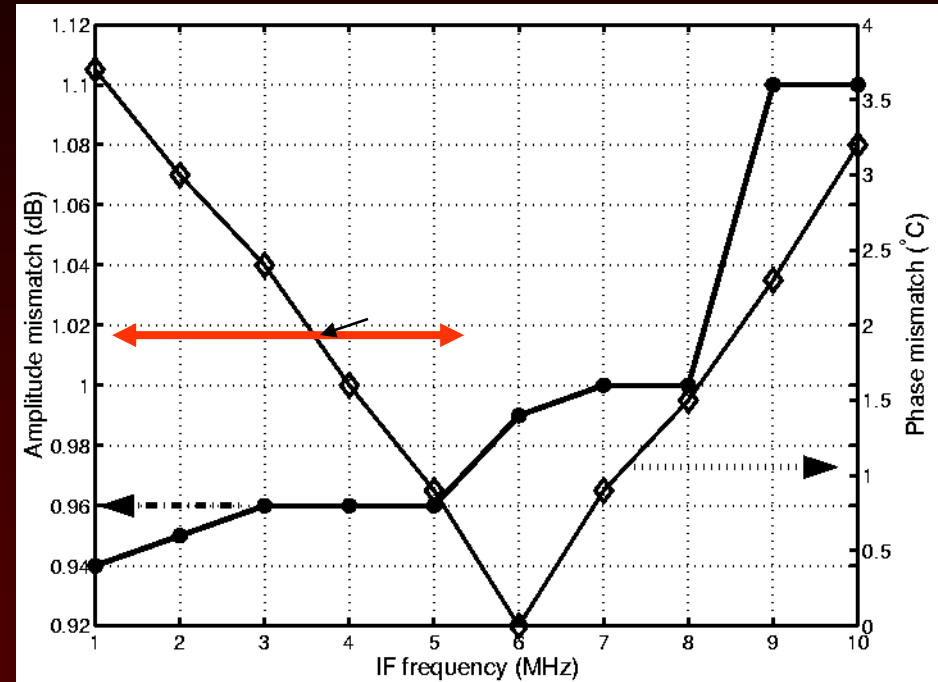

Tuning Range:
2.391 – 2.498 GHz

Worst case measurement

Phase error $\approx 3^\circ$

Magnitude error $\approx 1\text{dB}$


Summary of FS Testing Results

Parameter	Value	Units
Frequency Range	2400 - 2500	GHz
Phase Noise	-124	dBc @ 3MHz
Settling Time	150	μ s
Reference Spur	-35	dBc
Power Consumption	31.25	mW
I/Q Mismatch		
Phase	< 3	°
Amplitude	< 1	dB


Summary of Testing Results

- Power Consumption Distribution

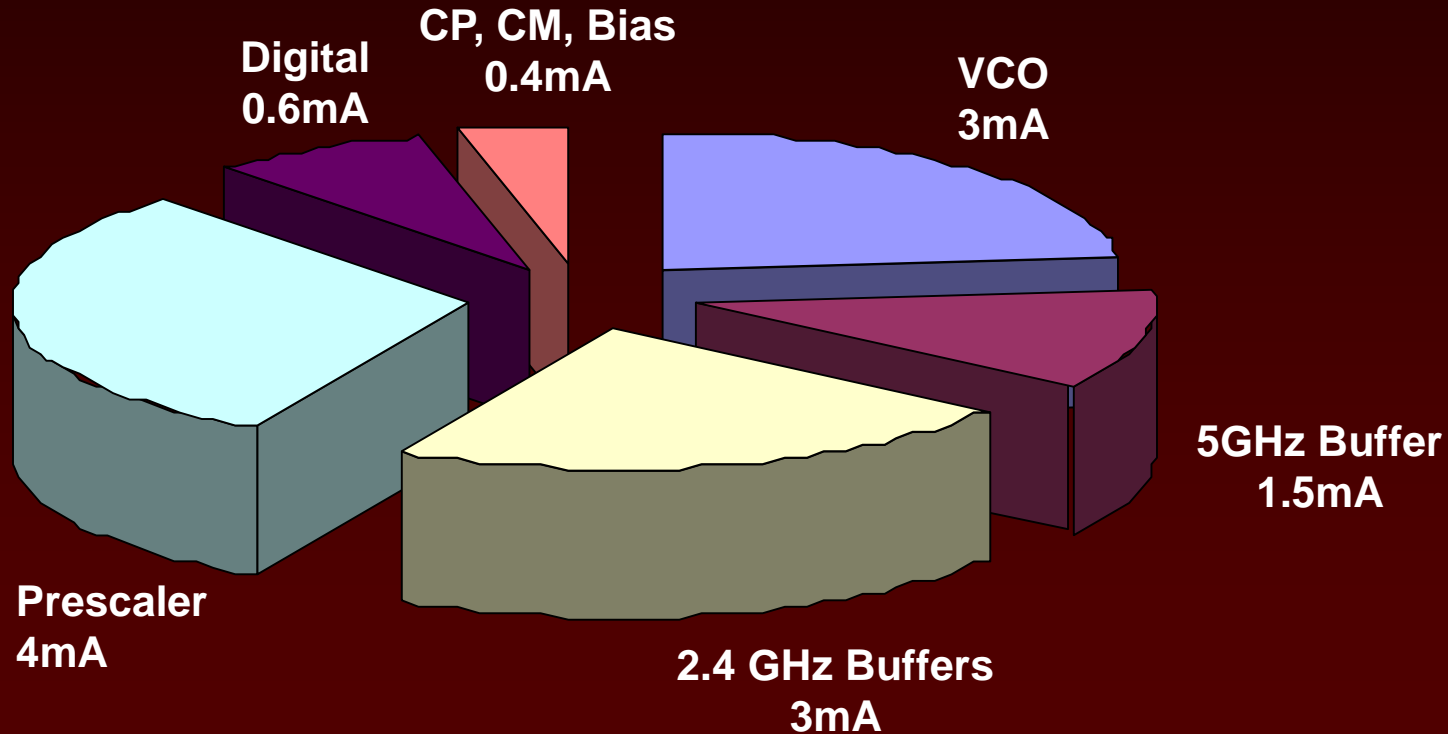Total current consumption = 12.5mA
with buffers



Die Micrograph

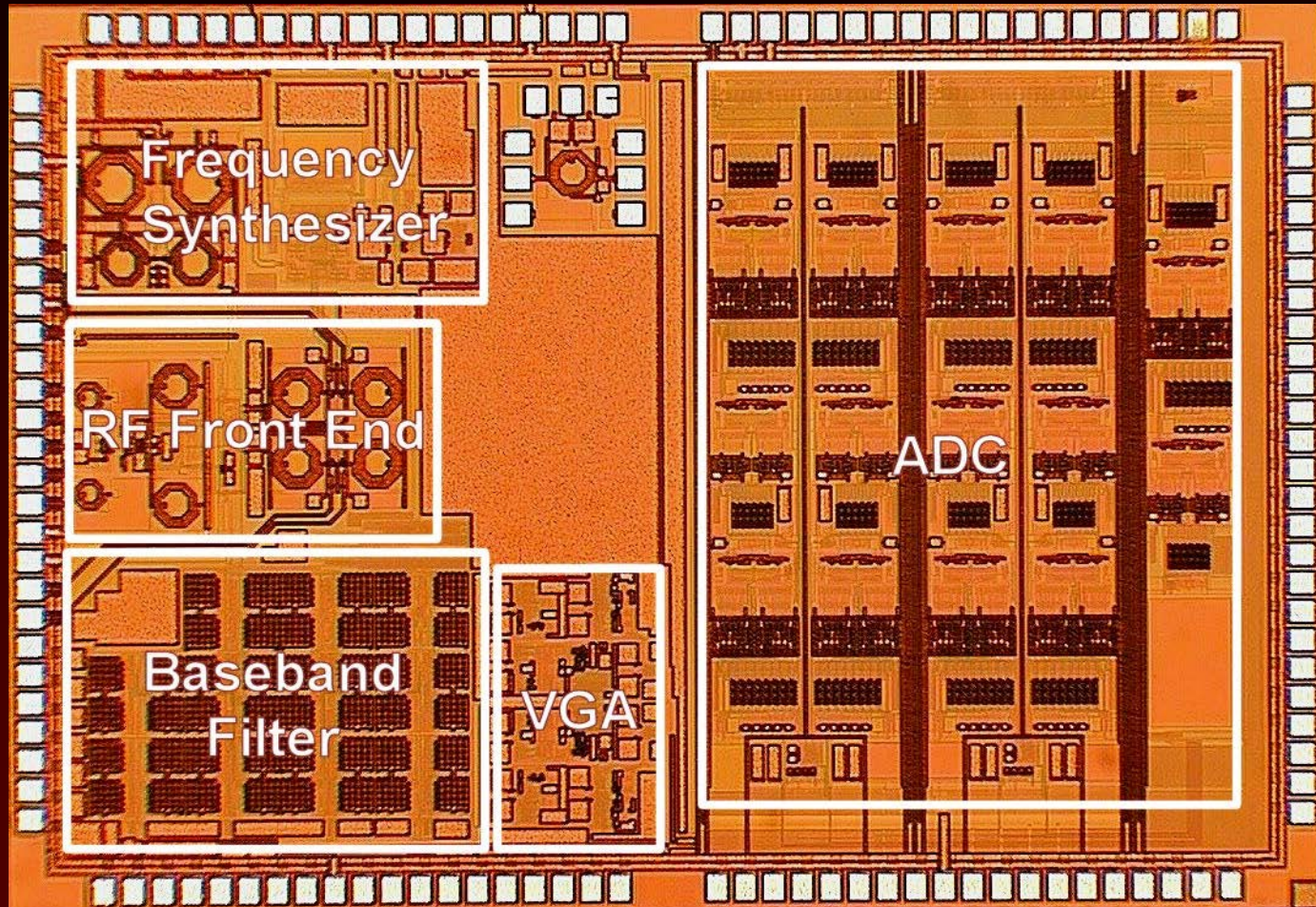

- Die Area: 21 mm²
- Synthesizer Area: 1.87 mm²
- Package: TQFP 128pins

A Multi-standard Frequency Synthesizer


Sung Tae Moon

April 4, 2003

Bluetooth + WLAN 802.11b Specification

	Bluetooth	WLAN 802.11b
• Band	2.4~2.48	2.4~2.472 GHz
• Channel	1 MHz	5 MHz
• Settling	239 μs_{MAX}	220 μs_{MAX}
• Phase noise	-124 dBc @3 MHz	-126 dBc @25 MHz
• Accuracy	± 75 kHz	± 60 kHz


Bluetooth + WLAN 802.11b Specification

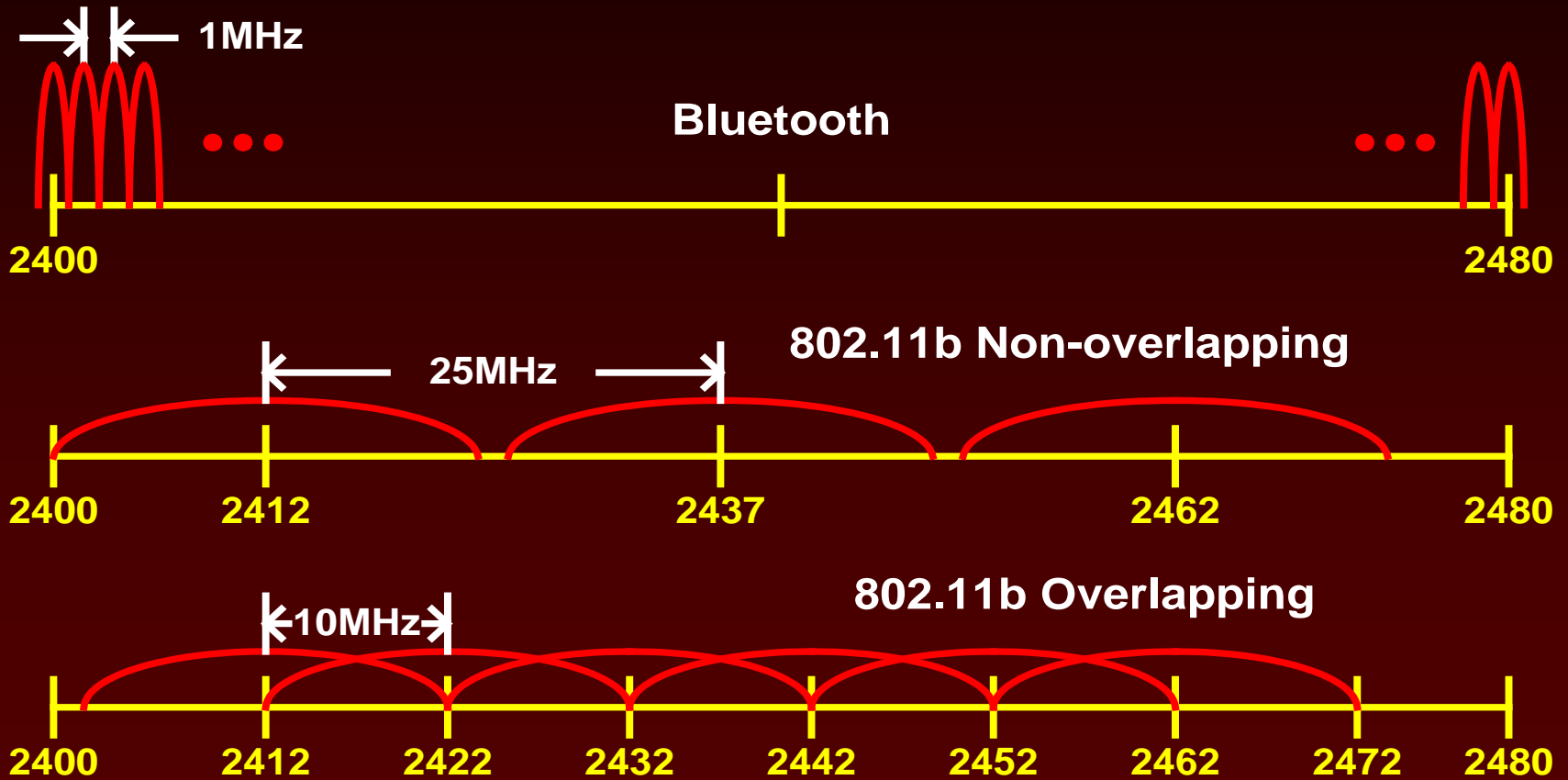

What's the Challenge?

- Limited loop bandwidth : 100 kHz
 - Results in slow settling
 - Adaptive dual-loop PLL
- Wide band VCO Necessary
 - Multi-frequency bands to allow for low K_{VCO} and wide tuning range
 - Automatic calibration to switch between bands


Adaptive Dual-loop PLL

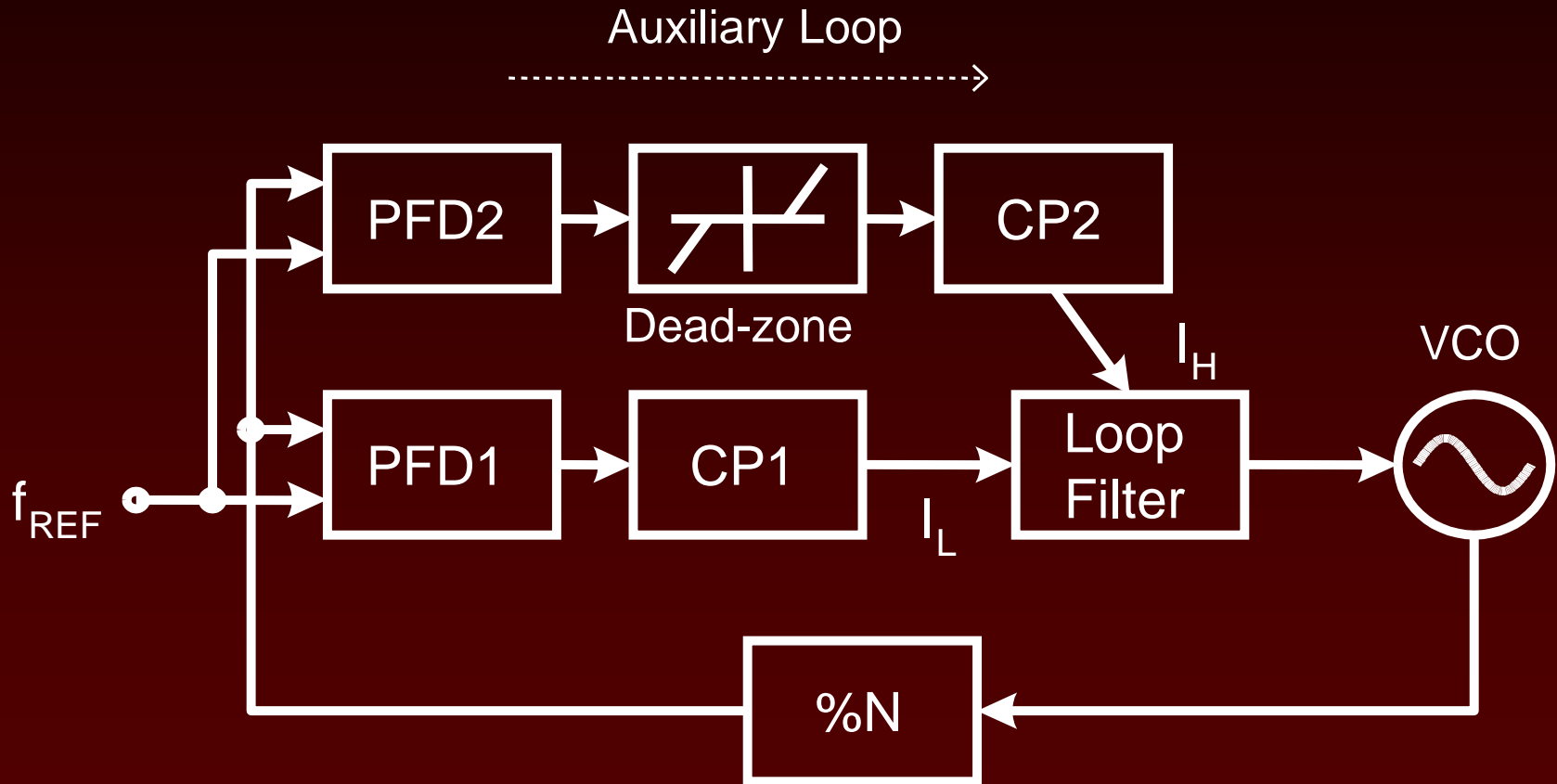


Adaptive Dual-loop PLL

- Less costly solution to limited loop-bandwidth problem
- Flexible Loop-bandwidth
- Glitch problem between bandwidth switching
- Smooth transition using dead-zone
- Improved dead-zone control



Dead-zone Control

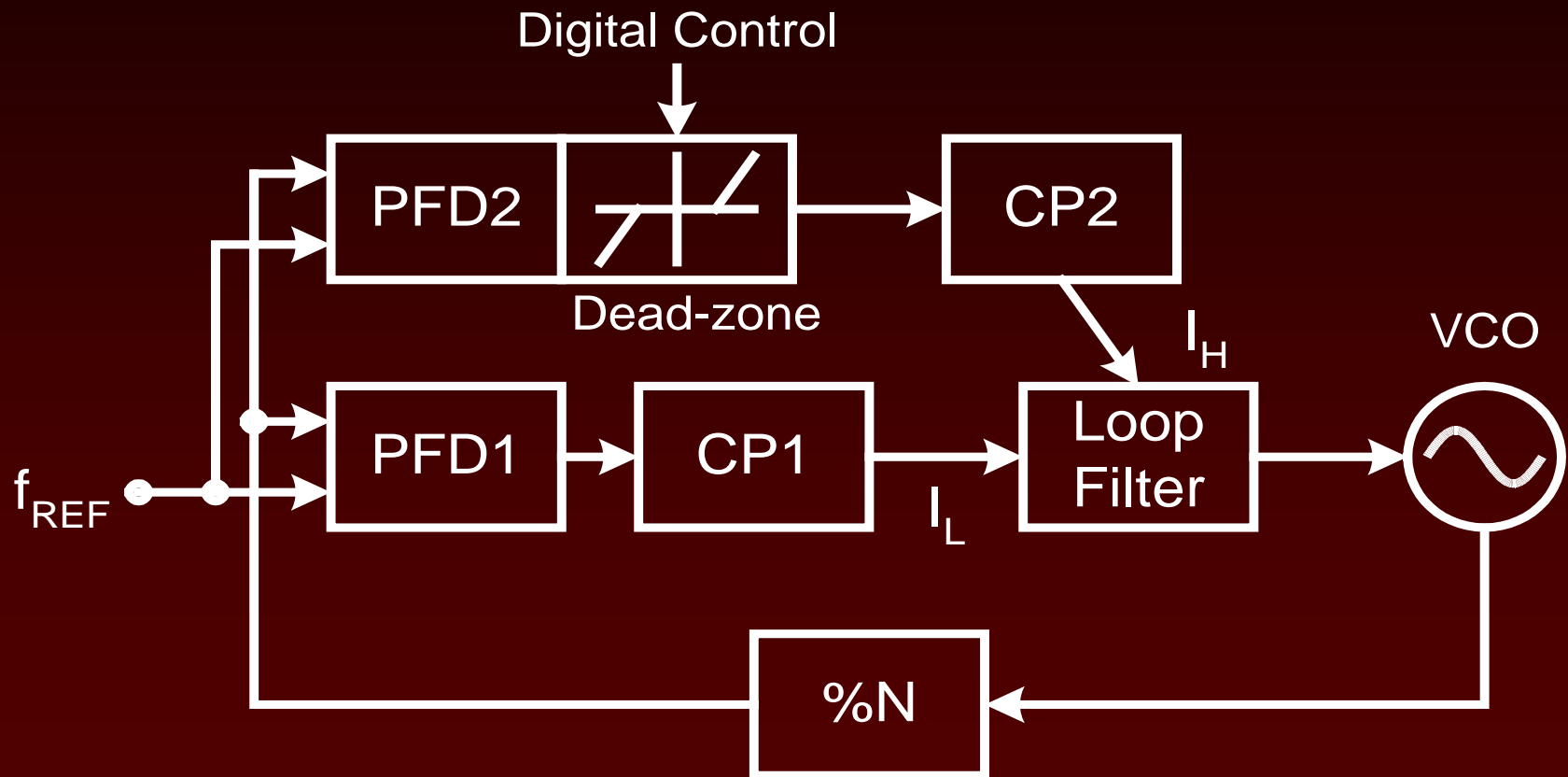

MATLAB simulation


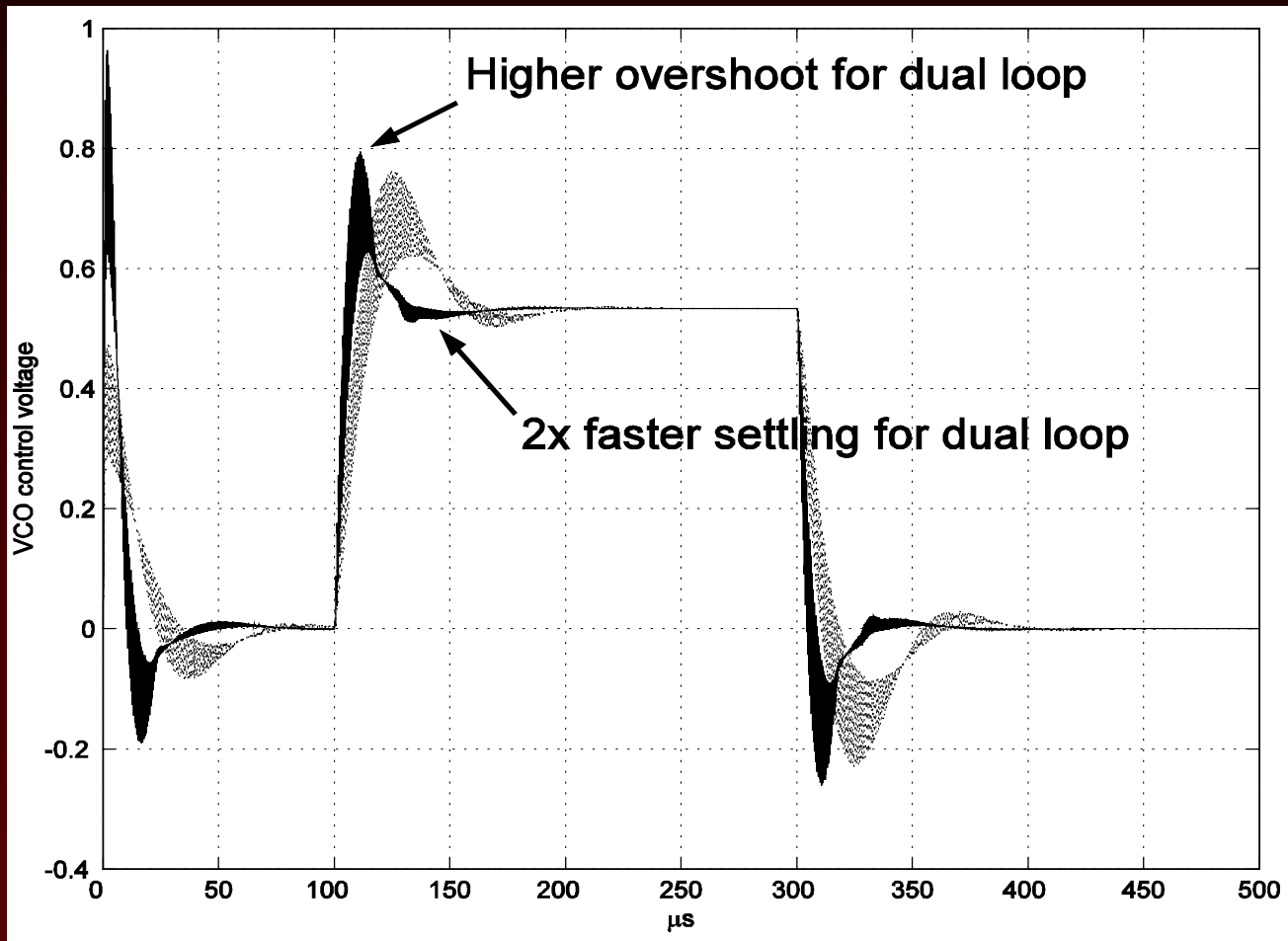


Wide-Band VCO with Calibration

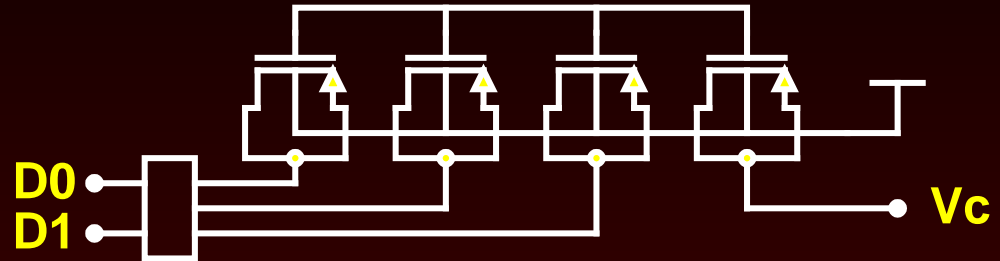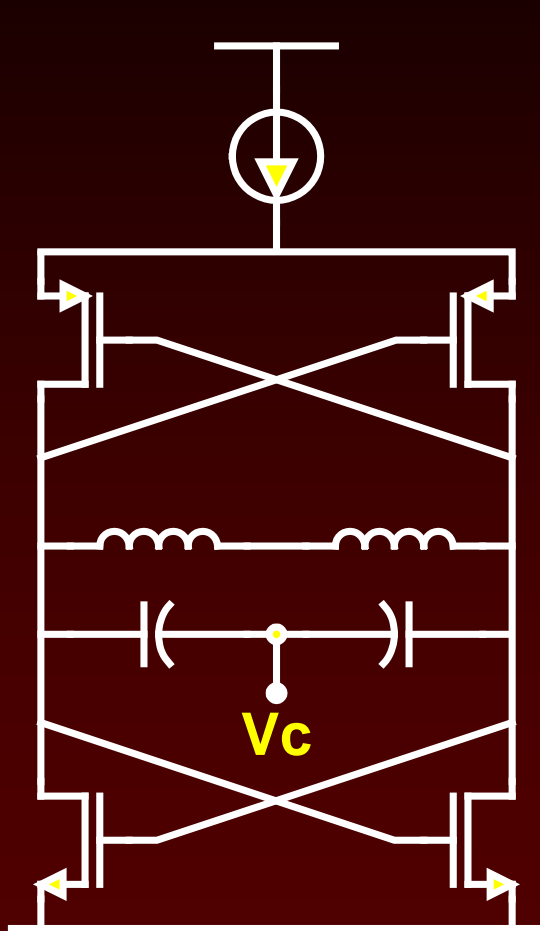

- Discrete capacitor array
 - Without array, tuning gain is too high
- With array, both wide band operation and low tuning gain are achieved
- Comparator loop for automatic calibration

Automatic Calibration

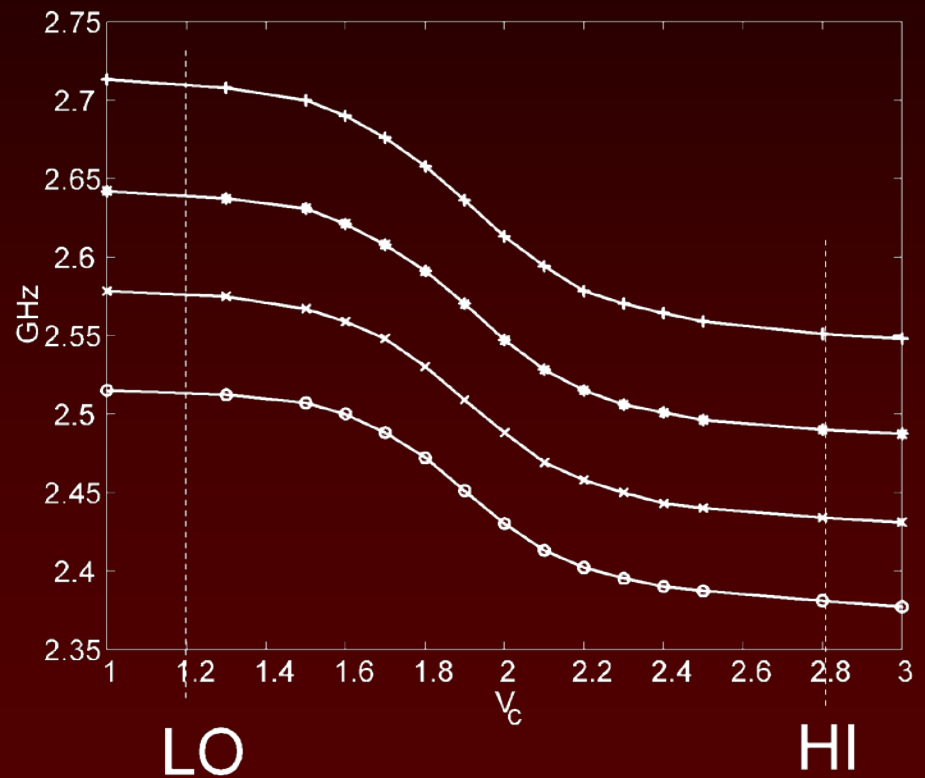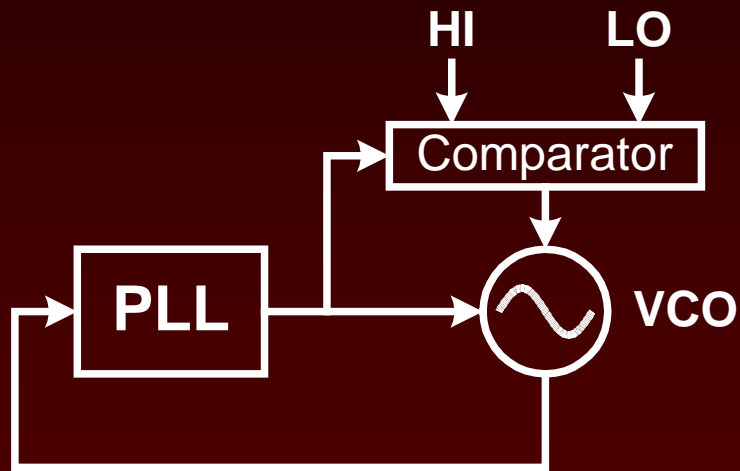

Next Time

- Fractional-N Frequency Synthesizers