

**Texas A&M University**  
**Department of Electrical and Computer Engineering**

**ECEN 720 – High-Speed Links**

**Spring 2015**

**Exam #1**

**Instructor: Sam Palermo**

- Please write your name in the space provided below
- Please verify that there are 7 pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!

Problem	Score	Max Score
1		30
2		20
3		10
4		15
5		25
<b>Total</b>		<b>100</b>

Name: SAM PALERMO


UIN: \_\_\_\_\_

Problem 1 (30 points)

a) A 1V step is launched onto the channel below at  $t=0$ ns. (20 points)



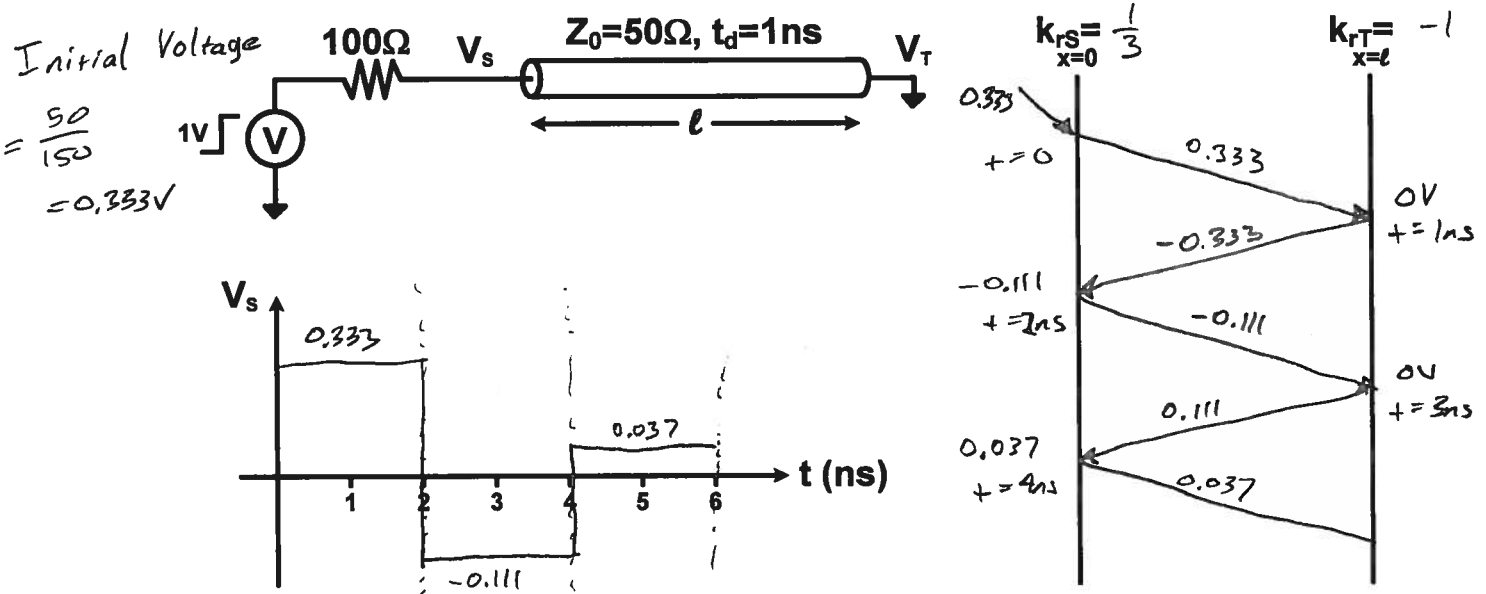
- i. Calculate the reflection coefficient at the source,  $k_{rS}$ , and at the end termination,  $k_{rT}$
- ii. Fill in the lattice diagram below until the source voltage,  $V_s$ , has reached to within 100mV of its final value.
- iii. Also plot the source voltage,  $V_s$ , and make sure to label the voltage values in the transient plot.

Source shorted to GND  $\Rightarrow$  Final  $V_s$  should be 0V



$$k_{rS} = \frac{Z_s - Z_0}{Z_s + Z_0} = \frac{100 - 50}{100 + 50} = \frac{1}{3} \quad k_{rT} = \frac{Z_T - Z_0}{Z_T + Z_0} = \frac{0 - 50}{0 + 50} = -1$$

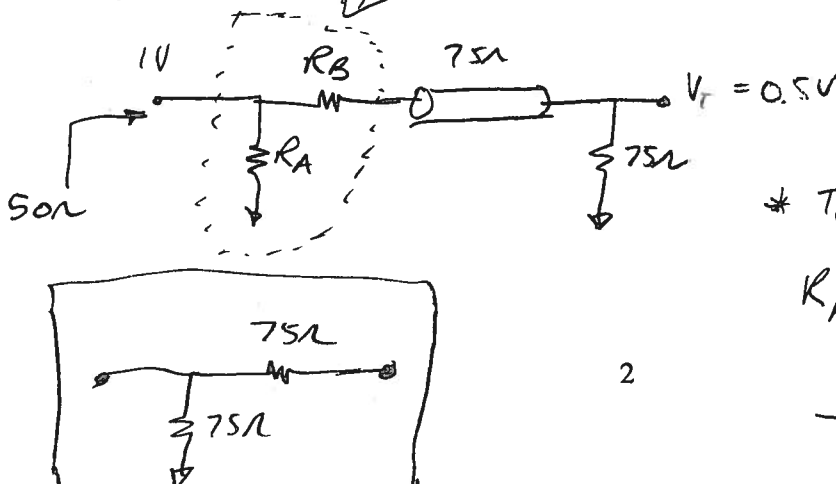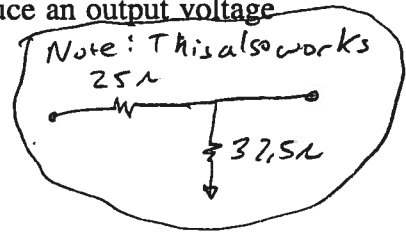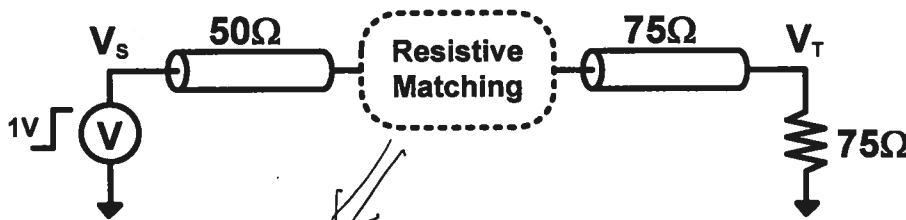b) For the circuit below, design a resistive matching network to eliminate any reflections of the forward traveling wave originating from the source,  $V_s$ , and also produce an output voltage  $V_T=0.5V$  with a 1V input step. (10 points)



\* To make  $V_T = 0.5V \Rightarrow R_B = 75\Omega$

\* To satisfy no reflections

$$R_A \parallel (R_B + 75) = 50$$


$$\frac{R_A (150)}{R_A + 150} = 50 \Rightarrow R_A = 75\Omega$$

Problem 2 (20 points)

A channel has the pulse response,  $y^{(1)}$ , below for a "1" bit.

- Find the channel's worst-case eye height at this bit rate.
- Give the channel's worst-case bit pattern at this bit rate. Make sure to label the cursor in the bit pattern.

$$y^{(1)} = [0.6 \ 0.25 \ 0.1 \ 0.05]$$

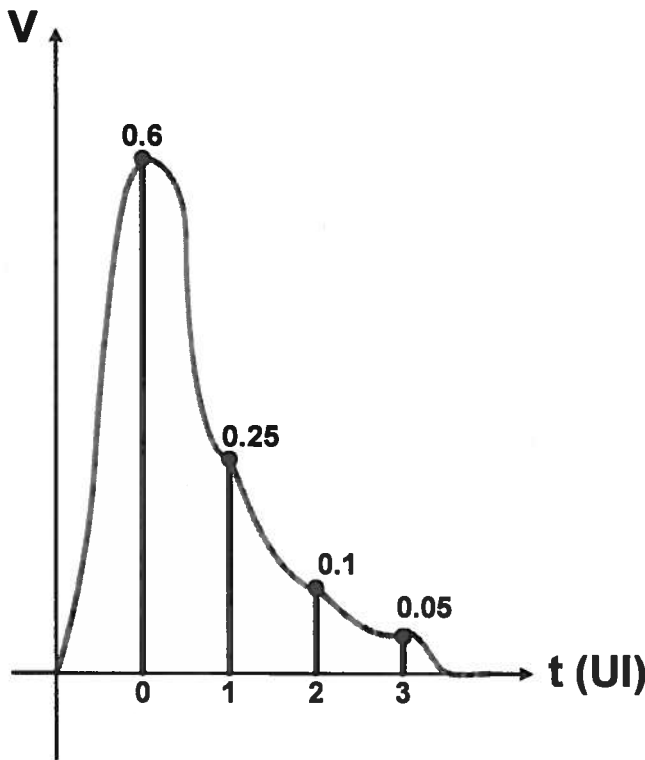

$$y_0^{(1)} = 0.6$$

$$\sum_{k \neq 0} y_k^{(1)} \Big|_{y < 0} = \phi$$

$$\sum_{k \neq 0} y_k^{(1)} \Big|_{y > 0} = 0.25 + 0.1 + 0.05 = 0.4$$

$$\text{W.C. Eye Height} = 2(0.6 - 0.4) = 0.4$$

To find W.C. Bit Pattern: Flip about cursor and invert all but cursor

$$[0.6 \ 0.25 \ 0.1 \ 0.05] \Rightarrow [-0.05 \ -0.1 \ -0.25 \ 0.6]$$

Then take sign

$$[-0.05 \ -0.1 \ -0.25 \ 0.6] \Rightarrow [-1 \ -1 \ -1 \ 1]$$

Worst-Case Eye Height = 0.4

Worst-Case Bit Pattern =  $[-1 \ -1 \ -1 \ 1]$  (Worst-case "1")


$[1 \ 1 \ 1 \ -1]$  (Worst-case "-1")

by linearity
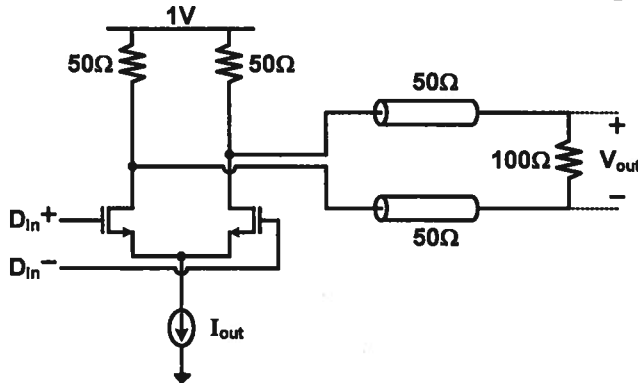
## Problem 3 (10 points)

Answer the following questions for the current-mode driver below

- Calculate the tail current  $I_{out}$  to generate a peak-to-peak differential voltage output swing of  $0.6V_{ppd}$ .
- Give the common-mode value of the output voltage with the  $0.6V_{ppd}$  output swing.



$$I_{out} = \frac{V_{ppd}}{R} = \frac{0.6V}{50\Omega} = 12mA$$

During "1" bit  $V_{out}^+ = 0.85V$   $V_{out}^- = 0.55V$

"-1" bit  $V_{out}^+ = 0.55V$   $V_{out}^- = 0.85V$

$$V_{out,CM} = \frac{0.85 + 0.55}{2} = 0.7V$$

$$I_{out} = 12mA$$

$$V_{out,CM} = 0.7V$$

Problem 4 (15 points)

For the circuit below, use the following NMOS parameters


$$K_{PN} = \mu_n C_{ox} = 600 \mu A/V^2, V_{TN} = 0.35V, \lambda_N = 0V^{-1}$$

and the following PMOS parameters

$$K_{PP} = \mu_p C_{ox} = 150 \mu A/V^2, V_{TP} = -0.35V, \lambda_P = 0V^{-1}$$

For the current-mode driver below

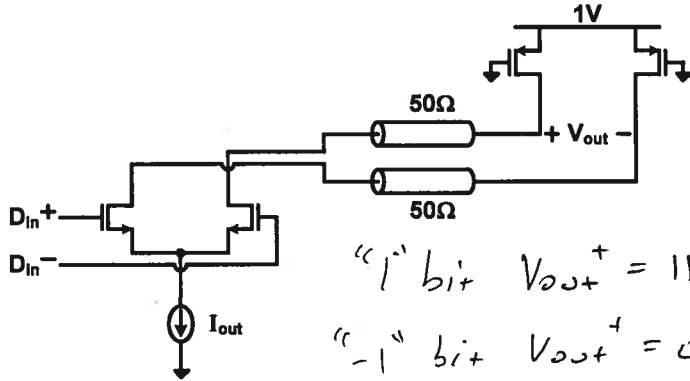- i. Calculate the tail current  $I_{out}$  to generate a peak-to-peak differential voltage output swing of  $600mV_{ppd}$ .
- ii. Give the common-mode value of the output voltage with the  $600mV_{ppd}$  output swing.
- iii. Give the PMOS termination transistors aspect ratios for proper termination. Include  $V_{SD}$  effects and optimize the termination at the output common-mode level.




$$I_{out} = \frac{V_{ppd}}{2R} = \frac{600mV}{2(50\Omega)} = 6mA$$

"1" bit  $V_{out+} = 1V, V_{out-} = 1V - 6mA(50\Omega) = 0.7V$

"-1" bit  $V_{out+} = 0.7V, V_{out-} = 1V$

$$V_{out,CM} = \frac{1+0.7}{2} = 0.85V$$

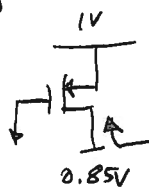\* Sizing PMOS termination at common-mode level



Looking into drain of PMOS in deep triode

$$R_p = \frac{1}{g_o} = \frac{1}{K_P \frac{W}{L} (V_{SG} - |V_{TP}| - V_{SD})}$$

$$\frac{W}{L} = \frac{1}{R_p K_P (V_{SG} - |V_{TP}| - V_{SD})} = \frac{1}{(50\Omega)(150\mu A/V^2)(1V - 0.35V - 0.15V)} = 267$$

$$I_{out} = 6mA$$


$$V_{out,CM} = 0.85V$$

$$(W/L)_P = 267$$

Problem 5 (25 points)

The NMOS sampler below is used to sample a 5GHz sinusoidal signal at  $t=0$ . Assume that the sampler displays the triangular sampling function,  $h(t)$ .

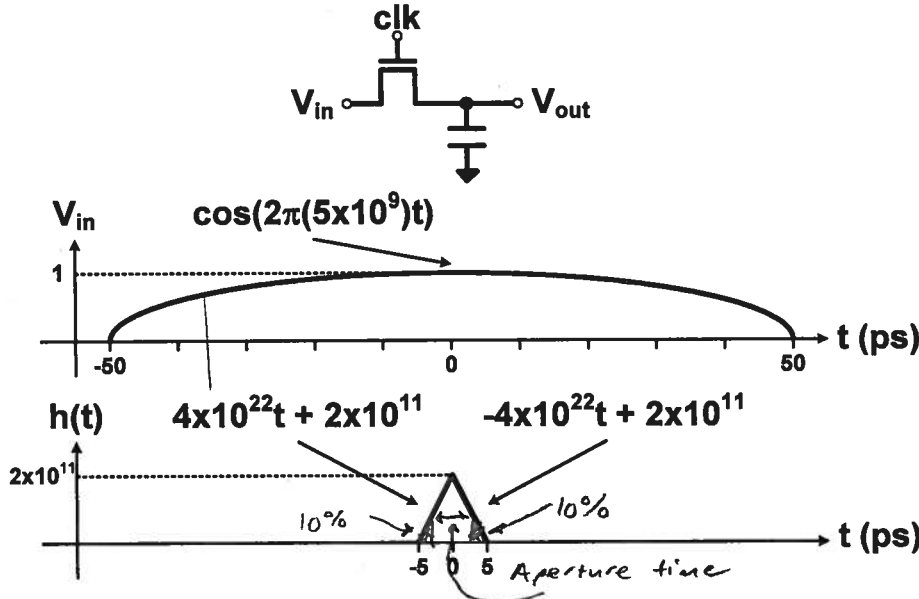- i. Setup, **but do not calculate**, the integral expression for the sampled output voltage.
- ii. Calculate the sampler aperture time from the sampling function. Assume that the aperture time is defined as the time where 80% of the sampler sensitivity is confined.




i. Sampled  $V_{out} = \int_{-\infty}^{\infty} V_{in}(t) h(t) dt$


$$= \int_{-5ps}^0 \cos(2\pi(5 \times 10^9)t) [4 \times 10^{22}t + 2 \times 10^{11}] dt + \int_0^{5ps} \cos(2\pi(5 \times 10^9)t) [-4 \times 10^{22}t + 2 \times 10^{11}] dt$$

ii. Need to find how much time = 10% of area of 0.1 because

$$\int_{-\infty}^{\infty} h(t) dt = 1$$

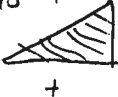$4 \times 10^{22}t$   
  
 Area = 0.1  $\Rightarrow \frac{1}{2} (4 \times 10^{22}t)(t) = 0.1 \Rightarrow t = 2.24ps$  for 10% area

$$\text{Aperture time} = 10ps - 2(2.24ps) = 5.53ps$$

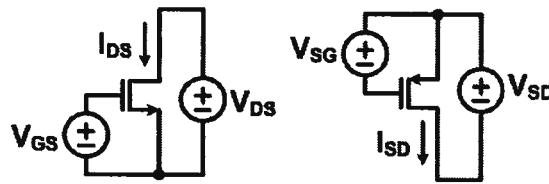**Key MOS Equations & Scratch Paper**

$$\text{Saturation: NMOS } I_{DS} = \frac{1}{2} K P_N \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$\text{Saturation: PMOS } I_{SD} = \frac{1}{2} K P_P \frac{W}{L} (V_{SG} - |V_{TP}|)^2$$

$$\text{Triode: NMOS } I_{DS} = K P_N \frac{W}{L} \left( V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$\text{Triode: PMOS } I_{SD} = K P_P \frac{W}{L} \left( V_{SG} - |V_{TP}| - \frac{V_{SD}}{2} \right) V_{SD}$$

$$\text{NMOS } g_m = \frac{\partial I_{DS}}{\partial V_{GS}}, \quad \text{PMOS } g_m = \frac{\partial I_{SD}}{\partial V_{SG}}$$

$$\text{NMOS } g_o = \frac{\partial I_{DS}}{\partial V_{DS}}, \quad \text{PMOS } g_o = \frac{\partial I_{SD}}{\partial V_{SD}}$$