

**Texas A&M University
Department of Electrical and Computer Engineering**

ECEN 720 – High-Speed Links

Spring 2017

Exam #1

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are **6** pages in your exam
- You may use one double-sided page of notes and equations for the exam
- Good Luck!


Problem	Score	Max Score
1		30
2		20
3		20
4		30
Total		100

Name: SAM PALERMO

UIN: _____


Problem 1 (30 points)

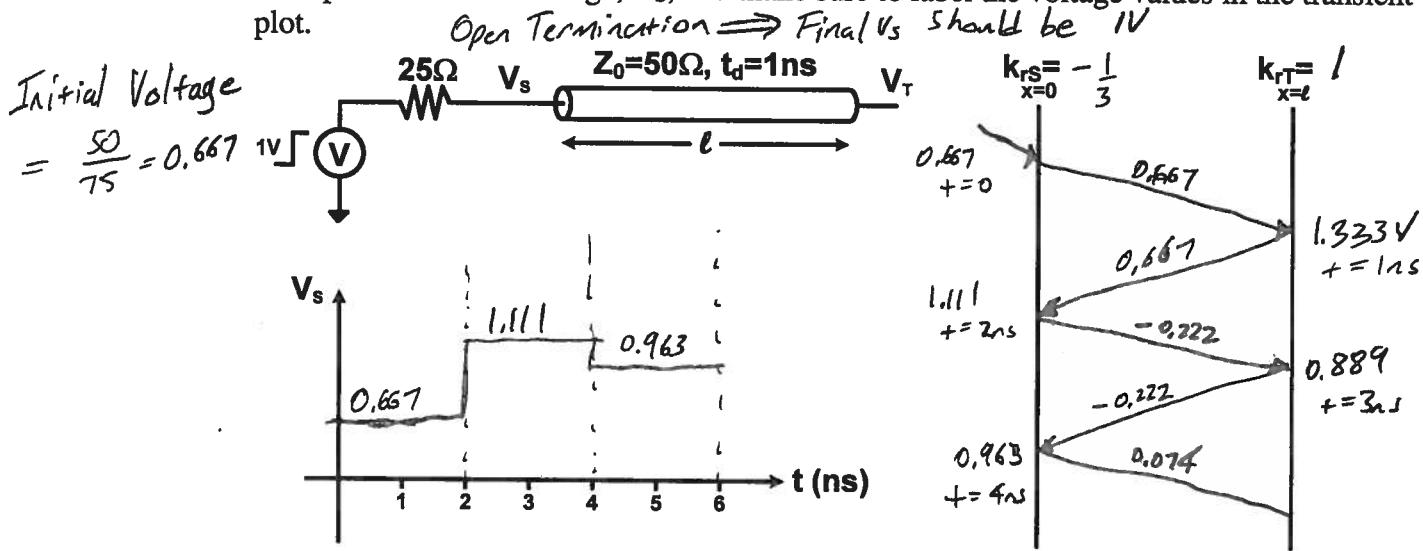- a) A 1V step is launched onto the channel below at $t=0\text{ns}$. (20 points)
- Calculate the reflection coefficient at the source, k_{rs} , and at the end termination, k_{rt}
 - Fill in the lattice diagram below until the source voltage, V_s , has reached to within 100mV of its final value.
 - Also plot the source voltage, V_s , and make sure to label the voltage values in the transient plot.



$$K_{rs} = \frac{Z_s - Z_0}{Z_s + Z_0} = \frac{25 - 50}{25 + 50} = -\frac{1}{3} \quad K_{rt} = \frac{Z_T - Z_0}{Z_T + Z_0} = \frac{\infty - 50}{\infty + 50} = +1$$

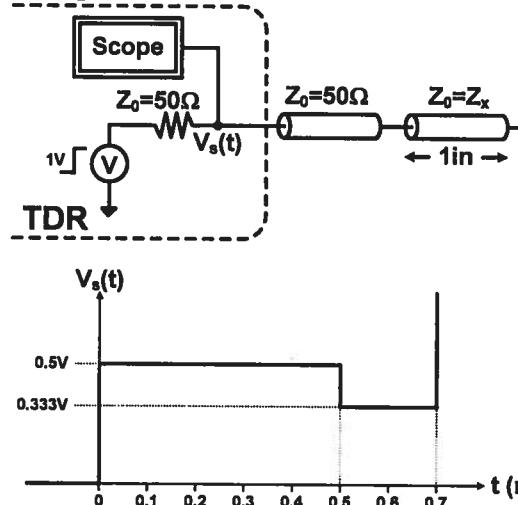- b) An ideal TDR ($t_r \sim 0$) yields the following response with a channel consisting of a 50Ω trace, a 1 inch trace with Z_x impedance, and ends in an open termination. Calculate Z_x and the equivalent L/in and C/in of the 1 inch trace. Assume all traces are loss-less. (15 points)



Z_x impedance discontinuity is detected at TDR at $t = 0.5\text{ns}$

$$Z_x = Z_0 \left(\frac{V(0.5\text{ns})}{IV - V(0.5\text{ns})} \right) = 50\Omega \left(\frac{0.333}{1 - 0.333} \right) = 25\Omega$$

$$Z_x = \sqrt{\frac{L}{C}}$$

$$t_d = \frac{1}{2\pi} = \sqrt{LC} = \frac{200\text{ps}}{2(1\text{in})} = 100 \frac{\text{ps}}{\text{in}}$$

$$\frac{L}{\text{in}} = Z_x + d = \sqrt{\frac{L}{C}} + LC = (25\Omega) \left(100 \frac{\text{ps}}{\text{in}} \right) = 2.5 \frac{\text{nH}}{\text{in}}$$

$$C = \frac{L}{Z_x^2} = \frac{2.5 \frac{\text{nH}}{\text{in}}}{(25\Omega)^2} = 4 \frac{\text{pF}}{\text{in}}$$

$$Z_x = 25\Omega$$

$$L/\text{in} = 2.5 \frac{\text{nH}}{\text{in}}$$


$$C/\text{in} = 4 \frac{\text{pF}}{\text{in}}$$

Problem 2 (20 points)

A channel has the pulse response, $y^{(1)}$, below for a "1" bit.

- Find the channel's worst-case eye height at this bit rate.
- Give the channel's worst-case bit pattern at this bit rate. Make sure to label the cursor in the bit pattern.

$$y^{(1)} = [0.1 \ 0.7 \ -0.1 \ 0.1]$$

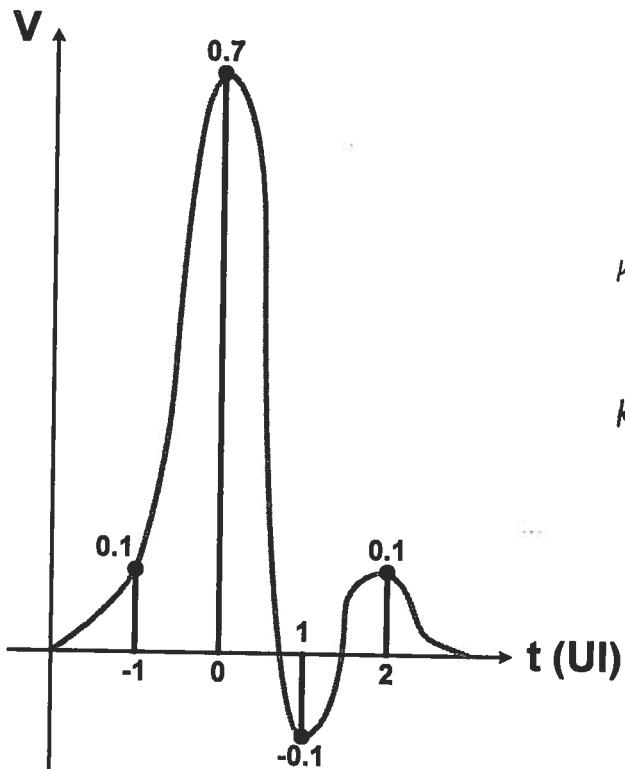

$$y_0^{(1)} = 0.7$$

$$\sum_{k \neq 0} y_k^{(1)} \Big|_{y < 0} = -0.1$$

$$\sum_{k \neq 0} y_k^{(1)} \Big|_{y > 0} = 0.1 + 0.1 = 0.2$$

$$W.C. Eye Height = 2(0.7 - 0.1 - 0.2) = 0.8$$

To find W.C. Bit Pattern : Flip around cursor and invert all but cursor

$$[0.1 \ 0.7 \ -0.1 \ 0.1] \Rightarrow [-0.1 + 0.1 \ 0.7 - 0.1]$$

Then take sign

$$[-0.1 + 0.1 \ 0.7 - 0.1] \Rightarrow [-1 \ 1 \ 1 \ -1]$$

$$\text{Worst-Case Eye Height} = 0.8 \quad \text{Cursors}$$

$$\text{Worst-Case Bit Pattern} = \begin{bmatrix} -1 & 1 & 1 & -1 \end{bmatrix} \quad (\text{Worst-Case } "1")$$

$$\begin{bmatrix} 1 & -1 & -1 & 1 \end{bmatrix} \quad (\text{Worst-Case } "-1")$$

by linearity

Problem 3 (20 points)

For the circuit below, use the following NMOS parameters


$$K_P = \mu_n C_{ox} = 600 \mu A/V^2, V_{TN} = 0.35V, \lambda_N = 0V^{-1}$$

and the following PMOS parameters

$$K_P = \mu_p C_{ox} = 150 \mu A/V^2, V_{TP} = -0.35V, \lambda_P = 0V^{-1}$$

For the current-mode driver below

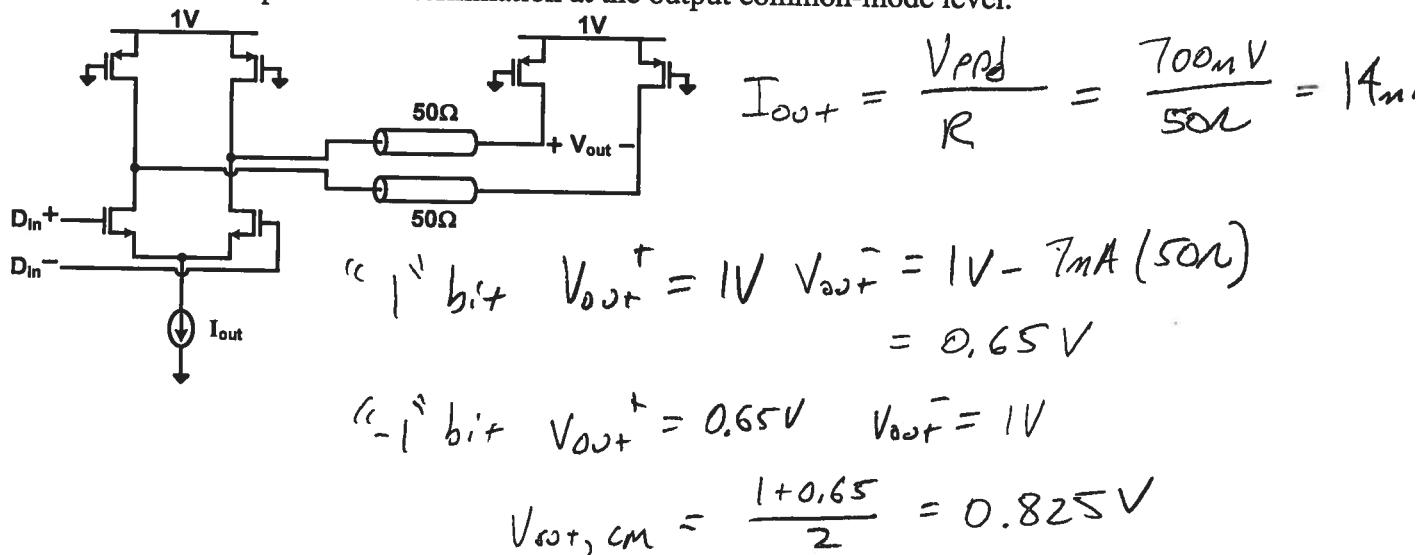- Calculate the tail current I_{out} to generate a peak-to-peak differential voltage output swing of $700mV_{ppd}$.
- Give the common-mode value of the output voltage with the $700mV_{ppd}$ output swing.
- Give the PMOS termination transistors aspect ratios for proper termination. Include V_{SD} effects and optimize the termination at the output common-mode level.



* Sizing PMOS termination at common-mode level

$$R_P = \frac{1}{g_o} = \frac{1}{K_P \frac{W}{L} (V_{SG} - |V_{TP}| - V_{SD})}$$

$$\frac{W}{L} = \frac{1}{R_P K_P (V_{SG} - |V_{TP}| - V_{SD})} = \frac{1}{(50\Omega)(150\mu A/V^2)(1V - 0.35V - 0.175V)}$$

$$I_{out} = 14mA$$


$$V_{out, CM} = 0.825V$$

$$(W/L)_P = 281$$

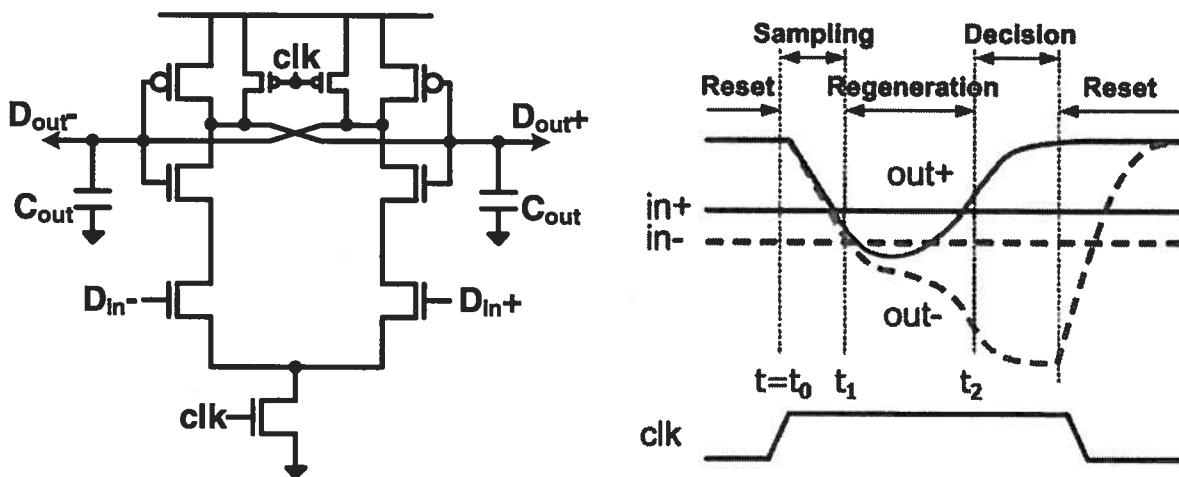Problem 4 (30 points)

This problem involves analyzing the maximum performance of the comparator below. Assume that the **Sample Time**=25ps and the **Sample Gain**=2.

- If the regeneration time constant $\tau_R=15\text{ps}$ and it is required to amplify a 10mV differential input voltage to 500mV for a reliable decision, what is the minimum time required to make a decision ($t_2 - t_0$)?
- Given the effective total regeneration transconductance $g_{mr}=500\mu\text{A/V}$, what is the maximum total output capacitance that the comparator can drive and maintain the 15ps τ_R ?



Sample Gain = 2 \Rightarrow Need to amplify $10\text{mV}(2) = 20\text{mV} + 0$
 $500\text{mV} \Rightarrow$ Need a regeneration time

$$\tau_R \ln(g_R) = 15\text{ps} \ln\left(\frac{500\text{mV}}{20\text{mV}}\right) = 48.3\text{ps}$$


$$\begin{aligned} \text{Decision Time} &= \text{Sample Time} + \text{Regeneration Time} \\ &= 25\text{ps} + 48.3\text{ps} = 73.3\text{ps} \end{aligned}$$

$$\text{Max } C_{out} = g_{mr} \tau_R = (500\mu\text{A/V})(15\text{ps}) = 7.5\text{fF}$$

$$\text{Min } (t_2 - t_0) = 73.3\text{ps}$$

$$\text{Max } C_{out} = 7.5\text{fF}$$

Key MOS Equations & Scratch Paper

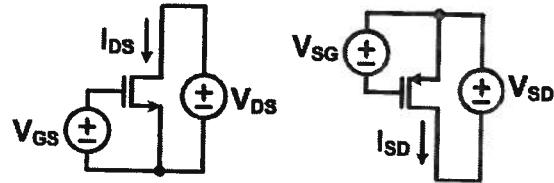

$$\text{Saturation: NMOS } I_{DS} = \frac{1}{2} K P_N \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$\text{Saturation: PMOS } I_{SD} = \frac{1}{2} K P_P \frac{W}{L} (V_{SG} - |V_{TP}|)^2$$

$$\text{Triode: NMOS } I_{DS} = K P_N \frac{W}{L} \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$\text{Triode: PMOS } I_{SD} = K P_P \frac{W}{L} \left(V_{SG} - |V_{TP}| - \frac{V_{SD}}{2} \right) V_{SD}$$

$$\text{NMOS } g_m = \frac{\partial I_{DS}}{\partial V_{GS}}, \quad \text{PMOS } g_m = \frac{\partial I_{SD}}{\partial V_{SG}}$$

$$\text{NMOS } g_o = \frac{\partial I_{DS}}{\partial V_{DS}}, \quad \text{PMOS } g_o = \frac{\partial I_{SD}}{\partial V_{SD}}$$