

**Texas A&M University  
Department of Electrical and Computer Engineering**

**ECEN 720 – High-Speed Links**

**Spring 2023**

**Exam #1**

**Instructor: Sam Palermo**

- Please write your name in the space provided below
- Please verify that there are 7 pages in your exam
- Good Luck!

Problem	Score	Max Score
1		30
2		20
3		25
4		25
<b>Total</b>		<b>100</b>


Name: SAM PALERMO

UIN: \_\_\_\_\_

Problem 1 (30 points)

a) A 1V step is launched onto the channel below at  $t=0$ ns. (20 points)

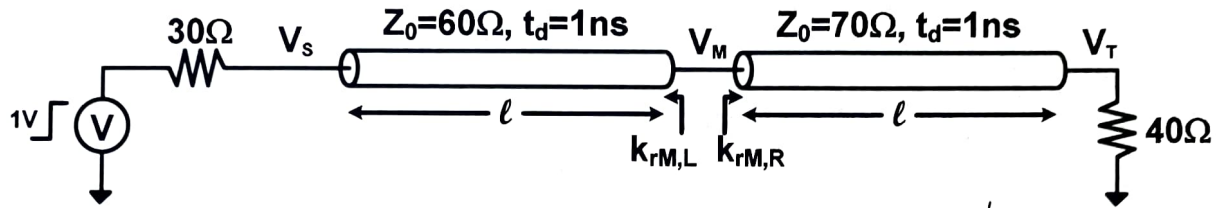- i. Calculate the reflection coefficient at the source,  $k_{rS}$ , at the middle point for right traveling signals,  $k_{rM,R}$ , and left traveling signals,  $k_{rM,L}$ , and the end termination,  $k_{rT}$
- ii. Fill in the lattice diagram below until  $t=4$ ns.
- iii. Also plot the source voltage,  $V_S$ , and the termination voltage,  $V_T$  until 4ns.






$$k_{rS} = \frac{30 - 60}{30 + 60} = -\frac{1}{3}$$

$$k_{rM,L} = \frac{60 - 70}{60 + 70} = -\frac{1}{13}$$


$$k_{rM,R} = \frac{70 - 60}{70 + 60} = \frac{1}{13}$$

$$k_{rT} = \frac{40 - 70}{40 + 70} = -\frac{3}{11}$$

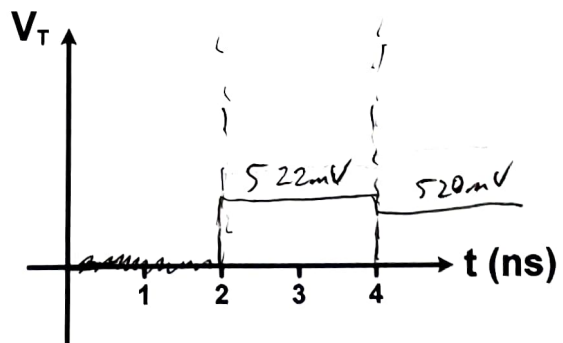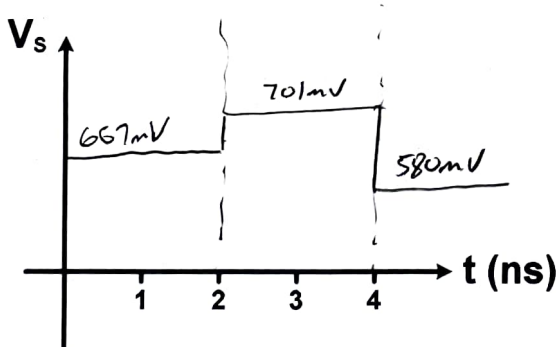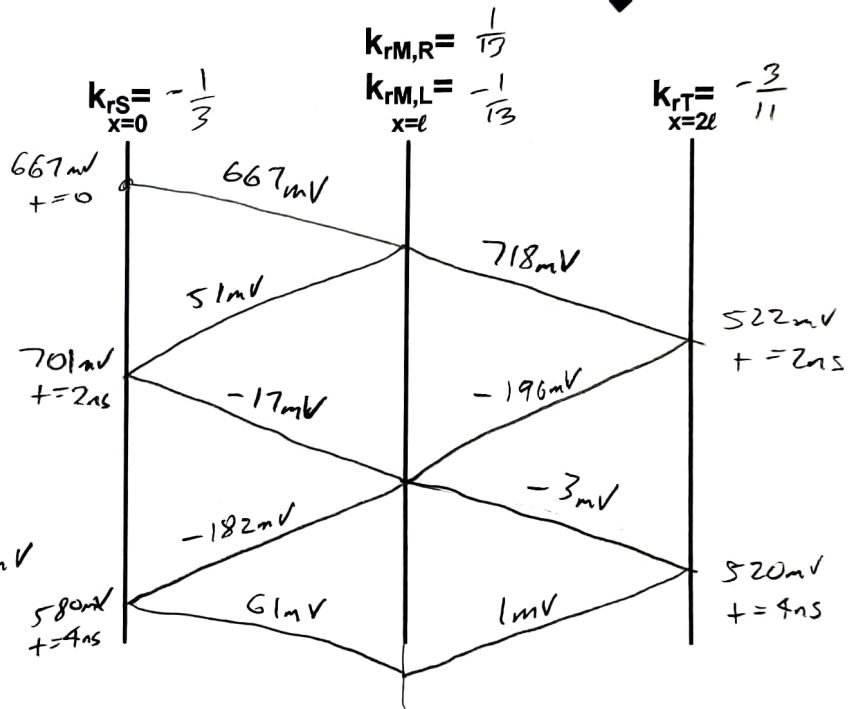
$$V_{\text{Initial Voltage}} = \frac{60}{30 + 60} (1V) = 667mV$$



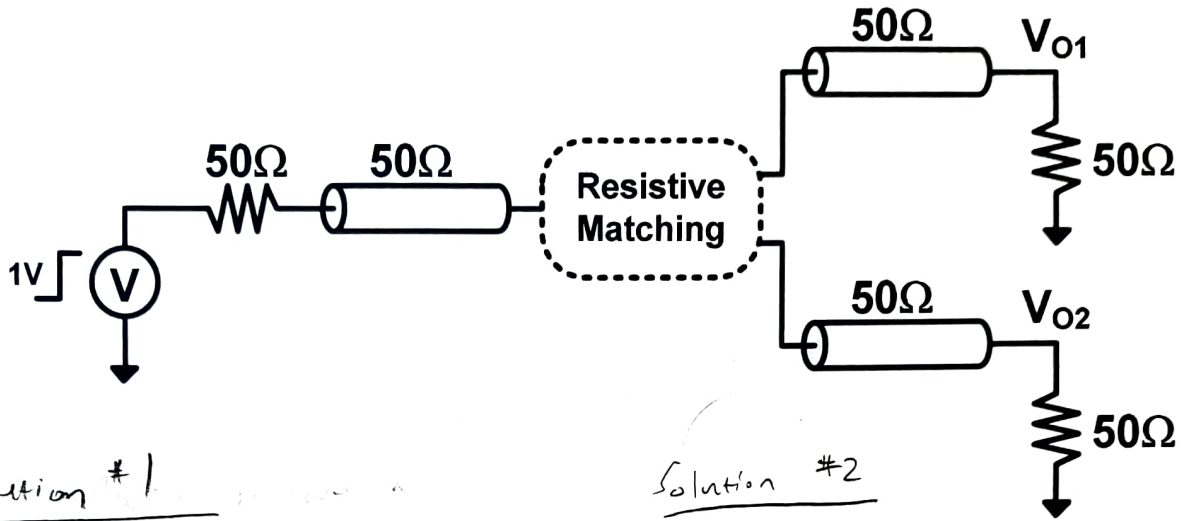- b) For the circuit below, design a three-terminal resistive matching network to eliminate any reflections in any direction and make  $V_{O1}=V_{O2}$ . If a 1V step is launched onto the network, what is the step value at the two outputs? (10 points)



Solution #1

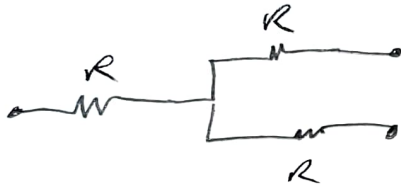


$$R + (R+50) \parallel (R+50) = 50$$

$$R + \frac{R+50}{2} = 50$$

$$3R = 50$$

$$R = 16.7\Omega$$

Solution #2

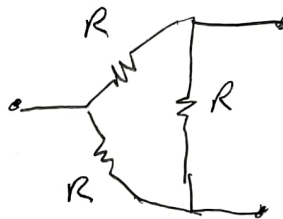


$$R + (R+50) \parallel (R+50) = 50$$

$$\frac{R+50}{2} = 50$$

$$R = 50$$

Equivalent Circuit

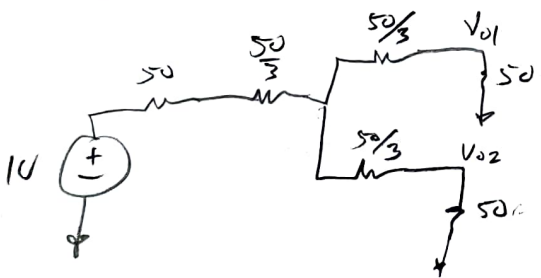

$$V_{O1} = V_{O2} = \frac{\left(\frac{50}{50 + \frac{50}{3}}\right) \left(\frac{50 + \frac{50}{3}}{2}\right)}{50 + \frac{50}{3} + \frac{50 + \frac{50}{3}}{2}} = 0.25V$$

Equivalent Circuit




$$V_{O1} = V_{O2} = \frac{\left(\frac{50}{50 + 50}\right) \left(\frac{50 + 50}{2}\right)}{50 + \frac{50 + 50}{2}} = 0.25V$$

Problem 2 (20 points)

A channel has the pulse response,  $y^{(1)}$ , below for a "1" bit.

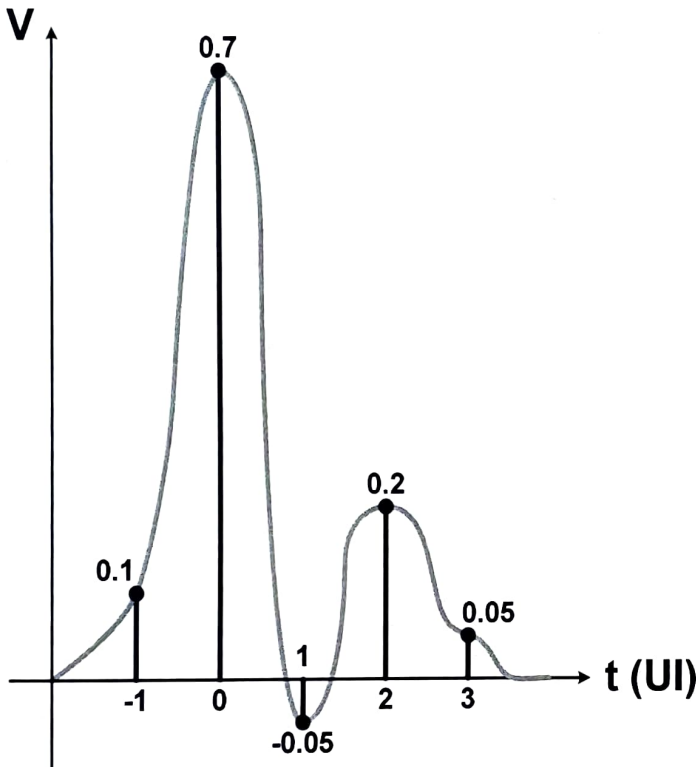- a. Find the channel's worst-case eye height at this bit rate.
- b. Give the channel's worst-case bit pattern at this bit rate.

$y^{(1)} = [0.1 \ 0.7 \ -0.05 \ 0.2 \ 0.05]$



$y_0^{(1)} = 0.7$

$\sum_{k \neq 0} y^{(k)} \Big|_{y < 0} = -0.05$

$\sum_{k \neq 0} y^{(k)} \Big|_{y > 0} = 0.1 + 0.2 + 0.05 = 0.35$

W.L. Eye Height =  $2(0.7 - 0.05 - 0.35) = 0.6$

To Find W.C. Bit Pattern: Flip around cursor and invert all but cursor

$[0.1 \ 0.7 \ -0.05 \ 0.2 \ 0.05] \Rightarrow [-0.05 \ -0.2 \ 0.05 \ 0.7 \ -0.1]$

Then take sign

$[-0.05 \ -0.2 \ 0.05 \ 0.7 \ -0.1] \Rightarrow [-1 \ -1 \ 1 \ 1 \ -1]$


Worst-Case Eye Height = 0.6      Cursors

Worst-Case Bit Pattern =  $[-1 \ -1 \ 1 \ 1 \ -1]$       Worst-case "1"

$[1 \ 1 \ -1 \ -1 \ 1]$       Worst-case "0"

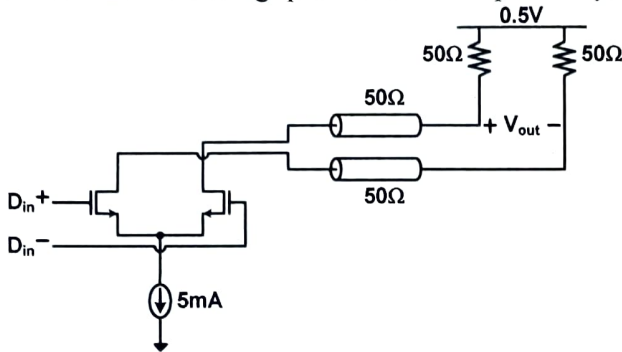Problem 3 (25 points)

Answer the following questions for the pull-only, differential current-mode driver shown below.



- a. What is the peak-to-peak differential output swing,  $V_{d,1} - V_{d,0}$  ?
- b. What is the average power consumption of the driver?


$$V_{d,1} - V_{d,0} = IR - (-IR) = 2IR = 2(5mA)(50\Omega) = 500mV$$

$$V_{out,dpp} = V_{d,1} - V_{d,0} = 500mV$$

$$P_{avg} = 5mA(0.5V) = 2.5mW$$

$$\text{Average Power} = 2.5mW$$

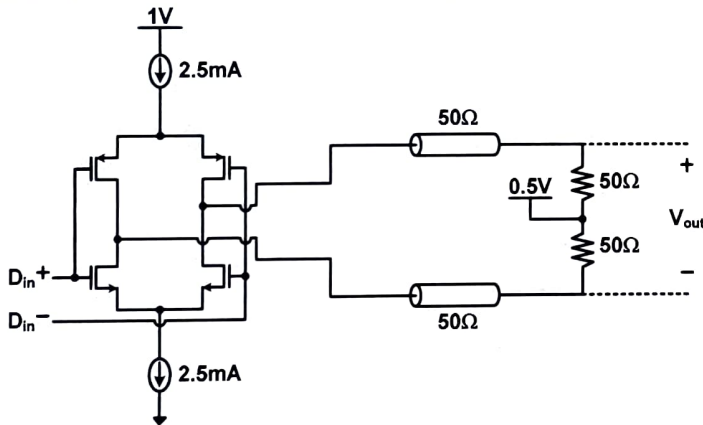Now consider the push-pull differential current-mode driver shown below. **Note that the bias current has been reduced from 5mA to 2.5mA.**



$$V_{d,1} - V_{d,0} =$$

$$2IR - (-2IR) = 4IR$$

$$= 4(2.5mA)(50\Omega) = 500mV$$

- c. What is the peak-to-peak differential output swing,  $V_{d,1} - V_{d,0}$  ?
- d. What is the average power consumption of the driver?

$$P_{avg} = 2.5mA(1V) = 2.5mW$$

$$V_{out,dpp} = V_{d,1} - V_{d,0} = 500mV$$

$$\text{Average Power} = 2.5mW$$


- e. Why doesn't this push-pull driver dissipate half the power of the pull-only driver, for the same signal swing? In particular, explain the factor that constrains the supply voltage (1V) or the termination voltage (0.5V).

For the push-pull driver, we need both the top (PMOS) and the bottom (NMOS) current sources to stay in saturation. Thus, we need about 5 times the supply voltage.

Problem 4 (25 points)

The NMOS sampler below is used to sample a 5GHz sinusoidal signal at  $t=0$ . Assume that the sampler displays the triangular sampling function,  $h(t)$ .

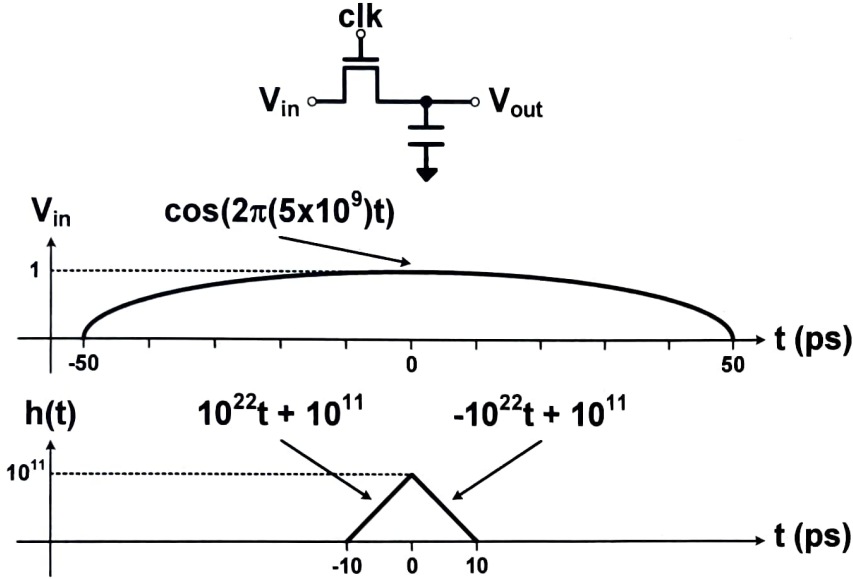- i. Setup, **but do not calculate**, the integral expression for the sampled output voltage.
- ii. Calculate the sampler aperture time from the sampling function. Assume that the aperture time is defined as the time where 80% of the sampler sensitivity is confined.




i. Sampled  $V_{out} = \int_{-\infty}^{\infty} V_{in}(t) h(t) dt$

$$= \int_{-10ps}^0 \cos(2\pi(5 \times 10^9)t) [10^{22}t + 10^{11}] dt + \int_0^{10ps} \cos(2\pi(5 \times 10^9)t) [-10^{22}t + 10^{11}] dt$$

ii. Need to find how much time = 10% of area or 0.1 because

$$\int_{-\infty}^{\infty} h(t) dt = 1$$

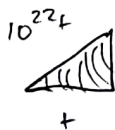


Area = 0.1  $\frac{1}{2}(10^{22}t)(t) = 0.1 \Rightarrow t = 4.47ps$  for 10% area

Aperture time =  $20ps - 2(4.47ps)$

= 11.1ps

### Key MOS Equations & Scratch Paper

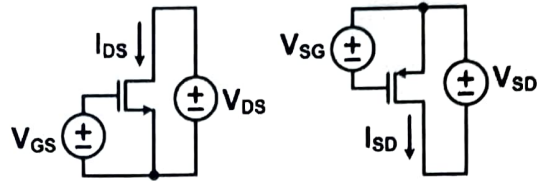

$$\text{Saturation: NMOS } I_{DS} = \frac{1}{2} K P_N \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$\text{Saturation: PMOS } I_{SD} = \frac{1}{2} K P_P \frac{W}{L} (V_{SG} - |V_{TP}|)^2$$

$$\text{Triode: NMOS } I_{DS} = K P_N \frac{W}{L} \left( V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$\text{Triode: PMOS } I_{SD} = K P_P \frac{W}{L} \left( V_{SG} - |V_{TP}| - \frac{V_{SD}}{2} \right) V_{SD}$$

$$\text{NMOS } g_m = \frac{\partial I_{DS}}{\partial V_{GS}}, \quad \text{PMOS } g_m = \frac{\partial I_{SD}}{\partial V_{SG}}$$

$$\text{NMOS } g_o = \frac{\partial I_{DS}}{\partial V_{DS}}, \quad \text{PMOS } g_o = \frac{\partial I_{SD}}{\partial V_{SD}}$$