

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 720 – High-Speed Links

Spring 2025

Exam #1

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are 6 pages in your exam
- Good Luck!

Problem	Score	Max Score
1		30
2		30
3		20
4		20
Total		100

Name: SAM PALERMO




UIN: _____

Problem 1 (30 points)



a) A 1V step is launched onto the channel below at $t=0$ ns. (20 points)

   - i. Calculate the reflection coefficient at the source, k_{rS} , and at the end termination, k_{rT}
- ii. Fill in the lattice diagram below until the source voltage, V_S , has reached to within 100mV of its final value.
- iii. Also plot the source voltage, V_S , and make sure to label the voltage values in the transient plot.



Initial Voltage
 $1V \left(\frac{50}{150} \right) = 0.333V$



  b) For the circuit below, design a resistive matching network to eliminate any reflections of the forward traveling wave originating from the source, V_S , and also produce an output voltage $V_T=0.5V$ with a 1V input step. (10 points)



Solution #1

  

*To make $V_T = 0.5V \Rightarrow R_B = 75\Omega$

*To satisfy no reflections

$$R_A \parallel (R_B + 75) = 50$$

$$\frac{R_A(150)}{R_A + 150} = 50$$


$$R_A = 75\Omega$$

Problem 2 (30 points)

A channel has the pulse response, $y^{(1)}$, below for a "1" symbol.

- Find the channel's worst-case eye height at this bit rate for **PAM2** modulation.
- Give the channel's worst-case **PAM2** bit pattern at this bit rate. Make sure to label the cursor in the bit pattern.
- Find the channel's worst-case eye height at this symbol rate for **PAM4** modulation.
 
$$y^{(1)} = [0.6 \quad 0.25 \quad 0.1 \quad 0.05]$$



$$y_0^{(1)} = 0.6$$

$$\sum_{k \neq 0} y_k^{(1)} \Big|_{y < 0} = \phi$$

$$\sum_{k \neq 0} y_k^{(1)} \Big|_{y > 0} = 0.25 + 0.1 + 0.05 = 0.4$$

PAM2 W.C. Eye Height

$$2(0.6 - 0.4) = 0.4$$

PAM2 W.C. Bit Pattern

$$[0.6 \quad 0.25 \quad 0.1 \quad 0.05] \Rightarrow \begin{bmatrix} -0.05 & -0.1 & -0.25 & 0.6 \\ & & & \uparrow \text{cursor} \\ -1 & -1 & -1 & 1 \end{bmatrix}$$

$$\text{PAM4 W.C. Eye Height} : 2\left(\frac{0.6}{3} - 0.4\right) = -0.4$$

PAM2 Worst-Case Eye Height = 0.4


PAM2 Worst-Case Bit Pattern = $[-1 \quad -1 \quad -1 \quad 1]$ (Worst case "1")

PAM4 Worst-Case Eye Height = -0.4

 Problem 3 (20 points)

Answer the following questions for the current-mode driver below

- Calculate the tail current I_{out} to generate a peak-to-peak differential voltage output swing of $0.6V_{ppd}$.
- Give the common-mode value of the output voltage with the $0.6V_{ppd}$ output swing.



$$I_{out} = \frac{V_{ppd}}{R} = \frac{0.6V}{50\Omega} = 12mA$$

During "1" bit $V_{out}^+ = 0.85V$ $V_{out}^- = 0.55V$
 "0" bit $V_{out}^+ = 0.55V$ $V_{out}^- = 0.85V$

$$V_{out,CM} = \frac{0.85 + 0.55}{2} = 0.7V$$

$$I_{out} = 12mA$$

$$V_{out,CM} = 0.7V$$

Problem 4 (20 points)

For the circuit below, use the following NMOS parameters


$$K_{PN} = \mu_n C_{ox} = 600 \mu A/V^2, V_{TN} = 0.35V, \lambda_N = 0V^{-1}$$

and the following PMOS parameters

$$K_{PP} = \mu_p C_{ox} = 150 \mu A/V^2, V_{TP} = -0.35V, \lambda_P = 0V^{-1}$$

For the current-mode driver below

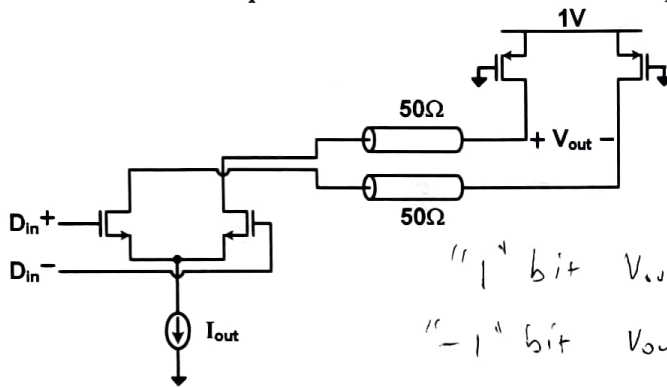- i. Calculate the tail current I_{out} to generate a peak-to-peak differential voltage output swing of $600mV_{ppd}$.
- ii. Give the common-mode value of the output voltage with the $600mV_{ppd}$ output swing.
- iii. Give the PMOS termination transistors aspect ratios for proper termination. Include V_{SD} effects and optimize the termination at the output common-mode level.




$$I_{out} = \frac{V_{ppd}}{2R} = \frac{600mV}{2(50)} = 6mA$$

"1" bit $V_{out}^- = 1V, V_{out}^+ = 1V - 6mA(50\Omega) = 0.7V$
 "-1" bit $V_{out}^+ = 0.7V, V_{out}^- = 1V$

$$V_{out,CM} = \frac{1+0.7}{2} = 0.85V$$

 * Sizing PMOS termination at common-mode level



$$R_p = \frac{1}{g_o} = \frac{1}{K_{PP} \frac{W}{L} (V_{GS} - |V_{TP}| - V_{SD})}$$

$$\left(\frac{W}{L}\right)_p = \frac{1}{R_p K_{PP} (V_{GS} - |V_{TP}| - V_{SD})} = \frac{1}{(50\Omega)(150\mu A/V^2)(1V - 0.35V - 0.15V)}$$


$$= 267$$

$$I_{out} = 6mA$$

$$V_{out,CM} = 0.85V$$

$$(W/L)_p = 267$$

Key MOS Equations & Scratch Paper

 

$$\text{Saturation: NMOS } I_{DS} = \frac{1}{2} K P_N \frac{W}{L} (V_{GS} - V_{TN})^2$$

$$\text{Saturation: PMOS } I_{SD} = \frac{1}{2} K P_P \frac{W}{L} (V_{SG} - |V_{TP}|)^2$$

$$\text{Triode: NMOS } I_{DS} = K P_N \frac{W}{L} \left(V_{GS} - V_{TN} - \frac{V_{DS}}{2} \right) V_{DS}$$

$$\text{Triode: PMOS } I_{SD} = K P_P \frac{W}{L} \left(V_{SG} - |V_{TP}| - \frac{V_{SD}}{2} \right) V_{SD}$$

$$\text{NMOS } g_m = \frac{\partial I_{DS}}{\partial V_{GS}}, \quad \text{PMOS } g_m = \frac{\partial I_{SD}}{\partial V_{SG}}$$

$$\text{NMOS } g_o = \frac{\partial I_{DS}}{\partial V_{DS}}, \quad \text{PMOS } g_o = \frac{\partial I_{SD}}{\partial V_{SD}}$$