

Texas A&M University
Department of Electrical and Computer Engineering

ECEN 720 – High-Speed Links

Spring 2023

Exam #2

Instructor: Sam Palermo

- Please write your name in the space provided below
- Please verify that there are 7 pages in your exam
- Good Luck!

| Problem | Score | Max Score |
|--------------|-------|------------|
| 1 | | 35 |
| 2 | | 30 |
| 3 | | 35 |
| Total | | 100 |

Name: _____

SAM PALERMO



UIN: _____

TABLE 13-1. Q_{BER} as a Function of the Bit Error Rate

| BER | Q_{BER} | BER | Q_{BER} | BER | Q_{BER} |
|--------------------|------------------|---------------------|------------------|-----------------------|------------------|
| 1×10^{-3} | 6.180 | 1×10^{-10} | 12.723 | 1×10^{-17} | 16.987 |
| 1×10^{-4} | 7.438 | 1×10^{-11} | 13.412 | 1×10^{-18} | 17.514 |
| 1×10^{-5} | 8.530 | 1×10^{-12} | 14.069 | 1×10^{-19} | 18.026 |
| 1×10^{-6} | 9.507 | 1×10^{-13} | 14.698 | 1×10^{-20} | 18.524 |
| 1×10^{-7} | 10.399 | 1×10^{-14} | 15.301 | 1×10^{-21} | 19.010 |
| 1×10^{-8} | 11.224 | 1×10^{-15} | 15.882 | 1×10^{-22} | 19.484 |
| 1×10^{-9} | 11.996 | 1×10^{-16} | 16.444 | 7.7×10^{-24} | 20.000 |

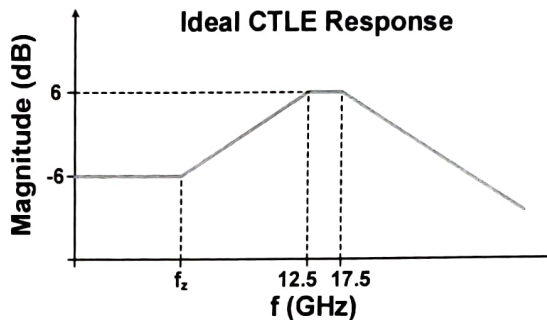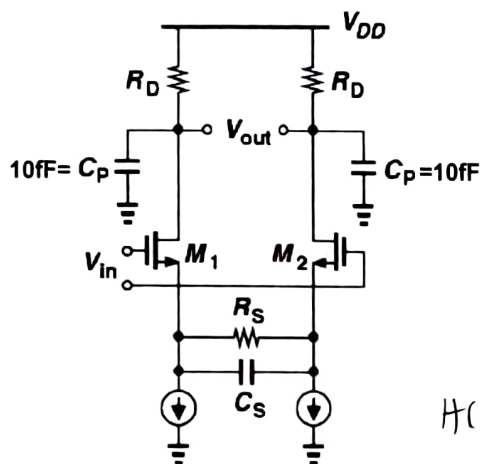Problem 1 (35 points)

This problem involves the design of an active continuous-time linear equalizer (CTLE) for a 25Gb/s system. The CTLE should have a bandwidth of 17.5GHz, an ideal peaking at 12.5GHz that is 12dB higher than the low-frequency gain of -6dB. Assuming the maximum zero frequency, give the input transistor's g_m and the values for R_D , R_S , and C_S . You can neglect all of the transistor capacitors, i.e. only consider capacitors that are explicitly drawn in your analysis. Also assume that all transistors operate in the saturation region and have infinite output resistance.



$$H(s) = \left(\frac{g_m}{C_p} \right) \frac{s + \frac{1}{R_D C_p}}{\left(s + \frac{1 + g_m R_S / 2}{R_S C_S} \right) \left(s + \frac{1}{R_D C_p} \right)}$$

$$\omega_{p2} = 2\pi f_{p2} = \frac{1}{R_D C_p} \Rightarrow R_D = \frac{1}{2\pi f_{p2} C_p} = \frac{1}{2\pi (17.5 \text{ GHz}) (10 \text{ fF})} = 910 \Omega$$

$$\text{Ideal Peaking} = \frac{\omega_{p1}}{\omega_z} = 12 \text{ dB} = 4 \Rightarrow \omega_z = \frac{\omega_{p1}}{4} = \frac{2\pi (12.5 \text{ GHz})}{4} = 2\pi (3.125 \text{ GHz})$$

$$\text{Gain BW} = A_{DC} \frac{\omega_{p1}}{\omega_z} \omega_{p2} = \frac{1}{2} (4) (2\pi 17.5 \text{ GHz}) = 2\pi (35 \text{ GHz})$$

$$\frac{g_m}{C_p} = 2\pi (35 \text{ GHz}) \Rightarrow g_m = 2\pi (35 \text{ GHz}) (10 \text{ fF}) = 2.2 \text{ mA/V}$$

$$\text{DC gain} = \frac{g_m R_D}{1 + \frac{g_m R_S}{2}} = \frac{1}{2} \Rightarrow R_S = \frac{\left(g_m R_D - \frac{1}{2} \right) 4}{g_m} = \frac{6}{g_m} = 2.73 \text{ k}\Omega$$

$$R_D = 910 \Omega$$

$$R_S = 2.73 \text{ k}\Omega$$

$$C_S = 18.7 \text{ fF}$$

$$\omega_z = \frac{1}{R_S C_S} \Rightarrow C_S = \frac{1}{R_S \omega_z} = \frac{1}{(2.73 \text{ k}\Omega) (2\pi) (3.125 \text{ GHz})} = 18.7 \text{ fF}$$

- i. If I want to decrease the ideal peaking ratio to 6dB without changing the first pole, ω_{p1} , how should I change the CTLE?

$$\text{ideal peaking ratio} = 1 + \frac{g_m R_s}{2} = 2$$

$$\Rightarrow \text{Change } R_s \text{ to } R_s = \frac{2}{g_m} = \frac{2}{2.2 \text{ mA/V}} = 910 \Omega$$

However, this will have some impact on ω_{p1} , so we need to

change C_s also

$$\omega_{p1} = \frac{1 + g_m R_s / 2}{R_s C_s} \Rightarrow C_s = \frac{1 + g_m R_s / 2}{R_s \omega_{p1}} = \frac{2}{(910 \Omega)(2\pi)(125 \text{ GHz})}$$

$$\boxed{\begin{array}{l} R_s = 910 \Omega \\ C_s = 28 \text{ fF} \end{array}}$$

- ii. If I want to move the zero frequency f_z to 1GHz without impacting the original ideal peaking ratio of 12dB, how should I change the CTLE?

$$\begin{aligned} \text{Ideal Peaking Ratio} &= \frac{\omega_{p1}}{\omega_z} = \frac{1 + \frac{g_m R_s}{2}}{R_s C_s} (R_s C_s) \\ &= 1 + \frac{g_m R_s}{2} \end{aligned}$$

$$\omega_z = \frac{1}{R_s C_s} \Rightarrow \text{Can tune } C_s \text{ w/o impacting peaking}$$

$$C_s = \frac{1}{R_s \omega_z} = \frac{1}{(2.73 \text{ k}\Omega)(2\pi)(1 \text{ GHz})}$$


$$\boxed{C_s = 58.3 \text{ fF}}$$

Problem 2 (30 points)

This problem involves the voltage noise budgeting of a serial link system. Here we will conservatively assume that all distributions combine in a worst-case manner. The system consists of a transmitter with a 3-tap FIR filter which sends NRZ bits over a channel to a receiver modeled as a simple amplifier followed by a comparator. Each receiver block has a noise component which should be referred to the receiver input.

Attenuation = $1 - \sum k_n = 1 - 0.7 = 0.3$

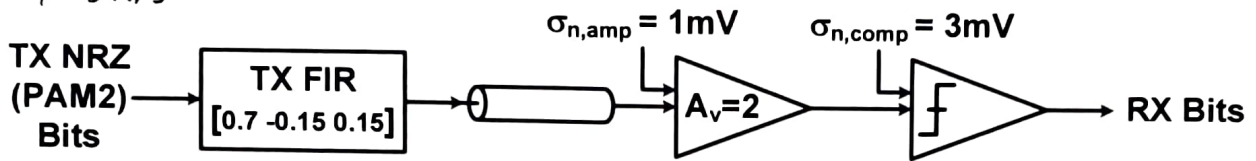$\sigma_{RN} = \sqrt{1.2^2 + (\frac{3}{2})^2} = 1.81mV$



Complete the following noise budget table assuming a TX peak differential swing of $0.5V_{ppd}$ and a target $BER=10^{-15}$. You can refer to the Q_{BER} table on page 2 if needed. (10 points)

| Parameter | K_n | RMS | Value (BER= 10^{-15}) |
|--------------------------------------|-------|----------|--------------------------|
| Peak Differential Swing, V_{swing} | | | 0.5V |
| RX Offset + Sensitivity | | | 5mV |
| Power Supply Noise | | | 10mV |
| Residual ISI | 0.05 | | = 25mV |
| Crosstalk | 0.05 | | = 25mV |
| Random Noise | | = 1.81mV | = 28.7mV |
| Attenuation (TX FIR) | = 0.3 | | = 150mV |
| Total Noise | | | = 243.7mV |
| Differential Eye Height Margin | | | = 256.3mV |

What is the minimum peak differential swing, V_{swing} , for a $BER=10^{-15}$, i.e. as the differential eye height margin goes to zero?

$V_{swing}(1 - \sum k_n) \geq \text{Fixed Noise}$

$V_{swing} \geq \frac{\text{Fixed Noise}}{1 - \sum k_n} = \frac{43.7mV}{1 - 0.4} = 72.8mV$

What is the minimum peak differential swing, V_{swing} , for a $BER=10^{-12}$, i.e. as the differential eye height margin goes to zero?


Fixed noise decreases due to consideration of less

For $BER=10^{-12} \Rightarrow RN = 14.069(1.81mV) = 25.5mV$ random noise

$V_{swing} \geq \frac{40.5mV}{1 - 0.4} = 67.5mV$

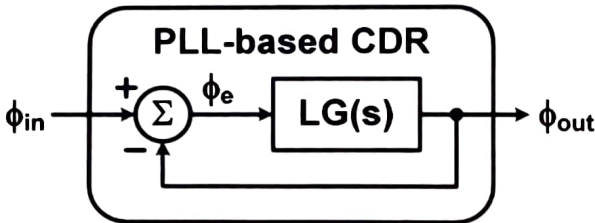Problem 3 (35 points)

This problem investigates a simple PLL-based CDR which can be modeled by the simplified transfer function below. Assume that the only source of random noise in the PLL-based CDR below is from the VCO, which has $\kappa = 5 \times 10^{-9} \sqrt{s}$ and the PLL has a loop bandwidth $f_L = 10\text{MHz}$. What is the **self-referenced accumulated rms jitter**, $\sigma_T = \sqrt{2}\sigma_x$?



$$\sigma_T = \sqrt{2} \sigma_x = \kappa \sqrt{\Delta T} = \kappa \sqrt{\frac{1}{2\pi f_L}}$$

$$= 5 \times 10^{-9} \sqrt{5} \sqrt{\frac{1}{2\pi(10\text{MHz})}} = 631\text{fs}$$

$$\frac{\phi_{out}(s)}{\phi_{in}(s)} = \frac{LG(s)}{1 + LG(s)} \approx \frac{1}{1 + \frac{s}{2\pi f_L}}$$

$$\sigma_T = 631\text{fs}$$

Assume that the PLL is used in a 25Gb/s NRZ half-rate system and the 12.5GHz VCO has a duty cycle error of $\pm 1\text{ps}$ which you can model as a deterministic jitter component, $DJ = 2\text{ps}$. Including this DJ and the **transmit-clock referenced** σ_x above, what is the 25Gb/s timing margin for a $BER = 10^{-15}$?


$$\text{Total jitter (BER} = 10^{-15}) = DJ + Q\sigma_x = 2\text{ps} + 15.882 \left(\frac{631\text{fs}}{\sqrt{2}} \right) = 9.09\text{ps}$$

$$\text{Timing Margin} = 40\text{ps} - 9.09\text{ps} = 30.91\text{ps}$$

$$= 0.77\text{UI}$$

$$25\text{Gb/s timing margin (BER} = 10^{-15}) = 30.91\text{ps}$$

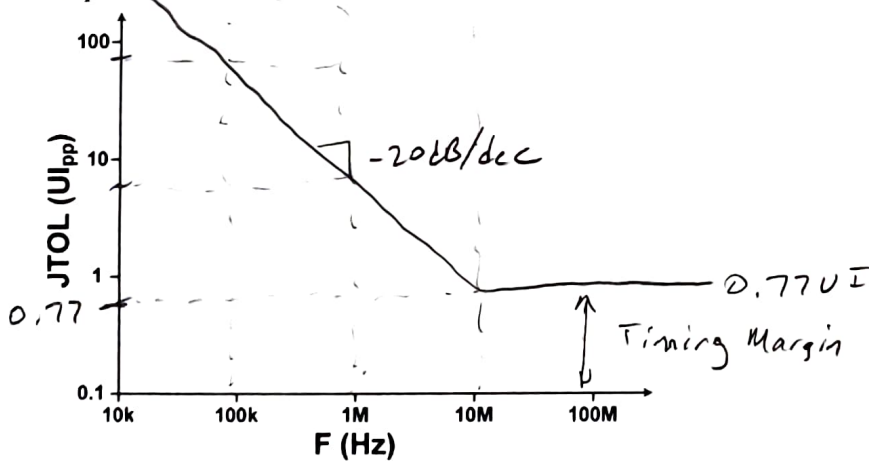Using this timing margin value and assuming that the input data has ONLY a sinusoidal jitter component, sketch the jitter tolerance plot versus frequency. Label the high frequency timing margin and the key frequencies and slopes in the plot.



$$JTOL(s) = \frac{TM}{1 - \frac{D_{jitter}(s)}{\Phi_{in}(s)}}$$