

ECEN689: Special Topics in High-Speed Links Circuits and Systems Spring 2010

Lecture 11: Transmitter Circuits



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University


Announcements

- Exam 1 is tentatively scheduled for March 12
- Homework 3 will be posted tomorrow
- Reading
 - Dally 11.1-11.3

Agenda


- Transmitter circuits
 - Current-mode drivers
 - Voltage-mode drivers
 - Slew rate control

High-Speed Electrical Link System

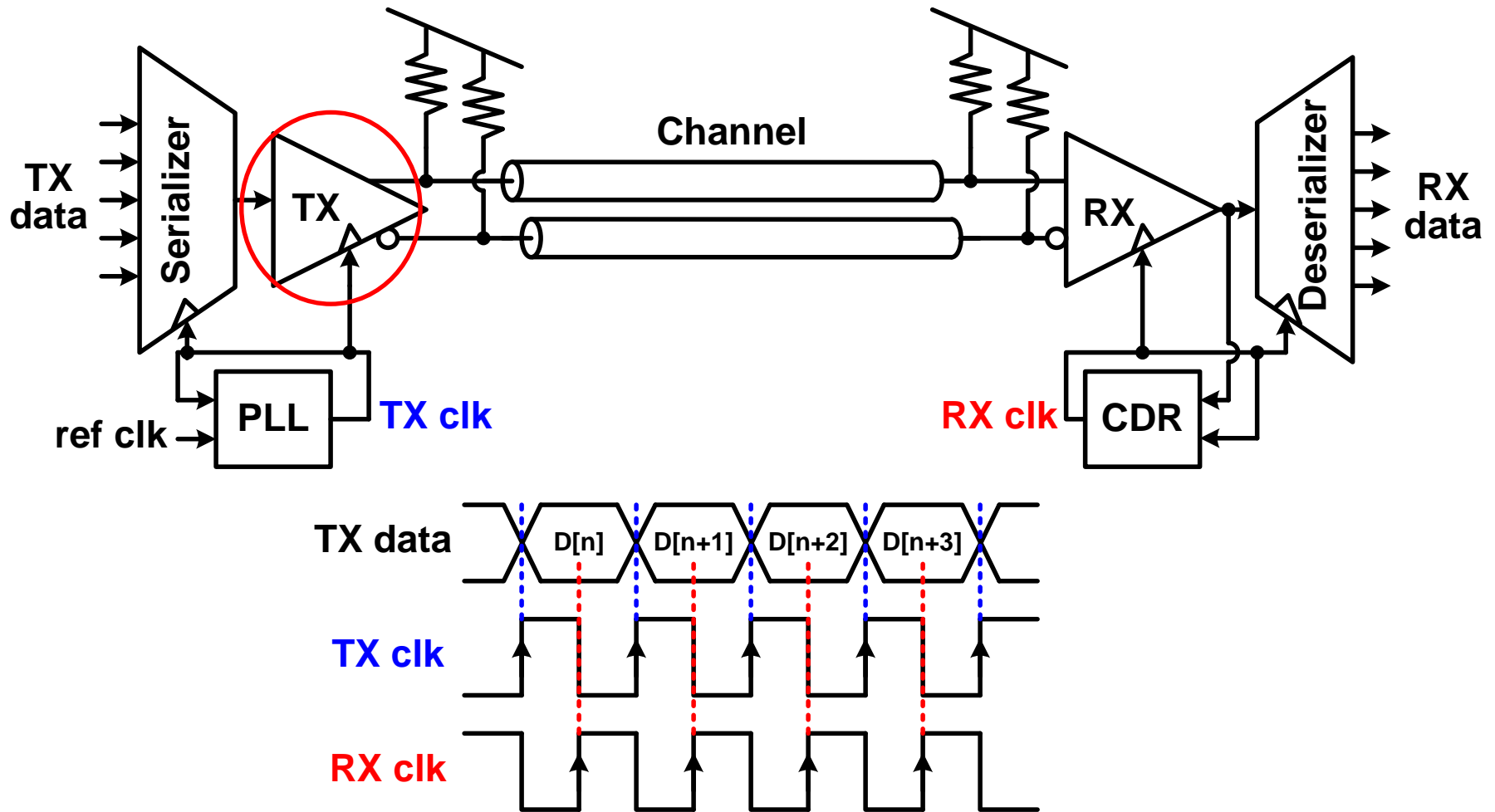


Current vs Voltage-Mode Driver

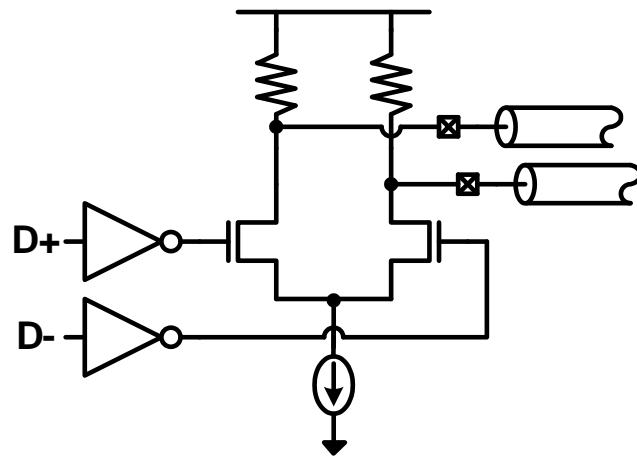- Signal integrity considerations (min. reflections) requires 50Ω driver output impedance
- To produce an output drive voltage
 - Current-mode drivers use Norton-equivalent parallel termination
 - Easier to control output impedance
 - Voltage-mode drivers use Thevenin-equivalent series termination
 - Potentially $\frac{1}{2}$ to $\frac{1}{4}$ the current for a given output swing




Current-Mode

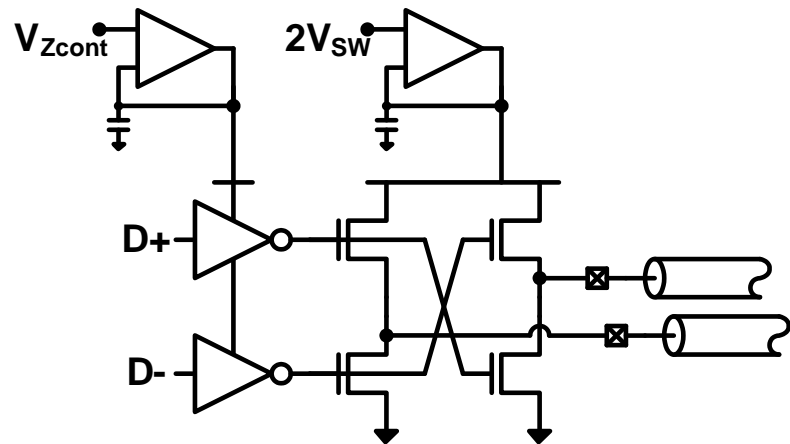


Voltage-Mode

Push-Pull Current-Mode Driver

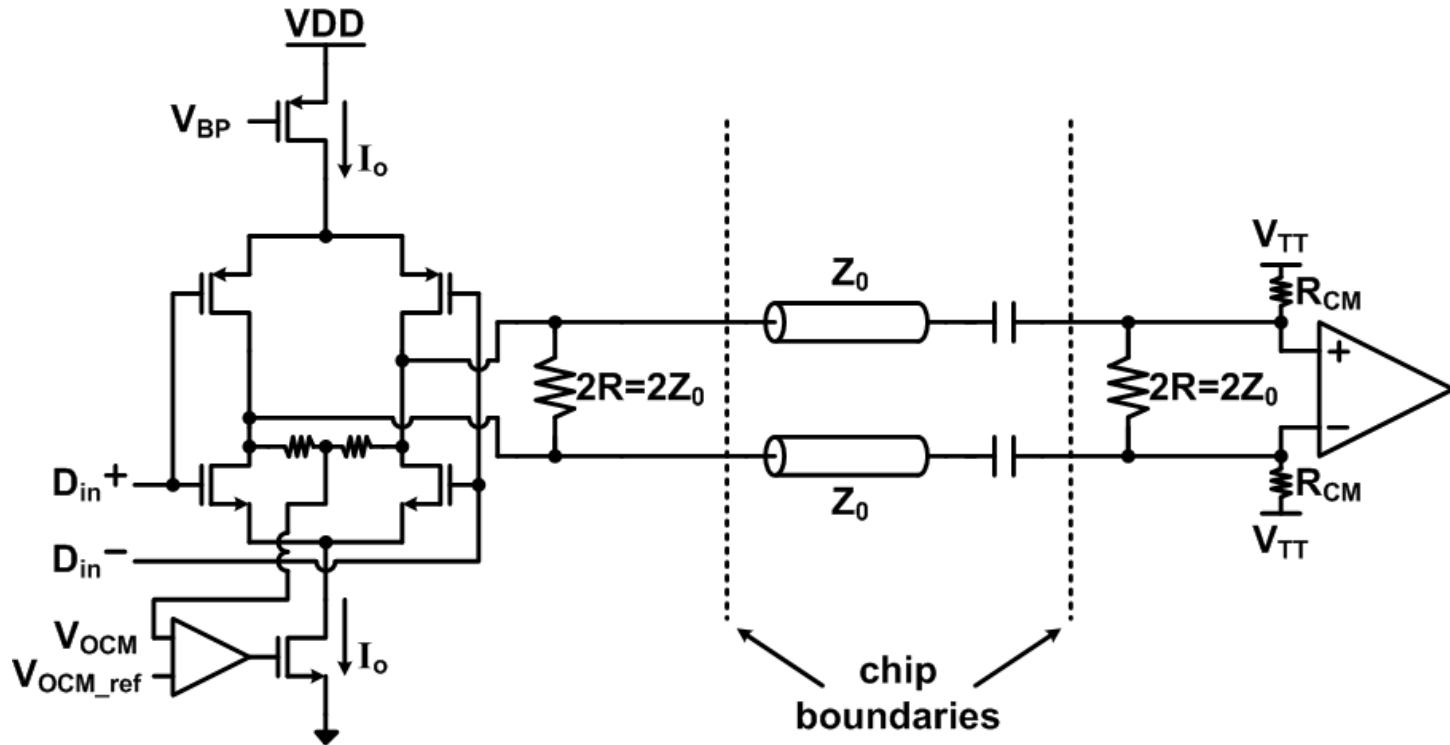


- Used in Low-Voltage Differential Signals (LVDS) standard
- Driver current is ideally constant, resulting in low di/dt noise
- Dual current sources allow for good PSRR, but headroom can be a problem in low-voltage technologies
- Differential RX swing is $\pm I_o R$ with double termination

Current-Mode Logic (CML) Driver

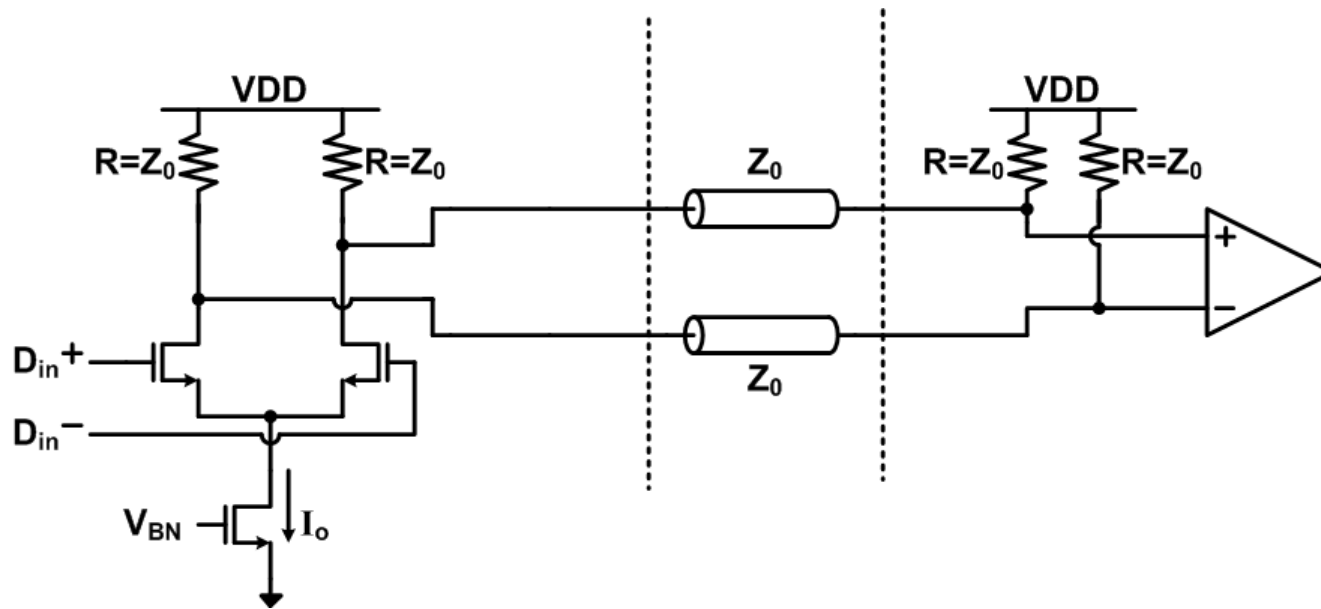

- Used in most high performance serial links
- Low voltage operation relative to push-pull driver
 - High output common-mode keeps current source saturated
- Can use DC or AC coupling
 - AC coupling requires data coding
- Differential RX swing is $\pm I_o R/2$ with double termination

Current-Mode Current Levels

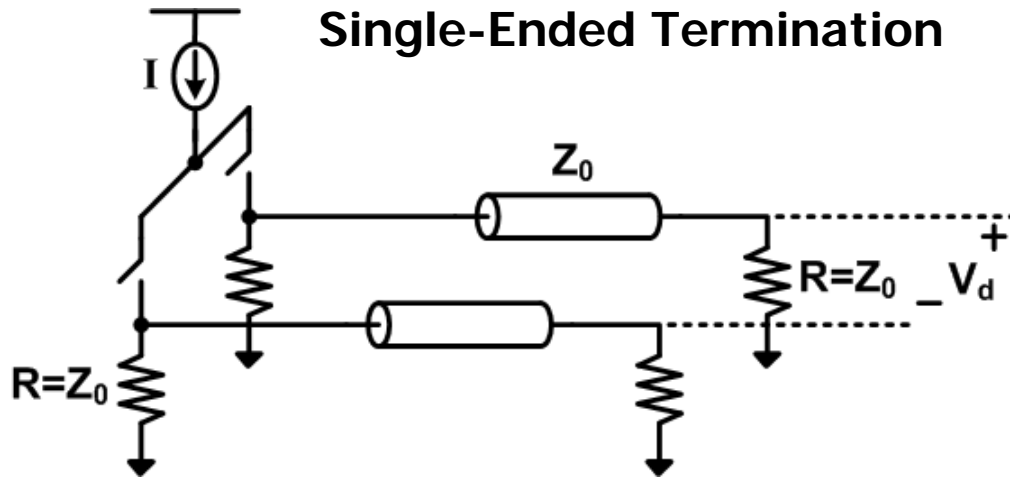


$$V_{d,1} = (I/2)R$$

$$V_{d,0} = -(I/2)R$$

$$V_{d,pp} = IR$$

$$I = \frac{V_{d,pp}}{R}$$

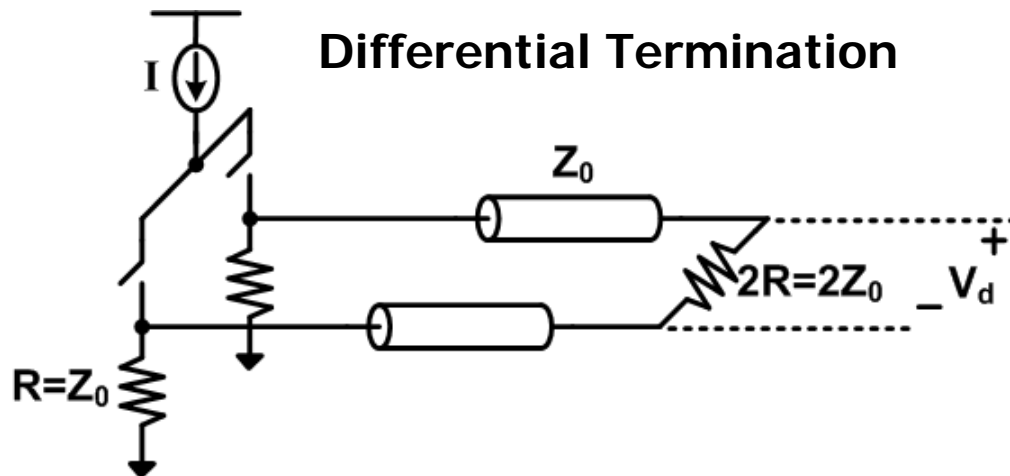

$$V_{d,1} = (I/4)(2R)$$


$$V_{d,0} = -(I/4)(2R)$$

$$V_{d,pp} = IR$$

$$I = \frac{V_{d,pp}}{R}$$

Voltage-Mode Current Levels

Single-Ended Termination

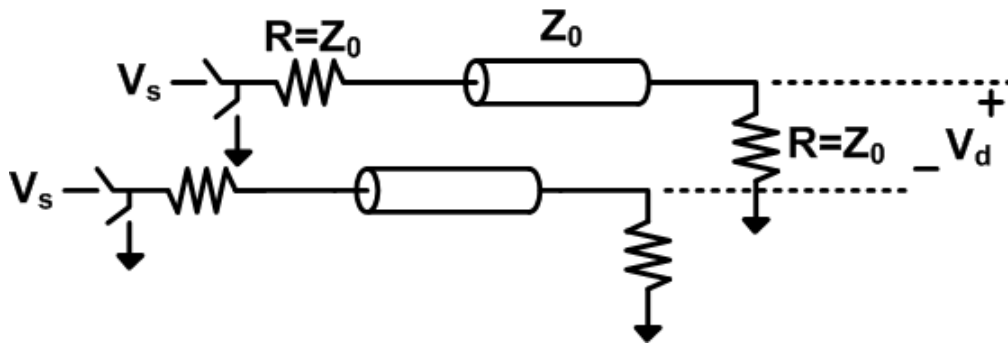

$$V_{d,1} = (V_s/2)$$


$$V_{d,1} = -(V_s/2)$$

$$V_{d,pp} = V_s$$

$$I = (V_s/2R)$$

$$I = \frac{V_{d,pp}}{2R}$$

Differential Termination

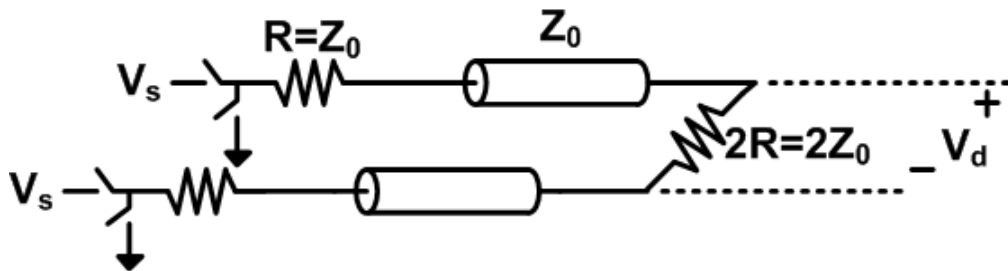

$$V_{d,1} = (V_s/2)$$

$$V_{d,1} = -(V_s/2)$$

$$V_{d,pp} = V_s$$

$$I = (V_s/4R)$$

$$I = \frac{V_{d,pp}}{4R}$$

Current-Mode vs Voltage-Mode Summary


Driver/Termination	Current Level	Normalized Current Level
Current-Mode/SE	$V_{d,pp}/Z_0$	1x
Current-Mode/Diff	$V_{d,pp}/Z_0$	1x
Voltage-Mode/SE	$V_{d,pp}/2Z_0$	0.5x
Voltage-Mode/Diff	$V_{d,pp}/4Z_0$	0.25x

- An ideal voltage-mode driver with differential RX termination enables a *potential* 4x reduction in driver power
- *Actual* driver power levels also depend on
 - Output impedance control
 - Pre-driver power
 - Equalization implementation

Voltage-Mode Drivers

- Voltage-mode driver implementation depends on output swing requirements
- For low-swing (<400-500mVpp), an all NMOS driver is suitable
- For high-swing, CMOS driver is used


Low-Swing Voltage-Mode Driver

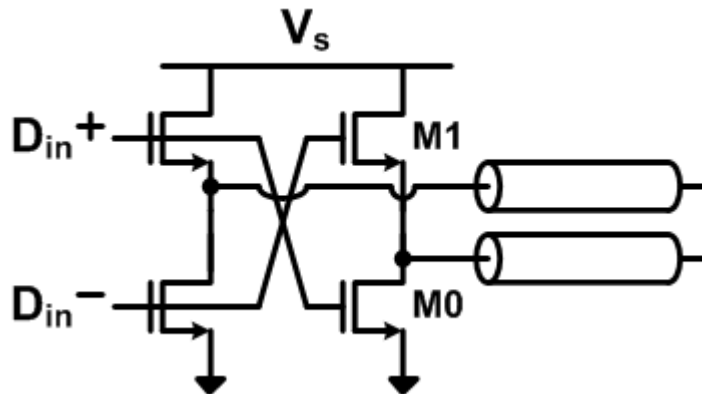

$$V_s < \frac{4}{3}(V_{DD} - V_{t1} - V_{OD1}) \text{ (Diff. Term)}$$

$$V_s < 2(V_{DD} - V_{t1} - V_{OD1}) \text{ (SE Term)}$$


High-Swing Voltage-Mode Driver

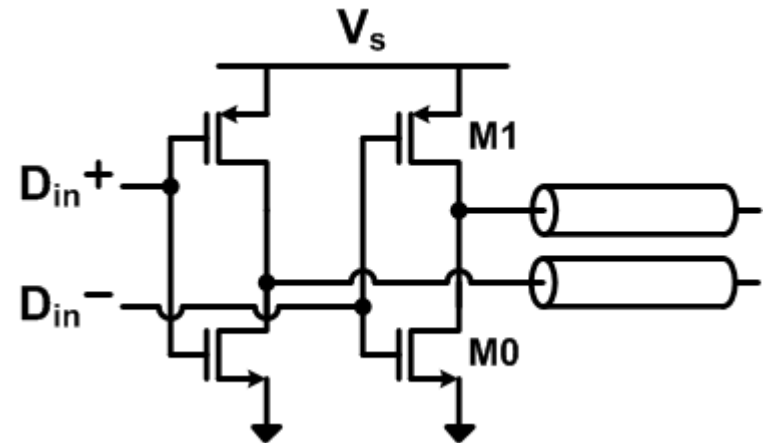

$$V_s > |V_{t1}| + V_{OD1}$$


Low-Swing VM Driver Impedance Control

[Poulton JSSC 2007]

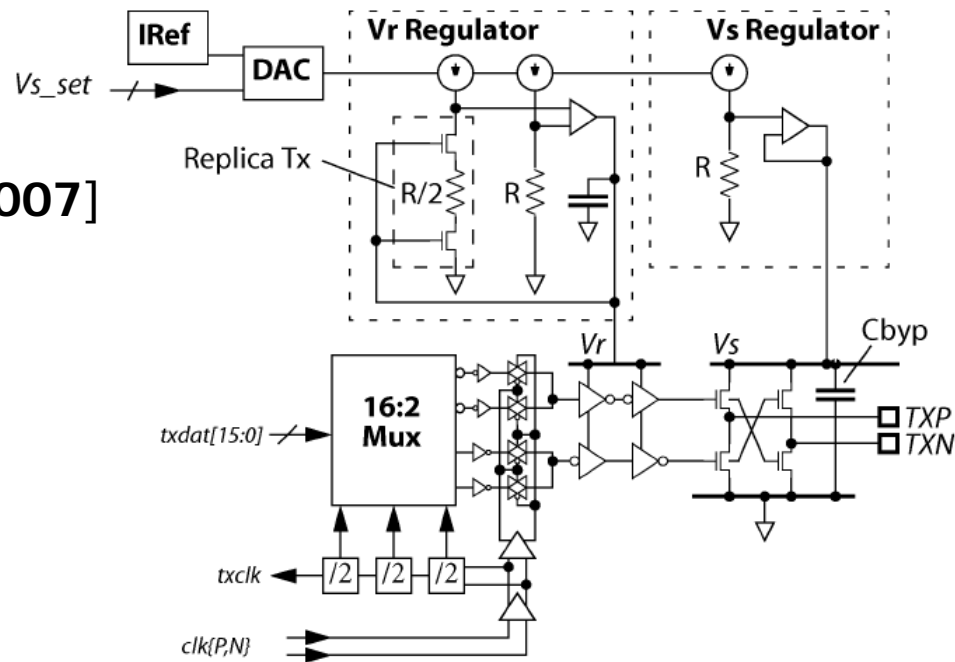


- A linear regulator sets the output stage supply, V_s
- Termination is implemented by output NMOS transistors
- To compensate for PVT and varying output swing levels, the pre-drive supply is adjusted with a feedback loop
- The top and bottom output stage transistors need to be sized differently, as they see a different V_{OD}

High-Swing VM Driver Impedance Control

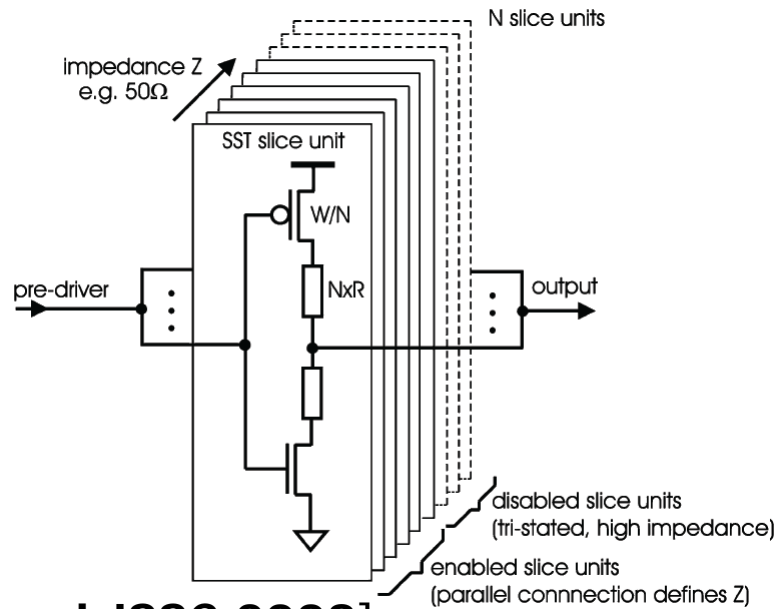

[Kossel JSSC 2008]

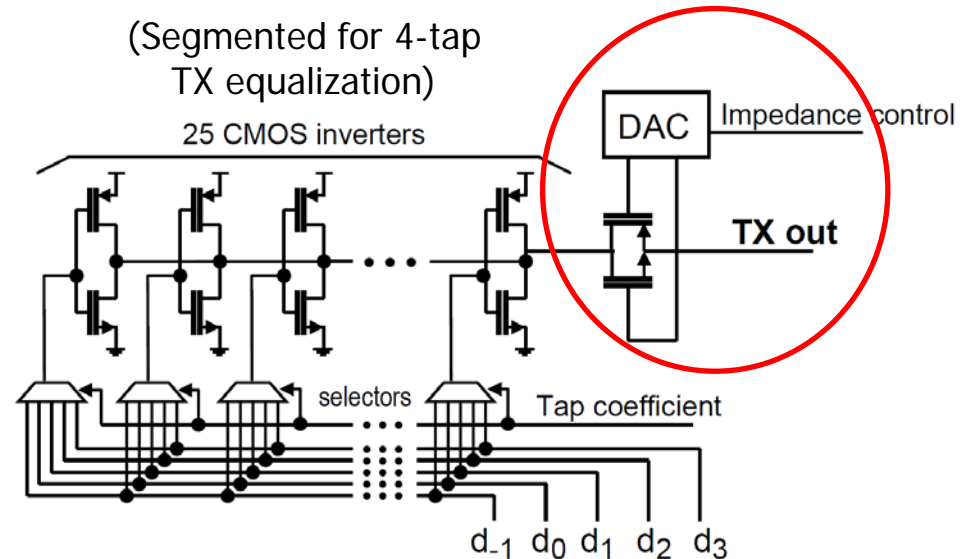



[Fukada ISSCC 2008]

- High-swing voltage-mode driver termination is implemented with a combination of output driver transistors and series resistors
- To meet termination resistance levels (50Ω), large output transistors are required
 - Degrades potential power savings vs current-mode driver

TX Driver Slew Rate Control

- Output transition times should be controlled
 - Too slow
 - Limits max data rate
 - Too fast
 - Can excite resonant circuits, resulting in ISI due to ringing
 - Cause excessive crosstalk
- Slew rate control reduces reflections and crosstalk

Slew Rate Control w/ Segmented Driver

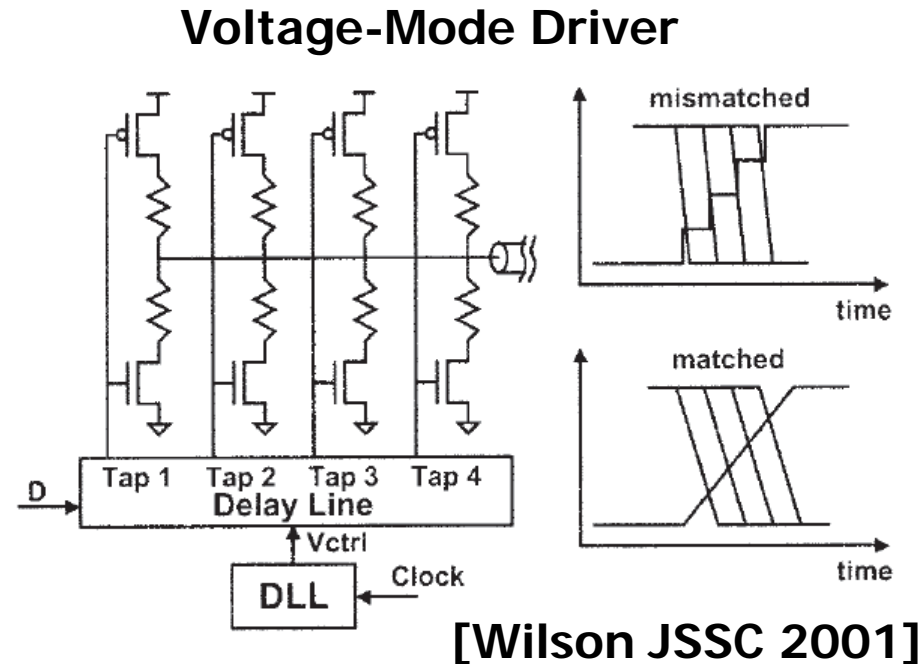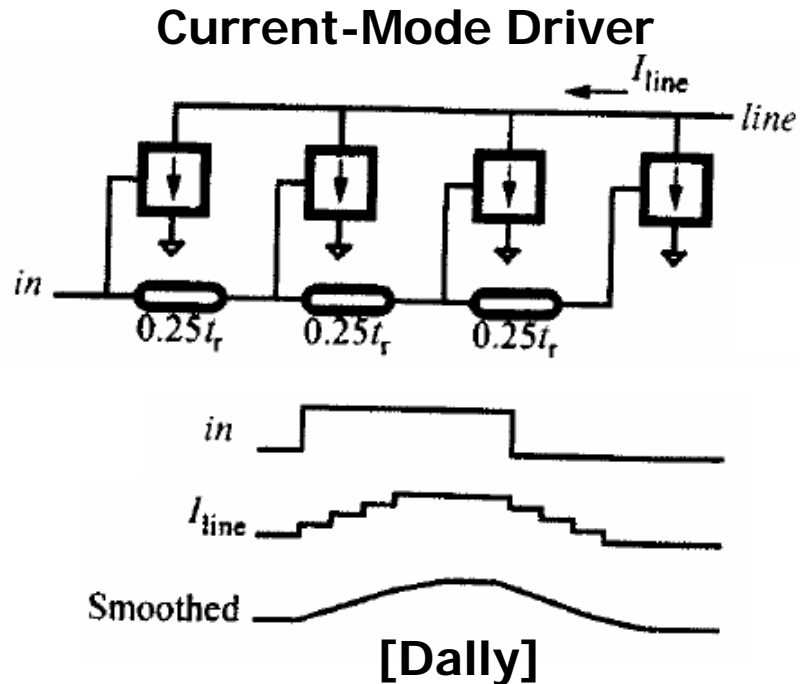

- Slew rate control can be implemented with a segmented output driver
- Segments turn-on time are spaced by $1/n$ of desired transition time
- Predriver transition time should also be controlled

Next Time

- TX circuit speed limitations
 - Clock distribution
 - Multiplexing circuits

- Receiver Circuits