

# ECEN689: Special Topics in High-Speed Links Circuits and Systems Spring 2010

---

## Lecture 16: Equalization Introduction



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

# Announcements

---


- HW4 due Wednesday 5PM
  - Any issues?
- Exam 1 is March 12
  - 9:10-10:10AM (10 extra minutes)
  - Closed book w/ one standard note sheet
    - 8.5"x11" front & back
  - Bring your calculator

# Agenda


---

- Equalization theory and circuits
  - Equalization overview
  - Equalization implementations
    - TX FIR
    - RX FIR
    - RX CTLE
    - RX DFE
  - Setting coefficients
  - Equalization effectiveness
  - Alternate/future approaches






# High-Speed Electrical Link System

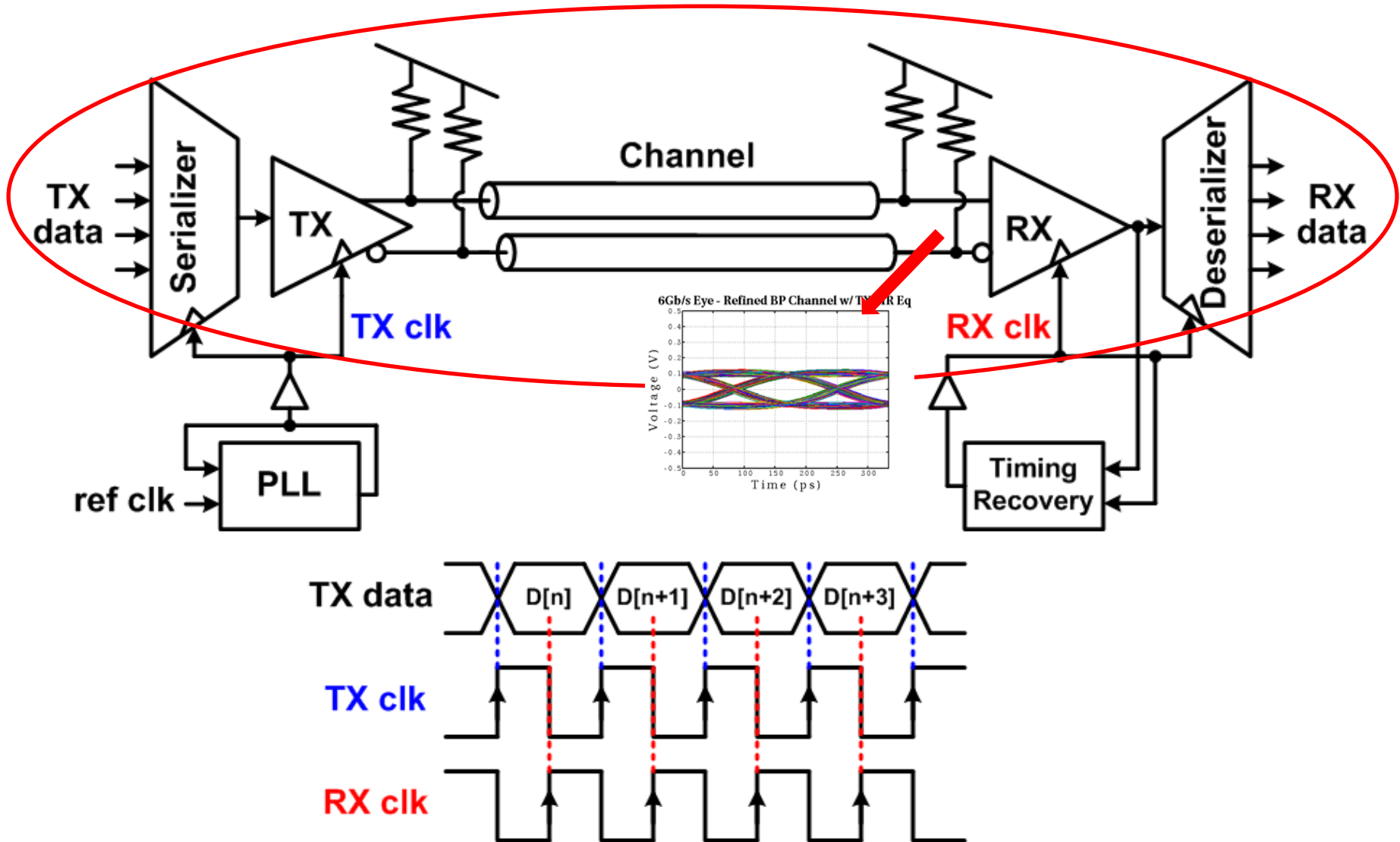






# Link with Equalization

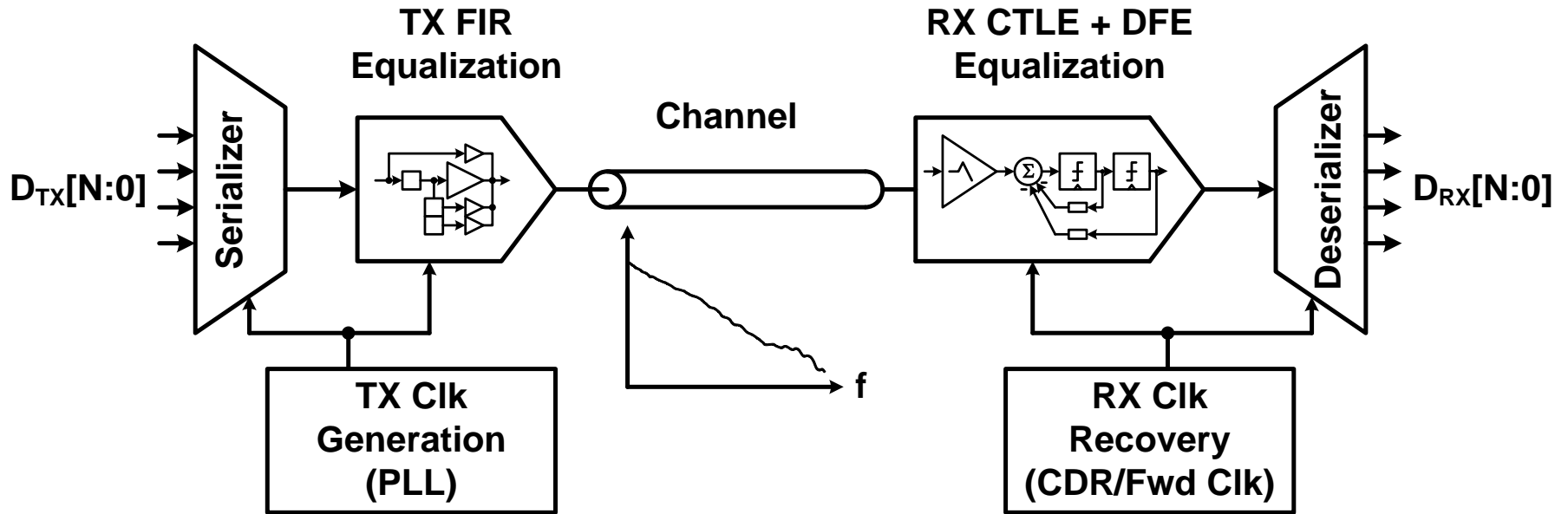

# Channel Performance Impact

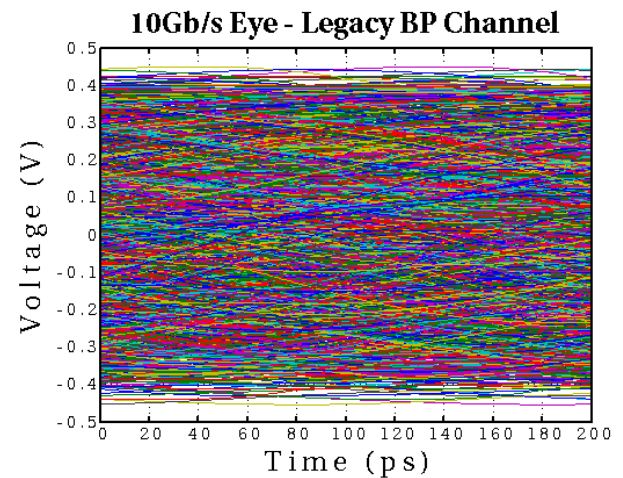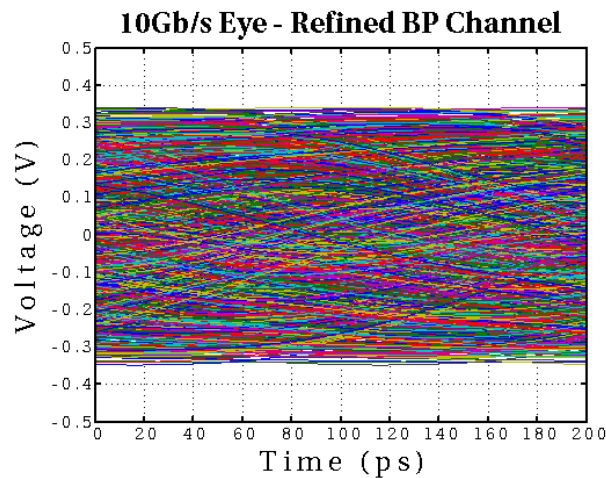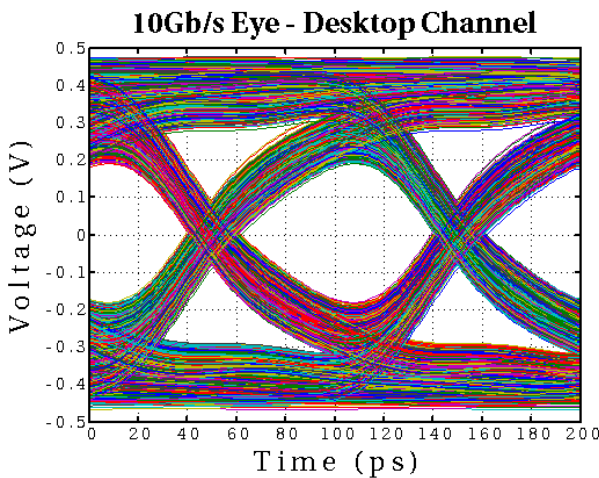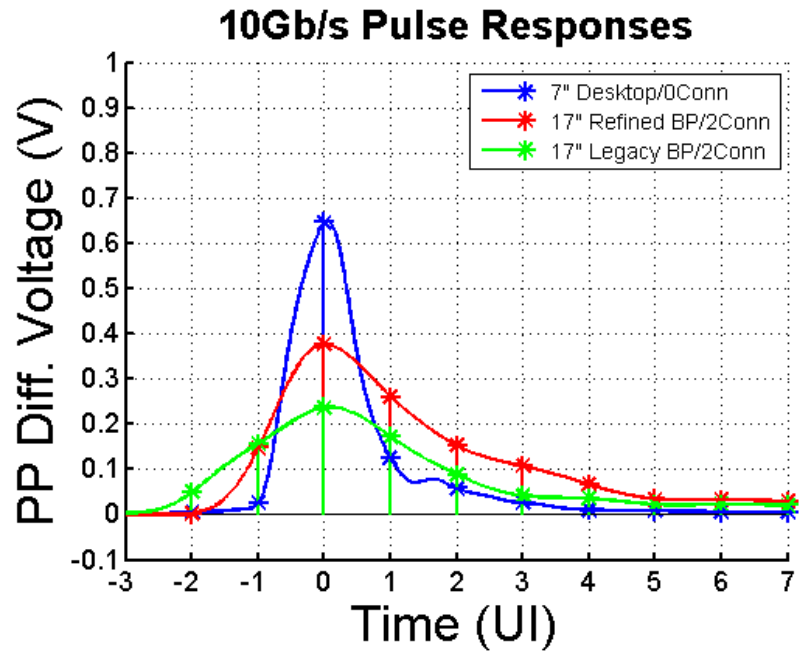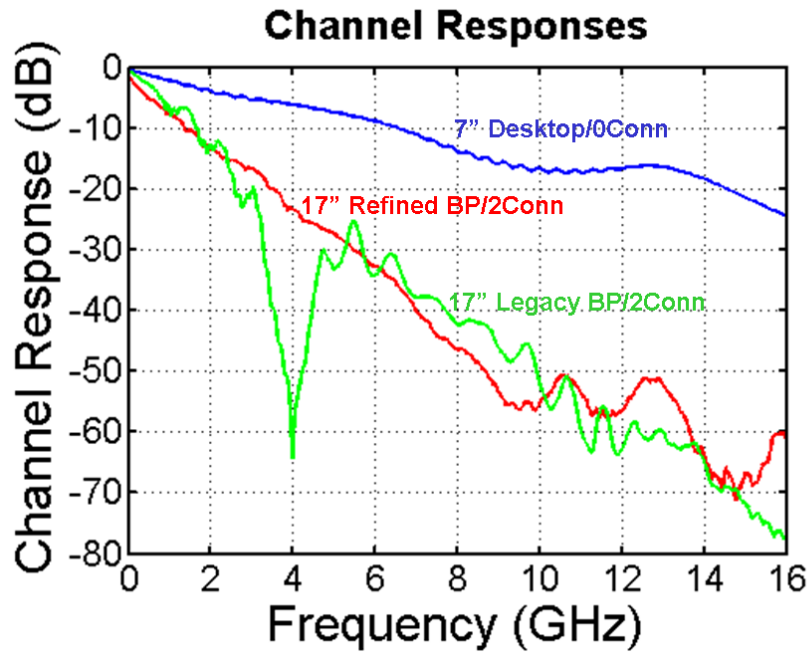


# Channel Performance Impact

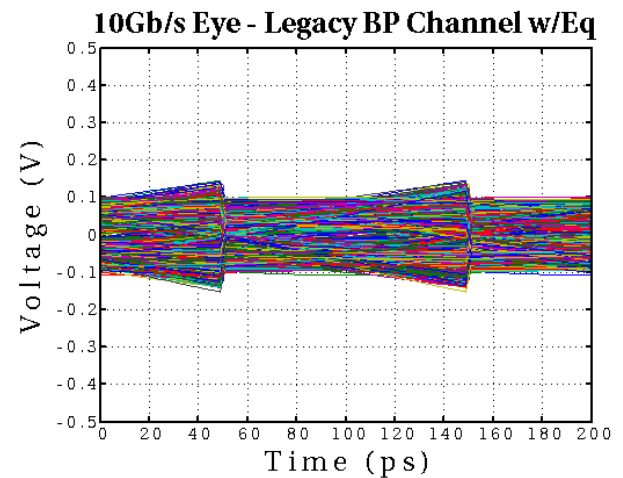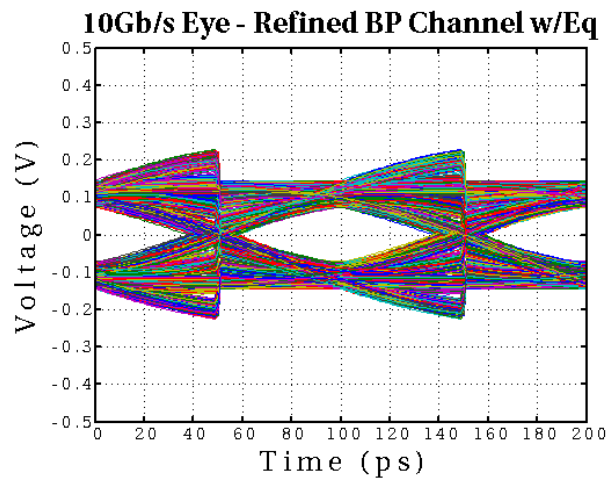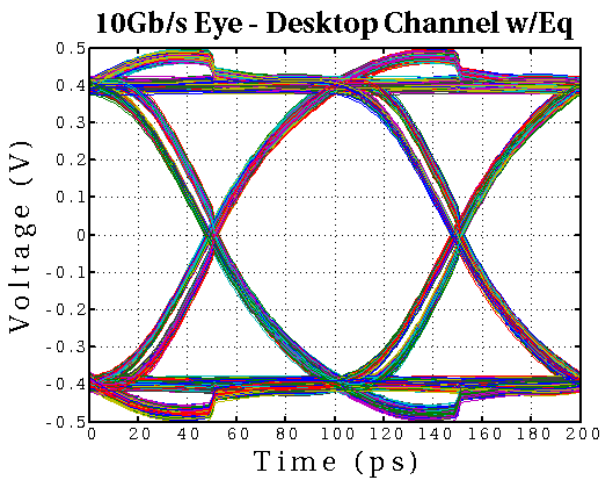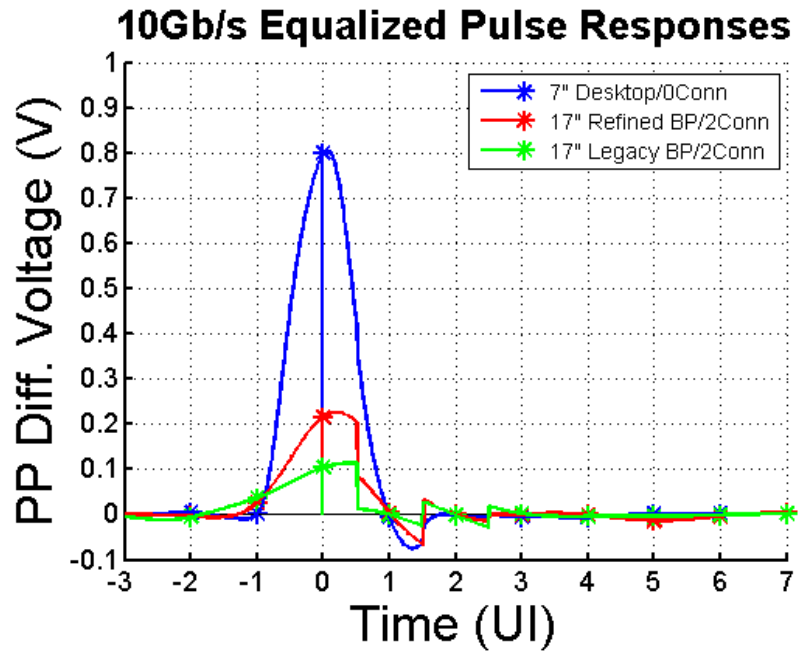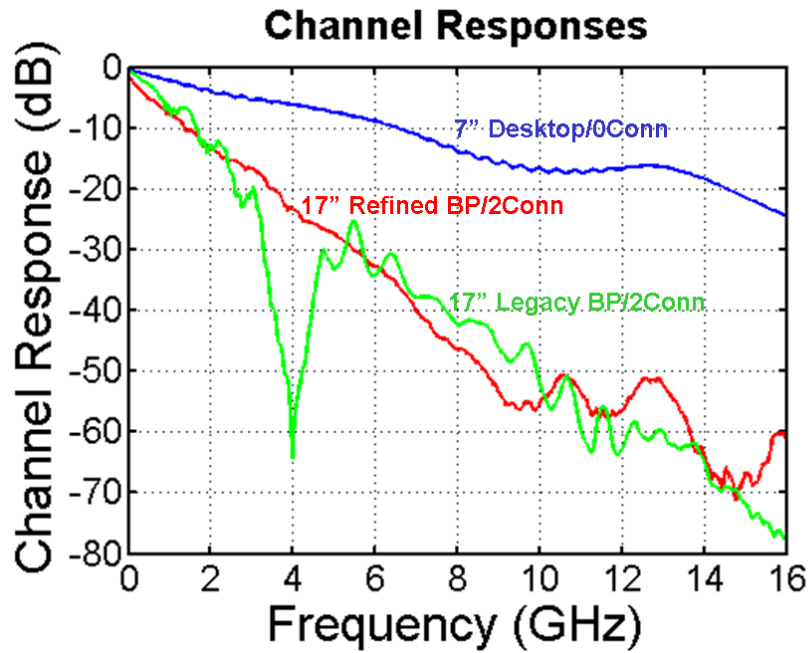
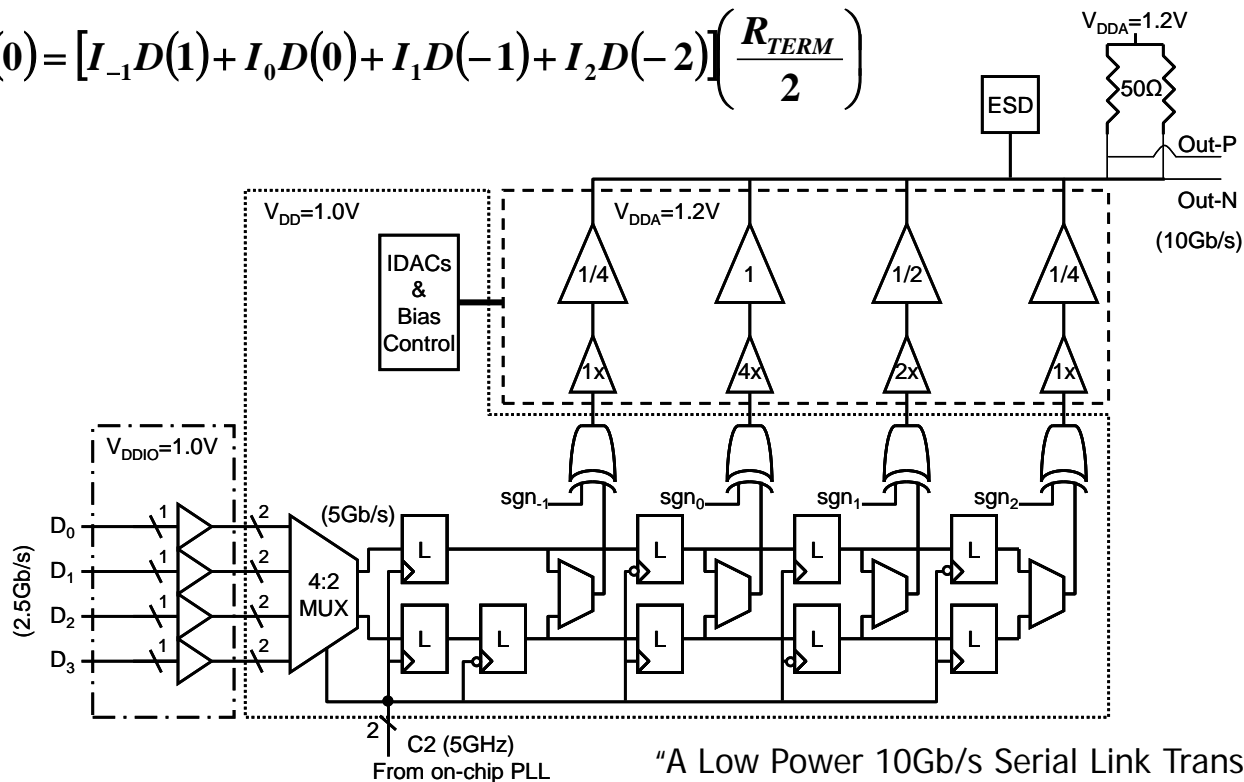
# TX FIR Equalization

- TX FIR filter pre-distorts transmitted pulse in order to invert channel distortion at the cost of attenuated transmit signal (de-emphasis)




$$V_{out}(0) = [I_{-1}D(1) + I_0D(0) + I_1D(-1) + I_2D(-2)] \left( \frac{R_{TERM}}{2} \right)$$



"A Low Power 10Gb/s Serial Link Transmitter in 90-nm CMOS," A. Rylyakov et al., CSICS 2005



# 6Gb/s TX FIR Equalization Example

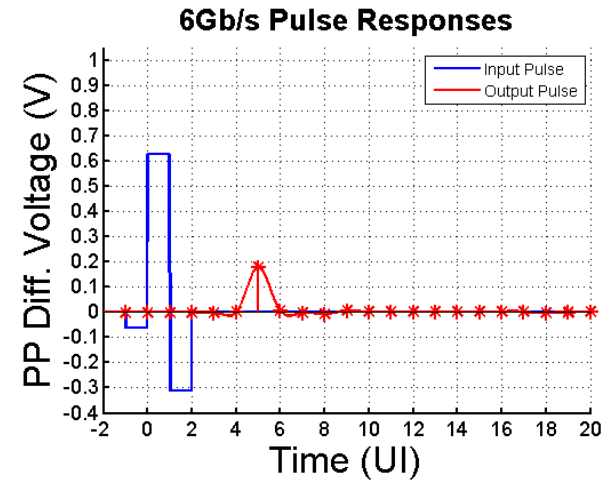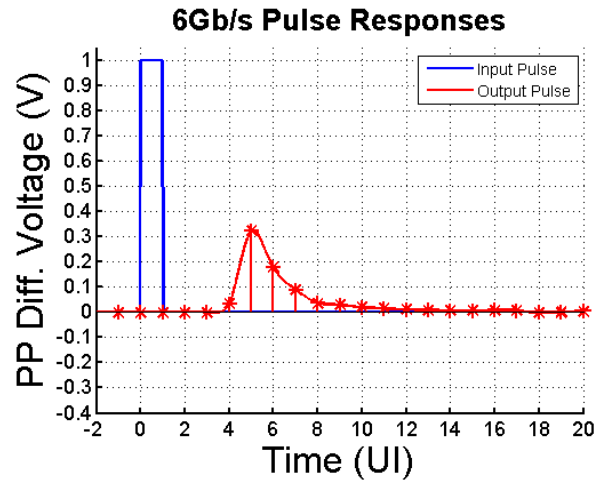
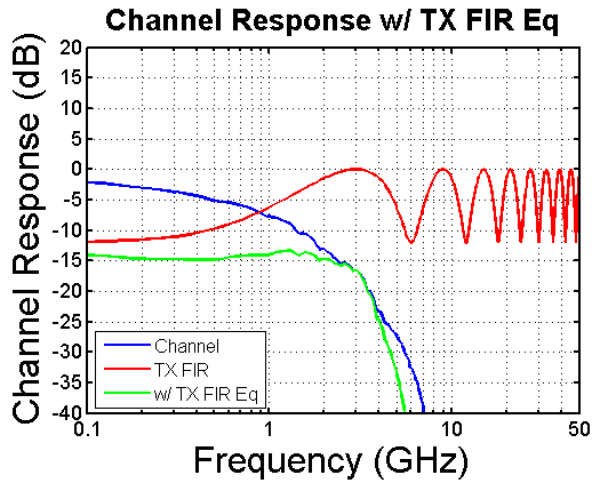


- Pros


- Simple to implement
- Can cancel ISI in precursor and beyond filter span
- Doesn't amplify noise
- Can achieve 5-6bit resolution

- Cons

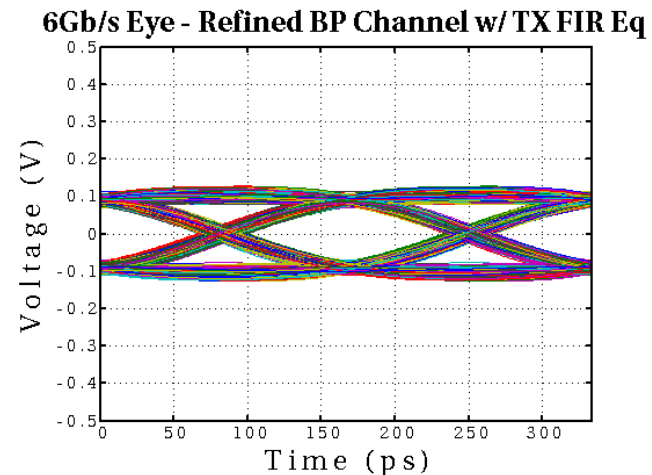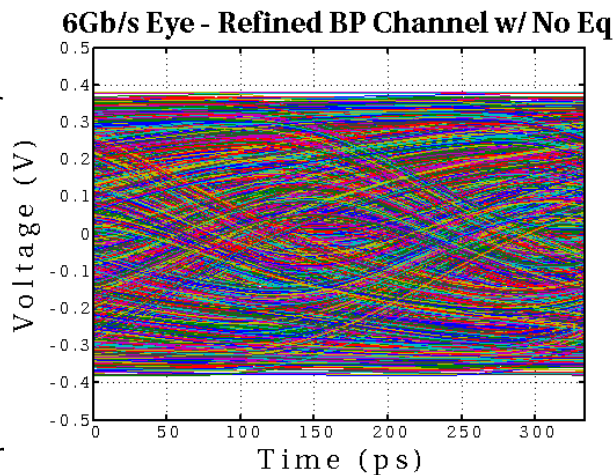- Attenuates low frequency content due to peak-power limiter
- Need a "back-channel" to tune filter taps




# RX Equalization #1: RX FIR

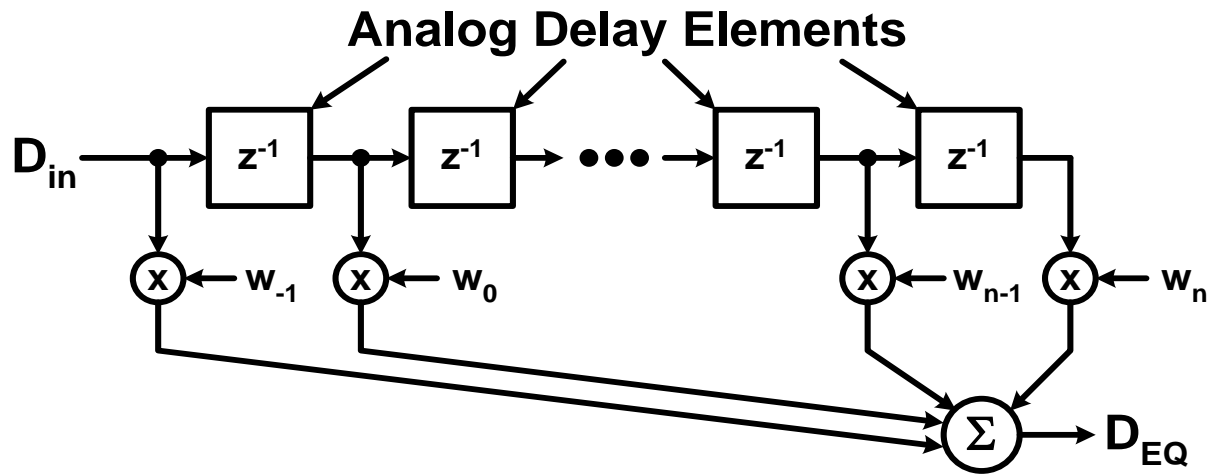



- Pros
  - With sufficient dynamic range, can amplify high frequency content (rather than attenuate low frequencies)
  - Can cancel ISI in pre-cursor and beyond filter span
  - Filter tap coefficients can be adaptively tuned without any back-channel
- Cons
  - Amplifies noise/crosstalk
  - Implementation of analog delays
  - Tap precision

Eye-Pattern Diagrams at 1Gb/s on CAT5e\*


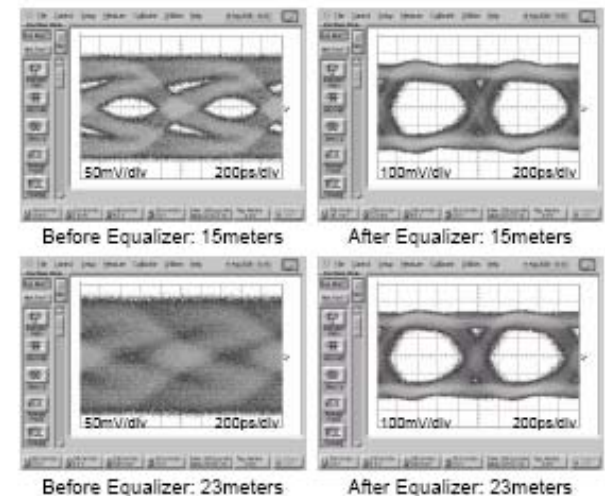


\*D. Hernandez-Garduno and J. Silva-Martinez, "A CMOS 1Gb/s 5-Tap Transversal Equalizer based on 3<sup>rd</sup>-Order Delay Cells," ISSCC, 2007.


# RX Equalization #2: RX CTLE

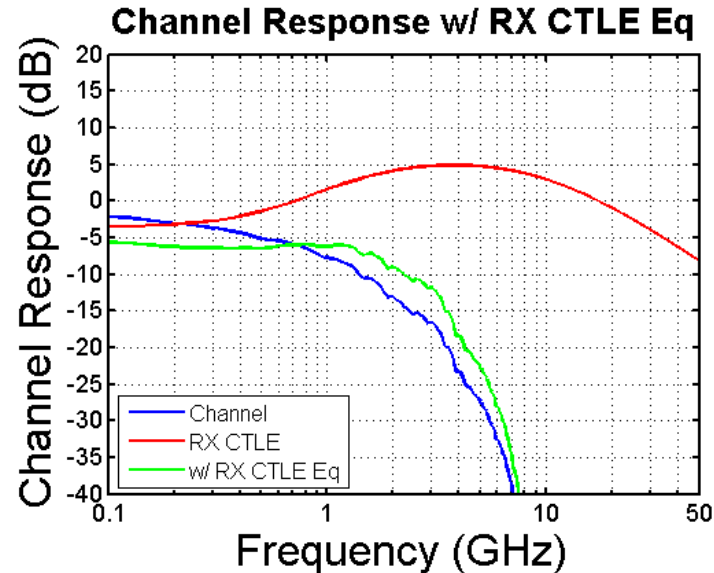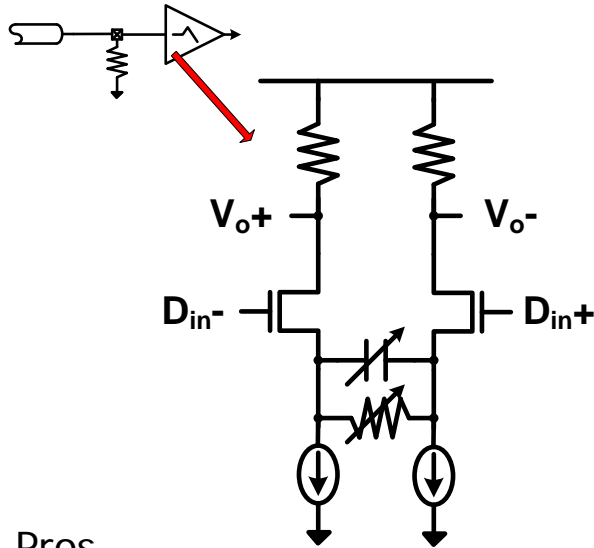

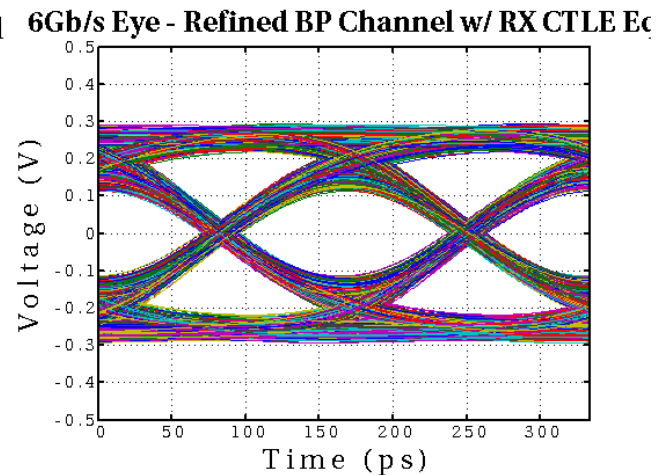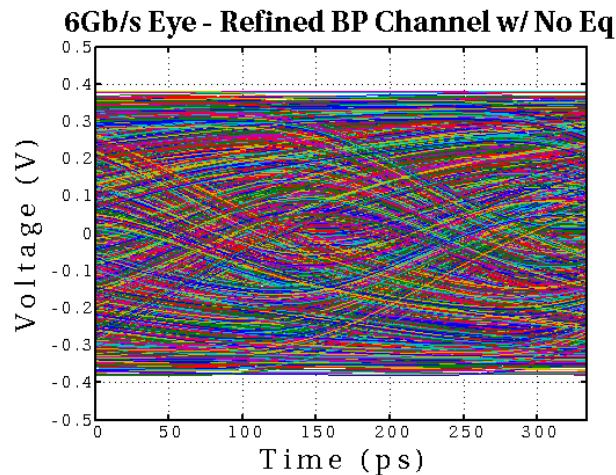
- Pros
  - Provides gain and equalization with low power and area overhead
  - Can cancel both pre-cursor and long-tail ISI
- Cons
  - Generally limited to 1st order compensation
  - Amplifies noise/crosstalk
  - PVT sensitivity
  - Can be hard to tune



# RX Equalization #3: RX DFE

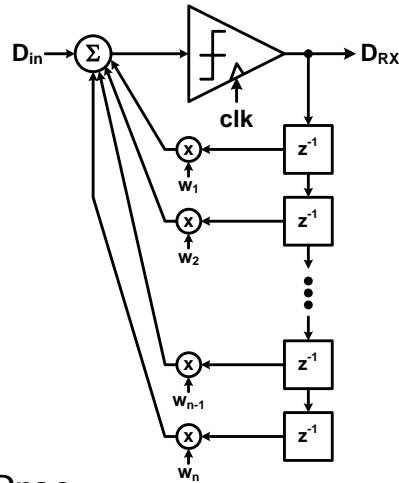


Refined BP Channel 6Gb/s Pulse Responses

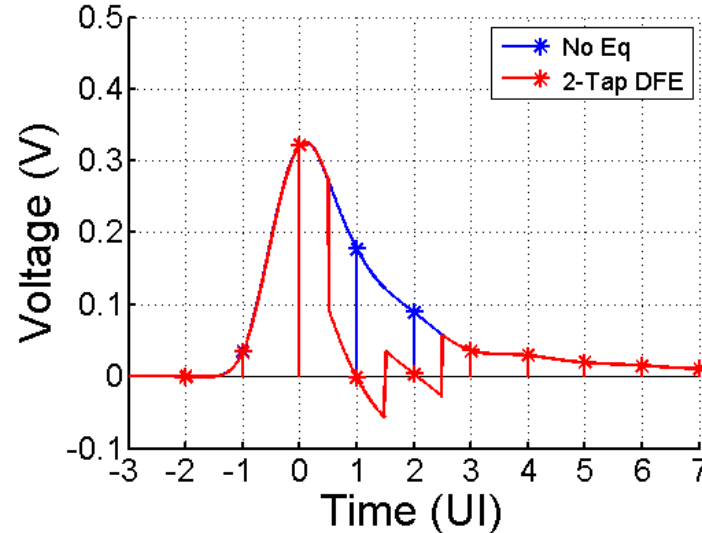


- Pros
  - No noise and crosstalk amplification
  - Filter tap coefficients can be adaptively tuned without any back-channel
- Cons
  - Cannot cancel precursor ISI
  - Critical feedback timing path
  - Timing of ISI subtraction complicates CDR phase detection

6Gb/s Eye - Refined BP Channel w/ No Eq

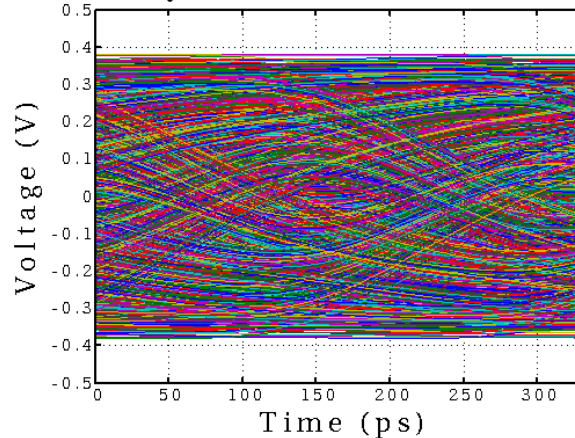


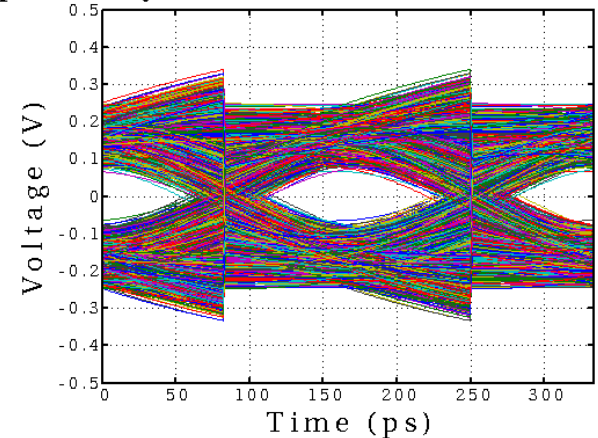6Gb/s Eye - Refined BP Channel w/ RX DFE Eq




# Equalization Effectiveness

## Channel Responses

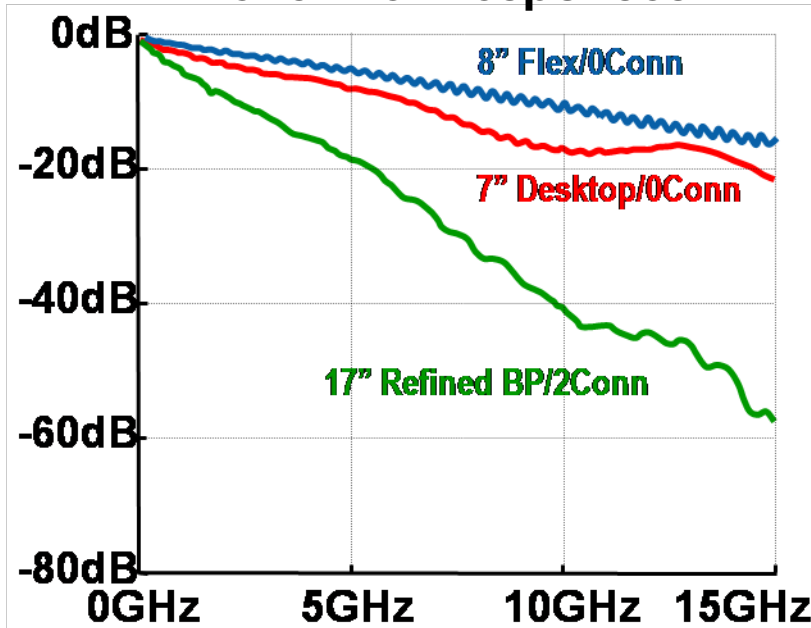

## Eq. Complexity vs Max. Data Rate

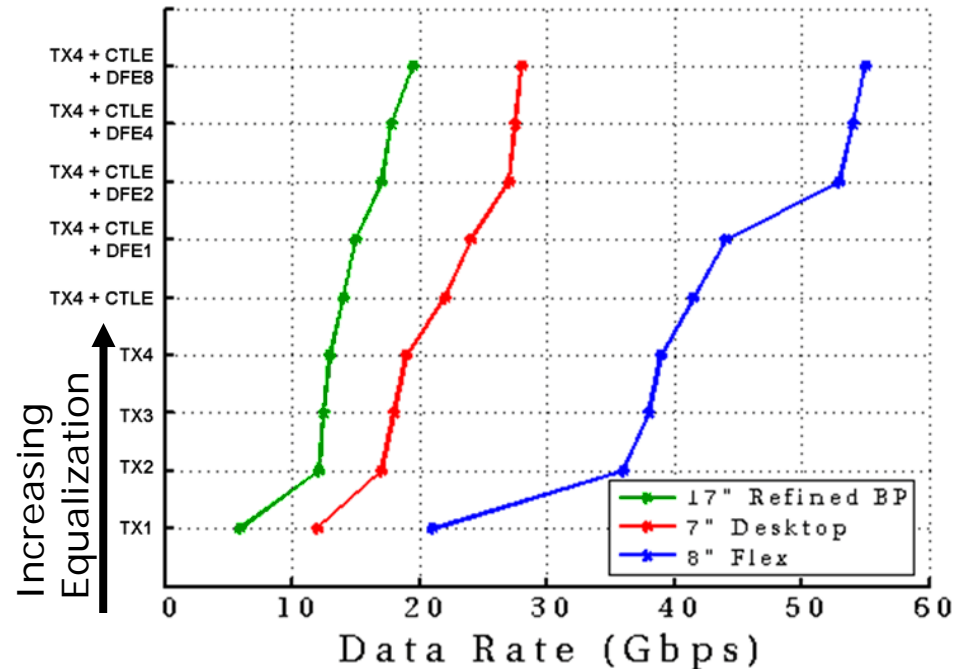

- Some observations:
  - Big initial performance boost with 2-tap TX eq.
  - With only TX eq., not much difference between 2 to 4-tap
  - RX equalization, particularly DFE, allows for further performance improvement
    - Caution – hard to build fast DFEs due to critical timing path

# Next Time

---

- Equalization theory and circuits
  - Equalization implementations
    - TX FIR
    - RX FIR
    - RX CTLE
    - RX DFE
  - Setting coefficients
  - Equalization effectiveness
  - Alternate/future approaches