

ECEN689: Special Topics in High-Speed Links Circuits and Systems Spring 2010

Lecture 25: Clocking Architectures



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University


Announcements

- Project Preliminary Report #1 due April 16 (in class)
- Exam 2 is April 30
- Reading
 - Will post some clocking papers





Agenda

- Project Overview
- HW5 Discussion
- Clocking Architectures

HW5 Comparator Survey

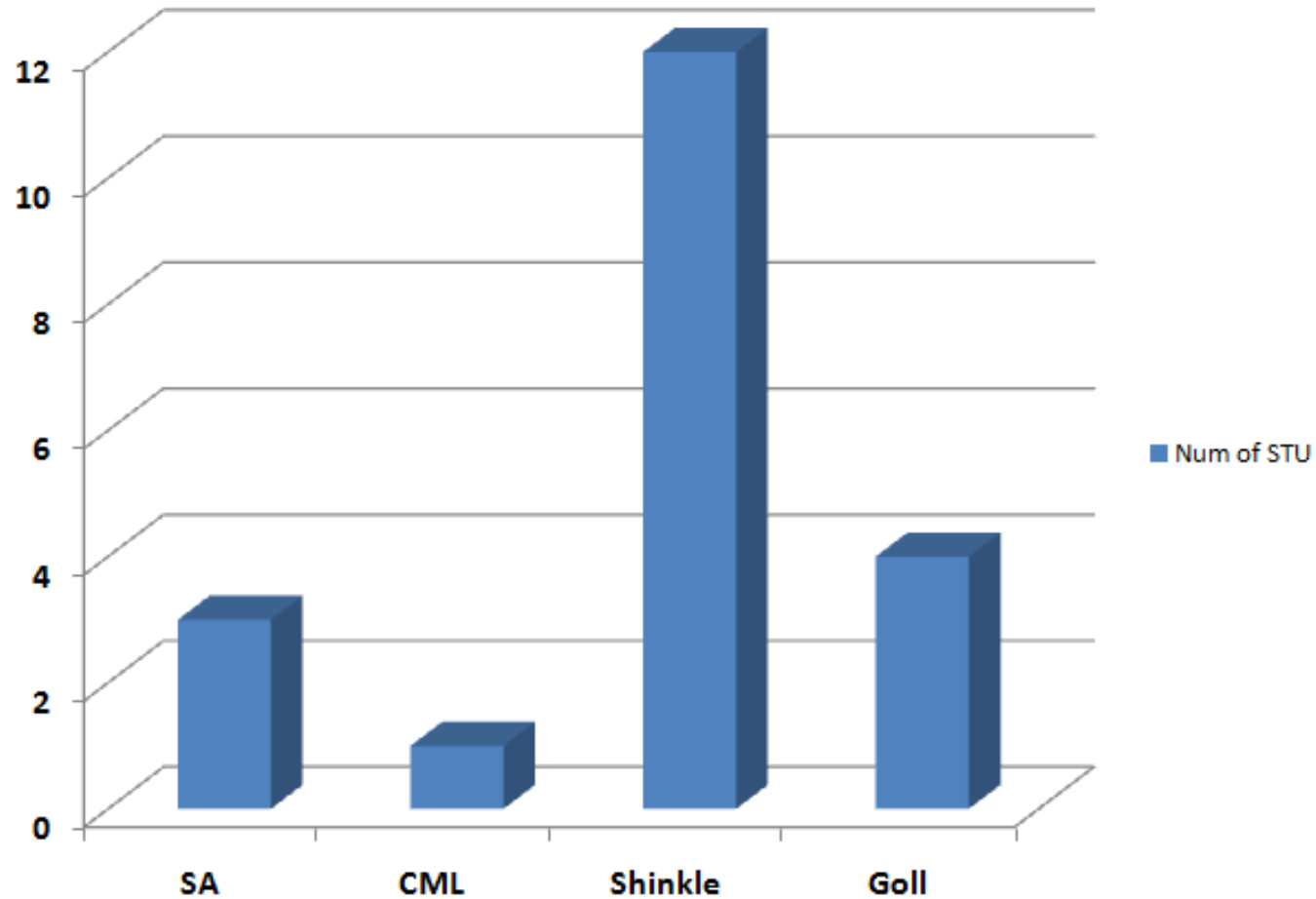


HW5 Comparator Delay vs VDD

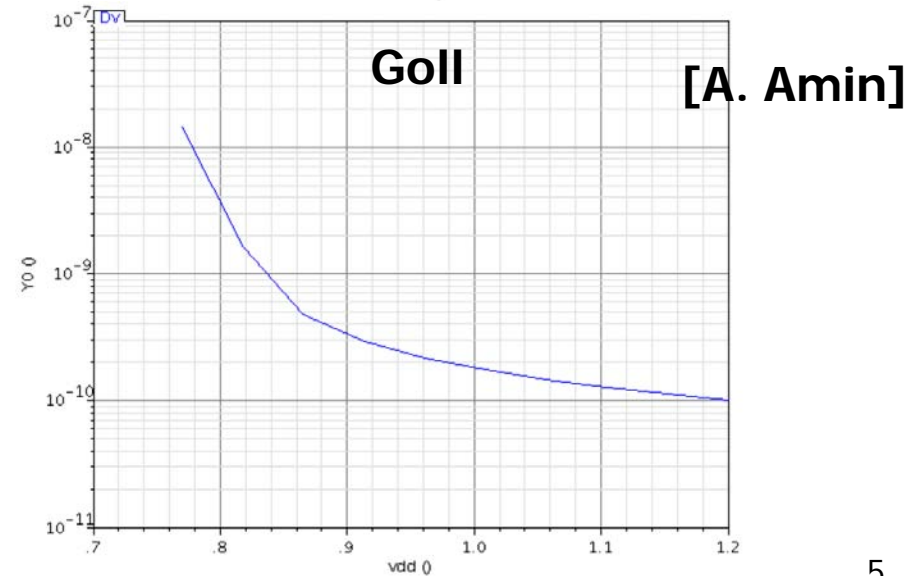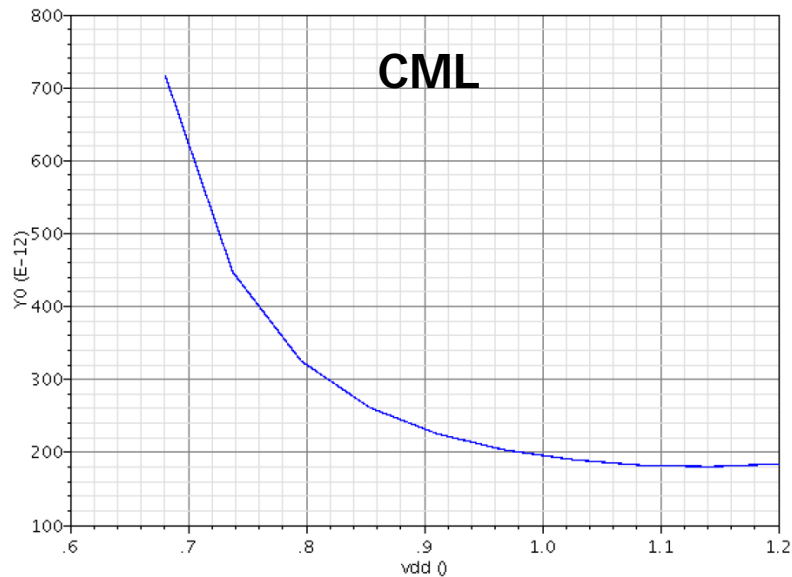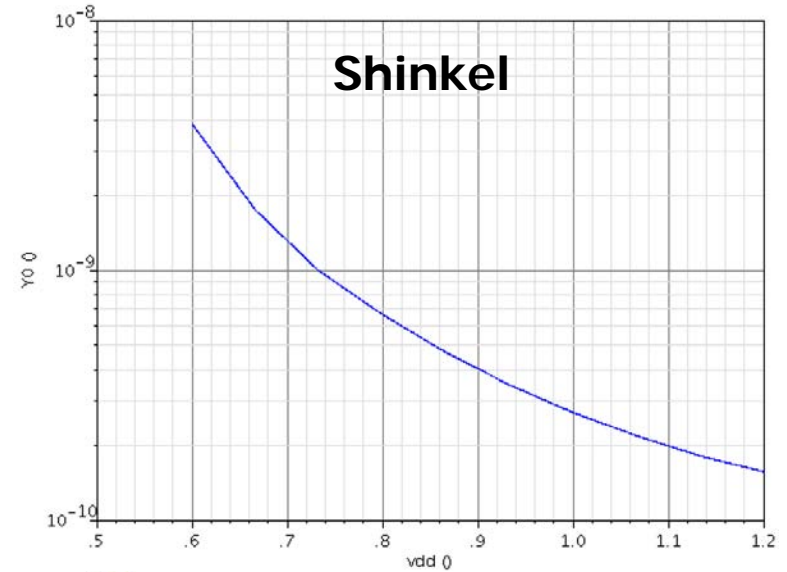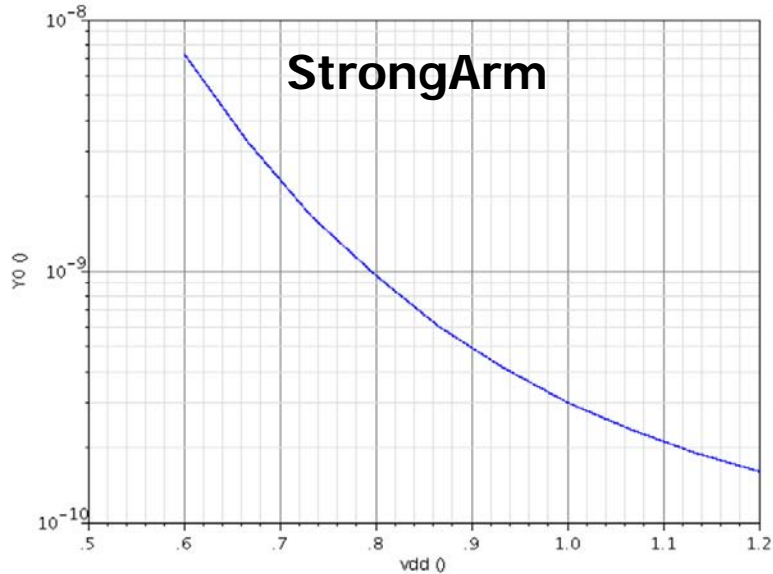


HW5 Comparator ISF

StrongArm: 30ps

 


Shinkel: 20ps

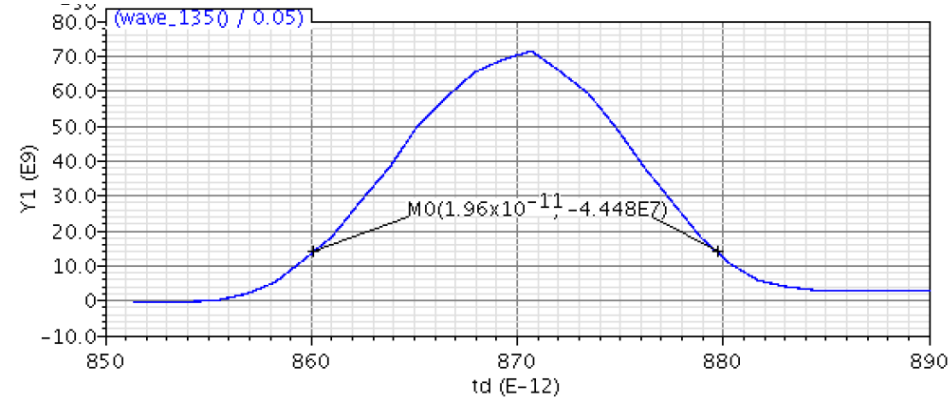


[A. Amin]


CML: 60ps

 


Goll: 34ps

 

High-Speed Electrical Link System

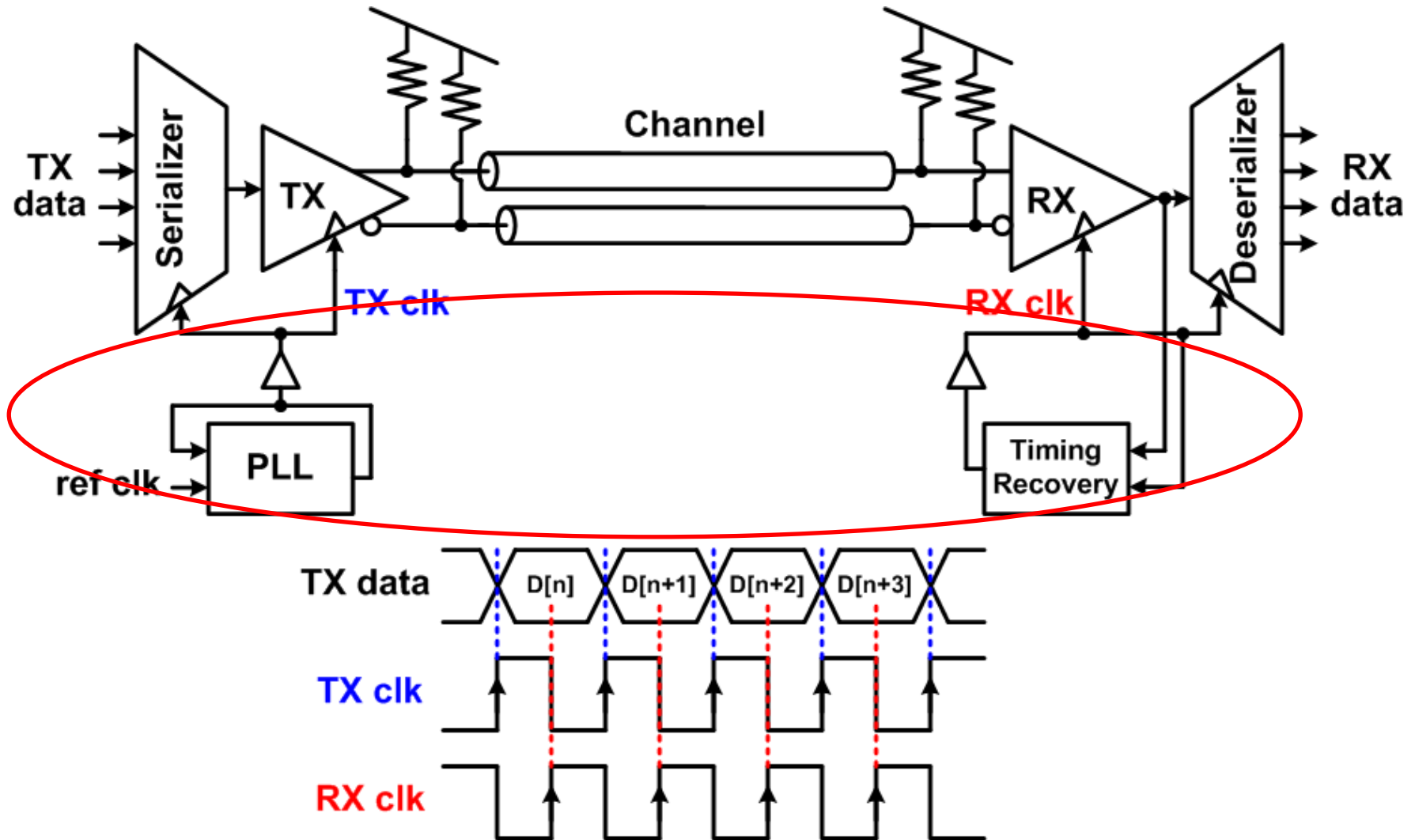


Clocking Terminology

 


Synchronous

 - Every chip gets same frequency AND phase
- Used in low-speed busses




Mesochronous

 - Same frequency, but unknown phase
- Requires phase recovery circuitry
 - Can do with or without full CDR
- Used in fast memories, internal system interfaces, MAC/Packet interfaces



Plesiochronous

 - Almost the same frequency, resulting in slowly drifting phase
- Requires CDR
- Widely used in high-speed links



Asynchronous


- No clocks at all
- Request/acknowledge handshake procedure
- Used in embedded systems, Unix, Linux

[Poulton]

I/O Clocking Architectures

- Three basic I/O architectures
 - Common Clock (Synchronous)
 - Forward Clock (Source Synchronous)
 - Embedded Clock (Clock Recovery)
- These I/O architectures are used for varying applications that require different levels of I/O bandwidth
- A processor may have one or all of these I/O types
- Often the same circuitry can be used to emulate different I/O schemes for design reuse

Common Clock I/O Architecture

 


[Krauter]

- Common in original computer systems
- Synchronous system
- Common bus clock controls chip-to-chip transfers
- Requires equal length routes to chips to minimize clock skew
- Data rates typically limited to $\sim 100\text{Mb/s}$

Common Clock I/O Cycle Time

Cycle time to meet setup time

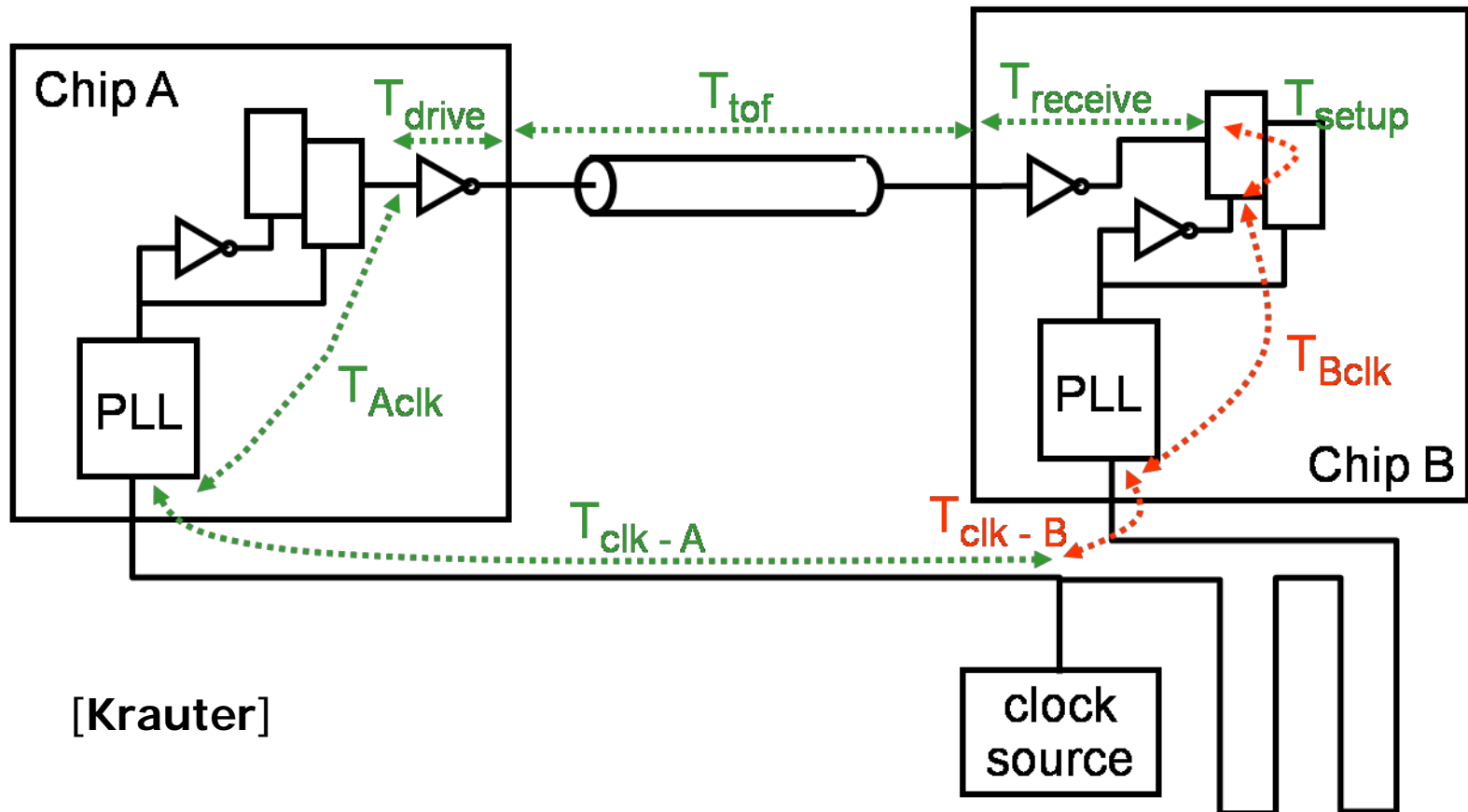
$$\max(T_{\text{clk-A}} + T_{\text{Aclk}} + T_{\text{drive}} + T_{\text{tof}} + T_{\text{receive}} + T_{\text{setup}}) - \min(T_{\text{Bclk}} - T_{\text{clk-B}}) < T_{\text{cycle}}$$



Common Clock I/O Limitations


- Difficult to control clock skew and propagation delay
- Need to have tight control of absolute delay to meet a given cycle time
- Sensitive to delay variations in on-chip circuits and board routes
- Hard to compensate for delay variations due to low correlation between on-chip and off-chip delays
- While commonly used in on-chip communication, offers limited speed in I/O applications

Forward Clock I/O Architecture

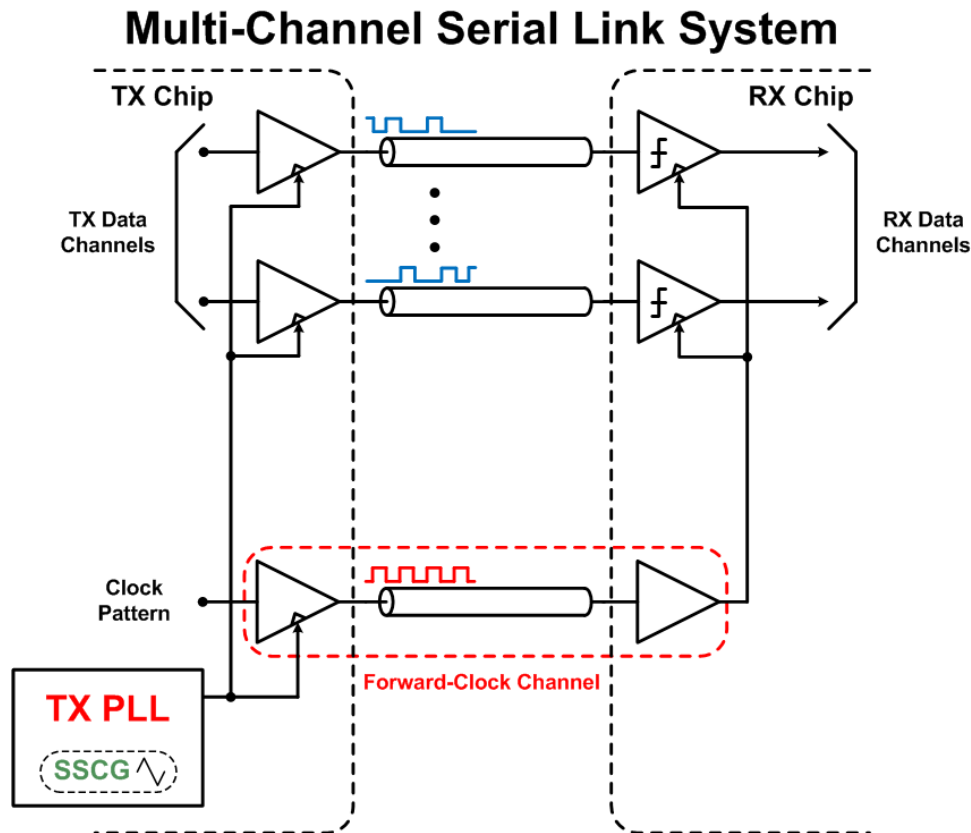


- Common high-speed reference clock is forwarded from TX chip to RX chip
 - Mesochronous system
- Used in processor-memory interfaces and multi-processor communication
 - Intel QPI
 - Hypertransport
- Requires one extra clock channel
- “Coherent” clocking allows low-to-high frequency jitter tracking
- Need good clock receive amplifier as the forwarded clock is attenuated by the channel

Forward Clock I/O Limitations

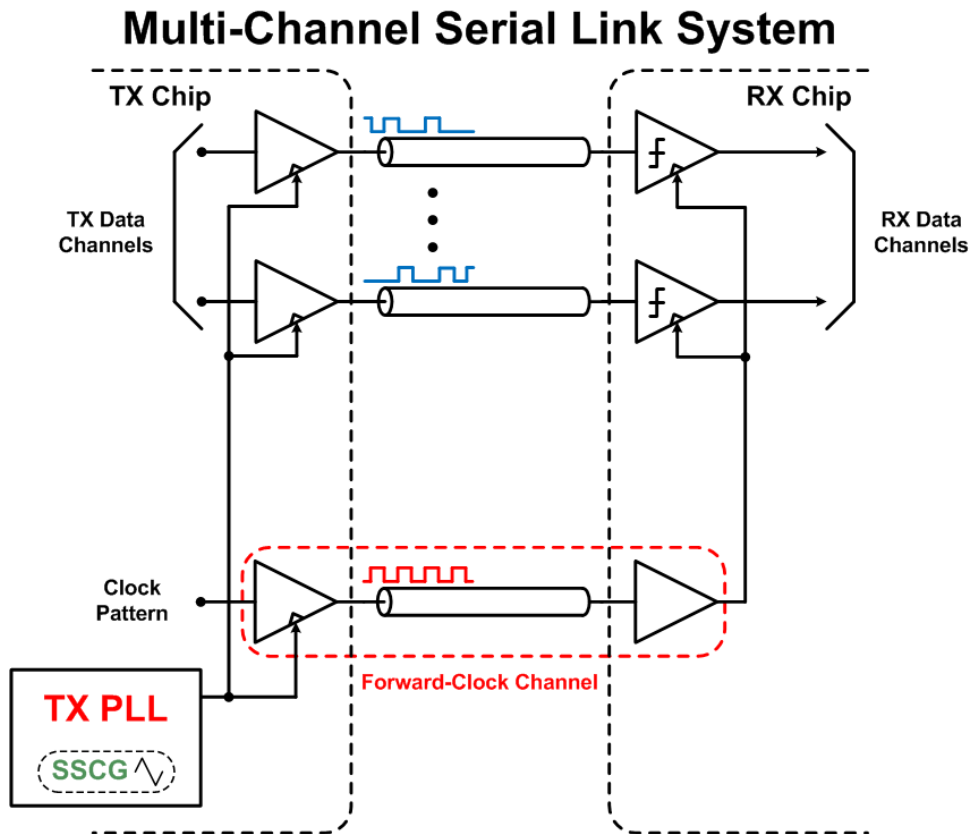


- Clock skew can limited forward clock I/O performance
 - Driver strength and loading mismatches
 - Interconnect length mismatches
- Low pass channel causes jitter amplification
- Duty-Cycle variations of forwarded clock

Forward Clock I/O De-Skew

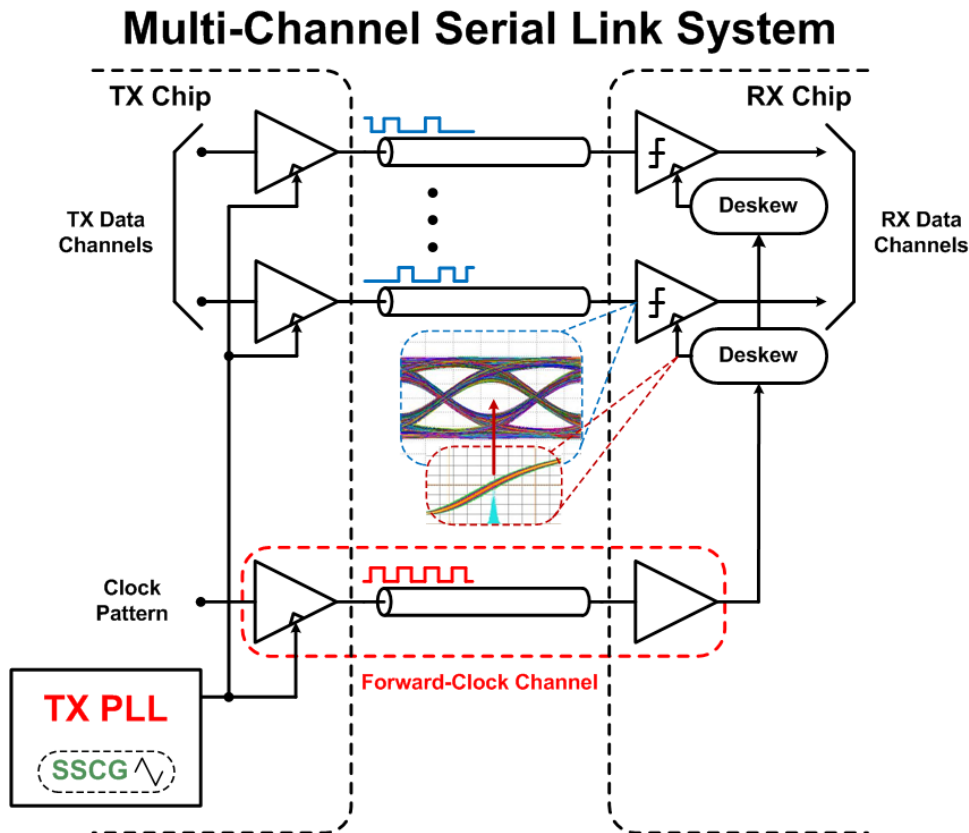


- Per-channel de-skew allows for significant data rate increases
- Sample clock adjusted to center clock on the incoming data eye
- Implementations
 - Delay-Locked Loop and Phase Interpolators
 - Injection-Locked Oscillators
- Phase Acquisition can be
 - BER based – no additional input phase samplers
 - Phase detector based implemented with additional input phase samplers periodically powered on

Forward Clock I/O Circuits

 


- TX PLL
- TX Clock Distribution
- Replica TX Clock Driver
- Channel
- Forward Clock Amplifier
- RX Clock Distribution
- De-Skew Circuit
 - DLL/PI
 - Injection-Locked Oscillator

Embedded Clock I/O Limitations

 

- Jitter tracking limited by CDR bandwidth
 - Technology scaling allows CDRs with higher bandwidths which can achieve higher frequency jitter tracking
- Generally more hardware than forward clock implementations
 - Extra input phase samplers

Embedded Clock I/O Circuits

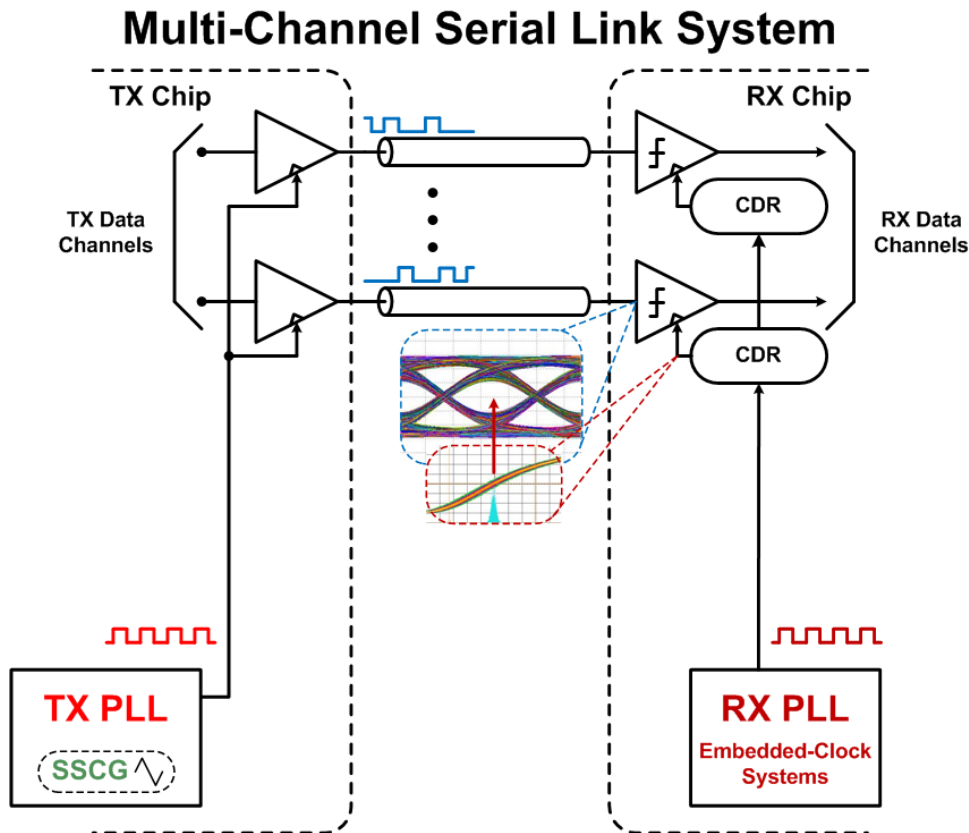

- TX PLL
- TX Clock Distribution
- CDR
 - Per-channel PLL-based
 - Dual-loop w/ Global PLL &
 - Local DLL/PI
 - Local Phase-Rotator PLLs
 - Global PLL requires RX clock distribution to individual channels

Next Time

- PLL