

ECEN689: Special Topics in High-Speed Links Circuits and Systems Spring 2010

Lecture 26: Phase-Locked Loops



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

Announcements

- Project Preliminary Report #1 due April 16 (in class)
- Exam 2 is April 30
- Reading
 - Posted clocking papers
 - Website additional links has PLL and jitter tutorials
- Majority of today's material from Fischette tutorial and M. Mansuri's PhD thesis (UCLA)


Agenda

- PLL modeling

Introduction


- A phase-locked loop (PLL) is a negative feedback system where an oscillator-generated signal is phase AND frequency locked to a reference signal
- PLLs applications
 - Frequency synthesis
 - Multiplying a 100MHz reference clock to 10GHz
 - Skew cancellation
 - Phase aligning an internal clock to an I/O clock
 - Clock recovery
 - Extract from incoming data stream the clock frequency and optimum phase of high-speed sampling clocks
 - Modulation/De-modulation
 - Wireless systems
 - Spread-spectrum clocking

PLL Block Diagram

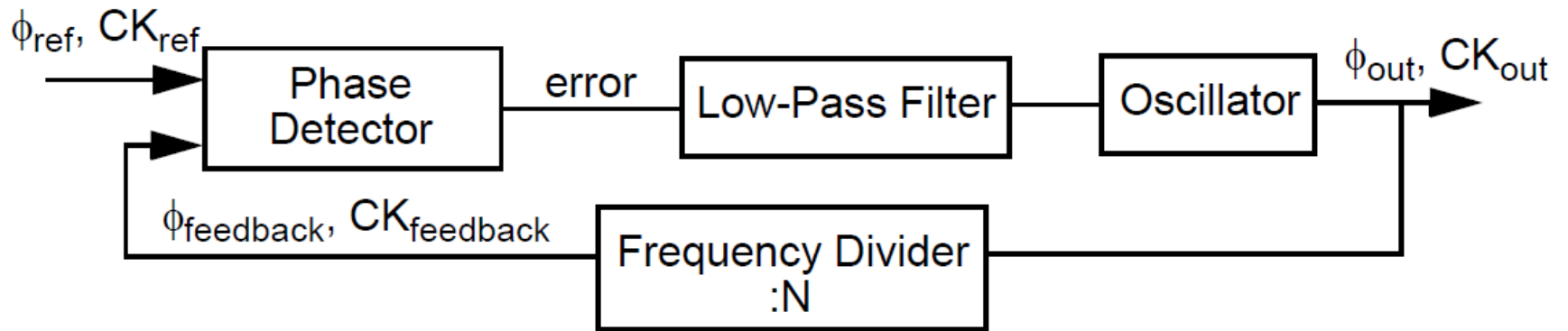



[Mansuri]

Linear PLL Model

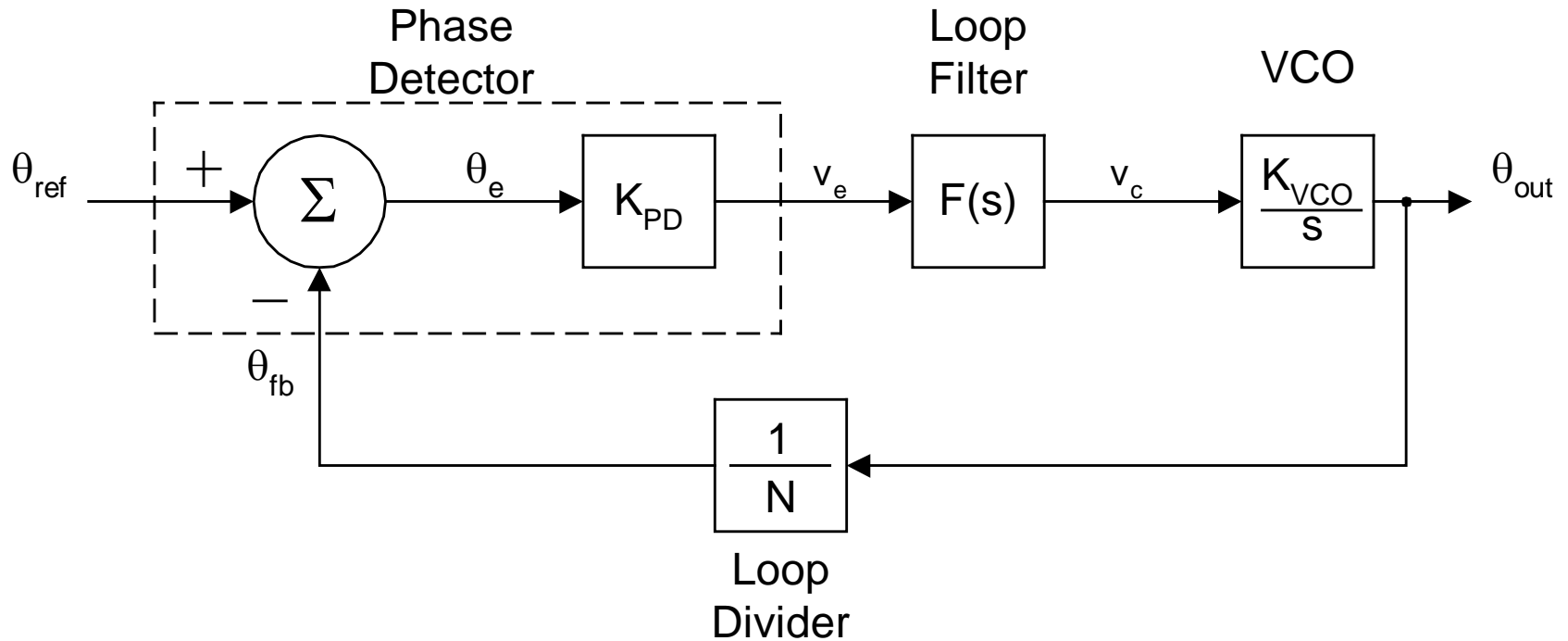


Understanding PLL Frequency Response

- Linear “small-signal” analysis is useful for understand PLL dynamics if
 - PLL is locked (or near lock)
 - Input phase deviation amplitude is small enough to maintain operation in lock range
- Frequency domain analysis can tell us how well the PLL tracks the input phase as it changes at a certain frequency
- PLL transfer function is different depending on which point in the loop the output is responding to

 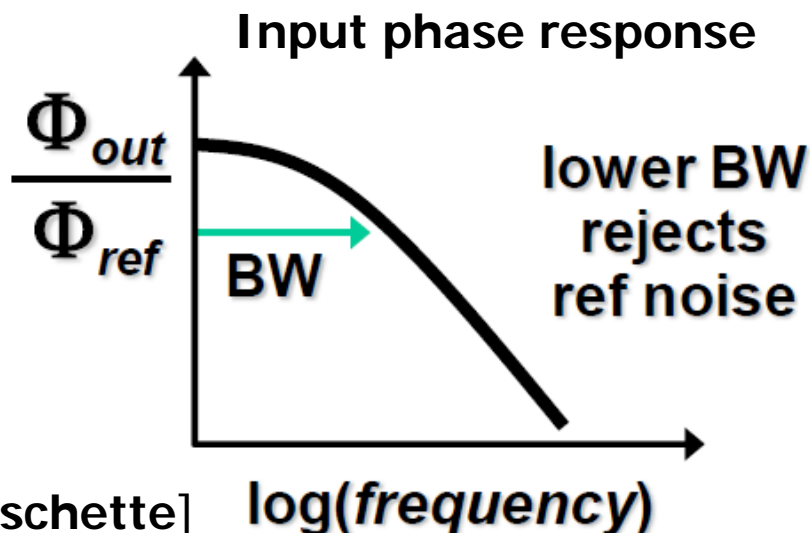


Phase Detector

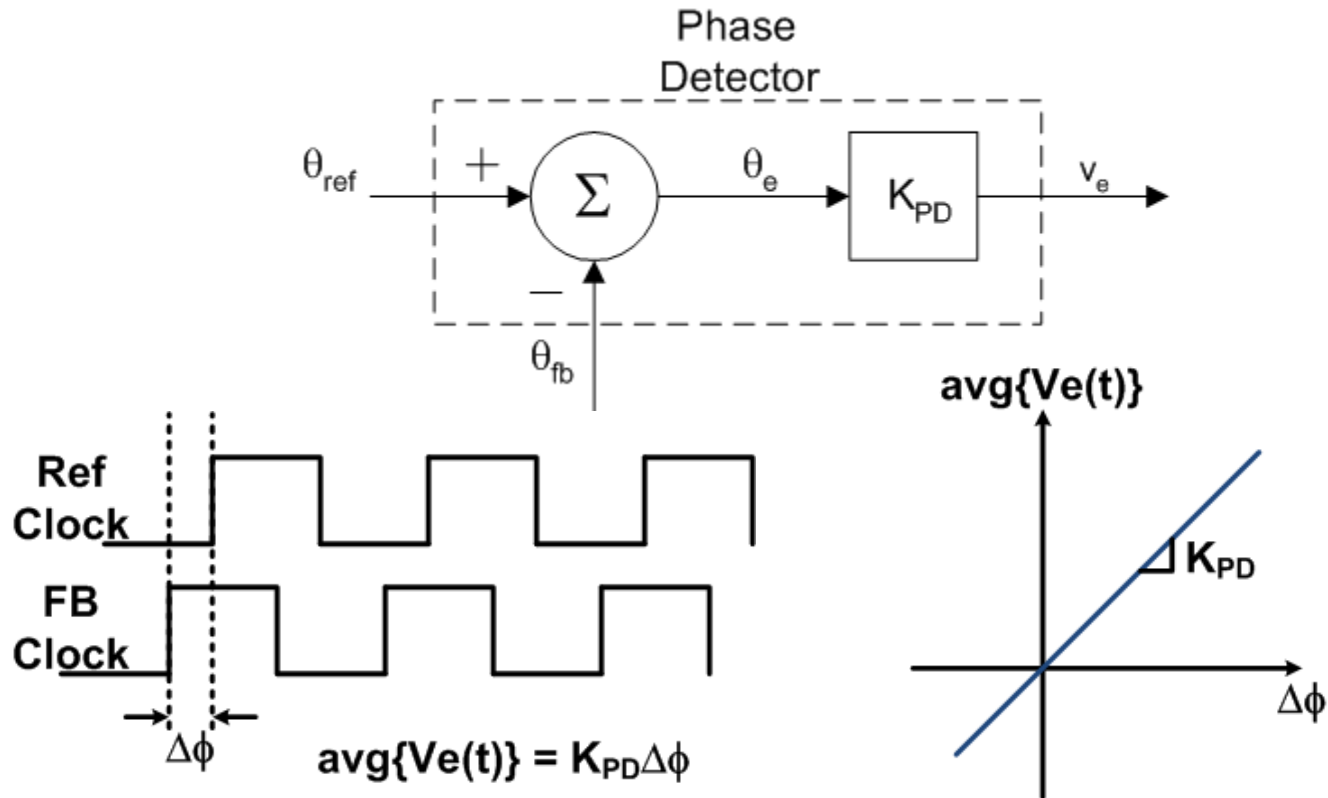


- Detects phase difference between feedback clock and reference clock
- The loop filter will filter the phase detector output, thus to characterize phase detector gain, extract average output voltage (or current for charge-pump PLLs)

Loop Filter

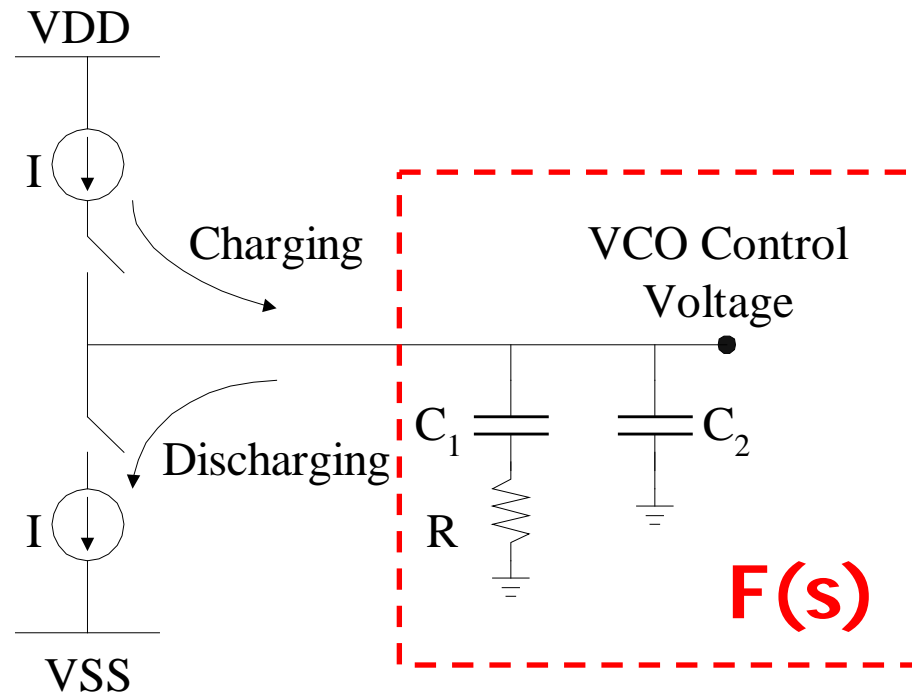

- Lowpass filter extracts average of phase detector error pulses

Voltage-Controlled Oscillator

 


$$\omega_{out}(t) = \omega_0 + \Delta\omega_{out}(t) = \omega_0 + K_{VCO}v_c(t)$$


- Time-domain phase relationship

$$\theta_{out}(t) = \int \Delta\omega_{out}(t)dt = K_{VCO} \int v_c(t)dt$$

Laplace Domain Model

 

Loop Divider

 


- Time-domain model


$$\omega_{fb}(t) = \frac{1}{N} \omega_{out}(t)$$

$$\theta_{fb}(t) = \int \frac{1}{N} \omega_{out}(t) dt = \frac{1}{N} \theta_{out}(t)$$

Linear PLL Model

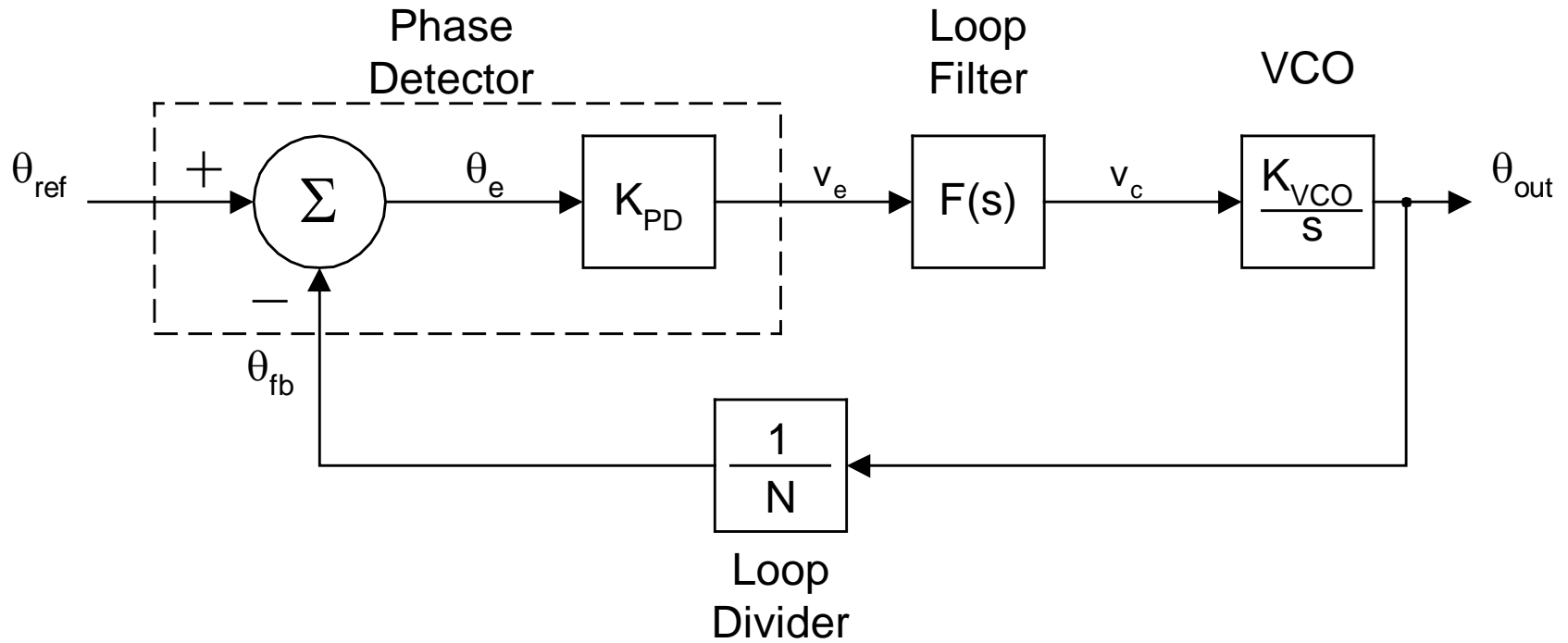


Charge-Pump PLL Linear Model

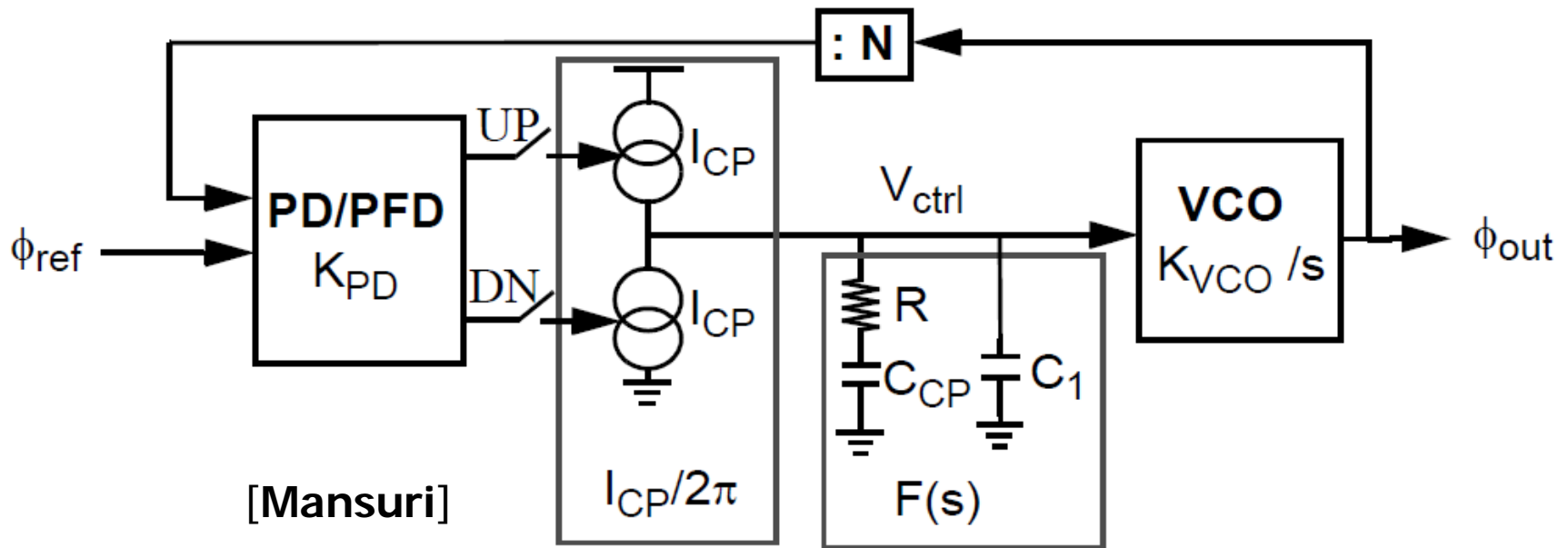

- Charge-pump supplies current to loop filter capacitor which integrates it to produce the VCO control voltage
- For stability, a zero is added with the resistor which gives a proportional gain term

Open-Loop PLL Transfer Function


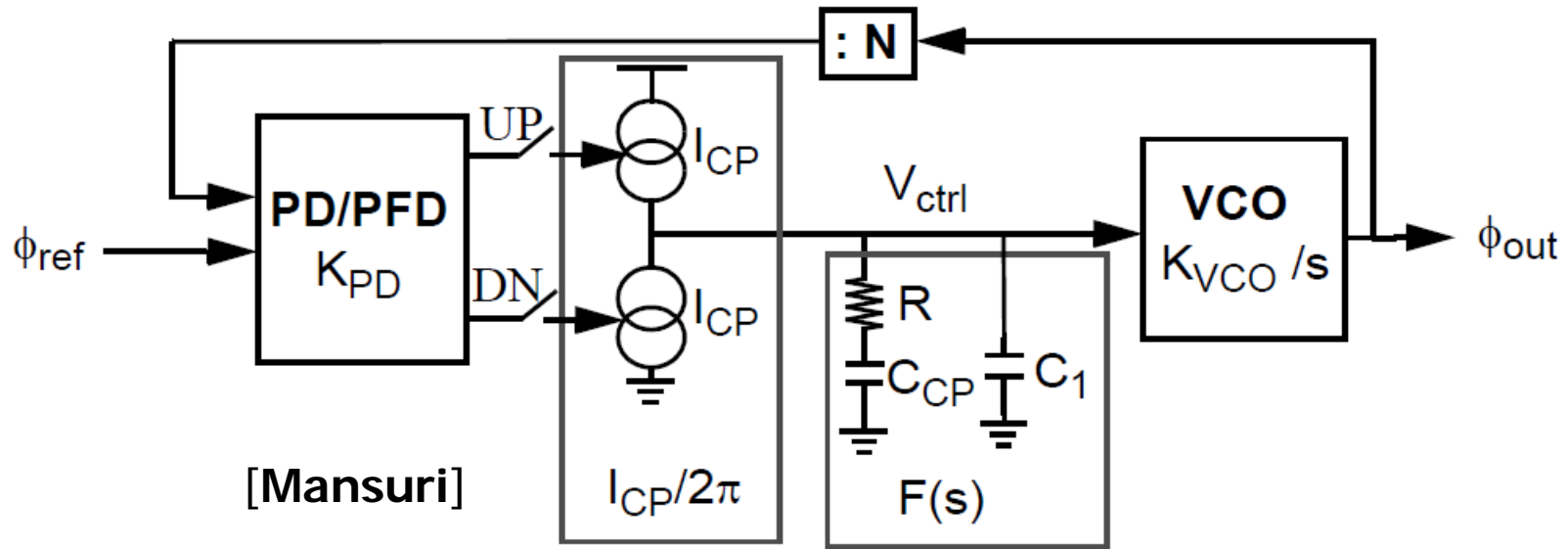


$$H_{open}(s) = K_{PFD} \cdot I_{CP}/2\pi \cdot F(s) \cdot K_{VCO}/s$$


$$\text{ignoring } C_1: H_{open}(s) = K_{PFD} \cdot \frac{I_{CP}}{2\pi \cdot C_{CP}} \cdot (1 + RC_{CP}s) \cdot \frac{K_{VCO}}{s^2}$$

$$\text{with } C_1: H_{open}(s) = K_{PFD} \cdot \frac{I_{CP}}{2\pi \cdot (C_{CP} + C_1)} \cdot (1 + RC_{CP}s) \cdot \frac{K_{VCO}}{s^2 \cdot [1 + R(C_{CP} || C_1)s]}$$

Open-Loop PLL Transfer Function

 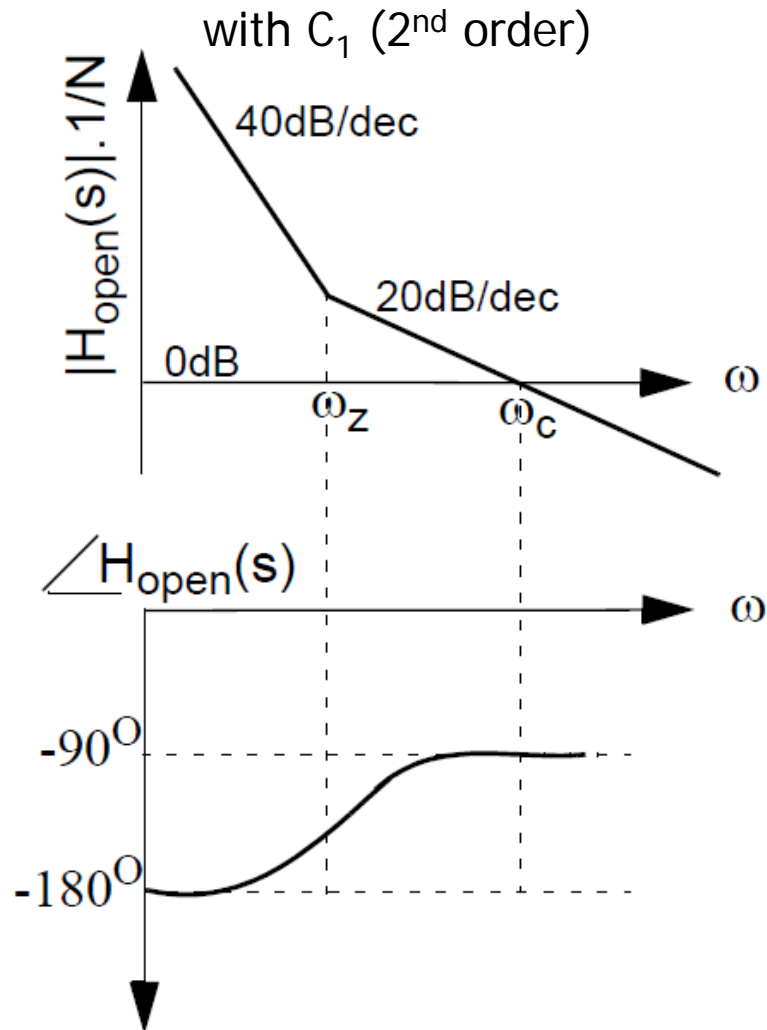

Closed-Loop PLL Transfer Function

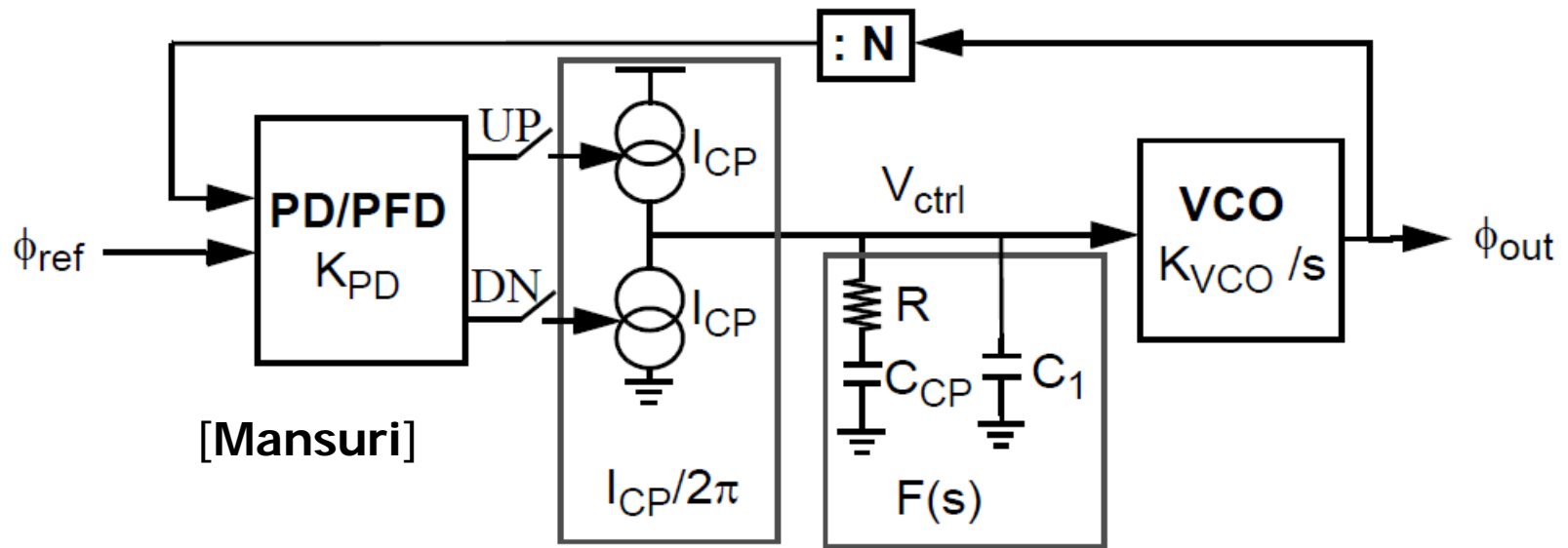

$$\frac{\phi_{out}(s)}{\phi_{in}} = H_{closed}(s) = \frac{H_{open}(s)}{1 + H_{open}(s) \cdot 1/N}$$

ignoring C_1 :

$$\frac{\phi_{out}(s)}{\phi_{in}} = \frac{K_{Loop} \cdot (1 + RC_{CP}s)}{s^2 + (K_{Loop}/N)RC_{CP}s + K_{Loop}/N}$$

$$K_{Loop} = K_{PFD} \cdot K_{VCO} \cdot I_{CP} / (2\pi C_{CP})$$

PLL Natural Frequency and Damping Factor

$$\frac{\phi_{out}(s)}{\phi_{in}} = \frac{K_{Loop} \cdot (1 + RC_{CP}s)}{s^2 + (K_{Loop}/N)RC_{CP}s + K_{Loop}/N}$$

Standard 2nd-order denominator: $s^2 + 2\zeta\omega_n s + \omega_n^2$


Natural Frequency: $\omega_n = \sqrt{\frac{K_{Loop}}{N}}$

Damping Factor: $\zeta = \frac{\omega_n}{2 \cdot \omega_z}$

Loop Bandwidth: $\omega_{3dB} = \omega_n \left(a + \sqrt{a^2 + 1} \right)^{1/2}$

$$a = 2\zeta^2 + 1 - \frac{\omega_n N}{K_{PD} K_{VCO}} \left(4\zeta - \frac{\omega_n N}{K_{PD} K_{VCO}} \right)$$


Damping Factor Impact

 

[Fischette]


- If damping factor is too low, frequency peaking occurs
 - Damping factor ~ 1 is usually preferred
- Excessively high damping also causes peaking
 - Need 3rd order model to observe this

Damping Factor Impact

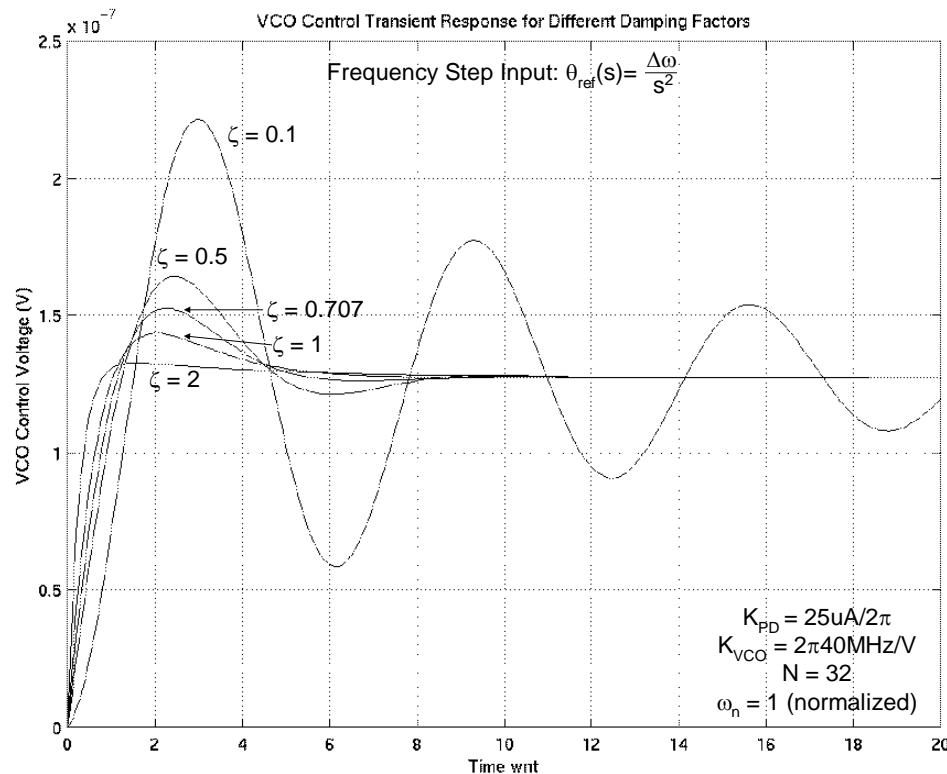


- Peaking in frequency domain leads to ringing in the time domain

PLL Noise Transfer Function

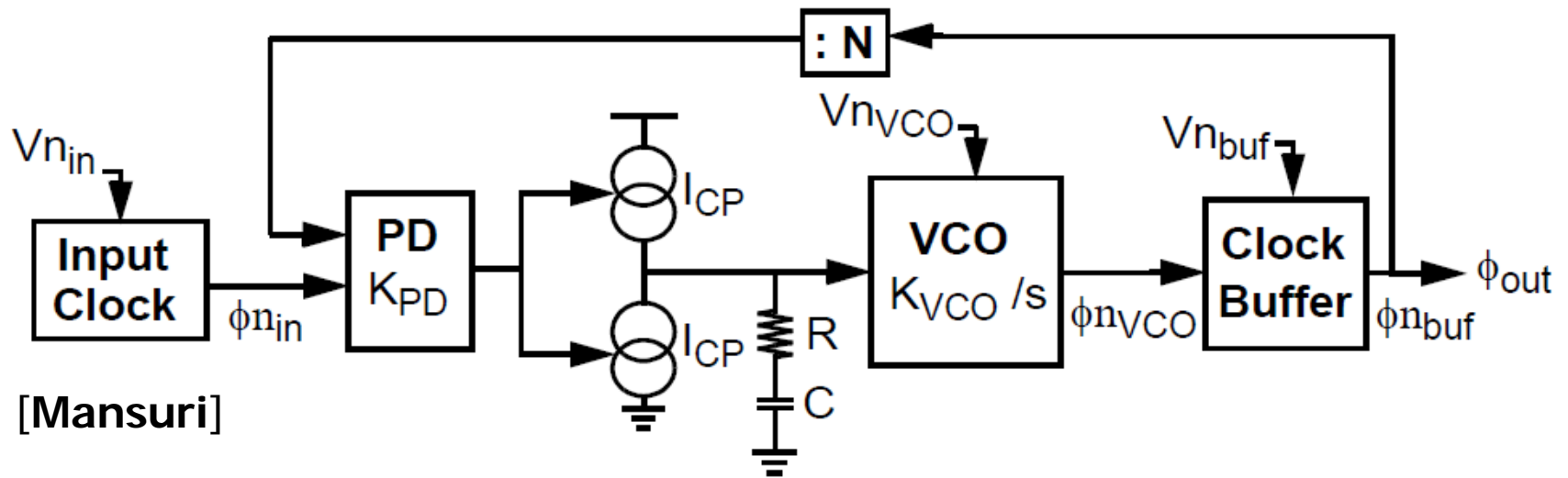

Noise Transfer Functions

 

Next Time

- PLL modeling
- PLL circuits