

# ECEN689: Special Topics in High-Speed Links Circuits and Systems Spring 2010

---

## Lecture 27: PLL Circuits



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

# Announcements

---

- Project Preliminary Report #1 due now
- Exam 2 is still April 30
- Reading
  - Posted clocking papers
  - Website additional links has PLL and jitter tutorials
- Majority of today's material from Fischette tutorial and M. Mansuri's PhD thesis (UCLA)


# Agenda

---

- PLL noise transfer functions
- PLL circuits


# Forward Clock I/O Circuits

## Multi-Channel Serial Link System

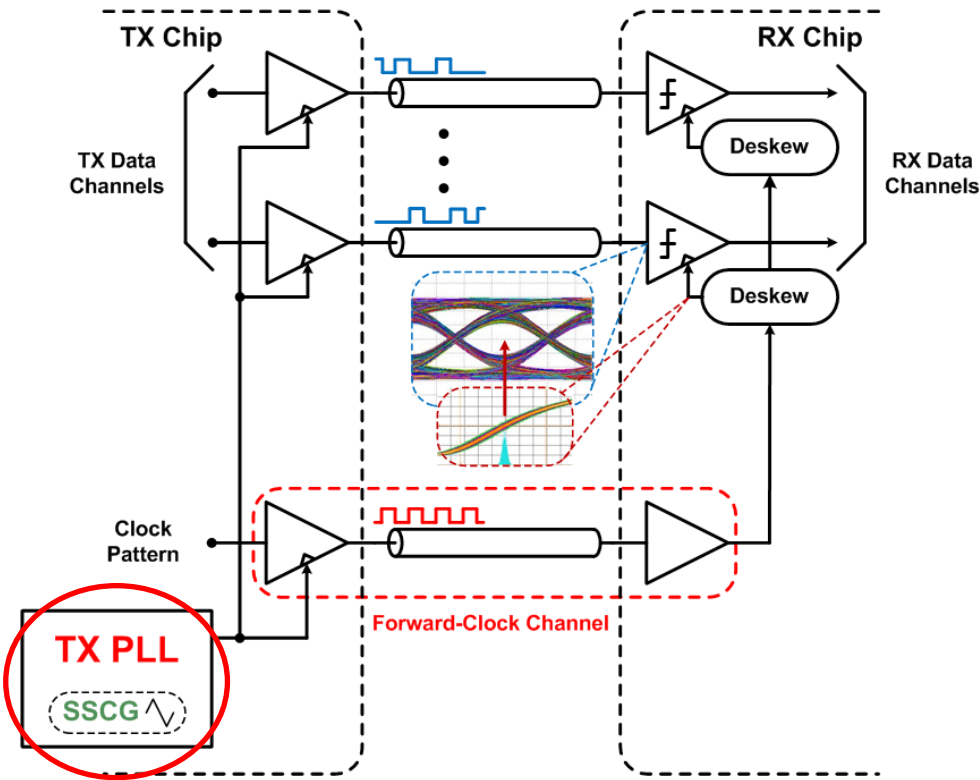

- TX PLL
- TX Clock Distribution
- Replica TX Clock Driver
- Channel
- Forward Clock Amplifier
- RX Clock Distribution
- De-Skew Circuit
  - DLL/PI
  - Injection-Locked Oscillator


# Embedded Clock I/O Circuits

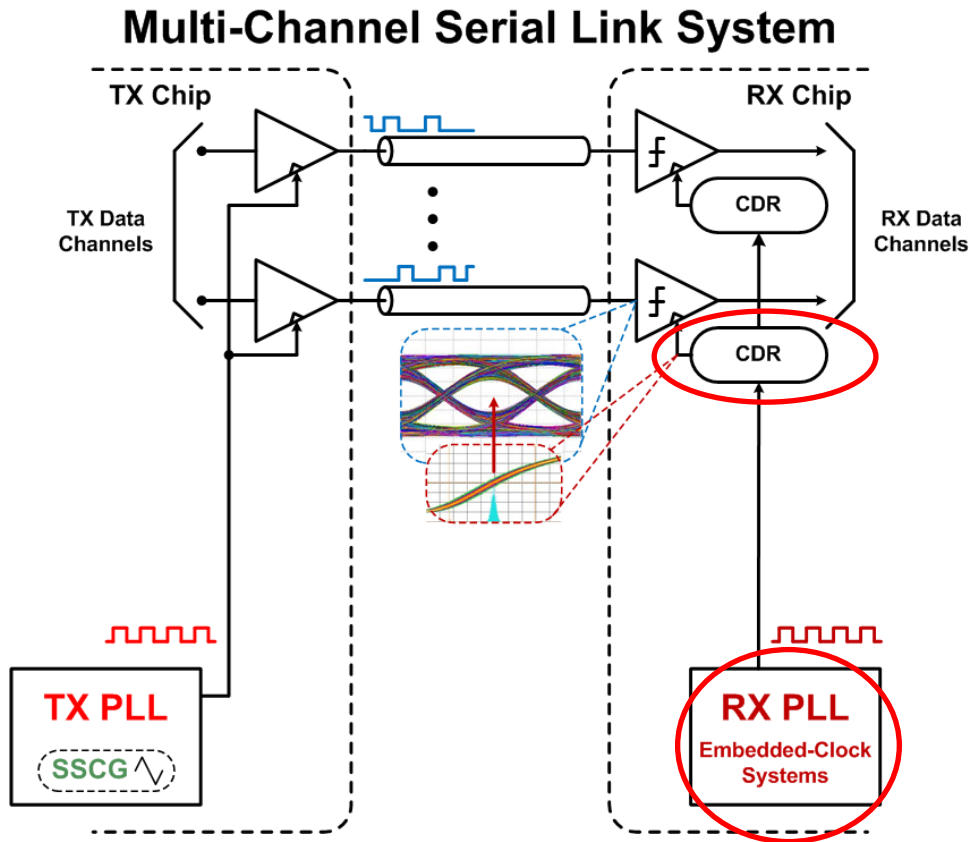

- TX PLL
- TX Clock Distribution
- CDR
  - Per-channel PLL-based
  - Dual-loop w/ Global PLL &
    - Local DLL/PI
    - Local Phase-Rotator PLLs
    - Global PLL requires RX clock distribution to individual channels

# Input Noise Transfer Function

[Mansuri]

 


Input Phase Noise: 
$$H_{n_{IN}}(s) = \frac{\phi_{out}}{\phi_{n_{IN}}} = \frac{K_{Loop}(RCs+1)}{s^2 + \left(\frac{K_{Loop}}{N}\right)RCs + \frac{K_{Loop}}{N}} = \frac{N(2\zeta\omega_n s + \omega_n^2)}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

Voltage Noise on Input Clock Source: 
$$T_{n_{IN}}(s) = \frac{\phi_{out}}{v_{n_{IN}}} = \left(\frac{\phi_{out}}{\phi_{n_{IN}}}\right)\left(\frac{K_o}{s}\right) = \frac{K_o K_{Loop}(RCs+1)}{s\left(s^2 + \left(\frac{K_{Loop}}{N}\right)RCs + \frac{K_{Loop}}{N}\right)}$$

# VCO Noise Transfer Function

[Mansuri]

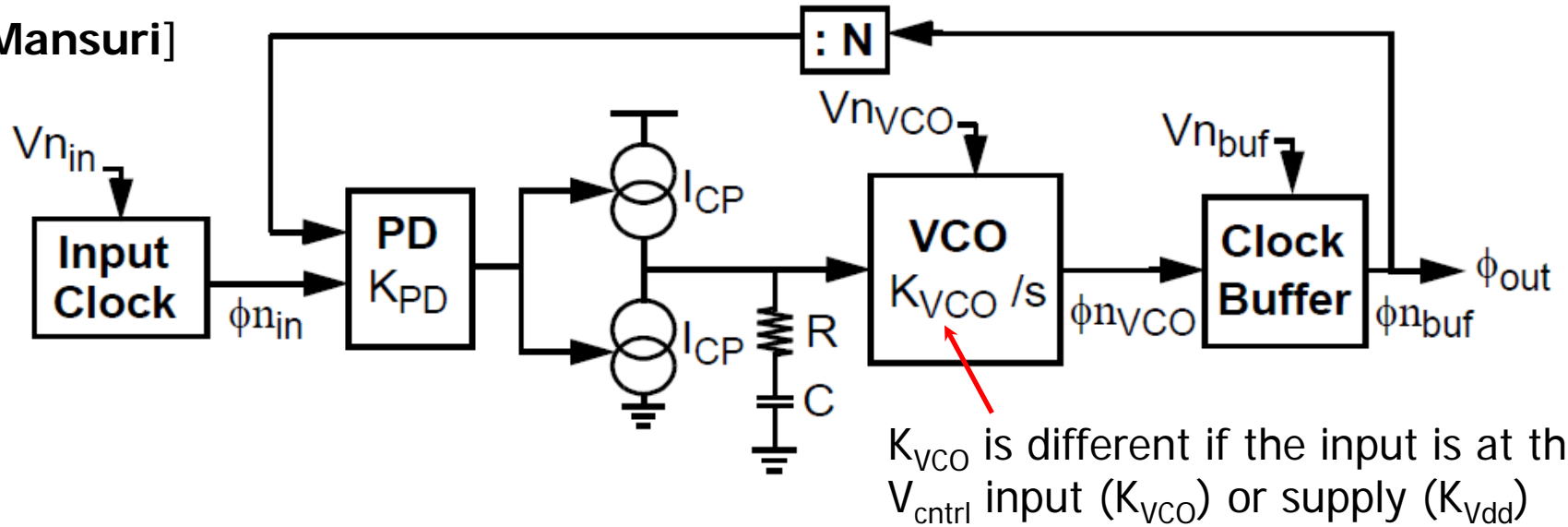

VCO Phase Noise:


$$H_{n_{vco}}(s) = \frac{\phi_{out}}{\phi_{n_{vco}}} = \frac{s^2}{s^2 + \left(\frac{K_{Loop}}{N}\right)RCs + \frac{K_{Loop}}{N}} = \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

Voltage Noise on VCO Inputs:

$$T_{n_{vco}}(s) = \frac{\phi_{out}}{v_{n_{vco}}} = \left(\frac{\phi_{out}}{\phi_{n_{vco}}}\right) \left(\frac{K_{VCO}}{s}\right) = \frac{K_{VCO}s}{s^2 + \left(\frac{K_{Loop}}{N}\right)RCs + \frac{K_{Loop}}{N}}$$

# Clock Buffer Noise Transfer Function

[Mansuri]

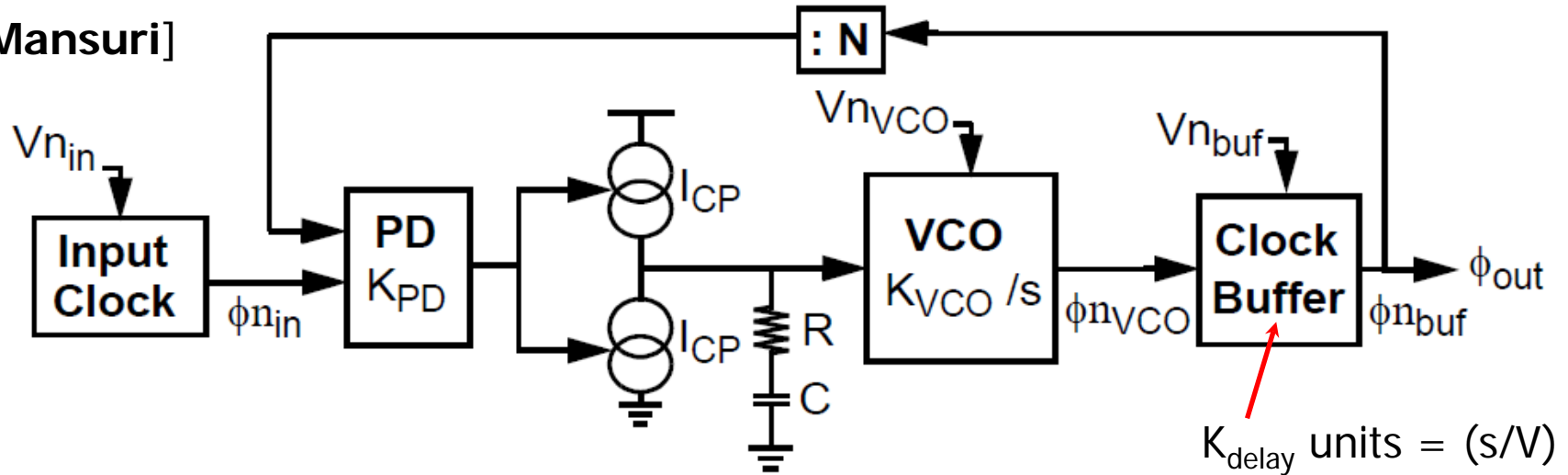


$$\text{Output Phase Noise: } H_{n_{buf}}(s) = \frac{\phi_{out}}{\phi_{n_{buf}}} = \frac{s^2}{s^2 + \left(\frac{K_{Loop}}{N}\right)RCs + \frac{K_{Loop}}{N}} = \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

Voltage Noise on Buffer Inputs:

$$T_{n_{buf}}(s) = \frac{\phi_{out}}{v_{n_{buf}}} = \left(\frac{\phi_{out}}{\phi_{n_{buf}}}\right) \left(\frac{K_{delay}\omega_{VCO}}{\frac{s}{\omega_{buf}} + 1}\right) = \left(\frac{K_{delay}\omega_{VCO}}{\frac{s}{\omega_{buf}} + 1}\right) \frac{s^2}{s^2 + \left(\frac{K_{Loop}}{N}\right)RCs + \frac{K_{Loop}}{N}} \approx \frac{K_{delay}\omega_{VCO}s^2}{s^2 + \left(\frac{K_{Loop}}{N}\right)RCs + \frac{K_{Loop}}{N}}$$




# Noise Transfer Functions

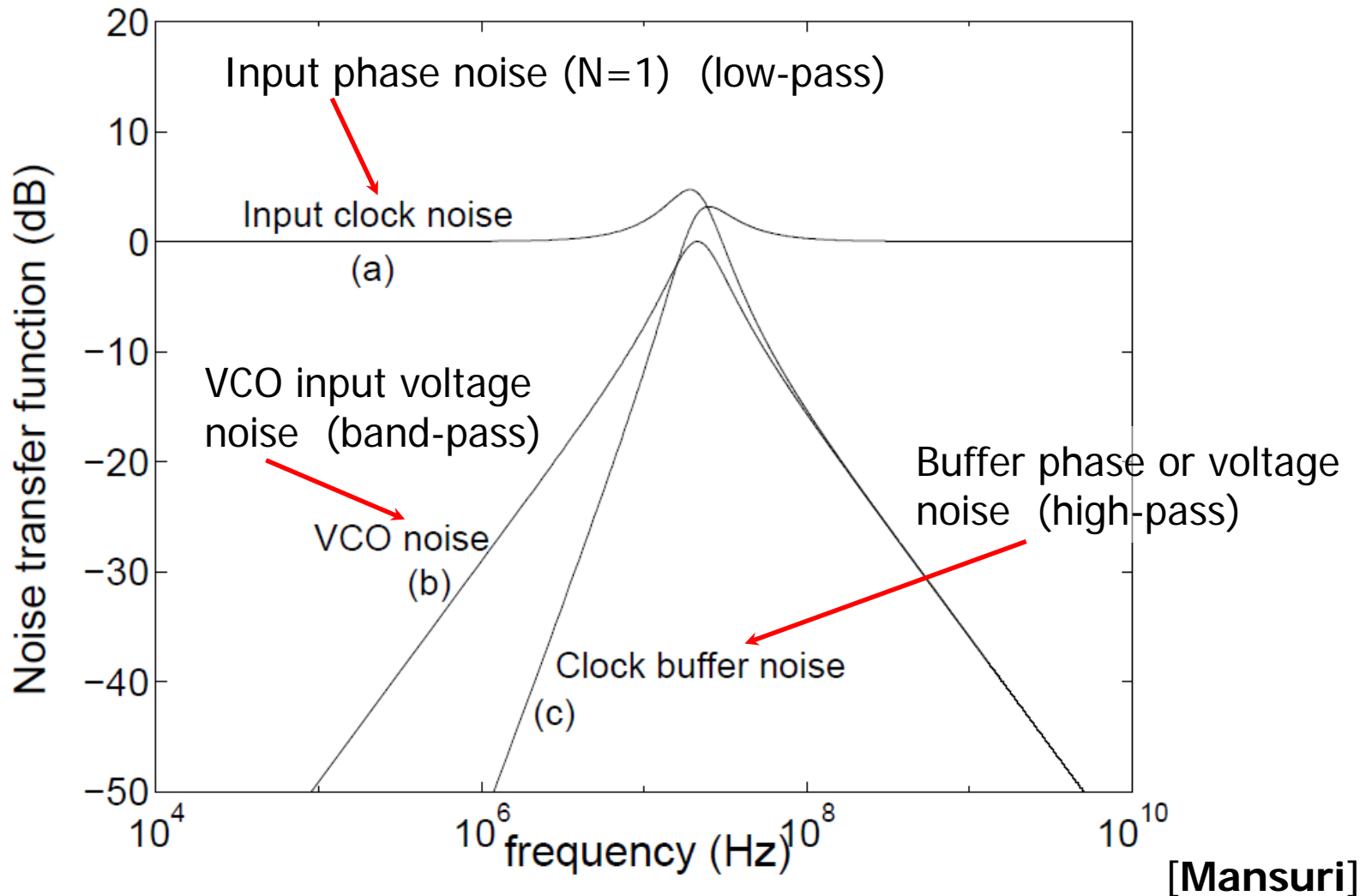

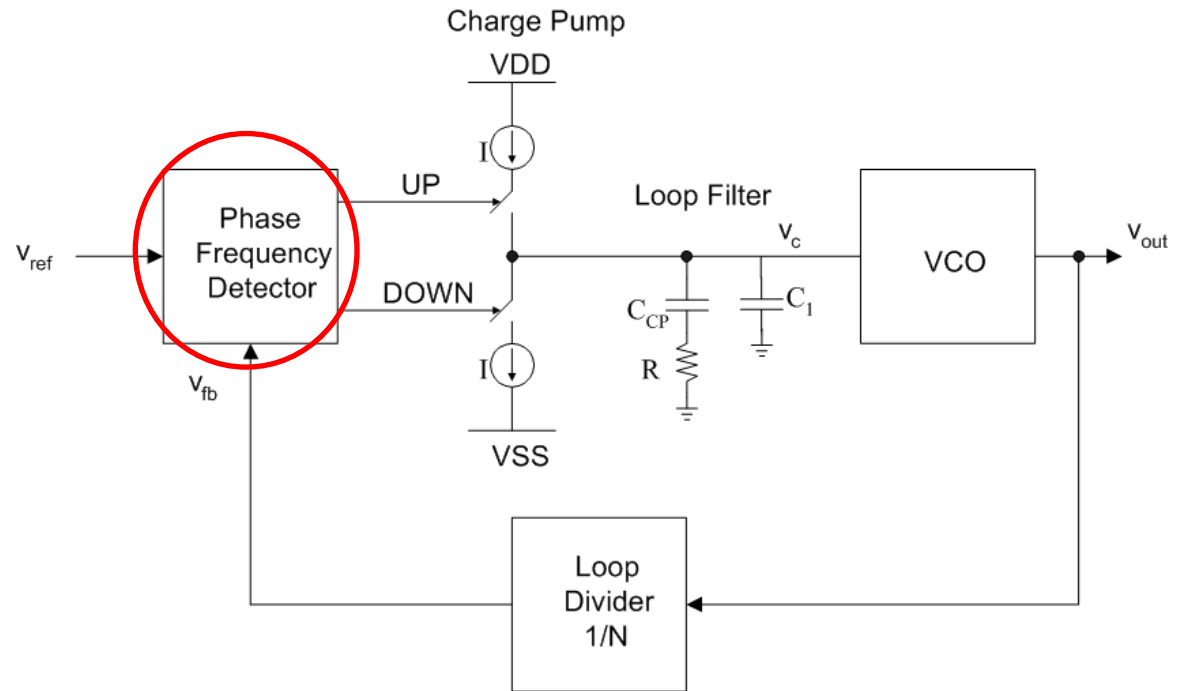
# Charge-Pump PLL Circuits

- Phase Detector
- Charge-Pump
- Loop Filter
- VCO
- Divider




# Phase Detector

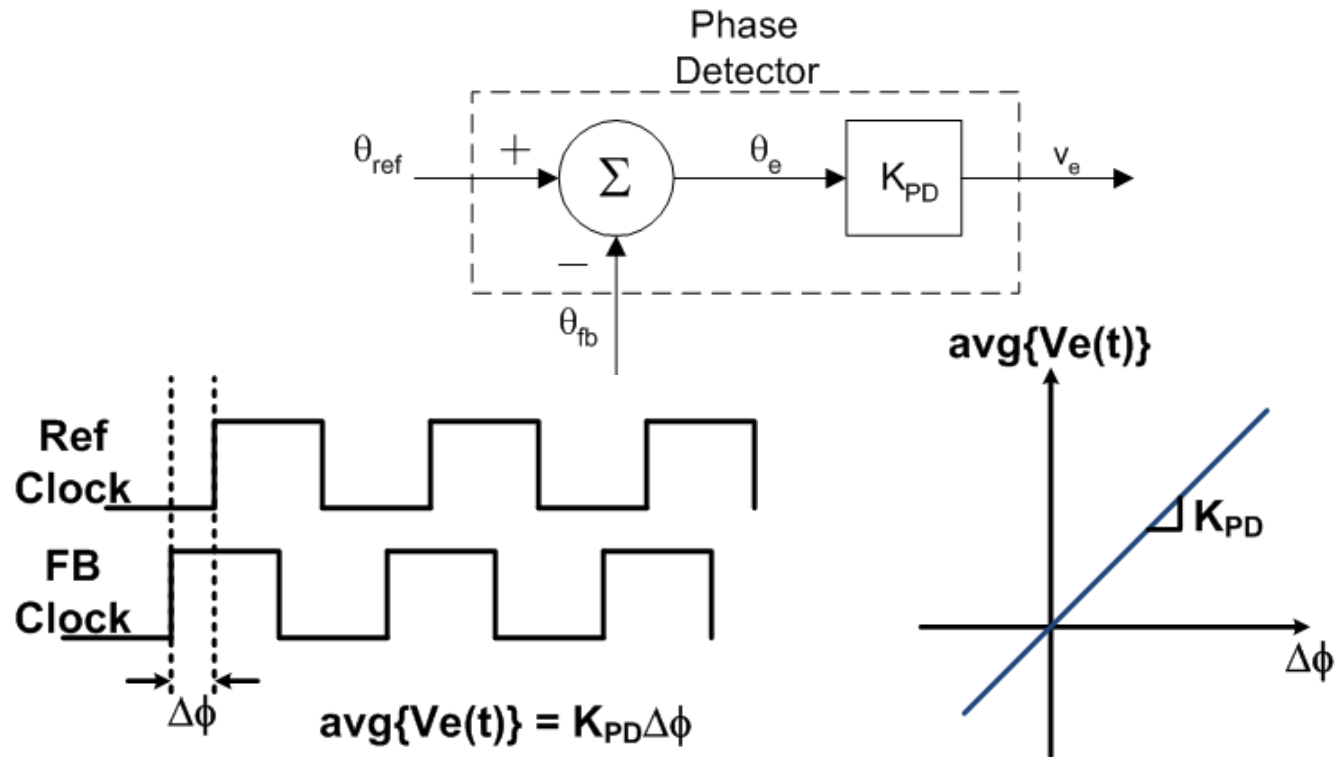

- Detects phase difference between feedback clock and reference clock
- The loop filter will filter the phase detector output, thus to characterize phase detector gain, extract average output voltage (or current for charge-pump PLLs)
- Can be analog or digital


# Analog Multiplier Phase Detector

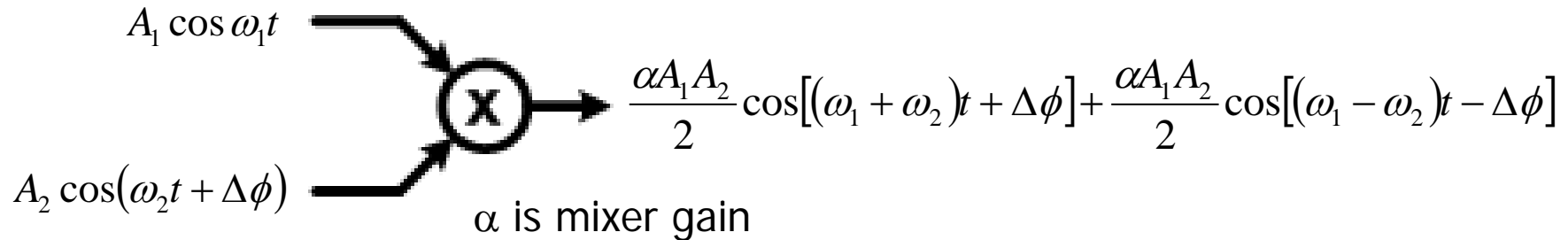

- If  $\omega_1 = \omega_2$  and filtering out high-frequency term


$$\overline{y(t)} = \frac{\alpha A_1 A_2}{2} \cos \Delta\phi$$

 - Near  $\Delta\phi$  lock region of  $\pi/2$ :  $\overline{y(t)} \approx \frac{\alpha A_1 A_2}{2} \left( \frac{\pi}{2} - \Delta\phi \right)$




[Razavi]

# XOR Phase Detector

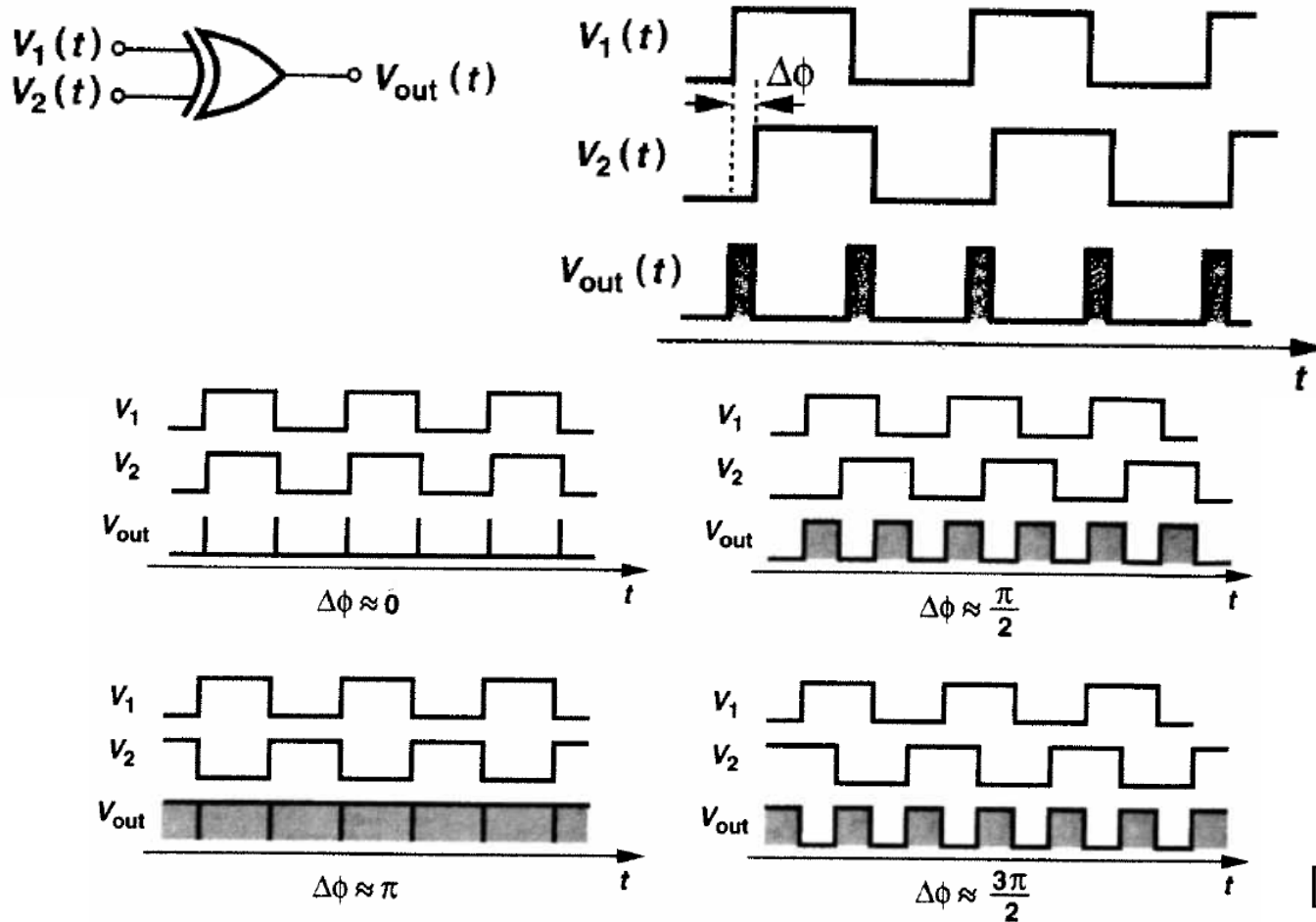


- Sensitive to clock duty cycle

# XOR Phase Detector

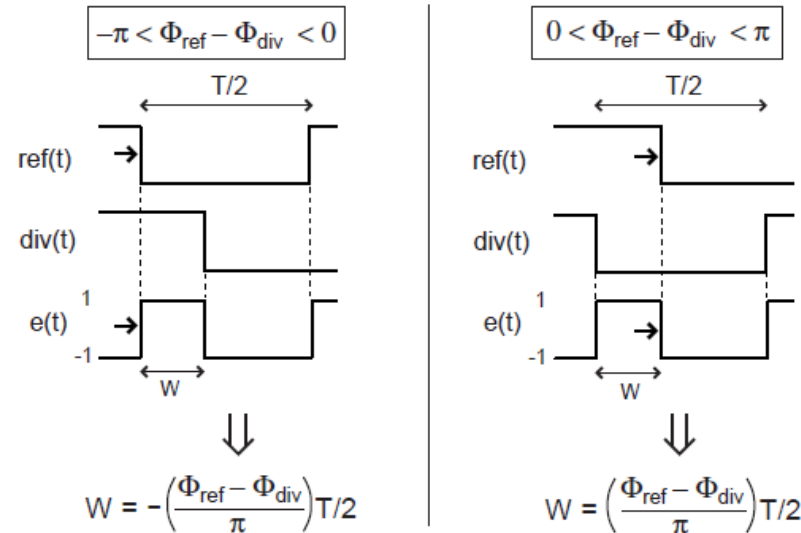


[Perrott]

 

 
# Cycle Slipping

- If there is a frequency difference between the input reference and PLL feedback signals the phase detector can jump between regions of different gain
  - PLL is no longer acting as a linear system



# Cycle Slipping

 



[Perrott]

- If frequency difference is too large the PLL may not lock


  
# Phase Frequency Detector (PFD)


- Phase Frequency Detector allows for wide frequency locking range, potentially entire VCO tuning range
- 3-stage operation with UP and DOWN outputs
- Edge-triggered results in duty cycle insensitivity



# PFD Transfer Characteristic

UP=1 & DN=-1



avg{e(t)}

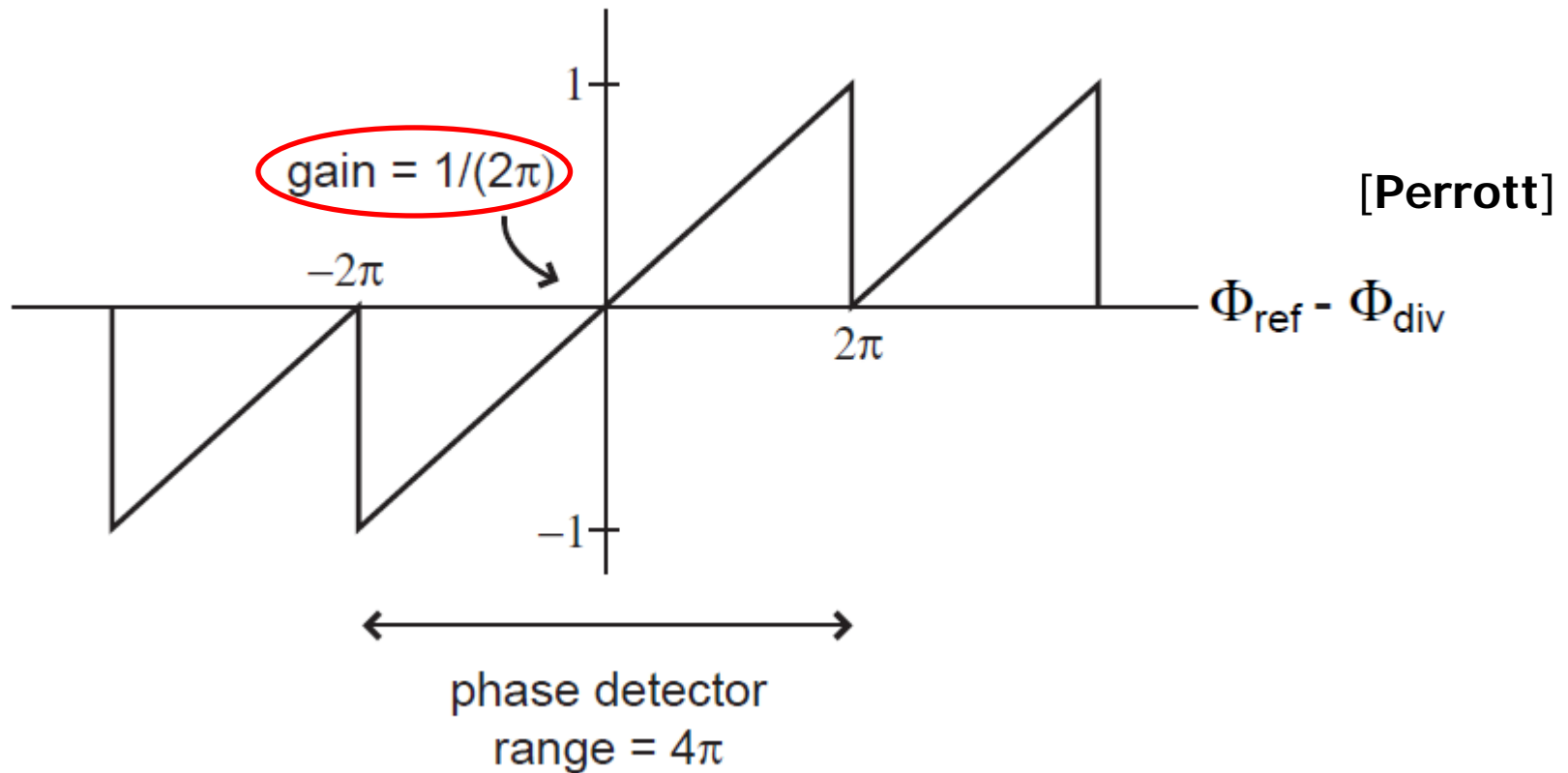

- Constant slope and polarity asymmetry about zero phase allows for wide frequency range operation

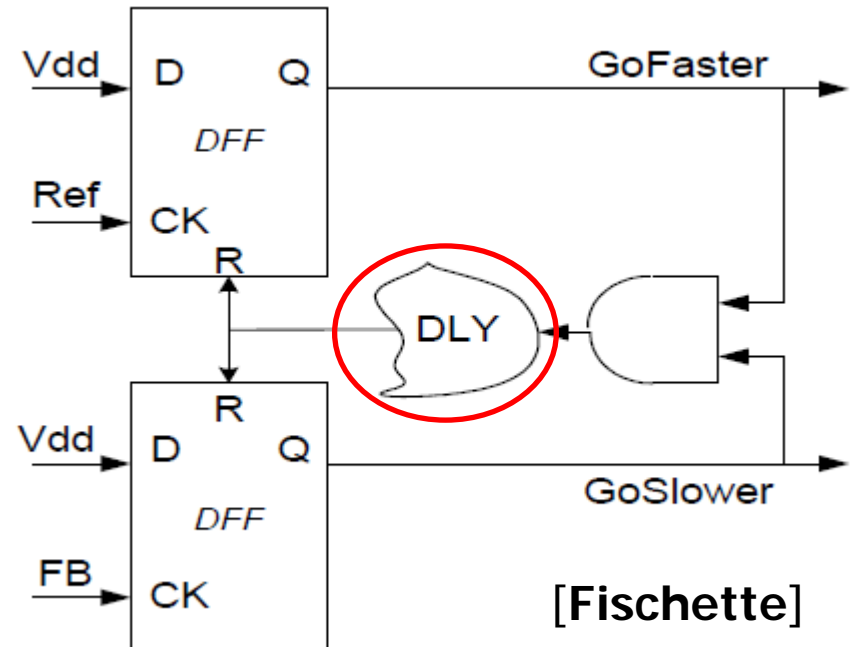 
# PFD Deadzone

- If phase error is small, then short output pulses are produced by PFD
- Cannot effectively propagate these pulses to switch charge pump
- Results in phase detector “dead zone” which causes low loop gain and increased jitter
- Solution is to add delay in PFD reset path to force a minimum UP and DOWN pulse length



# PFD Operation


---

 


[Fischette]
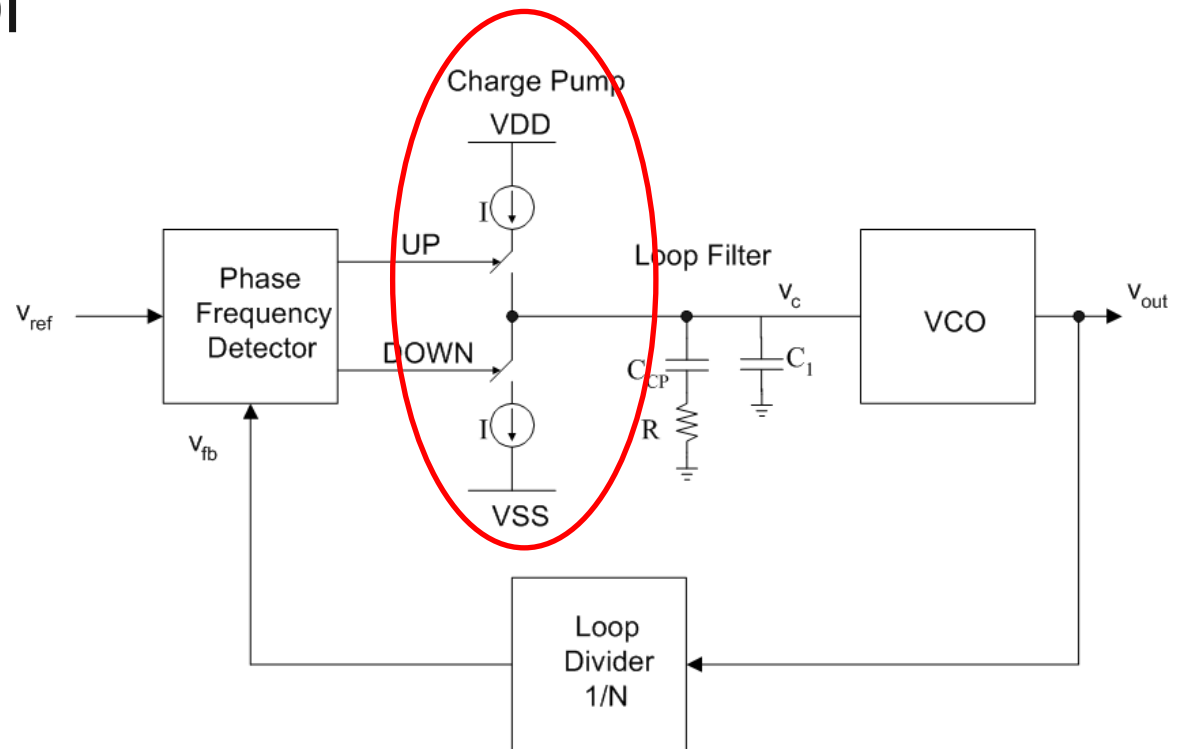
# Charge-Pump PLL Circuits

- Phase Detector
- Charge-Pump
- Loop Filter
- VCO
- Divider




# Charge Pump

 

- Converts PFD output signals to charge
- Charge is proportional to PFD pulse widths

$$\text{PFD-CP Gain: } \left( \frac{1}{2\pi} \right) I_{CP}$$



# Simple Charge Pump

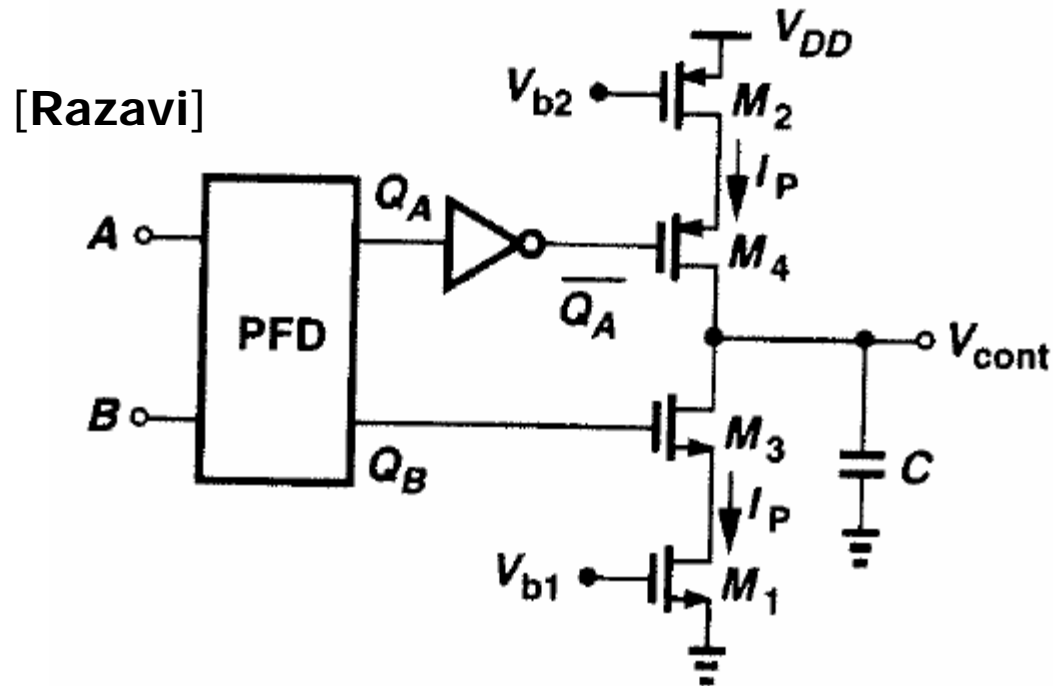

- Issues

- Switch resistance can vary  $V_{ctrl}$  due to body effect
- Charge injection from switches onto  $V_{ctrl}$
- Charge sharing between current source drain nodes and  $V_{ctrl}$

# Charge Pump Mismatch

  


[Razavi]

- PLL will lock with static phase error
- Extra "ripple" on  $V_{ctrl}$ 
  - Results in frequency domain spurs at the reference clock frequency offset from the carrier



# Charge Pump w/ Improved Matching

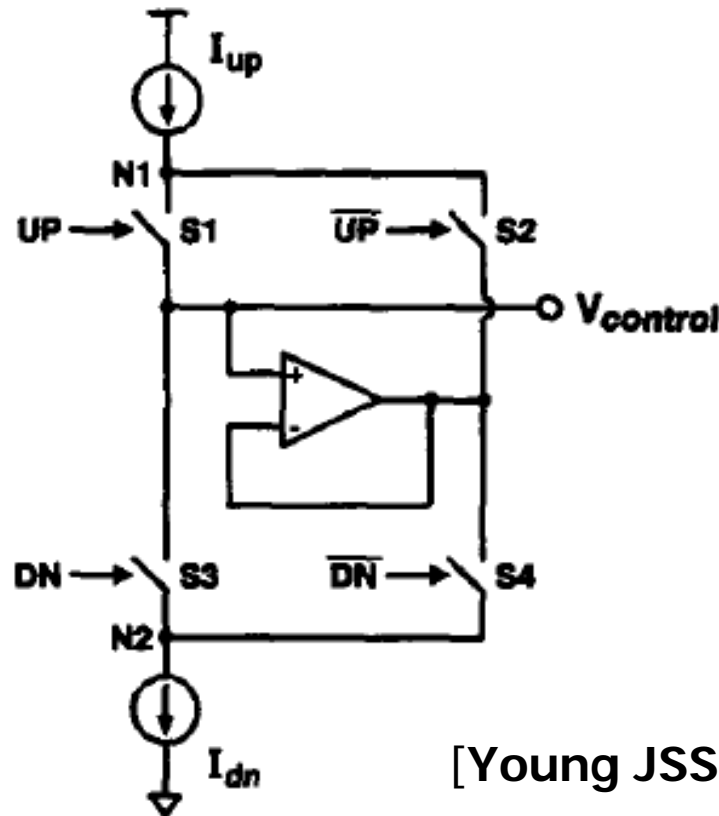


[Young JSSC 1992]

- Amplifier keeps current source  $V_{ds}$  voltages constant resulting in reduced transient current mismatch
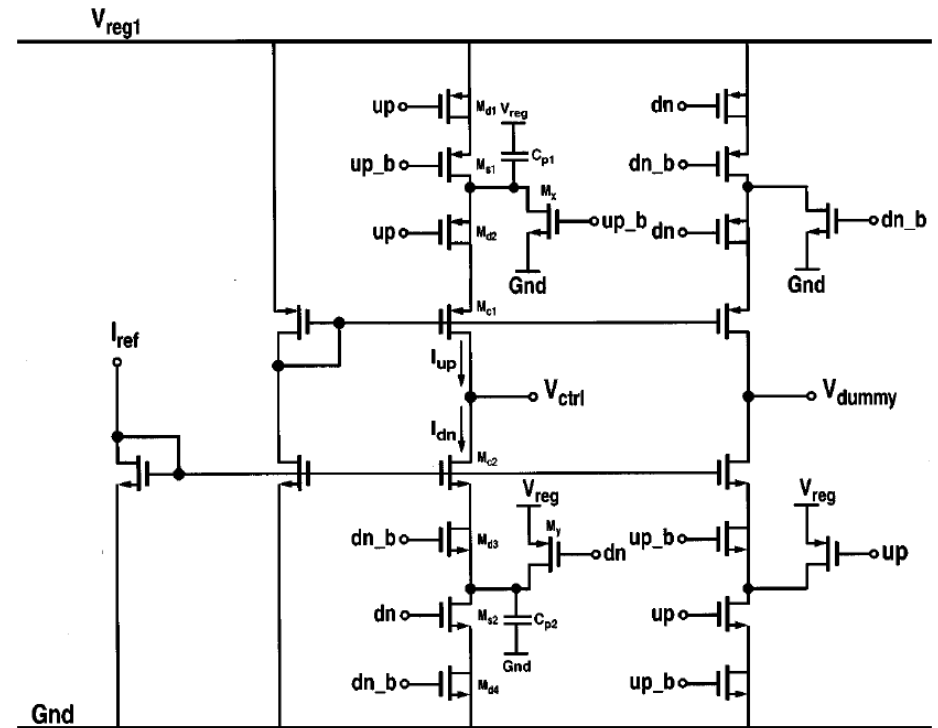
# Charge Pump w/ Reversed Switches


- Swapping switches reduces charge injection
  - MOS caps ( $M_{d1-4}$ ) provide extra charge injection cancellation
- Helper transistors  $M_x$  and  $M_y$  quickly turn-off current source
- Dummy branch helps to match PFD loading




[Ingino JSSC 2001]
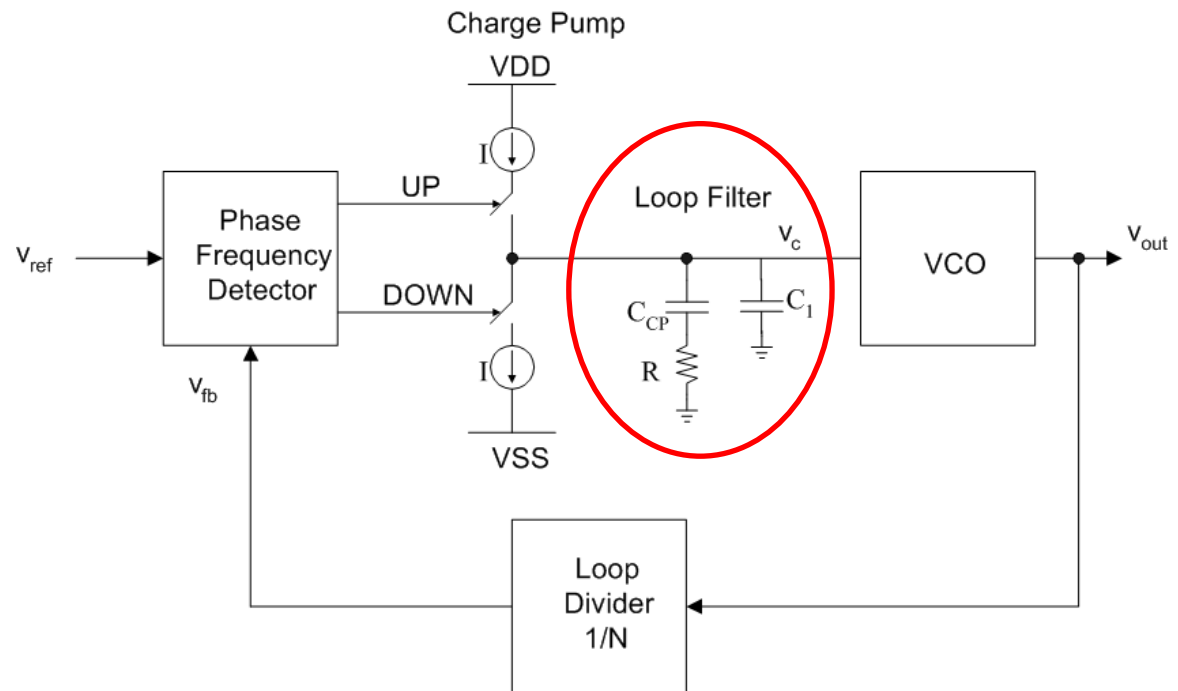
# Charge-Pump PLL Circuits

- Phase Detector
- Charge-Pump
- **Loop Filter**
- VCO
- Divider




# Loop Filter

 


- Lowpass filter extracts average of phase detector error pulses

# Loop Filter Transfer Function

- Neglecting secondary capacitor,  $C_2$

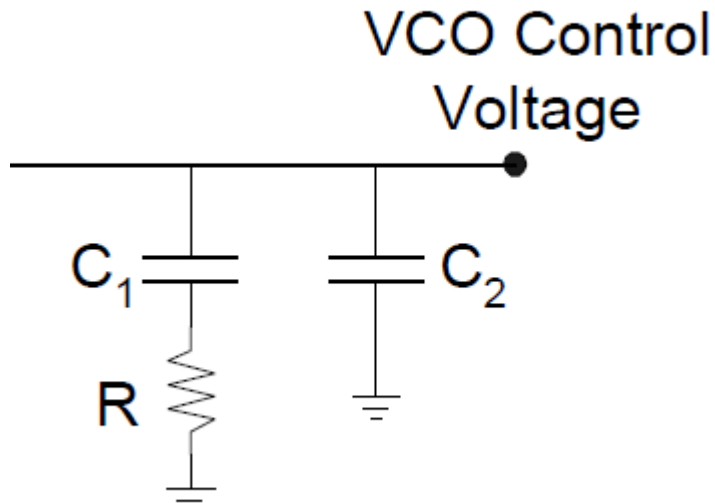

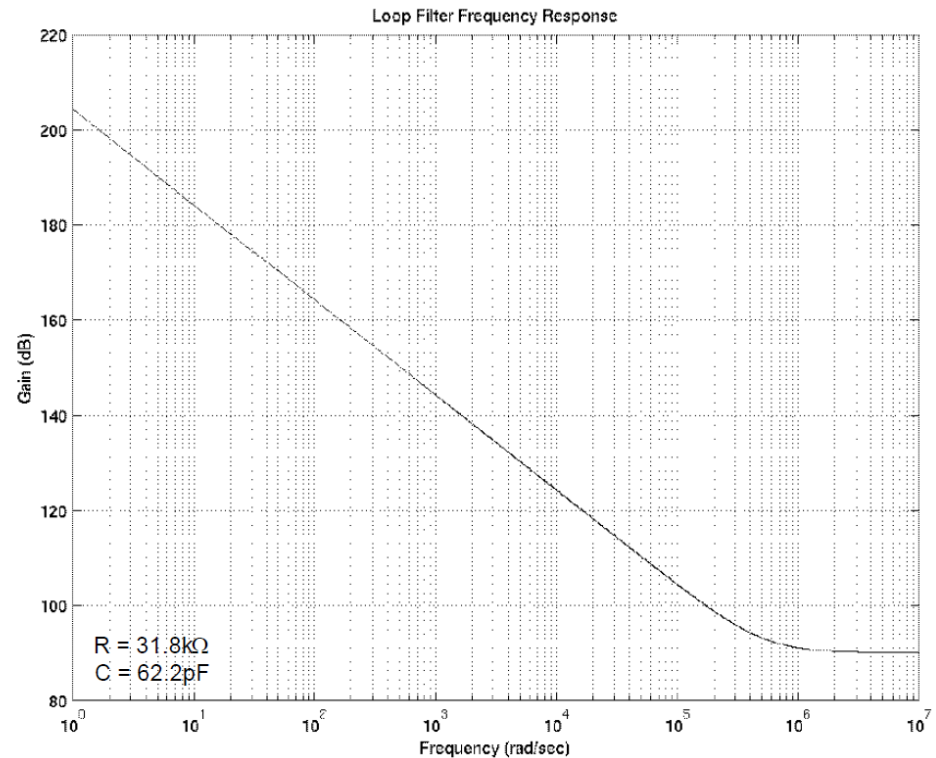
$$F(s) = \frac{V_c(s)}{I_e(s)} = \frac{R \left( s + \frac{1}{RC_1} \right)}{s}$$




# Loop Filter Transfer Function

- With secondary capacitor,  $C_2$

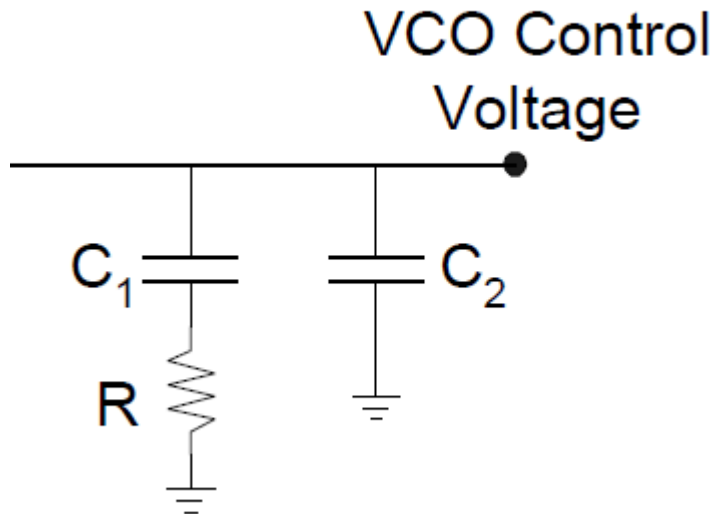

$$Z(s) = \frac{1}{C_2} \left( s + \frac{1}{RC_1} \right) \frac{1}{s^2 + \frac{s(C_1 + C_2)}{RC_1 C_2}}$$

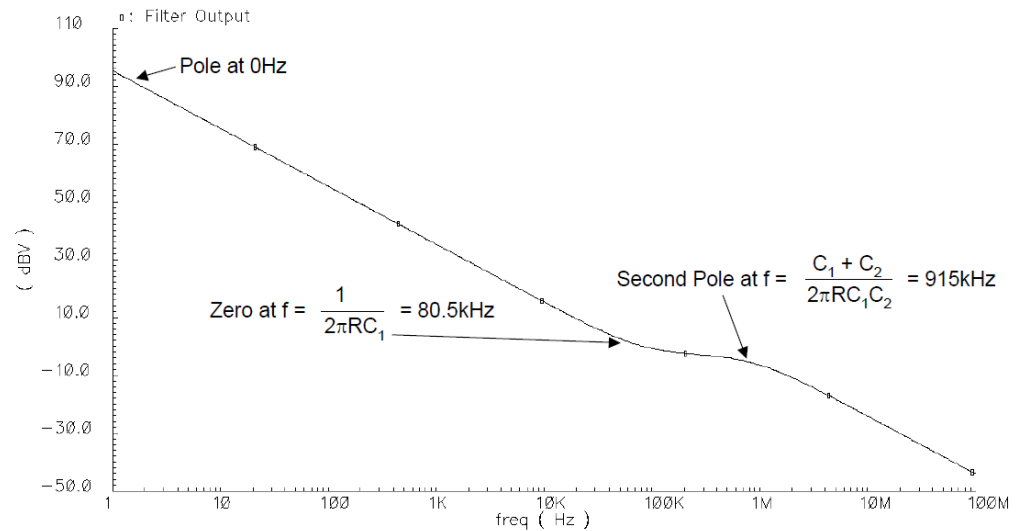
Layout Extracted Loop Filter Frequency Response




# Why have C2?

- Secondary capacitor smoothes control voltage ripple
- Can't make too big or loop will go unstable
  - $C_2 < C_1/10$  for stability
  - $C_2 > C_1/50$  for low jitter

PLL Synthesizing a 380MHz Signal

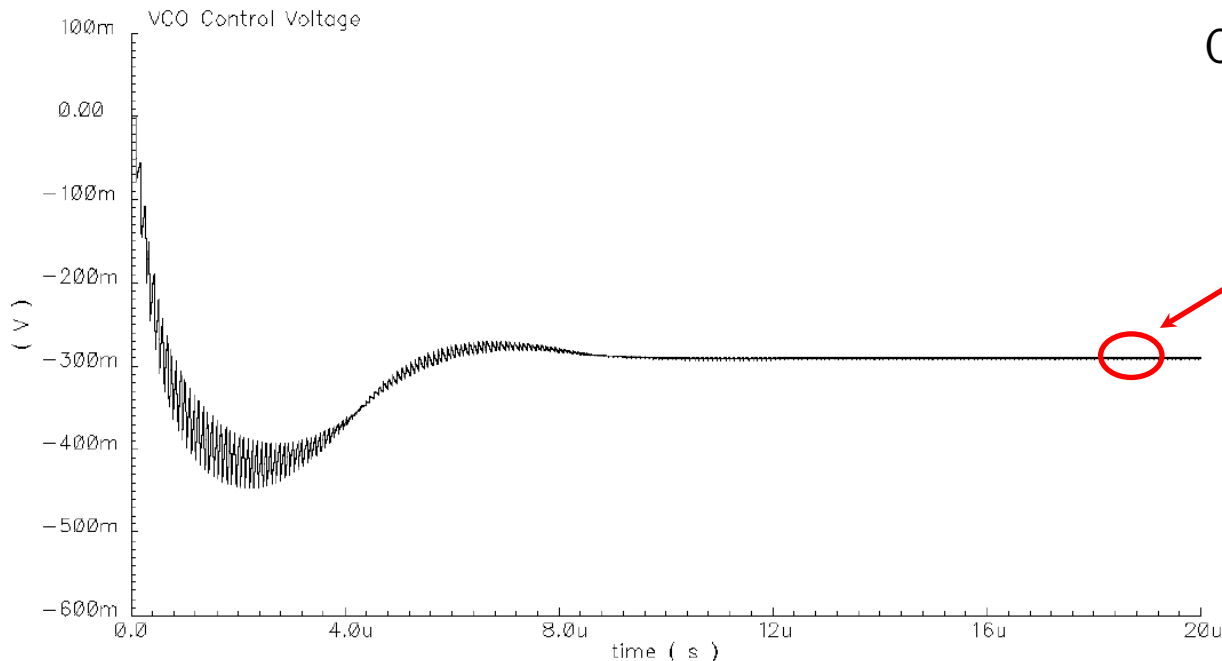

Control Voltage Ripple

 

# Filter Capacitors


---

- To minimize area, we would like to use highest density caps
- Thin oxide MOS cap gate leakage can be an issue
  - Similar to adding a non-linear parallel resistor to the capacitor
  - Leakage is voltage and temperature dependent
  - Will result in excess phase noise and spurs
- Metal caps or thick oxide caps are a better choice
  - Trade-off is area
- Metal cap density can be  $< 1/10$  thin oxide caps
- Filter cap frequency response can be relatively low, as PLL loop bandwidths are typically 1-50MHz



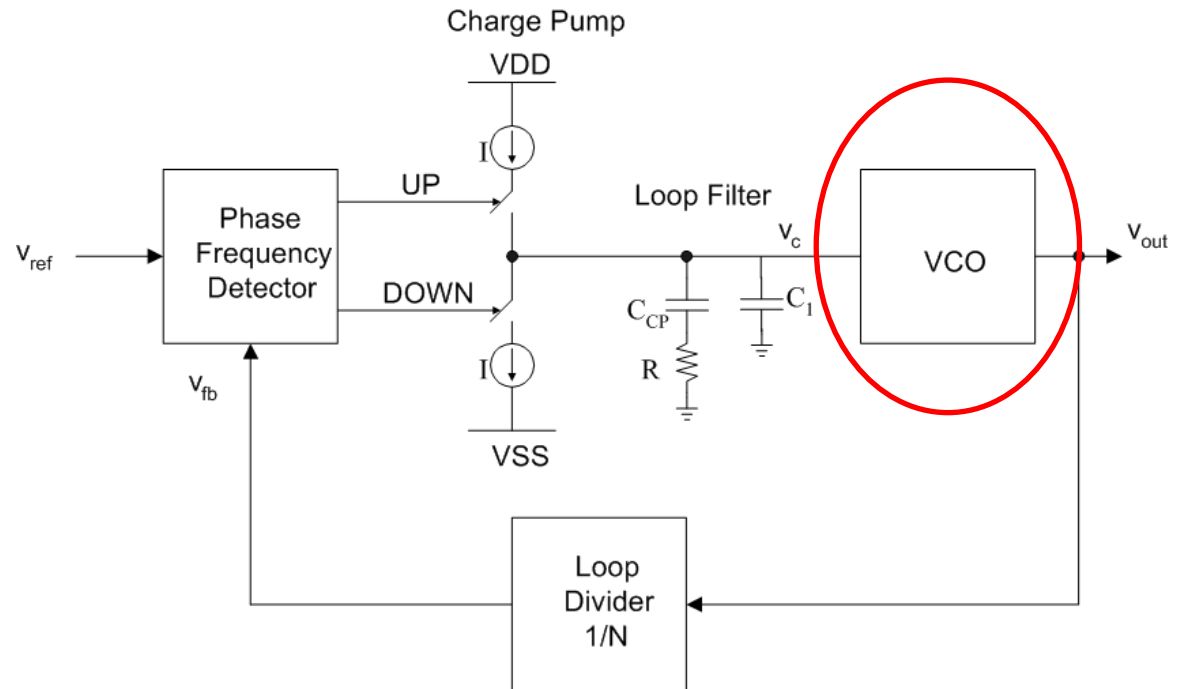
# Charge-Pump PLL Circuits

- Phase Detector
- Charge-Pump
- Loop Filter
- VCO
- Divider



# Voltage-Controlled Oscillator

 


$$\omega_{out}(t) = \omega_0 + \Delta\omega_{out}(t) = \omega_0 + K_{VCO}v_c(t)$$

- Time-domain phase relationship

$$\theta_{out}(t) = \int \Delta\omega_{out}(t)dt = K_{VCO} \int v_c(t)dt$$


Laplace Domain Model

 
 
# Voltage-Controlled Oscillators (VCO)


- Ring Oscillator

- Easy to integrate
- Wide tuning range (5x)
- Higher phase noise




- LC Oscillator

 - Large area
- Narrow tuning range (20-30%)
- Lower phase noise



# Barkhausen's Oscillation Criteria


---

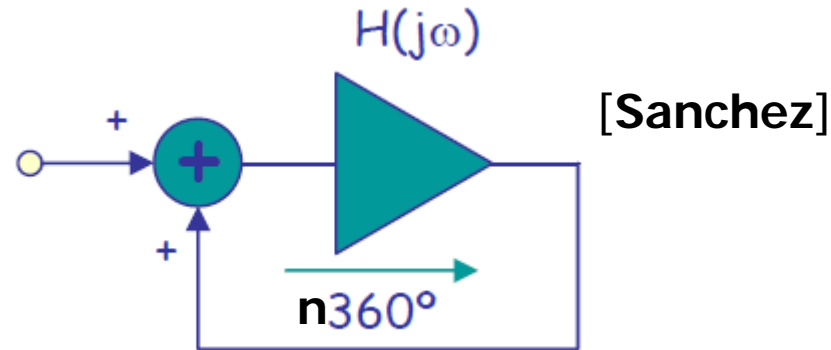

Closed-loop transfer function:  $\frac{H(j\omega)}{1-H(j\omega)}$

- Sustained oscillation occurs if  $H(j\omega)=1$
- 2 conditions:
  - Gain = 1 at oscillation frequency  $\omega_0$
  - Total phase shift around loop is  $n360^\circ$  at oscillation frequency  $\omega_0$

# Ring Oscillator Example

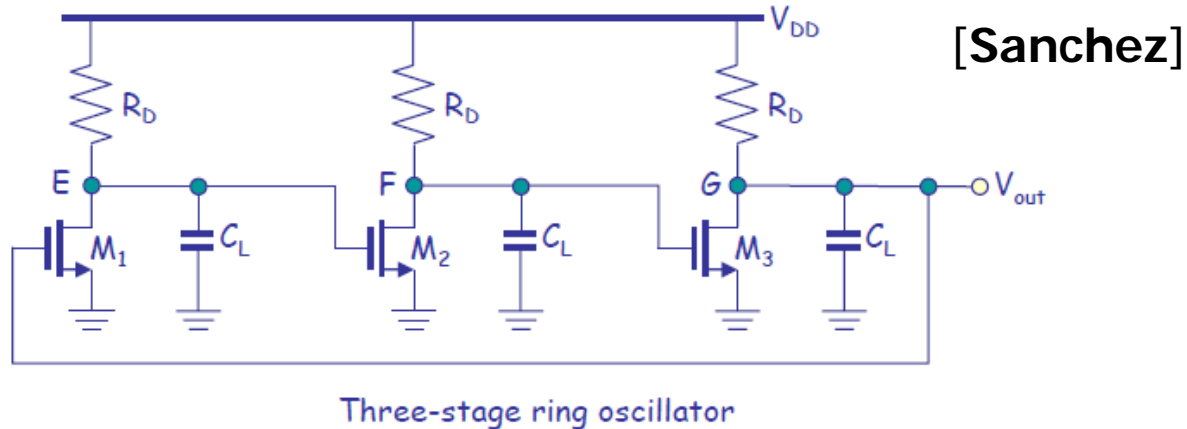

$$H(s) = -\frac{A_0^3}{\left(1 + \frac{s}{\omega_0}\right)^3}$$

$$\omega_{osc} = \sqrt{3}\omega_0$$


$$\tan^{-1} \frac{\omega_{osc}}{\omega_0} = 60^\circ$$

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{-A_0^3}{1 + \frac{A_0^3}{\left(1 + s/\omega_0\right)^3}} = \frac{-A_0^3}{\left(1 + s/\omega_0\right)^3 + A_0^3}$$

$$\frac{A_0^3}{\left[\sqrt{1 + \left(\frac{\omega_{osc}}{\omega_0}\right)^2}\right]^3} = 1$$

$$A_0 = 2$$

# Ring Oscillator Example

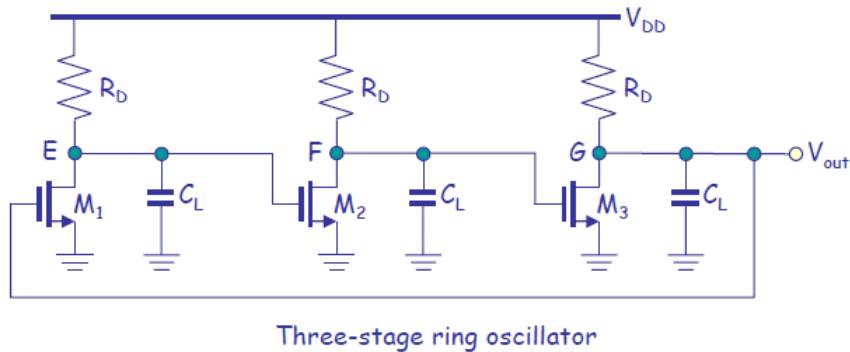

- 4-stage oscillator
  - $A_0 = \sqrt{2}$
  - Phase shift =  $45^\circ$

$$H(s) = -\frac{A_0^3}{\left(1 + \frac{s}{\omega_0}\right)^3}$$

$$\omega_{osc} = \sqrt{3}\omega_0$$

$$\tan^{-1} \frac{\omega_{osc}}{\omega_0} = 60^\circ$$

- Easier to make a larger-stage oscillator oscillate, as it requires less gain and phase shift per stage

$$\frac{V_{out}(s)}{V_{in}(s)} = \frac{-A_0^3}{1 + \frac{A_0^3}{\left(1 + s/\omega_0\right)^3}} = \frac{-A_0^3}{\left(1 + s/\omega_0\right)^3 + A_0^3}$$

$$\frac{A_0^3}{\left[\sqrt{1 + \left(\frac{\omega_{osc}}{\omega_0}\right)^2}\right]^3} = 1$$

$$A_0 = 2$$

[Sanchez]

# Next Time

---

- PLL wrap-up
- CDRs