

ECEN689: Special Topics in High-Speed Links Circuits and Systems Spring 2010

Lecture 29: PLL Wrap-Up



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

Announcements


- Project Preliminary Report #2 due Monday April 26 in class
- Exam 2 is April 30
- Project feedback meetings
 - Wednesday 10:30-12
- Will post paper on Bandpass filtering of forwarded clocks

Agenda


- Clock Dividers
- PLL Design Example
- CDR Introduction

Charge-Pump PLL Circuits

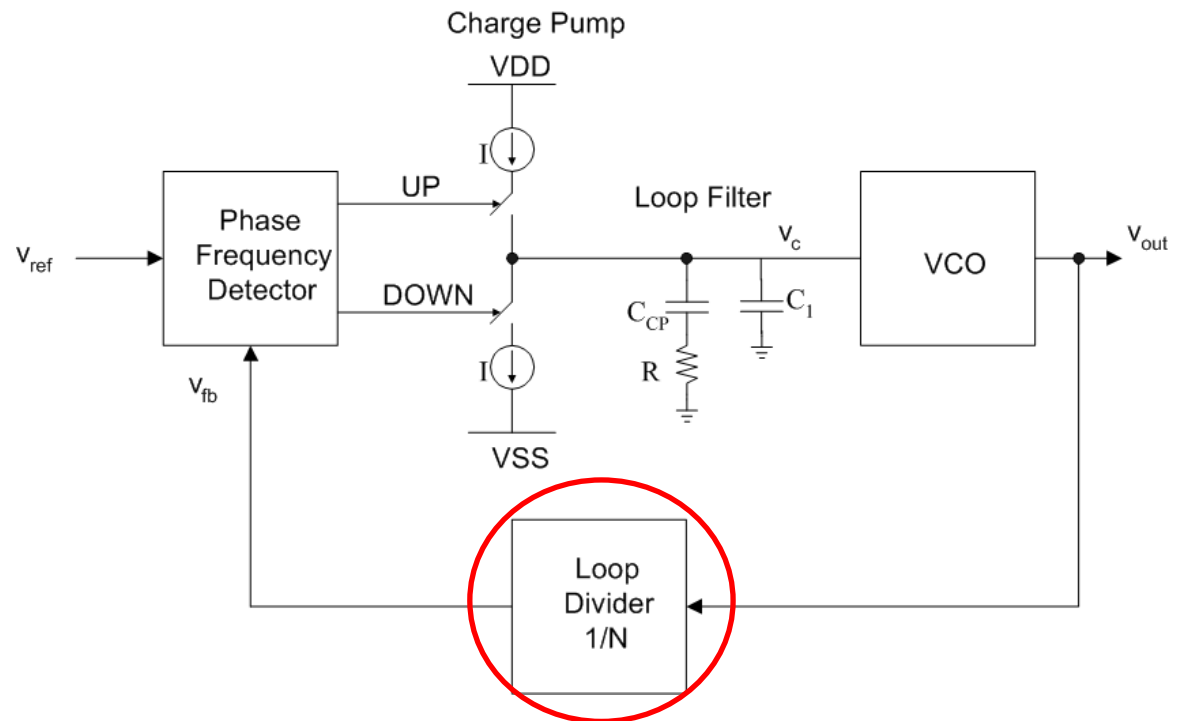- Phase Detector
- Charge-Pump
- Loop Filter
- VCO
- Divider



Loop Divider


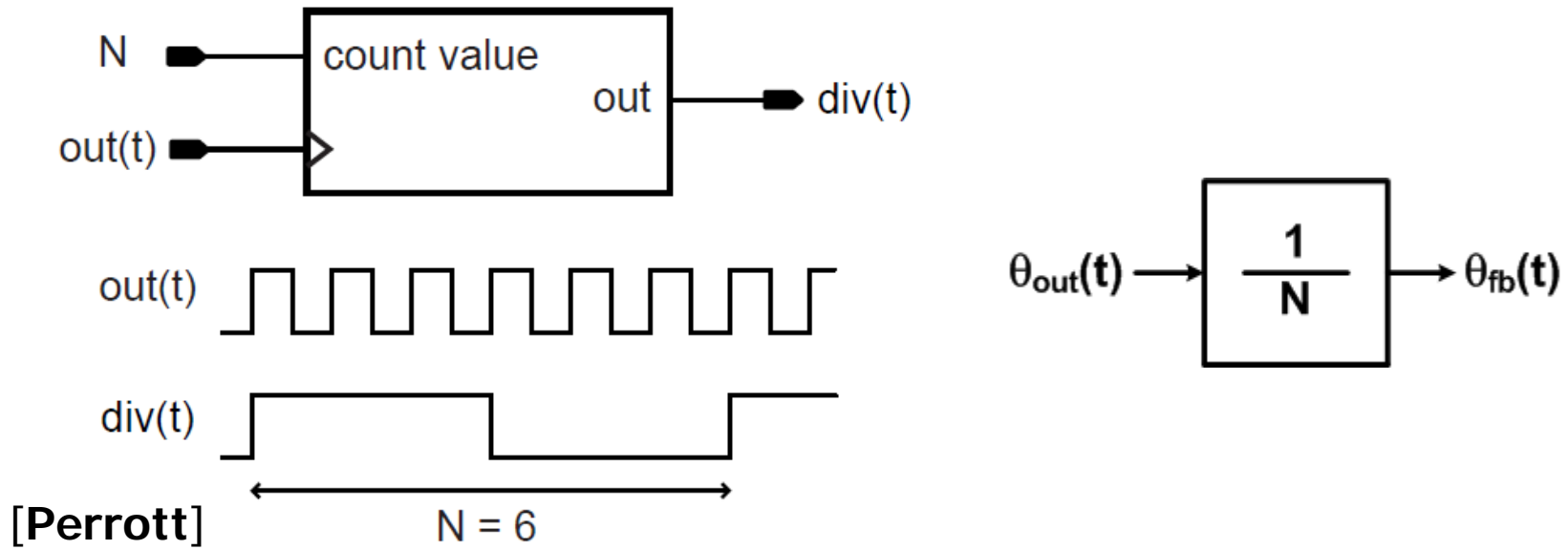


- Time-domain model


$$\omega_{fb}(t) = \frac{1}{N} \omega_{out}(t)$$

$$\theta_{fb}(t) = \int \frac{1}{N} \omega_{out}(t) dt = \frac{1}{N} \theta_{out}(t)$$

Basic Divide-by-2

 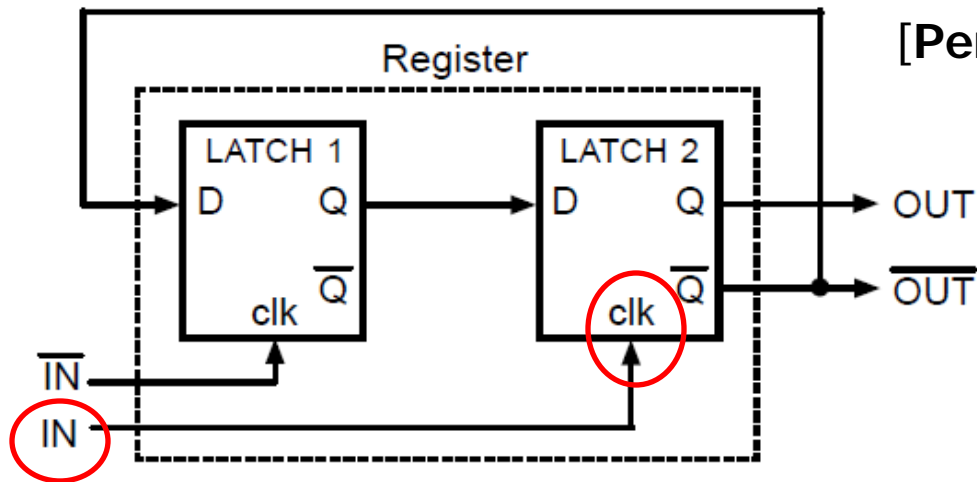

 
- Divide-by-2 can be realized by a flip-flop in “negative feedback”
- Divider should operate correctly up to the maximum output clock frequency of interest **PLUS** some margin



[Fischette]

Divide-by-2 with TSPC FF


True Single Phase Clock Flip-Flop

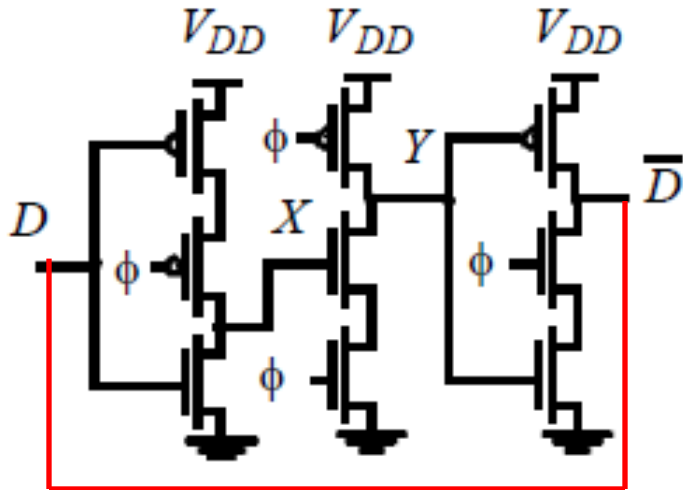


- Advantages
 - Reasonably fast, compact size, and no static power
 - Requires only one phase of the clock
- Disadvantages
 - Signal needs to propagate through three gates per input cycle
 - Need full swing CMOS inputs
 - Dynamic flip-flop may have issues at very low frequency operation (test mode) depending on process leakage

Divider Equivalent Circuit

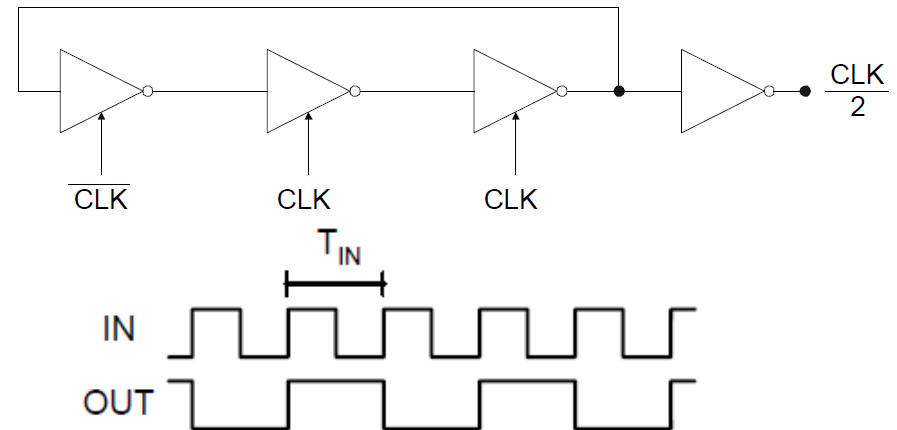Note: output inverter not in left schematic



Divide-by-2 with CML FF

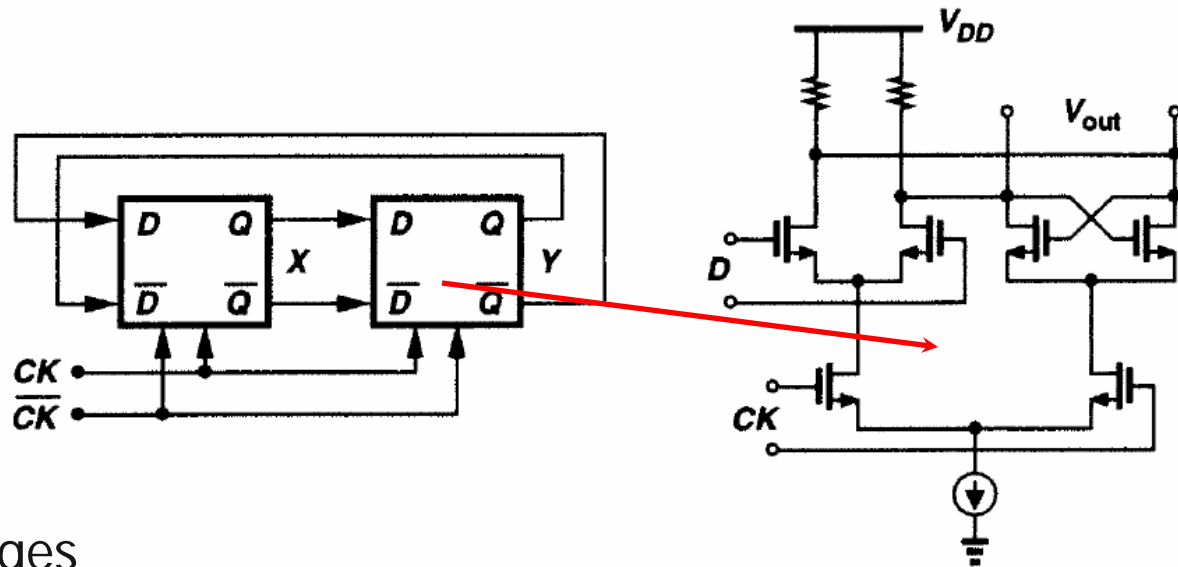


[Razavi]

- Advantages
 - Signal only propagates through two CML gates per input cycle
 - Accepts CML input levels
- Disadvantages
 - Larger size and dissipates static power
 - Requires differential input
 - Need tail current biasing
- Additional speedup (>50%) can be achieved with shunt peaking inductors


Binary Dividers: Asynchronous vs Synchronous

Asynchronous Divider

 

- Advantages
 - Each stage runs at lower frequency, resulting in reduced power
 - Reduced high frequency clock loading
- Disadvantage
 - Jitter accumulation


Synchronous Divider

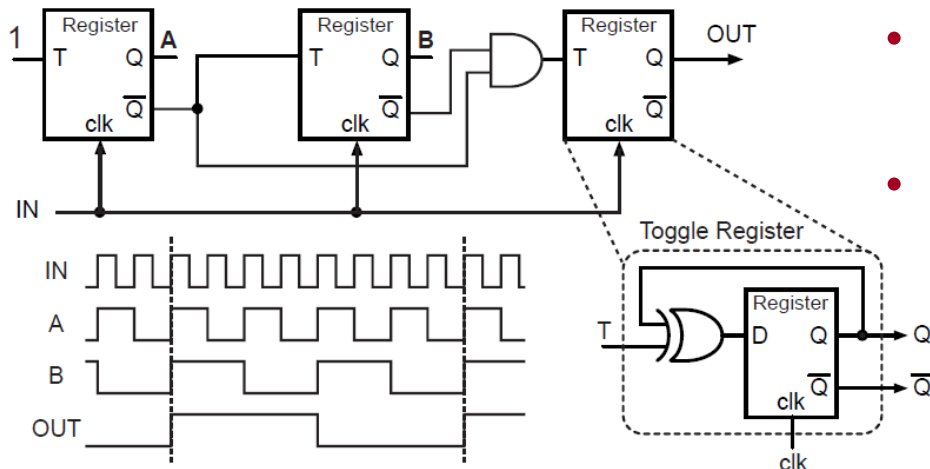

- Advantage
 - Reduced jitter
- Disadvantage
 - All flip-flops work at maximum frequency, resulting in high power
 - Large loading on high frequency clock


Jitter in Asynchronous vs Synchronous Dividers

Asynchronous

 

- Jitter accumulates with the clock-to-Q delays through the divider
- Extra divider delay can also degrade PLL phase margin


Synchronous

 


[Perrott]

- Divider output is “sampled” with high frequency clock
- Jitter on divider clock is similar to VCO output
- Minimal divider delay

Dual Modulus Prescalers

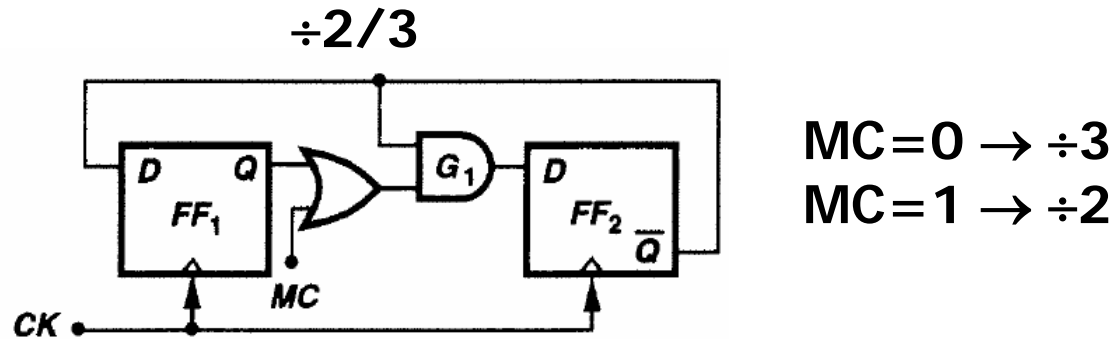

[Razavi]

 


Synchronous $\div 3/4$

Asynchronous $\div 4$


- For /15, first prescaler circuit divides by 3 once and 4 three times during the 15 cycles

Injection-Locked Frequency Dividers

LC-oscillator type (/2)

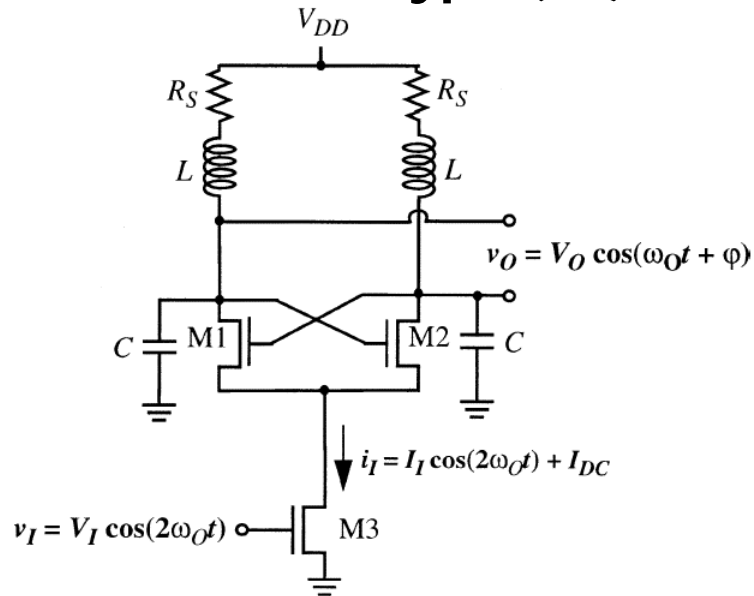

Ring-oscillator type (/3)

 

[Verma JSSC 2003, Rategh JSSC 1999]

[Lo CICC 2009]

- Superharmonic injection-locked oscillators (ILOs) can realize frequency dividers
- Faster and lower power than flip-flop based dividers
- Injection locking range can be limited

Example PLL Design Procedure

- Design procedure for a 100-300MHz frequency synthesizer
- Step 1 – Determine VCO Tuning Range
 - Needs to be at least the output frequency range plus some margin (10-20%) dependent on PVT tolerance

VCO Tuning Range = 100 - 300MHz*

- *Note if you want the frequency extremes (100 or 300MHz) you probably want to add some margin here
- Step 2 – Determine Loop Division Ratio, N
 - This is a function of what reference clocks you have access to, loop bandwidth, dominant noise sources

$$N = 32$$

- Step 3 – Determine Damping Factor
 - Damping factors between 0.5 and 2 are reasonable, with 0.7 or 1 commonly chosen

$$\zeta = \frac{1}{\sqrt{2}} \approx 0.707$$

Example PLL Design Procedure

- Step 4 – Determine natural frequency, ω_n
 - This is a function of the desired loop bandwidth and also the damping factor
 - **Maximum loop bandwidth should be less than 1/10th the input reference clock for the loop to act as a continuous-time system**

$$\text{Lowest Input Reference Frequency} = \frac{100\text{MHz}}{32} = 3.125\text{MHz}$$

- Set the loop bandwidth with some margin - 75% of max value


$$\omega_{3dB} = (0.75)(2\pi)312.5\text{kHz} = 1.47\text{Mrad/s}$$

- For a damping factor of 0.707

$$\omega_n = \frac{\omega_{3dB}}{2.06} = \frac{1.47\text{Mrad/s}}{2.06} = 714\text{krad/s}$$

 Example PLL Design Procedure

- Step 5 – Determine K_{VCO}
 - This is a function of the VCO and charge pump operating voltage range
 - Here I use a combination of discrete tuning caps, resulting in multiple frequency bands over the total frequency range



$$K_{VCO} = \frac{(2\pi)65\text{MHz}}{1.6\text{V}} = 255 \text{ Mrad/sV}$$

- Step 6 – Determine Charge Pump Current & Filter Cap

$$\text{Set } I = 25 \mu\text{A}$$




$$C_1 = \frac{(25 \mu\text{A}) \left(255 \frac{\text{Mrad}}{\text{sV}} \right)}{2\pi(32) \left(714 \frac{\text{krad}}{\text{s}} \right)^2} = 62.2 \text{ pF}$$

- Step 7 – Determine Filter R and Secondary Cap



$$R = \frac{2\zeta}{\omega_n C_1} = \frac{2(0.707)}{\left(714 \frac{\text{krad}}{\text{s}} \right) (62.2 \text{ pF})} = 31.8 \text{ k}\Omega$$

$$C_2 < \frac{C_1}{10} = 6.22 \text{ pF} \Rightarrow C_2 = 6 \text{ pF}$$

PLL Linear Phase Model

  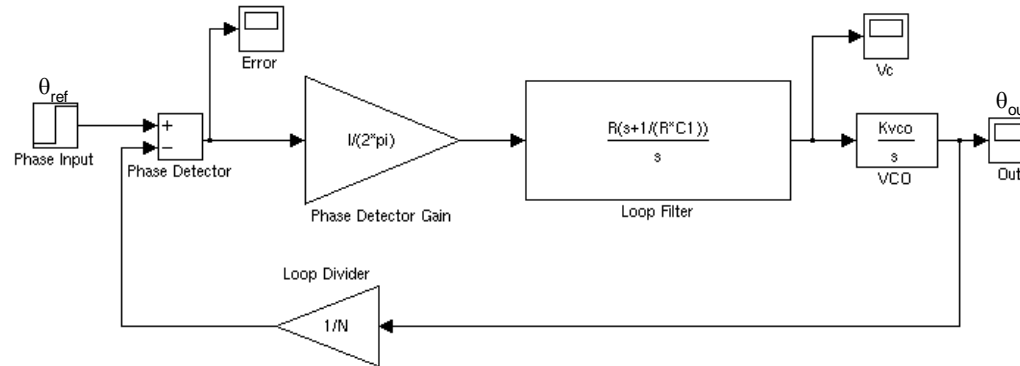

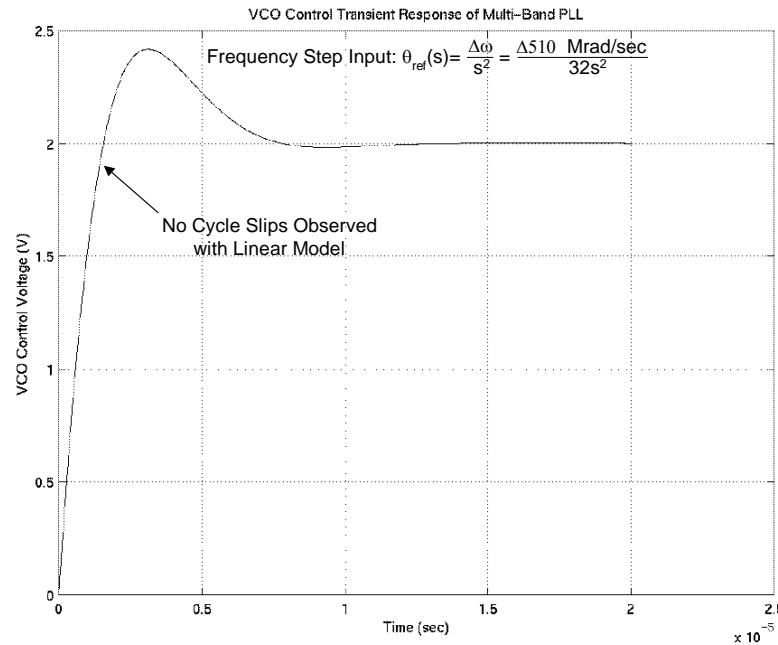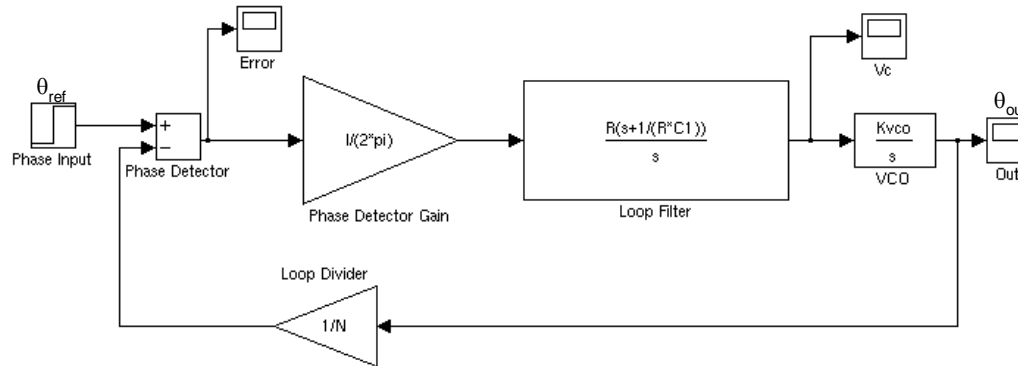PLL Linear Phase Model: Frequency Step Response





PLL Behavioral Model

- From my MSc thesis:
http://www.ece.tamu.edu/~spalermo/docs/msc_thesis_sam_palermo.pdf
- Written in SpectreHDL
- Also look at CppSim: <http://www.cppsim.com/>



```
// Multi-Band Phase Locked Loop Frequency Synthesizer Macromodel
// Main Spectre File
// Samuel Palermo
simulator lang=spectre
include "/home/samuel/research/pll/macromodels/pd/dig_pfd/dig_pfd.def"
include "/home/samuel/research/pll/macromodels/lpf/lpf.def"
ahdl_include "/home/samuel/research/pll/macromodels/vco/vco.def"
ahdl_include "/home/samuel/research/pll/macromodels/vco/switch_vco.def"
ahdl_include
+ "/home/samuel/research/pll/macromodels/divider/divider.def"
include "/home/samuel/research/pll/macromodels/vco/reference.def"
// Power Supply
vdd dd 0 vsource dc=1
// Reference Signal
xref 0 control fref reference
vcontrol control 0 vsource type=pwl wave=[0 0.64 1u 0.64]
// Digital Tri-State Phase/Frequency Comparator
xdig_pfd 0 dd fref fvco up upbar down downbar dig_pfd
// Charge Pump
iup dd 1 isource dc=25u
idown 2 0 isource dc=25u
gup 1 vd up 0 relay vt1=0 vt2=1 ropen=100M rclosed=1m
gupbar 1 0 upbar 0 relay vt1=0 vt2=1 ropen=100M rclosed=1m
gdown vd 2 down 0 relay vt1=0 vt2=1 ropen=100M rclosed=1m
gdownbar dd 2 downbar 0 relay vt1=0 vt2=1 ropen=100M rclosed=1m
// Loop Filter
xfilter 0 vd lpf
gvdgnd vd 0 vd_gnd 0 relay vt1=0 vt2=1 ropen=100M rclosed=10
// Voltage Controlled Oscillator
// xvco vd out vco (gain=40e6 fc=256e6)
xvco 0 vd out nv_temp vd_gnd
+ switch_vco (u=0.8 d=-0.8 gain=40e6 fc=256e6)
// Divider
xdivider 0 out fvco buffer n_temp divider (divisor=32)
op dc
```

```
timedom tran stop=20u step=20p ic=all maxstep=20p skipdc=yes relref=alllocal
simulator lang=spice
.ic vd=0
save vd control fref fvco nv_temp vd_gnd
.OPTIONS rawfmt=psfbin save=selected diagnose=yes vabstol=.01
+ reitot=.99
*****
// Digital Phase Frequency Detector Macromodel
// Samuel Palermo
subckt dig_pfd (gnd dd fref fvco up upbar down downbar)
ahdl_include "/home/samuel/research/pll/macromodels/pd/dig_pfd/dff.def"
ahdl_include
+ "/home/samuel/research/pll/macromodels/pd/dig_pfd/nand.def"
xdffup gnd dd fref up upbar r dff
xdffdown gnd dd fvco down downbar r dff
xnand gnd up down r nand
ends dig_pfd
*****
// D Flip Flop Macromodel
// Samuel Palermo
module dff(gnd, D, CLK, Q, QBAR, R) ()
node [V, I] gnd, D, CLK, Q, QBAR, R ;
{
  real Q_temp;
  real QBAR_temp;
  initial {
    Q_temp=0;
    QBAR_temp=1;
  }
  analog {
    if ($threshold (V(CLK, gnd)-1, 1)) {
      if (V(D,gnd)==1) {
        Q_temp=1;
        QBAR_temp=0;
      }
      else {
        Q_temp=0;
        QBAR_temp=1;
      }
    }
    if (V(R, gnd)==0) {
      Q_temp=0;
      QBAR_temp=1;
    }
  }
}
```

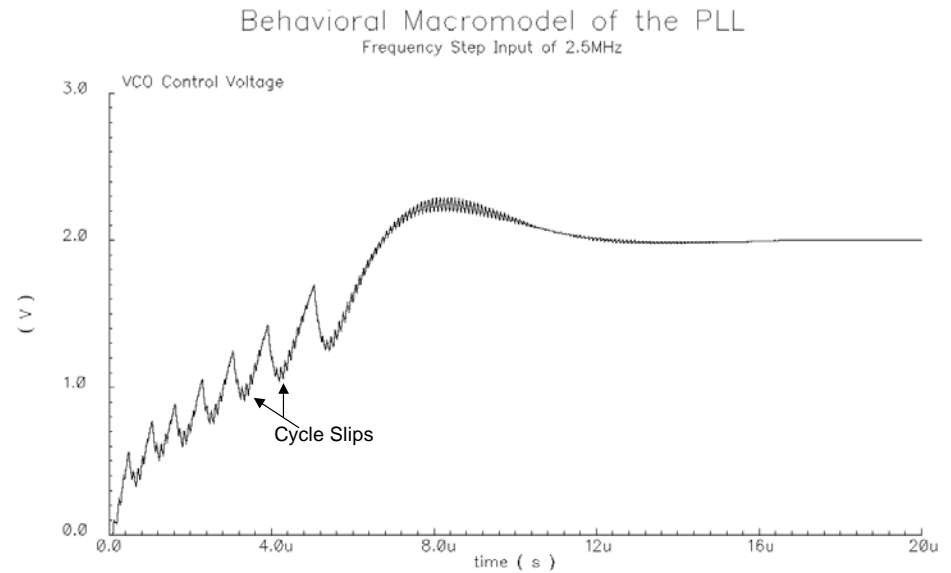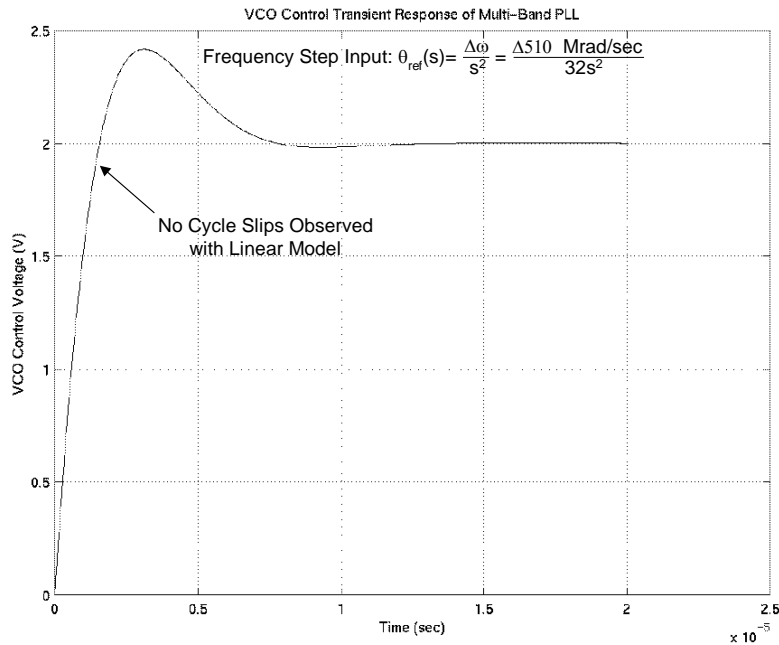
PLL Frequency Step Response: Linear vs Behavioral Model



PLL Lab Results

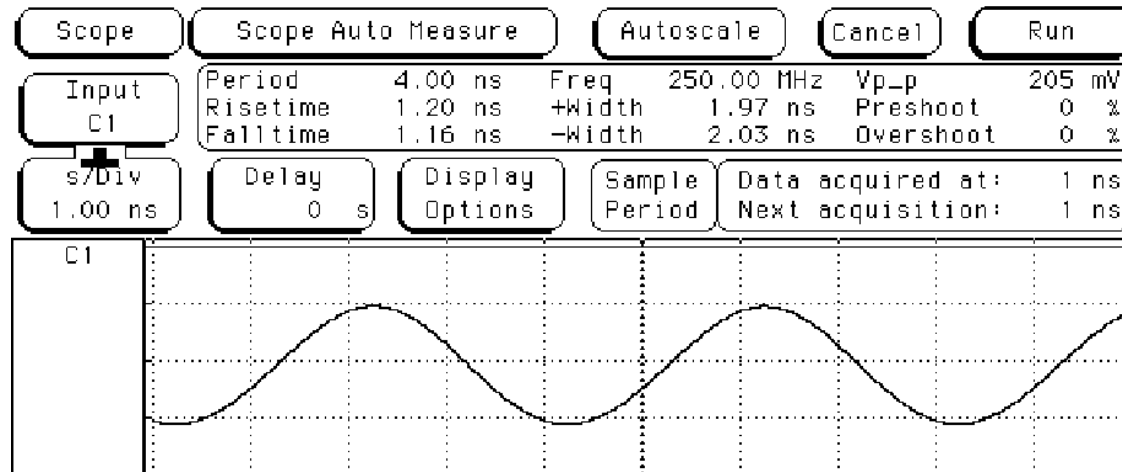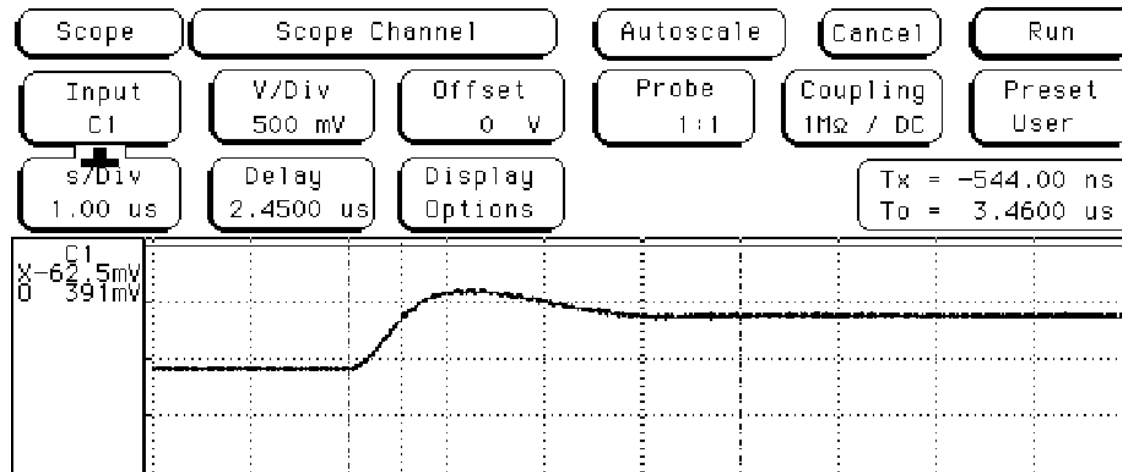


Embedded Clock I/O Circuits

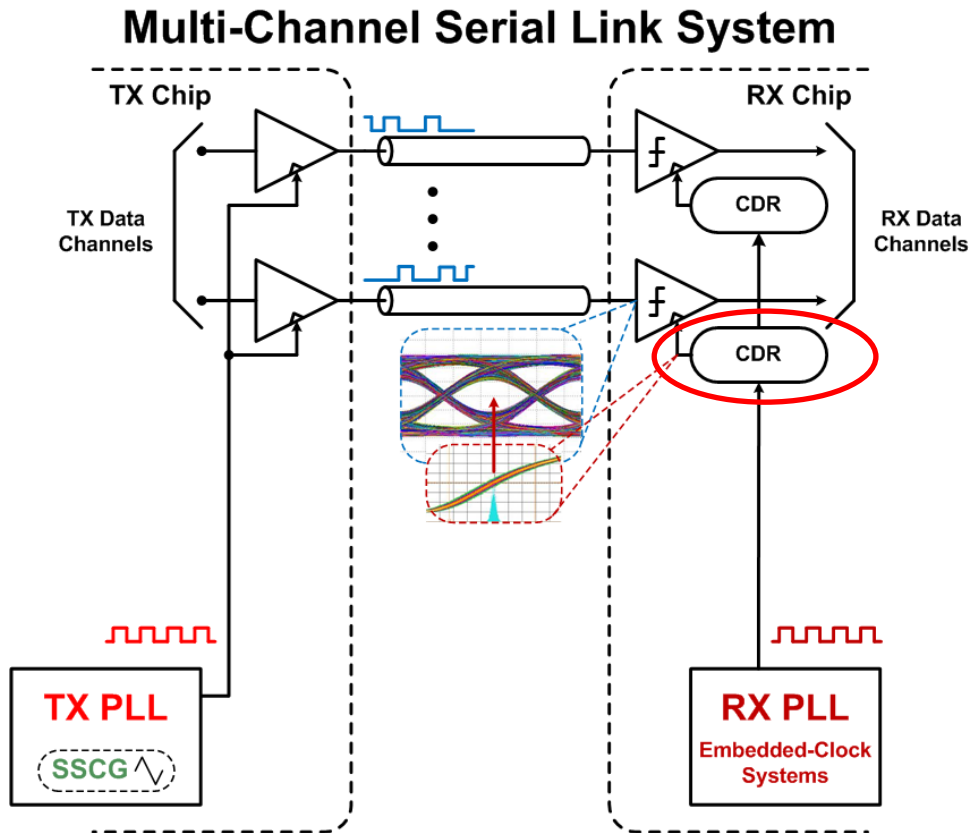


- TX PLL
- TX Clock Distribution
- **CDR**
 - Per-channel PLL-based
 - Dual-loop w/ Global PLL &
 - Local DLL/PI
 - Local Phase-Rotator PLLs
 - Global PLL requires RX clock distribution to individual channels

Embedded Clocking (CDR)

PLL-based CDR

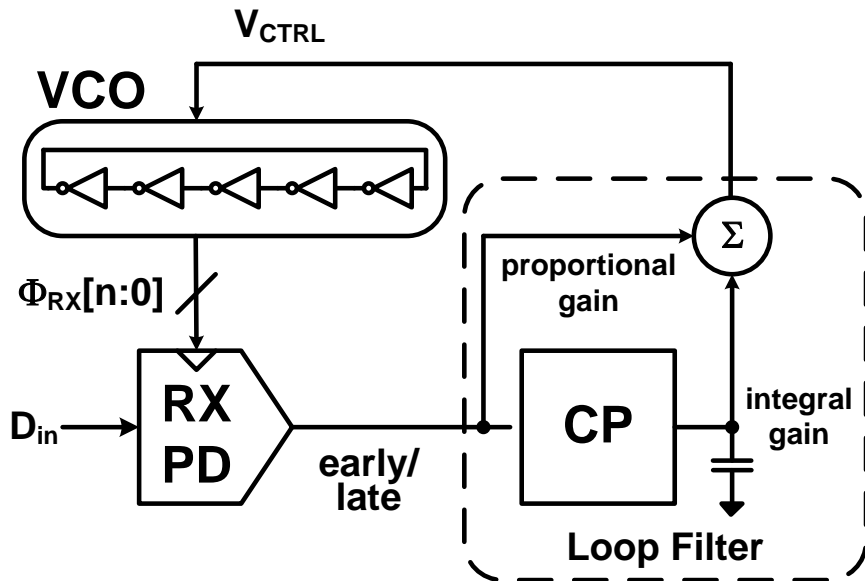

Dual-Loop CDR

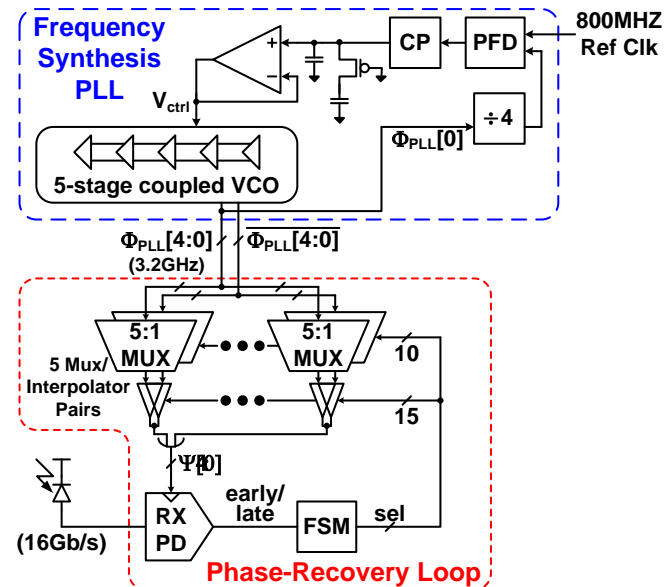

- Clock frequency and optimum phase position are extracted from incoming data
- Phase detection continuously running
- Jitter tracking limited by CDR bandwidth
 - With technology scaling we can make CDRs with higher bandwidths and the jitter tracking advantages of source synchronous systems is diminished
- Possible CDR implementations
 - Stand-alone PLL
 - "Dual-loop" architecture with a PLL or DLL and phase interpolators (PI)
 - Phase-rotator PLL

Next Time

- CDRs