

# ECEN689: Special Topics in High-Speed Links Circuits and Systems Spring 2010

---

## Lecture 30: CDRs



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

# Announcements

---


- Project Preliminary Report #2 due Monday April 26 in class
- Exam 2 is April 30
- Posted Fwd Clock Bandpass Filtering Paper
- Will Post
  - CDR Papers
  - Example PLL models

# Agenda

---

- CDR overview
- CDR Phase Detectors
- Analog & Digital CDRs


# Embedded Clock I/O Circuits

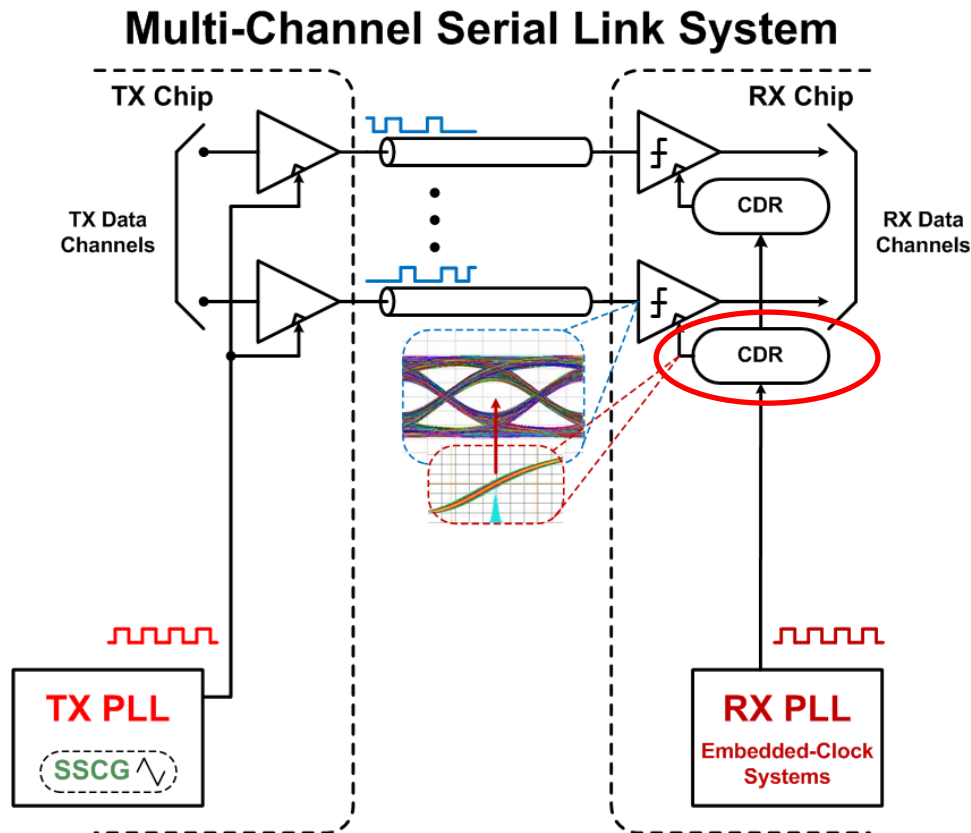


- TX PLL
- TX Clock Distribution
- CDR
  - Per-channel PLL-based
  - Dual-loop w/ Global PLL &
    - Local DLL/PI
    - Local Phase-Rotator PLLs
    - Global PLL requires RX clock distribution to individual channels

# Embedded Clocking (CDR)

## PLL-based CDR

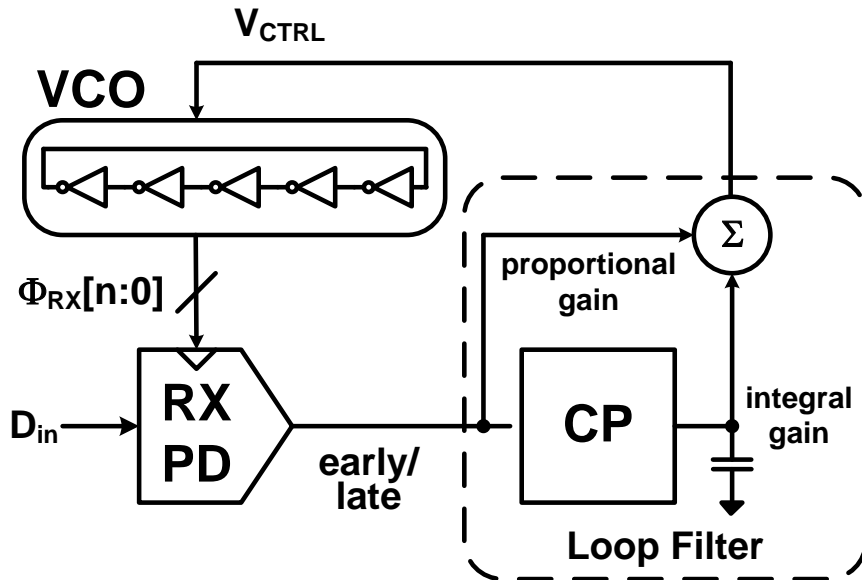

## Dual-Loop CDR

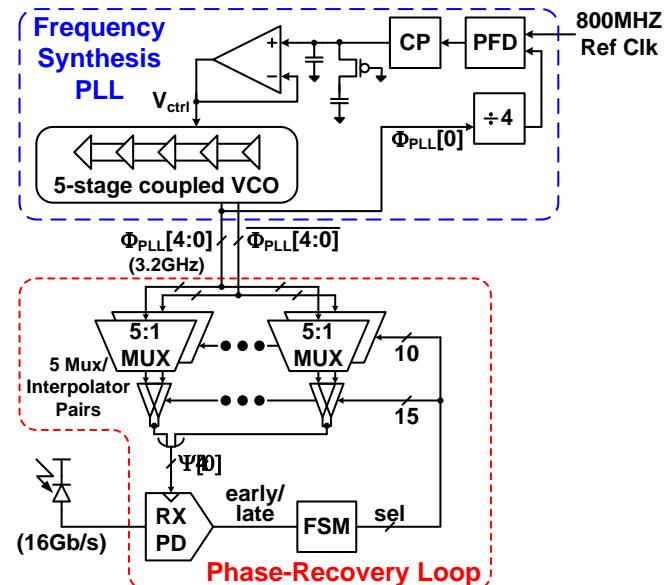



- Clock frequency and optimum phase position are extracted from incoming data
- Phase detection continuously running
- Jitter tracking limited by CDR bandwidth
  - With technology scaling we can make CDRs with higher bandwidths and the jitter tracking advantages of source synchronous systems is diminished
- Possible CDR implementations
  - Stand-alone PLL
  - "Dual-loop" architecture with a PLL or DLL and phase interpolators (PI)
  - Phase-rotator PLL

# CDR Phase Detectors


---

- CDR phase detectors compare the phase between the input data and the recovered clock sampling this data and provides information to adjust the sampling clocks' phase
- Phase detectors can be linear or non-linear
- Linear phase detectors provide both **sign and magnitude** information regarding the sampling phase error
  - Hogge
- Non-linear phase detectors provide **only sign** information regarding the sampling phase error
  - Alexander or 2x-Oversampled or Bang-Bang
  - Oversampling ( $>2$ )
  - Baud-Rate

# Hogge Phase Detector

 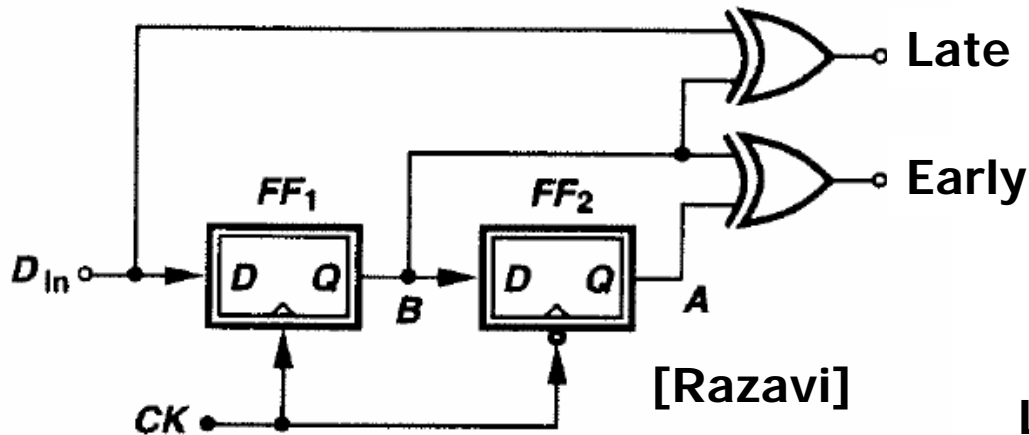


(Late – Early)  
Output Pulse Width

 


$$K_{PD} = \frac{1}{\pi} (TD)$$

- Linear phase detector
- For phase transfer 0rad is w.r.t optimal  $T_b/2$  spacing between sampling clock and data
  - $\phi_e = \phi_{in} - \phi_{clk}$
- TD is the transition density – no transitions, no information
  - A value of 0.5 can be assumed for random data

# Hogge Phase Detector Nonidealities

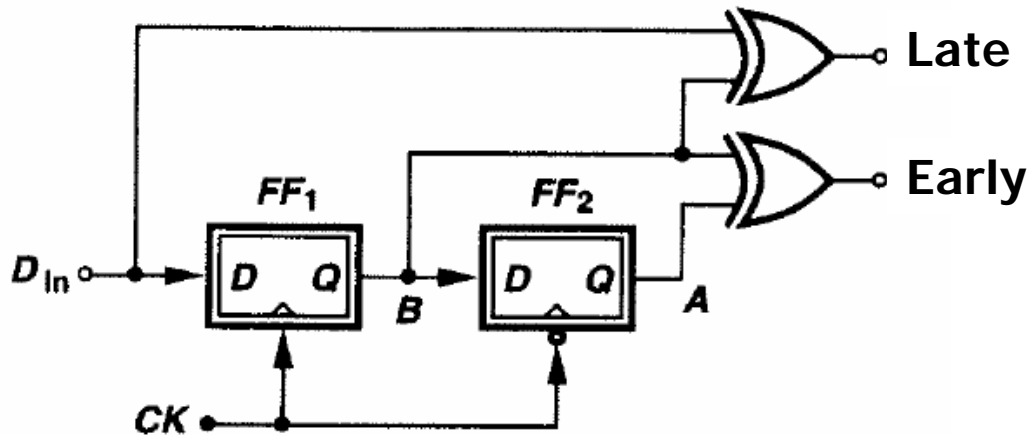


[Razavi]

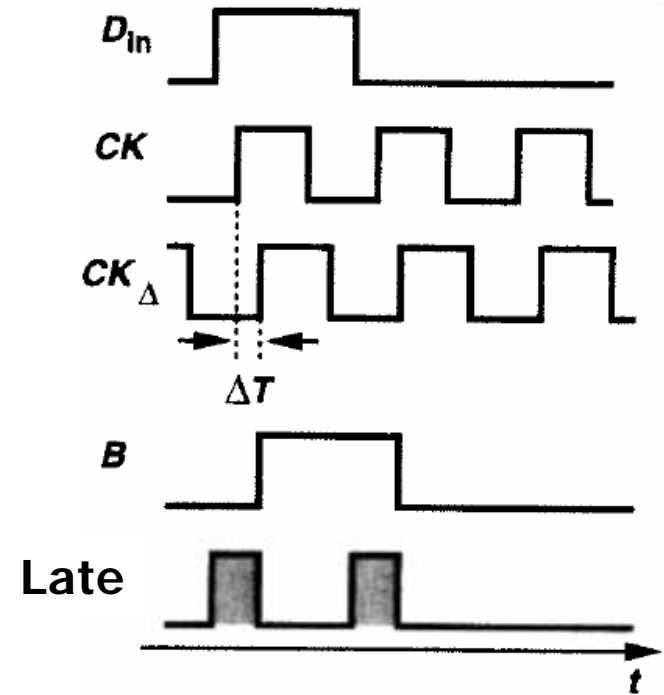

- **Flip-Flop Clk-to-Q delay** widens Late pulse, but doesn't impact Early pulse
- CDR will **lock with a phase shift** to equalize to Early and Late pulse widths



# Hogge Phase Detector Nonidealities

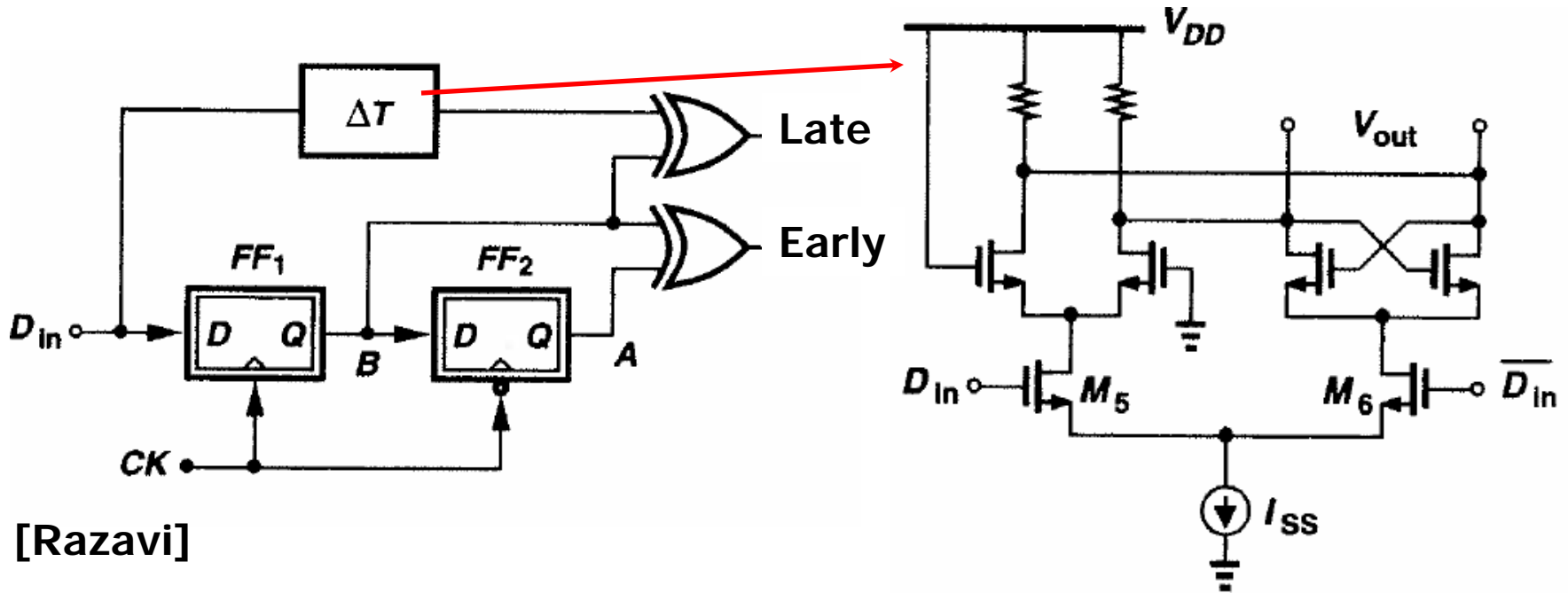

[Razavi]

- CDR phase shift compensated with a dummy delay element
- Other issues:
  - Need extremely high-speed XOR gates
  - Phase skew between Early and Late signals induces a “triwave” disturbance (ripple) on the control voltage

# Alexander (2x-Oversampled) Phase Detector

- Most commonly used CDR phase detector
- Non-linear (Binary) "Bang-Bang" PD
  - Only provides sign information of phase error (not magnitude)
- Phase detector uses 2 data samples and one "edge" sample
- Data transition necessary




$$D_n \oplus D_{n+1}$$

- If "edge" sample is same as second bit (or different from first), then the clock is sampling "late"

$$E_n \oplus D_n$$


- If "edge" sample is same as first bit (or different from second), then the clock is sampling "early"

$$E_n \oplus D_{n+1}$$

   

[Sheikholeslami]
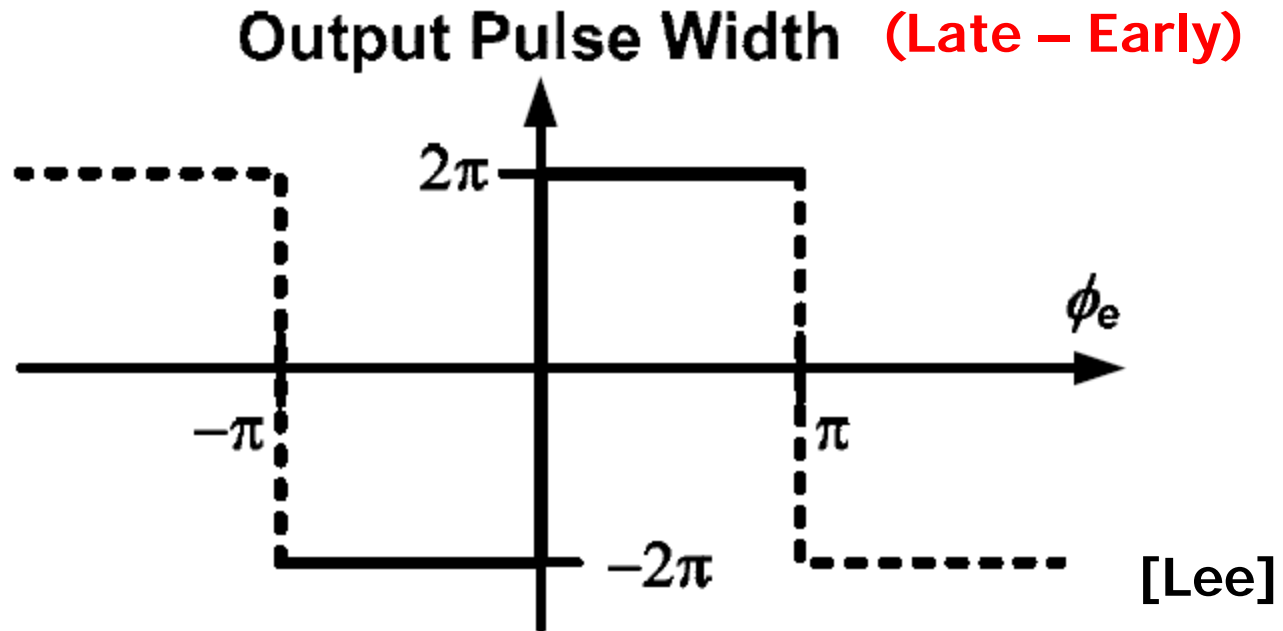
# Alexander Phase Detector Characteristic (No Noise)




- Phase detector only outputs phase error sign information in the form of a late OR early pulse whose width doesn't vary
- Phase detector gain is ideally infinite at zero phase error
  - Finite gain will be present with noise, clock jitter, sampler metastability, ISI

# Alexander Phase Detector Characteristic (With Noise)


- Total transfer characteristic is the convolution of the ideal PD transfer characteristic and the noise PDF
- Noise linearizes the phase detector over a phase region corresponding to the peak-to-peak jitter

$$K_{PD} \approx \frac{2}{J_{PP}}(TD)$$

 - TD is the transition density – no transitions, no information
  - A value of 0.5 can be assumed for random data




# Oversampling Phase Detectors

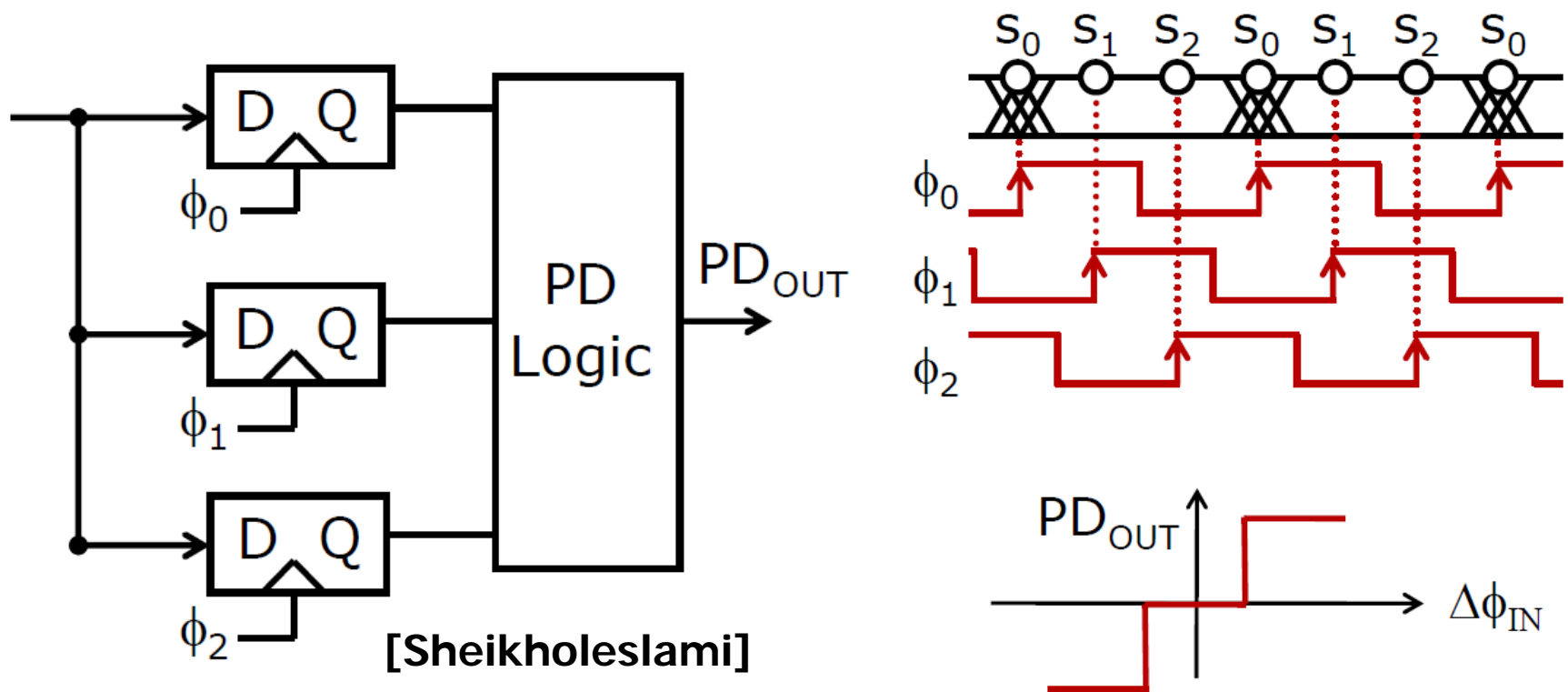

- Multiple clock phases are used to sample incoming data bits
- PD can have multiple output levels
  - Can detect rate of phase change for frequency acquisition
 
# Mueller-Muller Baud-Rate Phase Detector

- Baud-rate phase detector only requires one sample clock per symbol (bit)
- Mueller-Muller phase detector commonly used
- Attempting to equalize the amplitude of samples taken before and after a pulse






*Locked Condition:  $h(\tau_k - T_b) = h(\tau_k + T_b)$*

*Early Clock:  $h(\tau_k - T_b) < h(\tau_k + T_b)$*

*Late Clock:  $h(\tau_k - T_b) > h(\tau_k + T_b)$*
 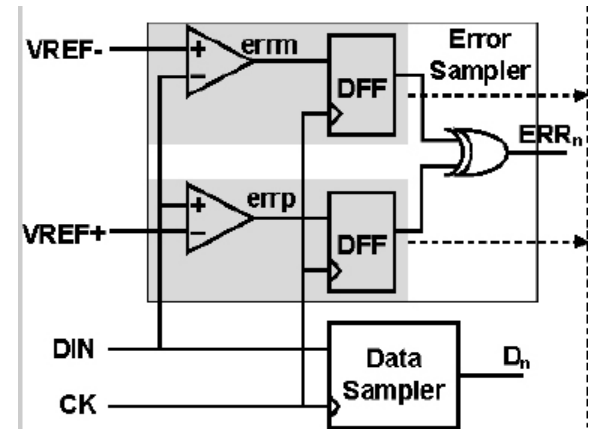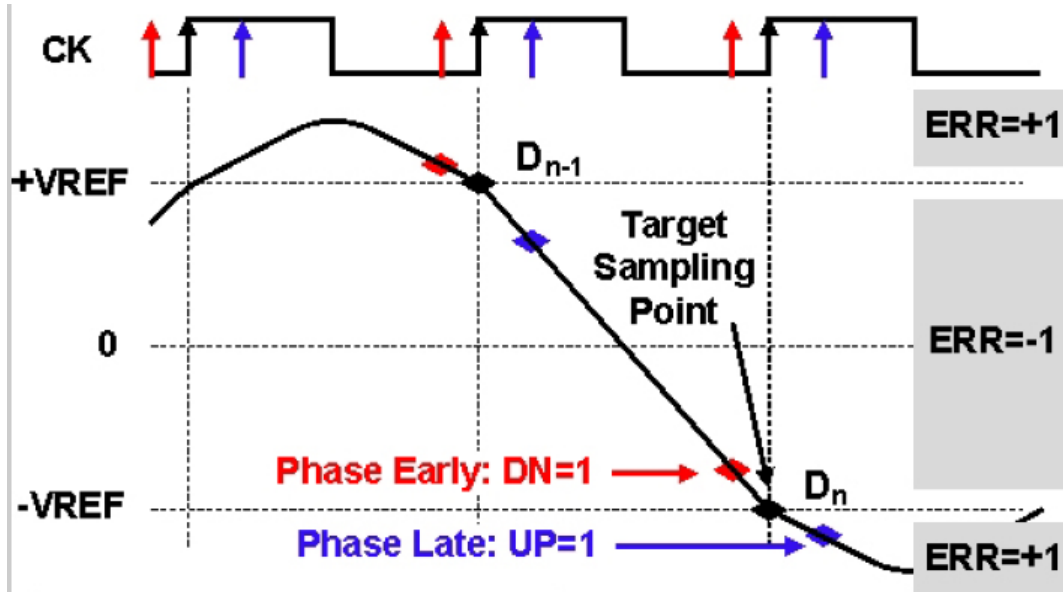
# Mueller-Muller Baud-Rate Phase Detector



**Phase Error:**  
 $\Delta T_n = D_n \times D_{n-1} \times (ERR_n - ERR_{n-1})$


Phase detector output truth table

$\Delta T_n$	UP	DN
+1	1	0
0	0	0
-1	0	1

$d_j$	$d_{j-1}$	$e_j$	$e_{j-1}$	$\phi_{errj}$
1	-1	1	-1	LATE
-1	1	1	-1	LATE
1	-1	-1	1	EARLY
-1	1	-1	1	EARLY
All other cases				HOLD

[Spagna ISSCC 2010]

# Analog PLL-based CDR

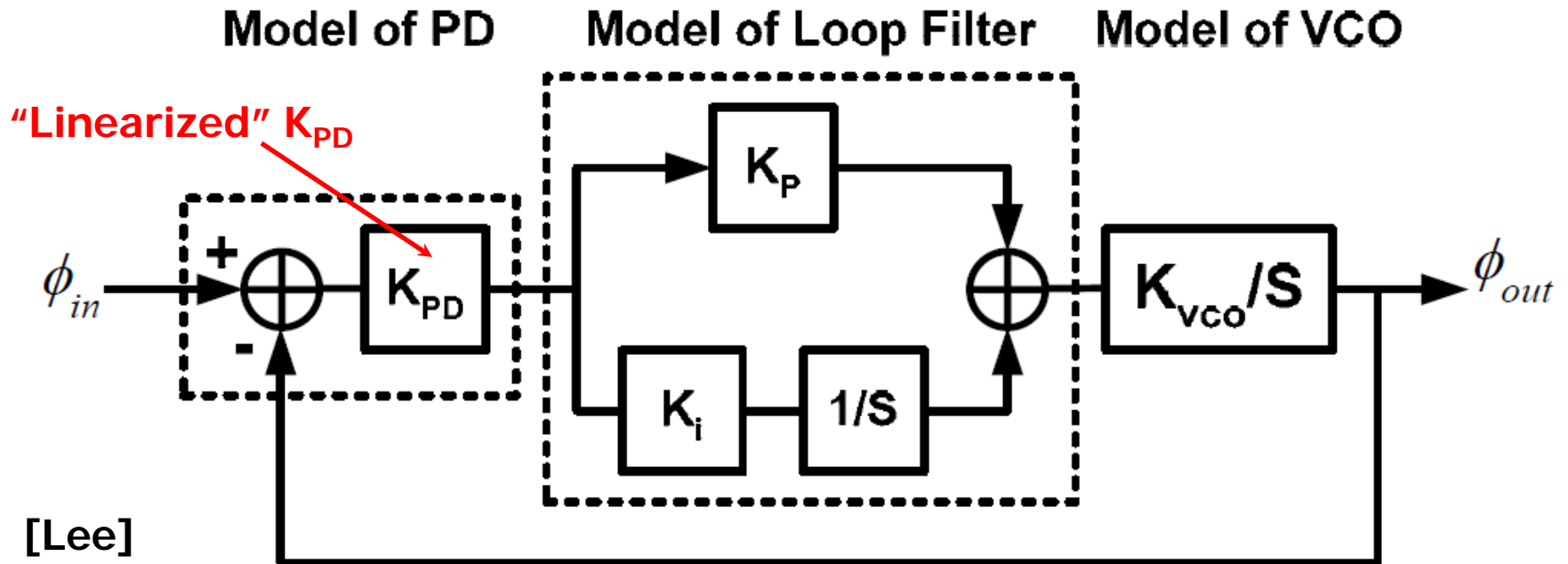


$$\frac{\phi_{out}}{\phi_{in}} = \frac{s \cdot K_P \cdot K_{PD} \cdot K_{VCO} + K_i \cdot K_{PD} \cdot K_{VCO}}{s^2 + s \cdot K_P \cdot K_{PD} \cdot K_{VCO} + K_i \cdot K_{PD} \cdot K_{VCO}}$$

$$K_P = I_C \cdot R \quad K_i = \frac{I_C}{C} \quad \omega_n = \sqrt{K_i \cdot K_{PD} \cdot K_{VCO}} \quad \zeta = \frac{K_P}{K_i} \cdot \frac{\omega_n}{2}$$





# Analog PLL-based CDR

 

[Lee]


- CDR “bandwidth” will vary with input phase variation amplitude with a non-linear phase detector
- Final performance verification should be done with a time-domain non-linear model

# Digital PLL-based CDR

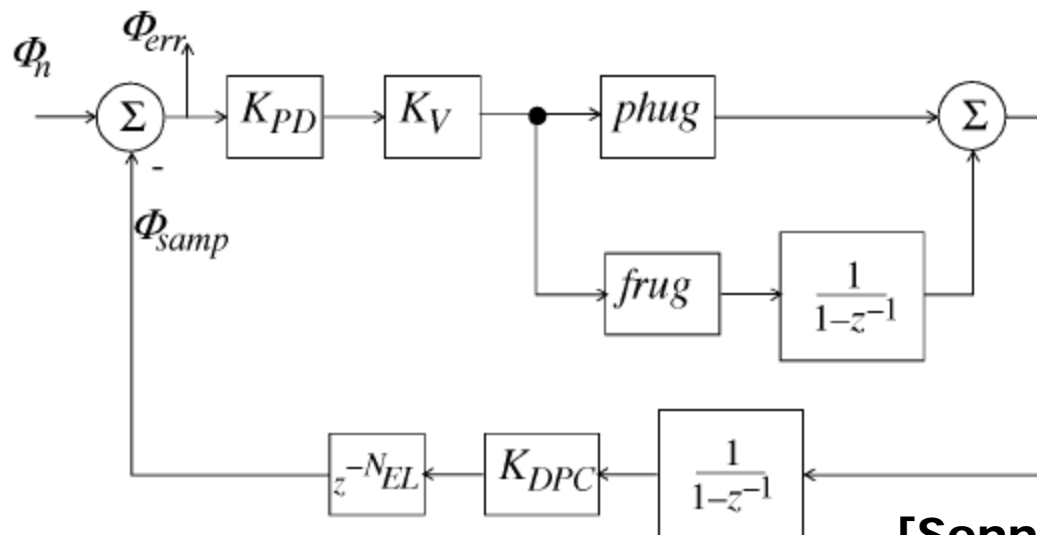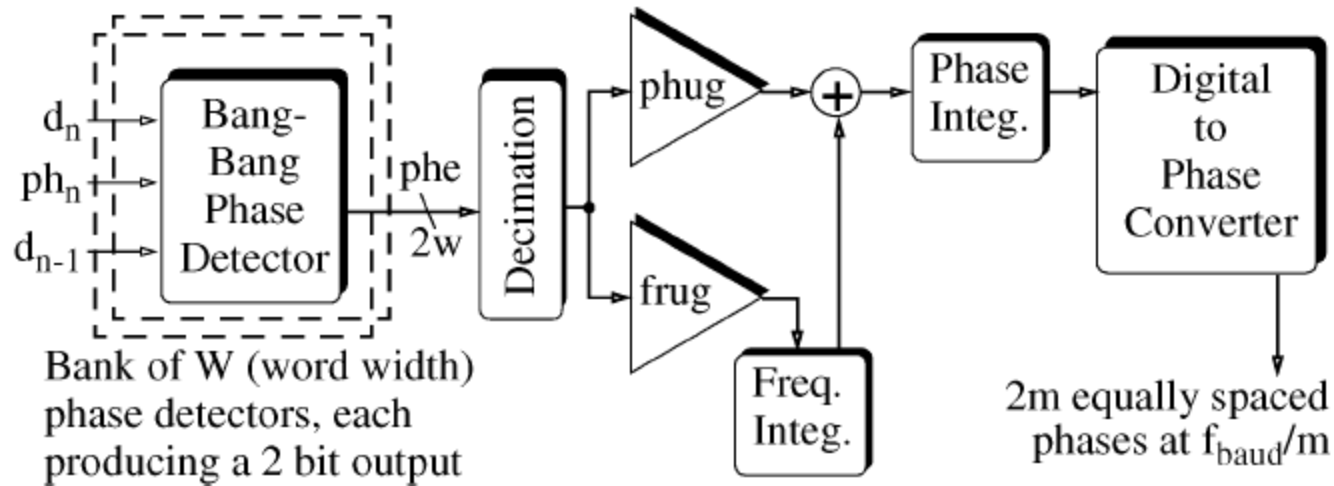

[Sonntag JSSC 2006]

# Digital PLL-based CDR

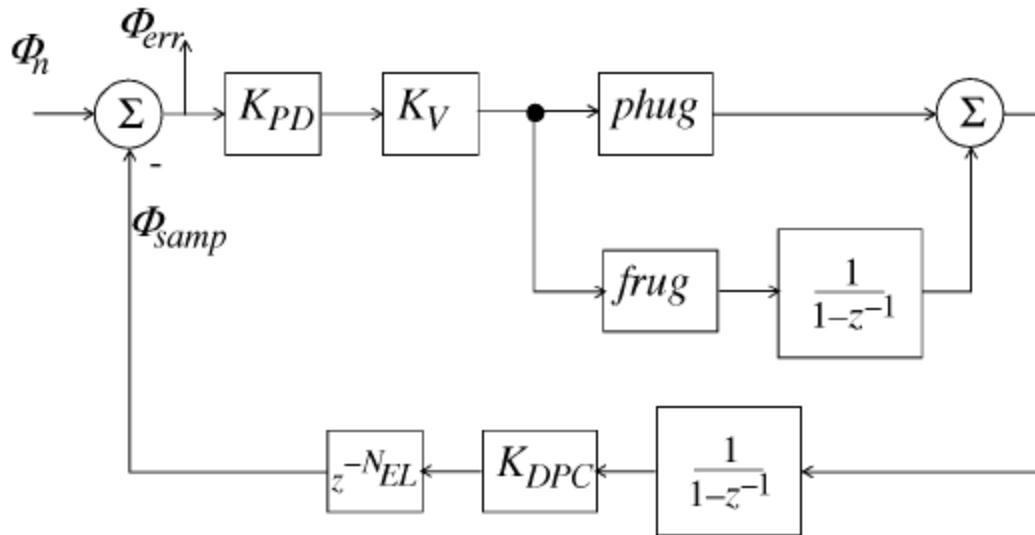


Open-Loop Gain:

$$L(z^{-1}) = \left( \frac{K_{PD}K_VK_{DPC}}{1 - z^{-1}} \right) \left( phug + \frac{frug}{(1 - z^{-1})} \right) z^{-N_{EL}}.$$

$$\Phi_{samp}/\Phi_{in} = (L(e^{-j\omega})) / (1 + L(e^{-j\omega}))$$

[Sonntag JSSC 2006]

# Digital PLL-based CDR

 

[Sonntag JSSC 2006]

# Next Time

---

- CDR circuits