

ECEN689: Special Topics in High-Speed Links Circuits and Systems Spring 2010

Lecture 31: CDR Architectures



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University


Announcements

- Project Preliminary Report #2 due now
 - Feedback meetings on Friday 10:30-12
- Exam 2 is April 30
- Final Project Report Due May 4

Agenda



- Analog & digital CDRs
- Analog dual-loop CDRs
- Digital dual-loop CDRs
- Phase Interpolators
- Delay-Locked Loops

Embedded Clock I/O Circuits

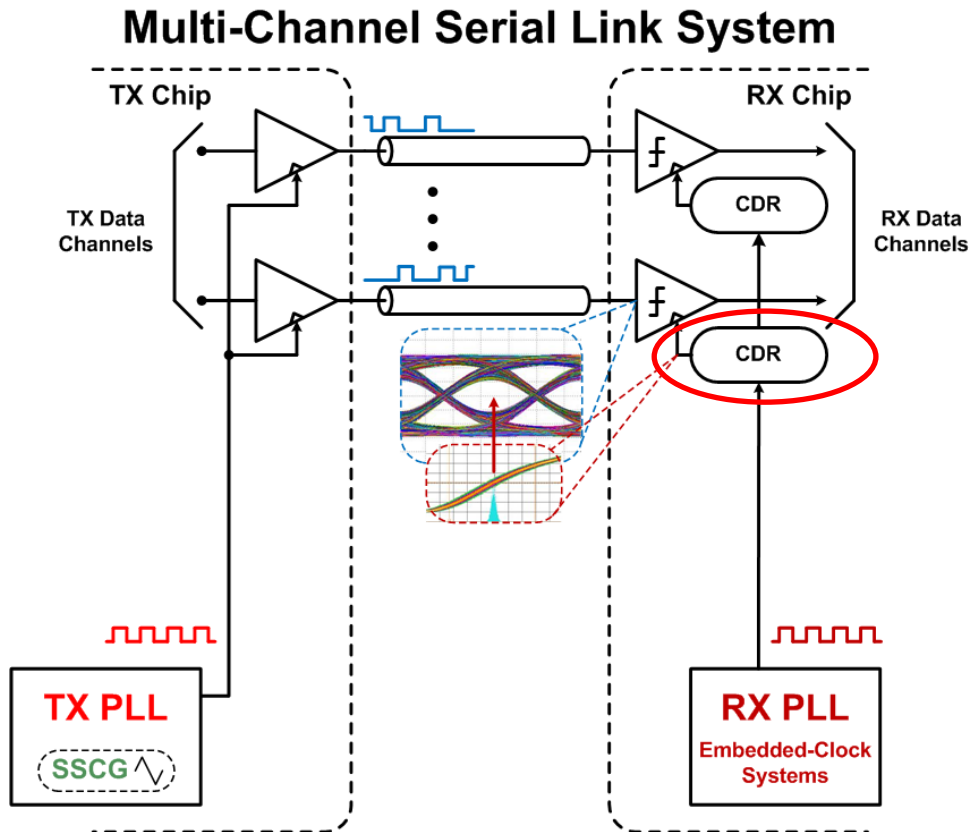


- TX PLL
- TX Clock Distribution
- CDR
 - Per-channel PLL-based
 - Dual-loop w/ Global PLL &
 - Local DLL/PI
 - Local Phase-Rotator PLLs
 - Global PLL requires RX clock distribution to individual channels

Embedded Clocking (CDR)

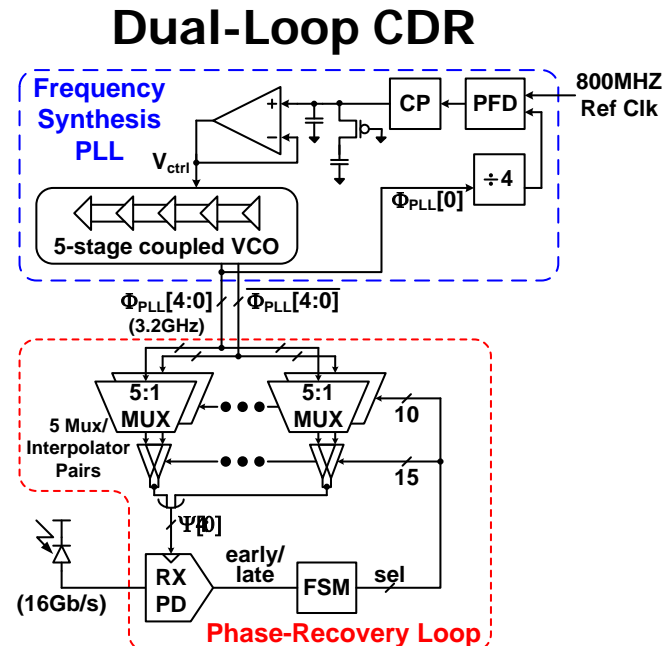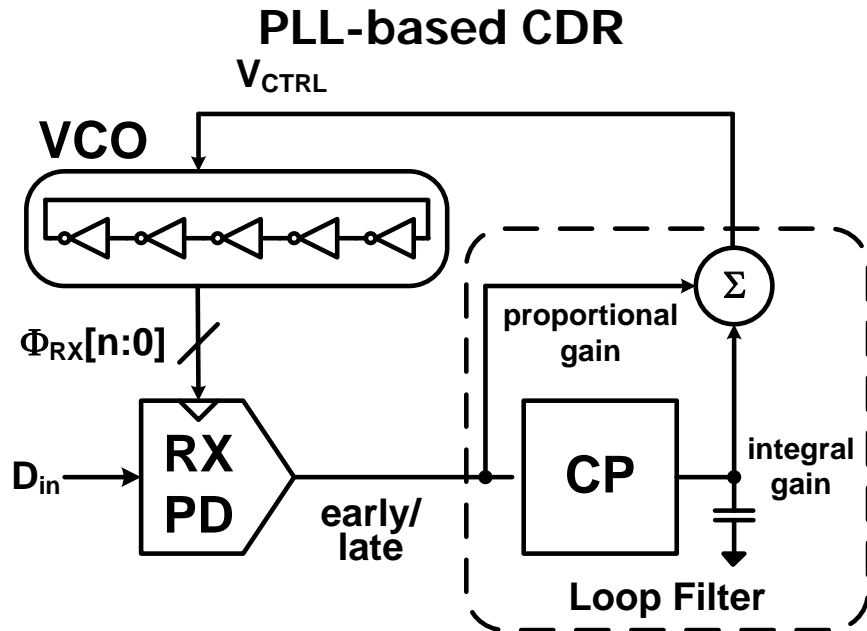

- Clock frequency and optimum phase position are extracted from incoming data
- Phase detection continuously running
- Jitter tracking limited by CDR bandwidth
 - With technology scaling we can make CDRs with higher bandwidths and the jitter tracking advantages of source synchronous systems is diminished
- Possible CDR implementations
 - Stand-alone PLL
 - "Dual-loop" architecture with a PLL or DLL and phase interpolators (PI)
 - Phase-rotator PLL


Analog PLL-based CDR

 

$$\frac{\phi_{out}}{\phi_{in}} = \frac{s \cdot K_P \cdot K_{PD} \cdot K_{VCO} + K_i \cdot K_{PD} \cdot K_{VCO}}{s^2 + s \cdot K_P \cdot K_{PD} \cdot K_{VCO} + K_i \cdot K_{PD} \cdot K_{VCO}}$$

$$K_P = I_C \cdot R \quad K_i = \frac{I_C}{C} \quad \omega_n = \sqrt{K_i \cdot K_{PD} \cdot K_{VCO}} \quad \zeta = \frac{K_P}{K_i} \cdot \frac{\omega_n}{2}$$



Analog PLL-based CDR

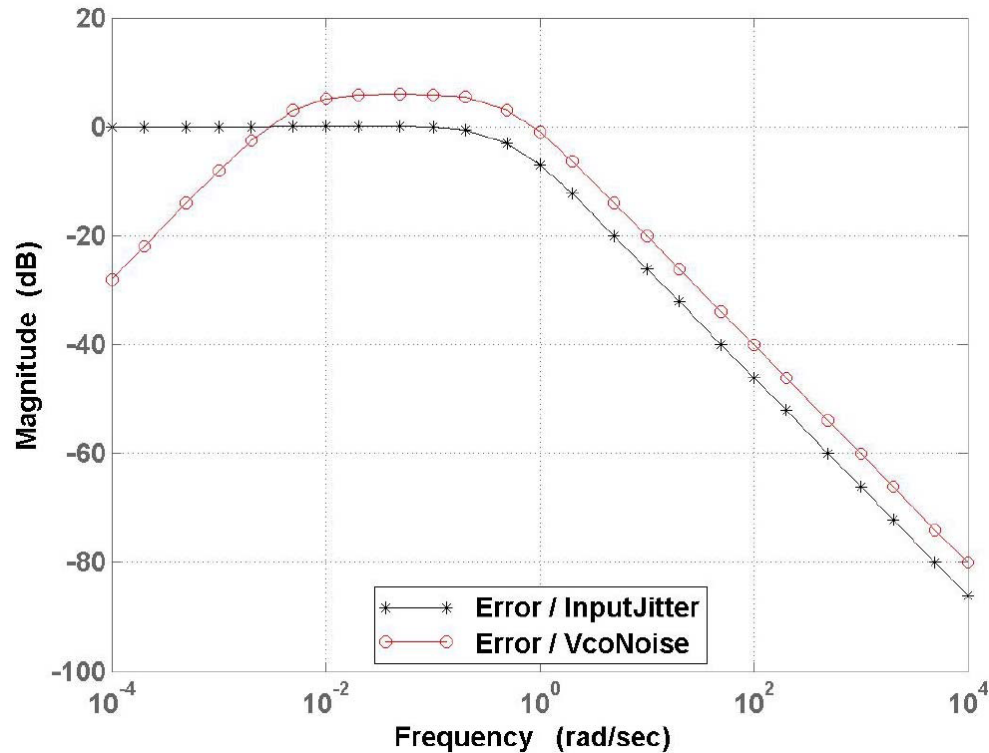

[Lee]


- CDR “bandwidth” will vary with input phase variation amplitude with a non-linear phase detector
- Final performance verification should be done with a time-domain non-linear model

Digital PLL-based CDR

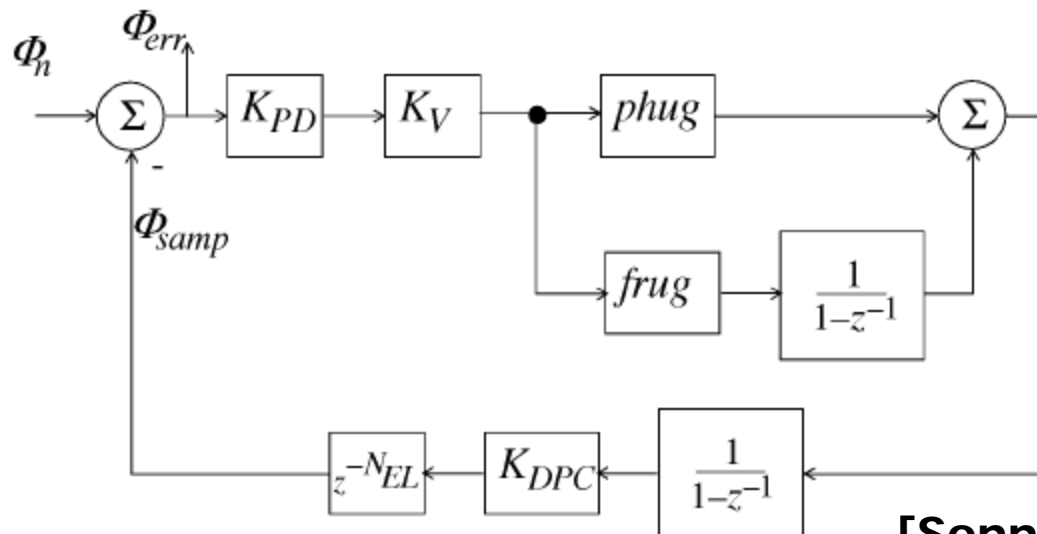 

[Sonntag JSSC 2006]

Digital PLL-based CDR

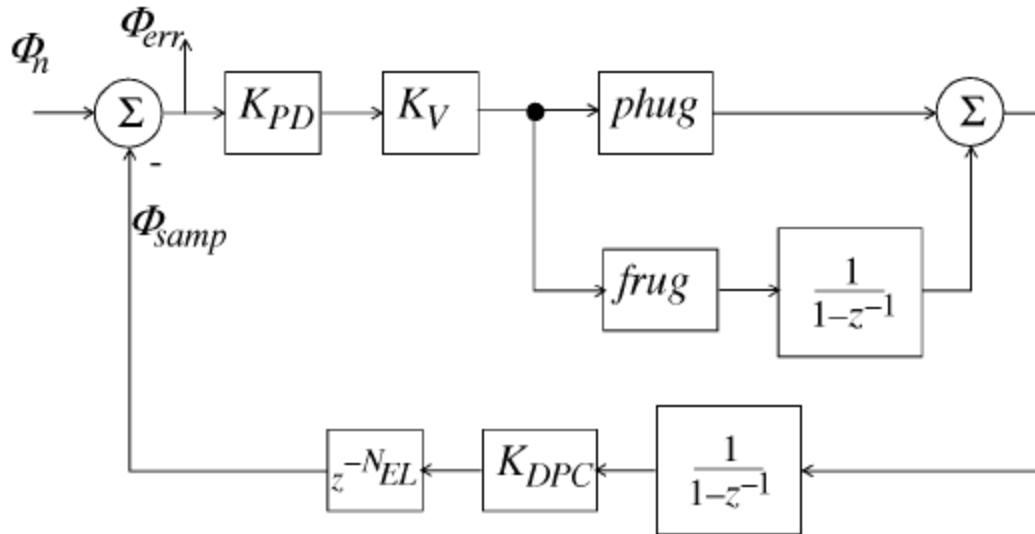


Open-Loop Gain:

$$L(z^{-1}) = \left(\frac{K_{PD}K_VK_{DPC}}{1 - z^{-1}} \right) \left(phug + \frac{frug}{(1 - z^{-1})} \right) z^{-N_{EL}}.$$

$$\Phi_{\text{samp}}/\Phi_{\text{in}} = (L(e^{-j\omega})) / (1 + L(e^{-j\omega}))$$


[Sonntag JSSC 2006]

Digital PLL-based CDR

 

[Sonntag JSSC 2006]


Single-Loop CDR Issues

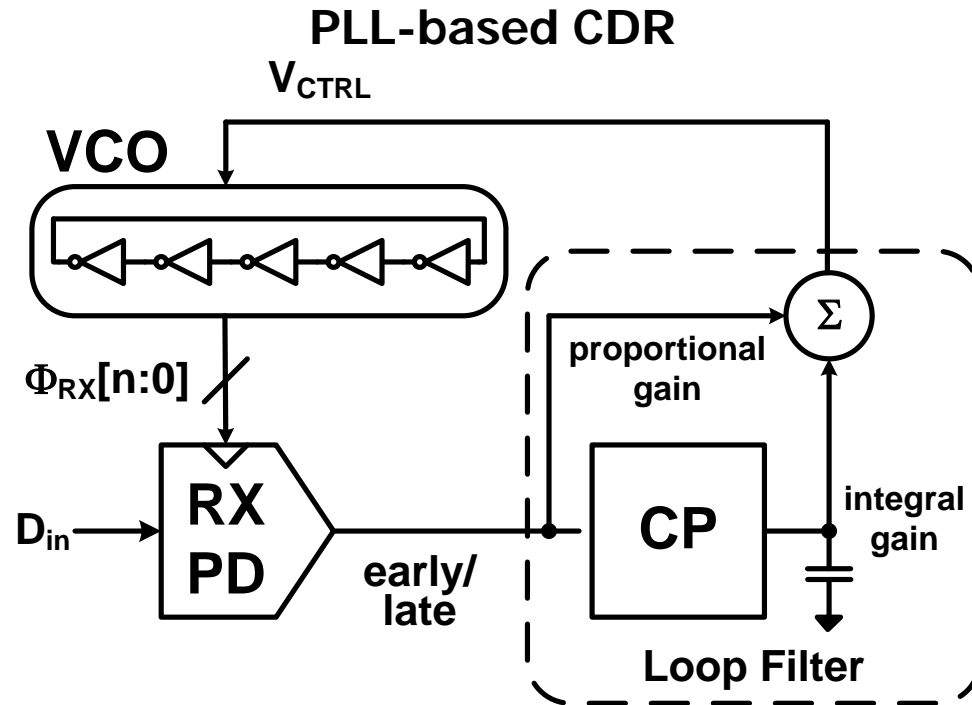


- Phase detectors have limited frequency acquisition range
 - Results in long lock times or not locking at all
 - Can potentially lock to harmonics of correct clock frequency
- VCO frequency range varies with voltage and temperature

Phase and Frequency Tracking Loops

[Hsieh]

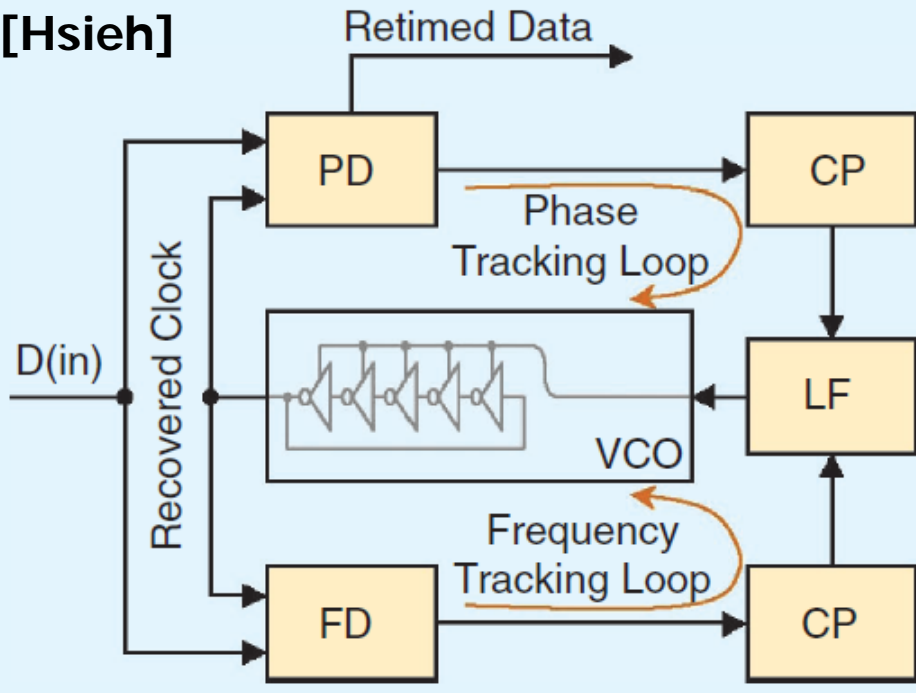

Frequency Detector

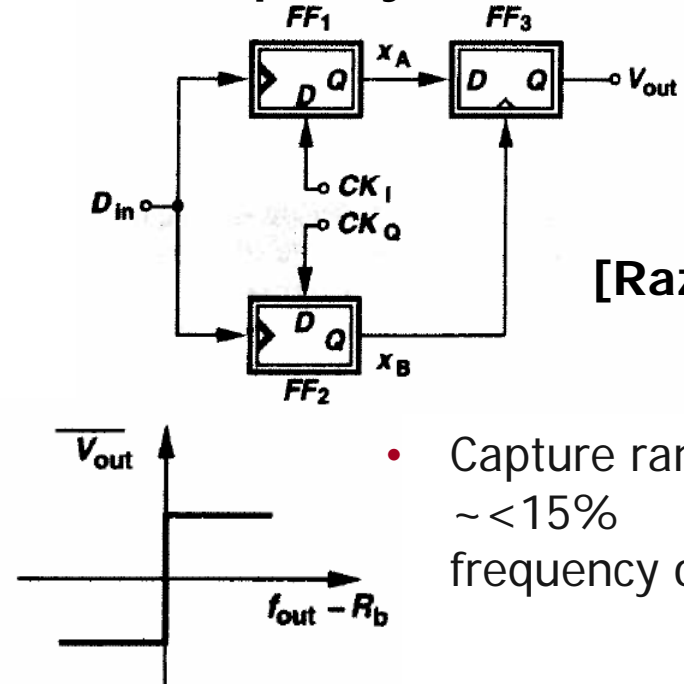


[Razavi]

- Frequency tracking loop operates during startup or loss of phase lock
 - Ideally should be mostly off in normal operation
- Frequency loop bandwidth typically much smaller than phase loop bandwidth to prevent loop interaction

Analog Dual-Loop CDR w/ Two VCOs

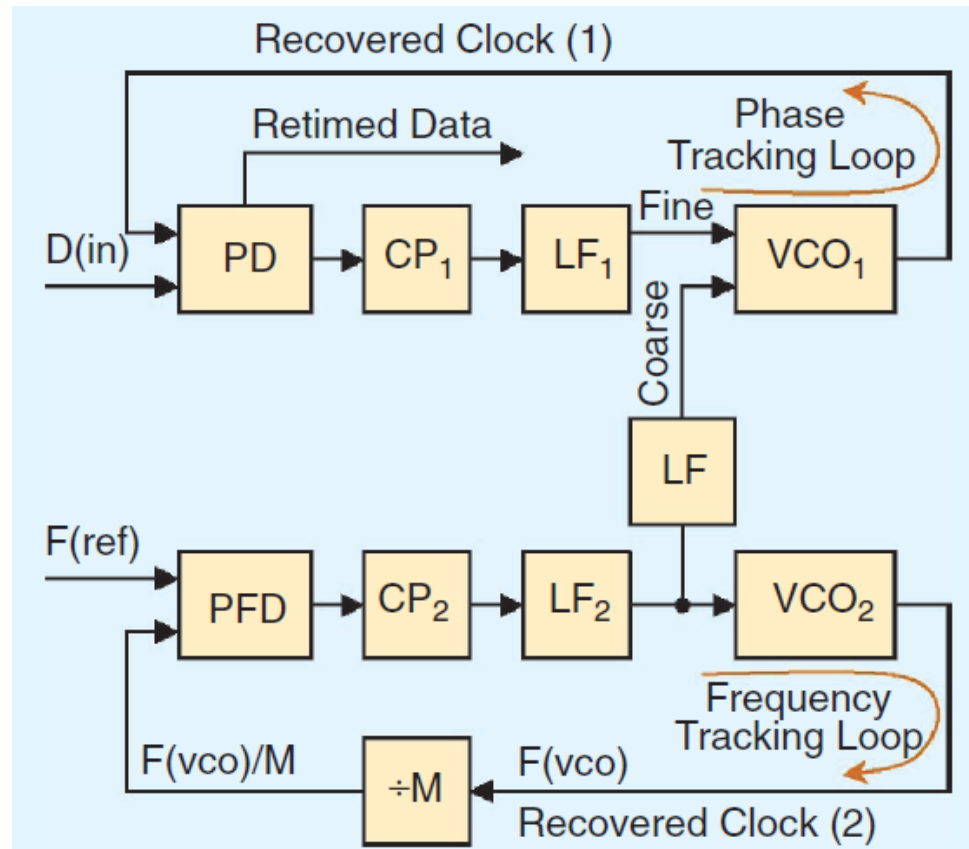
- Frequency synthesis loop with replica VCO provides a “coarse” control voltage to set phase tracking loop frequency
- Frequency loop can be a global PLL shared by multiple channels
- Issues
 - VCO matching
 - VCO pulling
 - Distributing voltage long distances



[Hsieh]

Analog Dual-Loop CDR w/ One VCO

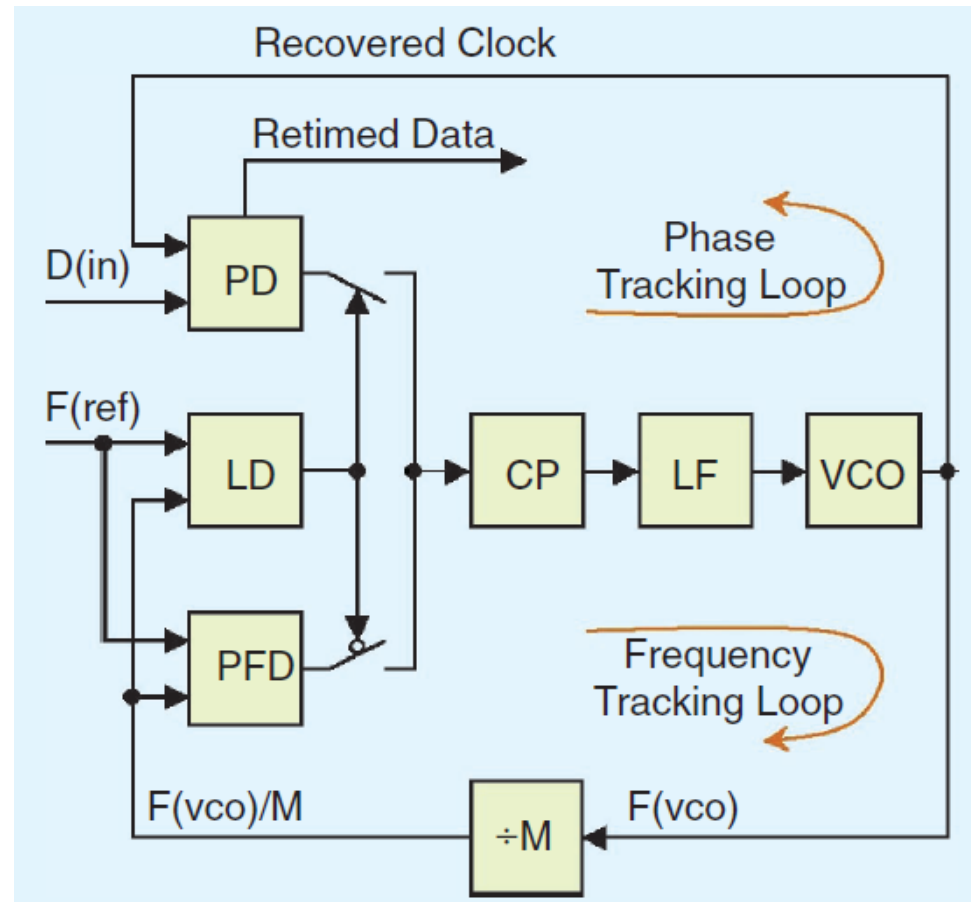
- Frequency loop operates during startup or loss of phase lock
 - Ideally should be mostly off in normal operation
- Input reference clock simplifies frequency loop design
- Care must be taken when switching between loops to avoid disturbing VCO control voltage and loose frequency lock



[Hsieh]

Phase Interpolator (PI) Based CDR


- Frequency synthesis loop produces multiple clock phases used by the phase interpolators
- Phase interpolator mixes between input phases to produce a fine sampling phase
 - Ex: Quadrature 90° PI inputs with 5 bit resolution provides sampling phases spaced by $90^\circ / (2^5 - 1) = 2.9^\circ$
- Digital phase tracking loop offers advantages in robustness, area, and flexibility to easily reprogram loop parameters

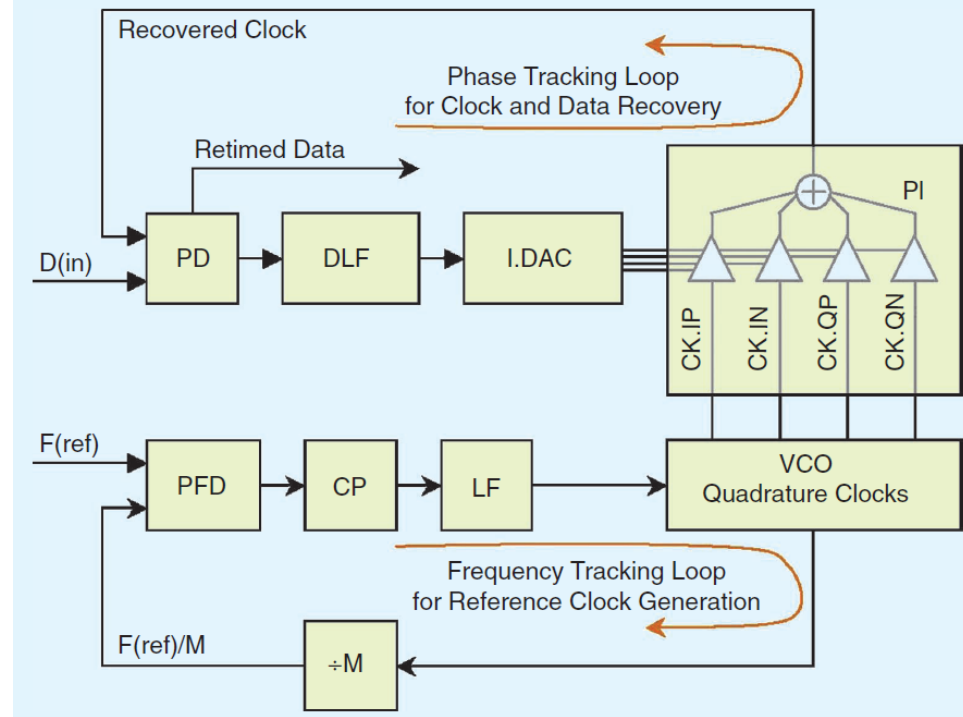

[Hsieh]


Phase Interpolator (PI) Based CDR

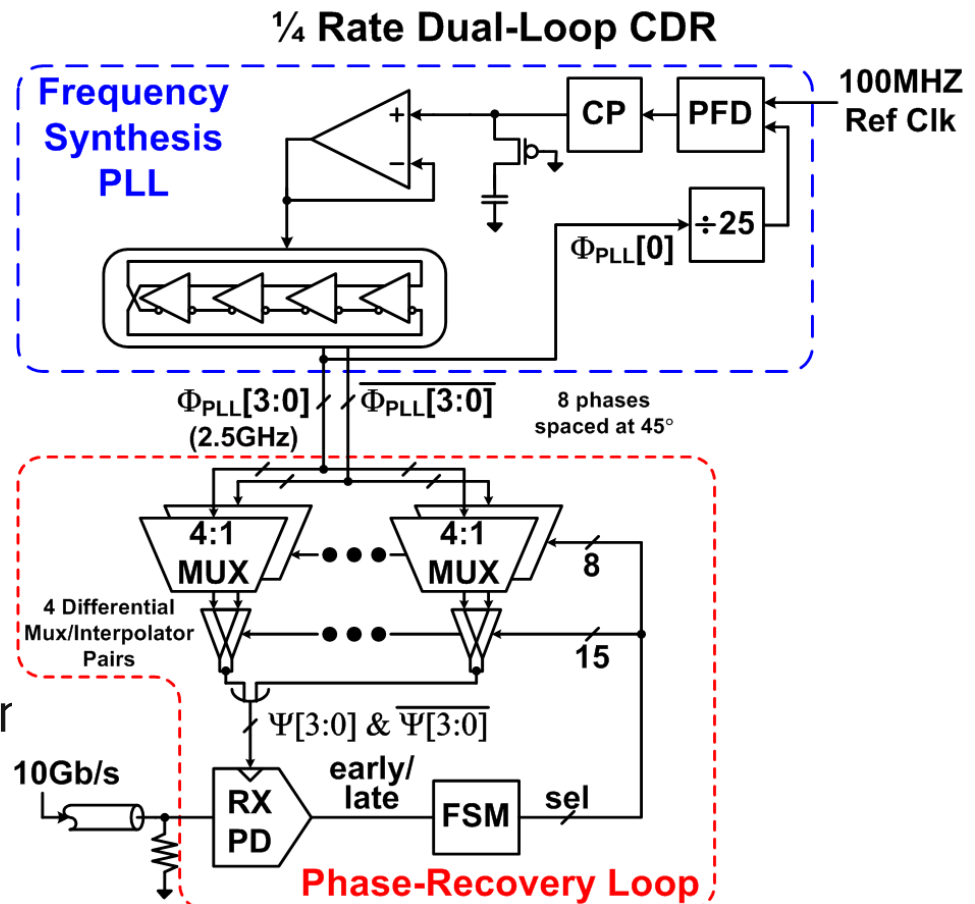- Frequency synthesis loop can be a global PLL
- Can be difficult to distribute multiple phases long distance
 - Need to preserve phase spacing
 - Clock distribution power increases with phase number
 - If CDR needs more than 4 phases consider local phase generation




DLL Local Phase Generation

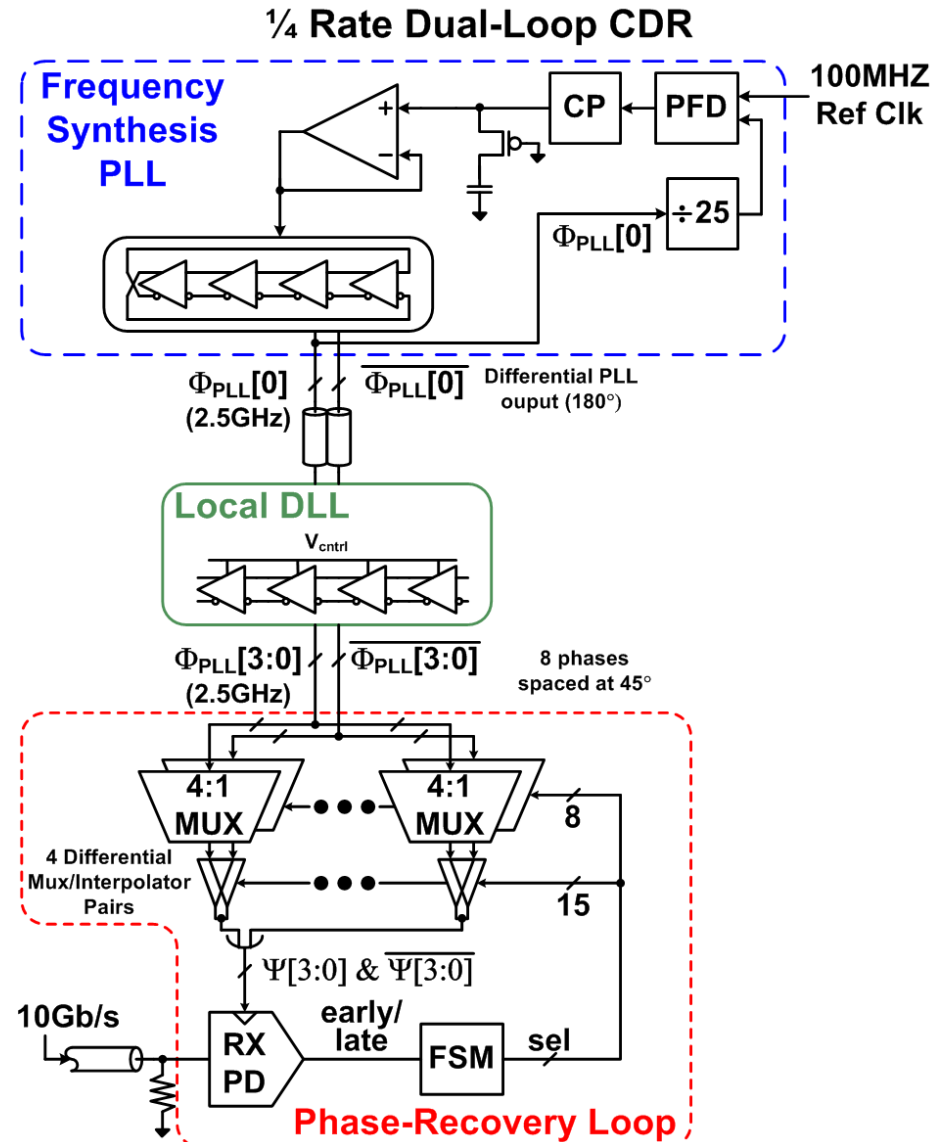- Only differential clock is distributed from global PLL
- Delay-Locked Loop (DLL) locally generates the multiple clock phases for the phase interpolators
 - DLL can be per-channel or shared by a small number (4)
- Same architecture can be used in a forwarded-clock system
 - Replace frequency synthesis PLL with forwarded-clock signals




Phase Rotator PLL

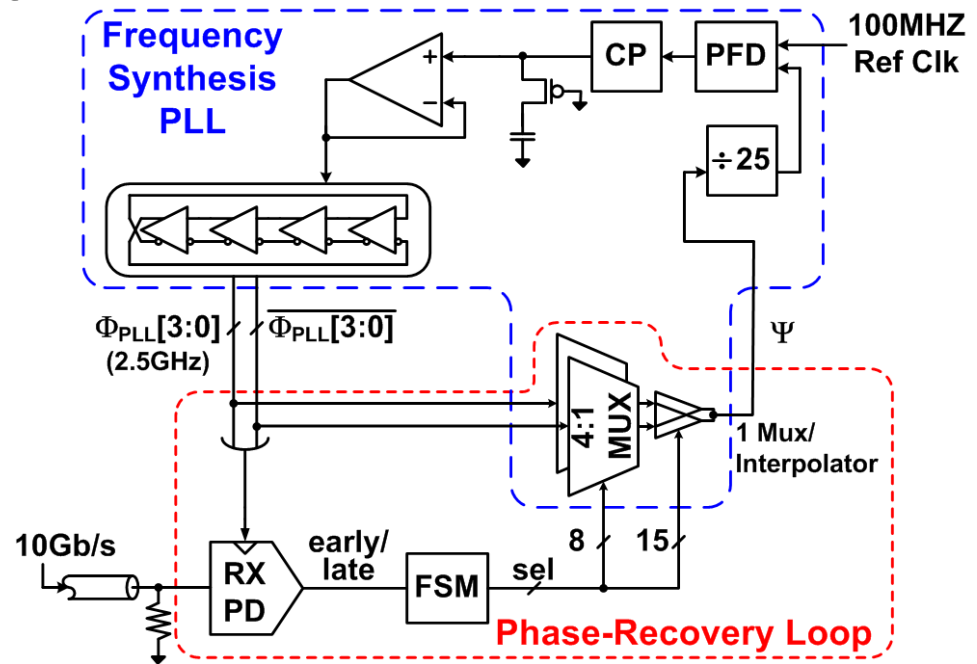- Phase interpolators can be expensive in terms of power and area
- Phase rotator PLL places **one** interpolator in PLL feedback to adjust all VCO output phases simultaneously
- Now frequency synthesis and phase recovery loops are coupled
 - Need PLL bandwidth greater than phase loop
 - Useful in filtering VCO noise




Phase Interpolators

 - Phase interpolators realize digital-to-phase conversion (DPC)
- Produce an output clock that is a weighted sum of two input clock phases
- Common circuit structures
 - Tail current summation interpolation
 - Voltage-mode interpolation
- Interpolator code mapping techniques
 - Sinusoidal
 - Linear




Phase Interpolator Examples

Tail-Current Summation

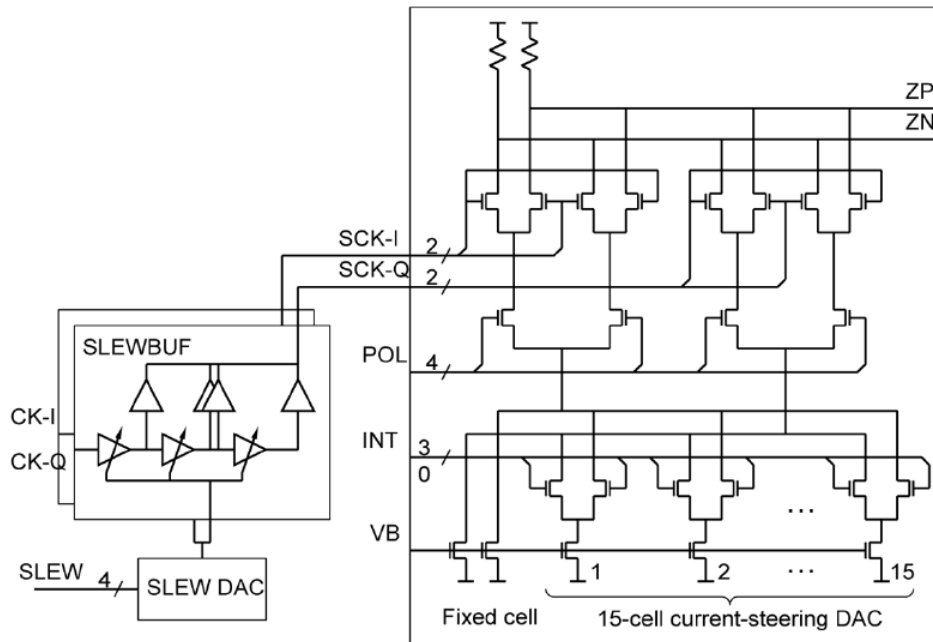


[Bulzacchelli JSSC 2006]

Voltage-Mode Summation

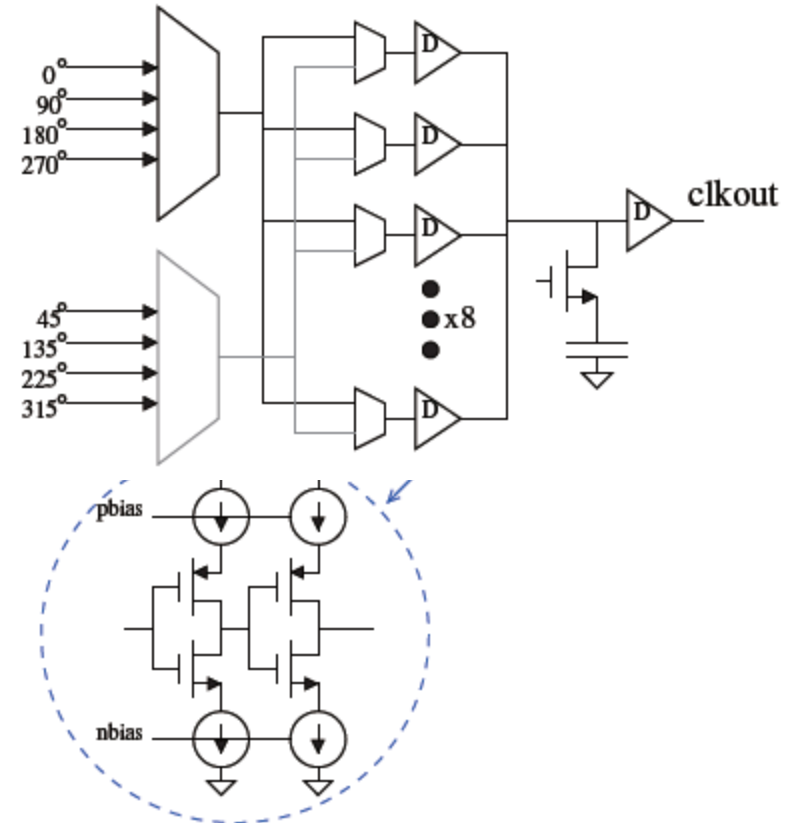

[Joshi VLSI Symp 2009]


Delay-Locked Loop (DLL)

 

[Sidiropoulos JSSC 1997]

- DLLs lock delay of a voltage-controlled delay line (VCDL)
- Typically lock the delay to 1 or $\frac{1}{2}$ input clock cycles
 - If locking to $\frac{1}{2}$ clock cycle the DLL is sensitive to clock duty cycle
- DLL does not self-generate the output clock, only delays the input clock

Delay-Locked Loop (DLL)

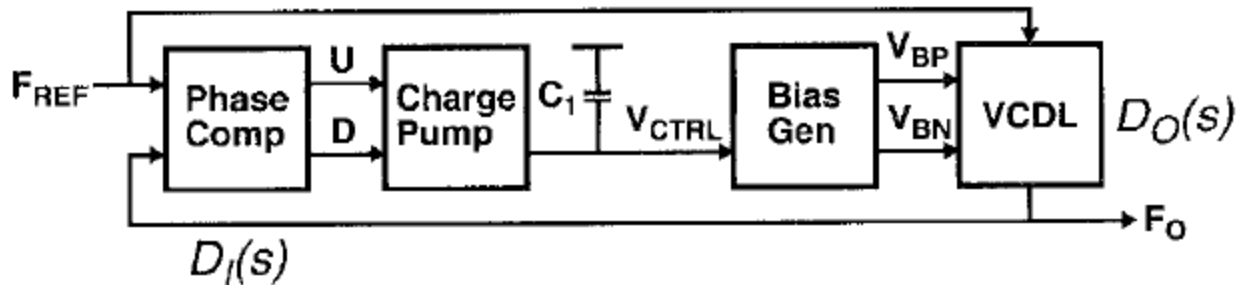

[Maneatis JSSC 1996]

$$\frac{D_O(s)}{D_I(s)} = \frac{1}{1 + s/\omega_N}$$

$$\omega_N = I_{CH} \cdot K_{DL} \cdot F_{REF} \cdot \frac{1}{C_1}$$

- First-order loop as delay line doesn't introduce a pole
- VCDL doesn't accumulate jitter like a VCO
- DLL doesn't filter input jitter

Next Time

- CDR Wrap-Up
 - PI
 - DLL
 - Jitter Properties
- Injection-Locked Oscillator De-Skew