

ECEN689: Special Topics in High-Speed Links Circuits and Systems Spring 2011

Lecture 3: Transmission Lines



Sam Palermo

Analog & Mixed-Signal Center

Texas A&M University

Announcements

- HW1 due 1/28
 - One page summary of recent link design paper
- Lecture Reference Material
 - Dally, Chapter 3.1 – 3.4


Agenda

- Transmission Lines
 - Propagation constant
 - Characteristic impedance
 - Loss
 - Reflections
 - Termination examples
 - Differential transmission lines

Wire Models

- Model Types

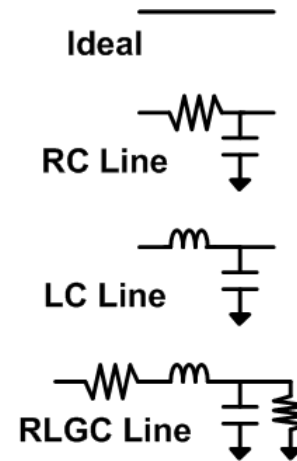
- Ideal
- Lumped C, R, L
- RC transmission line
- LC transmission line
- RLGC transmission line



- Condition for LC or RLGC model (vs RC) $f_0 \geq \frac{R}{2\pi L}$

| Wire | R | L | C | >f (LC wire) |
|---|---------|---------|---------|--------------|
| AWG24 Twisted Pair | 0.08Ω/m | 400nH/m | 40pF/m | 32kHz |
| PCB Trace | 5Ω/m | 300nH/m | 100pF/m | 2.7MHz |
| On-Chip Min. Width M6 (0.18μm CMOS node) | 40kΩ/m | 4μH/m | 300pF/m | 1.6GHz |

RLGC Transmission Line Model

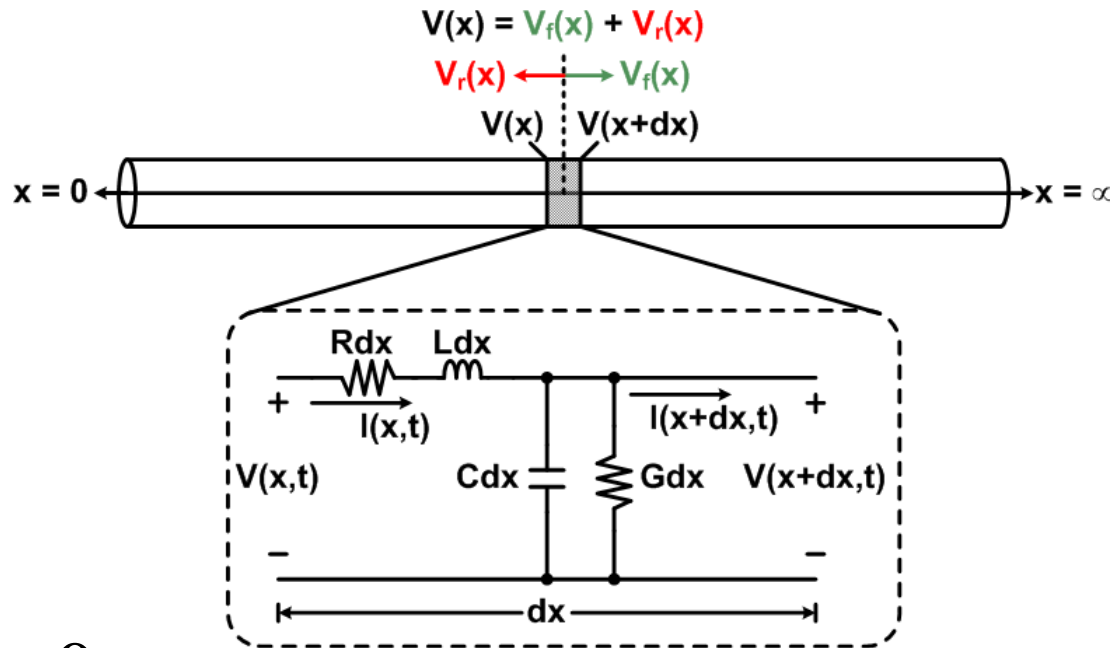

As $dx \rightarrow 0$

$$\frac{\partial V(x,t)}{\partial x} = -RI(x,t) - L \frac{\partial I(x,t)}{\partial t} \quad (1)$$

$$\frac{\partial I(x,t)}{\partial x} = -GV(x,t) - C \frac{\partial V(x,t)}{\partial t} \quad (2)$$

(1) }
 (2) } **General Transmission Line Equations**

Time-Harmonic Transmission Line Eqs.

- Assuming a traveling sinusoidal wave with angular frequency, ω

$$\frac{dV(x)}{dx} = -(R + j\omega L)I(x) \quad (3)$$

$$\frac{dI(x)}{dx} = -(G + j\omega C)V(x) \quad (4)$$

- Differentiating (3) and plugging in (4) (and vice versa)

$$\frac{d^2V(x)}{dx^2} = \gamma^2 V(x) \quad (5)$$

$$\frac{d^2I(x)}{dx^2} = \gamma^2 I(x) \quad (6)$$

Time-Harmonic
Transmission
Line Equations

- where γ is the **propagation constant**

$$\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} \quad (\text{m}^{-1})$$

Transmission Line Propagation Constant

- Solutions to the Time-Harmonic Line Equations:

$$V(x) = V_f(x) + V_r(x) = V_{f0}e^{-\gamma x} + V_{r0}e^{\gamma x}$$

$$I(x) = I_f(x) + I_r(x) = I_{f0}e^{-\gamma x} + I_{r0}e^{\gamma x}$$

where $\gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$ (m⁻¹)

- What does the propagation constant tell us?
 - Real part (α) determines attenuation/distance (Np/m)
 - Imaginary part (β) determines phase shift/distance (rad/m)
 - **Signal phase velocity**


$$v = \omega / \beta \quad (\text{m/s})$$

Transmission Line Impedance, Z_0

- For an infinitely long line, the voltage/current ratio is Z_0
- From time-harmonic transmission line eqs. (3) and (4)

$$Z_0 = \frac{V(x)}{I(x)} = \sqrt{\frac{R + j\omega L}{G + j\omega C}} \quad (\Omega)$$

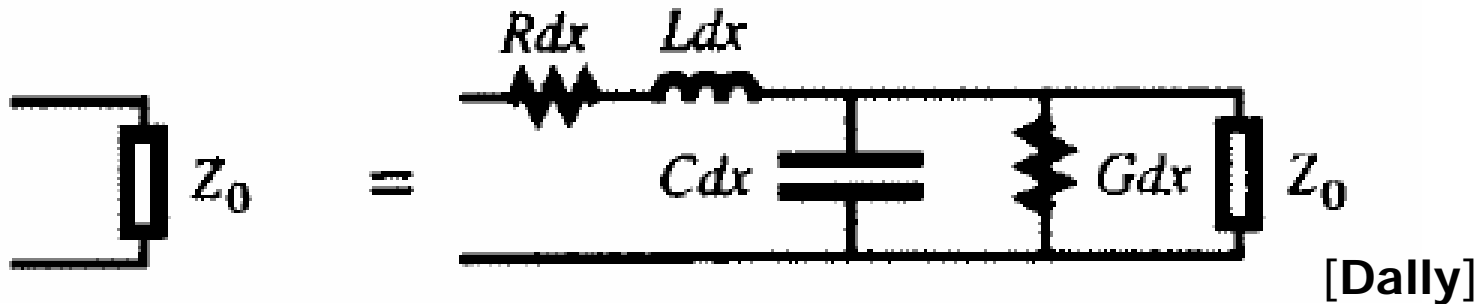- Driving a line terminated by Z_0 is the same as driving an infinitely long line



Lossless LC Transmission Lines

- If $R_{dx} = G_{dx} = 0$

$$\gamma = \alpha + j\beta = j\omega\sqrt{LC}$$



$$\alpha = 0 \rightarrow \text{No Loss!}$$

$$\beta = \omega\sqrt{LC}$$

- Waves propagate w/o distortion
 - Velocity and impedance independent of frequency
 - Impedance is purely real

$$v = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

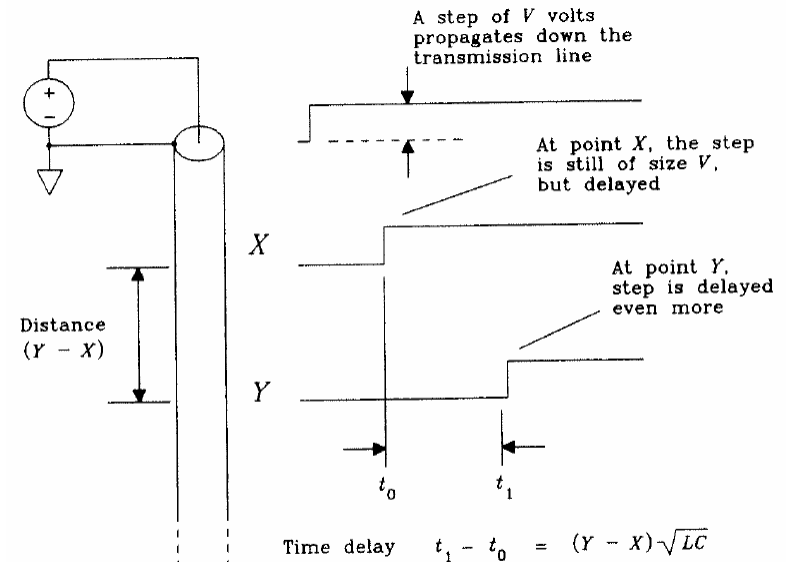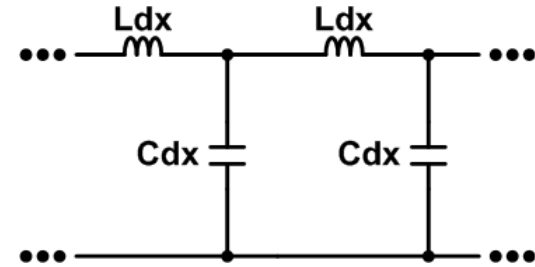

[Johnson]

Low-Loss LRC Transmission Lines

- If $R/\omega L$ and $G/\omega C \ll 1$
- Behave similar to ideal LC transmission line, but ...

- Experience resistive and dielectric loss
- Frequency dependent propagation velocity results in dispersion
 - Fast step, followed by slow DC tail

$$\begin{aligned}\gamma &= \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} \\ &\cong j\omega\sqrt{LC} \left(1 - j \frac{RC + GL}{\omega LC} \right)^{\frac{1}{2}} \\ &\cong \frac{R}{2Z_0} + \frac{GZ_0}{2} + j\omega\sqrt{LC} \left[1 + \frac{1}{8} \left(\frac{R}{\omega L} \right)^2 + \frac{1}{8} \left(\frac{G}{\omega C} \right)^2 \right] \\ &= \alpha_R + \alpha_D + j\beta\end{aligned}$$

$$\alpha_R \cong \frac{R}{2Z_0}$$

$$\alpha_D \cong \frac{GZ_0}{2}$$

Resistive Loss


Dielectric Loss

$$\beta \cong \omega\sqrt{LC} \left[1 + \frac{1}{8} \left(\frac{R}{\omega L} \right)^2 + \frac{1}{8} \left(\frac{G}{\omega C} \right)^2 \right]$$

$$v \cong \left(\sqrt{LC} \left[1 + \frac{1}{8} \left(\frac{R}{\omega L} \right)^2 + \frac{1}{8} \left(\frac{G}{\omega C} \right)^2 \right] \right)^{-1}$$

Skin Effect (Resistive Loss)

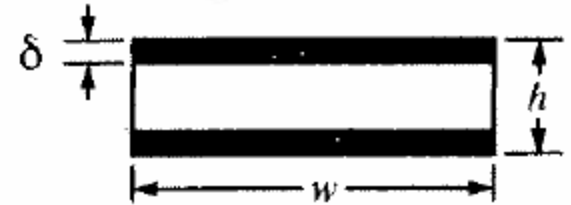- High-frequency current density falls off exponentially from conductor surface
- Skin depth, δ , is where current falls by e^{-1} relative to full conductor
 - Decreases proportional to $\sqrt{\text{frequency}}$
- Relevant at critical frequency f_s where skin depth equals half conductor height (or radius)
 - Above f_s resistance/loss increases proportional to $\sqrt{\text{frequency}}$



[Dally]

$$J = e^{-\frac{d}{\delta}} \quad \delta = (\pi f \mu \sigma)^{-\frac{1}{2}}$$

For rectangular conductor:

$$f_s = \frac{\rho}{\pi \mu \left(\frac{h}{2}\right)^2}$$

$$R(f) = R_{DC} \left(\frac{f}{f_s}\right)^{\frac{1}{2}}$$

$$\alpha_R = \frac{R_{DC}}{2Z_0} \left(\frac{f}{f_s}\right)^{\frac{1}{2}}$$

Skin Effect (Resistive Loss)


5-mil Stripguide

$$R_{DC} = 7 \Omega/m, f_s = 43 \text{ MHz}$$

30 AWG Pair

$$R_{DC} = 0.08 \Omega/m, f_s = 67 \text{ kHz}$$
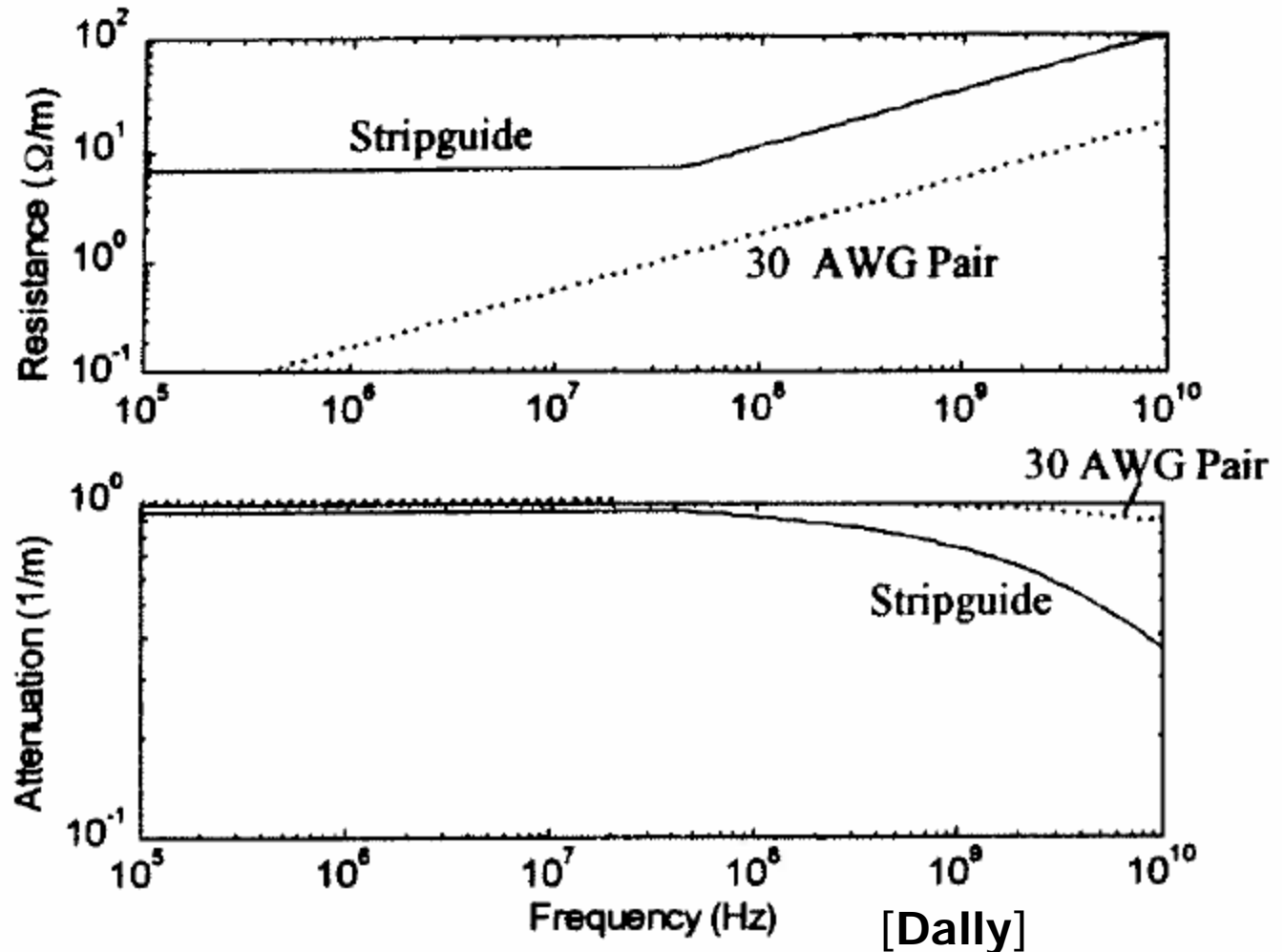
$$\alpha_R = \frac{R_{DC}}{2Z_0} \left(\frac{f}{f_s} \right)^{\frac{1}{2}}$$



Dielectric Absorption (Loss)

- An alternating electric field causes dielectric atoms to rotate and absorb signal energy in the form of heat
- Dielectric loss is expressed in terms of the loss tangent
- Loss increases directly proportional to frequency

$$\tan \delta_D = \frac{G}{\omega C}$$


TABLE 3-4 Electrical Properties of PC Board Dielectrics

| Material | ϵ_r | $\tan \delta_D$ |
|--|--------------|-----------------|
| Woven glass, epoxy resin ("FR-4") | 4.7 | 0.035 |
| Woven glass, polyimide resin | 4.4 | 0.025 |
| Woven glass, polyphenylene oxide resin (GETEK) | 3.9 | 0.010 |
| Woven glass, PTFE resin (Teflon) | 2.55 | 0.005 |
| Nonwoven glass, PTFE resin | 2.25 | 0.001 |



[Dally]

$$\alpha_D = \frac{GZ_0}{2} = \frac{2\pi f C \tan \delta_D \sqrt{L/C}}{2} = \pi f \tan \delta_D \sqrt{LC}$$

Total Wire Loss

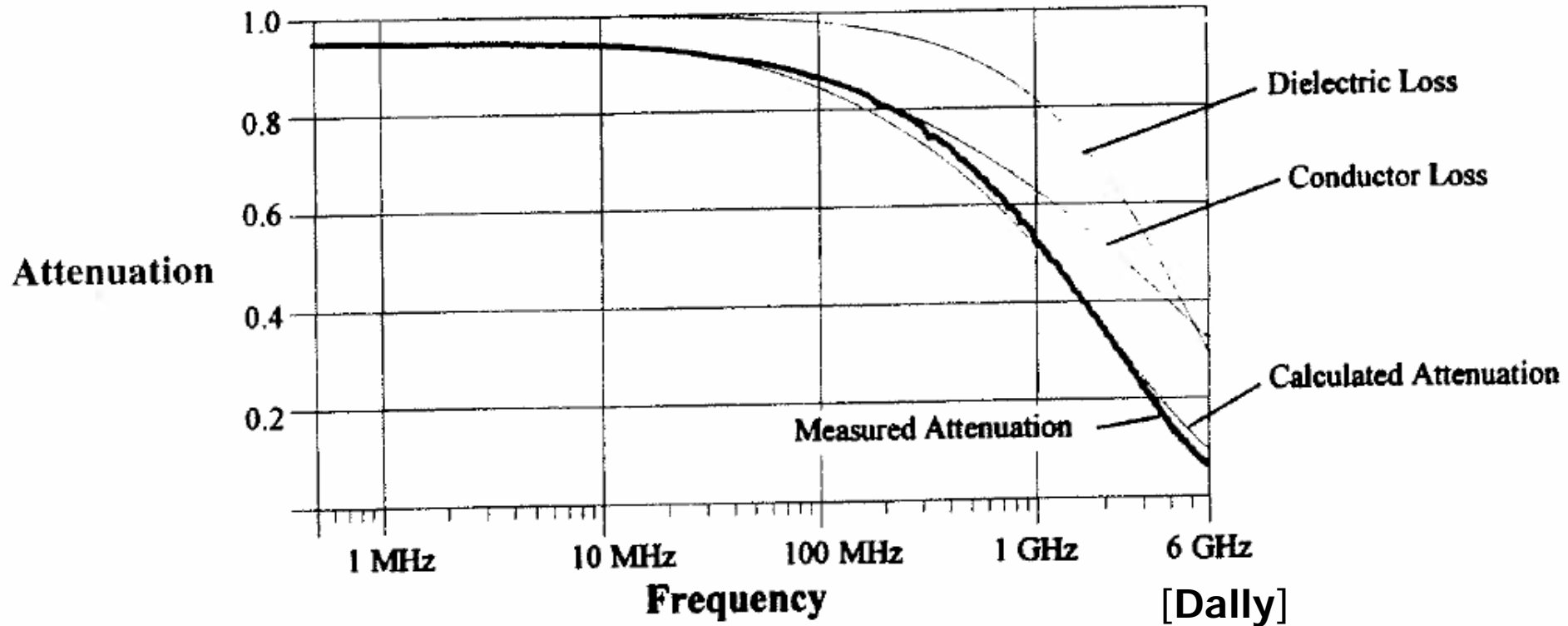

Reflections & Telegrapher's Eq.

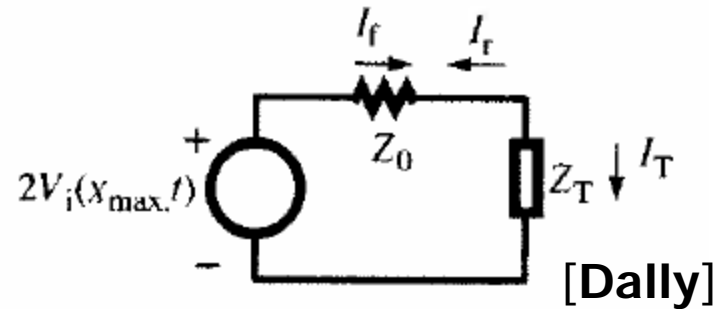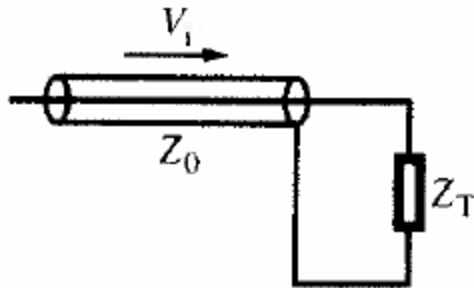

- With a Thevenin-equivalent mode of the line:

Termination Current:
$$I_T = \frac{2V_i}{Z_0 + Z_T}$$

- KCL at Termination:

$$I_r = I_f - I_T$$


$$I_r = \frac{V_i}{Z_0} - \frac{2V_i}{Z_T + Z_0}$$

$$I_r = \frac{V_i}{Z_0} \left(\frac{Z_T - Z_0}{Z_T + Z_0} \right)$$

Telegrapher's Equation or
Reflection Coefficient

$$k_r = \frac{I_r}{I_i} = \frac{V_r}{V_i} = \frac{Z_T - Z_0}{Z_T + Z_0}$$

Termination Examples - Ideal

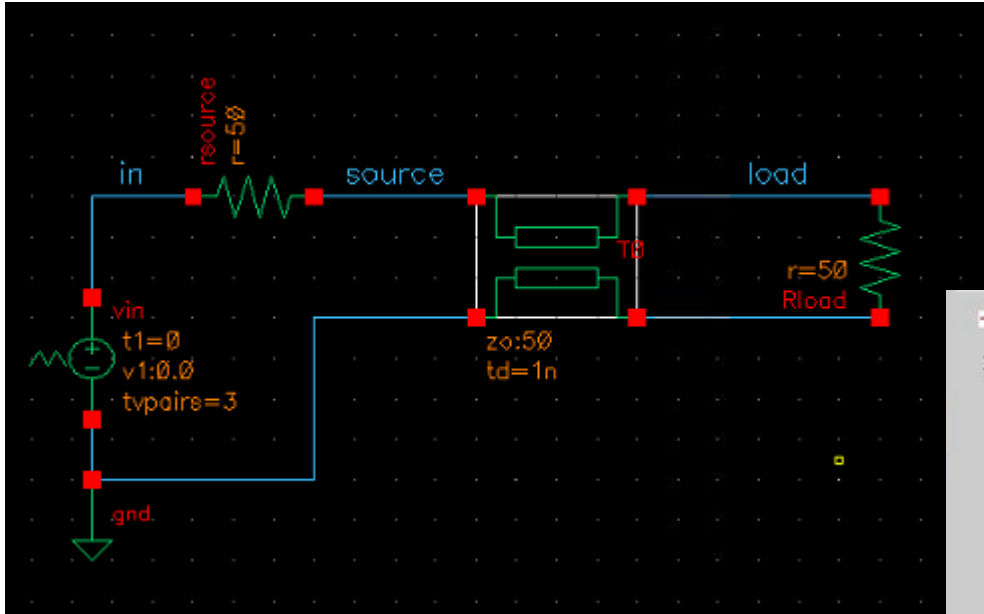

$$R_S = 50\Omega$$


$$Z_0 = 50\Omega, t_d = 1\text{ns}$$

$$R_T = 50\Omega$$


$$V_i = 1V \left(\frac{50}{50 + 50} \right) = 0.5V$$

$$k_{rT} = \frac{50 - 50}{50 + 50} = 0$$

$$k_{rS} = \frac{50 - 50}{50 + 50} = 0$$

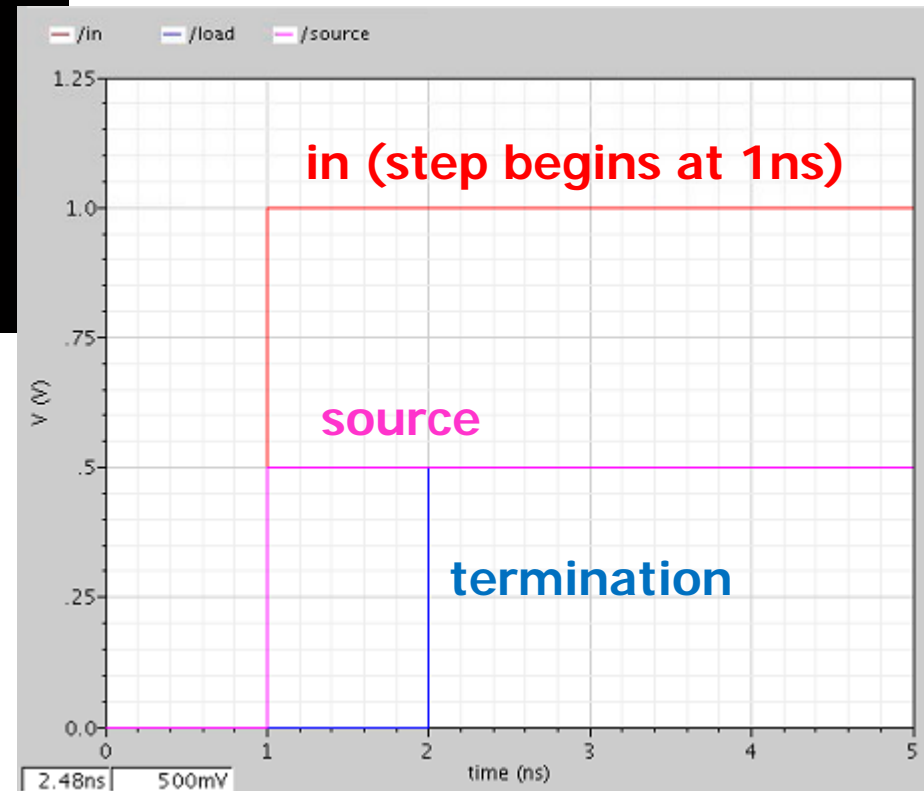

Termination Examples - Open

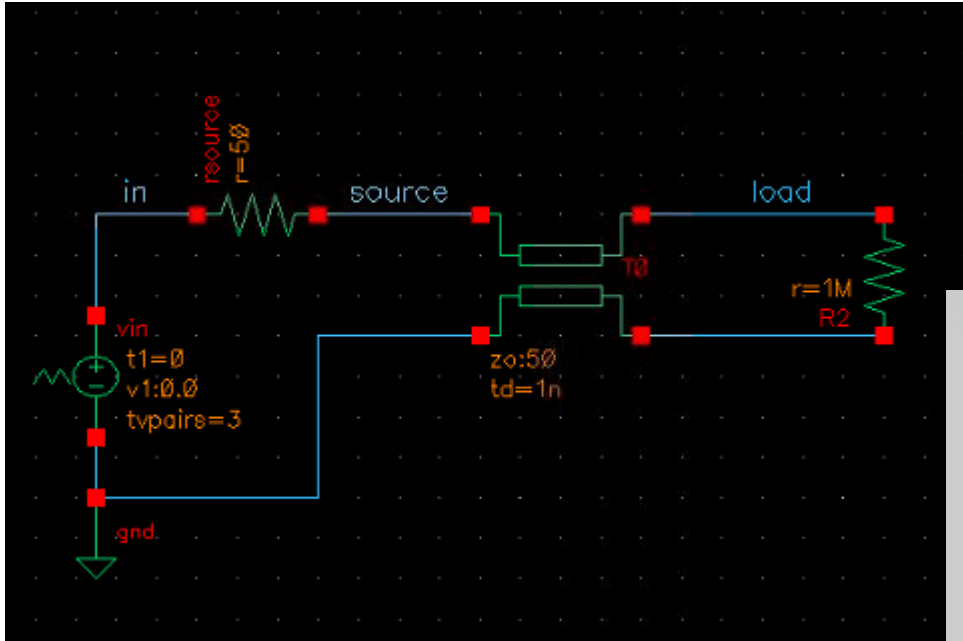

$$R_S = 50\Omega$$


$$Z_0 = 50\Omega, t_d = 1\text{ns}$$

$$R_T \sim \infty (1\text{M}\Omega)$$


$$V_i = 1V \left(\frac{50}{50 + 50} \right) = 0.5V$$

$$k_{rT} = \frac{\infty - 50}{\infty + 50} = +1$$

$$k_{rS} = \frac{50 - 50}{50 + 50} = 0$$

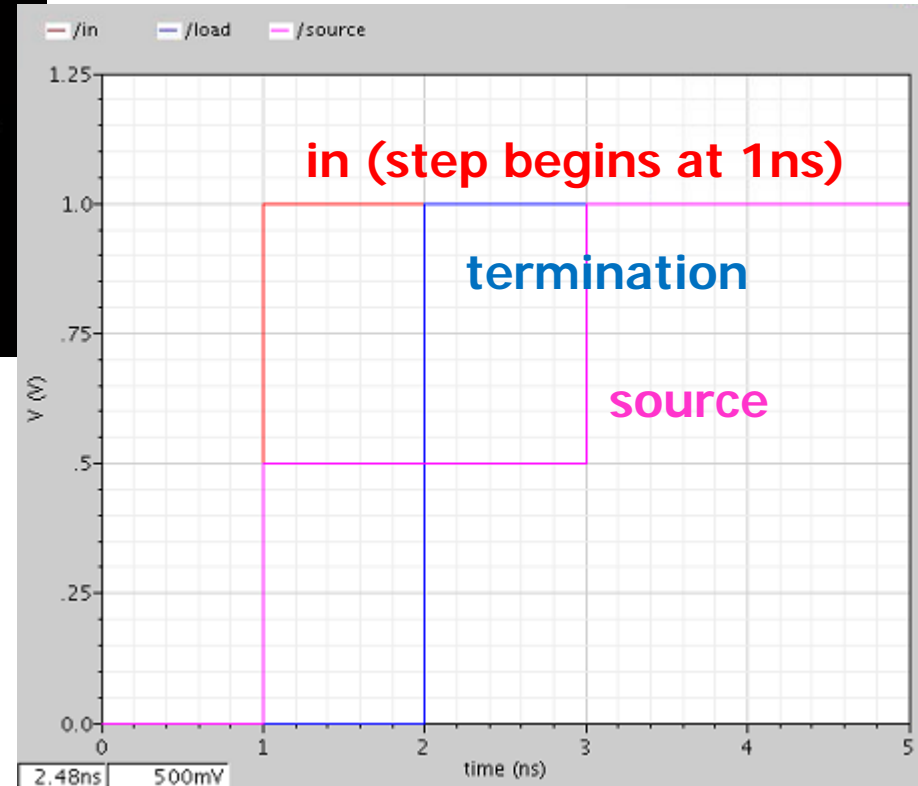

Termination Examples - Short

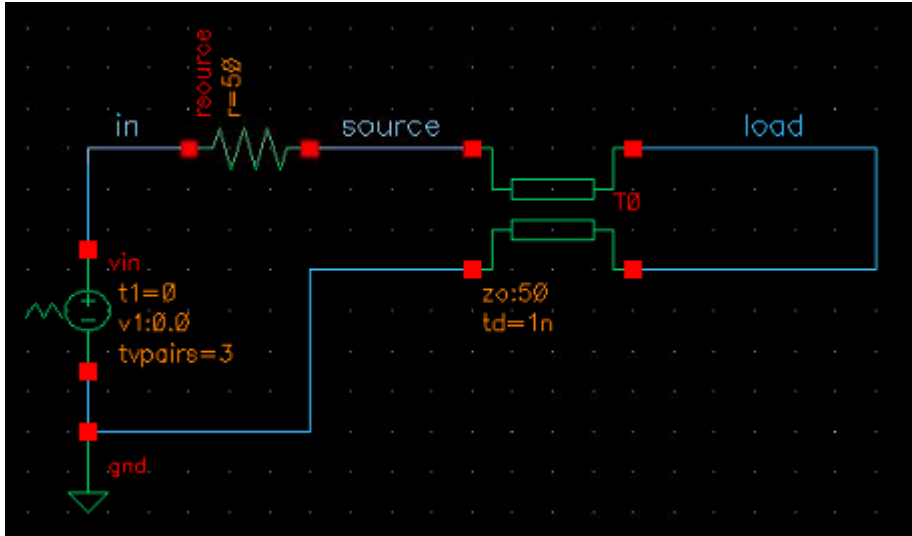

$$R_S = 50\Omega$$


$$Z_0 = 50\Omega, t_d = 1\text{ns}$$

$$R_T = 0\Omega$$


$$V_i = 1V \left(\frac{50}{50 + 50} \right) = 0.5V$$

$$k_{rT} = \frac{0 - 50}{0 + 50} = -1$$

$$k_{rS} = \frac{50 - 50}{50 + 50} = 0$$

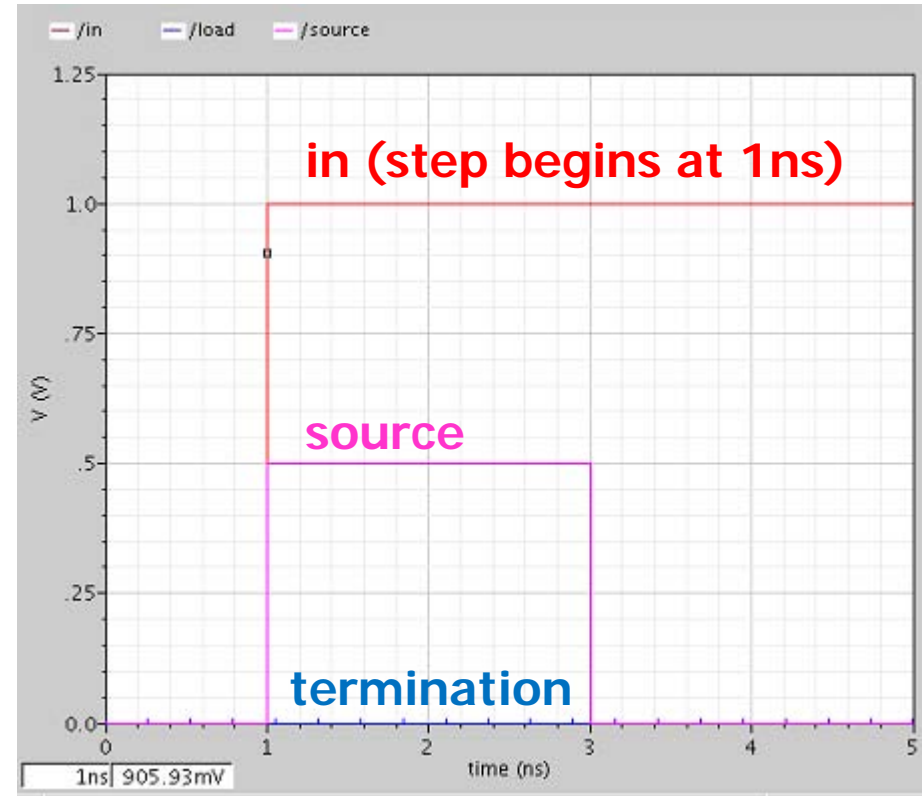

Arbitrary Termination Example

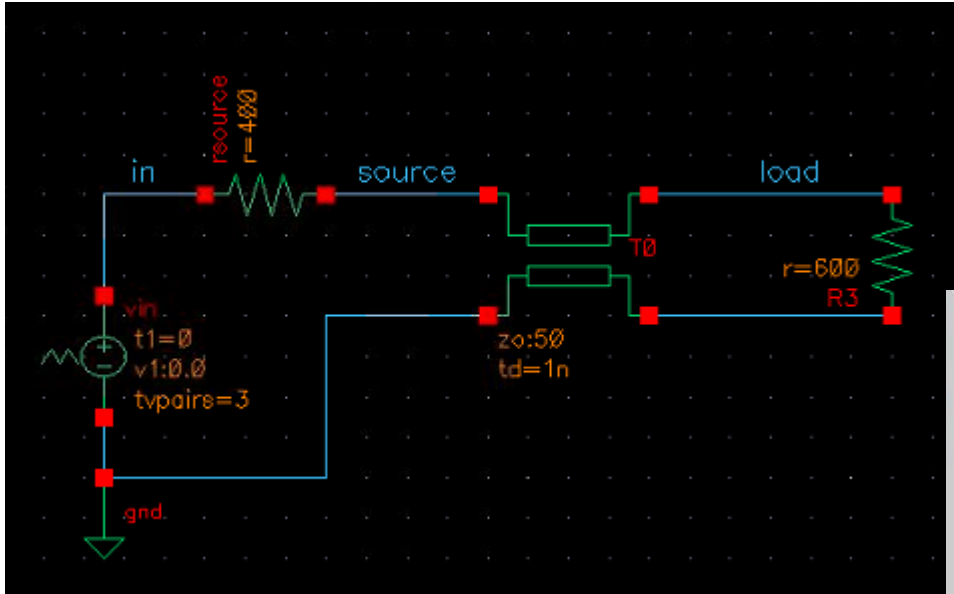

$$R_S = 400\Omega$$


$$Z_0 = 50\Omega, t_d = 1\text{ns}$$

$$R_T = 600\Omega$$

$$V_i = 1V \left(\frac{50}{400 + 50} \right) = 0.111V$$

$$k_{rT} = \frac{600 - 50}{600 + 50} = 0.846$$
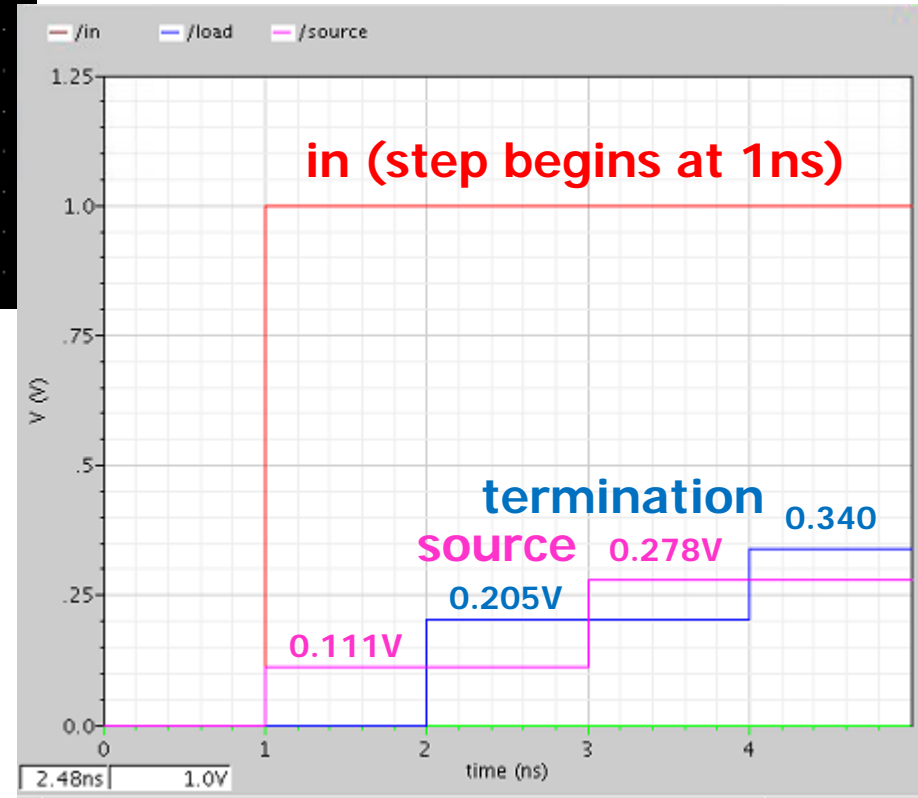
$$k_{rS} = \frac{400 - 50}{400 + 50} = 0.778$$





Lattice Diagram


$$R_S = 400\Omega$$

$$Z_0 = 50\Omega, t_d = 1\text{ns}$$


$$R_T = 600\Omega$$

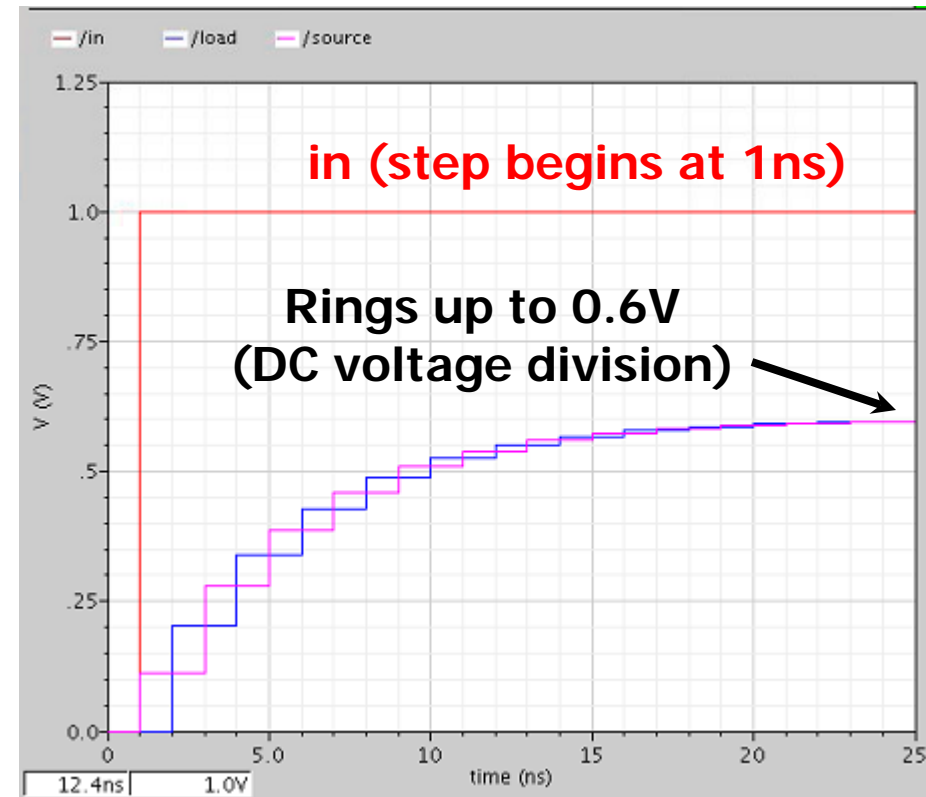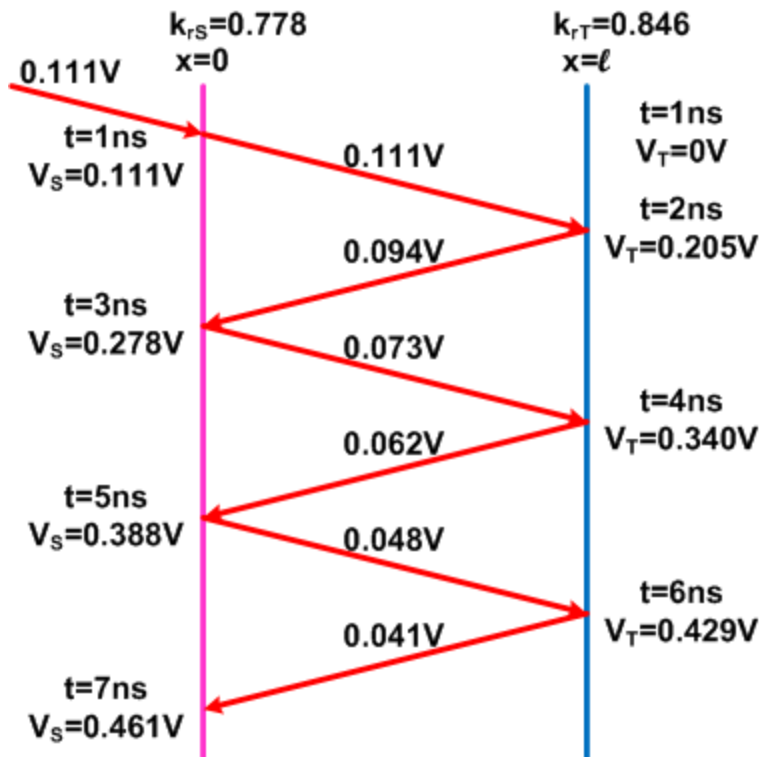


Termination Reflection Patterns

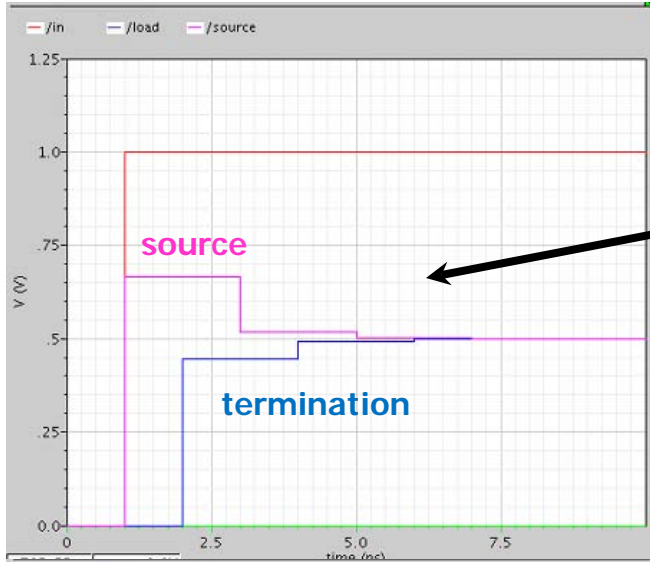

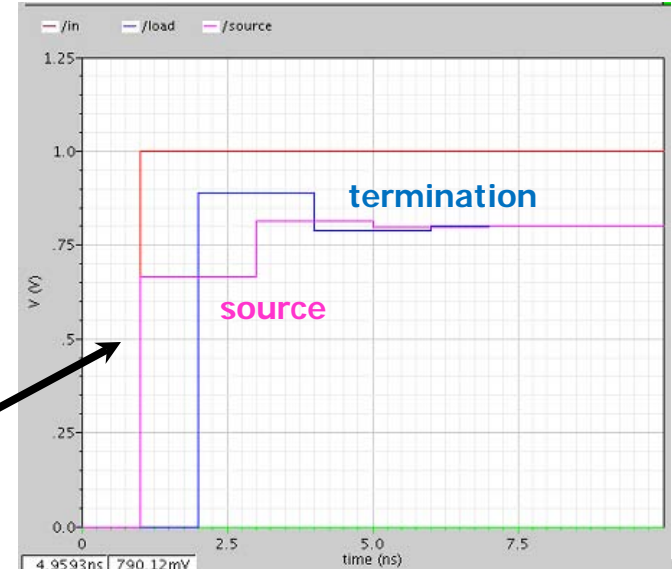
$R_S = 25\Omega, R_T = 100\Omega$
 $kr_S < 0 \text{ \& } kr_T > 0$
Voltages Oscillate



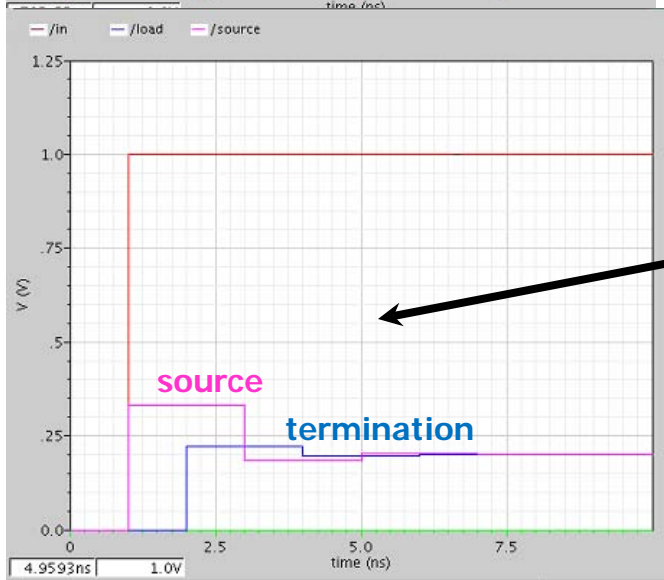$R_S = 100\Omega, R_T = 100\Omega$
 $kr_S > 0 \text{ \& } kr_T > 0$
Voltages Ring Up




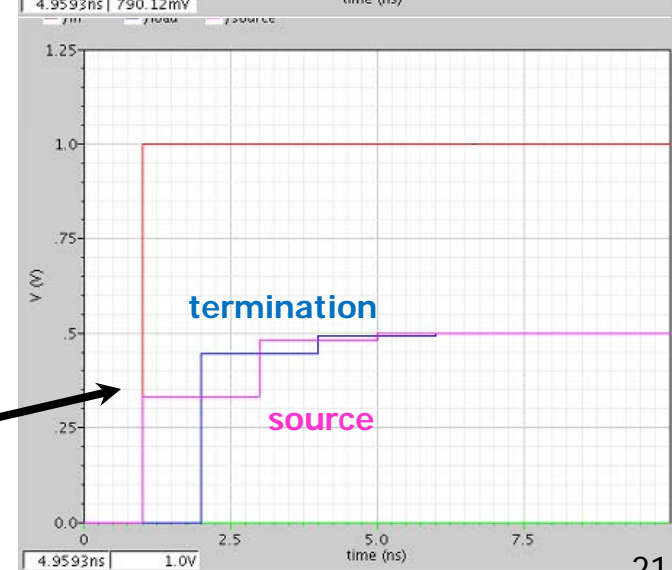$R_S = 100\Omega, R_T = 25\Omega$
 $kr_S > 0 \text{ \& } kr_T < 0$
Voltages Oscillate




Termination Schemes

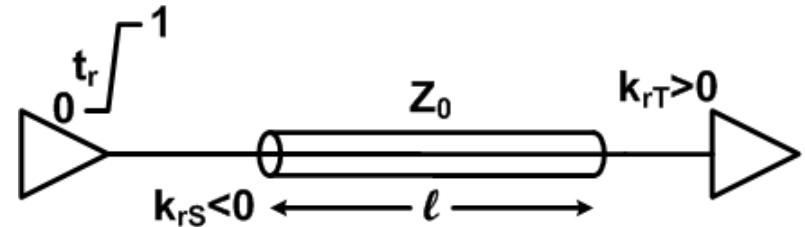- No Termination
 - Little to absorb line energy
 - Can generate oscillating waveform
 - Line must be **very short** relative to signal transition time
 - $n = 4 - 6$
 - Limited off-chip use
- Source Termination
 - Source output takes 2 steps up
 - Used in moderate speed point-to-point connections



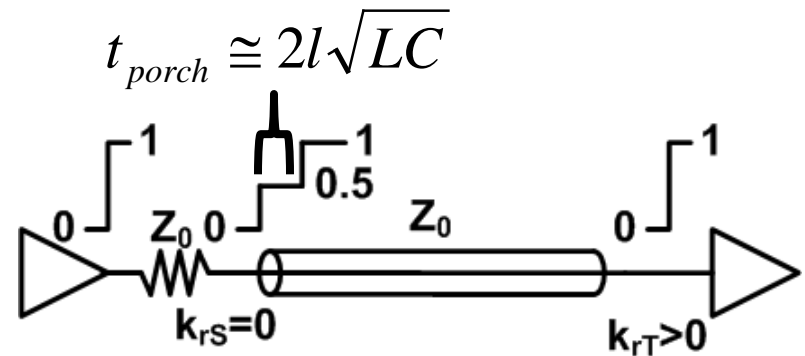
$$t_r > nT_{\text{round-trip}} = 2nl\sqrt{LC}$$




$$t_{\text{porch}} \cong 2l\sqrt{LC}$$

Termination Schemes

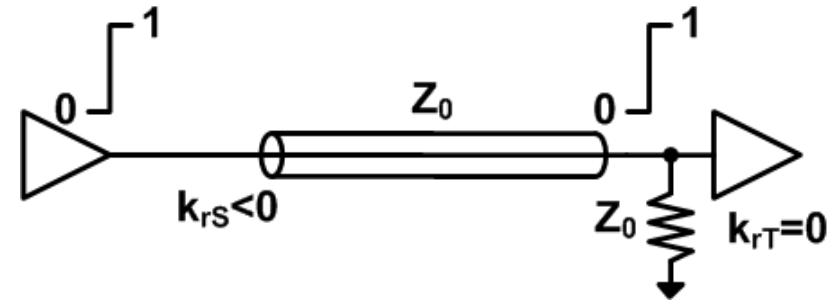- Receiver Termination
 - No reflection from receiver
 - Watch out for intermediate impedance discontinuities
 - Little to absorb reflections at driver




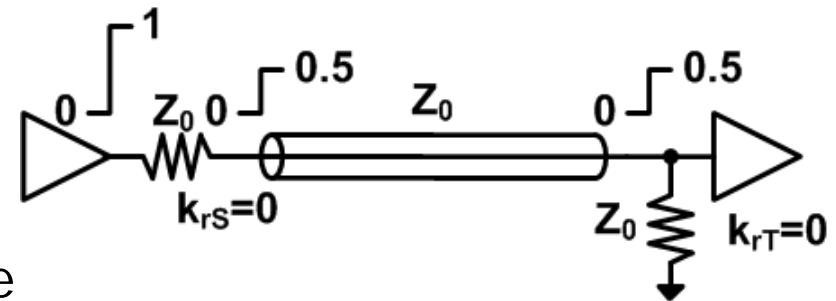- Double Termination
 - Best configuration for min reflections
 - Reflections absorbed at both driver and receiver
 - Get half the swing relative to single termination
 - Most common termination scheme for high performance serial links



Differential Transmission Lines

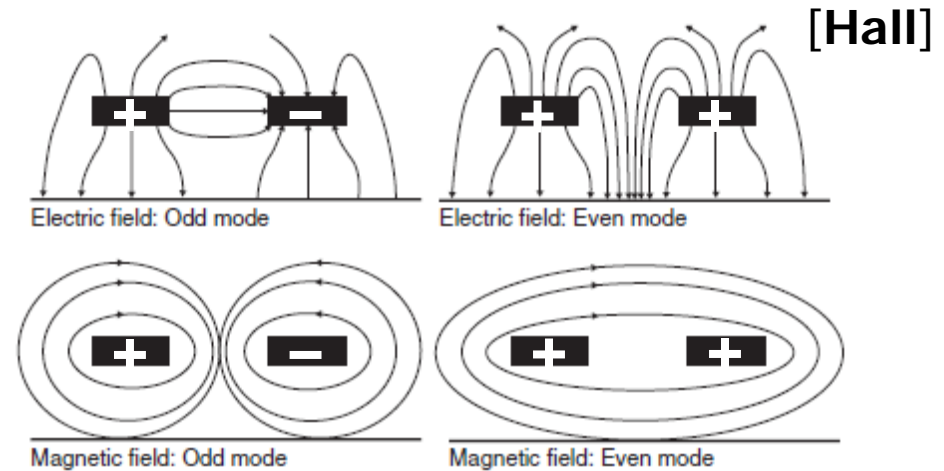- Differential signaling advantages
 - Self-referenced
 - Common-mode noise rejection
 - Increased signal swing
 - Reduced self-induced power-supply noise
- Requires 2x the number of signaling pins relative to single-ended signaling
 - But, smaller ratio of supply/signal (return) pins
 - Total pin overhead is typically 1.3-1.8x (vs 2x)




- Even mode
 - When equal voltages drive both lines, only one mode propagates called even mode
- Odd mode
 - When equal in magnitude, but out of phase, voltages drive both lines, only one mode propagates called odd mode

Balanced Transmission Lines

- Even (common) mode excitation
 - Effective $C = C_C$
 - Effective $L = L + M$
- Odd (differential) mode excitation
 - Effective $C = C_C + 2C_d$
 - Effective $L = L - M$

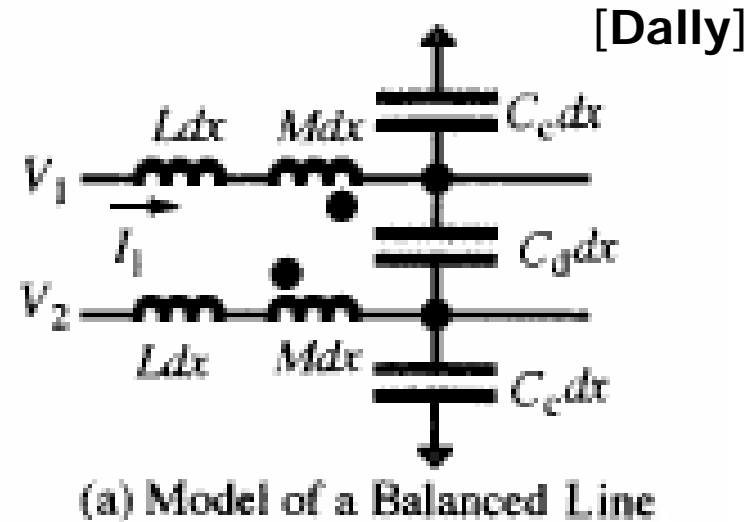
$$Z_{DIFF} = 2Z_{odd}, \quad Z_{CM} = \frac{Z_{even}}{2}$$



$$Z_{even} = \left(\frac{L + M}{C_c} \right)^{1/2}$$

$$Z_{odd} = \left(\frac{L - M}{C_c + 2C_d} \right)^{1/2}$$

PI-Termination

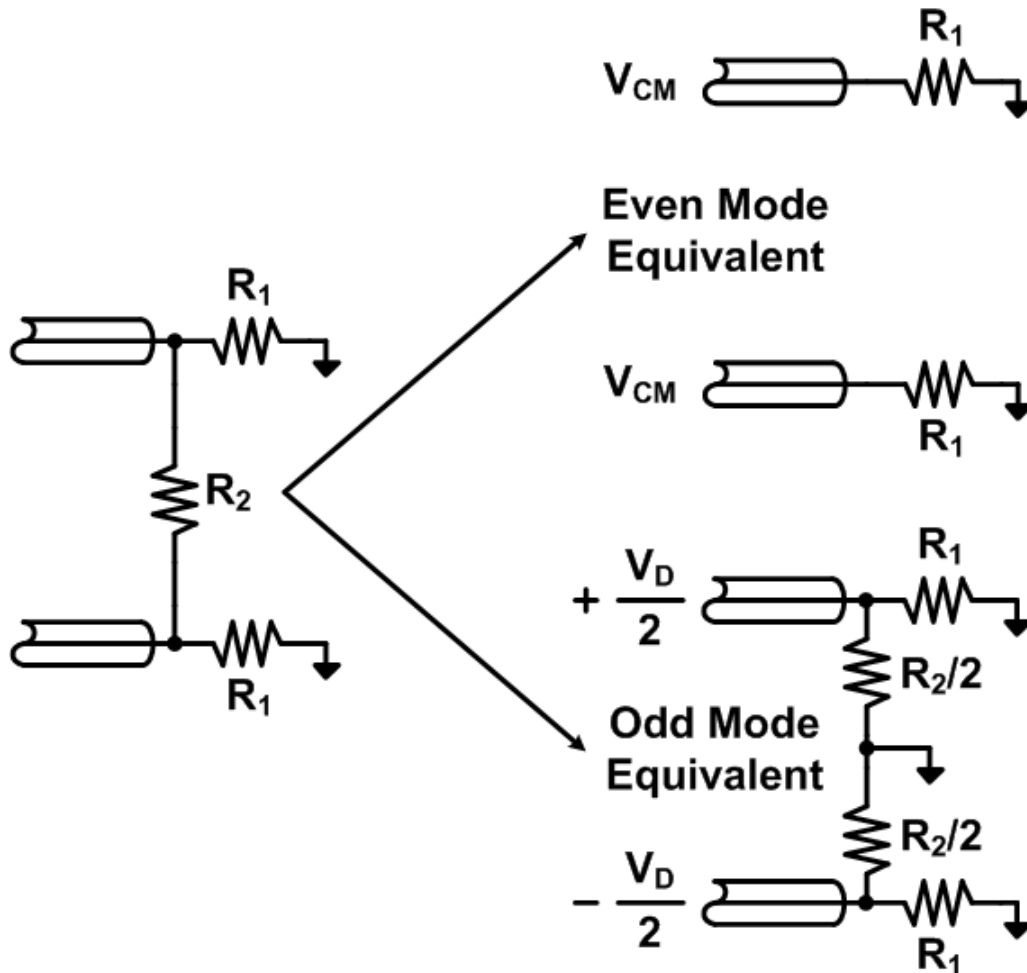


$$Z_{even} = R_1$$

$$Z_{odd} = R_1 \parallel R_2/2 = Z_{even} \parallel R_2/2$$



$$R_2 = 2 \left(\frac{Z_{odd} Z_{even}}{Z_{even} - Z_{odd}} \right)$$

T-Termination


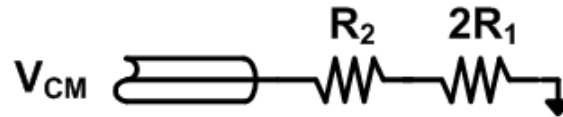


Even Mode
Equivalent

$$Z_{even} = R_2 + 2R_1$$

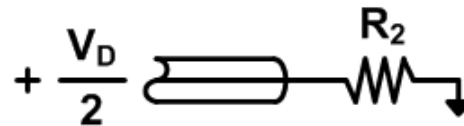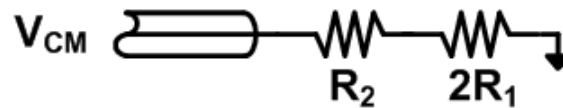

Odd Mode
Equivalent

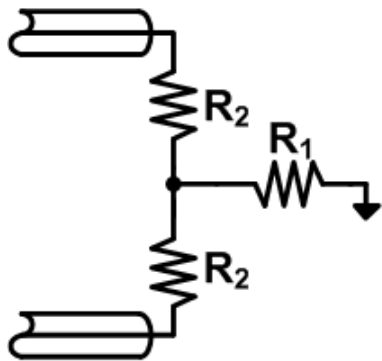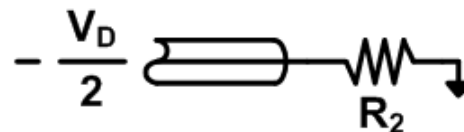

$$Z_{odd} = R_2$$

$$R_1 = \frac{1}{2}(Z_{even} - Z_{odd})$$

Next Time

- Channel modeling
 - Time domain reflectometer (TDR)
 - Network analysis