

ECEN720: High-Speed Links Circuits and Systems Spring 2025

Lecture 3: Time-Domain Reflectometry & S-Parameter Channel Models



Sam Palermo
Analog & Mixed-Signal Center
Texas A&M University

Announcements

- Prelab 1 and Lab Report 1 due Feb 4
- Prelab 2 and Lab Report 2 due Feb 11
- Reference Material Posted on Website
 - TDR theory application note
 - S-parameter notes


Agenda

- Interconnect measurement techniques
 - Time-domain reflectometry (TDR)
 - Network analyzer
- S-parameters
- Cascading S-parameter models
- Full S-parameter channel model
- Transient simulations
 - Impulse response generation
 - Eye diagrams
 - Inter-symbol interference

Lecture References



- Majority of TDR material from Dally Chapter 3.4, 3.6 - 3.7
- Majority of s-parameter material from Hall "Advanced Signal Integrity for High-Speed Digital Designs" Chapter 9

Interconnect Modeling

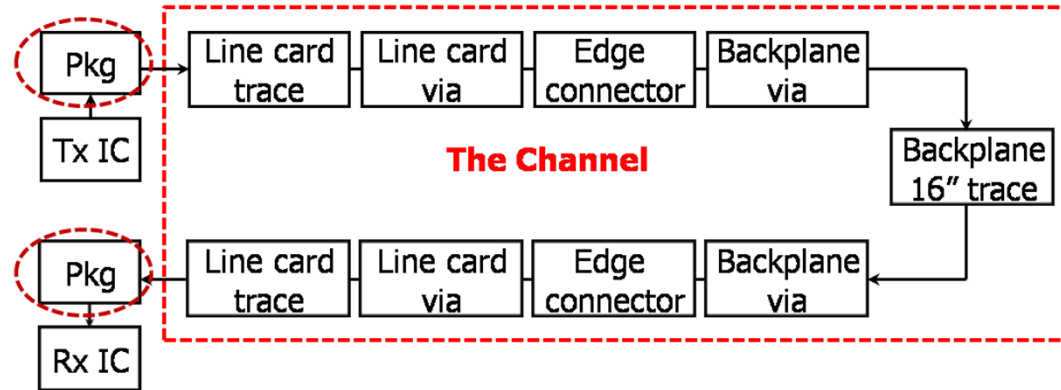


- Why do we need interconnect models?
 - Perform hand calculations and simulations (Spice, Matlab, etc...)
 - Locate performance bottlenecks and make design trade-offs
- Model generation methods
 - Electromagnetic CAD tools
 - Actual system measurements
- Measurement techniques
 - Time-Domain Reflectometer (TDR)
 - Network analyzer (frequency domain)

Time-Domain Reflectometer (TDR)

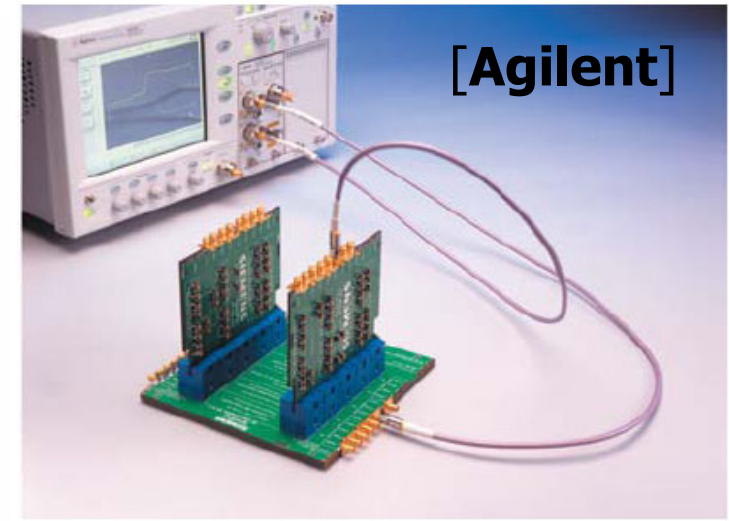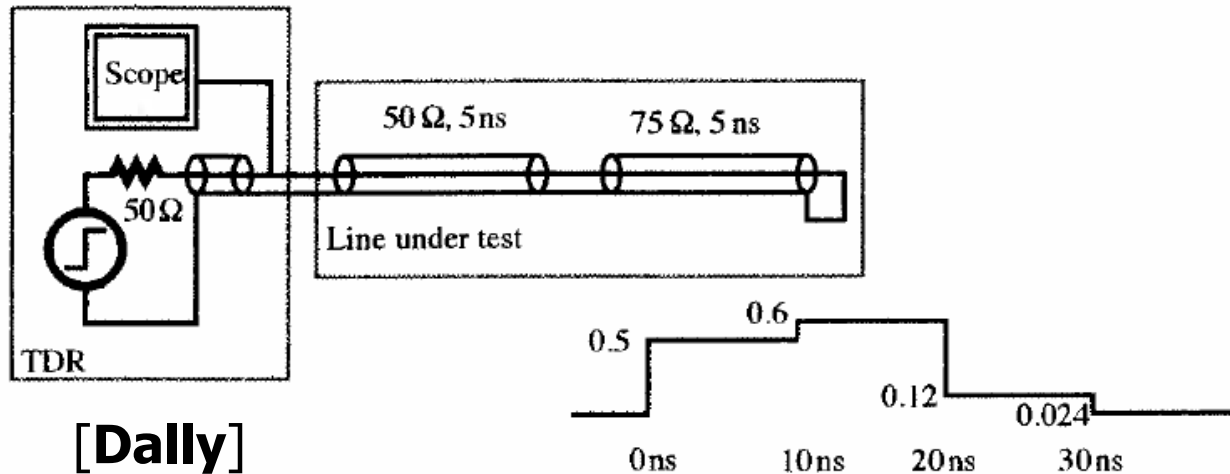

- TDR consists of a fast step generator and a high-speed oscilloscope
- TDR operation
 - Outputs fast voltage step onto channel
 - Observe voltage at source, which includes reflections
 - Voltage magnitude can be converted to impedance
 - Impedance discontinuity location can be determined by delay
- Only input port access to characterize channel

TDR Impedance Calculation

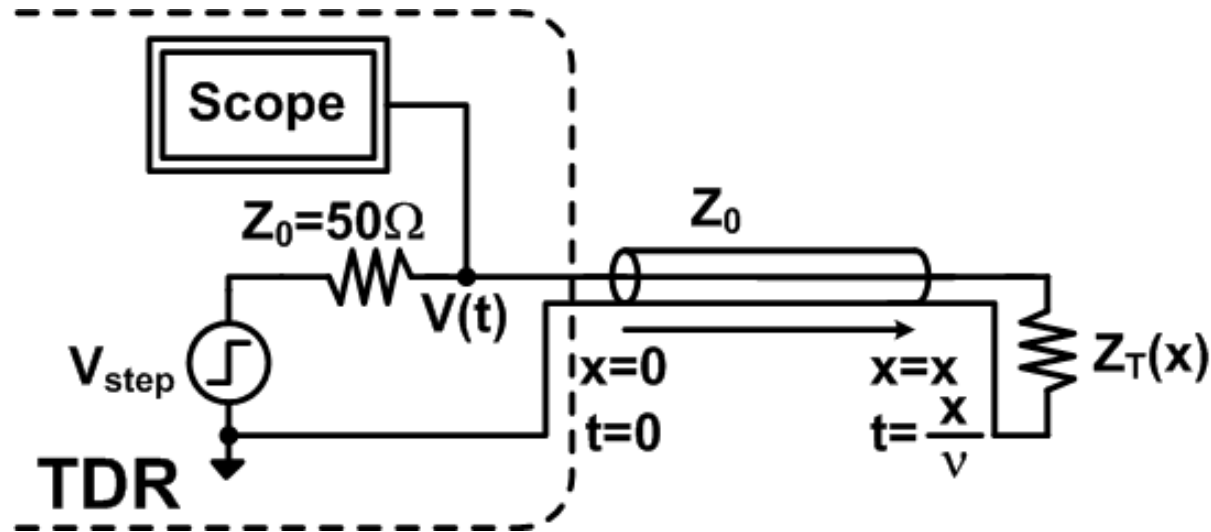

$$k_r(t) = \frac{V_r(t)}{V_i} = \frac{Z_T(t) - Z_0}{Z_T(t) + Z_0}$$



$$Z_T(t) = Z_0 \left(\frac{1 + k_r(t)}{1 - k_r(t)} \right) = Z_0 \left(\frac{V_i + V_r(t)}{V_i - V_r(t)} \right) = Z_0 \left(\frac{V(t)}{2V_i - V(t)} \right)$$

$$\text{If } V_{\text{STEP}} = 1V \Rightarrow V_i = 0.5V$$



$$\boxed{Z_T(t) = Z_0 \left(\frac{V(t)}{1V - V(t)} \right) \quad Z_T(x) = Z_T \left(t = \frac{2x}{v} \right)}$$

TDR Waveforms (Open & Short)

- Open termination

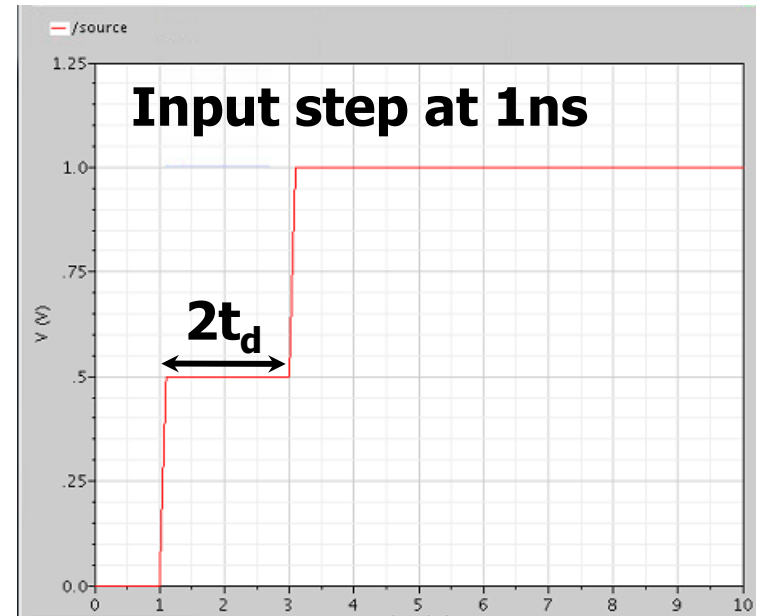
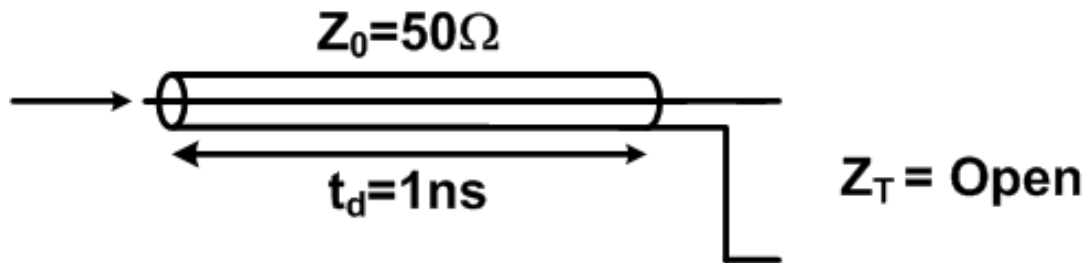


- Short termination

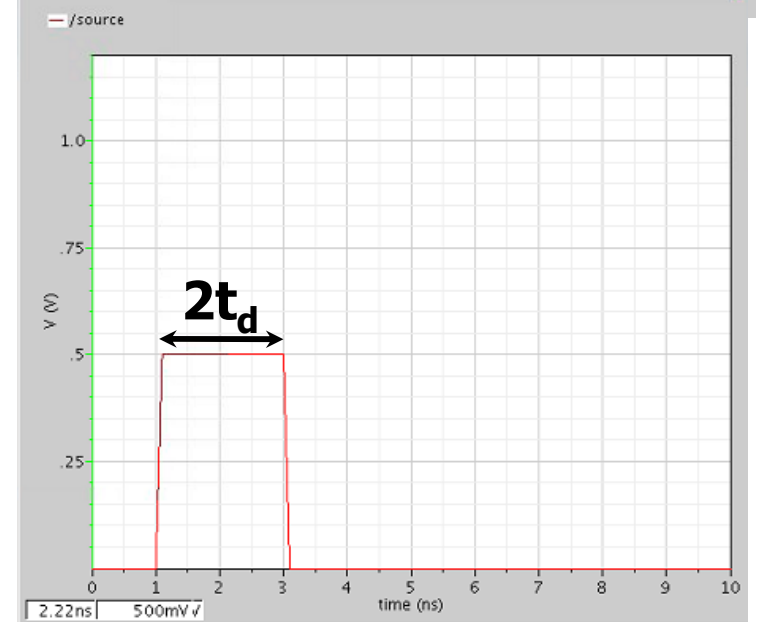
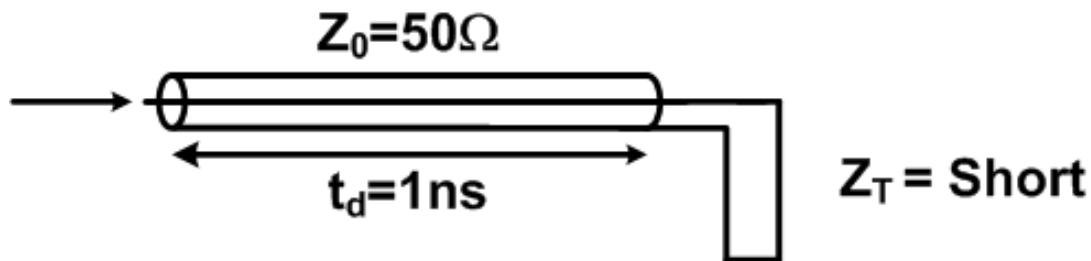


TDR Waveforms (Matched & Mismatched)

- Matched termination

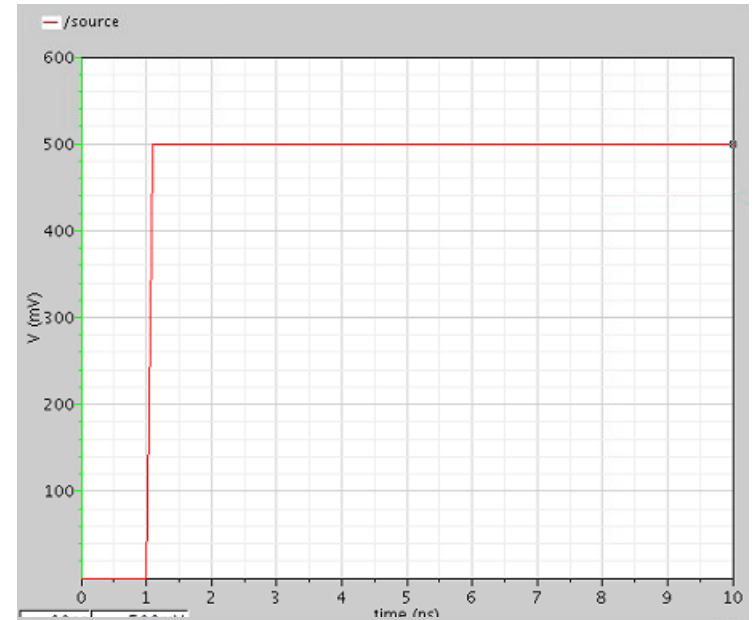
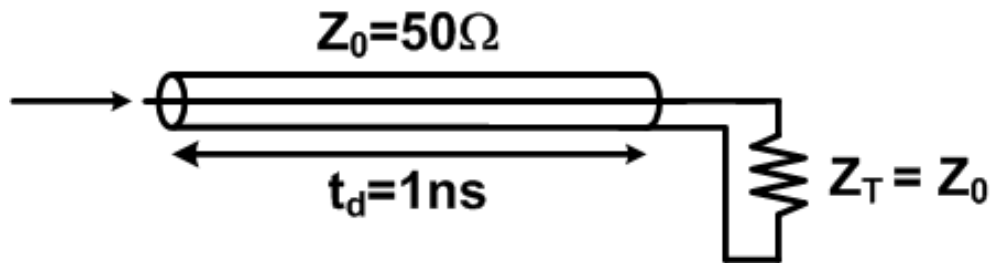


- Mismatched termination

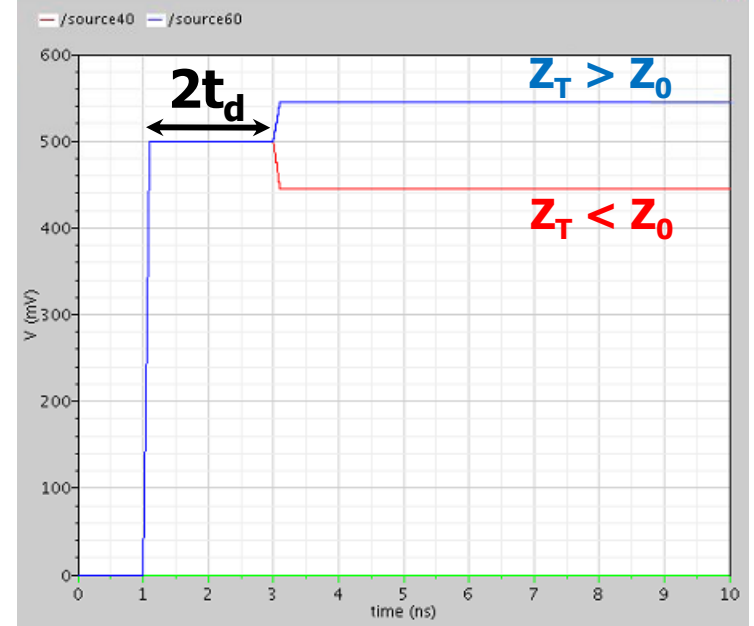
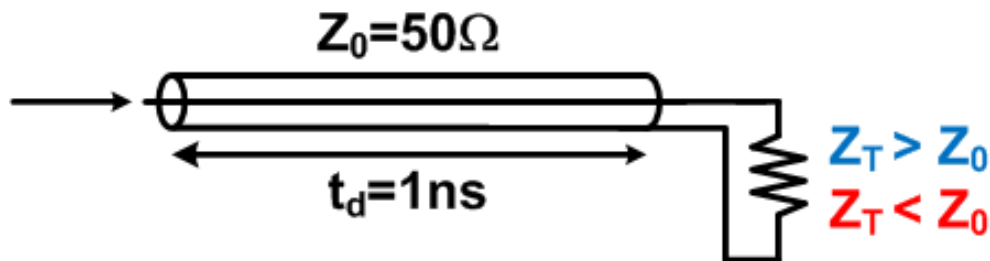


TDR Waveforms (C & L Discontinuity)

- Shunt C discontinuity

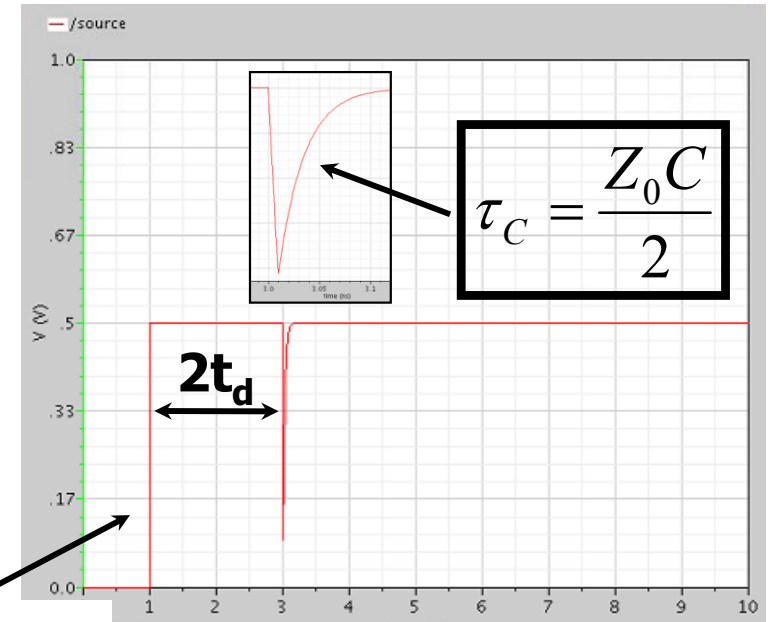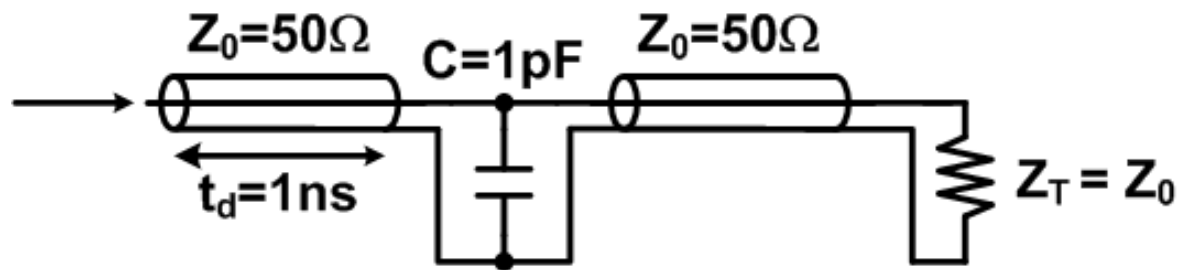

- Series L discontinuity

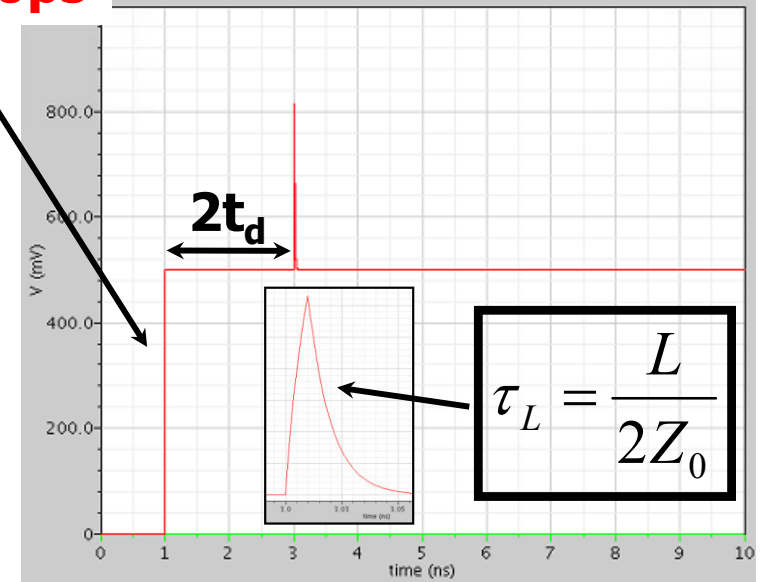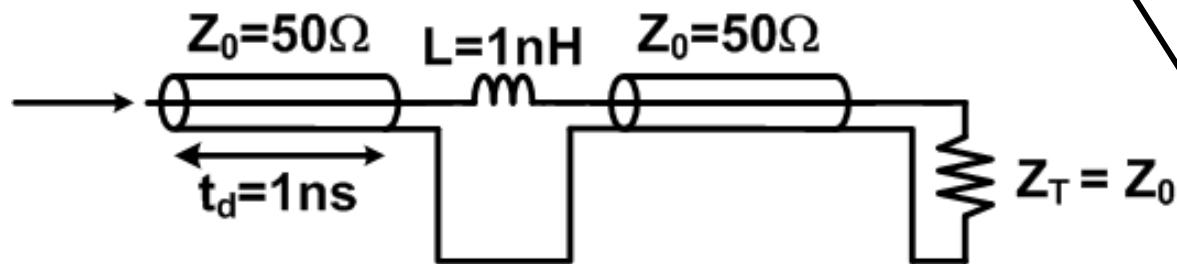

Peak voltage spike magnitude:

$$\frac{\Delta V}{V} = \left(\frac{\tau}{t_r} \right) \left[1 - e^{\left(-\frac{t_r}{\tau} \right)} \right]$$

$t_r = 10\text{ps}$




TDR Rise Time and Resolution

- TDR spatial resolution is set by step risetime


$$\Delta x > t_r v$$

- Step risetime degrades with propagation through channel
 - Dispersion from skin-effect
 - Lump discontinuities low-pass filter the step
- Causes difficulty in estimating L & C values
- Channel filtering can actually compensate for lump discontinuity spikes 😊



TDR Multiple Reflections

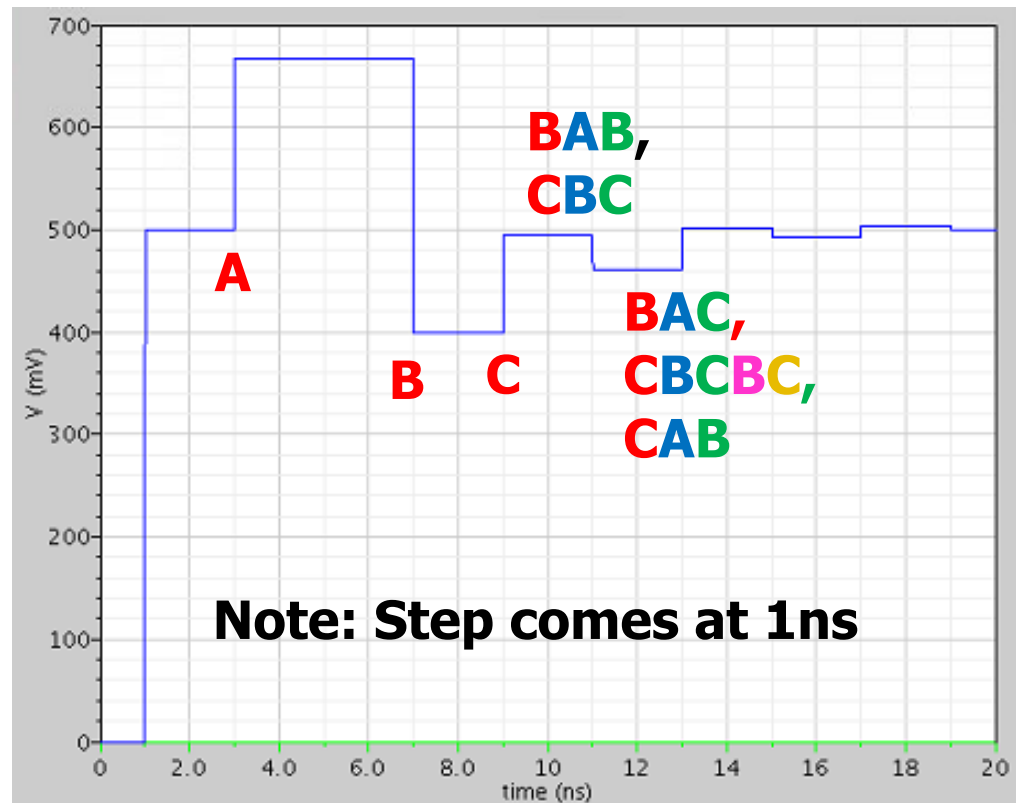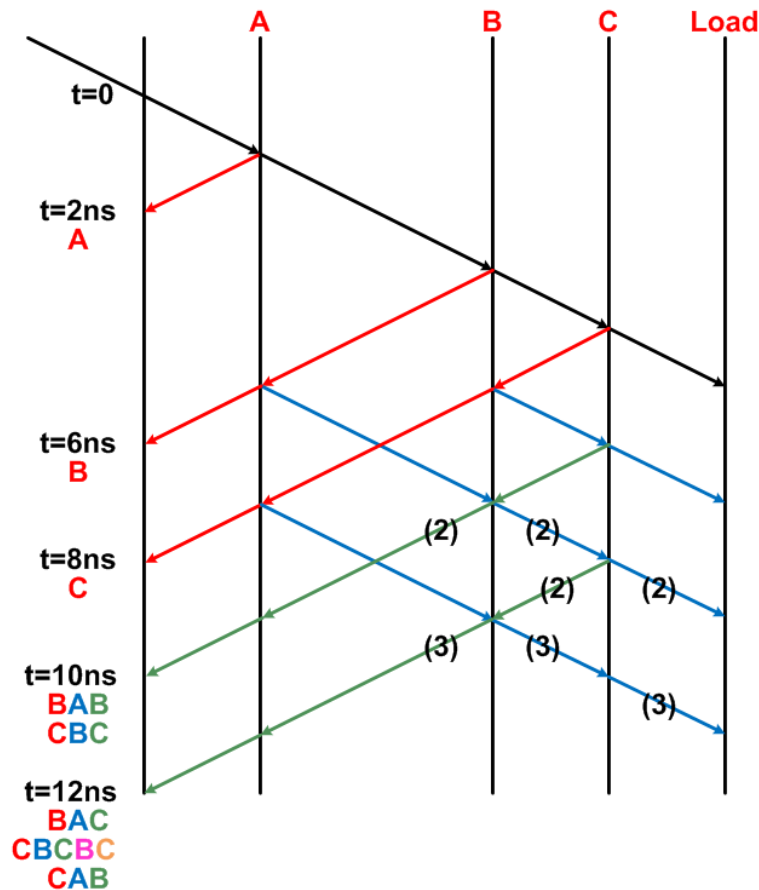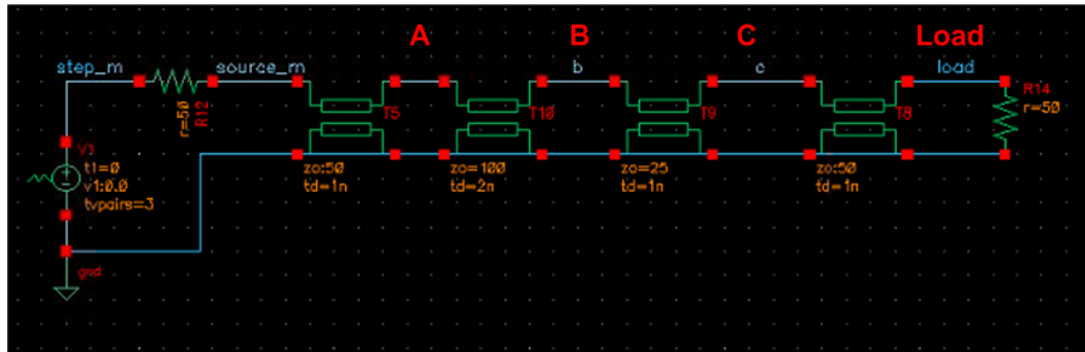


Time-Domain Transmission (TDT)

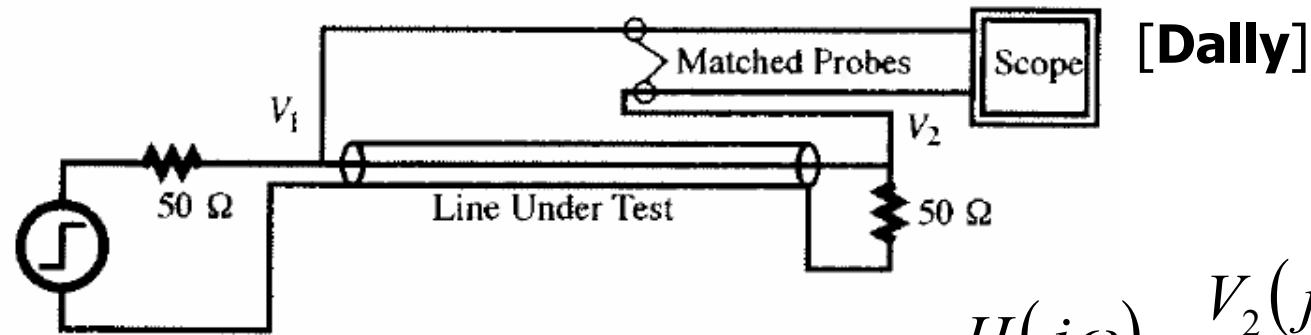

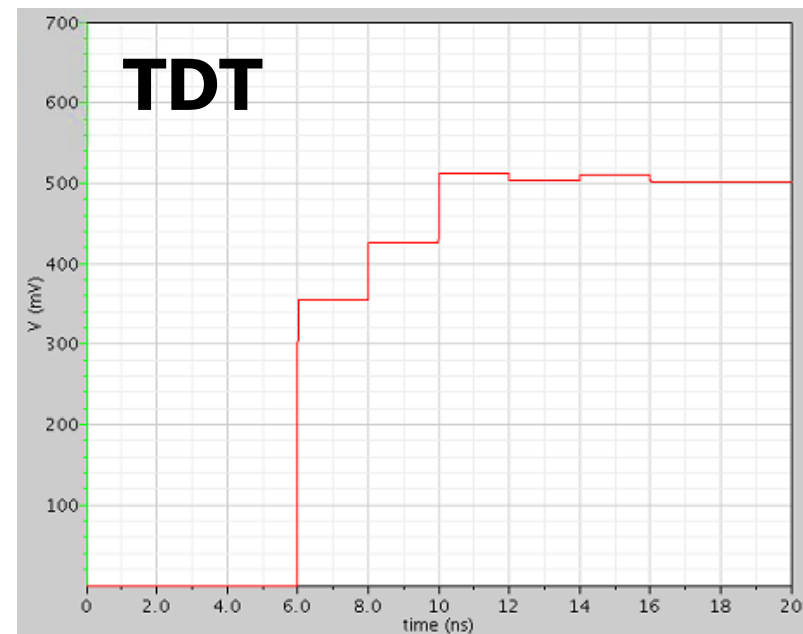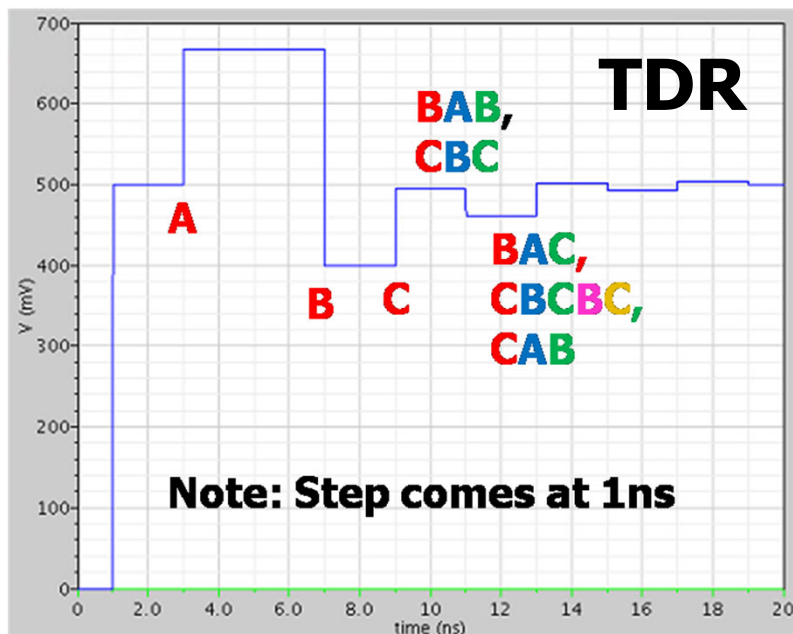- Can measure channel transfer function
 - Hard to isolate impedance discontinuities, as they are superimposed on a single rising edge
- $$H(j\omega) = \frac{V_2(j\omega)}{V_1(j\omega)}$$





Network Analyzer

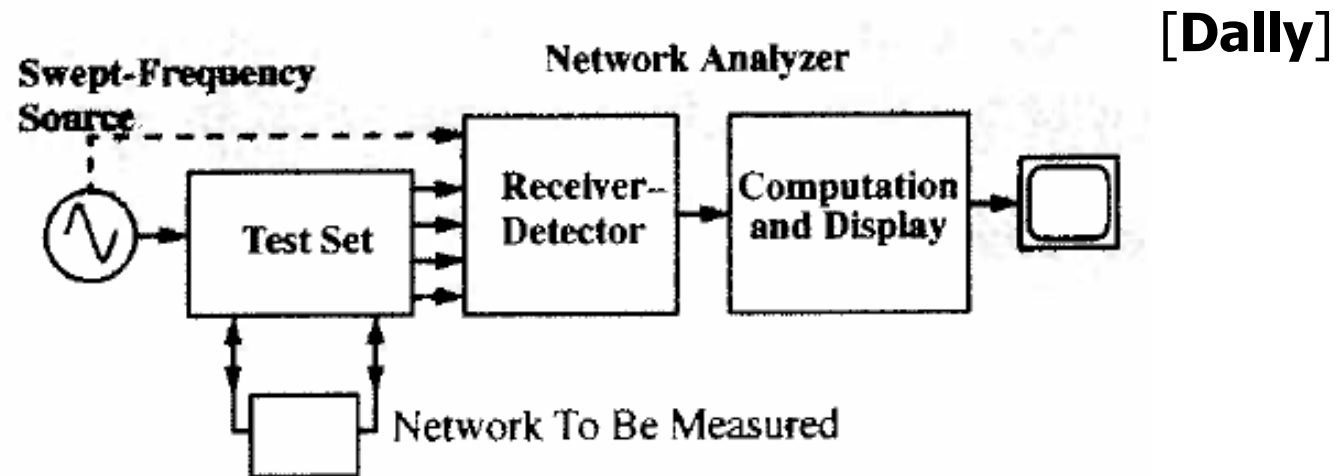


- Stimulates network with swept-frequency source
- Measures network response amplitude and phase
- Can measure transfer function, scattering matrices, impedance, ...
- Test set is configured differently for each kind of measurement to be performed

Directional Coupler

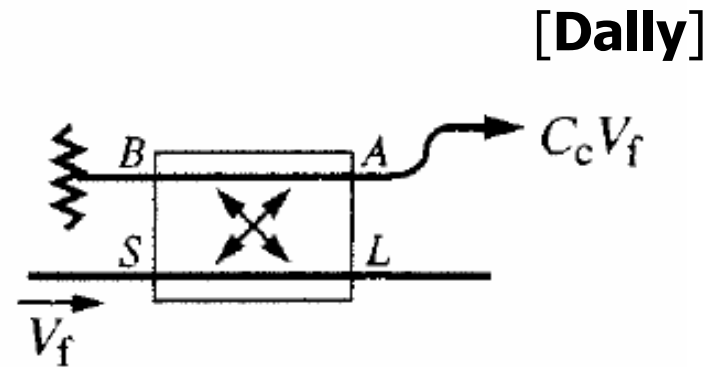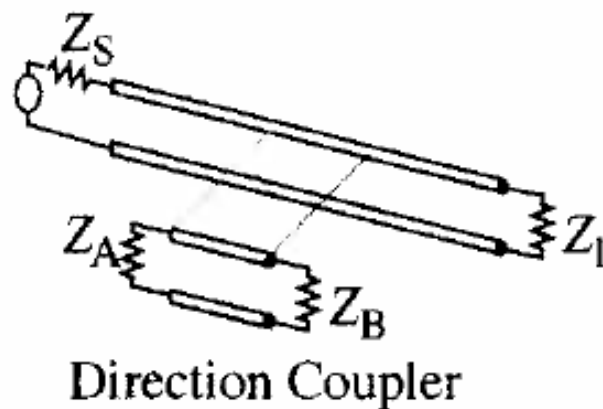


- Test sets in high-frequency network analyzers make use of directional couplers
- Directional couplers are two transmission lines coupled over a short distance
- If the short line is properly terminated, it allows for the voltage across Z_A to be proportional to the forward traveling wave and the voltage across Z_B to be proportional to any reflected wave

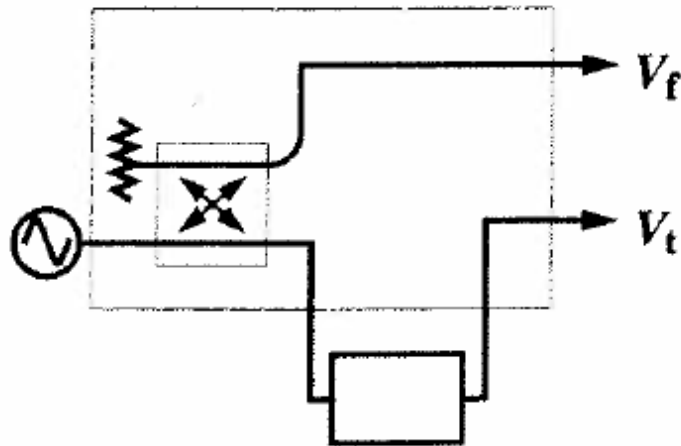Transfer Function & Impedance Measurements



Test Set for Transfer Function

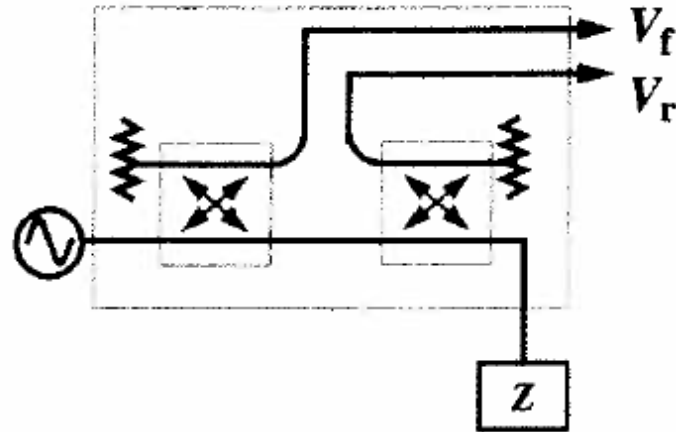


Test Set for Impedance Measurements

[Dally]

- Transfer function measurement
 - The input signal is from a directional coupler which samples the forward traveling wave
 - The network output serves as the output
- Impedance measurement
 - The input signal is from a directional coupler which samples the forward traveling wave
 - The reflected wave from the network is compared with this input to characterize the impedance over frequency

Scattering (S) Parameters

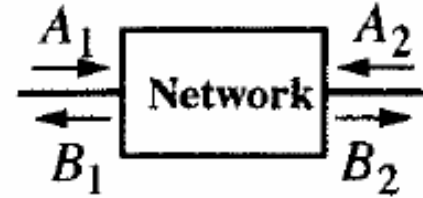
- Why S Parameters?
 - Easy to measure
 - Y, Z parameters need open and short conditions
 - S parameters are obtained with nominal termination
 - S parameters based on incident and reflected wave ratio



The diagram shows a rectangular box labeled "Network". On the left side, there are two horizontal arrows: the top one points right and is labeled A_1 , the bottom one points left and is labeled B_1 . On the right side, there are two horizontal arrows: the top one points left and is labeled A_2 , the bottom one points right and is labeled B_2 .

$$\begin{bmatrix} B_1 \\ B_2 \end{bmatrix} = \underbrace{\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}}_{\text{S-matrix}} \cdot \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} \quad [\text{Dally}]$$

Formal S-Parameter Definitions

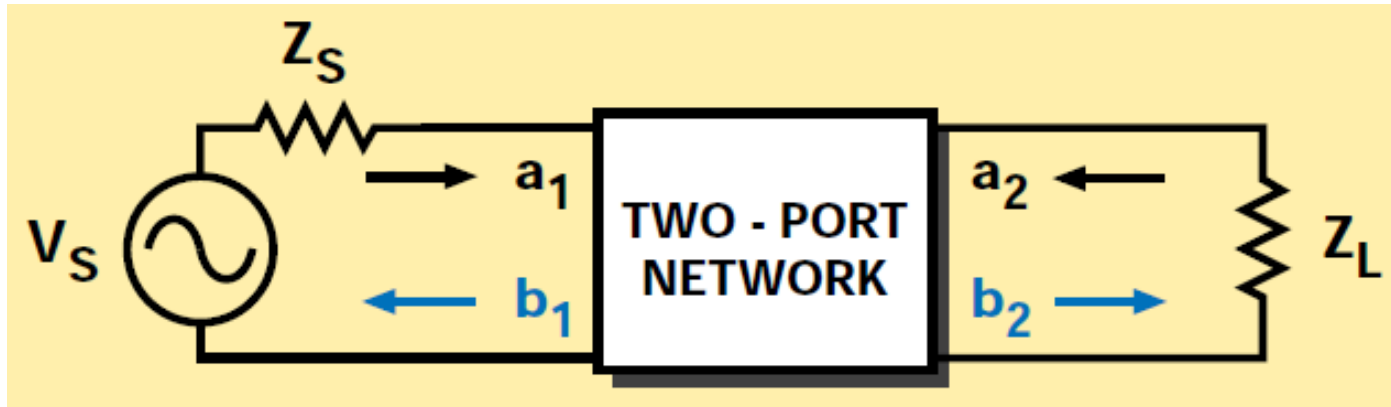

[Agilent]

$$s_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = \text{Input reflection coefficient with the output port terminated by a matched load } (Z_L = Z_0 \text{ sets } a_2=0)$$

$$s_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} = \text{Output reflection coefficient with the input terminated by a matched load } (Z_S = Z_0 \text{ sets } V_S=0)$$


$$s_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} = \text{Forward transmission (insertion) gain with the output port terminated in a matched load.}$$

$$s_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} = \text{Reverse transmission (insertion) gain with the input port terminated in a matched load.}$$

Cascading S-Parameters

- Network analysis allows cascading of independently characterized structures
- However, can't directly cascade s-parameter matrices and multiply
- Must first convert to an ABCD matrix (or T matrix)

ABCD Parameters

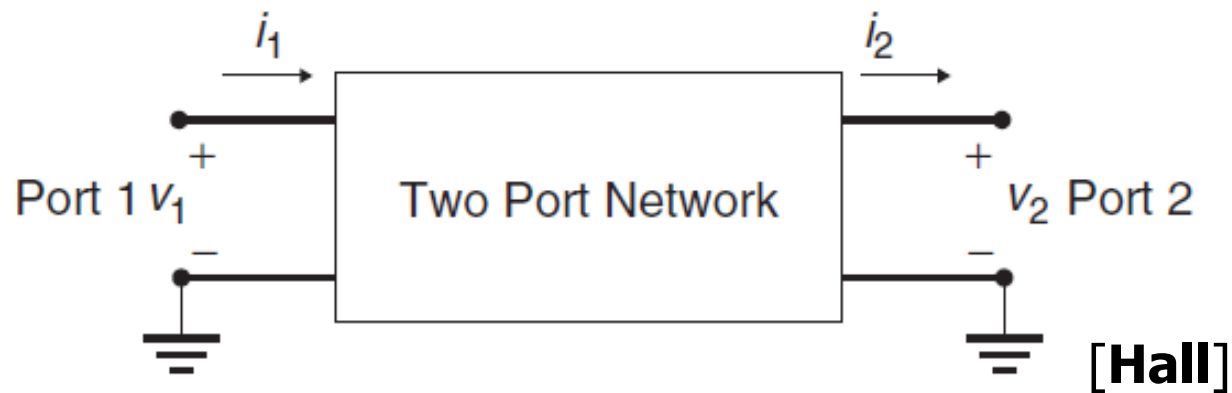

$$A = \left. \frac{v_1}{v_2} \right|_{i_2=0} \quad B = \left. \frac{v_1}{i_2} \right|_{v_2=0} \quad C = \left. \frac{i_1}{v_2} \right|_{i_2=0} \quad D = \left. \frac{i_1}{i_2} \right|_{v_2=0}$$

$$\begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \bullet \begin{bmatrix} v_2 \\ i_2 \end{bmatrix}$$

Converting Between S & ABCD Parameters

TABLE 9-3. Relationships Between Two-Port S and $ABCD$ Parameters^a


$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \quad \begin{bmatrix} \frac{B - Z_n(D - A + CZ_n)}{B + Z_n(D + A + CZ_n)} & \frac{2Z_n(AD - BC)}{B + Z_n(D + A + CZ_n)} \\ \frac{2Z_n}{B + Z_n(D + A + CZ_n)} & \frac{B - Z_n(A - D + CZ_n)}{B + Z_n(D + A + CZ_n)} \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \quad \begin{bmatrix} \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{2S_{21}} & Z_n \frac{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}} \\ \frac{1}{Z_n} \frac{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}} & \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{2S_{21}} \end{bmatrix}$$

^a Z_n is the termination impedance at the ports.


[Hall]

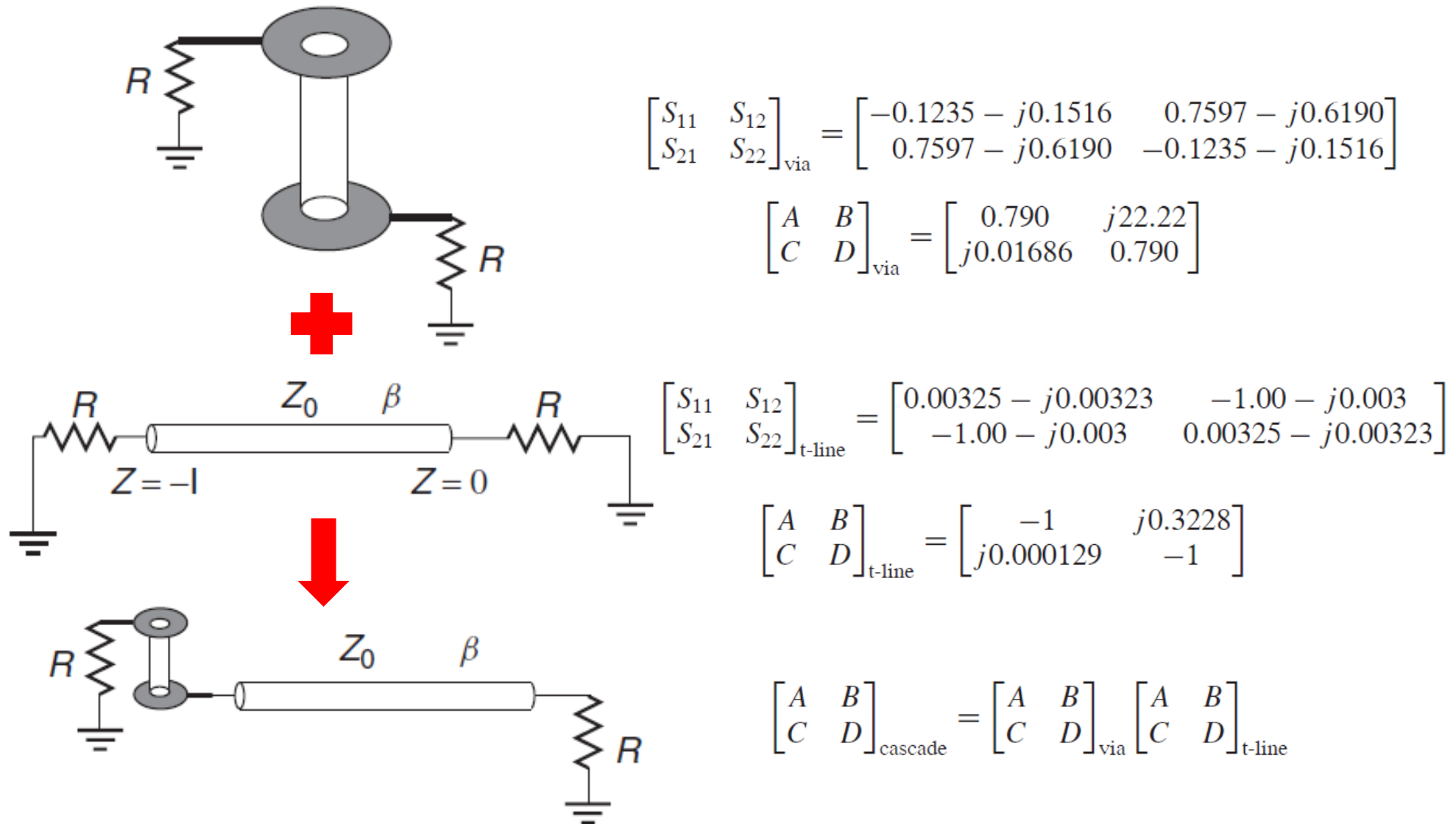Example: Cascaded Via & Transmission Line



- Taken from "Advanced Signal Integrity for High-Speed Digital Designs" by Hall

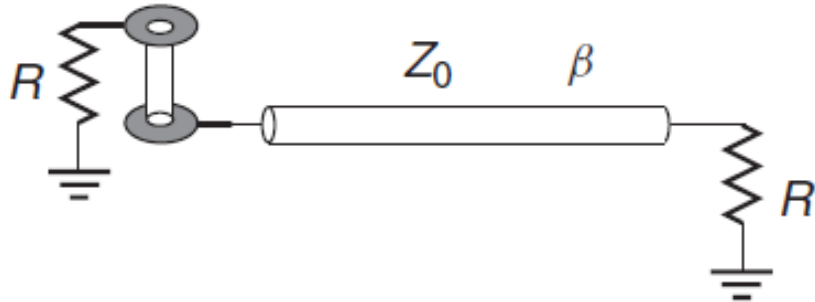Example: Cascaded Via & Transmission Line




$$\begin{aligned}
 \begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{cascade}} &= \begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{via}} \begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\text{t-line}} \\
 &= \begin{bmatrix} 0.790 & j22.22 \\ j0.01686 & 0.790 \end{bmatrix} \cdot \begin{bmatrix} -1 & j0.3228 \\ j0.000129 & -1 \end{bmatrix} \\
 &= \begin{bmatrix} -0.790 & -j21.965 \\ -j0.01686 & -0.795 \end{bmatrix}
 \end{aligned}$$

- Using conversion table:

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix}_{\text{cascade}} = \begin{bmatrix} -0.1259 - j0.1553 & -0.7635 + j0.6186 \\ -0.7645 + j0.6182 & -0.1200 - j0.1565 \end{bmatrix}$$

- Can also use T matrixes to cascade
- Taken from "Advanced Signal Integrity for High-Speed Digital Designs" by Hall

S-Parameter Channel Example

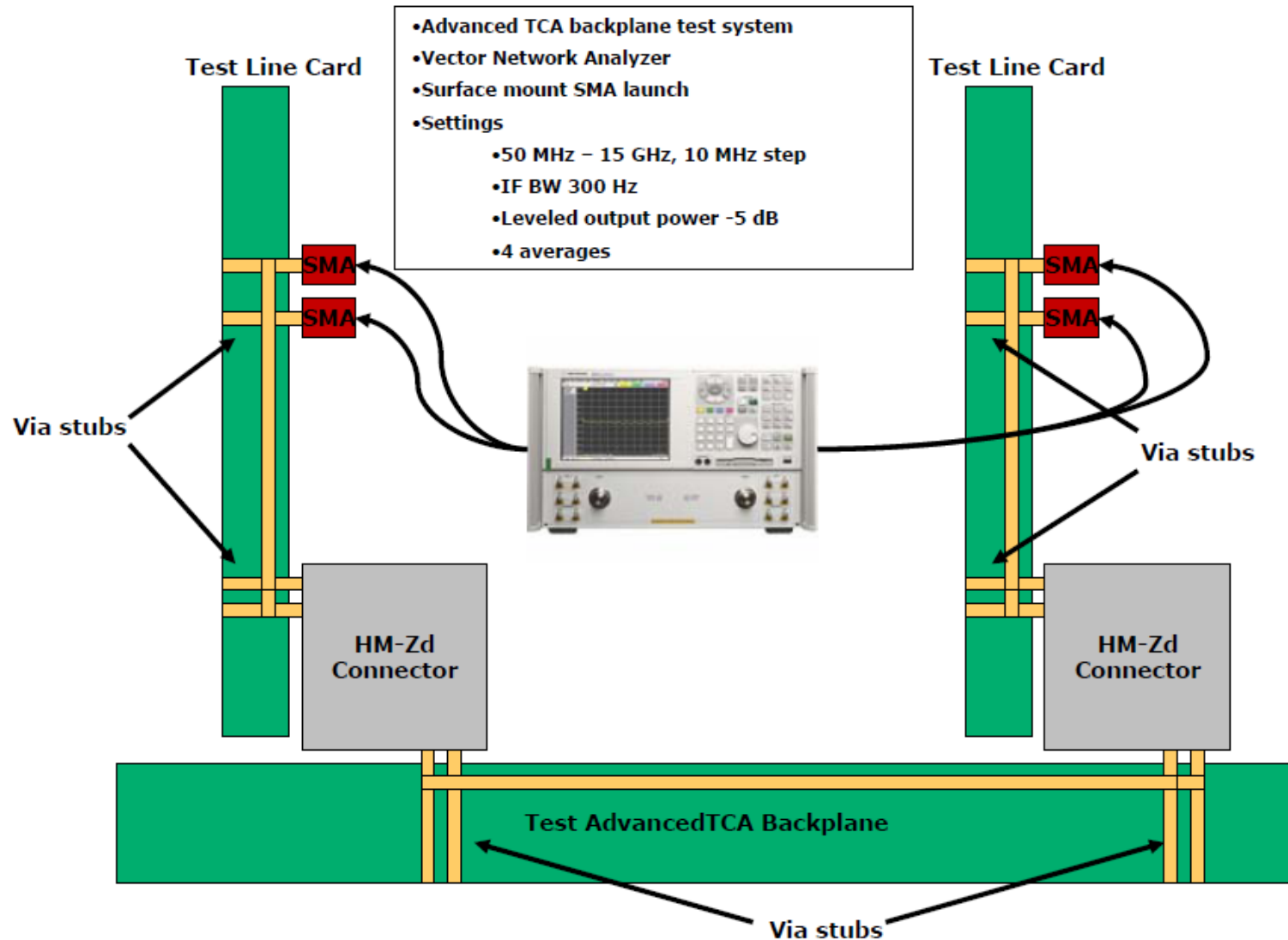

[Peters, IEEE Backplane Ethernet Task Force]


S-Parameter Channel Example (4-port differential)

```
! peters_01_060512v channel thru response
# HZ S RI R 50
!
! FREQ S11 S12 S13 S14
! S21 S22 S23 S24
! S31 S32 S33 S34
! S41 S42 S43 S44
!
! REAL IMAG REAL IMAG REAL IMAG REAL IMAG
5.00000000e+007 6.279266901548e-002 -5.256007502766e-002 -1.995363973143e-001 -9.018006169275e-001 7.405252014369e-002 -1.653914717779e-002 4.694410796534e-004 2.855671737566e-003
-1.993592781969e-001 -9.017752677900e-001 6.847049395661e-002 -3.537762509466e-002 6.592975593456e-004 2.600733690373e-003 7.478976460177e-002 -1.488182269791e-002
7.438370524663e-002 -1.650568516548e-002 6.663957537997e-004 2.723661634513e-003 5.641343731365e-002 -5.693035832892e-002 -2.070369894915e-001 -8.986367167361e-001
3.380698172980e-004 2.715033111885e-003 7.497765935351e-002 -1.488546535615e-002 -2.063544808970e-001 -9.002700655374e-001 6.856095801756e-002 -3.019606086420e-002
6.00000000e+007 4.829977376755e-002 -6.288238652440e-002 -4.923832497425e-001 -7.721510464035e-001 6.298956599590e-002 -3.938489680891e-002 1.125377257145e-003 1.921732299021e-003
-4.925547500023e-001 -7.726263821707e-001 6.163450406360e-002 -4.486265928179e-002 1.299644022342e-003 1.492436402394e-003 6.462146347807e-002 -3.736630924981e-002
6.308085276969e-002 -3.947655302643e-002 1.386741613180e-003 1.653454474207e-003 4.393874455850e-002 -6.448913049207e-002 -4.992743919180e-001 -7.660808533046e-001
1.280875740087e-003 1.936760526874e-003 6.482369657086e-002 -3.743006383763e-002 -4.995203164654e-001 -7.674804458241e-001 6.284893613667e-002 -4.132139739274e-002
```

Data from 50MHz to 15GHz in
10MHz steps



```
1.49900000e+010 -1.884123481138e-001 3.522933794755e-001 9.493645552321e-004 2.735890006358e-004 2.939002692375e-002 -8.676465491258e-003 -2.207496924854e-004 1.236065259912e-004
9.463443060684e-004 3.105615146344e-004 -1.742347383703e-001 4.813685271232e-002 -6.152705437030e-004 1.614752661571e-003 6.774475978813e-002 9.617239585695e-003
2.953403838205e-002 -8.707827389646e-003 -6.226849675423e-004 1.637610280621e-003 -1.595766021694e-001 3.757605914955e-001 -1.809501624148e-004 -7.061855554470e-004
-2.613575703191e-004 1.368108929760e-004 6.788329666403e-002 9.551687705500e-003 -2.146293806886e-004 -7.363580847286e-004 -1.199804891859e-001 7.697336952293e-002
1.50000000e+010 -1.883176013184e-001 3.545614742110e-001 9.524680768441e-004 -5.404222971799e-005 2.935126165241e-002 -1.235086132268e-002 -1.616280086909e-004 2.347368458649e-004
1.039250921080e-003 -6.032017103742e-005 -1.649137634331e-001 4.966164587830e-002 -6.748937194262e-005 1.689652681670e-003 6.725041473699e-002 1.961009613152e-003
2.959693594806e-002 -1.251203706381e-002 -2.927441863297e-005 1.747754847916e-003 -1.531702433245e-001 3.773014940454e-001 -3.769459376261e-004 -5.671620228005e-004
-2.089293612250e-004 2.303682313561e-004 6.740524959192e-002 1.672663579641e-003 -4.385850073691e-004 -5.810569604703e-004 -1.121319455376e-001 7.458173831411e-002
```

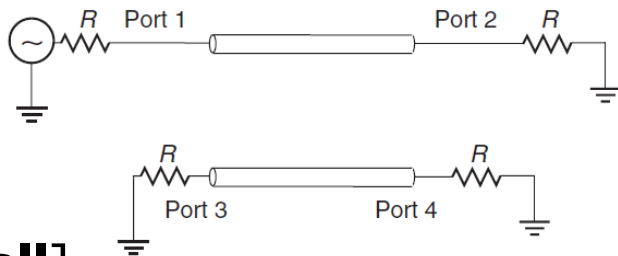


[Hall]

$$\begin{bmatrix} b_1 \\ b_2 \\ b_3 \\ b_4 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \\ a_4 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix} \begin{bmatrix} v \\ 0 \\ -v \\ 0 \end{bmatrix}$$

$$S_{dd11} = \left. \frac{b_{d1}}{a_{d1}} \right|_{a_2=a_4=0} = \frac{1}{2} (S_{11} + S_{33} - S_{13} - S_{31})$$


$$S_{dd21} = \left. \frac{b_{d2}}{a_{d1}} \right|_{a_2=a_4=0} = \frac{1}{2} (S_{21} + S_{43} - S_{23} - S_{41})$$

S-Parameter Channel Example

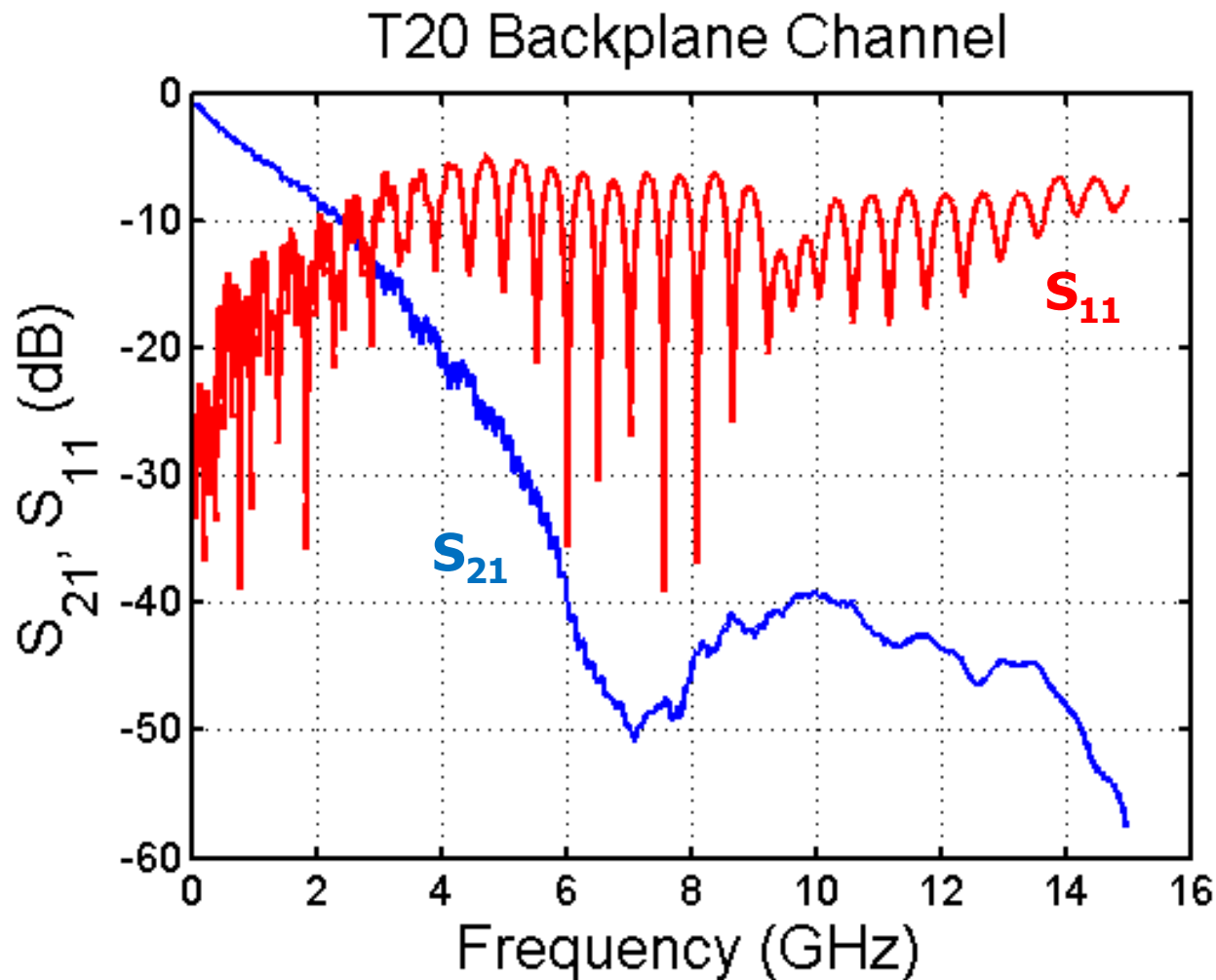

Impulse Response

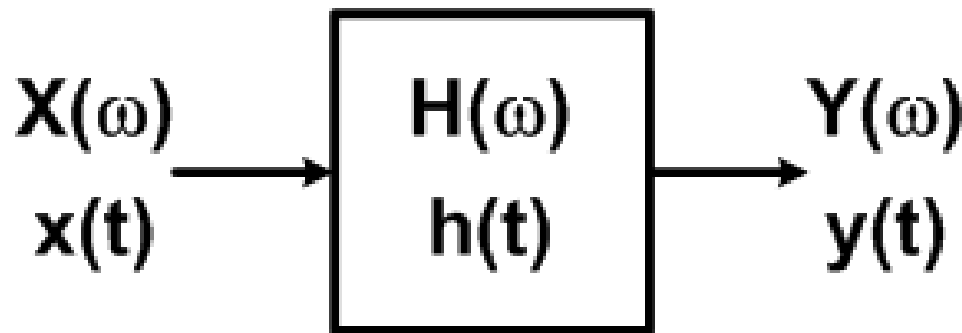- Channel impulse responses are used in
 - Time domain simulations
 - Link analysis tools



$$Y(\omega) = H(\omega)X(\omega)$$

$$y(t) = h(t) * x(t) = \int_{-\infty}^{\infty} h(t - \tau)x(\tau) d\tau$$


$$h(t) = F^{-1}\{H(\omega)\}$$

Generating an Impulse Response from S-Parameters

- Perform the inverse Fourier transform on the s-parameter of interest
- Step 1: For ifft, produce negative frequency values and append to s-parameter data in the following manner

$$S(-f) = S(f)^*$$

$$h(t) = F^{-1} \{S(\omega)\}$$

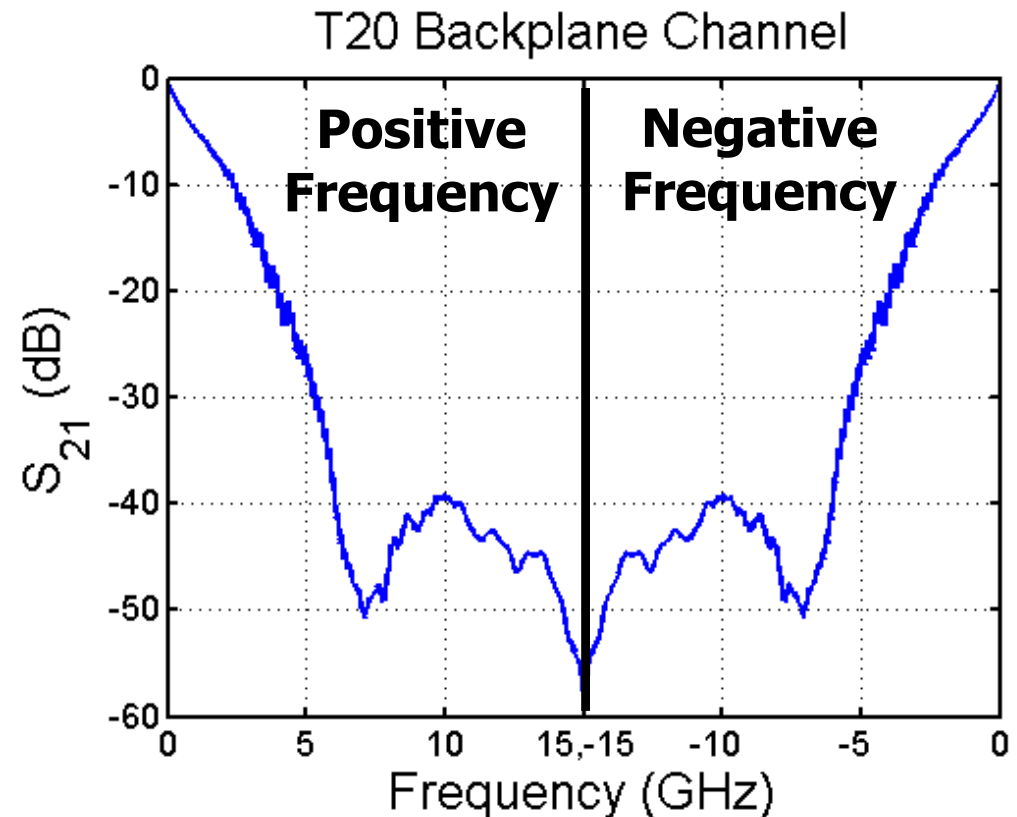


Increasing Impulse Response Resolution

- Could perform ifft now, but will get an impulse response with time resolution of

$$\frac{1}{2f_{\max}} = \frac{1}{2(15\text{GHz})} = 33.3\text{ps}$$



- To improve impulse response resolution expand frequency axis and “zero pad”

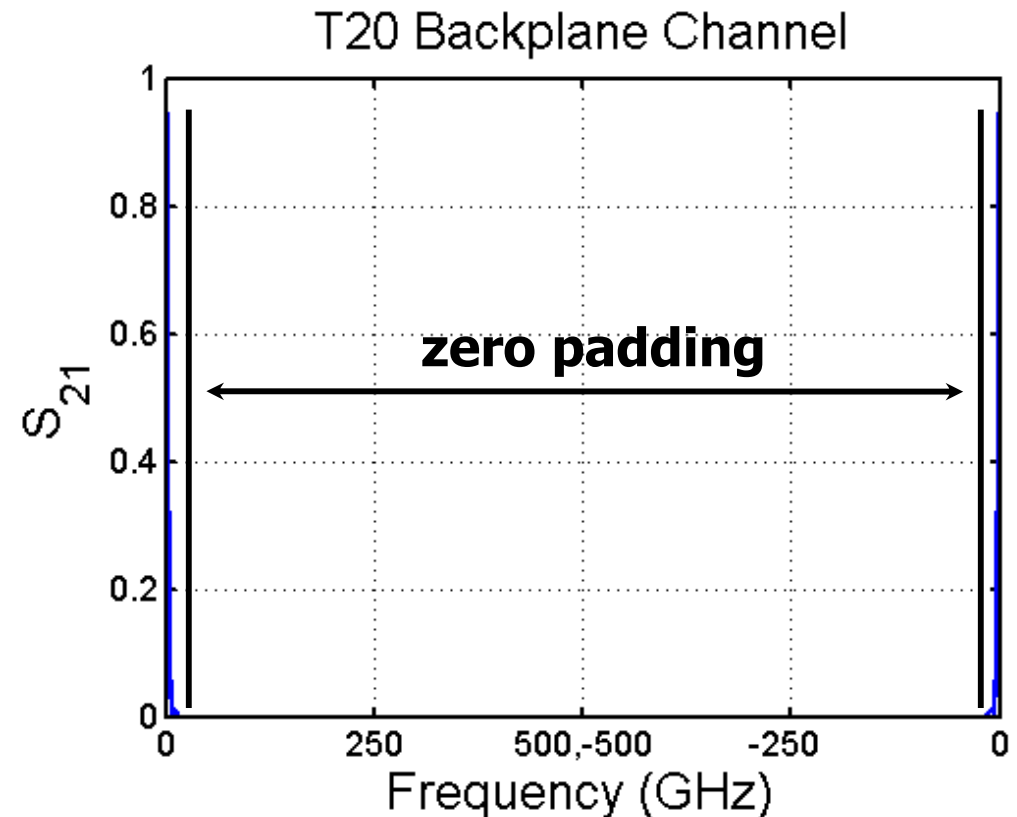For 1ps resolution:
zero pad to +/-500GHz




Channel Impulse Response

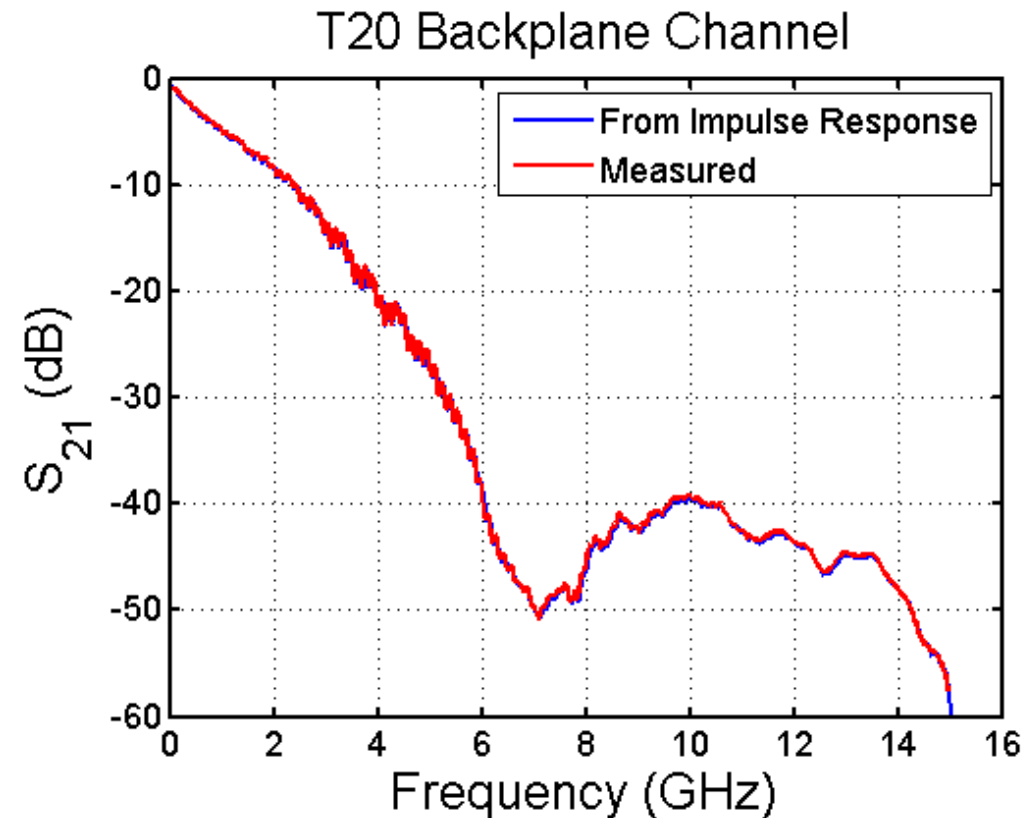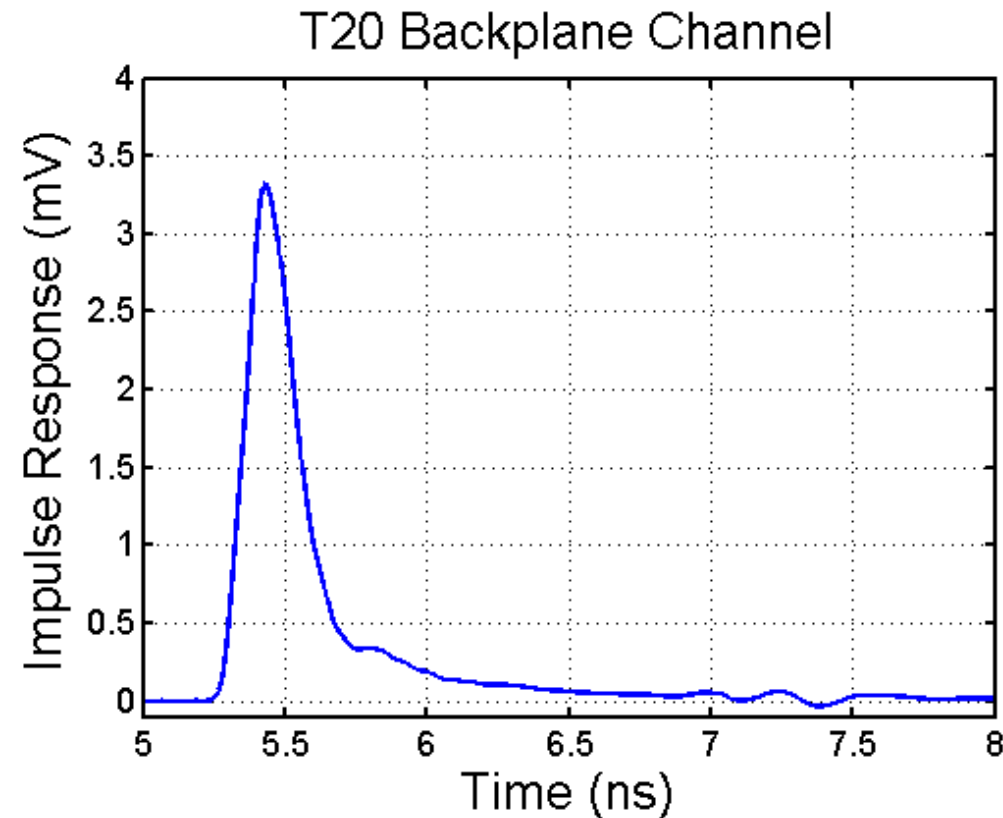- Now perform ifft to produce impulse response
- Can sanity check by doing an fft on impulse response and comparing to measured data




Impulse Response of Different Channels


Channel Responses

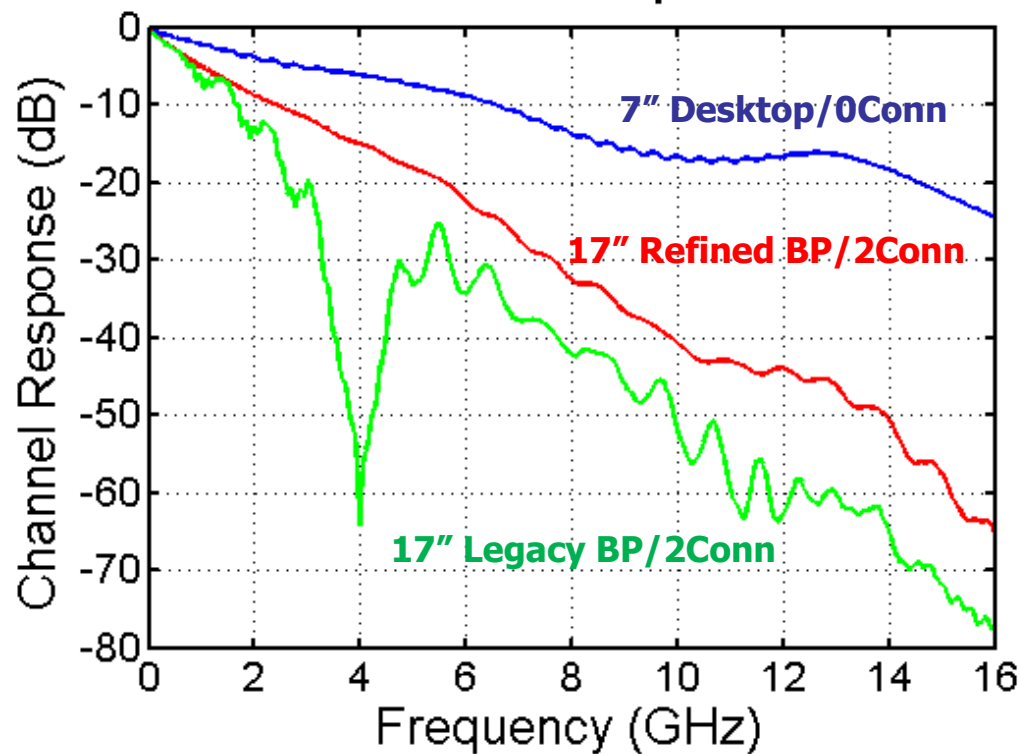




Channel Impulse Responses

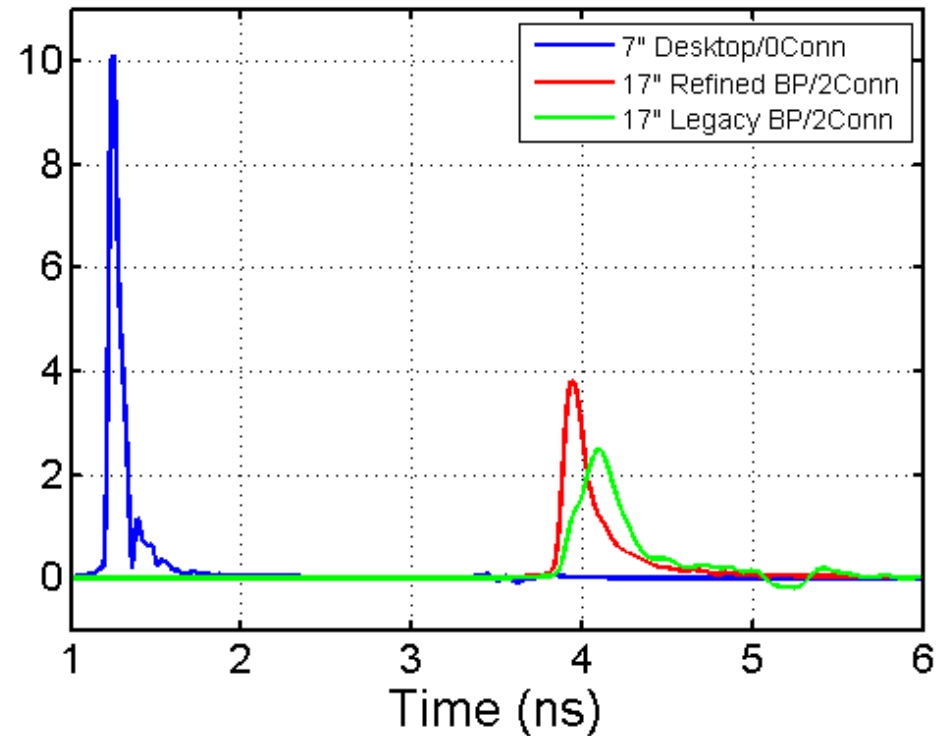





Channel Transient Response

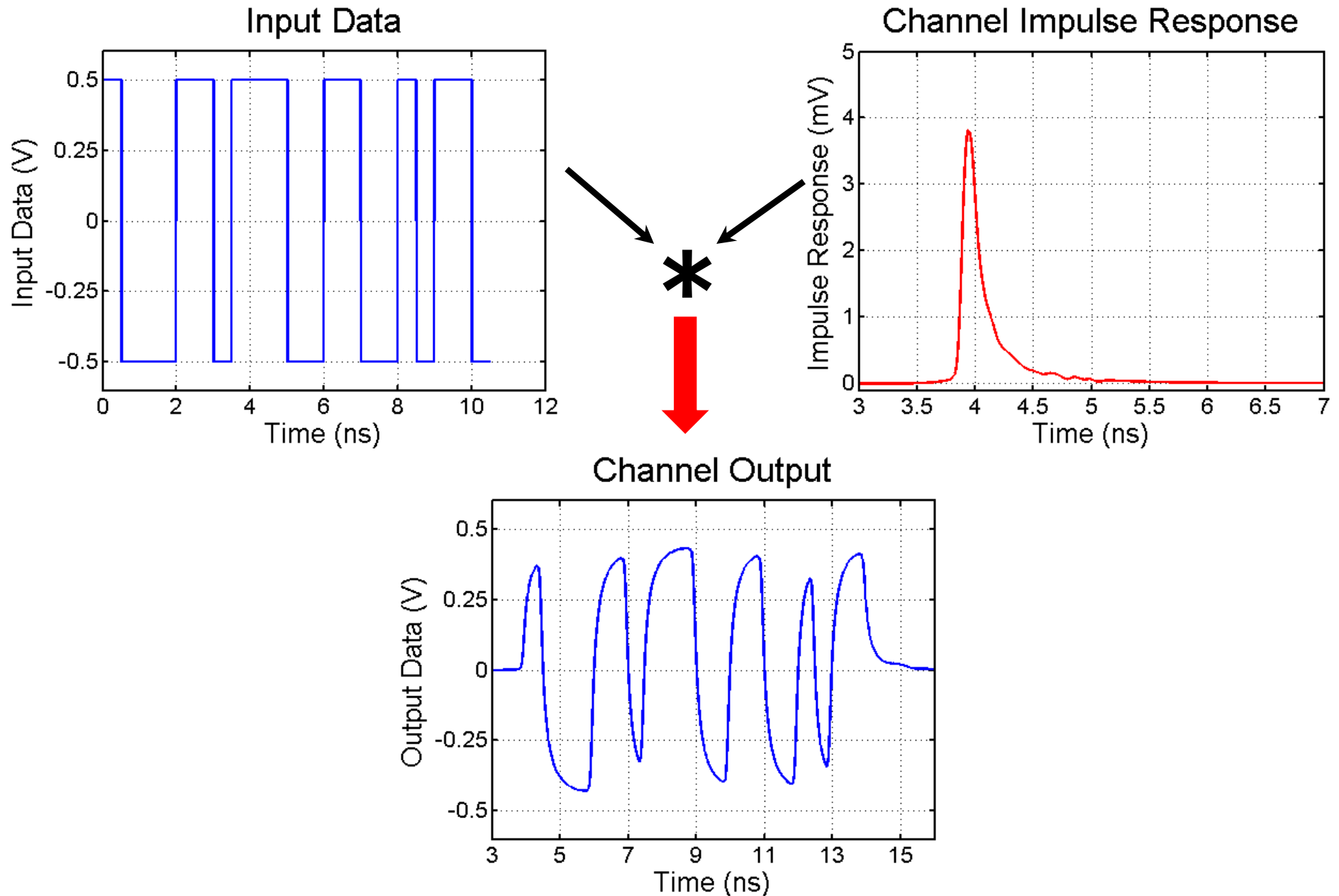





Eye Diagrams

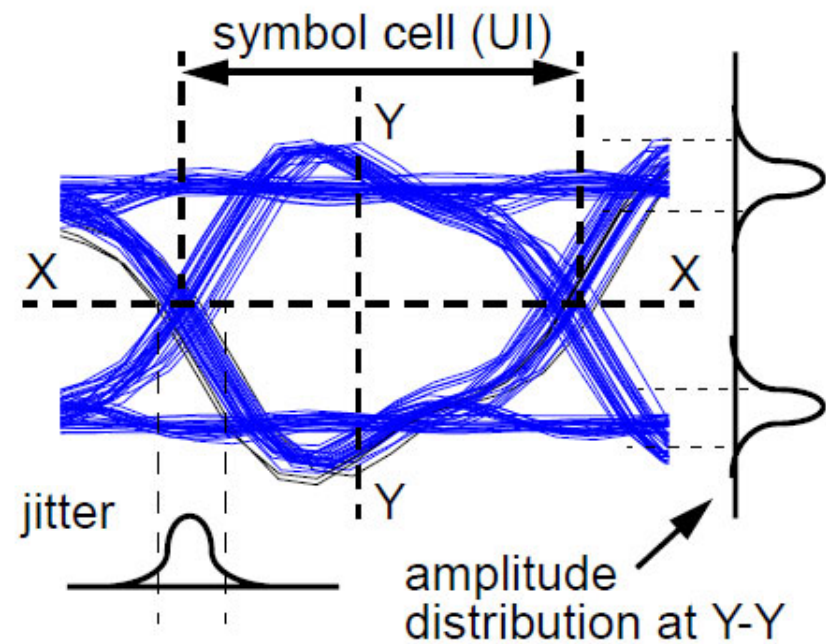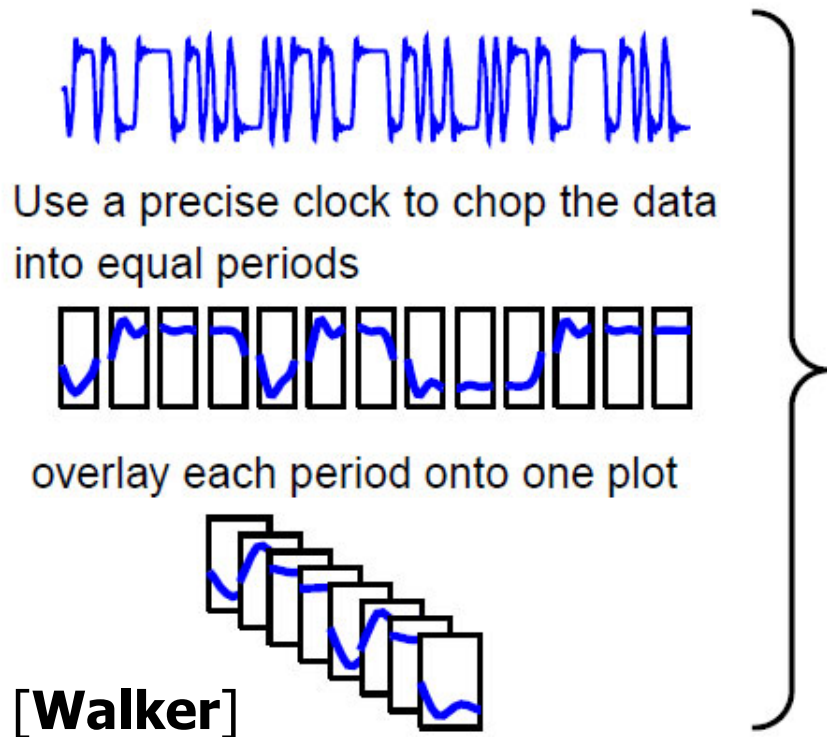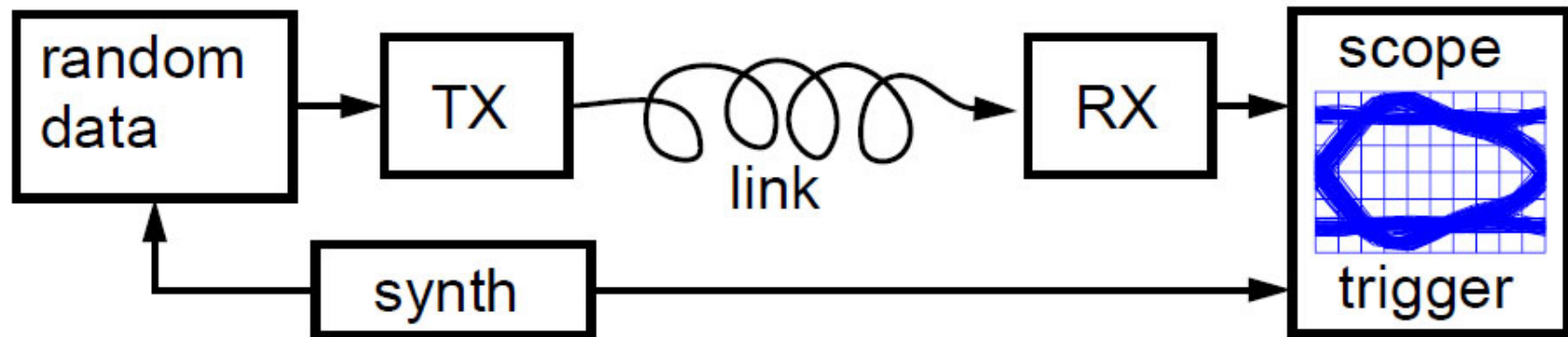

Eye Diagrams vs Data Rate

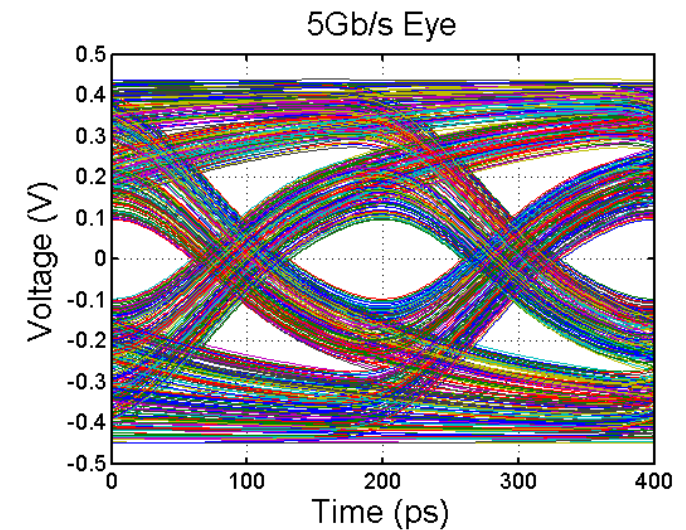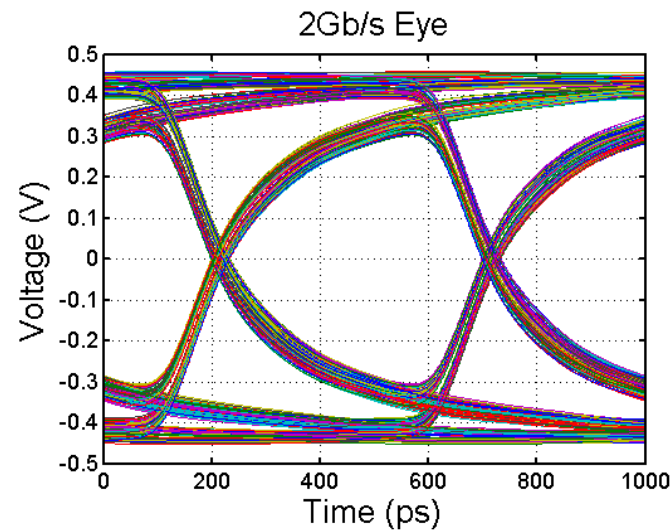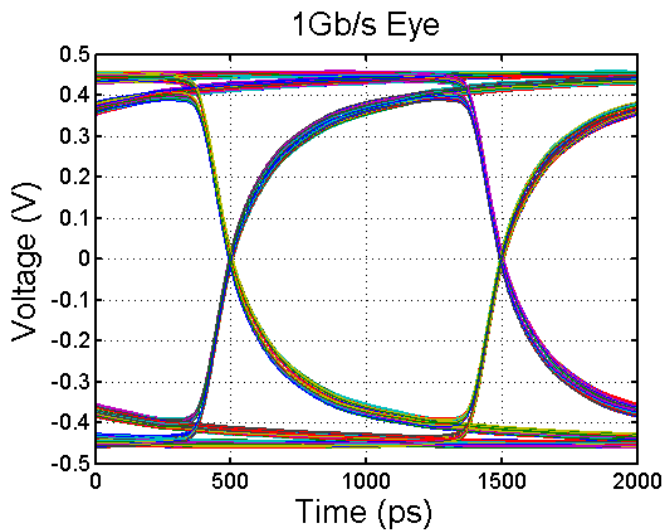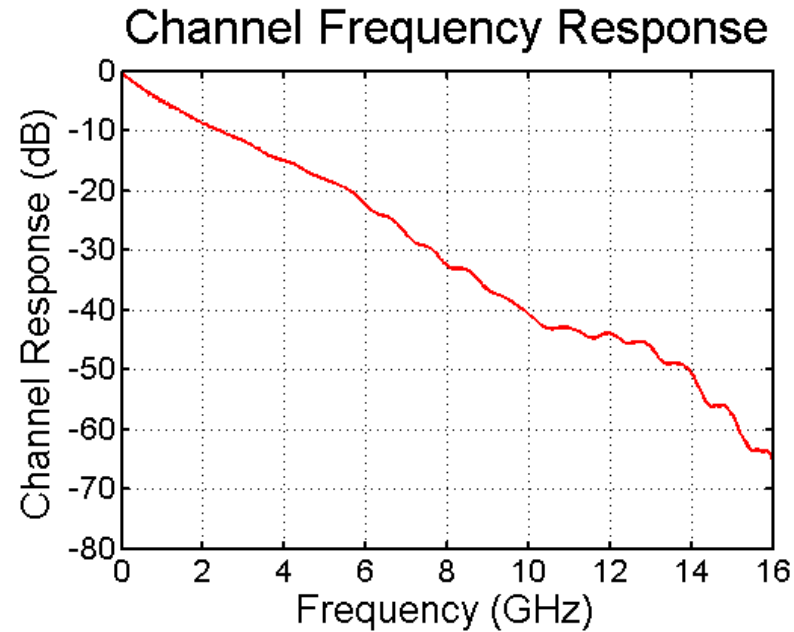


Eye Diagrams vs Channel

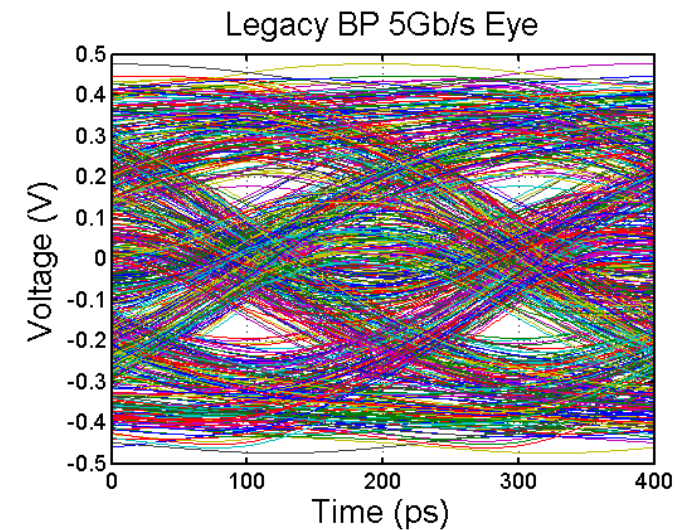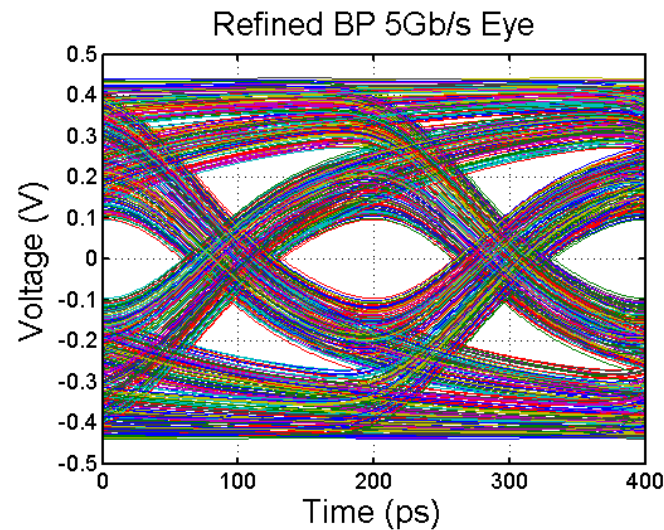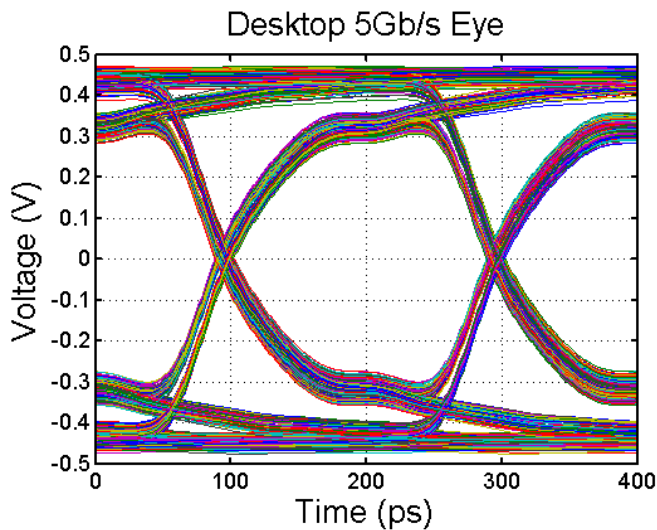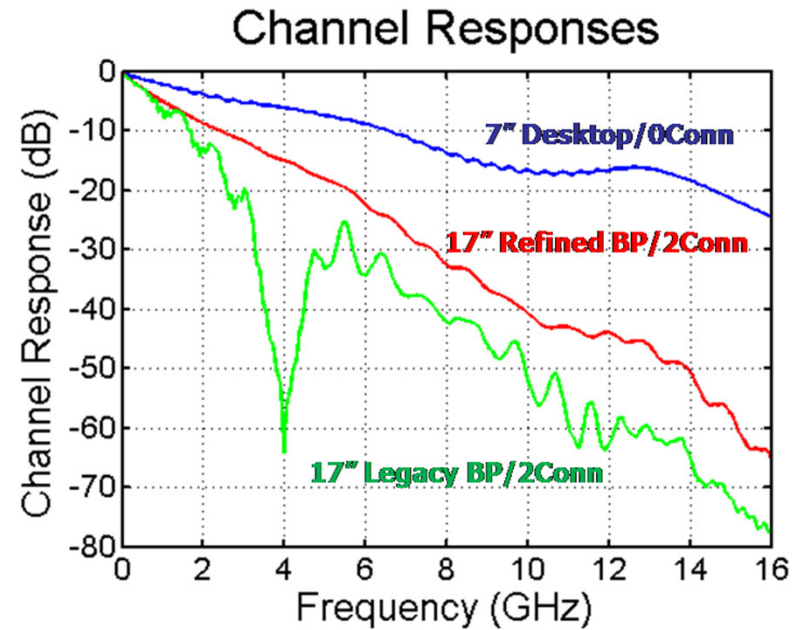


Inter-Symbol Interference (ISI)

- Previous bits residual state can distort the current bit, resulting in inter-symbol interference (ISI)
- ISI is caused by
 - Reflections, Channel resonances, Channel loss (dispersion)

Legacy BP 5Gb/s Pulse Response

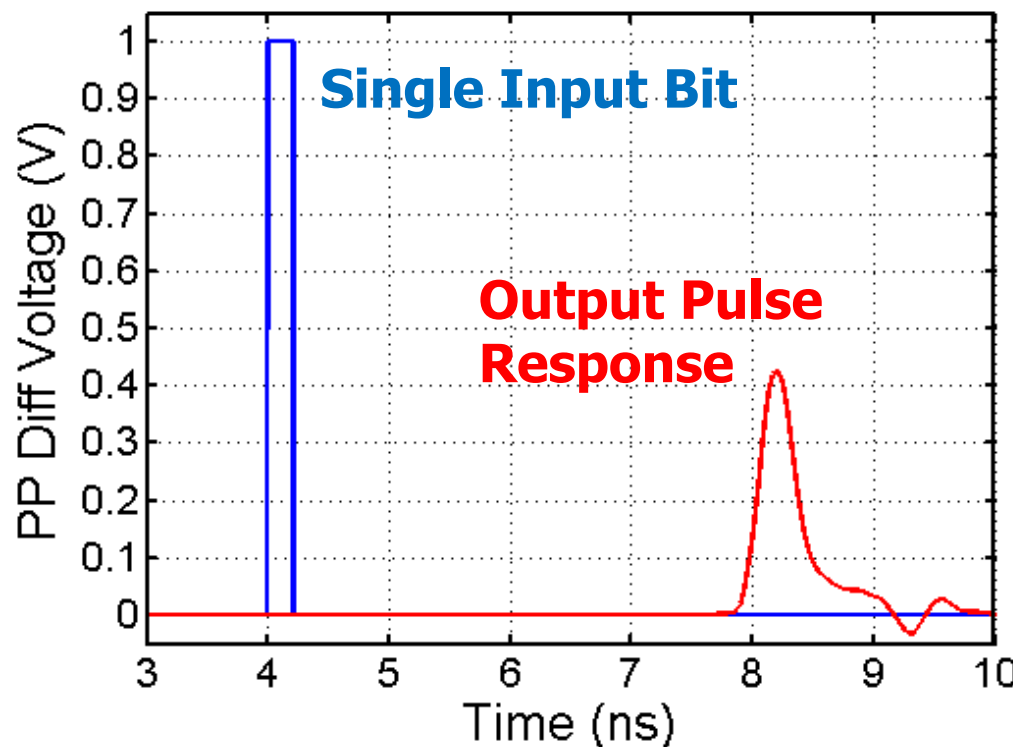


Legacy BP 5Gb/s Pulse Response

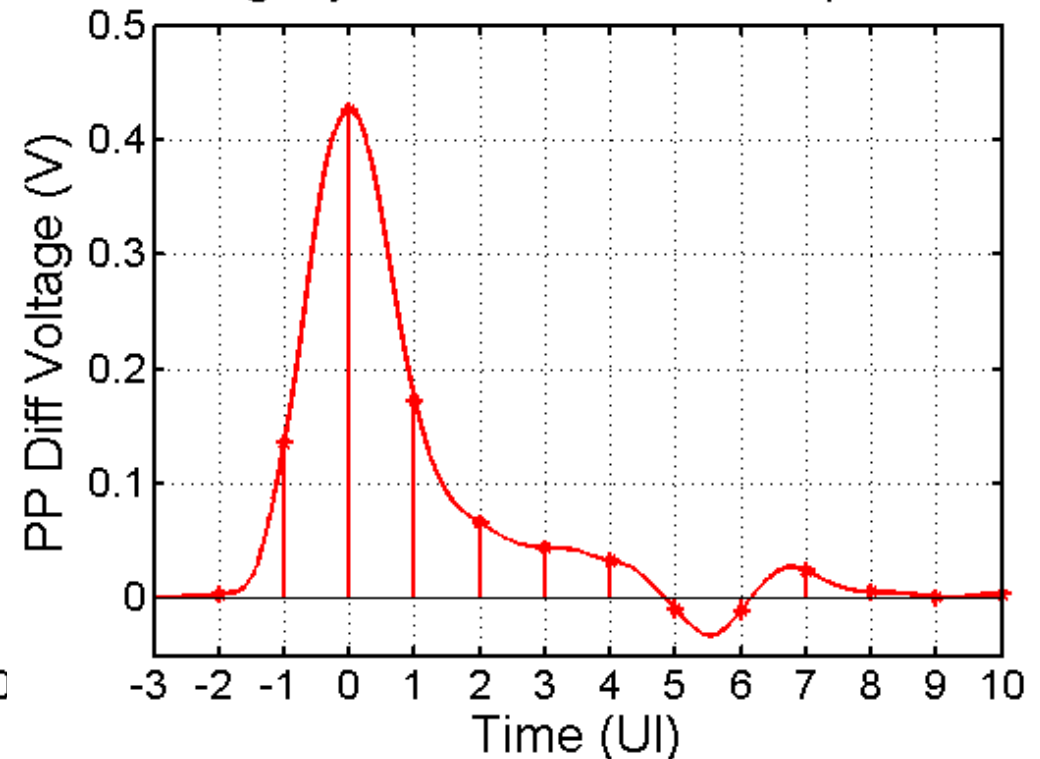

ISI Impact

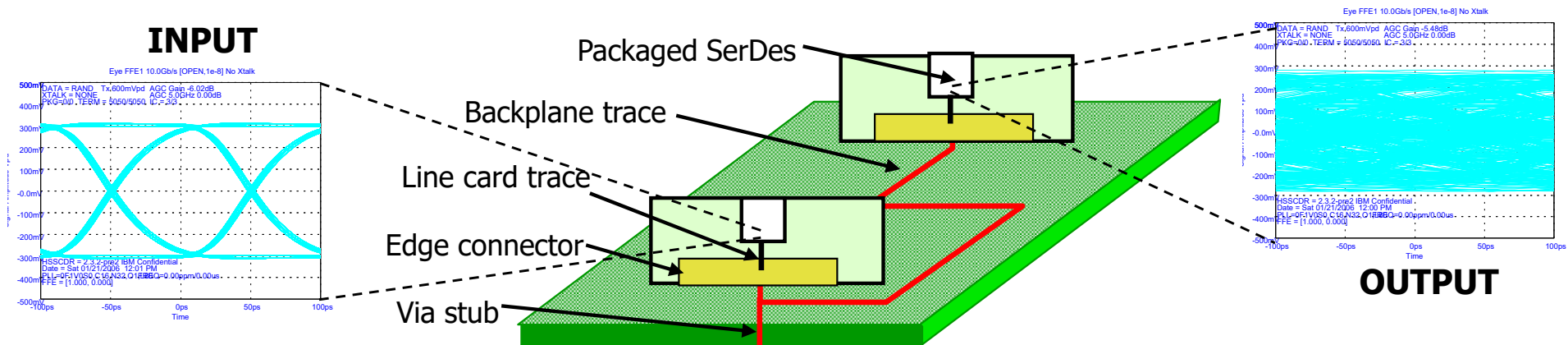- At channel input (TX output), eye diagram is wide open
- As data pulses propagate through channel, they experience dispersion and have significant ISI
 - Result is a closed eye at channel output (RX input)



[Meghelli (IBM) ISSCC 2006]

Next Time

- Channel pulse response model
- Modulation schemes