

ECEN689: Special Topics in High-Speed Links Circuits and Systems Spring 2011

Lecture 8: Termination & TX Driver Circuits



Sam Palermo


Analog & Mixed-Signal Center

Texas A&M University

Announcements & Agenda

- Reading
 - Will post some papers on voltage-mode drivers
- Termination Circuits
- TX Driver Circuits


High-Speed Electrical Link System

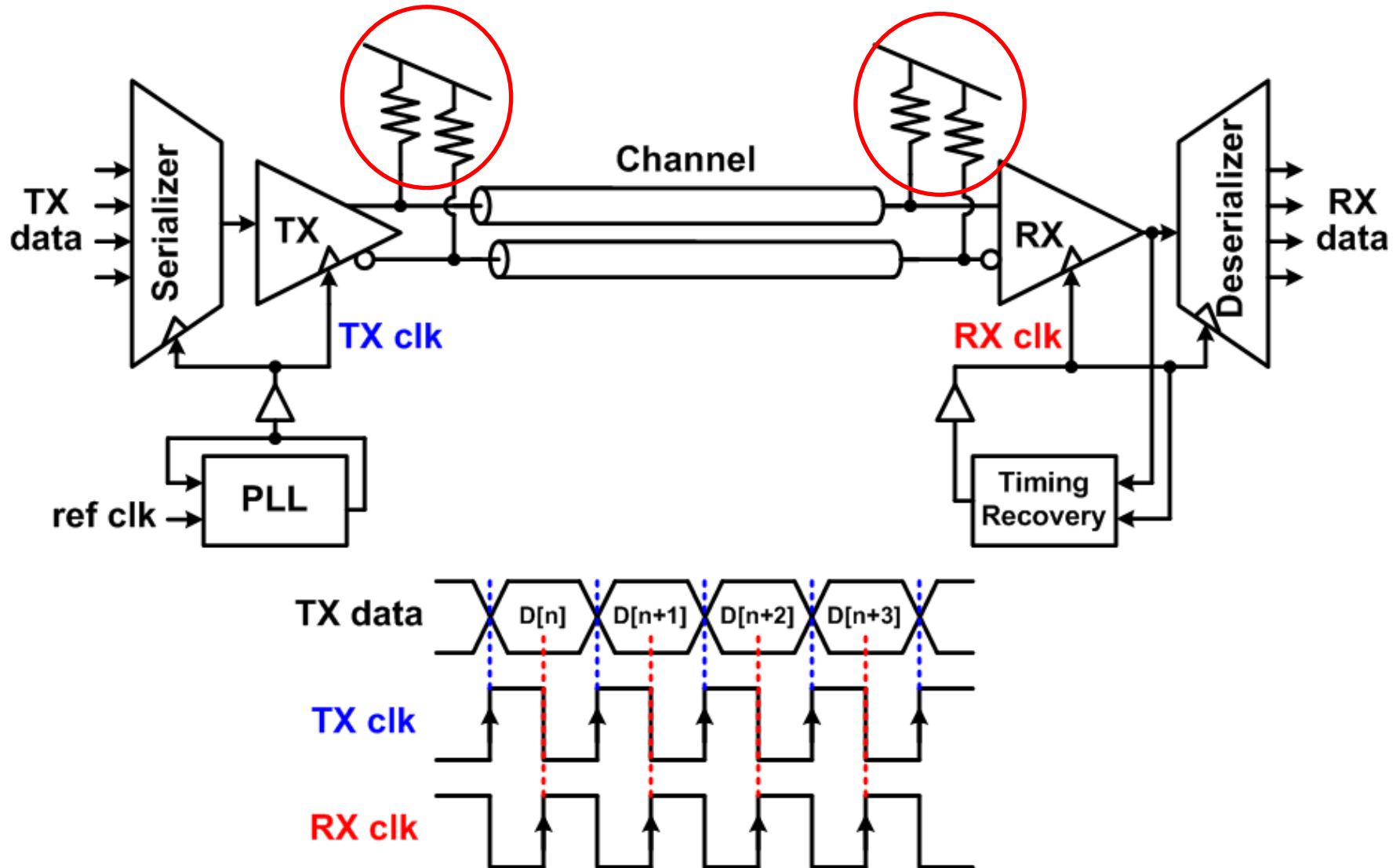

Termination

- Off-chip vs on-chip
- Series vs parallel
- DC vs AC Coupling
- Termination circuits


Off-Chip vs On-Chip Termination

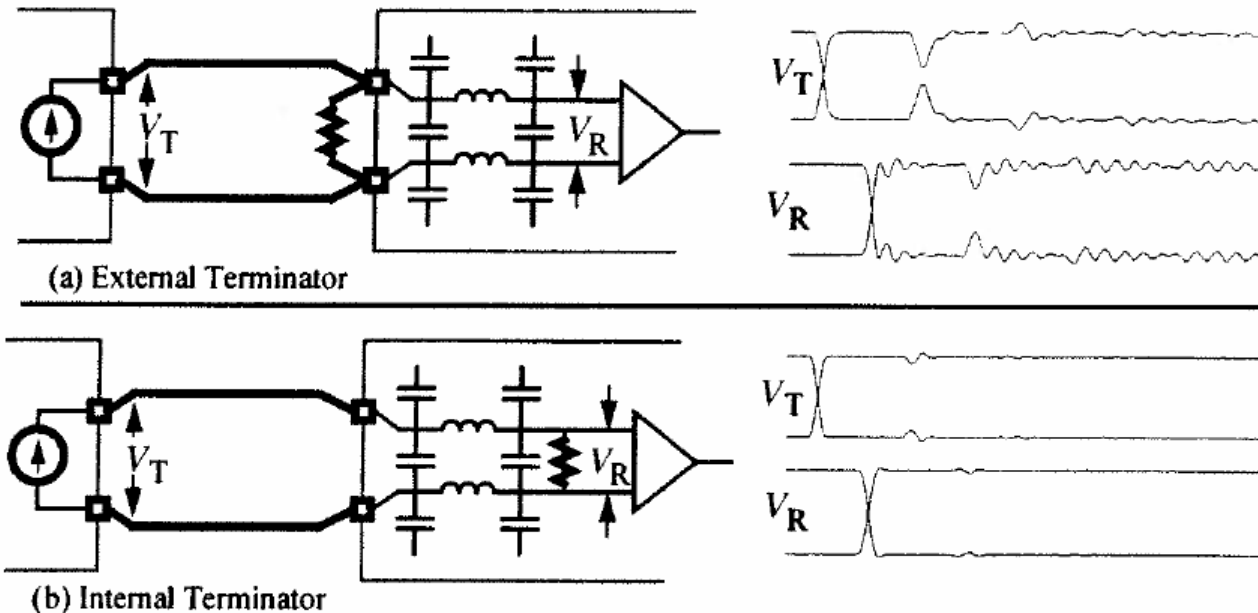


- Package parasitics act as an unterminated stub which sends reflections back onto the line
- On-chip termination makes package inductance part of transmission line

Series vs Parallel Termination



Series Termination

 

Parallel Termination

 


Double Termination

  


- Low impedance voltage-mode driver typically employs series termination
- High impedance current-mode driver typically employs parallel termination
- Double termination yields best signal quality
 - Done in majority of high performance serial links

AC vs DC Coupled Termination

 - DC coupling allows for uncoded data
- RX common-mode set by transmitter signal level



 - AC coupling allows for independent RX common-mode level
- Now channel has low frequency cut-off
 - Data must be coded




Passive Termination

- Choice of integrated resistors involves trade-offs in manufacturing steps, sheet resistance, parasitic capacitance, linearity, and ESD tolerance
- Integrated passive termination resistors are typically realized with unsalicided poly, diffusion, or n-well resistors
- Poly resistors are typically used due to linearity and tighter tolerances, but they typically vary +/-30% over process and temperature


Resistor Options (90nm CMOS)

Resistor	Poly	N-diffusion	N-well
Sheet R (Ω/sq)	90 \pm 10	300 \pm 50	450 \pm 200
VC1(V ⁻¹)	0	10 ⁻³	8x10 ⁻³
Parasitic Cap	2-3fF/ μm^2 (min L poly)	0.9fF/ μm^2 (area), 0.04fF/ μm (perimeter)	0.2fF/ μm^2 (area), 0.7fF/ μm (perimeter)

Active Termination

 

 
- Transistors must be used for termination in CMOS processes which don't provide resistors
- Triode-biased FET works well for low-swing ($<500\text{mV}$)
 - Adding a diode connected FET increases linear range
- Pass-gate structure allows for differential termination



Adjustable Termination

- FET resistance is a function of gate overdrive

 
$$R_{FET} = \frac{1}{\mu C_{ox} (W/L)(V_{GS} - V_t)}$$



[Dally]


- Large variance in FET threshold voltage requires adjustable termination structures
- Calibration can be done with an analog control voltage or through digital “trimming”
 - Analog control reduces V_{GS} and linear range
 - Digital control is generally preferred

Termination Digital Control Loop

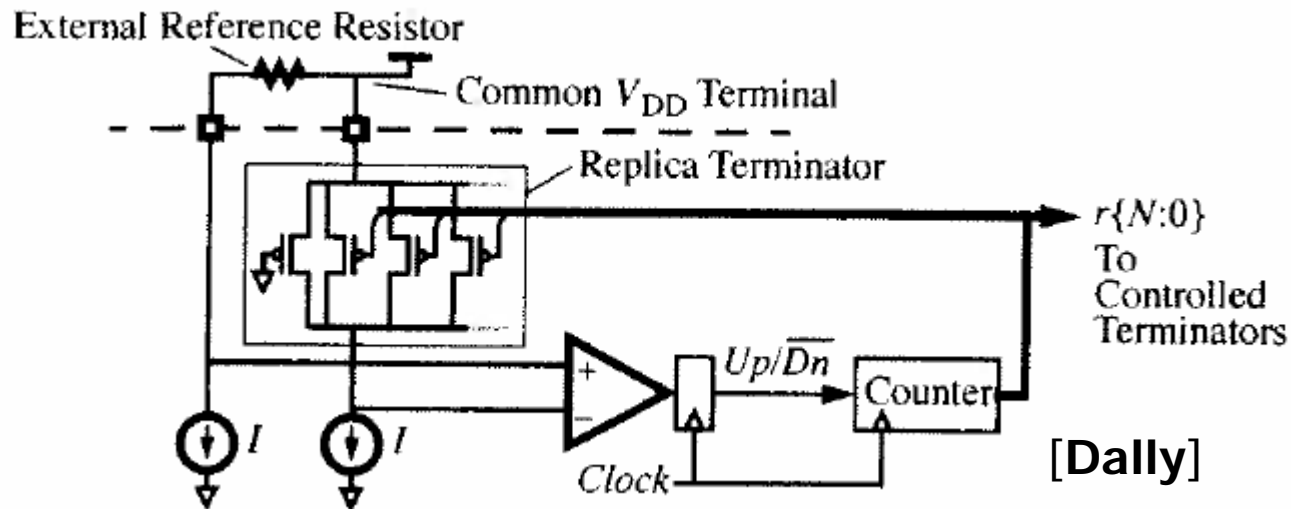

- Off-chip precision resistor is used as reference
- On-chip termination is varied until voltages are within an LSB
 - Dither filter typically used to avoid voltage noise
- Control loop may be shared among several links, but with increased nanometer CMOS variation per-channel calibration may be necessary

High-Speed Electrical Link System

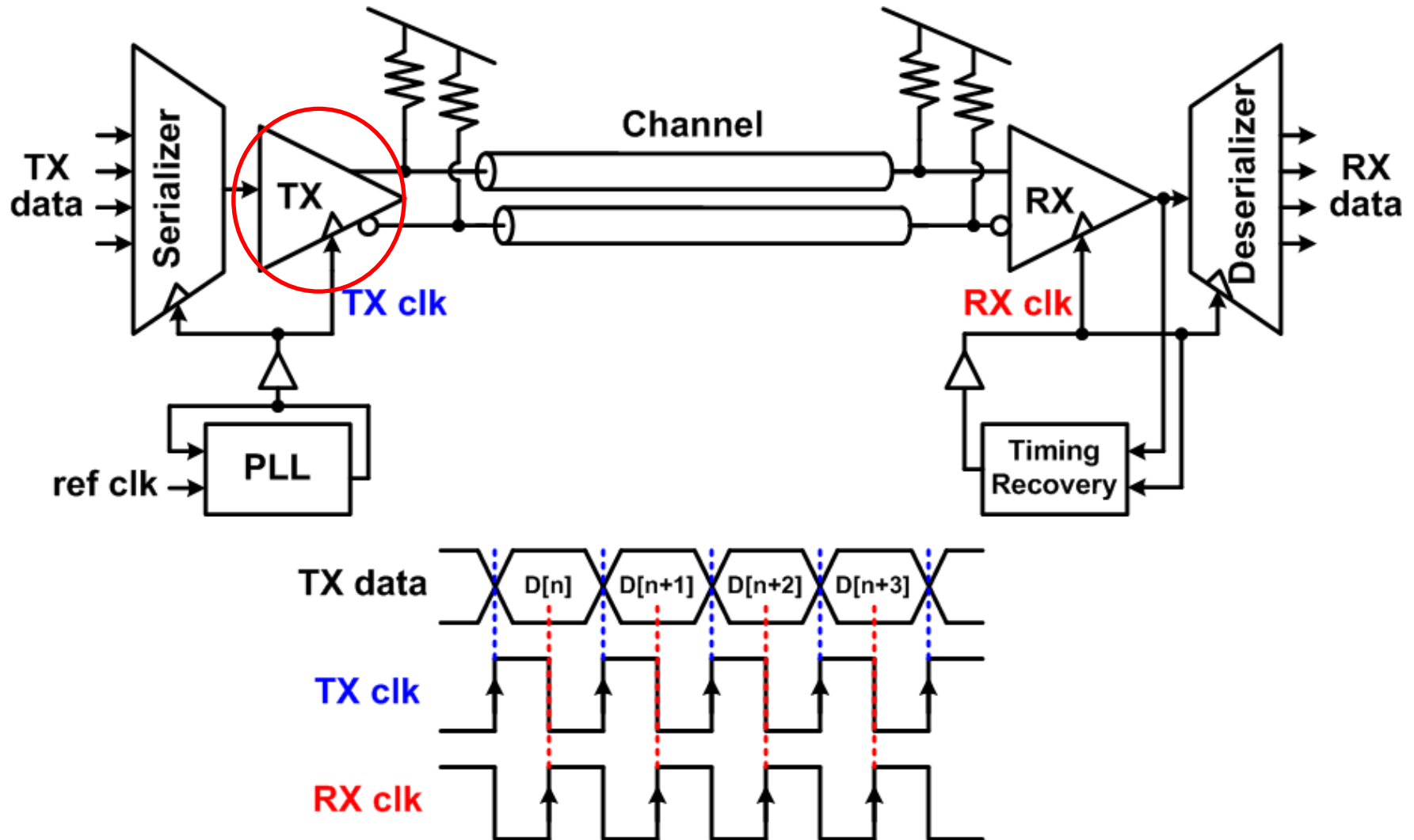


TX Driver Circuits


- Single-ended vs differential signaling
- Current-mode drivers
- Voltage-mode drivers
- Slew-rate control

Single-Ended Signaling

 - Finite supply impedance causes significant Simultaneous Switching Output (SSO) noise (xtalk)
- Necessitates large amounts of decoupling capacitance for supplies and reference voltage
 - Decap limits I/O area more than circuitry




Differential Signaling

 


- A difference between voltage or current is sent between two lines
- Requires 2x signal lines relative to single-ended signaling, but less return pins
- Advantages
 - Signal is self-referenced
 - Can achieve twice the signal swing
 - Rejects common-mode noise
 - Return current is ideally only DC

Current vs Voltage-Mode Driver

 - Signal integrity considerations (min. reflections) requires 50Ω driver output impedance
- To produce an output drive voltage
 - Current-mode drivers use Norton-equivalent parallel termination
 - Easier to control output impedance
 - Voltage-mode drivers use Thevenin-equivalent series termination
 - Potentially $\frac{1}{2}$ to $\frac{1}{4}$ the current for a given output swing




Current-Mode

 


Voltage-Mode

Push-Pull Current-Mode Driver

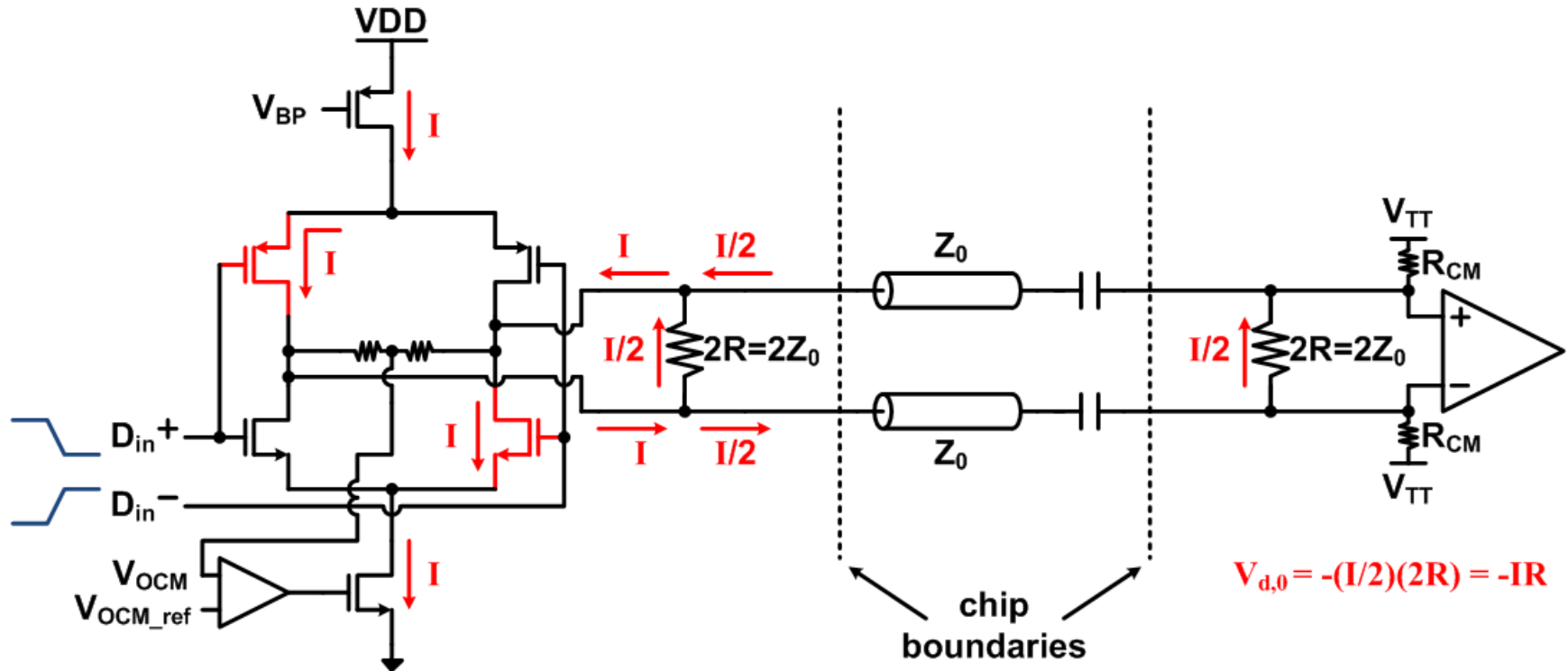

- Used in Low-Voltage Differential Signals (LVDS) standard
- Driver current is ideally constant, resulting in low dI/dt noise
- Dual current sources allow for good PSRR, but headroom can be a problem in low-voltage technologies
- Differential peak-to-peak RX swing is $\pm IR$ with double termination


Current-Mode Logic (CML) Driver

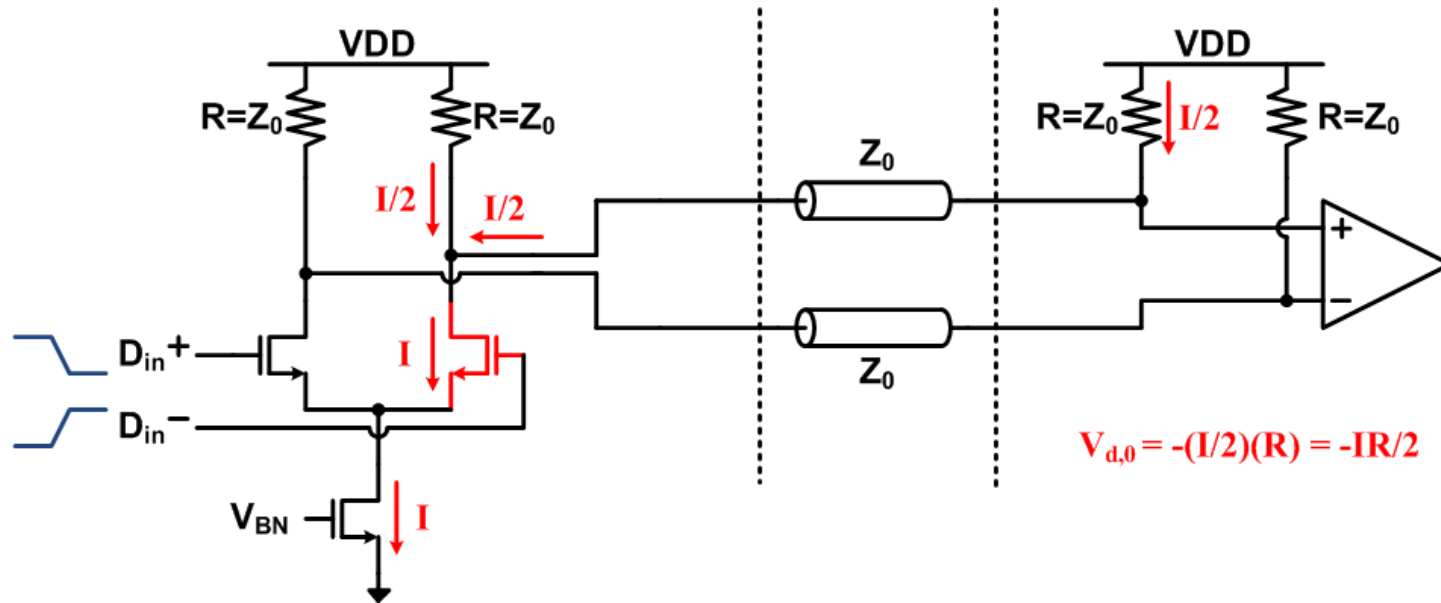

- Used in most high performance serial links
- Low voltage operation relative to push-pull driver
 - High output common-mode keeps current source saturated
- Can use DC or AC coupling
 - AC coupling requires data coding
- Differential pp RX swing is $\pm IR/2$ with double termination

Current-Mode Current Levels

Single-Ended Termination

 


$$V_{d,1} = (I/2)R$$

$$V_{d,0} = -(I/2)R$$

$$V_{d,pp} = IR$$

$$I = \frac{V_{d,pp}}{R}$$

Differential Termination

 

$$V_{d,1} = (I/4)(2R)$$


$$V_{d,0} = -(I/4)(2R)$$

$$V_{d,pp} = IR$$

$$I = \frac{V_{d,pp}}{R}$$

Voltage-Mode Current Levels

Single-Ended Termination

 

$$V_{d,1} = (V_s/2)$$


$$V_{d,1} = -(V_s/2)$$

$$V_{d,pp} = V_s$$

$$I = (V_s/2R)$$

$$I = \frac{V_{d,pp}}{2R}$$

Differential Termination

 

$$V_{d,1} = (V_s/2)$$

$$V_{d,1} = -(V_s/2)$$

$$V_{d,pp} = V_s$$

$$I = (V_s/4R)$$

$$I = \frac{V_{d,pp}}{4R}$$

Current-Mode vs Voltage-Mode Summary


Driver/Termination	Current Level	Normalized Current Level
Current-Mode/SE	$V_{d,pp}/Z_0$	1x
Current-Mode/Diff	$V_{d,pp}/Z_0$	1x
Voltage-Mode/SE	$V_{d,pp}/2Z_0$	0.5x
Voltage-Mode/Diff	$V_{d,pp}/4Z_0$	0.25x

- An ideal voltage-mode driver with differential RX termination enables a *potential* 4x reduction in driver power
- *Actual* driver power levels also depend on
 - Output impedance control
 - Pre-driver power
 - Equalization implementation

Voltage-Mode Drivers

- Voltage-mode driver implementation depends on output swing requirements
- For low-swing ($<400\text{-}500\text{mVpp}$), an all NMOS driver is suitable
- For high-swing, CMOS driver is used


Low-Swing Voltage-Mode Driver

 

$$V_s < \frac{4}{3}(V_{DD} - V_{t1} - V_{OD1}) \text{ (Diff. Term)}$$

$$V_s < 2(V_{DD} - V_{t1} - V_{OD1}) \text{ (SE Term)}$$


High-Swing Voltage-Mode Driver

 

$$V_s > |V_{t1}| + V_{OD1}$$


Low-Swing VM Driver Impedance Control

[Poulton JSSC 2007]

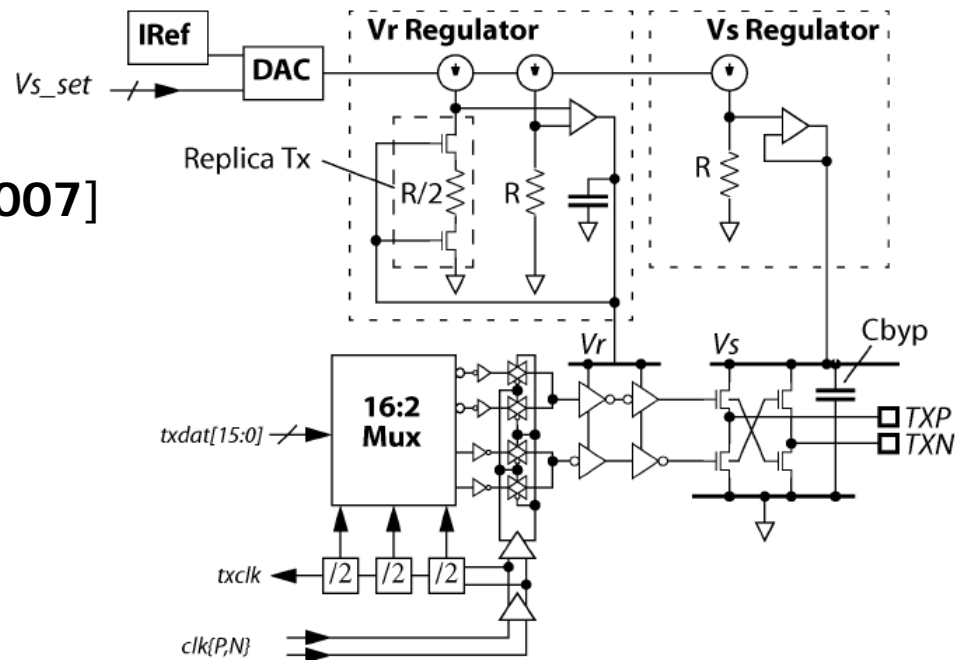


- A linear regulator sets the output stage supply, V_s
- Termination is implemented by output NMOS transistors
- To compensate for PVT and varying output swing levels, the pre-drive supply is adjusted with a feedback loop
- The top and bottom output stage transistors need to be sized differently, as they see a different V_{OD}

High-Swing VM Driver Impedance Control

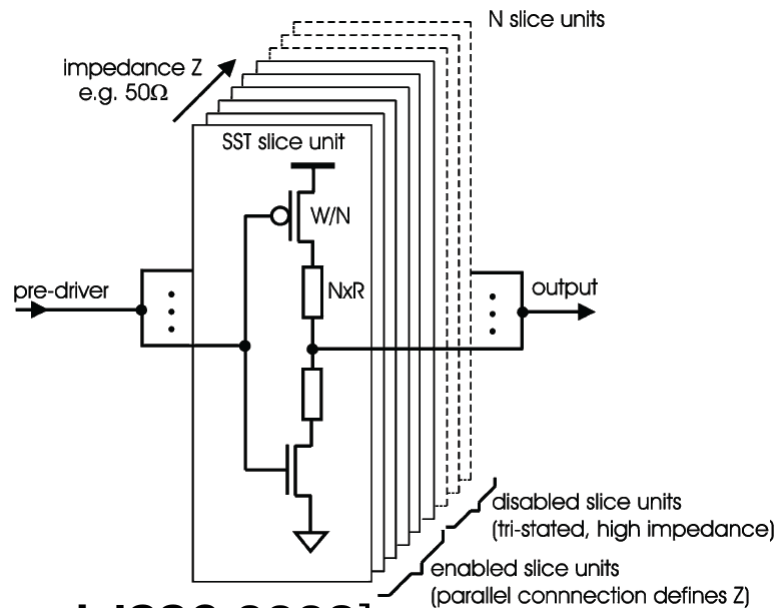

[Kossel JSSC 2008]

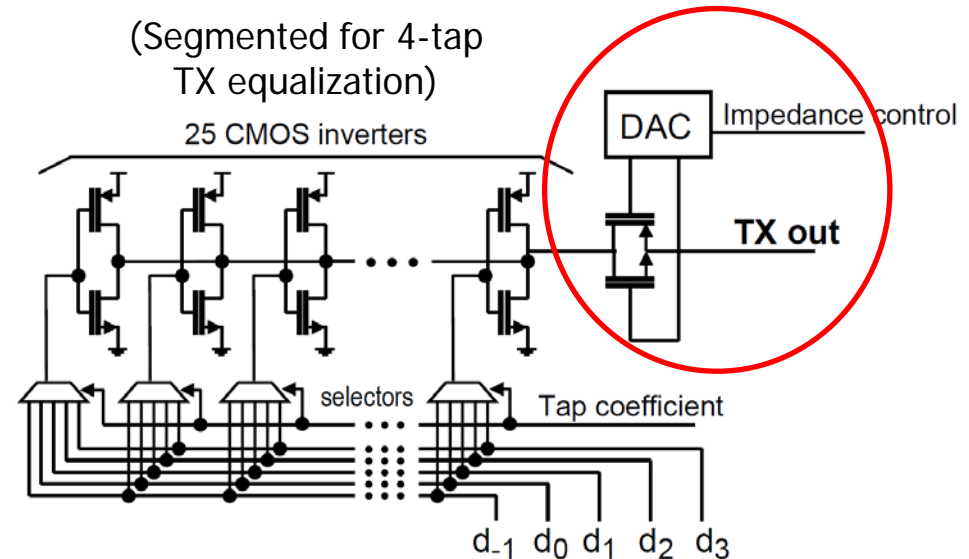



[Fukada ISSCC 2008]

- High-swing voltage-mode driver termination is implemented with a combination of output driver transistors and series resistors
- To meet termination resistance levels (50Ω), large output transistors are required
 - Degrades potential power savings vs current-mode driver


TX Driver Slew Rate Control

- Output transition times should be controlled
 - Too slow
 - Limits max data rate
 - Too fast
 - Can excite resonant circuits, resulting in ISI due to ringing
 - Cause excessive crosstalk
- Slew rate control reduces reflections and crosstalk




Slew Rate Control w/ Segmented Driver

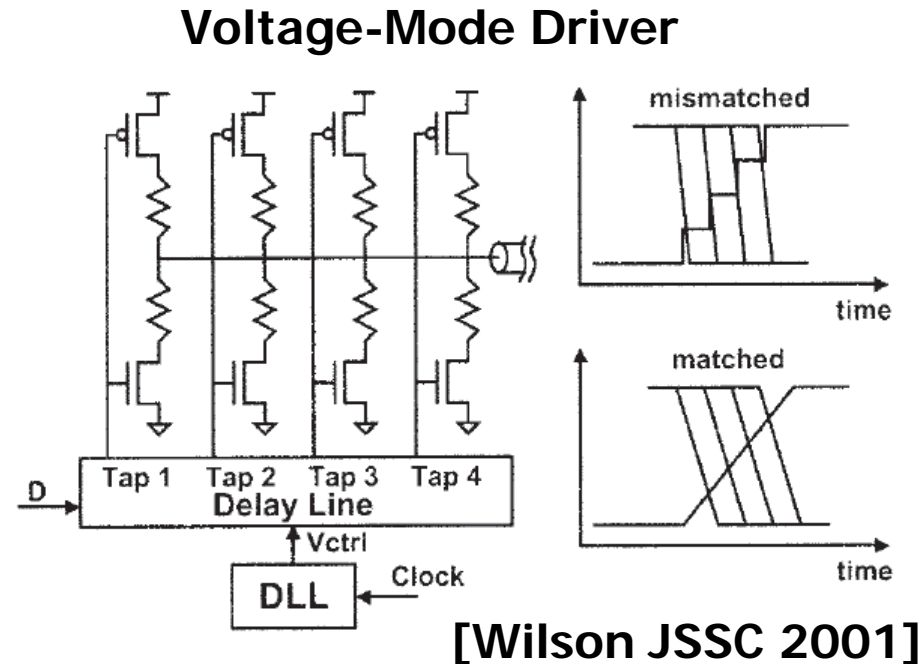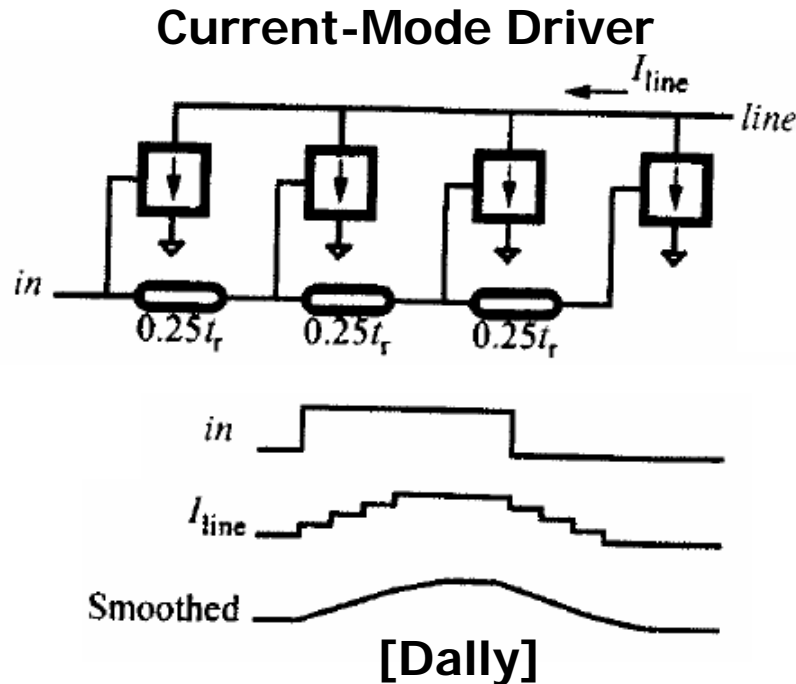

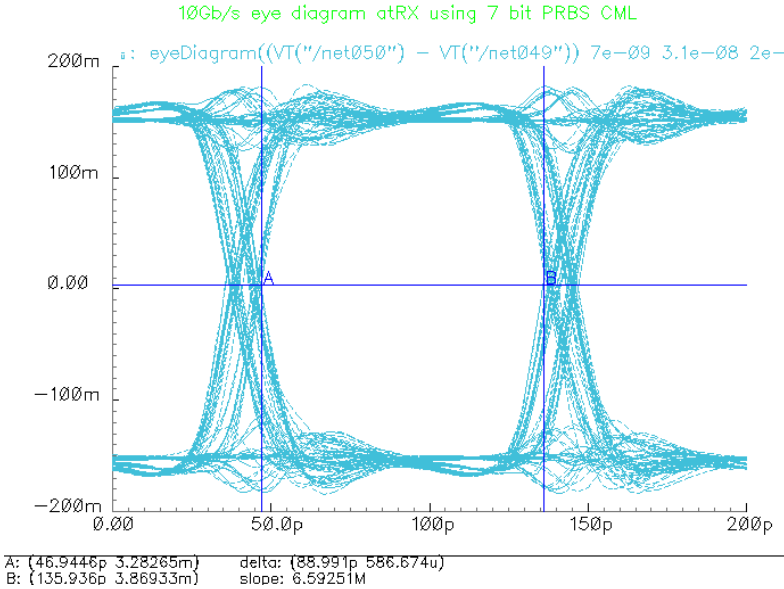- Slew rate control can be implemented with a segmented output driver
- Segments turn-on time are spaced by $1/n$ of desired transition time
- Predriver transition time should also be controlled



Voltage-Mode Driver Example

 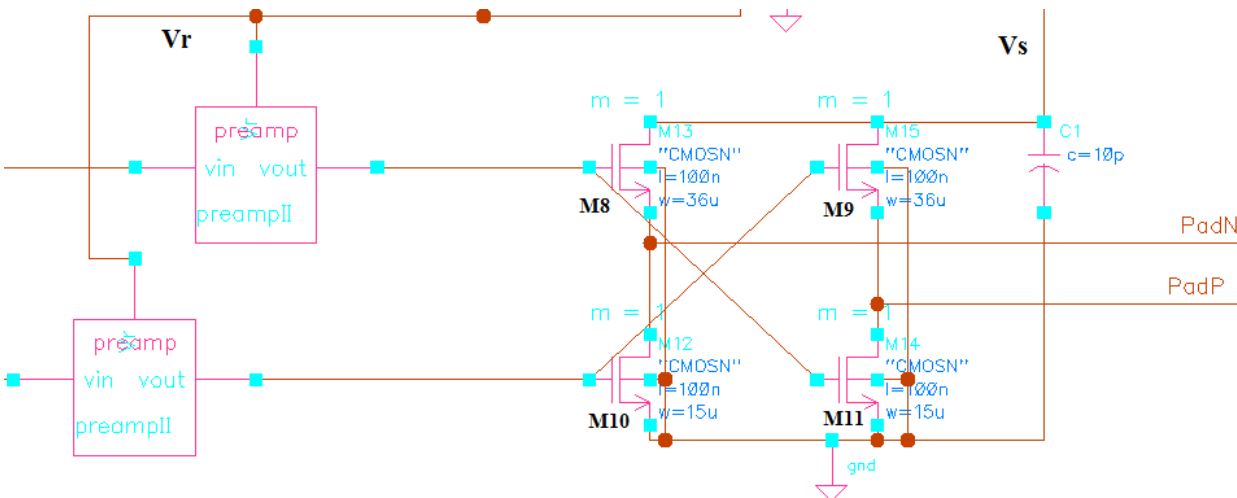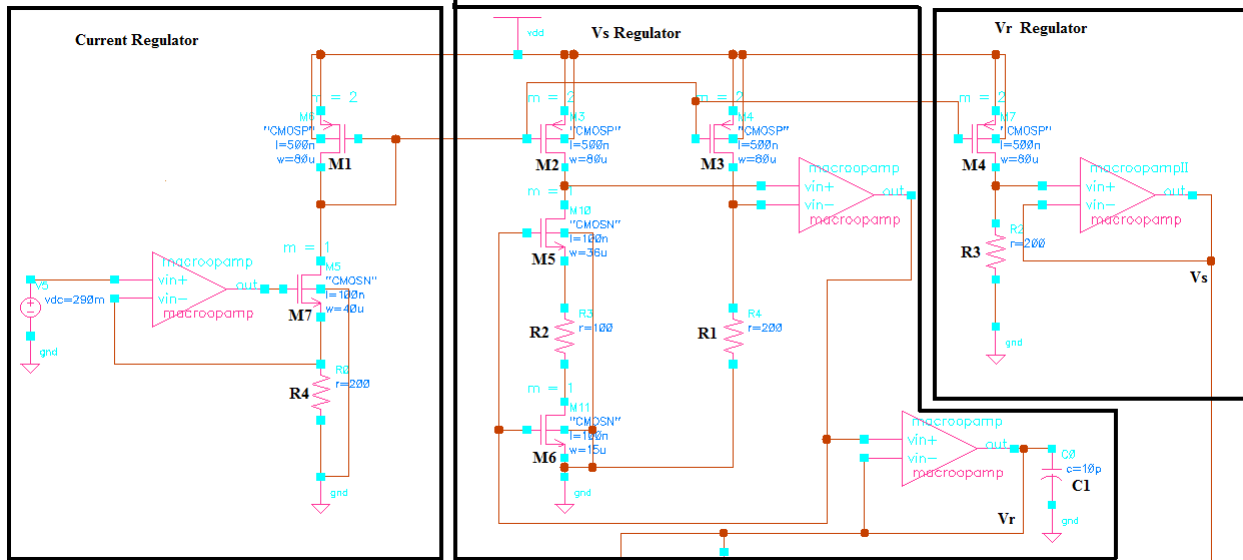

Next Time

- TX circuit speed limitations
 - Clock distribution
 - Multiplexing circuits
- Receiver Circuits