

# ECEN720: High-Speed Links Circuits and Systems Spring 2023

---

## Lecture 9: Noise Sources




Sam Palermo  
Analog & Mixed-Signal Center  
Texas A&M University

# Announcements

---

- Lab 5 Report & Prelab 6 due Mar 27
- Stateye theory paper posted on website

# Noise in High-Speed Link Systems

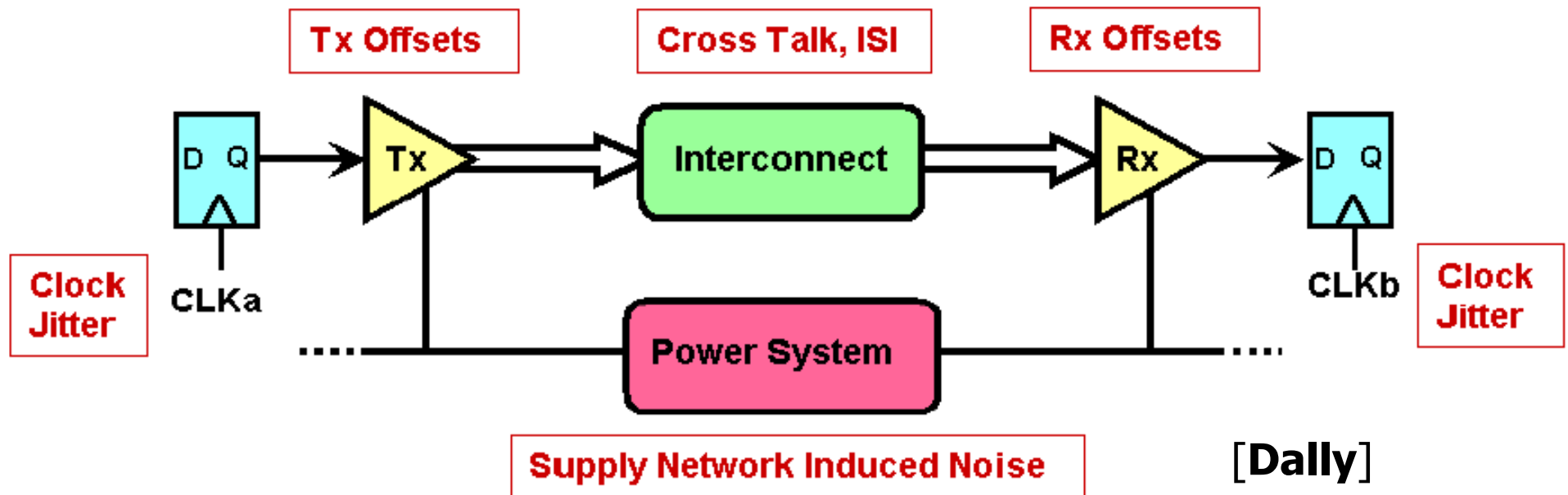

- Multiple noise sources can degrade link timing and amplitude margin

# Noise Source Overview

---

- Common “noise” sources
  - Power supply noise
  - Receiver offset
  - Crosstalk
  - Inter-symbol interference
  - Random noise
- Power supply noise
  - Switching current through finite supply impedance causes supply voltage drops that vary with time and physical location
- Receiver offset
  - Caused by random device mismatches
- Crosstalk
  - One signal (aggressor) interfering with another signal (victim)
  - On-chip coupling (capacitive)
  - Off-chip coupling (t-line)
    - Near-end
    - Far-end
- Inter-symbol interference
  - Signal dispersion causes signal to interfere with itself
- Random noise
  - Thermal & shot noise
  - Clock jitter components

# Bounded and Statistical Noise Sources

---

- Bounded or *deterministic* noise sources
  - Have theoretically predictable values with defined worst-case bounds
  - Allows for simple (but pessimistic) worst-case analysis
  - Examples
    - Crosstalk to small channel count
    - ISI
    - Receiver offset
- Statistical or *random* noise sources
  - Treat noise as a random process
    - Source may be psuedo-random
  - Often characterized w/ Gaussian stats
    - RMS value
    - Probability density function (PDF)
  - Examples
    - Thermal noise
    - Clock jitter components
    - Crosstalk to large channel count
- Understanding whether noise source is bounded or random is critical to accurate link performance estimation

# Proportional and Independent Noise Sources

---

- Some noise is *proportional* to signal swing
  - Crosstalk
  - Simultaneous switching power supply noise
  - ISI
- Can't overpower this noise
  - Larger signal = more noise
- Some noise is *independent* to signal swing
  - RX offset
  - Non-IO power supply noise
- Can overpower this noise

$$V_N = K_N V_S + V_{NI}$$

The diagram illustrates the equation  $V_N = K_N V_S + V_{NI}$ . Arrows point from the following labels to their corresponding terms in the equation:


- Total noise points to  $V_N$
- Proportional noise constant points to  $K_N$
- Signal swing points to  $V_S$
- Independent noise points to  $V_{NI}$

# Common Noise Sources

---

- Power supply noise
- Receiver offset
- Crosstalk
- Inter-symbol interference
- Random noise

# Power Supply Noise

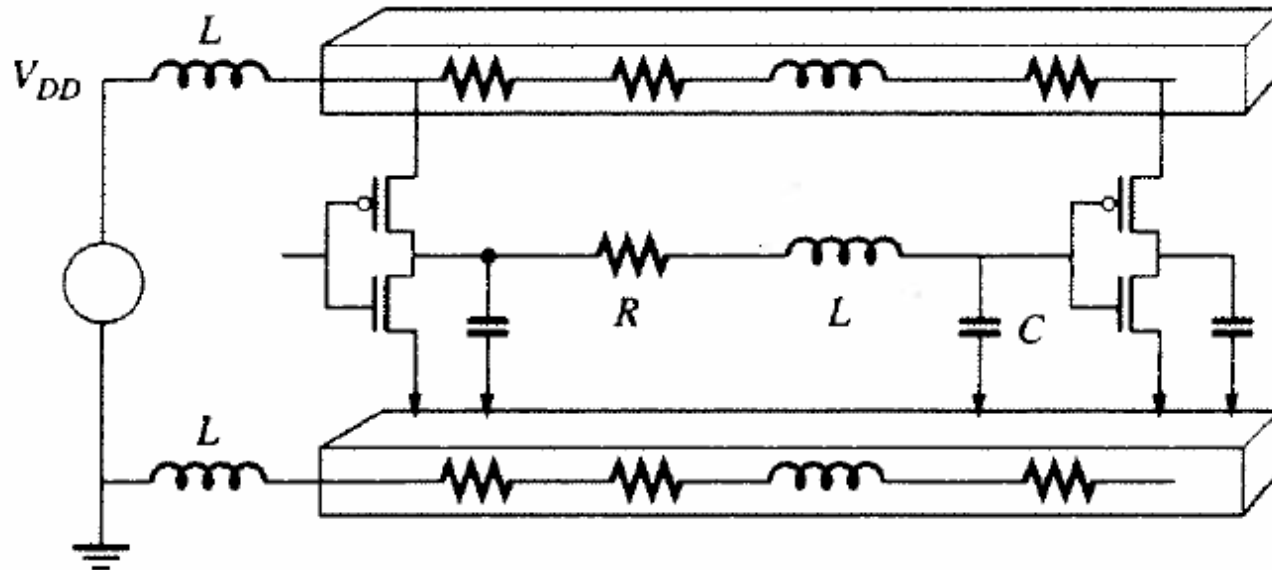


- Circuits draw current from the VDD supply nets and return current to the GND nets
- Supply networks have finite impedance
- Time-varying (switching) currents induce variations on the supply voltage
- Supply noise a circuit sees depends on its location in supply distribution network



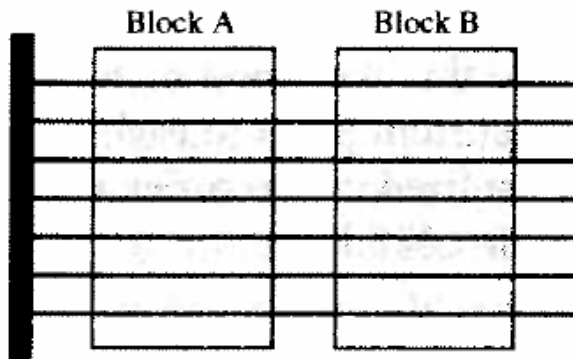
# Power Routing

---

Bad – Block B will experience excessive supply noise




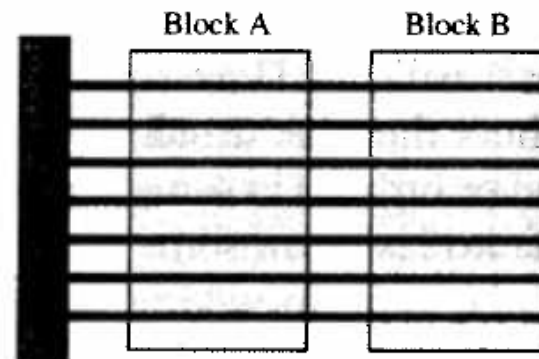Better – Block B will experience 1/2 supply noise, but at the cost of double the power routing through blocks




[Hodges]

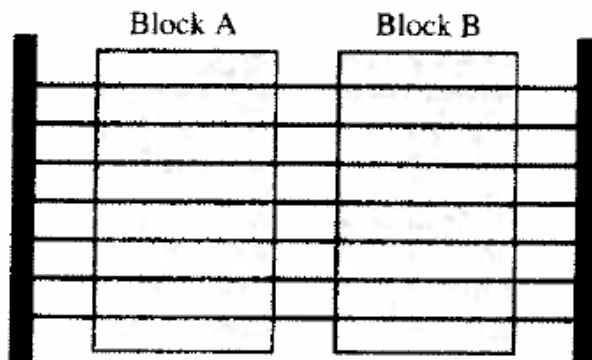Even Better – Block A & B will experience similar supply noise




Best – Block A & B are more isolated

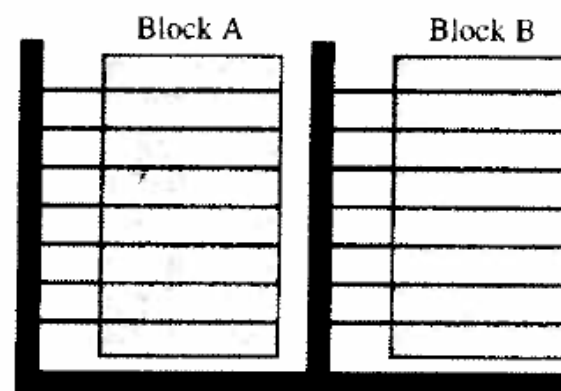

[Hodges]
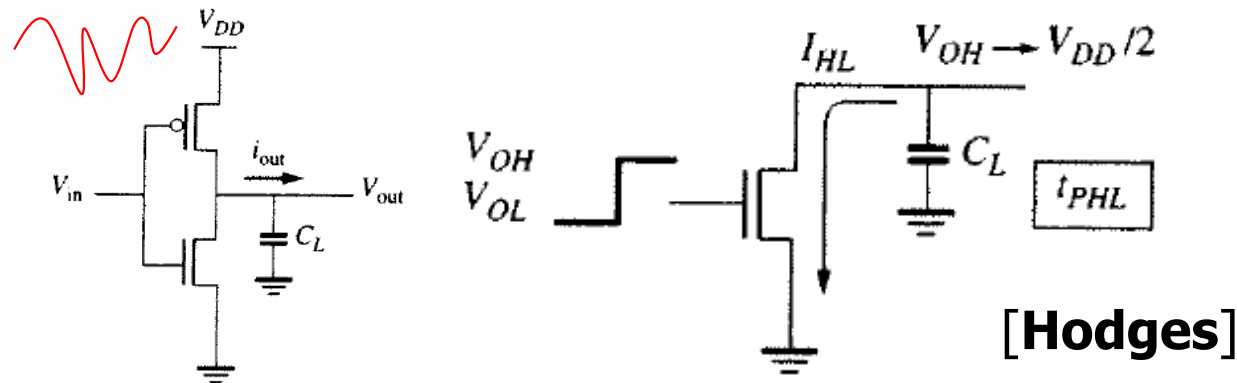
# Supply Induced Delay Variation

- Supply noise can induce variations in circuit delay
  - Results in deterministic jitter on clocks & data signals



$$t_{PHL} = \frac{C_L (V_{DD}/2)}{I_{DSATN}} = \frac{C_L (V_{DD}/2)}{\left( \frac{W_N v_{sat} C_{ox} (V_{DD} - V_{TN})^2}{V_{DD} - V_{TN} + E_{CN} L_N} \right)} \approx \frac{C_L V_{DD}}{2W_N v_{sat} C_{ox} (V_{DD} - V_{TN})}$$


$$\text{Delay} \propto \frac{V_{DD}}{V_{DD} - V_{TN}} \approx \propto V_{DD}$$

- CMOS delay is approximately directly proportional to VDD
  - More delay results in more deterministic jitter
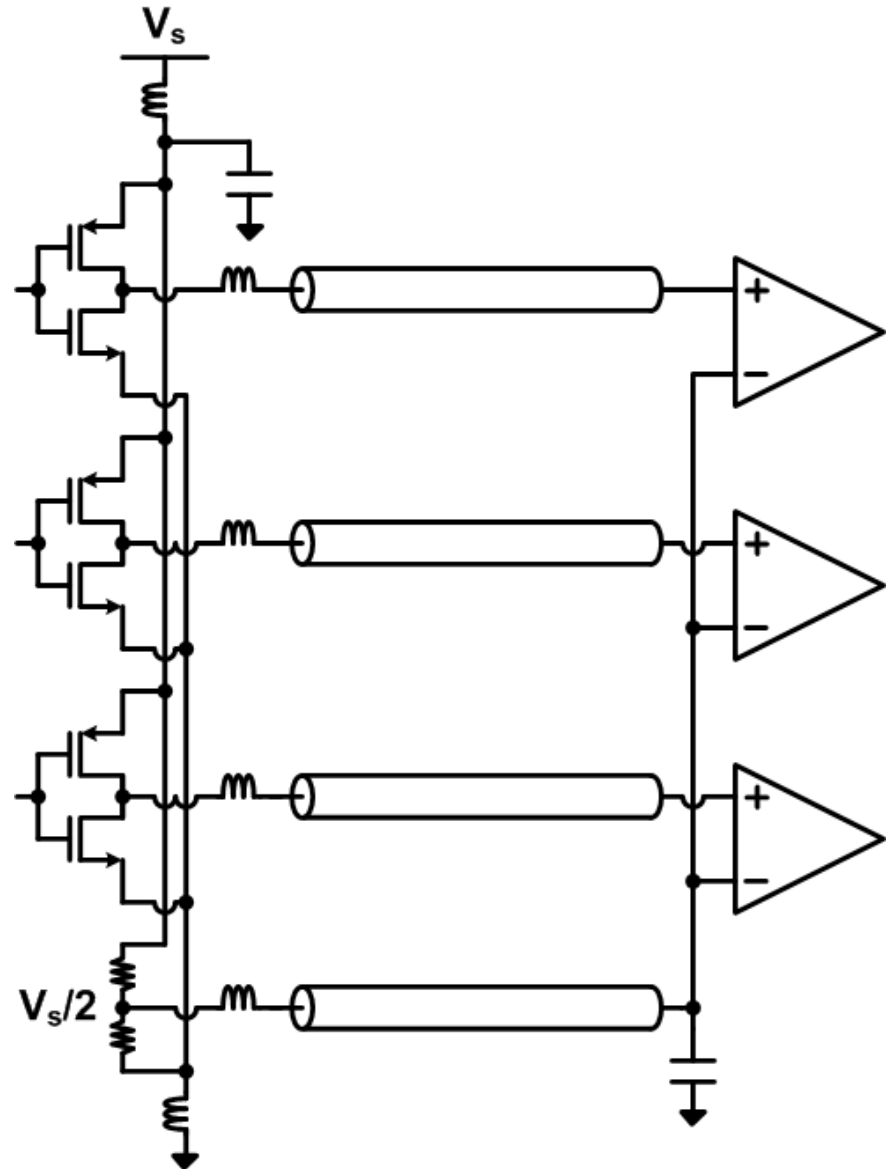
# Simultaneous Switching Noise

- Finite supply impedance causes significant Simultaneous Switching Output (SSO) noise (xtalk)
- SSO noise is proportional to number of outputs switching,  $n$ , and inversely proportional to signal transition time,  $t_r$

$$V_N = L \frac{i}{t_r} = n \frac{L V_s}{Z_0 t_r}$$




# Common Noise Sources

---

- Power supply noise
- Receiver offset
- Crosstalk
- Inter-symbol interference
- Random noise

# Receiver Input Referred Offset

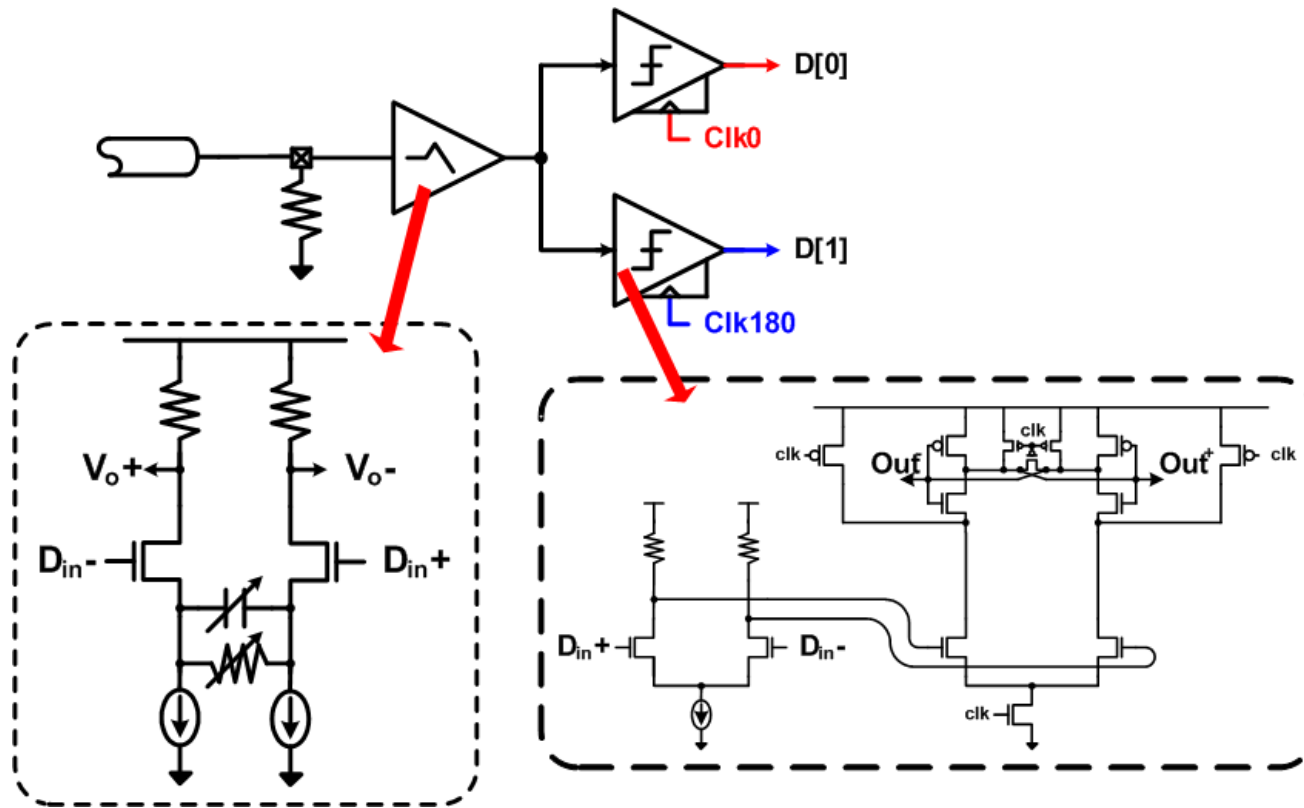

- The input referred offset is primarily a function of  $V_{th}$  mismatch and a weaker function of  $\beta$  (mobility) mismatch

$$\sigma_{V_t} = \frac{A_{V_t}}{\sqrt{WL}}, \quad \sigma_{\Delta\beta/\beta} = \frac{A_{\beta}}{\sqrt{WL}}$$

# Receiver Input Referred Offset

---

$$\sigma_{V_t} = \frac{A_{V_t}}{\sqrt{WL}}, \quad \sigma_{\Delta\beta/\beta} = \frac{A_{\beta}}{\sqrt{WL}}$$

- To reduce input offset 2x, we need to increase area 4x
  - Not practical due to excessive area and power consumption
  - Offset correction necessary to efficiently achieve good sensitivity
- Ideally the offset “A” coefficients are given by the design kit and Monte Carlo is performed to extract offset sigma
- If not, here are some common values:
  - $A_{V_t} = 1\text{mV}\mu\text{m}$  per nm of  $t_{\text{ox}}$ 
    - For our default 90nm technology,  $t_{\text{ox}}=2.8\text{nm} \rightarrow A_{V_t} \sim 2.8\text{mV}\mu\text{m}$
  - $A_{\beta}$  is generally near  $2\%\mu\text{m}$

# Common Noise Sources

---

- Power supply noise
- Receiver offset
- **Crosstalk**
- Inter-symbol interference
- Random noise

# Crosstalk


---

- Crosstalk is noise induced by one signal (aggressor) that interferes with another signal (victim)
- Main crosstalk sources
  - Coupling between on-chip (capacitive) wires
  - Coupling between off-chip (t-line/channel) wires
  - Signal return coupling
- Crosstalk is a proportional noise source
  - Cannot be reduced by scaling signal levels
  - Addressed by using proper signal conventions, improving channel and supply network, and using good circuit design and layout techniques


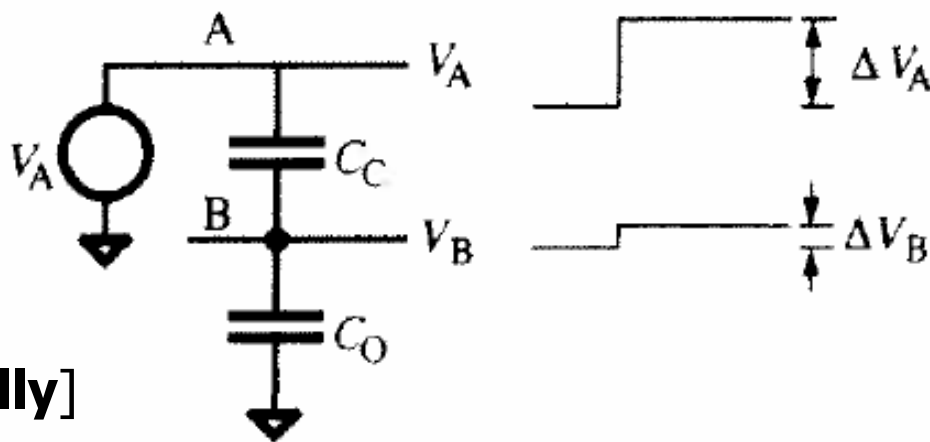
# Crosstalk to Capacitive Lines

- **On-chip wires** have significant capacitance to adjacent wires both on same metal layer and adjacent vertical layers
- Floating victim
  - Examples: Sample-nodes, domino logic
  - When aggressor switches
    - Signal gets coupled to victim via a capacitive voltage divider
    - Signal is not restored



$$\Delta V_B = k_c \Delta V_A$$

$$k_c = \frac{C_C}{C_C + C_O}$$


[Dally]

# Crosstalk to Driven Capacitive Lines

- Crosstalk to a driven line will decay away with a time-constant

$$\tau_{xc} = R_O (C_C + C_O)$$

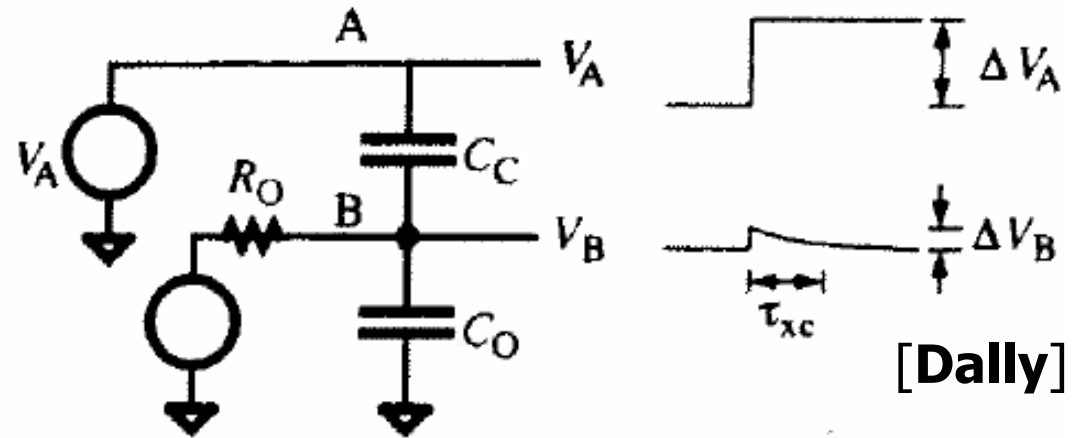- Peak crosstalk is inversely proportional to aggressor transition times,  $t_r$ , and driver strength ( $1/R_O$ )



**Ideal Unit Step :**


$$\Delta V_B(t) = k_c \exp\left(-\frac{t}{\tau_{xc}}\right)$$

**Step with Finite Rise Time,  $t_r$  :**

$$\Delta V_B(t) = \begin{cases} k_c \left(\frac{\tau_{xc}}{t_r}\right) \left[1 - \exp\left(-\frac{t}{\tau_{xc}}\right)\right] & \text{if } t < t_r \\ k_c \left(\frac{\tau_{xc}}{t_r}\right) \left[\exp\left(-\frac{t-t_r}{\tau_{xc}}\right) - \exp\left(-\frac{t}{\tau_{xc}}\right)\right] & \text{if } t \geq t_r \end{cases}$$
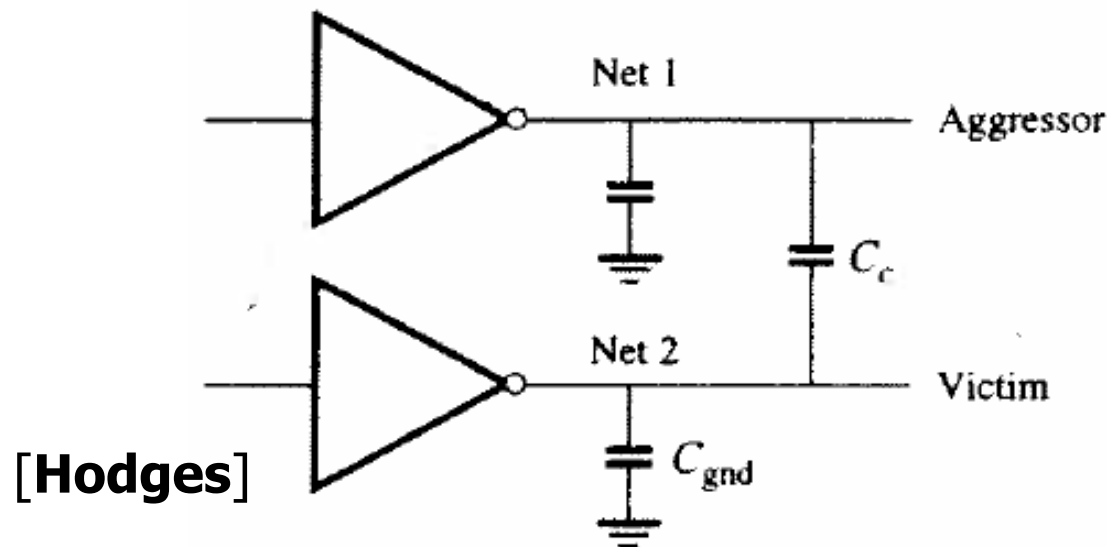
# Capacitive Crosstalk Delay Impact

- Aggressor transitioning near victim transition can modulate the victim's effective load capacitance
- This modulates the victim signal's delay, resulting in deterministic jitter



**Aggressor Static :**  $C_L = C_{gnd} + C_C$

**Aggressor Switching Same Way :**  $C_L = C_{gnd}$

**Aggressor Switching Opposite Way :**  $C_L = C_{gnd} + 2C_C$



# Mitigating Capacitive (On-Chip) Crosstalk

---

- Adjacent vertical metal layers should be routed perpendicular (Manhattan routing)
- Limit maximum parallel routing distance
- Avoid floating signals and use keeper transistors with dynamic logic
- Maximize signal transition time
  - Trade-off with jitter sensitivity
- For differential signals, periodically “twist” routing to make cross-talk common-mode
- Separate sensitive signals
- Use shield wires
- Couple DC signals to appropriate supply

# Transmission Line Crosstalk

- 2 coupled lines:

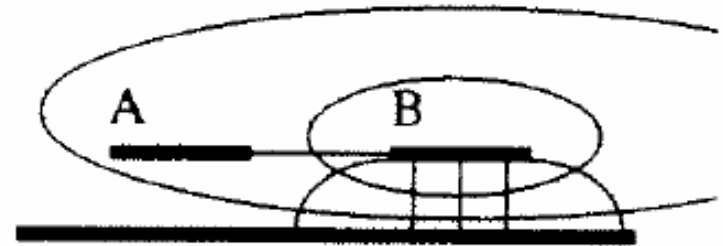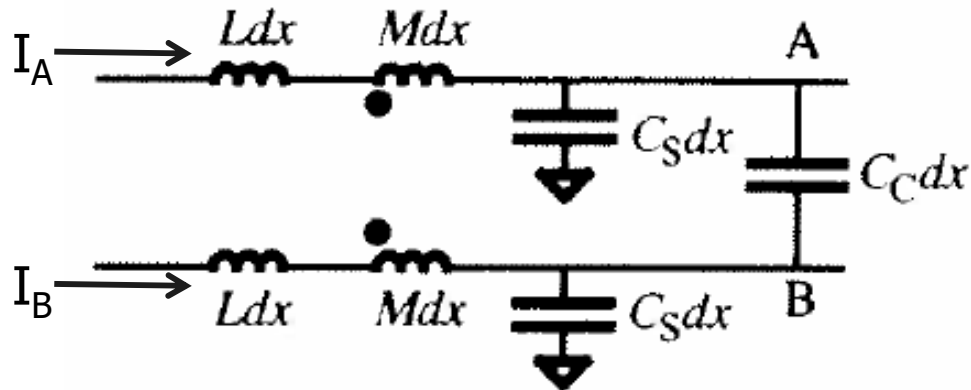

[Dally]



- Transient voltage signal on A is coupled to B capacitively

$$\frac{dV_B(x,t)}{dt} = k_{cx} \frac{dV_A(x,t)}{dt} \quad \text{where} \quad k_{cx} = \frac{C_C}{C_S + C_C}$$

- Capacitive coupling sends half the coupled energy in each direction with equal polarity

# Transmission Line Crosstalk

- 2 coupled lines:

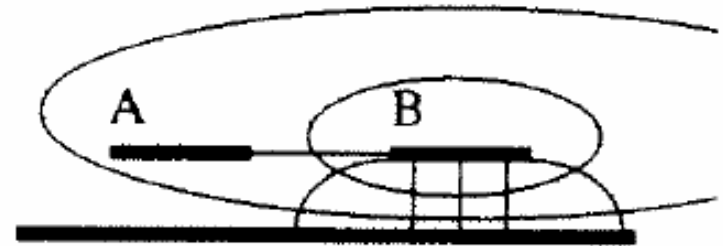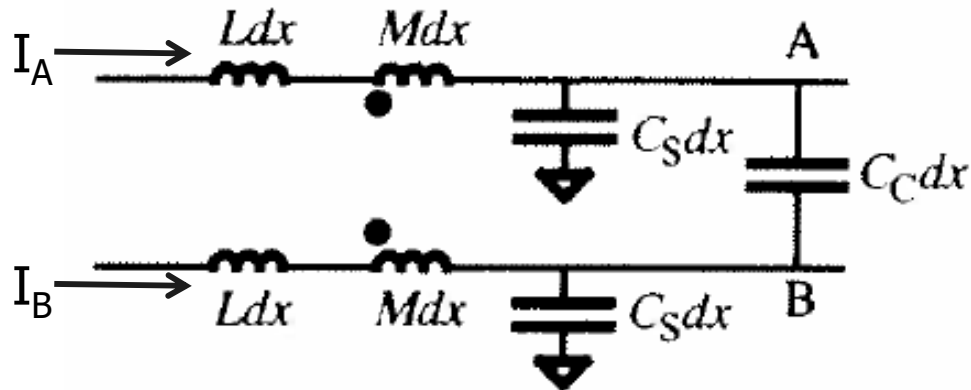

[Dally]

- Transient current signal on A is coupled to B through mutual inductance

$$\frac{\partial I_A(x,t)}{\partial t} = -\frac{\partial V_A(x,t)}{L\partial x}$$

$$\frac{dV_B(x,t)}{dx} = -M \frac{dI_A(x,t)}{dt} = \frac{M}{L} \left[ \frac{dV_A(x,t)}{dx} \right] = k_{lx} \frac{dV_A(x,t)}{dx} \quad \text{where} \quad \boxed{k_{lx} = \frac{M}{L}}$$

- Inductive coupling sends half the coupled energy in each direction with a negative forward traveling wave and a positive reverse traveling wave

# Near- and Far-End Crosstalk

[Hall]



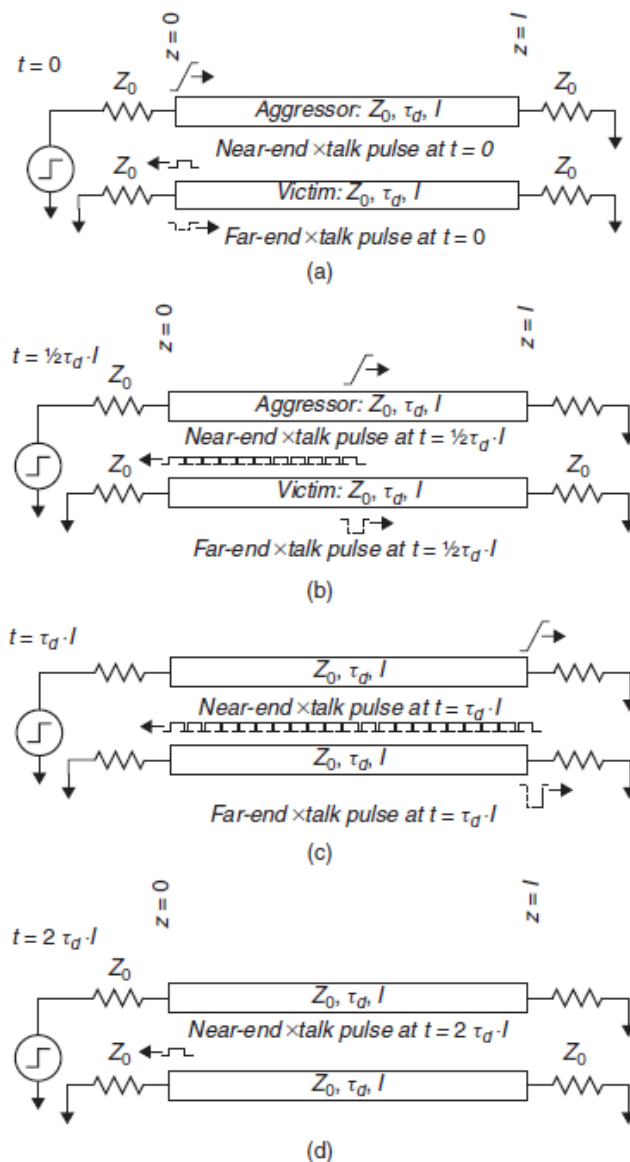


Figure 4-22 Summary of propagation of forward- and backward-coupled noise: (a) initial wave launch; (b) halfway down the line; (c) one full trip down the line; (d) round trip.

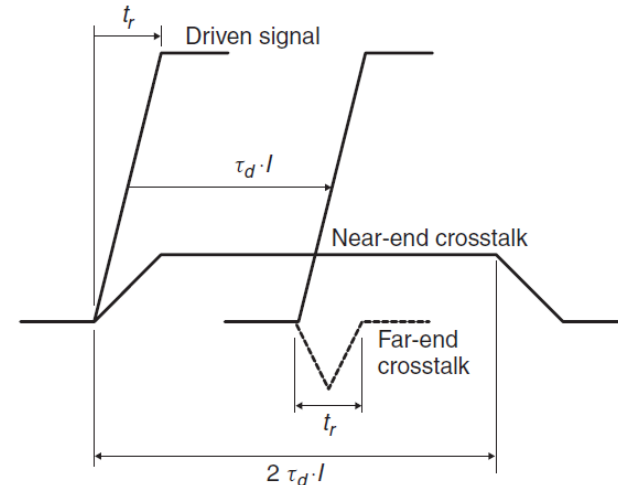


- Near-end crosstalk (NEXT) is immediately observed starting at the aggressor transition time and continuing for a round-trip delay
- Due to the capacitive and inductive coupling terms having the same polarity, the NEXT signal will have the same polarity as the aggressor
- Far-end crosstalk (FEXT) propagates along the victim channel with the incident signal and is only observed once
- Due to the capacitive and inductive coupling terms having the opposite polarity, the FEXT signal can have either polarity, and in a homogeneous medium (stripline) cancel out

# Near- and Far-End Crosstalk

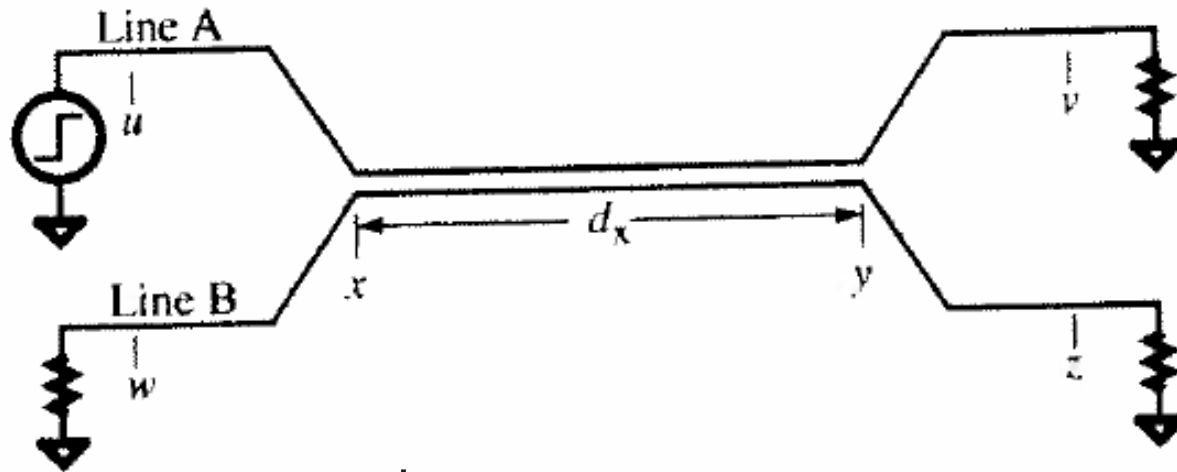

Reverse Coupling Coefficient  
 $k_{rx}$  (NEXT)

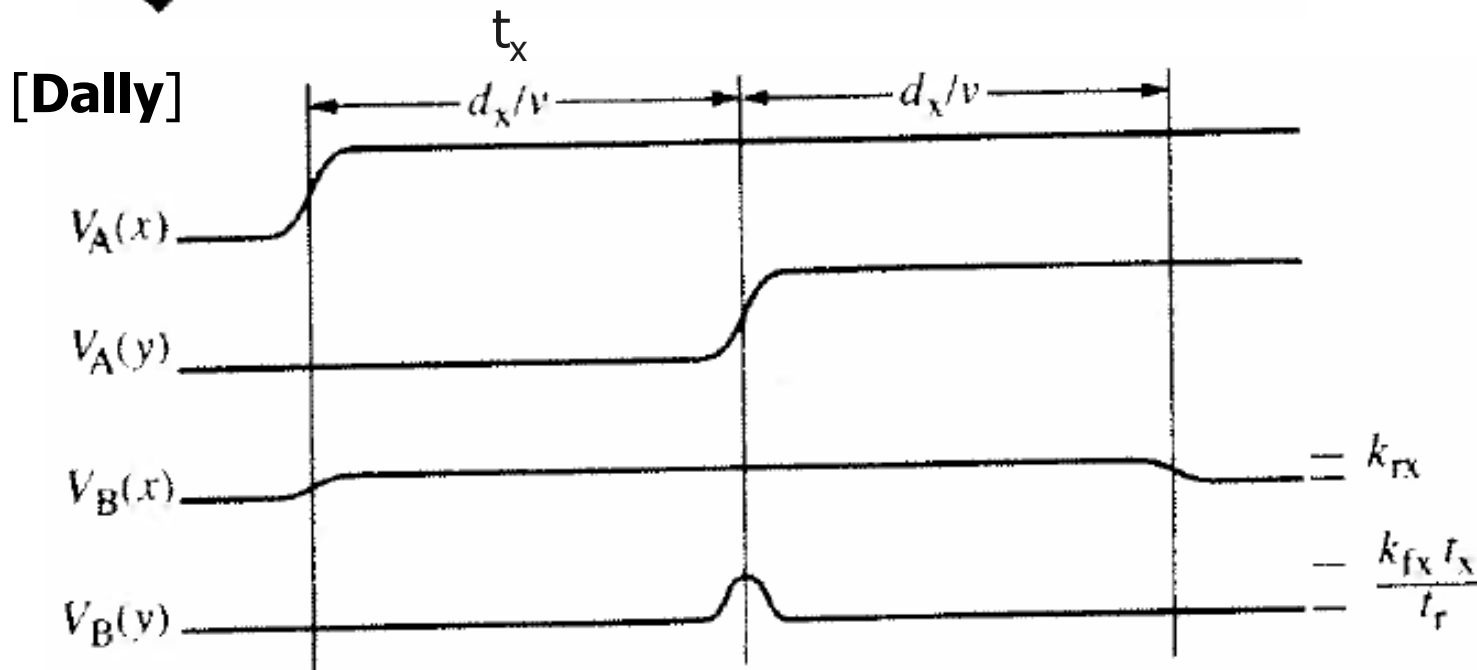Forward Coupling Coefficient  
 $k_{fx}$  (FEXT)



$$k_{rx} = \frac{(k_{cx} + k_{lx})}{4}$$


$$k_{fx} = \frac{(k_{cx} - k_{lx})}{2}$$

For derivation of  
 $k_{rx}$  and  $k_{fx}$ , see  
Dally 6.3.2.3



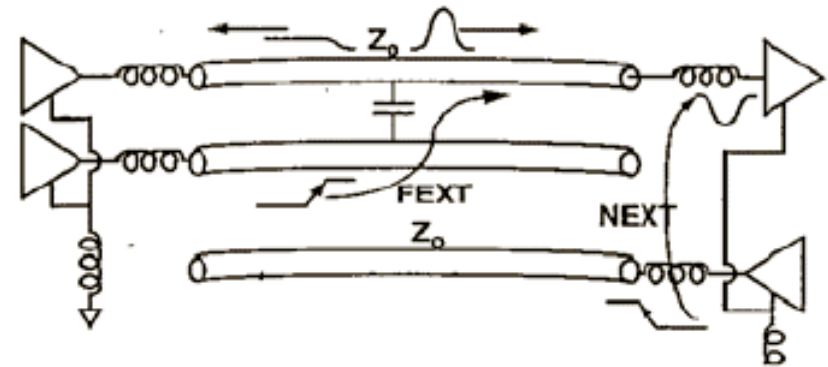
# Off-Chip Crosstalk

- Occurs mostly in package and board-to-board connectors
- FEXT is attenuated by channel response and has band-pass characteristic
- NEXT directly couples into victim and has high-pass characteristic




17" Server Channel Response

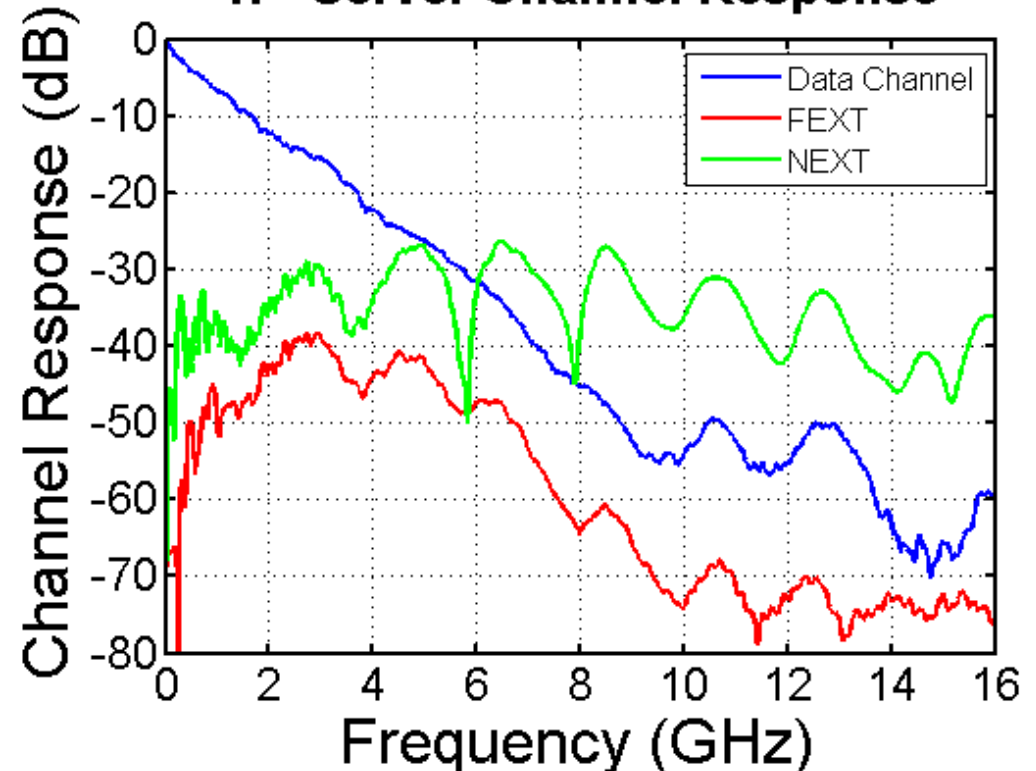
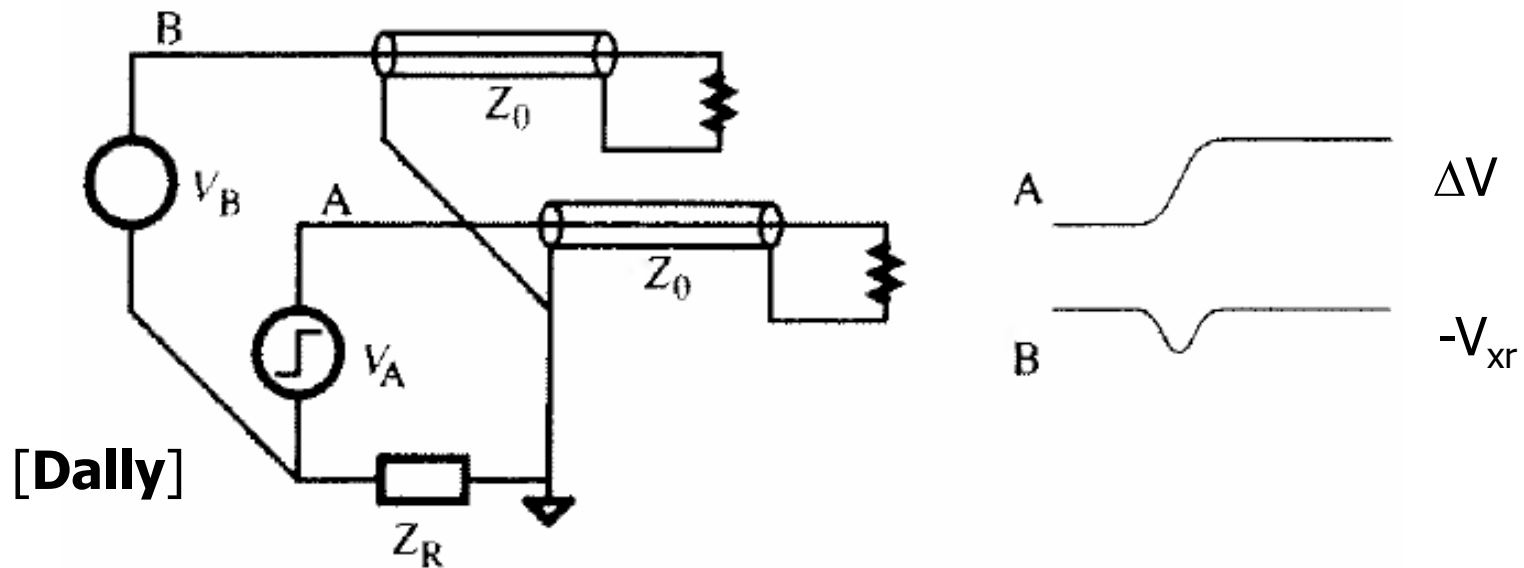
# Signal Return Crosstalk

- Shared return path with finite impedance
- Return currents induce crosstalk occurs among signals



$$\text{Return Crosstalk Voltage: } V_{xr} = \Delta V \frac{Z_R}{Z_0} = k_{xr} \Delta V$$

# Common Noise Sources


---

- Power supply noise
- Receiver offset
- Crosstalk
- Inter-symbol interference
- Random noise

# Inter-Symbol Interference (ISI)

- Previous bits residual state can distort the current bit, resulting in inter-symbol interference (ISI)

$$y^{(d_k)}(t) = c^{(d_k)}(t) * h(t)$$

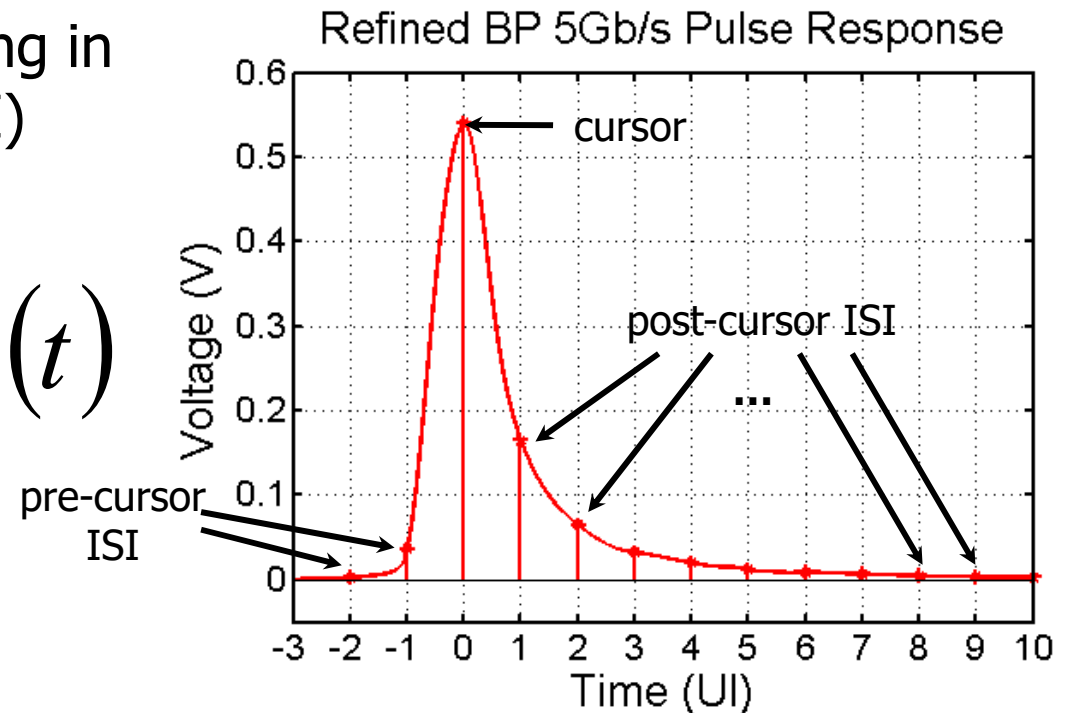



$y^{(1)}(t)$  sampled relative to pulse peak:

[... 0.003 0.036 0.540 0.165 0.065 0.033 0.020 0.012 0.009 ...]

$k = [ \dots -2 \quad 1 \quad 0 \quad 1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6 \quad \dots ]$

By Linearity:  $y^{(0)}(t) = -1 * y^{(1)}(t)$

# Peak Distortion Analysis Example

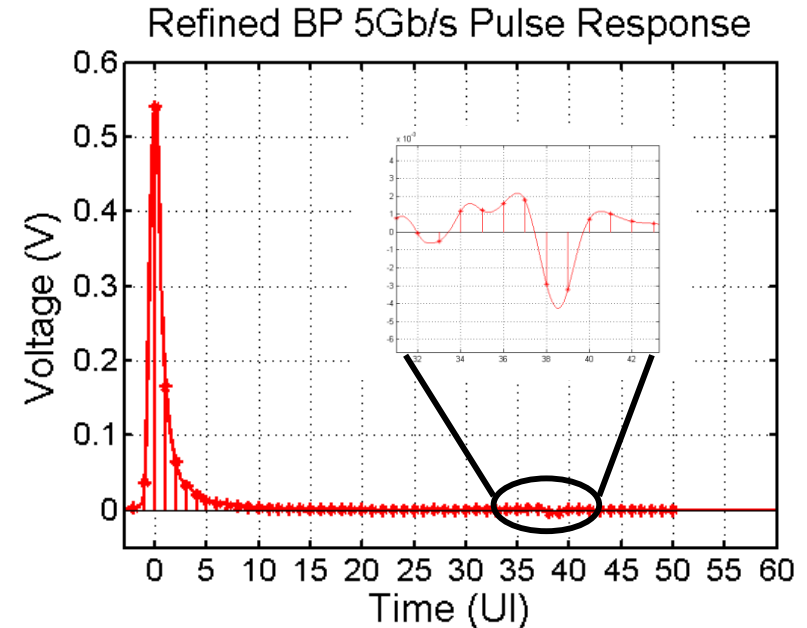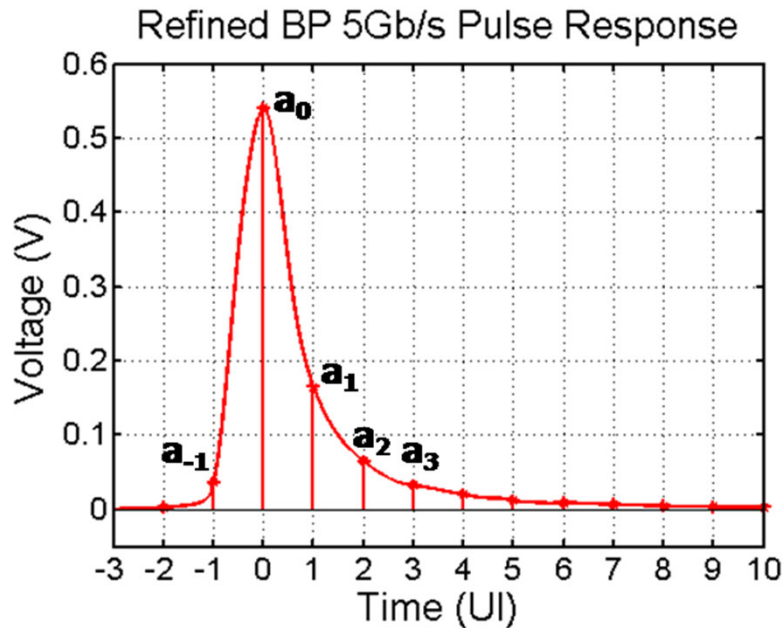


$$y_0^{(1)}(t) = 0.540$$

$$\sum_{\substack{k=-\infty \\ k \neq 0}}^{\infty} y^{(1)}(t - kT) \Big|_{y(t-kT) < 0} = -0.007$$


$$\sum_{\substack{k=-\infty \\ k \neq 0}}^{\infty} y^{(1)}(t - kT) \Big|_{y(t-kT) > 0} = 0.389$$
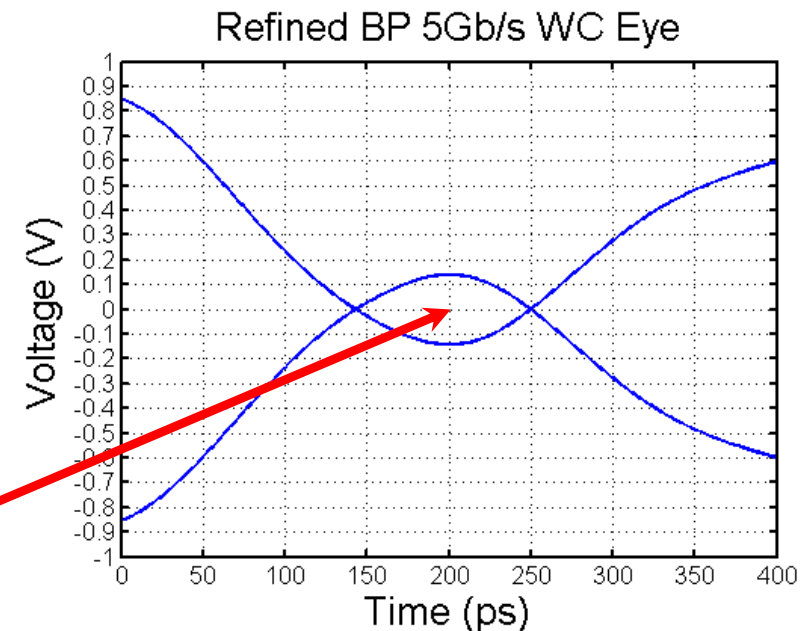
$$s(t) = 2(0.540 - 0.007 - 0.389) = 0.288$$



# Worst-Case Eye vs Random Data Eye

---




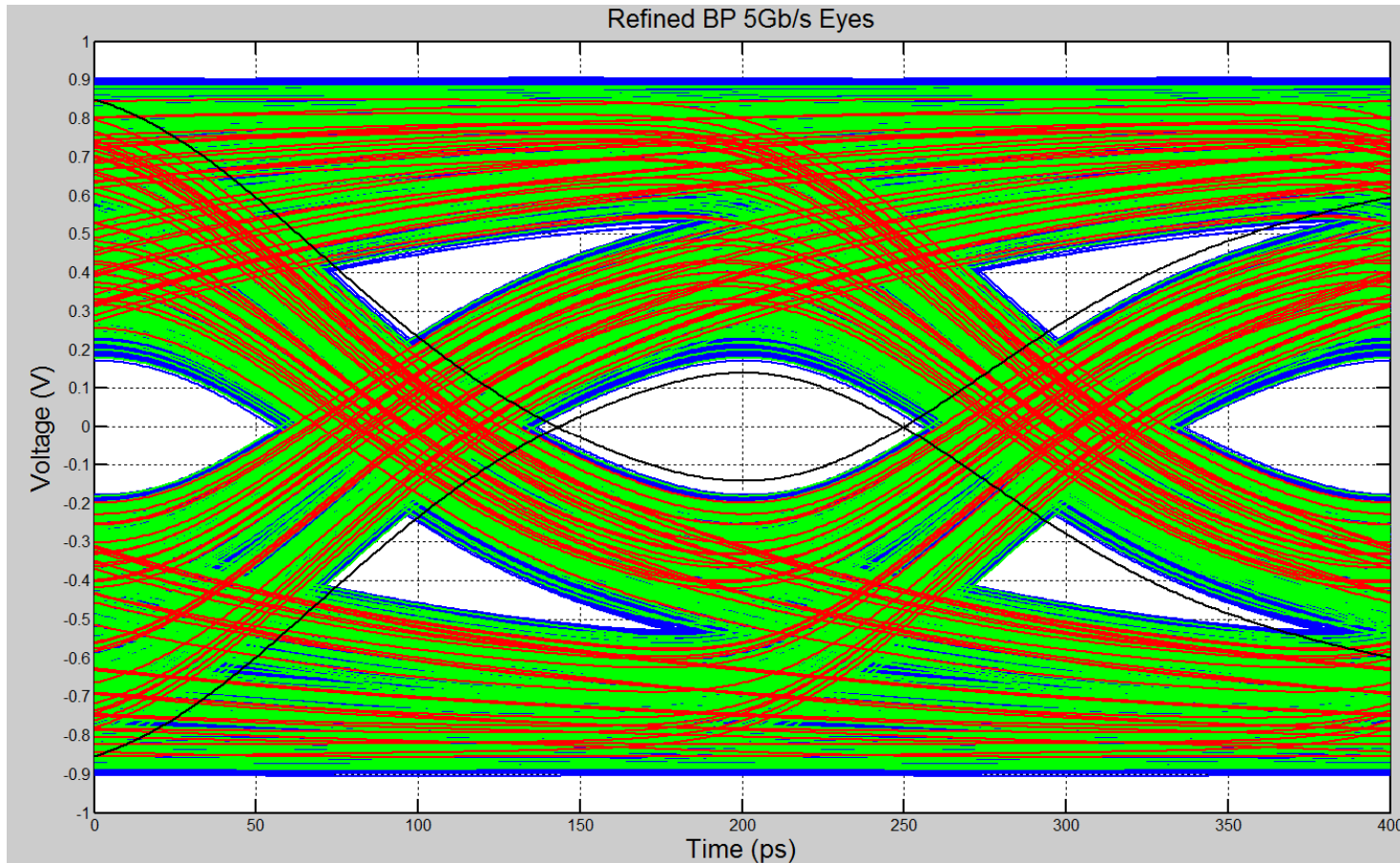


**Worst-Case Eye**  
**100 Random Bits**  
**1000 Random Bits**  
**1e4 Random Bits**


- Worst-case data pattern can occur at very low probability!
- Considering worst-case is too pessimistic
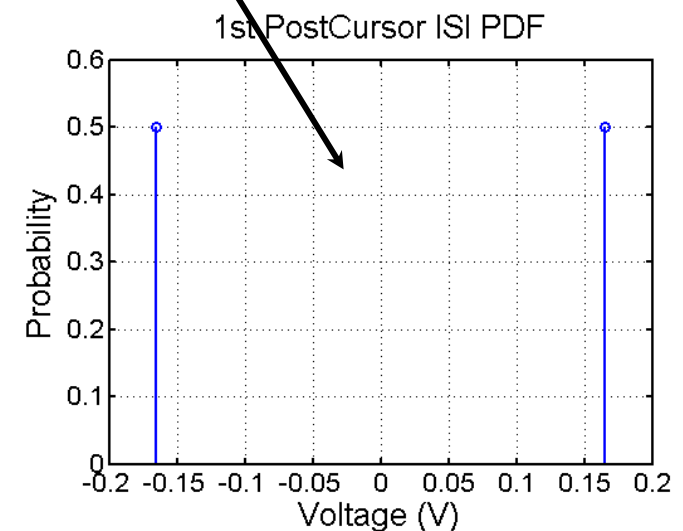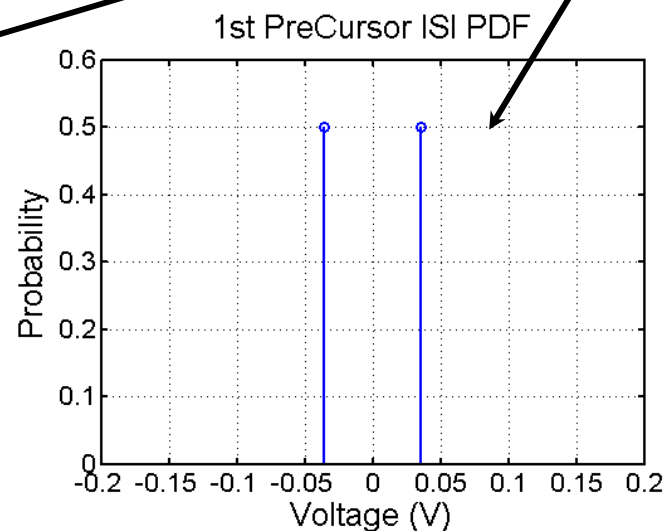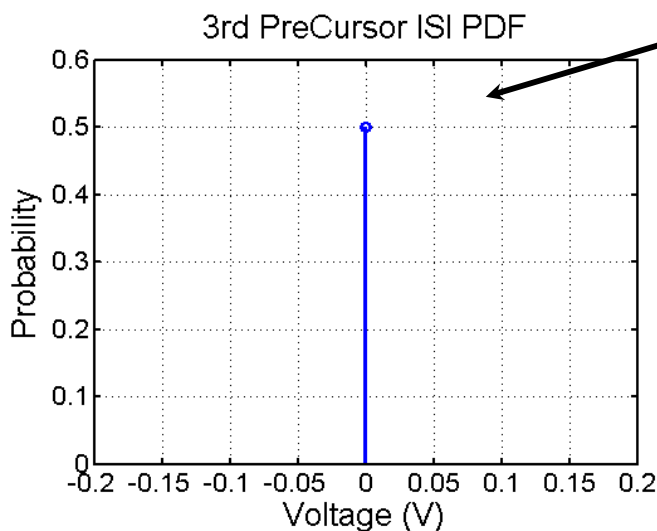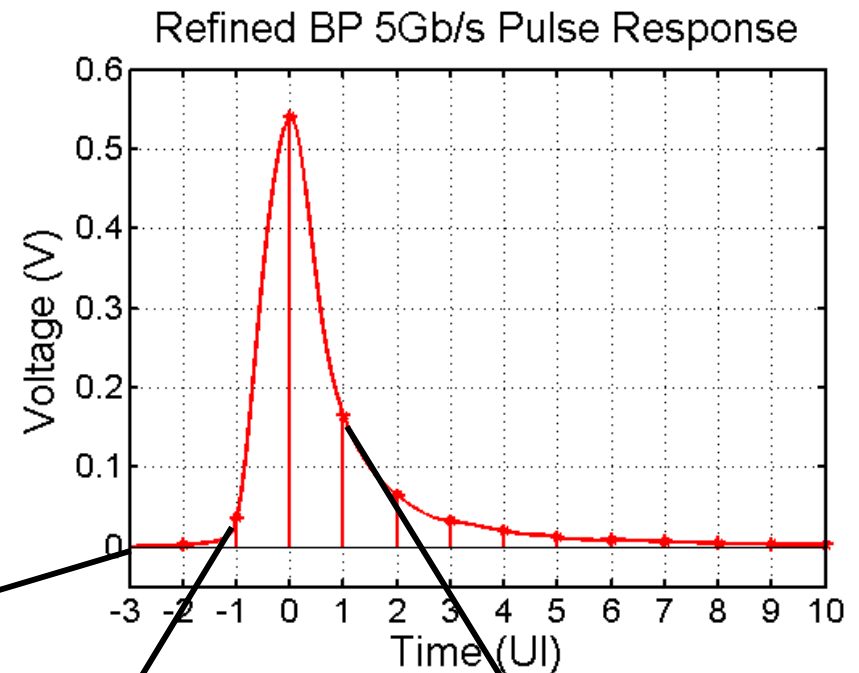
# Constructing ISI Probability Density Function (PDF)

- Using ISI probability density function will yield a more accurate BER performance estimate
- In order to construct the total ISI PDF, need to convolve all of the individual ISI term PDFs together
  - 50% probability of "1" symbol ISI and "-1" symbol ISI


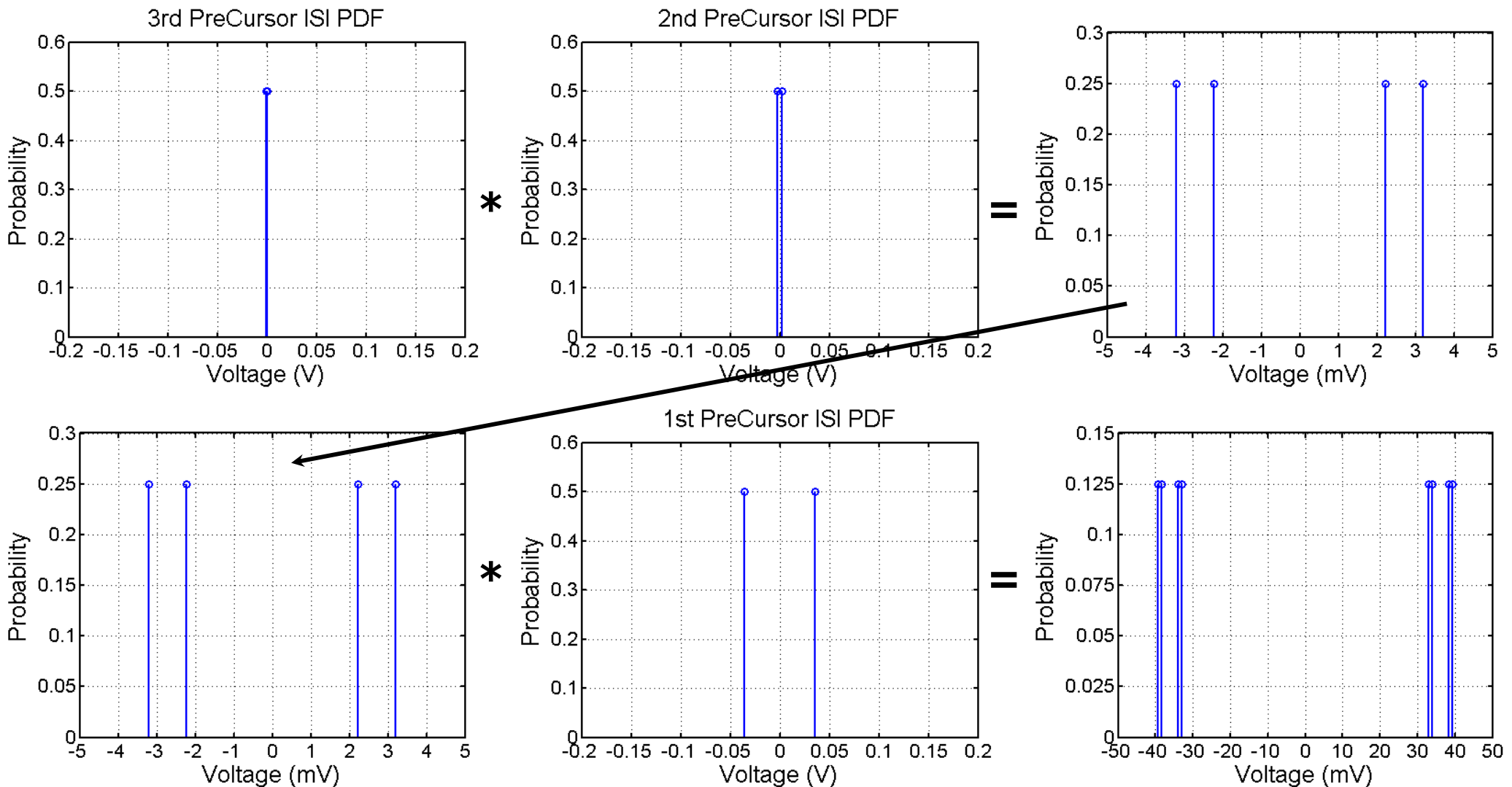
# Convolving Individual ISI PDFs Together




- Keep going until all individual PDFs convolved together




# Complete ISI PDF

---

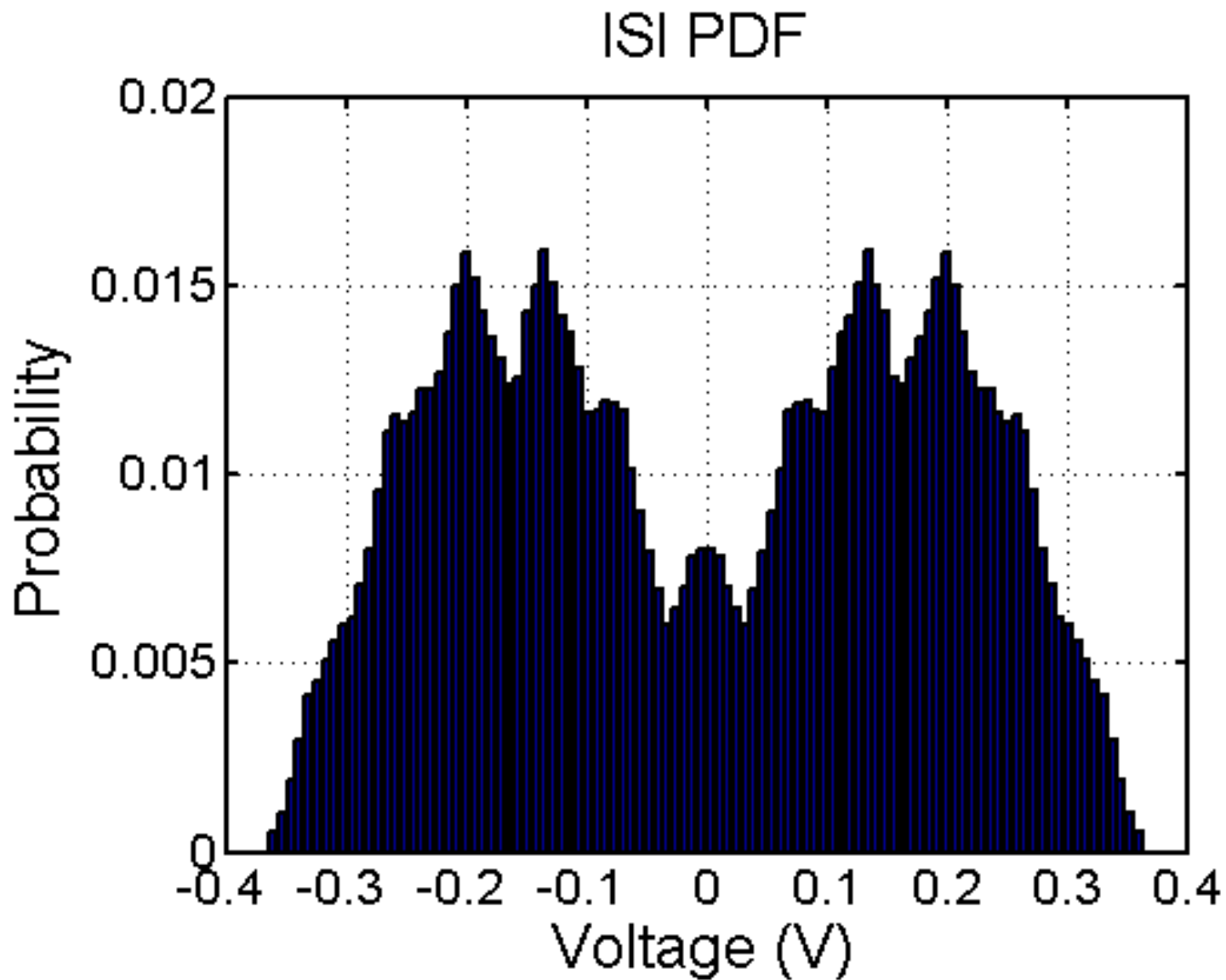

# Cursor PDF – Data 1


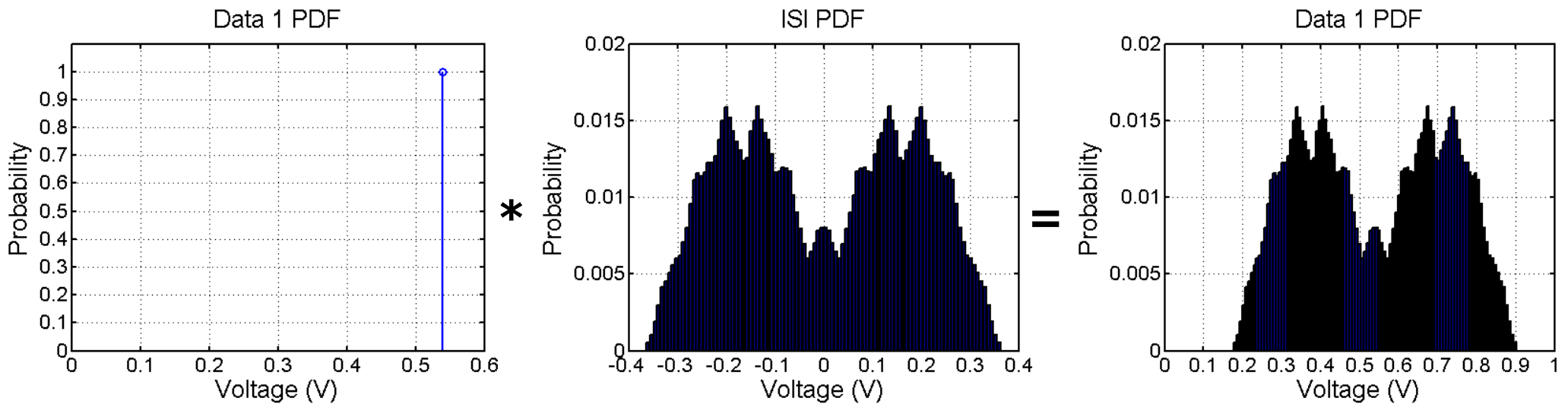


- Data 1 PDF is centered about the cursor value and varies from a maximum positive value to the worst-case value predicted by PDA
  - This worst-case value occurs at a low probability!





# Cursor Cumulative Distribution Function (CDF)

- For a given offset, what is the probability of a Data 1 error?
  - Data 1 error probability for a given offset is equal to the Data 1 CDF

$$BER(X) = \int_{-\infty}^X (PDF) dx$$

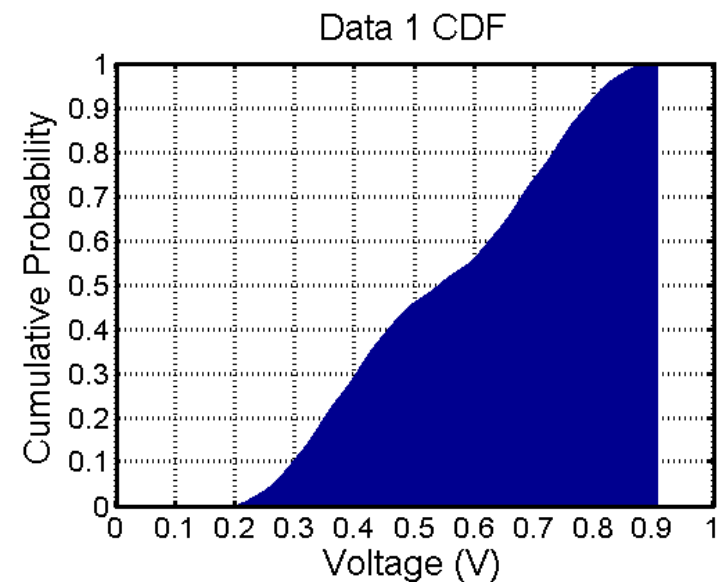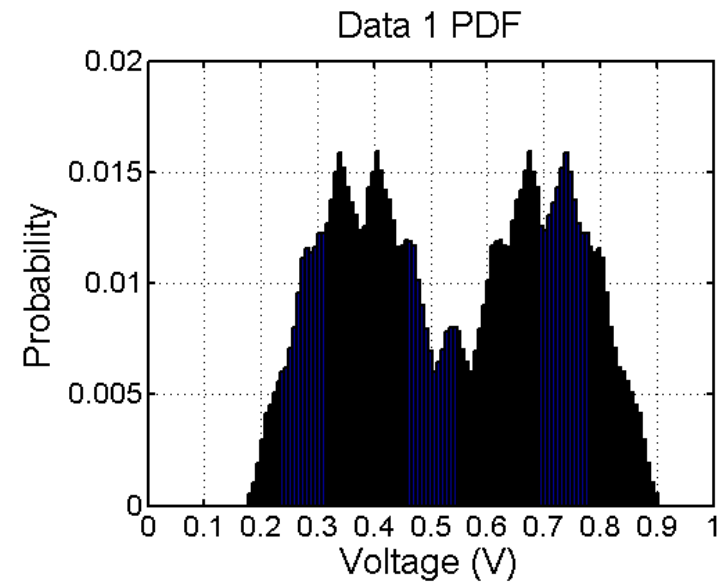


# Combining Cursor CDFs

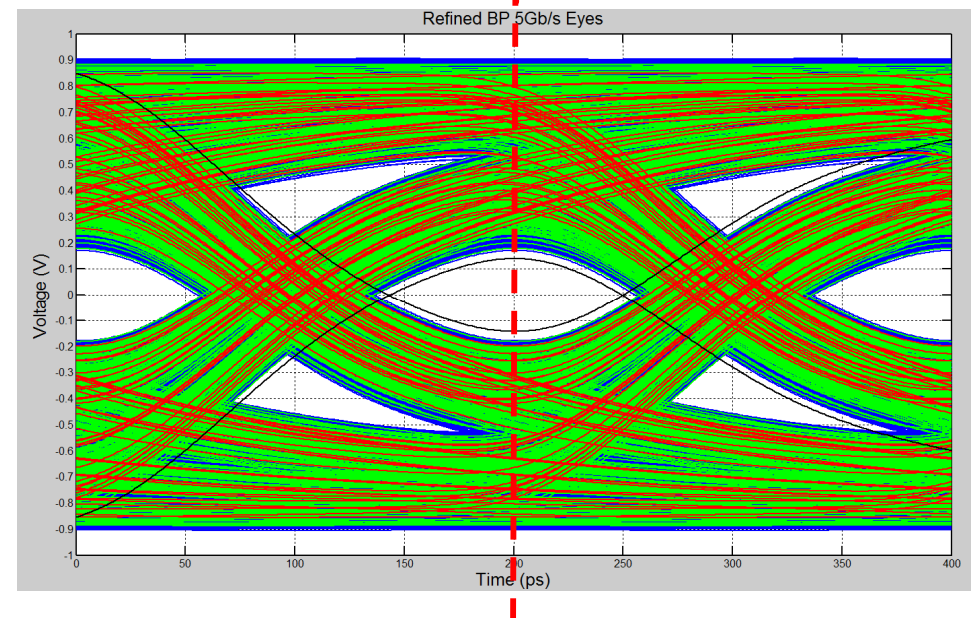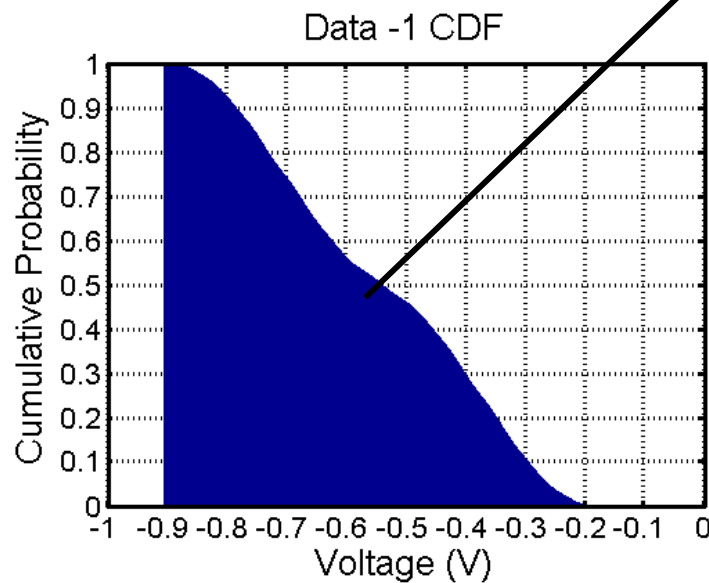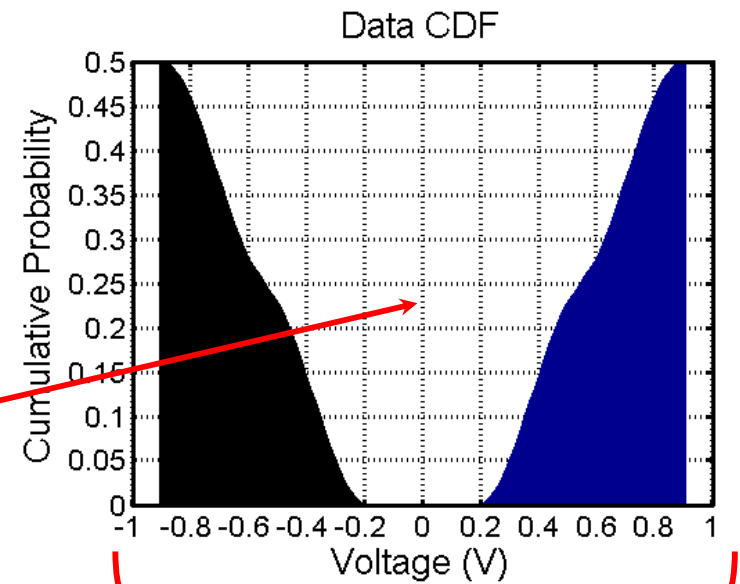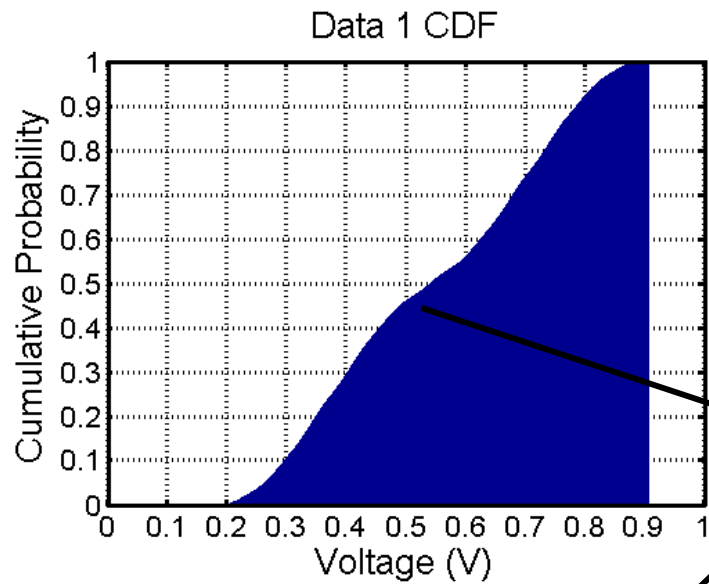
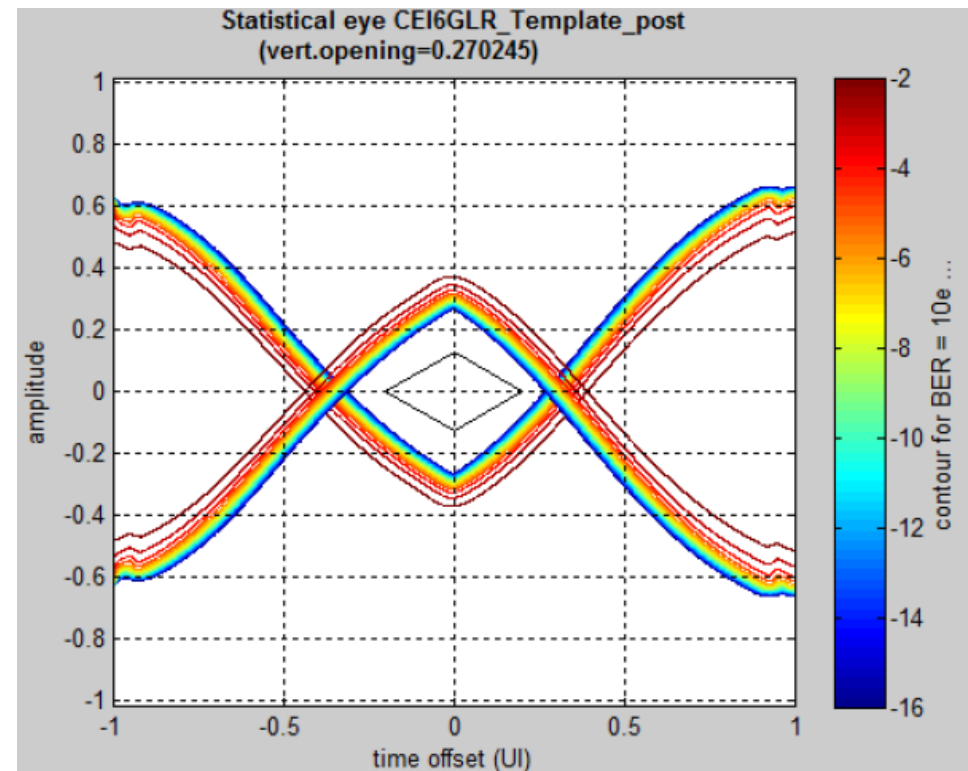
# Bit-Error-Rate (BER) Distribution Eye

- Statistical BER analysis tools use this technique to account for ISI distribution and also other noise sources
  - Example from Stateye
    - Note: Different channel & data rate from previous slides



# Common Noise Sources

---

- Power supply noise
- Receiver offset
- Crosstalk
- Inter-symbol interference
- Random noise

# Random Noise

---

- Random noise is unbounded and modeled statistically
  - Example: Circuit thermal and shot noise
- Modeled as a continuous random variable described by
  - Probability density function (PDF)
  - Mean,  $\mu$
  - Standard deviation,  $\sigma$


$$PDF = P_n(x), \quad \mu_n = \int_{-\infty}^{\infty} x P_n(x) dx, \quad \sigma_n^2 = \int_{-\infty}^{\infty} (x - \mu_n)^2 P_n(x) dx$$

# Gaussian Distribution


- Gaussian distribution is normally assumed for random noise
  - Larger sigma value results in increased distribution spread

$$P_n(x) = \frac{1}{\sqrt{2\pi}\sigma} e^{-\frac{(x-\mu_n)^2}{2\sigma^2}}$$

Gaussian Noise

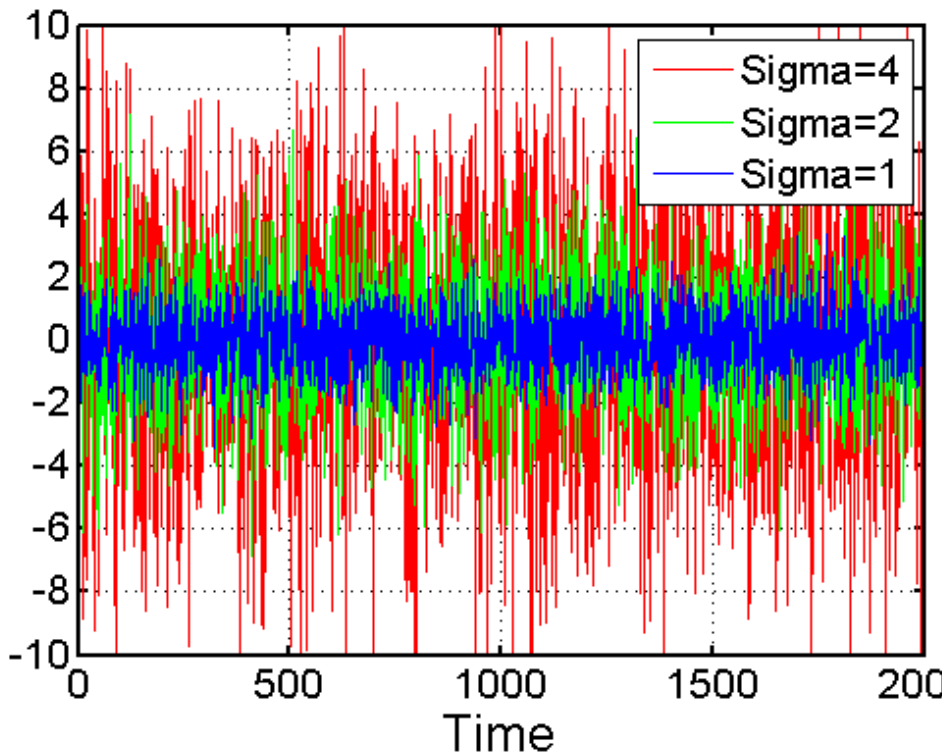


Gaussian PDFs

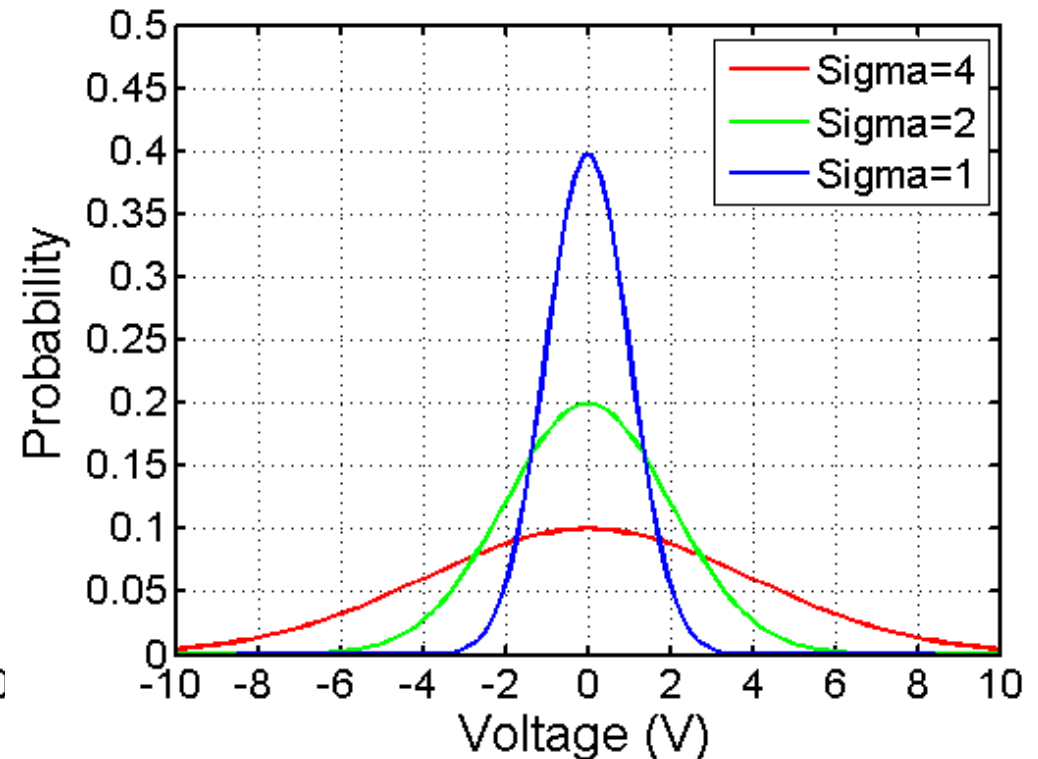



# Signal with Added Gaussian Noise

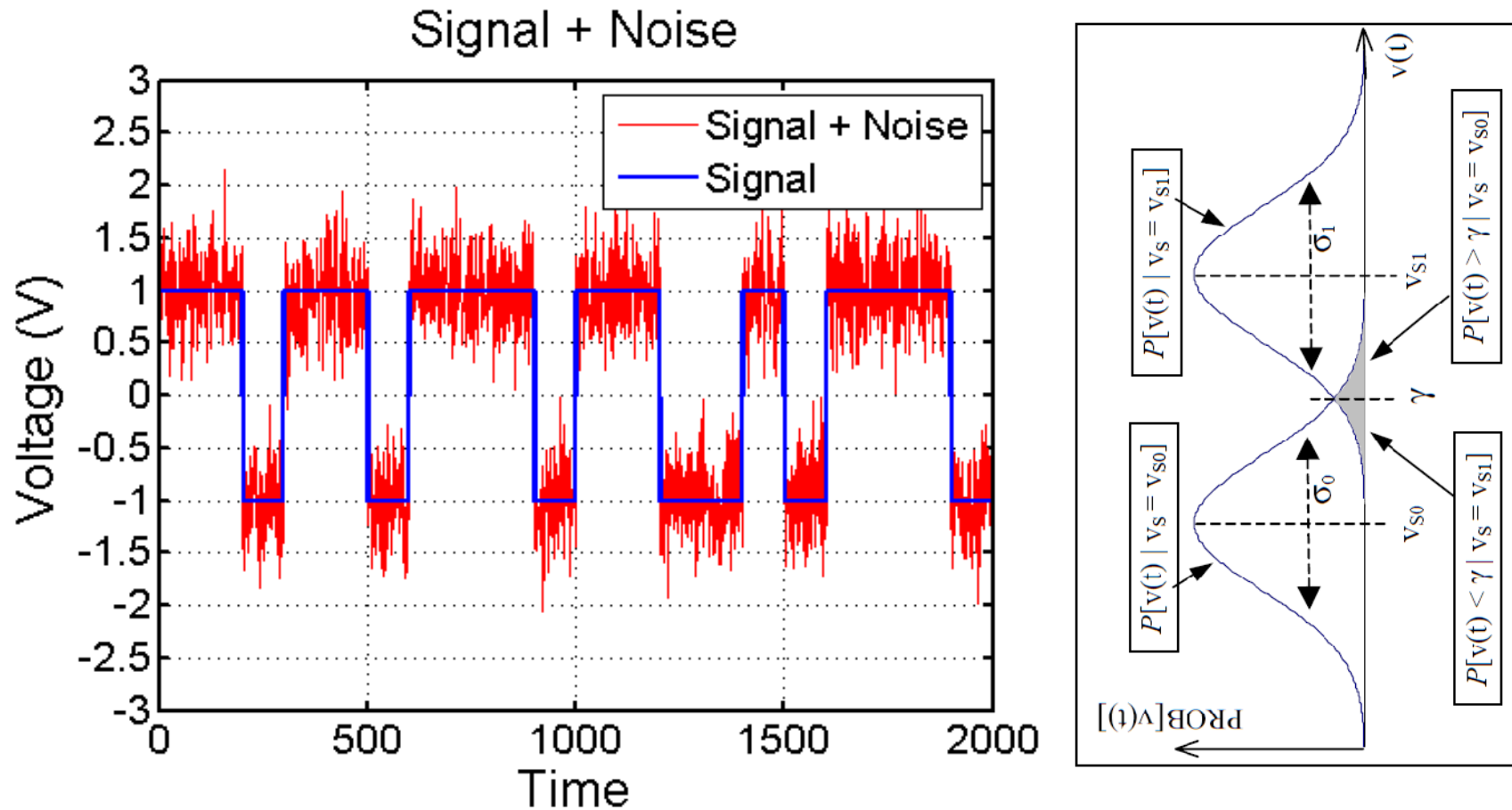


- Finite probability of noise pushing signal past threshold to yield an error
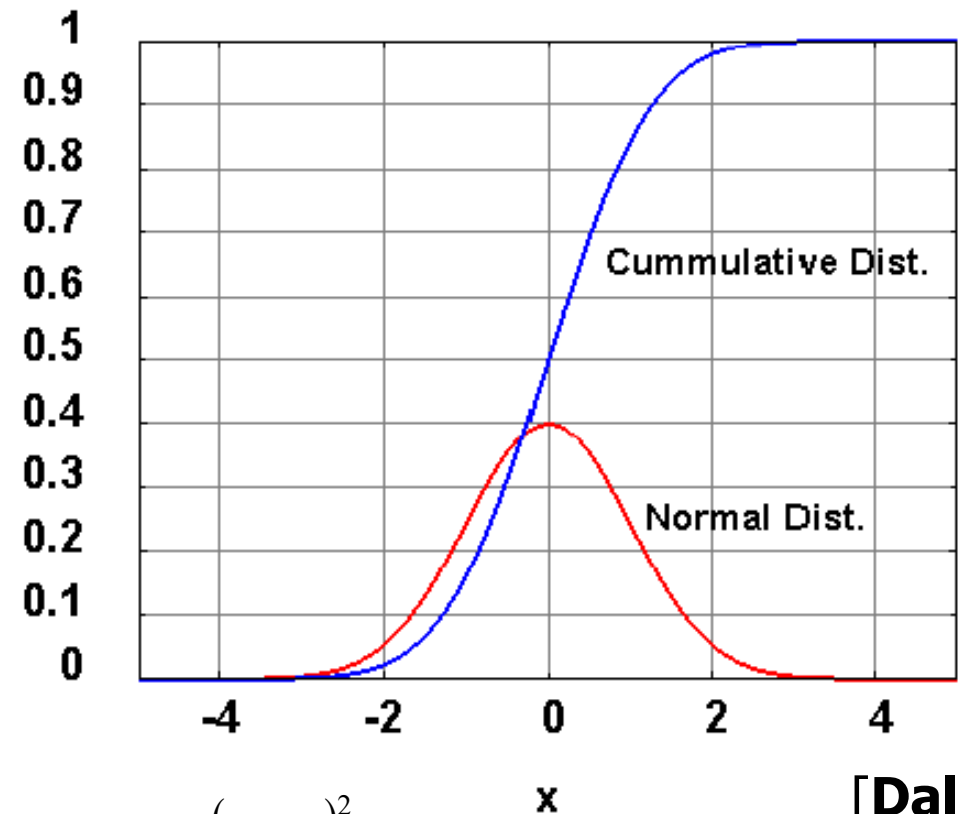
# Cumulative Distribution Function (CDF)

- The CDF tells what is the probability that the noise signal **is less than or equal to** a certain value

Standard Normal & Cumulative Distributions



[Dally]

$$\Phi_n(x) = \int_{u=-\infty}^x P_n(u) du = \int_{u=-\infty}^x \frac{1}{\sqrt{2\pi}\sigma} e^{-\frac{(u-\mu_n)^2}{2\sigma^2}} du$$

# Error and Complimentary Error Functions

---

- Error Function:

$$\text{erf}(x) = \frac{2}{\sqrt{\pi}} \int_{u=0}^x \exp(-u^2) du$$

- Relationship between normal CDF (0,1) and Error Function:

$$\Phi(x) = \frac{1}{2} \left[ 1 + \text{erf} \left( \frac{x}{\sqrt{2}} \right) \right]$$


- The complementary error function gives the probability that the noise will exceed a given value

$$\begin{aligned} Q(x) &= 1 - \Phi(x) = \frac{1}{2} \left[ 1 - \text{erf} \left( \frac{x}{\sqrt{2}} \right) \right] \\ &= \frac{1}{2} \text{erfc} \left( \frac{x}{\sqrt{2}} \right) \end{aligned}$$

$$Q_{\mu\sigma}(x) = \frac{1}{2} \text{erfc} \left( \frac{x - \mu}{\sigma\sqrt{2}} \right)$$

# Bit Error Rate (BER)

- Using erfc to predict BER:

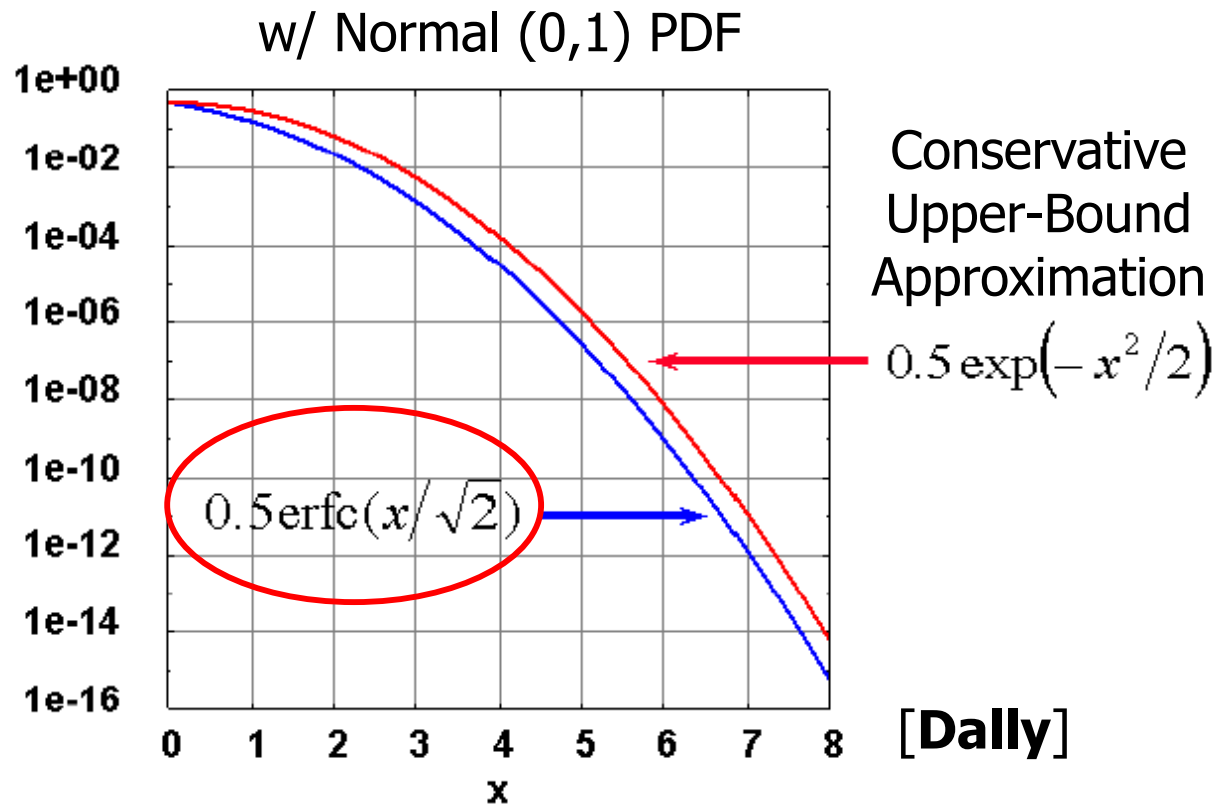

- Need a symbol of about  $7\sigma$  for  $\text{BER}=10^{-12}$ 
  - Peak-to-peak value will be  $2x$  this

# Noise Source Classifications

---


- Determining whether noise source is
  - Proportional vs Independent
  - Bounded vs Statistical
- is important in noise budgeting

	Proportional	Independent
Bounded	Residual ISI Crosstalk	RX Offset RX Sensitivity Power Supply Noise
Statistical	Large-Channel Crosstalk	Random Noise

# Noise Budget Example

- Peak TX differential swing of  $400\text{mV}_{\text{ppd}}$  equalized down 10dB
  - $\pm 200\text{mV} \rightarrow \pm 63\text{mV}$

Parameter	$K_n$	RMS	Value (BER= $10^{-12}$ )
Peak Differential Swing			0.4V
RX Offset + Sensitivity			5mV
Power Supply Noise			5mV
Residual ISI	0.05		20mV
Crosstalk	0.05		20mV
Random Noise		1mV	14mV
Attenuation	10dB = 0.684		0.274V
Total Noise			0.338V
Differential Eye Height Margin			62mV

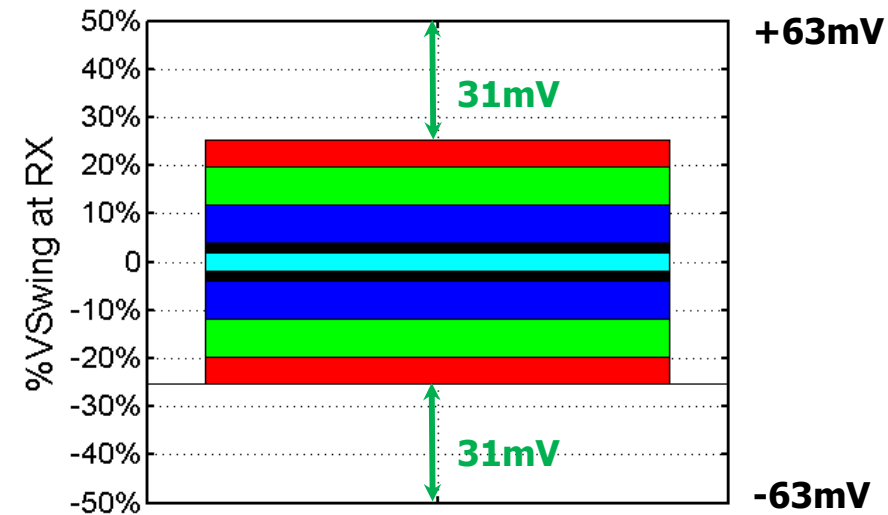

- Conservative analysis
  - Assumes all distributions combine at worst-case
- Better technique is to use statistical BER link simulators

# Next Time

---

- Timing Noise
- BER Analysis Techniques