


PRBS generation and Return Loss simulation

EE689 High Speed I/O

Dr Samuel Palermo

Library Setting

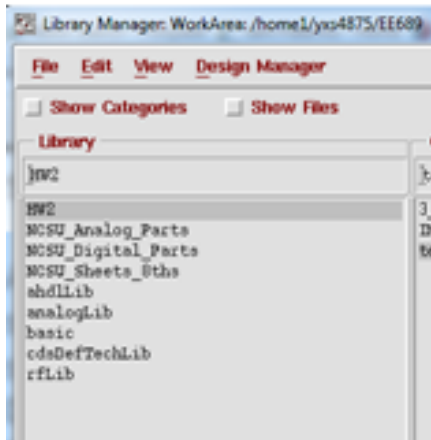Make Sure you see the ahdlLib and rLib in library Manager






```
eesuri:/home1/yxs4875/EE689>cat cds.lib
INCLUDE /baby/cadence/ic50/local/cdssetup/cds.lib

DEFINE rLib $CDS_INST_DIR/tools/dfII/samples/artist/rLib
DEFINE ahdlLib $CDS_INST_DIR/tools/dfII/samples/artist/ahdlLib
DEFINE analogLib $CDS/tools/dfII/etc/cdslib/artist/analogLib
DEFINE HW2 /home1/yxs4875/EE689/HW2
eesuri:/home1/yxs4875/EE689>
```



PRBS Generator

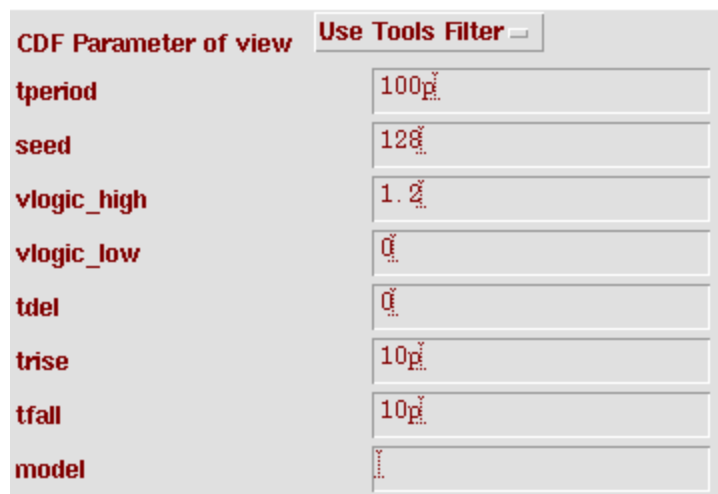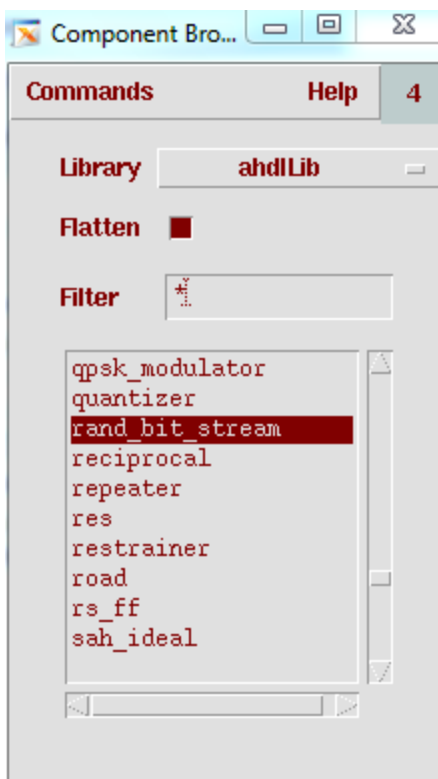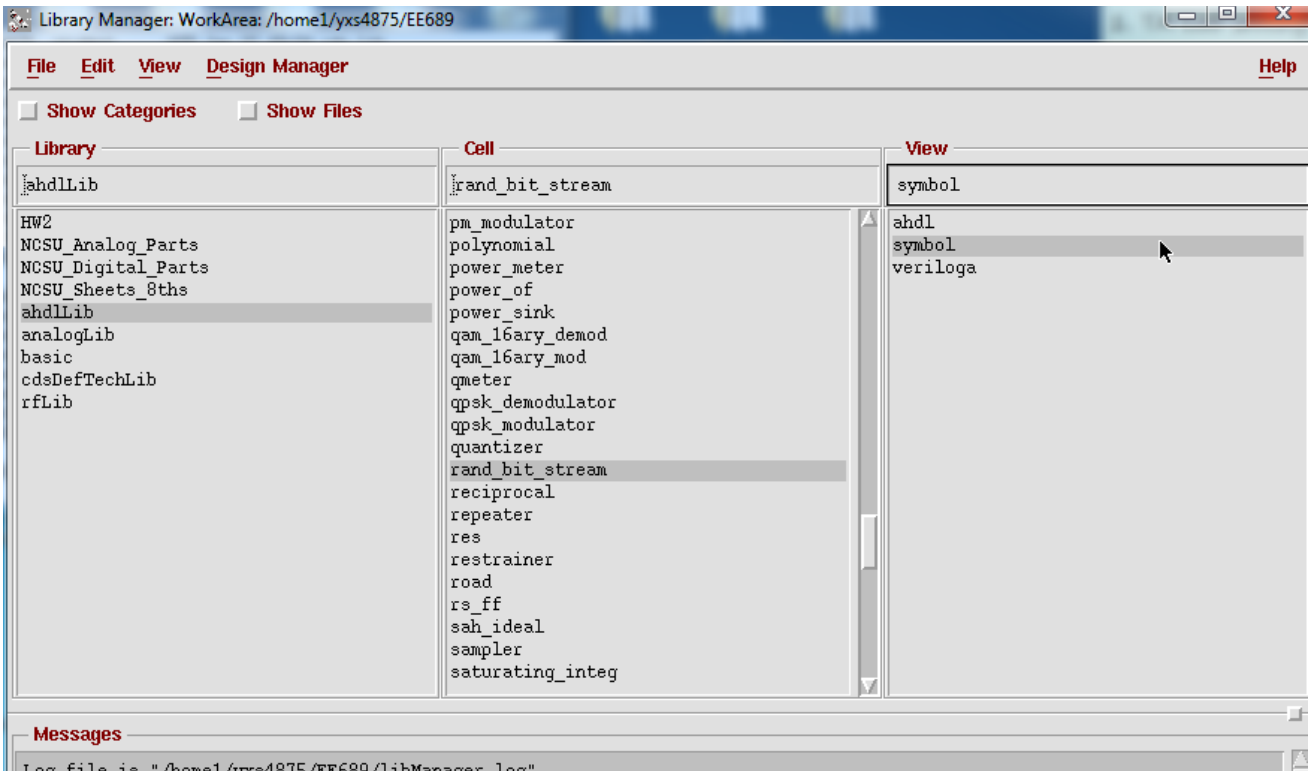We can find the rand_bit_stream in ahdlLib to generate prbs.
For setting, Tperiod is your 1UI time, and more detail we can see figures.




PRBS Generator + Channel

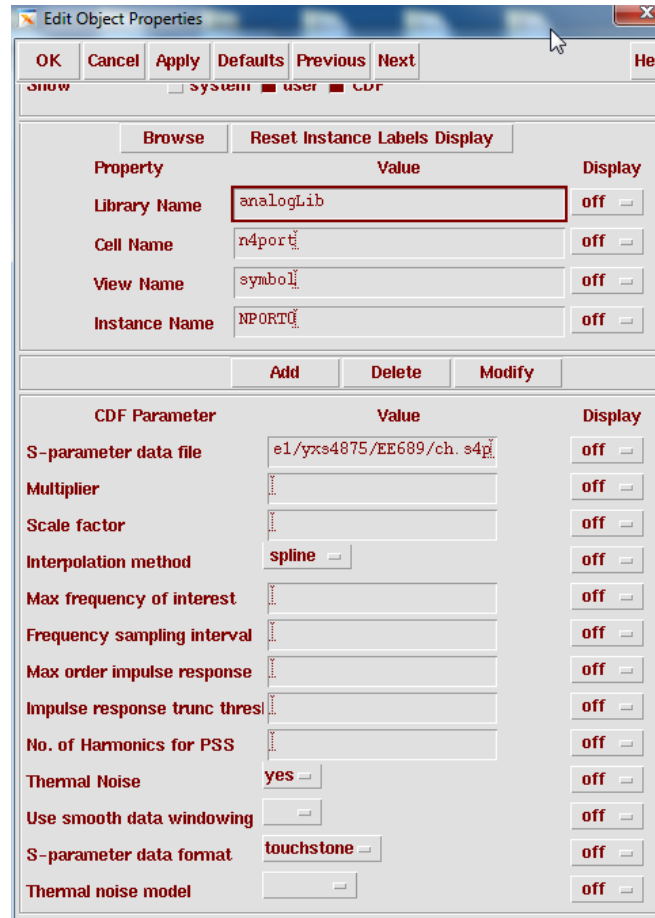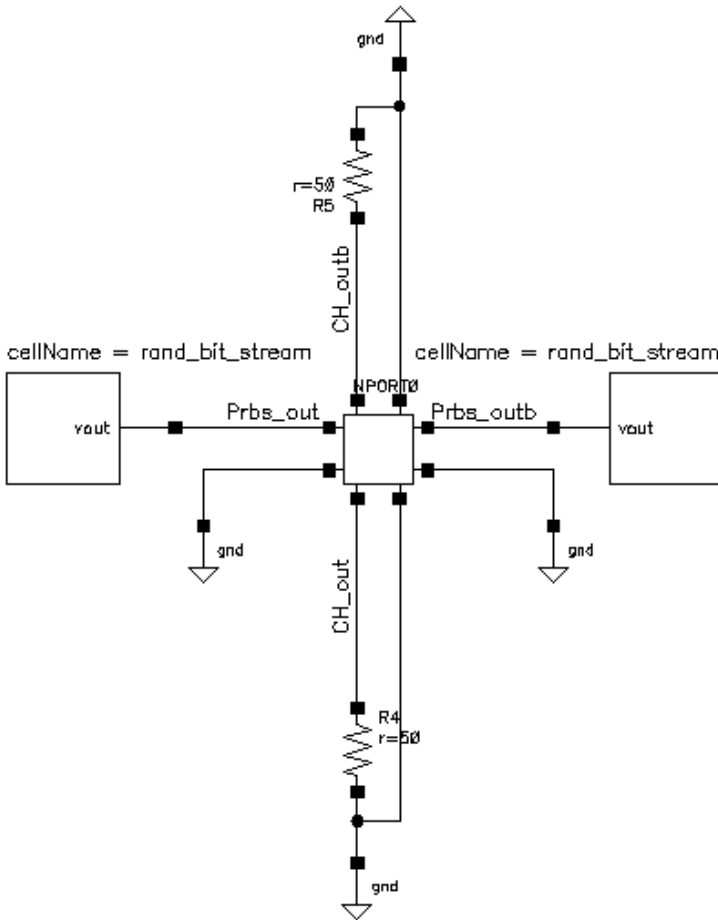Test bench for Transient Simulation with *.s4p files




To do transient simulation with touchstone file, we need to n4port model in analogLib. Actually channel name is peters_01_0605_B14_thru.s4p which you can download in class web site, but I change the name ch.s4p for convenient in here. Port 1 and 3 will be input and port 2 and 4 are output. We have to terminate with 50 ohms resistor in the output port.

10Gbs

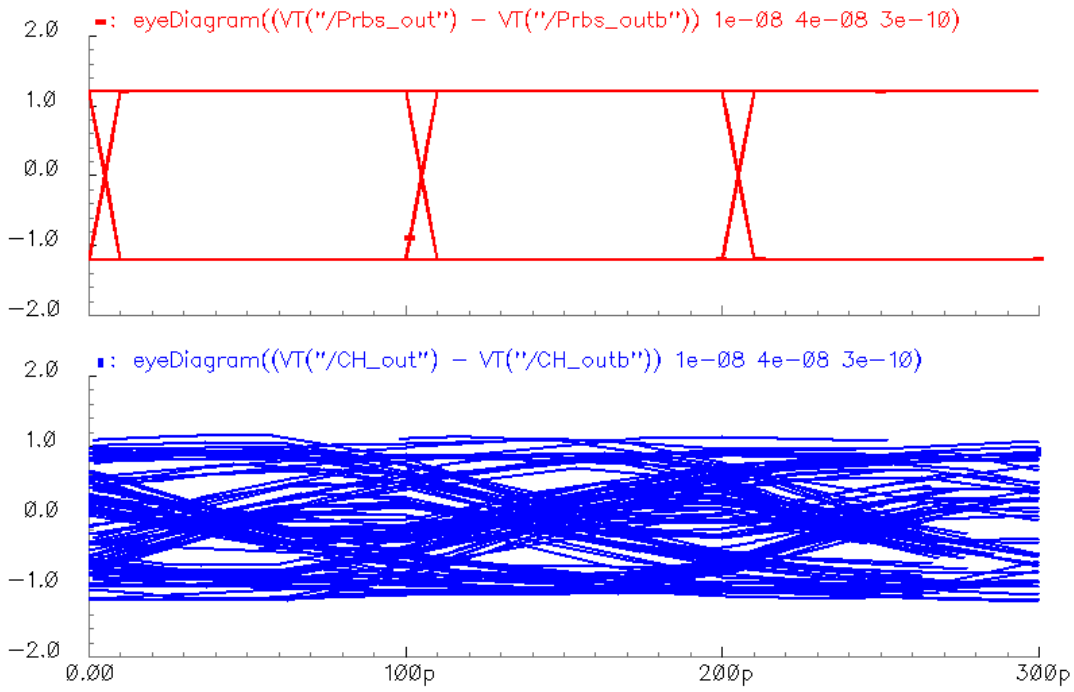


5Gbs

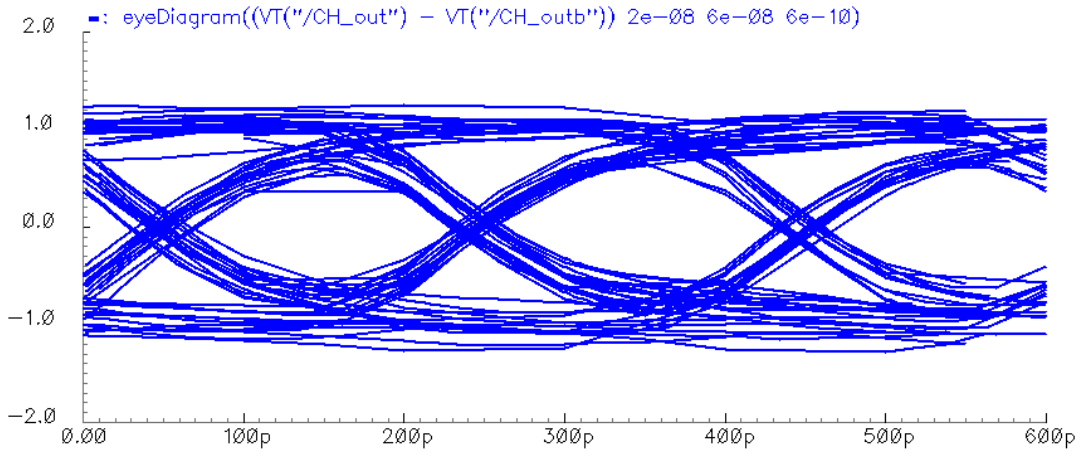

High Frequency Diff mode Return Loss

- ❑ Increased signal integrity
- ❑ Some standards require high performance RL Specification

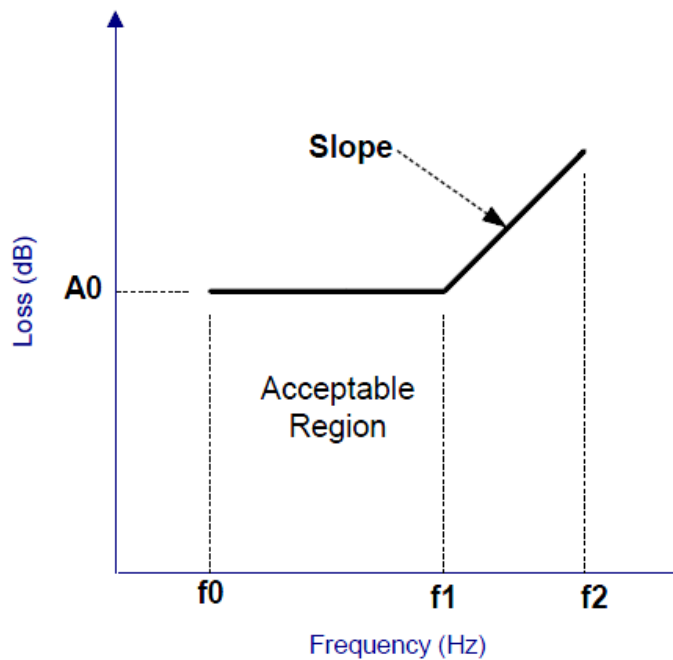
Driver and input differential return loss – CEI – SR short reach interface




| Parameter | Value | Units |
|-----------|------------------------------|--------|
| A0 | -8 | dB |
| f0 | 100 | MHz |
| f1 | $T_Baud \times \frac{3}{4}$ | Hz |
| f2 | $T_Baud \times \frac{3}{2}$ | Hz |
| Slope | 16.6 | dB/dec |

The differential return loss shall be better than A0 from f0 to f1 and better than $A0 + Slope \cdot \log_{10}(f/f1)$ where f is the frequency from f1 to f2.


Library for Balun

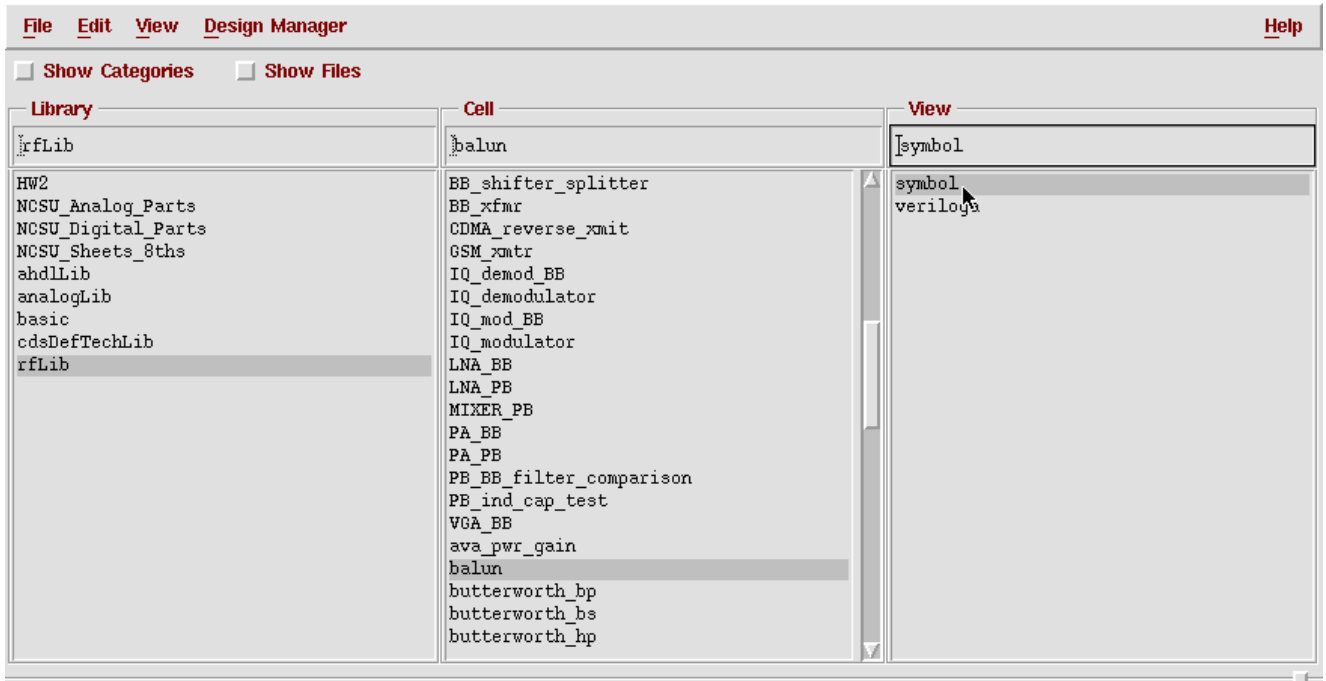

Test bench for RL measurement

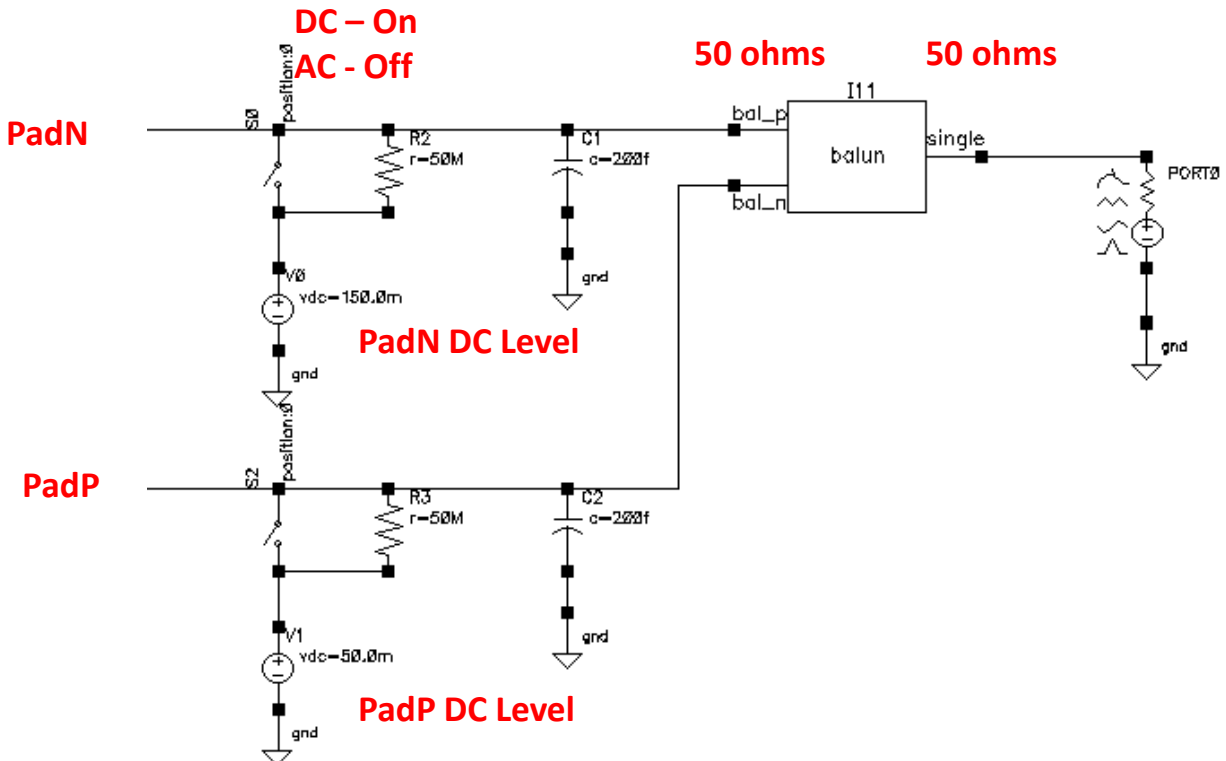

□ Voltage mode RL measurement

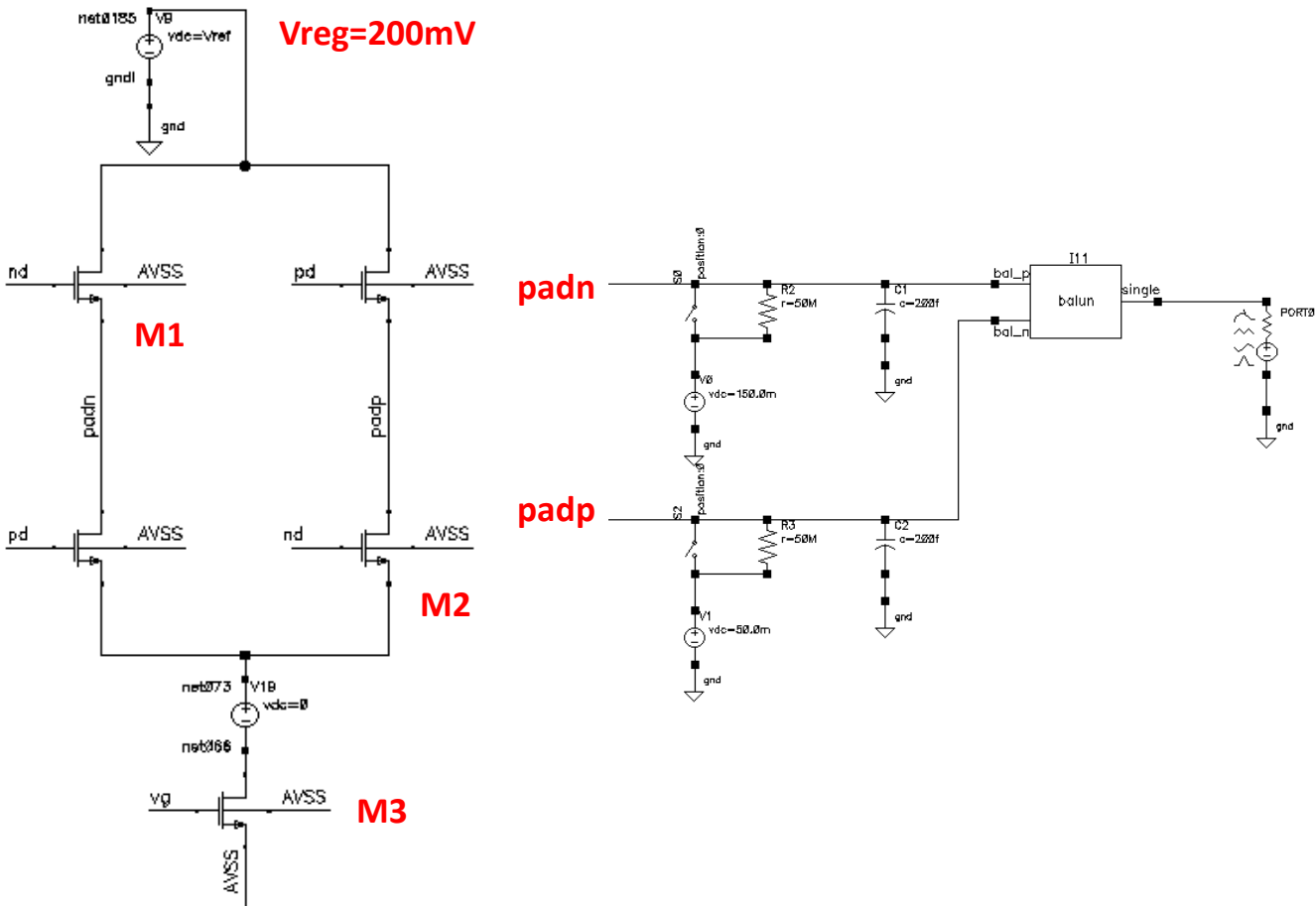

When nd is high, TR M1 sets 50ohm termination Resistor, and both M2 and M3 set 50ohm termination Resistor. As we can see, RL performance degrade at high frequency due to pad cap and parasitic cap.

