 


# ECEN 449 – Microprocessor System Design



Verilog

## Objectives of this Lecture Unit

- Get a feel for the basics of Verilog
  - The focus of this unit will be along two separate but equally relevant axes
    - We will cover the semantics of Verilog and different modeling styles
    - Also we will cover syntax issues. For this portion, additional resources are also provided on the website.
  - In general Verilog is quite rich, and therefore, there are many ways to achieve the same design goal
    - We will focus on the syntax that is most common, especially from a synthesizability point of view.

# Hardware Description Languages (HDLs)

- What is a HDL, why is it useful
- The Verilog HDL
- Modelling a simple circuit in Verilog
  - Gate level
  - Dataflow
  - Procedural
  - Synthesizable Verilog
- Testbenches
- Syntax coverage

# Hardware Description Language (HDLs)

- A HDL is a programming language which is tuned to describe hardware
- HDLs allow us to design and simulate a design at a higher level of abstraction
  - Result = higher designer productivity
- HDLs also have accompanying synthesis tools which allow the designer to obtain an implementation from HDL code.
  - Further improvement in designer productivity
- FPGA based design flows use HDLs heavily!

## Common HDLs

- There are mainly two HDLs in use today
  - Verilog HDL
  - VHDL
- VHDL is the somewhat more common
  - Standard developed by US DoD
  - VHDL = (Very High Speed Integrated Circuit) HDL
- We choose Verilog for this class because
  - It is easier to use and teach
  - Resembles “C” and hence easier to learn.
- Which one is “better”?
  - This is the topic of much debate

## Verilog HDL

- Verilog constructs are use defined *keywords*
  - Examples: **and**, **or**, **wire**, **input**, **output**
- One important construct is the **module**
  - Modules have inputs and outputs
  - Modules can be built up of Verilog primitives or of user defined submodules.

# A Structural Design - XOR

```
module xor_gate ( out, a, b );  
  input  a, b;  
  output out;  
  wire  abar, bbar, t1, t2;
```

## Built-in gates

```
  not invA (abar, a);  
  not invB (bbar, b);  
  and and1 (t1, a, bbar);  
  and and2 (t2, b, abar);  
  or  or1 (out, t1, t2);
```

endmodule

## Instance name

- Composition of primitive gates to form more complex module


module name

port list

declarations

statements

interconnections

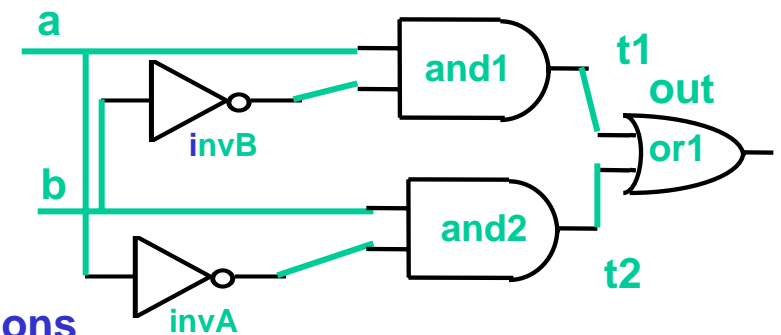

## Another Simple Circuit (in Structural Verilog)

 


Fig. 3-37 Circuit to Demonstrate HDL

```
module smpl_circuit(A,B,C,x,y);  
  input A,B,C;  
  output x,y;  
  wire e;  
  and g1(e,A,B);  
  not g2(y, C);  
  or g3(x,e,y);  
endmodule
```



# Structural Verilog

- Just specifies primitive gates and wires
  - In other words, the structure of a logical netlist
- Useful if you know exactly what logic you want to generate
  - Not useful for large designs, where we want to specify the design at a higher level of abstraction
    - It is crucial to design at a higher level of abstraction in this case, since structural design would be tedious and error prone
  - In such a case, we will describe the circuit at a high level of abstraction, and let the CAD tools realize the detailed design (by performing the steps of synthesis, mapping, placement+routing, and generation of the netlist (in an FPGA, this is the bitgen file))
  - In special cases, delay or area-critical sub-blocks can be designed in structural manner, while the rest of the logic could be at a higher level of abstraction (typically described in the behavioral fashion).

## Simple Circuit – Comments

- The module starts with **module** keyword and finishes with **endmodule**.
- Internal signals are named with **wire**.
- Comments follow `//`
- **input** and **output** are ports. These are placed at the start of the module definition.
- Each statement ends with a semicolon, except **endmodule**.

## Adding Delays

- To simulate a circuit's real world behaviour it is important that propagation delays are included.
- The units of time for the simulation can be specified with **timescale**.
  - Default is 1ns with precision of 100ps
- Component delays are specified as #(delay)
- BUT REMEMBER – these delays will NOT synthesize.
  - Useful only for simulation and verification of your design.

## Simple Circuit with Delay

```

module
circuit_with_delay
(A,B,C,x,y);

  input A,B,C;

  output x,y;

  wire e;

  and #(30) g1(e,A,B);
  or #(20) g3(x,e,y);
  not #(10) g2(y,C);

endmodule

```

 


Fig. 3-37 Circuit to Demonstrate HDL

Time (ns)	Input A B C	Output y e x
0	0 0 0	1 0 1
0	1 1 1	1 0 1
10	1 1 1	0 0 1
20	1 1 1	0 0 1
30	1 1 1	0 1 0
40	1 1 1	0 1 0
50	1 1 1	0 1 1

# Structural Model

- Built-in gate primitives:

`and, nand, nor, or, xor, xnor, buf, not, bufif0, bufif1, notif0, notif1`

- Usage:

`nand (out, in1, in2);` 2-input NAND without delay

`and #2 (out, in1, in2, in3);` 3-input AND with 2 t.u. delay

`not #1 N1(out, in);` NOT with 1 t.u. delay and instance name

`xor X1(out, in1, in2);` 2-input XOR with instance name

## Dataflow modelling

- Another level of abstraction is to model dataflow.
- In dataflow models, signals are continuously assigned values using the **assign** keyword.
- **assign** can be used with Boolean expressions.
  - Verilog uses **&** (and), **|** (or), **^** (xor) and **~** (not)
- Logic expressions and binary arithmetic are also possible.

```
assign #10 out = i1 & i2;
```

- Left hand side must be a net of some kind (scalar or vector), not a register
- Right hand side can be registers, nets.
- Continuous assignments are **always** active. Execution hard to trace
- They are evaluated whenever a right hand side operand changes value
- Delays (inertial) can be added to represent component delays
- LHS evaluates when there is an event on the RHS (therefore independent of ordering of **assign** statements in the code)

## Simple Circuit Boolean Expression

 


Fig. 3-37 Circuit to Demonstrate HDL

$$x = A.B + \bar{C}$$

$$y = \bar{C}$$

## Dataflow Description of Simple Circuit

```
//Circuit specified with Boolean equations
```

```
module circuit_bln (x,y,A,B,C);
```

```
    input A,B,C;
```

```
    output x,y;
```

```
    assign x = (A & B) | ~C;
```

```
    assign y = ~C ;
```


```
endmodule
```

} Order does not matter!


 
# Multiplexor

- Multiplexor is a combinational circuit where an input is chosen by a select signal.
  - Two input mux
  - output =A if select =1
  - output= B if select =0



## Dataflow description of 2-input Mux

- Conditional operator `?:` takes three operands:

```
condition? true_expression : false_expression
```

```
module mux2x1_df (A,B,select,OUT);  
    input A,B,select;  
    output OUT;  
    assign OUT = select ? A : B;  
endmodule
```

## Behavioural Modelling


- Represents circuits at functional and algorithmic level.
- Use procedural statements similar in concept to procedural programming languages (e.g. C, Java),
- Behavioural modelling is mostly used to represent sequential circuits.
- We still specify a module in Verilog with inputs and outputs...
  - But inside the module we write code to specify the behavior we want, NOT what gates (structure) to connect to make it happen
- Why use behavioral models
  - For high-level specs to drive logic synthesis tools

## Behavioural Modelling

- Behavioural models place procedural statements in a block after the **always** keyword.
- The **always** keyword takes a list of variables which represent a trigger condition. The block of statements is executed whenever the trigger is TRUE.
- The target variables are of type **reg**. This type retains its value until a new value is assigned.
- Behavioral models may also have **initial** blocks.
  - The block *executes only once*
  - By default, starts at time 0
  - Often used for initialization
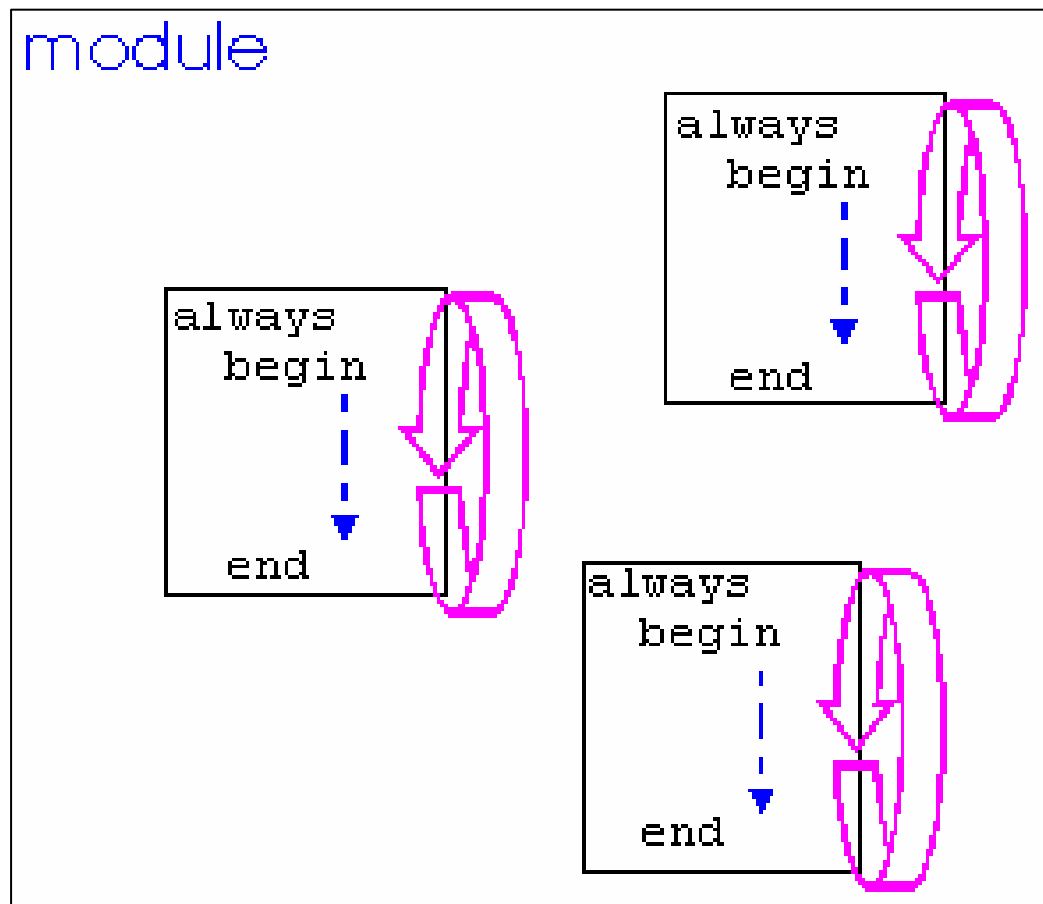
## Always Blocks

- Module may have any number of **always** blocks
- Allow us to represent parallelism in hardware.



## Behavioral Description of an XOR

```
module xorB(X, Y, Z);  
  input X, Y;  
  output Z;  
  reg Z;  
  always @ (X or Y)  
    Z = X ^ Y;  
endmodule
```

- Unusual parts of above Verilog
  - “always @ (X or Y)” => whenever X or Y changes, do the following statement
  - “reg” is only type of behavioral data that can be changed in assignment, so must redeclare Z
  - Default is single bit data types: X, Y, Z

## Behavioural description of 2-input Mux

```
module mux2x1_bh(A,B,select,OUT);  
  input A,B,select;  
  output OUT;  
  reg OUT;  
  always @ (select or A or B)  
    if (select == 1) OUT = A;  
    else OUT = B;  
endmodule
```

## Behavioral example

- Behavioral edge-triggered DFF implem

```
module dff(Q, D, Clk);  
  output Q;  
  input D, Clk;
```


```
  reg Q;  
  wire D, Clk;
```

```
  always @(posedge Clk)  
    Q = D;
```

```
endmodule
```



## Another Behavioral Example

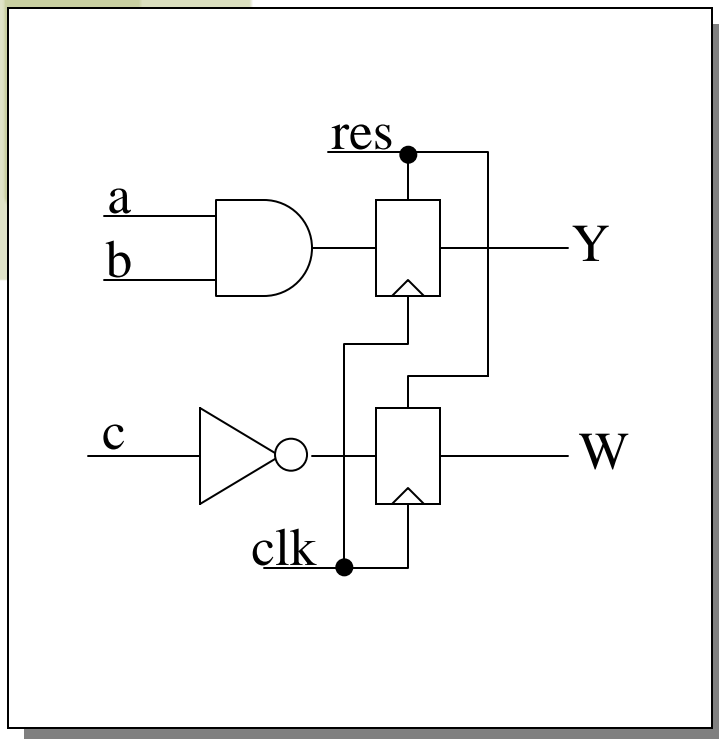

```
always @(res or posedge clk) begin
    if (res) begin
        Y = 0;
        W = 0;
    end
    else begin
        Y = a & b;
        W = ~c;
    end
end
```

# Blocking Assignments

- Represented with an = sign
  - All blocking assignments are executed in sequence

```
module dummy;
reg x, y, z;
reg [15:0] reg_a, reg_b;
integer count;
initial
begin
    x = 0; y = 1; z = 1;
    count = 0;
    reg_a = 16'b0;
    reg_b = reg_a;
    reg_a[2] = #15 1;
    reg_b[15:13] = #10 {x, y, z};
    count = count + 1;
end
```

## Non-blocking Assignments

- Represented with a **<= sign**
  - All non-blocking assignments are executed in parallel
  - Try not to mix with blocking assignments

```
module dummy;
reg x, y, z;
reg [15:0] reg_a, reg_b;
integer count;
initial
begin
    x = 0; y = 1; z = 1;
    count = 0;
    reg_a[2] <= #15 1;
    reg_b[15:13] <= #10 {x, y, z};
    count = count + 1;
end
```

## Blocking or Non-blocking???

- Blocking is harder to reason about.
- Also hardware does not work in a blocking (sequential way)
- So generally you should use non-blocking assignments
  - Easier to synthesize
  - Models parallelism which is inherent in the hardware

## Two kinds of Delays in Verilog


- Inertial Delay – consider the statement

```
assign #4 x = z;
```

  - It's delay behavior is called “inertial” delay
  - Applicable for gate level primitives and continuous assignments
- Transport delay – consider the statement

```
always @(z)  
y <= #4 z;
```

   - Its delay is called “transport” delay
  - Applicable in non-blocking assignments



## Delving Deeper

- So far, we saw how some sample circuits are represented in the three styles
- In the next part of this lecture unit, we will talk about
  - Logic values in Verilog
  - How to represent hierarchical designs
  - Testbenches
  - How to represent sequential logic
  - Synthesizability Tips
  - Syntax examples (will not go over in class in any detail, this portion of the notes is for your reference)

## Four-Valued Logic

- Verilog Logic Values
  - The underlying data representation allows for any bit to have one of four values
  - 1, 0, x (unknown), z (high impedance)
  - x — one of: 1, 0, z, or in the state of change
  - z — the high impedance output of a tri-state gate.
- What basis do these have in reality?
  - z ... An output is high impedance. Tri-stated outputs are a *real* electrical affect.
  - x ... not a real value. There is no *real* gate that drives an x on to a wire. x is used as a *debugging* aid. x means the simulator can't determine the answer and so maybe you should worry! All values in a simulation start as x.
- Verilog keeps track of more values than these in some situations.

## Four-Valued Logic

- Logic with multi-level logic values
  - Logic with these four values make sense
    - Nand anything with a 0, and you get a 1. This includes having an x or z on the other input. That's the nature of the nand gate
    - Nand two x's and you get an x — makes sense!
  - Note: z treated as an x on input. Their rows and columns are the same
  - If you forget to connect an input ... it will be seen as an z.
  - At the start of simulation, *everything* is an x.

		Input B			
		0	1	x	z
Input A	Nand	0	1	x	z
	0	1	1	1	1
	1	1	0	x	x
	x	1	x	x	x
z	1	x	x	x	




**A 4-valued truth table for a Nand gate with two inputs**


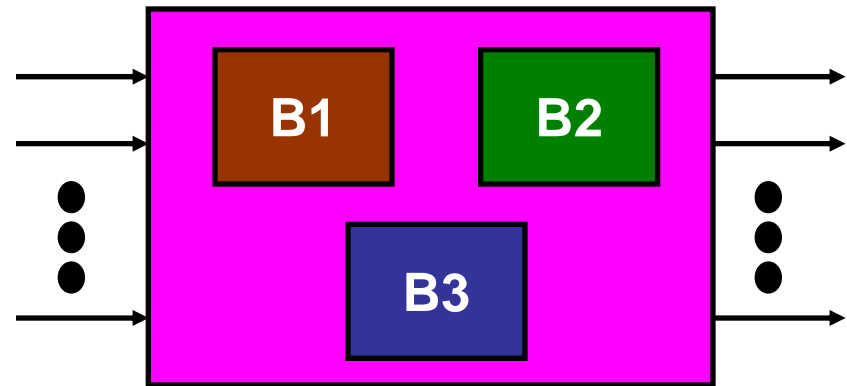
## How to Represent Hierarchy in your Design

- First write the modules for each block of the hierarchy
  - Then wire them up (next page)

```
module B1(a, b, c);  
    .....  
endmodule  
module B2(a, b, c, d);  
    .....  
endmodule  
module B3(x, y, z);  
    .....  
endmodule
```




## Port Mapping (Connecting things up)

```
module B1(q, w, e, f);  
    input q, w;  
    input [3:0] e;  
    output [1:0] f;  
    .....  
endmodule
```



```
module top(a,b,c,d);  
    .....  
    B1 b1(w, q, a, c);  
    .....  
endmodule
```

Module B1 declared

 


Module B1 instantiated,  
instance is called `myinst`  
in this case

## Example (Dataflow, with hierarchy)

  

```
module half_adder(S, C, A, B);  
output S, C;  
input A, B;  
  
wire S, C, A, B;  
  
assign S = A ^ B;  
assign C = A & B;  
  
endmodule
```
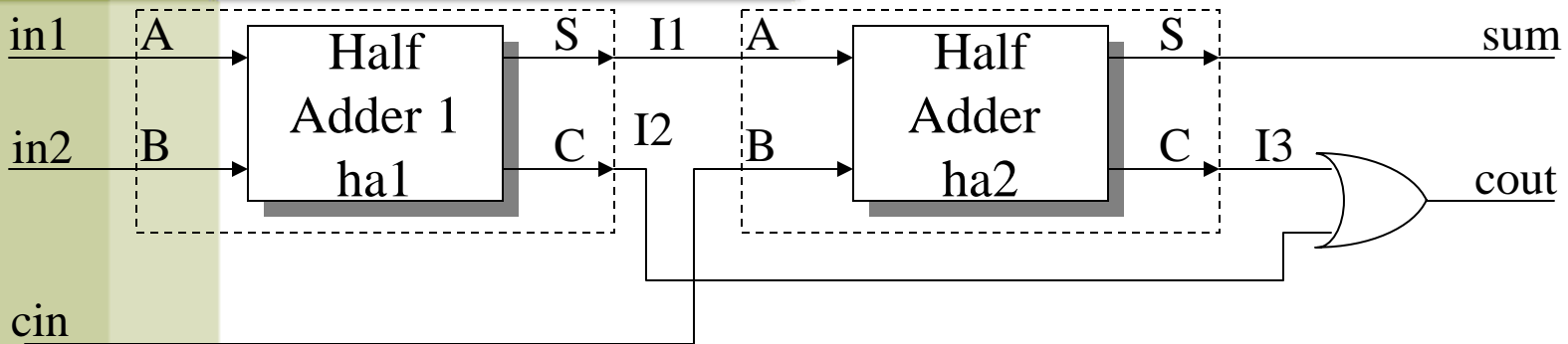
## Creating a Full Adder using Half Adder instances



```
module full_adder(sum, cout, in1, in2, cin);  
    output sum, cout;  
    input in1, in2, cin;
```

```
    wire sum, cout, in1, in2, cin;  
    wire I1, I2, I3;
```

Module  
name


```
    half_adder ha1(I1, I2, in1, in2);  
    half_adder ha2(sum, I3, I1, cin);
```

Instance  
name

```
    assign cout = I2 || I3;
```

```
endmodule
```


# Hierarchical Names

 

Remember to use instance names,  
not module names
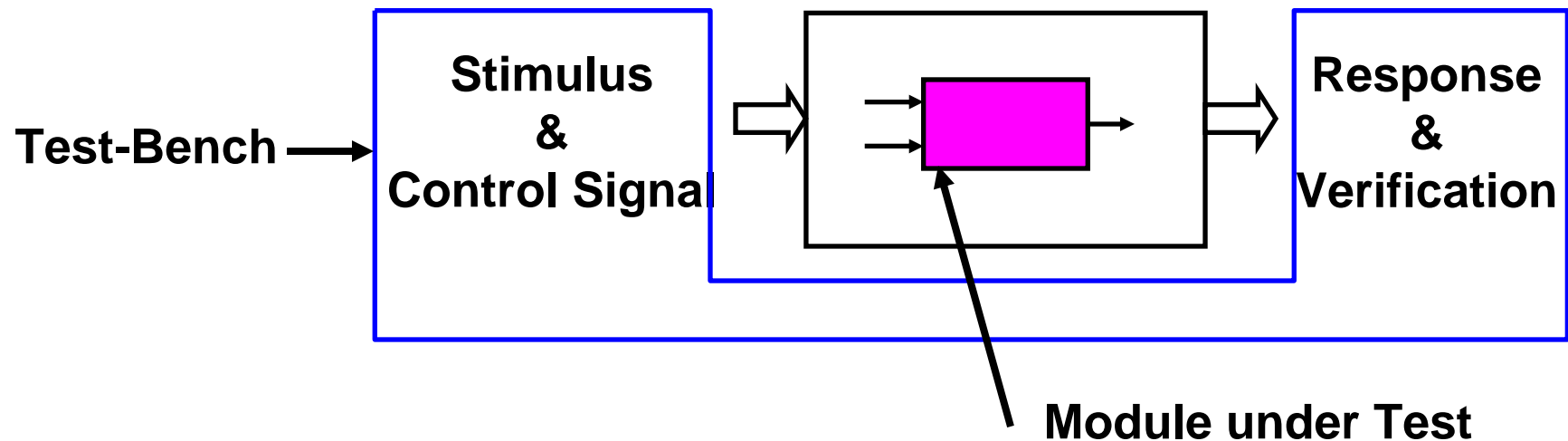
# Verification

- Use *testbench* to verify your design
  - Special Verilog file for simulating and testing your design
  - Instantiates the module to be tested
  - Contains code to apply stimulus to the module under test, and monitor the correctness of the response



## Sample Testbench

```
module top_test;
wire [1:0] t_out;    // Top's signals
reg [3:0] t_in;
reg clk;

top inst(t_out, t_in, clk); // Top's instance

initial begin      // Generate clock
    clk = 0;
    forever #10 clk = ~clk;
end

initial begin      // Generate remaining inputs
    $monitor($time, " %b -> %b", t_in, t_out);
    #5 t_in = 4'b0101;
    #20 t_in = 4'b1110;
    #20 t_in[0] = 1;
    #300 $finish;
end

endmodule
```

# Sequential Logic

```
//Parallel to Serial converter
```

```
module ParToSer(LD, X, out, CLK);
```

```
  input [3:0] X;
```

```
  input LD, CLK;
```

```
  output out;
```

```
  reg out;
```

```
  reg [3:0] Q;
```

```
  assign out = Q[0];
```

```
  always @ (posedge CLK)
```

```
    if (LD) Q=X;
```

```
    else Q = Q>>1;
```

```
endmodule // mux2
```


```
module FF (CLK,Q,D);
```

```
  input D, CLK;
```

```
  output Q; reg Q;
```

```
  always @ (posedge CLK) Q=D;
```

```
endmodule // FF
```

 

- Notes:

- “always @ (posedge CLK)” forces Q register to be rewritten every simulation cycle.

- “>>” operator does right shift (shifts in a zero on the left).

- Shifts on non-reg variables can be done with concatenation:

```
  wire [3:0] A, B;
```

```
  assign B = {1'b0, A[3:1]}
```



# Sequential Logic – another example

```
module mealy (A, CLK, Z);
  input A, CLK;
  output Z;
  reg Z;

  always @(posedge CLK)
    Pstate = Nstate;           // synchronous part
  always @(Pstate or A) begin: COMBINPART
    case (Pstate)
      ST0:
        if(A)
          begin
            Z=1;
            Nstate = ST3;
          end
        else
          Z=0;

      ST1:
        if(A)
          begin
            Z=0;
            Nstate = ST2;
          end
        else
          Z=0;
      <ETC><ETC>
    endcase
  end
endmodule
```

- Notes:
  - If we have a state machine updating on a rising clock edge, then we create the always block (triggered on the posedge of clock).
  - Also we write the state machine behavior as a case statement.
    - For example if we are in state ST0, and A is 1, then we move to state ST3 in the next clock.
  - This kind of code for a state machine is very similar to the state transition diagram based behavior. Hence easy to write.


## Synthesizability Tips

- If you want to synthesize your Verilog code, here are some tips
  - Do not use delays in your code
  - Watch for blocking and non-blocking assignments (next slide)
  - Watch out for complete assignments (2 slides after next)

# Blocking and Non-blocking

 
**Bad: Circuit from blocking assignment.**

```
always @(posedge clk)
begin
    b=a;
    a=b;
end
```



 **Good: Circuit from nonblocking assignment.**

```
always @(posedge clk)
begin
    b<=a;
    a<=b;
end
```



## “Complete” Assignments

- If an `always` block executes, and a variable is *not* assigned
  - Variable keeps its old value (this needs state!!)
  - Hence latch is inserted (inferred memory)
  - This is usually *not* what you want: dangerous for the novice!
- So to avoid this, any variable assigned in an `always` block should be assigned for any (and every!) execution of the block

## Incomplete Triggers






- Leaving out an input trigger usually results in a sequential circuit
- Example: The output of this “and” gate depends on the input history (a latch will be inferred on in2).

```
module and_gate (out, in1, in2);  
    input        in1, in2;  
    output       out;  
    reg          out;  
  
    always @(in1) begin  
        out = in1 & in2;  
    end  
  
endmodule
```

## Some Verilog Syntax Notes for Your Reference..

- You may find the following slides handy as a partial Verilog reference.
  - It is *not* meant to be a complete reference – see the resources on the class website for more detailed references.
  - It is meant to help you with the syntax for common Verilog constructs.

## User Identifiers

- Formed from {[A-Z], [a-z], [0-9], \_, \$}, but ..
- .. can't begin with \$ or [0-9]
  - myidentifier 
  - m\_y\_identifier 
  - 3my\_identifier 
  - \$my\_identifier 
  - \_myidentifier\$ 
- Case sensitivity
  - myid ≠ Myid

# Comments

- `//` The rest of the line is a comment
- `/*` Multiple line  
comment `*/`
- `/*` Nesting `/*` comments `*/` do **NOT** work `*/`



## Numbers in Verilog (i)

`<size>'<radix><value>`

No of  
bits

Binary → b or B  
Octal → o or O  
Decimal → d or D  
Hexadecimal → h or H

Consecutive chars  
0-f, x, z

- `8'h ax = 1010xxxx`
- `12'o 3zx7 = 011zzzxxx111`

## Numbers in Verilog (ii)

- You can insert “\_” for readability
  - 12'b 000\_111\_010\_100
  - 12'b 000111010100
  - 12'o 07\_24
- Bit extension
  - MS bit = 0, x or z  $\Rightarrow$  extend this
    - 4'b x1 = 4'b xx\_x1
  - MS bit = 1  $\Rightarrow$  zero extension
    - 4'b 1x = 4'b 00\_1x

} Represent the same number


## Numbers in Verilog (iii)

- If *size* is omitted it
  - is inferred from the *value* or
  - takes the simulation specific number of bits or
  - takes the machine specific number of bits
- If *radix* is omitted too .. decimal is assumed
  - $15 = \langle \text{size} \rangle' d 15$

## Nets (i)

- Can be thought as hardware wires driven by logic
- Equal  $z$  when unconnected
- Various types of nets
  - wire
  - wand (wired-AND)
  - wor (wired-OR)
  - tri (tri-state)
- In following examples: Y is evaluated, *automatically*, every time A or B changes


## Nets (ii)

 

```

wire Y; // declaration
assign Y = A & B;


```

 

```

wand Y; // declaration
assign Y = A;
assign Y = B;

```

 

```

tri Y; // declaration
assign Y = (dr) ? A : z;

```

		A	
		0	1
B	0	0	0
	1	0	1

		A	
		0	1
B	0	0	1
	1	1	1

# Registers

- Variables that store values
- Do not represent real hardware but ..
- .. real hardware can be implemented with registers
- Only one type: `reg`

```
reg A, C; // declaration
```

```
// assignments are always done inside a procedure
```

```
A = 1;
```

```
C = A; // C gets the logical value 1
```

```
A = 0; // C is still 1
```

```
C = 0; // C is now 0
```

- Register values are updated explicitly!!

# Vectors

- Represent buses

```
wire [3:0] busA;  
reg [1:4] busB;  
reg [1:0] busC;
```

- Left number is MS bit
- Slice management

$$\text{busC} = \text{busA}[2:1]; \quad \Leftrightarrow \quad \begin{cases} \text{busC}[1] = \text{busA}[2]; \\ \text{busC}[0] = \text{busA}[1]; \end{cases}$$

- Vector assignment (*by position!!*)

$$\text{busB} = \text{busA}; \quad \Leftrightarrow \quad \begin{cases} \text{busB}[1] = \text{busA}[3]; \\ \text{busB}[2] = \text{busA}[2]; \\ \text{busB}[3] = \text{busA}[1]; \\ \text{busB}[4] = \text{busA}[0]; \end{cases}$$

## Integer & Real Data Types

- Declaration

```
integer i, k;
```

```
real r;
```

- Use as registers (inside procedures)

```
i = 1; // assignments occur inside procedure
```

```
r = 2.9;
```

```
k = r; // k is rounded to 3
```

- Integers are not initialized!!

- Reals are initialized to *0.0*



## Time Data Type

- Special data type for simulation time measuring
- Declaration

```
time my_time;
```

- Use inside procedure

```
my_time = $time; // get current sim time
```

- Simulation runs at simulation time, not real time

## Arrays (i)

- Syntax

```
integer count[1:5]; // 5 integers
reg var[-15:16]; // 32 1-bit regs
reg [7:0] mem[0:1023]; // 1024 8-bit regs
```

- Accessing array elements

- Entire element: `mem[10] = 8'b 10101010;`
- Element subfield (needs temp storage):

```
reg [7:0] temp;
..
temp = mem[10];
var[6] = temp[2];
```

- Concatenating bits/vectors into a vector

- e.g., sign extend
- `B[7:0] = {A[3], A[3], A[3], A[3], A[3:0]};`
- `B[7:0] = {3{A[3]}, A[3:0]};`

- Style: Use `a[7:0] = b[7:0] + c;`

Not: `a = b + c;` // need to look at declaration

## Arrays (ii)

- **Limitation: Cannot access array subfield or entire array at once**

```
var[2:9] = ???; // WRONG!!
```

```
var = ???; // WRONG!!
```

- **No multi-dimensional arrays**

```
reg var[1:10] [1:100]; // WRONG!!
```

- **Arrays don't work for the Real data type**

```
real r[1:10]; // WRONG !!
```

# Strings

- Implemented with regs:


```
reg [8*13:1] string_val; // can hold up to 13 chars
..
string_val = "Hello Verilog";
string_val = "hello"; // MS Bytes are filled with 0
string_val = "I am overflowed"; // "I " is truncated
```

- Escaped chars:

- \n	newline
- \t	tab
- %%	%
- \\	\
- \"	"

# Logical Operators

- `&&` → logical AND
- `||` → logical OR
- `!` → logical NOT
- Operands evaluated to ONE bit value: *0*, *1* or *x*
- Result is ONE bit value: *0*, *1* or *x*
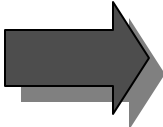
<code>A = 6;</code>		<code>A &amp;&amp; B → 1 &amp;&amp; 0 → 0</code>
<code>B = 0;</code>		<code>A    !B → 1    1 → 1</code>
<code>C = x;</code>		<code>C    B → x    0 → x</code>

but `C&&B=0`






## Bitwise Operators (i)

- $\&$  → bitwise AND
- $|$  → bitwise OR
- $\sim$  → bitwise NOT
- $\wedge$  → bitwise XOR
- $\sim \wedge$  or  $\wedge \sim$  → bitwise XNOR

- Operation on bit by bit basis for bitwise operators.

# Bitwise Operators (ii)

`a = 4'b1010;`  
`b = 4'b1100;`

 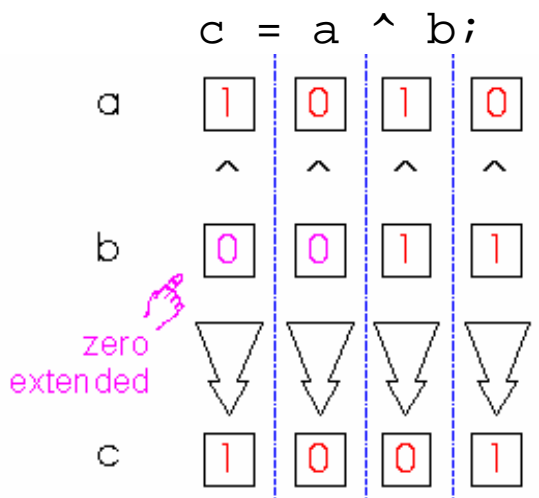   

`a = 4'b1010;`  
`b = 2'b11;`

## Reduction Operators

- `&` → AND
- `|` → OR
- `^` → XOR
- `~&` → NAND
- `~|` → NOR
- `~^` or `^~` → XNOR

- One multi-bit operand → One single-bit result

```
a = 4'b1001;
```

```
..
```

```
c = |a; // c = 1|0|0|1 = 1
```

- If  $A = 'b0110$ , and  $B = 'b0100$  then  $|B=1$ ,  $\&B=0$ ,  $\sim^A=1$
- If  $C=4'b01x0$ , then  $\wedge C=x$ .



# Shift Operators

- `>>` → shift right
- `<<` → shift left
- Result is same size as first operand, **always zero filled**

```
a = 4'b1010;  
...  
d = a >> 2;    // d = 0010  
c = a << 1;    // c = 0100
```

## Concatenation Operator

- `{op1, op2, ..}` → concatenates op1, op2, .. to single number
- Operands must be sized !!

```
reg a;  
reg [2:0] b, c;  
..
```

```
a = 1'b 1;
```

```
b = 3'b 010;
```

```
c = 3'b 101;
```

```
catx = {a, b, c};           // catx = 1_010_101
```

```
caty = {b, 2'b11, a};      // caty = 010_11_1
```

```
catz = {b, 1};            // WRONG !!
```

- Replication ..

```
catr = {4{a}, b, 2{c}};    // catr = 1111_010_101101
```

## Relational Operators

- $>$  → greater than
  - $<$  → less than
  - $>=$  → greater or equal than
  - $<=$  → less or equal than
- 
- Result is one bit value:  $0$ ,  $1$  or  $x$

$1 > 0 \quad \rightarrow 1$

$'b1x1 <= 0 \quad \rightarrow x$

$10 < z \quad \rightarrow x$

## Equality Operators

- `==` → logical equality
- `!=` → logical inequality
- `===` → case equality
- `!==` → case inequality

} Return *0*, *1* or *x*

} Return *0* or *1*

– `4'b 1z0x == 4'b 1z0x` → *x*


– `4'b 1z0x != 4'b 1z0x` → *x*

– `4'b 1z0x === 4'b 1z0x` → *1*

– `4'b 1z0x !== 4'b 1z0x` → *0*
 
# Conditional Operator

- `cond_expr ? true_expr : false_expr`
- Like a 2-to-1 mux ..



## Arithmetic Operators (i)

- +, -, \*, /, %
- If any operand is  $x$  the result is  $x$
- Negative registers:
  - regs can be assigned negative but are treated as unsigned

```
reg [15:0] regA;
```

```
..
```

```
regA = -4'd12;          // stored as  $2^{16}-12 = 65524$ 
```

```
regA/3                evaluates to 21861
```

## Arithmetic Operators (ii)

- Negative integers:
  - can be assigned negative values
  - different treatment depending on base specification or not

```
reg [15:0] regA;
```

```
integer intA;
```

```
..
```

```
intA = -12/3;    // evaluates to -4 (no base spec)
```

```
intA = -'d12/3; // evaluates to 1431655761 (base spec)
```


# Verilog Operators

Verilog Operator	Name	Functional Group
()	bit-select or part-select	
()	parenthesis	
! ~ &   ~& ~  ^ ~^ or ^~	logical negation negation reduction AND reduction OR reduction NAND reduction NOR reduction XOR reduction XNOR	Logical Bit-wise Reduction Reduction Reduction Reduction Reduction Reduction
+ -	unary (sign) plus unary (sign) minus	Arithmetic Arithmetic
{}	concatenation	Concatenation
{{}}	replication	Replication
* / %	multiply divide modulus	Arithmetic Arithmetic Arithmetic
+ -	binary plus binary minus	Arithmetic Arithmetic
<< >>	shift left shift right	Shift Shift

> >= < <=	greater than greater than or equal to less than less than or equal to	Relational Relational Relational Relational
== !=	logical equality logical inequality	Equality Equality
=== !==	case equality case inequality	Equality Equality
&	bit-wise AND	Bit-wise
^ ^~ or ~^	bit-wise XOR bit-wise XNOR	Bit-wise Bit-wise
	bit-wise OR	Bit-wise
&&	logical AND	Logical
	logical OR	Logical
?:	conditional	Conditional



# Operator Precedence

<code>+ - ! ~ unary</code>	highest precedence	
<code>* / %</code>		
<code>+ - (binary)</code>		
<code>&lt;&lt; &gt;&gt;</code>		
<code>&lt; &lt;= &gt; &gt;</code>		
<code>== != === !==</code>		
<code>&amp; ~&amp;</code>		
<code>^ ^~ ~^</code>		
<code>  ~ </code>		
<code>&amp;&amp;</code>		
<code>  </code>		
<code>?: conditional</code>		lowest precedence

Use parentheses to  
enforce your  
priority

## Verilog Variables

- wire
  - Variable used simply to connect components together
- reg
  - Variable that saves a value as part of a behavioral description
  - Usually corresponds to a wire in the circuit
  - Is *NOT* necessarily a register in the circuit
- usage:
  - Don't confuse reg assignments with the combinational continuous assign statement!
  - Reg should only be used with always blocks (sequential logic, to be presented ...)

# Verilog Module

- Corresponds to a circuit component
  - “Parameter list” is the list of external connections, aka “ports”
  - Ports are declared “input”, “output” or “inout”
    - inout ports used on tri-state buses
  - Port declarations imply that the variables are wires

```
module full_addr (A, B, Cin, S, Cout);  
  input      A, B, Cin;  
  output    S, Cout;  
  
  assign {Cout, S} = A + B + Cin;  
endmodule
```

Diagram annotations:

- “module name” points to `full_addr`
- “ports” points to the parameter list `(A, B, Cin, S, Cout)`
- “inputs/outputs” points to the declarations `input A, B, Cin;` and `output S, Cout;`

# Verilog Continuous Assignment

- Assignment is continuously evaluated
- `assign` corresponds to a connection or a simple component with the described function
- Target is *NEVER* a reg variable
- Dataflow style

```
assign A = X | (Y & ~Z);
```

use of Boolean operators  
(~ for bit-wise, ! for logical negation)

```
assign B[3:0] = 4'b01XX;
```

bits can take on four values  
(0, 1, X, Z)

```
assign C[15:0] = 4'h00ff;
```

variables can be n-bits wide  
(MSB:LSB)

```
assign #3 {Cout, S[3:0]} = A[3:0] + B[3:0] + Cin;
```

use of arithmetic operator

multiple assignment (concatenation)

delay of performing computation, only used by simulator, not synthesis

## Verilog if

- Same as C if statement

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
input [1:0] sel;    // 2-bit control signal
input A, B, C, D;
output Y;
reg Y;             // target of assignment

    always @(sel or A or B or C or D)
        if (sel == 2'b00) Y = A;
        else if (sel == 2'b01) Y = B;
        else if (sel == 2'b10) Y = C;
        else if (sel == 2'b11) Y = D;

endmodule
```

## Verilog if

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
input [1:0] sel;    // 2-bit control signal
input A, B, C, D;
output Y;
reg Y;             // target of assignment

    always @(sel or A or B or C or D)
        if (sel[0] == 0)
            if (sel[1] == 0) Y = A;
            else           Y = B;
        else
            if (sel[1] == 0) Y = C;
            else           Y = D;
endmodule
```

## Verilog case

- Sequential execution of cases
  - Only first case that matches is executed (no break)
  - Default case can be used

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
input [1:0] sel;          // 2-bit control signal
input A, B, C, D;
output Y;
reg Y;                   // target of assignment

always @(sel or A or B or C or D)
    case (sel)
        2'b00: Y = A;
        2'b01: Y = B;
        2'b10: Y = C;
        2'b11: Y = D;
    endcase
endmodule
```

|  
Conditions tested in  
top to bottom order  
↓

## Verilog case

- Without the default case, this example would create a latch for Y
- Assigning X to a variable means synthesis is free to assign any value

```
// Simple binary encoder (input is 1-hot)
module encode (A, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;           // 3-bit encoded output
reg    [2:0] Y;           // target of assignment

always @(A)
  case (A)
    8'b00000001: Y = 0;
    8'b00000010: Y = 1;
    8'b00000100: Y = 2;
    8'b00001000: Y = 3;
    8'b00010000: Y = 4;
    8'b00100000: Y = 5;
    8'b01000000: Y = 6;
    8'b10000000: Y = 7;
    default:      Y = 3'bX;           // Don't care when input is not 1-hot
  endcase
endmodule
```



## Verilog case (cont)

- Cases are executed sequentially
  - The following implements a *priority* encoder

```
// Priority encoder
module encode (A, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;           // 3-bit encoded output
reg    [2:0] Y;           // target of assignment

always @(A)
  case (1'b1)
    A[0]: Y = 0;
    A[1]: Y = 1;
    A[2]: Y = 2;
    A[3]: Y = 3;
    A[4]: Y = 4;
    A[5]: Y = 5;
    A[6]: Y = 6;
    A[7]: Y = 7;
    default: Y = 3'bX; // Don't care when input is all 0's
  endcase
endmodule
```

## Parallel case

- A priority encoder is more expensive than a simple encoder
  - If we know the input is 1-hot, we can tell the synthesis tools
  - **"parallel-case"** pragma says the order of cases does not matter

```
// simple encoder
module encode (A, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;           // 3-bit encoded output
reg    [2:0] Y;           // target of assignment

    always @(A)
        case (1'b1)      // synthesis parallel-case
            A[0]:    Y = 0;
            A[1]:    Y = 1;
            A[2]:    Y = 2;
            A[3]:    Y = 3;
            A[4]:    Y = 4;
            A[5]:    Y = 5;
            A[6]:    Y = 6;
            A[7]:    Y = 7;
            default: Y = 3'bX; // Don't care when input is all 0's
        endcase
    endmodule
```

## Verilog case x

- Like case, but cases can include 'X'
  - X bits not used when evaluating the cases
  - In other words, you don't care about those bits!

## case Example

```
// Priority encoder
module encode (A, valid, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;           // 3-bit encoded output
output valid;            // Asserted when an input is not all 0's
reg    [2:0] Y;           // target of assignment
reg    valid;

    always @(A) begin
        valid = 1;
        casex (A)
            8'bXXXXXXXX1: Y = 0;
            8'bXXXXXXXX10: Y = 1;
            8'bXXXXXX100: Y = 2;
            8'bXXXXX1000: Y = 3;
            8'bXXX10000: Y = 4;
            8'bXX100000: Y = 5;
            8'bX1000000: Y = 6;
            8'b10000000: Y = 7;
            default: begin
                valid = 0;
                Y = 3'bX; // Don't care when input is all 0's
            end
        endcase
    end
endmodule
```

# Verilog for

- for is similar to C
- for statement is executed at compile time (like macro expansion)
  - Useful for parameterized designs.

```
// simple encoder
module encode (A, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;           // 3-bit encoded output
reg     [2:0] Y;         // target of assignment

integer i;               // Temporary variables for program only
reg [7:0] test;

    always @(A) begin
        test = 8b'00000001;
        Y = 3'bX;
        for (i = 0; i < 8; i = i + 1) begin
            if (A == test) Y = N;
            test = test << 1;
        end
    end
endmodule
```

## Verilog while/repeat/forever

- `while (expression) statement`
  - Execute statement while expression is true
- `repeat (expression) statement`
  - Execute statement a fixed number of times
- `forever statement`
  - Execute statement forever

## full-case and parallel-case

- **// synthesis parallel\_case**
  - Tells compiler that ordering of cases is not important
  - That is, cases do not overlap
    - e. g., state machine - can't be in multiple states
  - Gives cheaper implementation
- **// synthesis full\_case**
  - Tells compiler that cases left out can be treated as don't cares
  - Avoids incomplete specification and resulting latches