

# **ECEN 248 -Introduction to Digital Systems Design (Spring 2008)**

---

**(Sections: 501 , 502 , 503 , 507)**

**Prof. Xi Zhang**

**ECE Dept, TAMU, 333N WERC**

**<http://dropzone.tamu.edu/~xizhang/ECEN248>**

# FSM for Sequence detector (Mealy Type)

---

- Unlike the Moore type machine, the output depends not only the current state, but also the current input.
-

# Sequences of input and output signals

---

Clock cycle:	$t_0$	$t_1$	$t_2$	$t_3$	$t_4$	$t_5$	$t_6$	$t_7$	$t_8$	$t_9$	$t_{10}$
$w$ :	0	1	0	1	1	0	1	1	1	0	1
$z$ :	0	0	0	0	1	0	0	1	1	0	0

Figure 8.22. Sequences of input and output signals.

---

# State diagram of an FSM

---

 


Figure 8.23. State diagram of an FSM that realizes the task in Figure 8.22.

- A: starting state, also the state after an input  $w=0$  is applied.
  - B:  $w=1$  in immediately preceding clock cycle.
-

# State table for the FSM

---


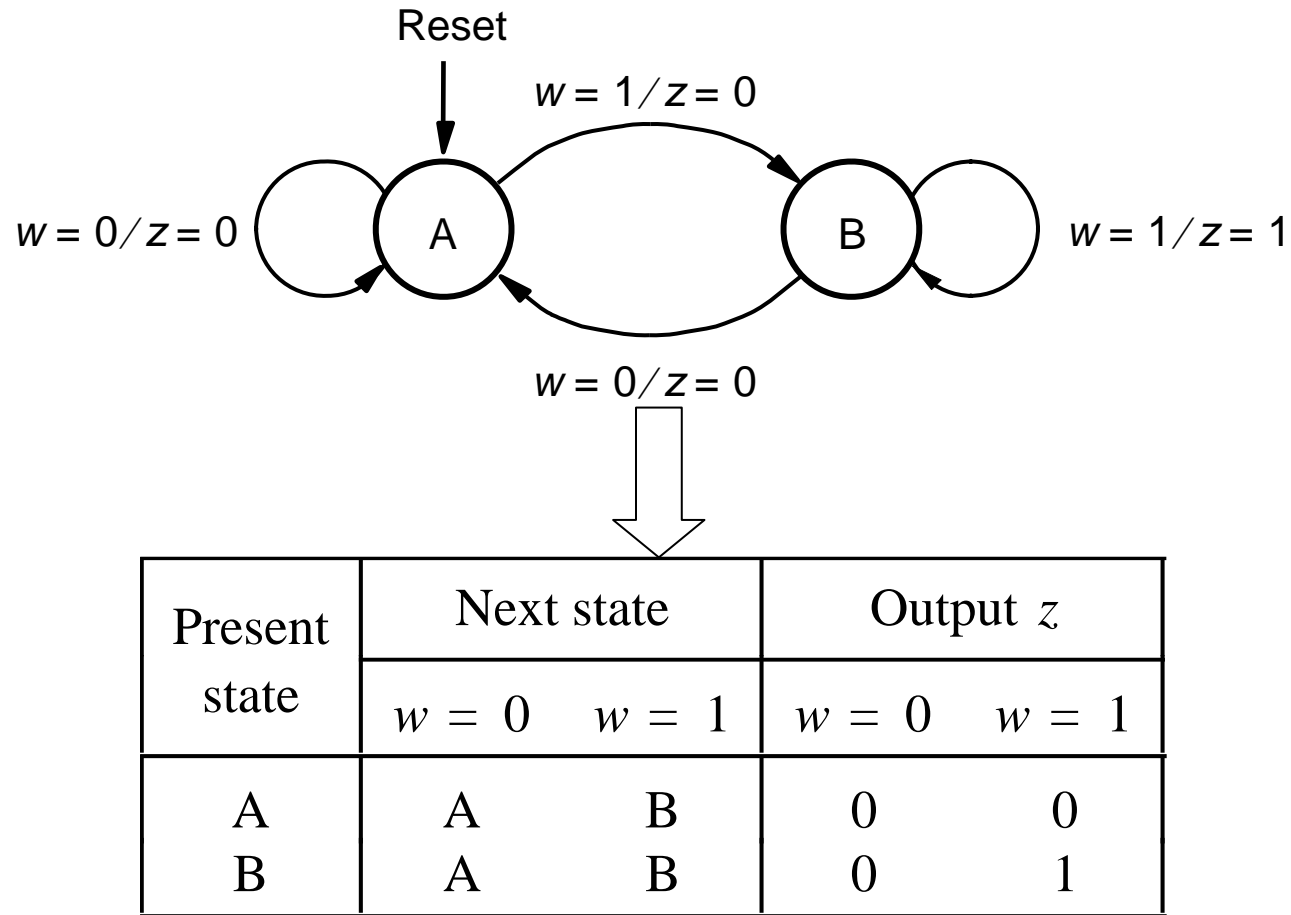


Figure 8.24. State table for the FSM in Figure 8.23.

---

# State-assigned table for the FSM

Present state	Next state		Output $z$	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

 


	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	$y$	$Y$	$Y$	$z$	$z$
A	0	0	1	0	0
B	1	0	1	0	1

Figure 8.25. State-assigned table for the FSM in Figure 8.24.

# Derivation of the logic expressions

---

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	$y$	$Y$	$Y$	$z$	$z$
A	0	0	1	0	0
B	1	0	1	0	1

 


$Y = D = w;$


$z = wy;$

---

# Implementation of FSM

 

(a) Circuit

 


(b) Timing diagram

Figure 8.26. Implementation of FSM in Figure 8.25.



# Circuit that implements the specification

---

 


(a) Circuit

---

Figure 8.27. Circuit that implements the specification in Figure 8.2.

# Circuit that implements the specification

---

 

(b) Timing diagram

---

Figure 8.27. Circuit that implements the specification in Figure 8.2.

Break page between Ch 8.3 and 8.5

---

---

# Example of the serial adder

- $A = a_{n-1} a_{n-2} \dots a_0$
- $B = b_{n-1} b_{n-2} \dots b_0$
- $S = s_{n-1} s_{n-2} \dots s_0 = A + B$

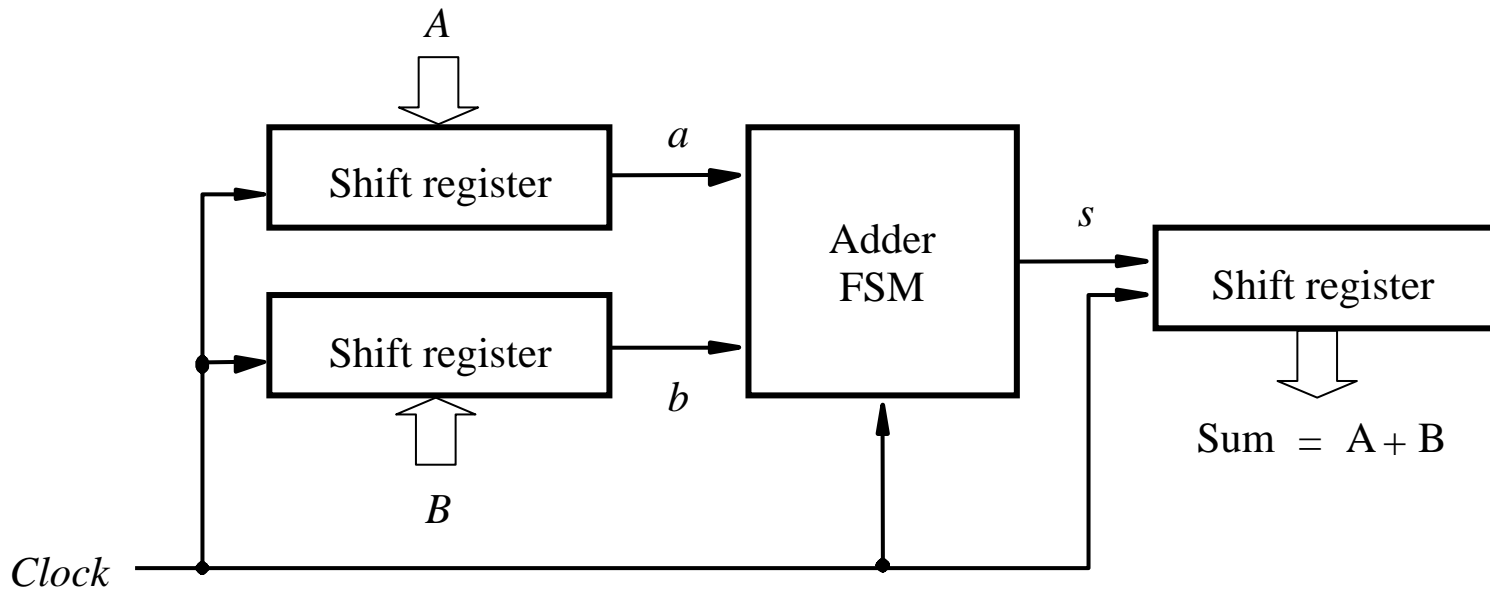


Figure 8.39. Block diagram for the serial adder.

# State diagram for the serial adder FSM

---


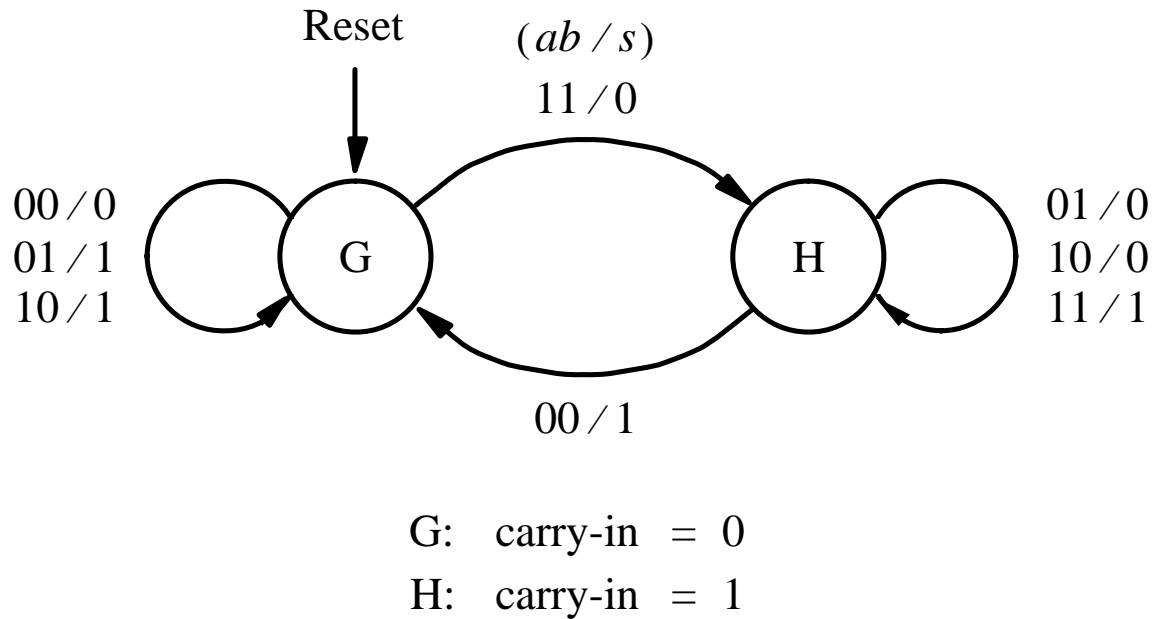


Figure 8.40. State diagram for the serial adder FSM.

---

# State table for the serial adder FSM

 

G: carry-in = 0

H: carry-in = 1


Present state	Next state				Output $s$			
	$ab = 00$	01	10	11	00	01	10	11
G	G	G	G	H	0	1	1	0
H	G	H	H	H	1	0	0	1

Figure 8.41. State table for the serial adder FSM.

# State-assigned table for the serial adder

---

Present state	Next state				Output $s$			
	$ab = 00$	01	10	11	00	01	10	11
G	G	G	G	H	0	1	1	0
H	G	H	H	H	1	0	0	1

 

Present state	Next state				Output			
	$ab = 00$	01	10	11	00	01	10	11
$y$	$Y$				$s$			
0	0	0	0	1	0	1	1	0
1	0	1	1	1	1	0	0	1

Figure 8.42. State-assigned table for Figure 8.41.

# Circuit for the serial adder

---

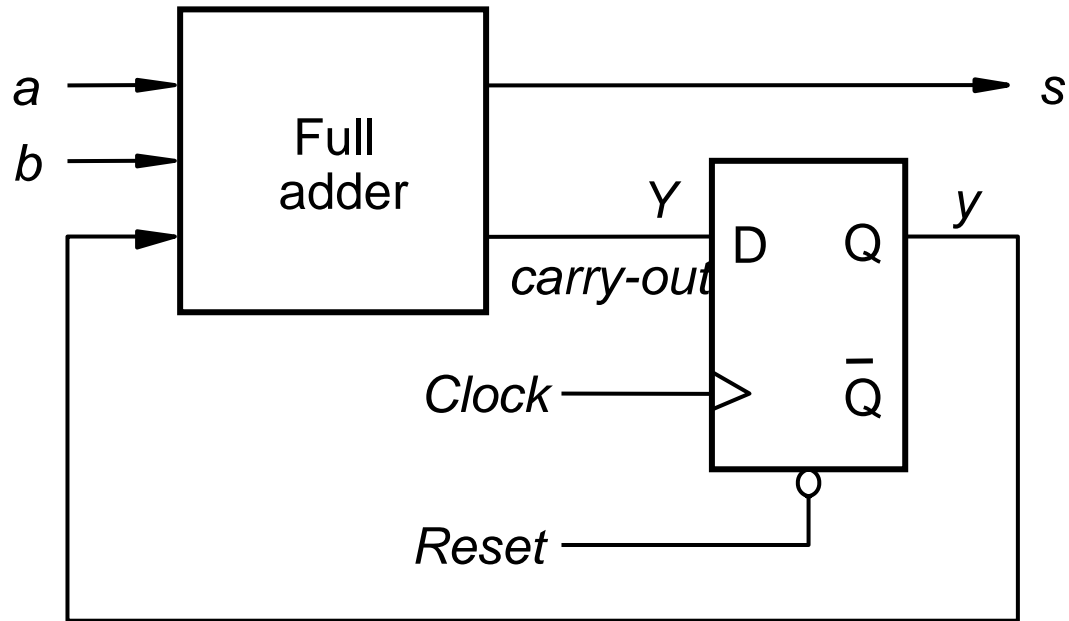


Figure 8.43. Circuit for the adder FSM in Figure 8.39.

---



# State diagram for the serial adder (Moore-type)

---


 


Figure 8.44. State diagram for the Moore-type serial adder FSM.

---
 
# State table for the Moore-type serial adder




Present state	Nextstate				Output $s$
	$ab = 00$	01	10	11	
$G_0$	$G_0$	$G_1$	$G_1$	$H_0$	0
$G_1$	$G_0$	$G_1$	$G_1$	$H_0$	1
$H_0$	$G_1$	$H_0$	$H_0$	$H_1$	0
$H_1$	$G_1$	$H_0$	$H_0$	$H_1$	1

Figure 8.45. State table for the Moore-type serial adder FSM.

# State-assigned table serial adder

Present state	Nextstate				Output $s$
	$ab = 00$	01	10	11	
$G_0$	$G_0$	$G_1$	$G_1$	$H_0$	0
$G_1$	$G_0$	$G_1$	$G_1$	$H_0$	1
$H_0$	$G_1$	$H_0$	$H_0$	$H_1$	0
$H_1$	$G_1$	$H_0$	$H_0$	$H_1$	1

 

Present state $y_2y_1$	Nextstate				Output $s$
	$ab = 00$	01	10	11	
	$Y_2Y_1$				
00	0 0	01	0 1	10	0
01	0 0	01	0 1	10	1
10	0 1	10	1 0	11	0
11	0 1	10	1 0	11	1

Figure 8.46. State-assigned table for Figure 8.45.

# Circuit for the Moore-type serial adder FSM

---

 


Figure 8.47. Circuit for the Moore-type serial adder FSM.

---