

3.1 (20points)

$$f = x_1' x_2' x_3 + x_1' x_2 x_3' + x_1 x_2' x_3' + x_1 x_2 x_3$$

Truth table:

x ₁	x ₂	x ₃	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Number of transistors:

Gate	NOT	3-input AND	4-input OR
Number of Gates	3	4	1
Number of Transistors per Gate	2	8	10

So, the total number of transistors is given as follows:

$$2 \times 3 + 8 \times 4 + 10 \times 1 = 48$$

Supplementary problem (20 points):

$$f = x_1 x_4 + x_1 (x_2 x_3)' (x_2 x_3' x_4)' + x_1' x_2' x_3 + x_1' x_2' x_3' x_4'$$

Truth table:

x_1	x_2	x_3	x_4	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

Number of transistors:

Gate	NOT	2-input AND	2-input NAND	3-input NAND	3-input AND	4-input AND	4-input OR
Number of Gates	4	1	1	1	2	1	1
Number of Transistors per Gate	2	6	4	6	8	10	10

So, the total number of transistors is given as follows:

$$2 \times 4 + 6 \times 1 + 4 \times 1 + 6 \times 1 + 8 \times 2 + 10 \times 1 + 10 \times 1 = 60$$