 



Chapter 7

7.1.




7.2. The circuit in Figure 7.3 can be modified to implement an SR latch by connecting S to the *Data* input and $S + R$ to the *Load* input. Thus the value of S is loaded into the latch whenever either S or R is asserted. Care must be taken to ensure that the *Data* signal remains stable while the *Load* signal is asserted.

7.3.


 


\bar{S}	\bar{R}	Q_a	Q_b
1	1	0/1	1/0 (no change)
1	0	0	1
0	1	1	0
0	0	1	1


7.4.

 


7.5.

  


7.6.

 


S	R	$Q(t+1)$
0	0	$Q(t)$
0	1	0
1	0	1
1	1	0

 

7.7.

 

7.8.

 

7.9. This circuit acts as a negative-edge-triggered JK flip-flop, in which $J = A$, $K = B$, $Clock = C$, $Q = D$, and $\bar{Q} = E$. This circuit is found in the standard chip called 74LS107A (plus a *Clear* input, which is not shown).

Chapter 8

8.1. The expressions for the inputs of the flip-flops are

$$\begin{aligned} D_2 &= Y_2 = \bar{w}y_2 + \bar{y}_1\bar{y}_2 \\ D_1 &= Y_1 = w \oplus y_1 \oplus y_2 \end{aligned}$$

The output equation is

$$z = y_1y_2$$

8.2. The excitation table for JK flip-flops is

Present state y_2y_1	Flip-flop inputs				Output z
	$w = 0$		$w = 1$		
	J_2K_2	J_1K_1	J_2K_2	J_1K_1	
00	1d	0d	1d	1d	0
01	0d	d0	0d	d1	0
10	d0	1d	d1	0d	0
11	d0	d1	d1	d0	1

The expressions for the inputs of the flip-flops are

$$\begin{aligned} J_2 &= \bar{y}_1 \\ K_2 &= w \\ J_1 &= \bar{w}y_2 + w\bar{y}_2 \\ K_1 &= J_1 \end{aligned}$$

The output equation is

$$z = y_1y_2$$

8.3. A possible state table is

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	E	C	0	0
C	E	D	0	0
D	E	D	0	1
E	F	B	0	0
F	A	B	0	1