

Supplementary problem:

Consider the circuit shown in the following Figure

(a) Show the truth table for the logic function f

(b) If each gate in the circuit is implemented as a CMOS gate, how many transistors are needed?

