

ECEN 248 -Introduction to Digital Systems Design (Spring 2008)

(Sections: 501, 502, 503, 507)

Prof. Xi Zhang

ECE Dept, TAMU, 333N WERC

<http://www.ece.tamu.edu/~xizhang/ECEN248>

Programmable logic device (PLD)

- ❑ A PLD is a general-purpose chip for implementing logic circuit.
 - ❑ It contains a collection of logic circuit elements that can be customized in different ways.
 - ❑ A PLD can be viewed as a “black box” that contains logic gates and **programmable switches**.
 - ❑ The programmable switches allow the logic gates inside the PLD to be connected together to implement logic circuits.
-

Programmable logic device as a black box

 


Figure 3.24. Programmable logic device as a black box.

Programmable logic devices

☐ Different types of PLD

■ Simple PLD (SPLD)

- ☐ Programmable logic array (PLA)

- ☐ Programmable array logic (PAL)

■ Complex PLD (CPLD)

■ Field-programmable gate arrays (FPGA)

Programmable logic array (PLA)

- PLA is developed based on the sum-of-product form.
- A PLA includes a circuit block called an **AND plane** (or AND array) and a circuit block called an **OR plane** (or OR array).
- Input \rightarrow Buffer/inverters \rightarrow And plane \rightarrow OR plane \rightarrow Output


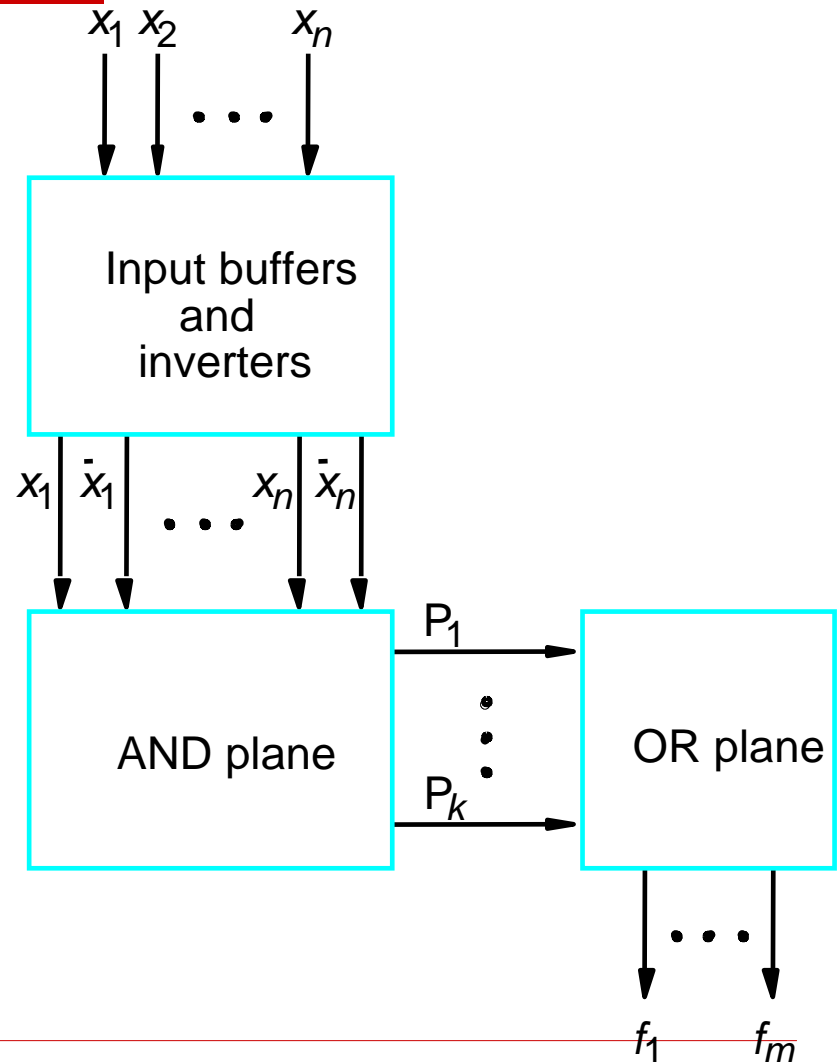


Figure 3.25. General structure of a PLA.

Gate-level diagram of a PLA

 

Output of And plane:

$$P_1 = x_1 x_2$$

$$P_2 = x_1 \bar{x}_3$$

$$P_3 = \bar{x}_1 \bar{x}_2 x_3$$

$$P_4 = x_1 x_3$$


Output of OR plane:

$$f_1 = x_1 x_2 + x_1 \bar{x}_3 + \bar{x}_1 \bar{x}_2 x_3$$

$$f_2 = x_1 x_2 + x_1 \bar{x}_2 \bar{x}_3 + x_1 x_3$$

Figure 3.26. Gate-level diagram of a PLA.

Customary schematic for the PLA

 

Output of And plane:

$$P_1 = x_1 x_2$$

$$P_2 = x_1 \bar{x}_3$$

$$P_3 = \bar{x}_1 \bar{x}_2 x_3$$

$$P_4 = x_1 x_3$$

Output of OR plane:

$$f_1 = x_1 x_2 + x_1 \bar{x}_3 + \bar{x}_1 \bar{x}_2 x_3$$

$$f_2 = x_1 x_2 + \bar{x}_1 \bar{x}_2 x_3 + x_1 x_3$$

Figure 3.27. Customary schematic for the PLA in Figure 3.26.

Programmable array logic (PAL) device

□ Programmable array logic (PAL) device

PAL is a programmable logic device similar to PLA.

□ Difference between PLA and PAL

- PLA: both AND plane and OR plane are programmable.
 - PAL: Only AND plane is programmable, while OR plane is fixed.
-

An example of a PAL

 


Figure 3.28. An example of a PLA.

Comparison between PLA and PAL

☐ Comparison between PLA and PAL

■ Drawbacks of PLA

- ☐ PLA were hard to be implemented
- ☐ PLA reduced the speed performance of circuits.

■ Advantage of PAL

- ☐ Simple to manufacturers
- ☐ Less expensive
- ☐ Better performance

■ Disadvantage of PAL

- ☐ Not flexible as compared PLA, because OR plane is fixed.
-

Complex Programmable Logic Device (CPLDs)

- ❑ SPLDs, including PLA, PAL, and etc, are useful for implementing a wide variety of small digital circuits.
 - ❑ CPLD are used to implement more sophisticated type of chip.
-

Complex Programmable Logic Device (CPLDs)

- A CPLD comprises multiple circuit blocks on a single chip, with internal wiring resources to connect the circuit blocks.
 - Each circuit block is similar to a PLA or a PAL
 - We will refer to the circuit blocks as PAL-like blocks.
-

Complex Programmable Logic Device (CPLDs)

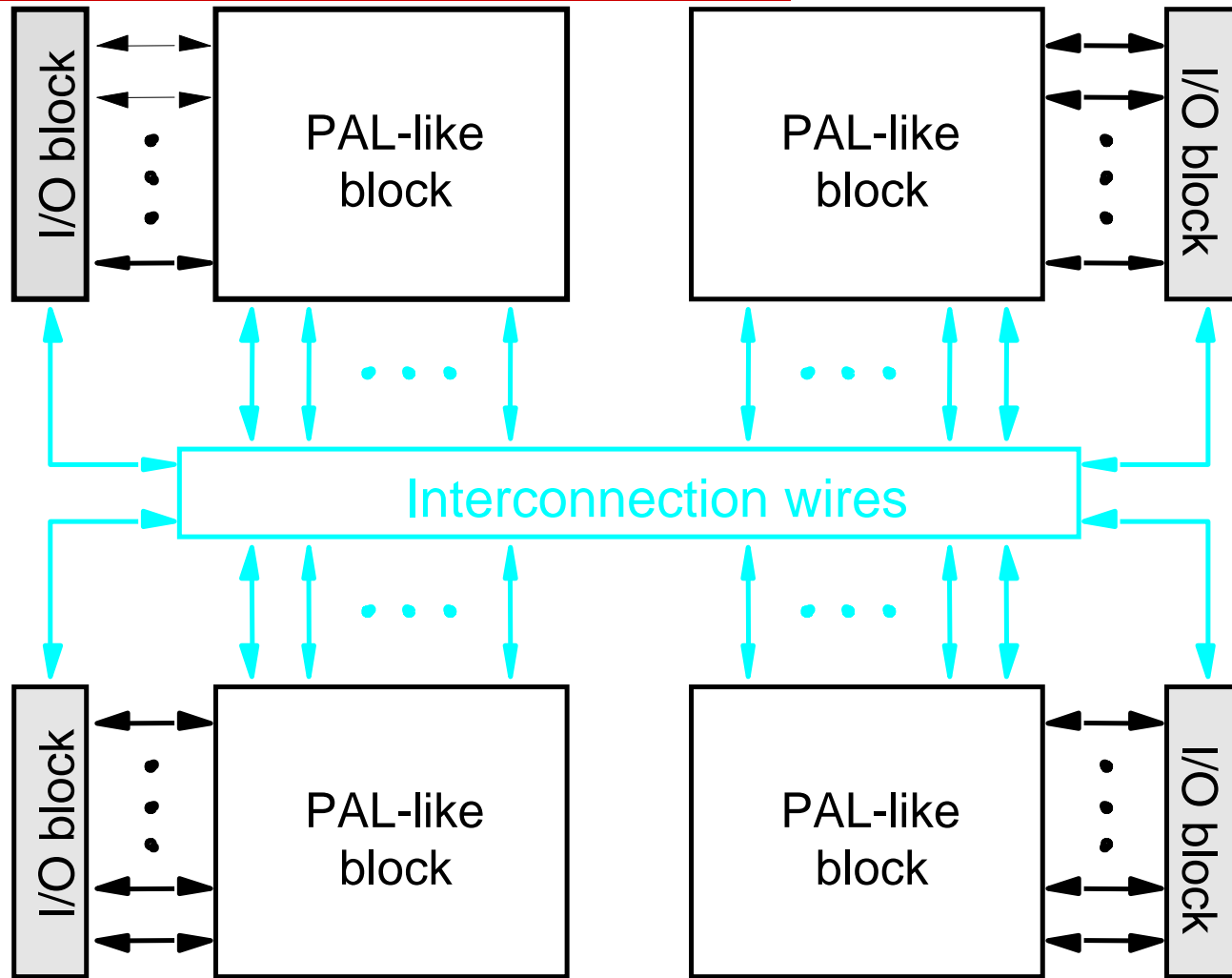


Figure 3.32. Structure of a complex programmable logic device (CPLD).


Field-Programmable Gate Arrays (FPGA)

- ❑ Larger and larger logic circuits need to accommodate in a single chip.
 - ❑ One way to quantify a circuit's size is to assume that the circuit is to be built using only simple logic gates and then estimate how many of these gates are needed.
 - ❑ A commonly used measure is the total number of two-input NAND gates. This measure is often called the number of **equivalent gates**.
 - ❑ By modern standards, a logic circuit with 10,000 gates is not large.
-

Field-Programmable Gate Arrays (FPGA)

- ❑ FPGA is a programmable logic device that supports implementation of relatively large logic circuits.
 - ❑ Not like CPLD, FPGAs do not contain AND or OR planes.
 - ❑ Instead, FPGAs provide logic blocks for connecting to the pins of the package, and interconnection wires and switches.
-

General structure of an FPGA

 


- The **logic blocks** are arranged in a two-dimensional array, depicted as hollow black box;
- The interconnection wires, depicted as solid blue box, are organized as horizontal and vertical **routing channels** between rows and columns of logic blocks.
- Programmable connections also exist between I/O blocks and the interconnection wires.
- FPGA can implement circuit of more than a million equivalent gates in size.

(a) General structure of an FPGA

Lookup Table (LUT)

- ❑ Lookup table (LUT) is the most commonly used logic block in FPGA.
 - ❑ A lookup table contains **storage cells** that are used to implement a small logic function.
 - ❑ Each cell is capable of holding a single logic value, either 0 or 1.
 - ❑ LUTs of various sizes may be created, where the size is defined by the number of inputs.
 - ❑ LUTs are implemented by using multiplexers.
-

Circuits for a two-input lookup table

 


(a) Circuit for a two-input LUT

Figure 3.36. A two-input lookup table (LUT).

Example of a two-input lookup table

| x_1 | x_2 | f_1 |
|-------|-------|-------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

(b) $f_1 = \bar{x}_1\bar{x}_2 + x_1x_2$

 

(c) Storage cell contents in the LUT

Figure 3.36. A two-input lookup table (LUT).

A three-input LUT


 


Figure 3.37. A three-input LUT.

 

- This section includes 3 lookup tables.
- Using the 3 lookup tables, we implement output function f .

$$f_1 = x_1 x_2$$

$$f_2 = \bar{x}_2 x_3$$



$$f = f_1 + f_2$$

Figure 3.39. A section example of a programmed FPGA.