

Agilent EEsof EDA

Impedance Matching Techniques for VLSI Packaging

This document is owned by Agilent Technologies, but is no longer kept current and may contain obsolete or inaccurate references. We regret any inconvenience this may cause. For the latest information on Agilent's line of EEsof electronic design automation (EDA) products and services, please go to:

www.agilent.com/find/eesof

Impedance Matching Techniques for VLSI Packaging



Agilent Technologies



Agilent Technologies

Impedance Matching Techniques for VLSI Package

Acknowledgement

Author : **Brock J. LaMeres, Ph.D.**

Co-Authors: **Rajesh Garg**
Kanupriya Gulati
Sunil P. Khatri, Ph.D

Texas A&M University

Texas A&M University

Texas A&M University



Problem Statement

- Reflections from interconnect will limit VLSI system performance
- This is caused by :
 - 1) Parasitics of the Package Interconnect
 - 2) Faster Risetimes in Off-chip Driver Circuitry



Agenda

1) Package Interconnect Parasitics

2) Proposed Solution


3) Experimental Results



Agilent Technologies

Impedance Matching Techniques for VLSI Package

Why is packaging limiting performance?

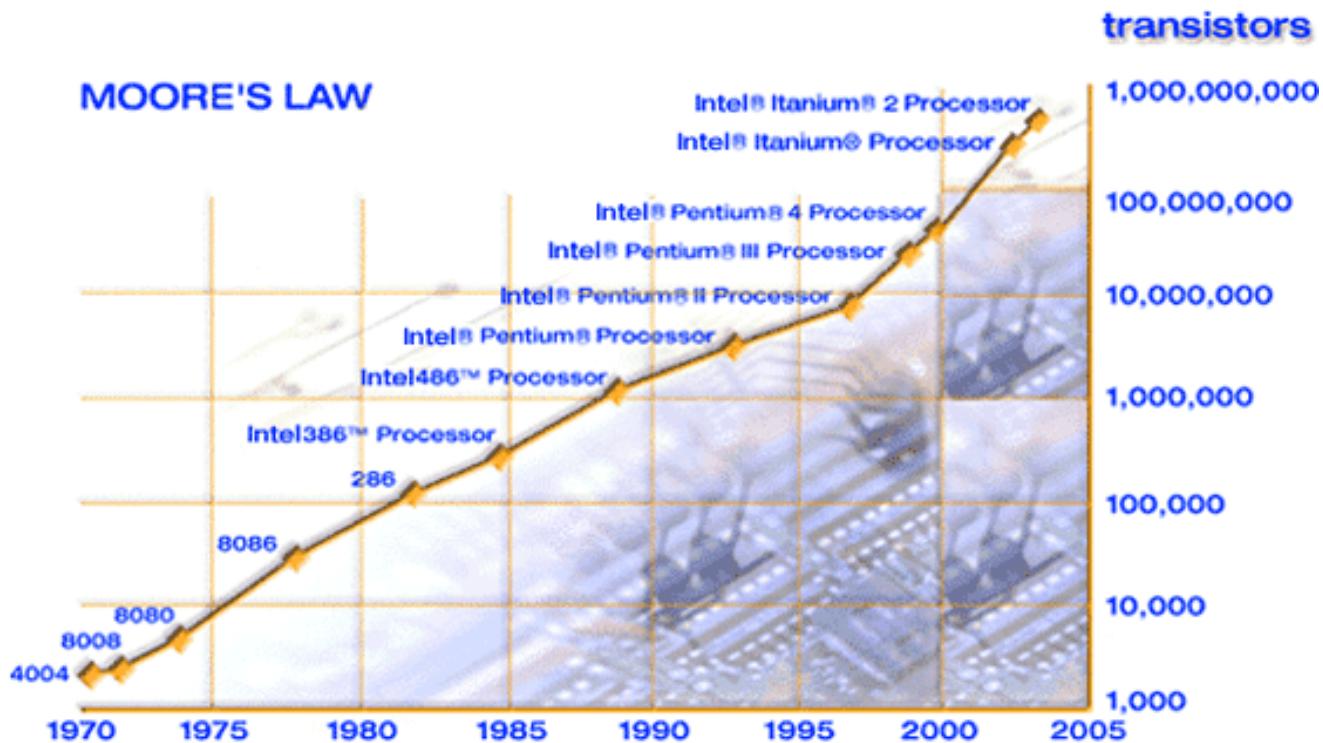

Transistor Technology is Outpacing Package Technology


Why is packaging limiting performance?

- Today's Package Interconnect Looks Inductive

- Long interconnect paths
- Large return loops

$$- L = \frac{\Phi}{I}$$


Wire Bond Inductance (~2.8nH)

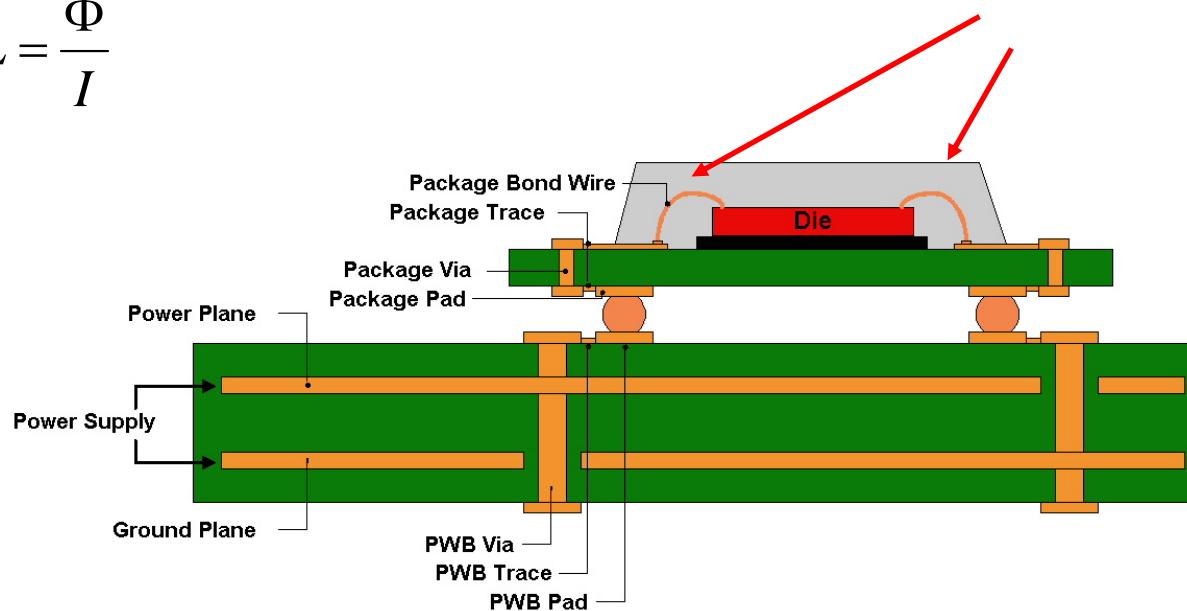

Why is packaging limiting performance?

- **Inductive Interconnect Leads to Reflections**

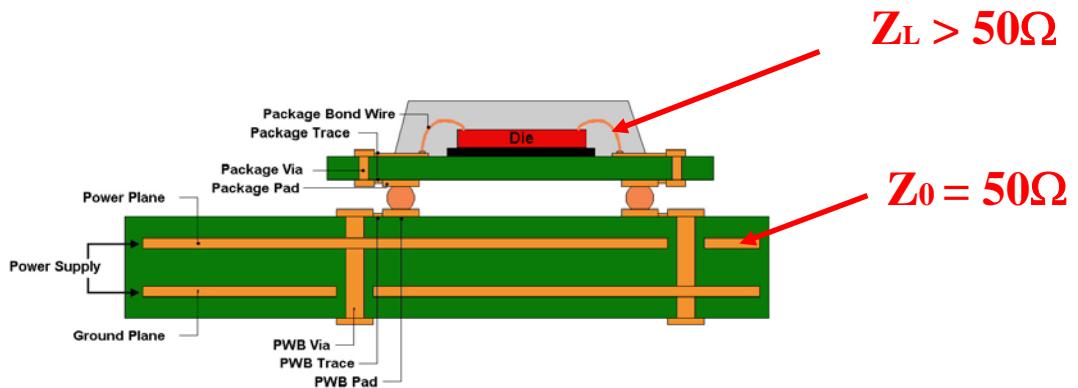
- Interconnect is not matched to system
- Reflections occur due to interconnect




$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

Why is packaging limiting performance?

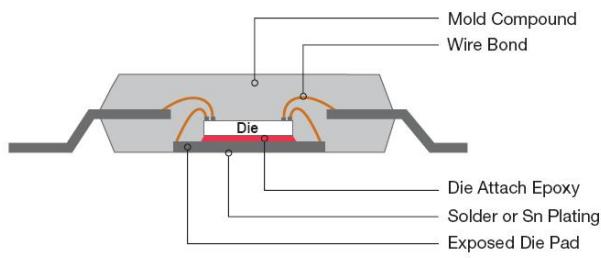
- **Aggressive Package Design Helps, but is expensive...**
 - 95% of VLSI design-starts are wire bonded
 - Goal: Extend the life of wire bonded packages



QFP – Wire Bond : 4.5nH → \$0.22 / pin

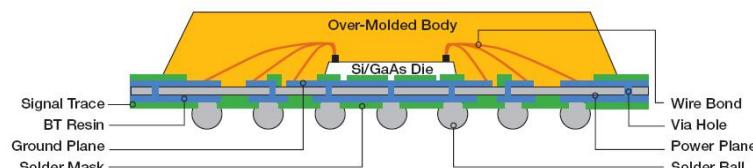

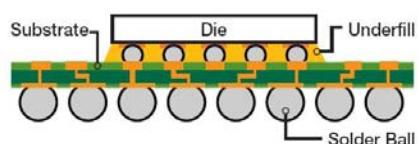BGA – Wire Bond : 3.7nH → \$0.34 / pin ***



BGA – Flip-Chip : 1.2nH → \$0.63 / pin



Why Now?

Cost

- Historically, the transistor delay has dominated performance.
- Inexpensive packaging has met the electrical performance needs.

Faster Risetimes

- As transistors shrink, faster risetimes can be created.
- Everything in the package becomes a transmission line.

Impedance Matching

- The impedance of the package is not matched to the system.
- This leads to reflections from the inductive wire bond in the package



Current Solution to Reflections


- **Live with the Signal Path Reflections**

1) Run the signals slow enough so that reflections are small

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} < 10\%$$

2) Terminate Signals on the Mother board so that reflections are absorbed

On Mother Board Termination

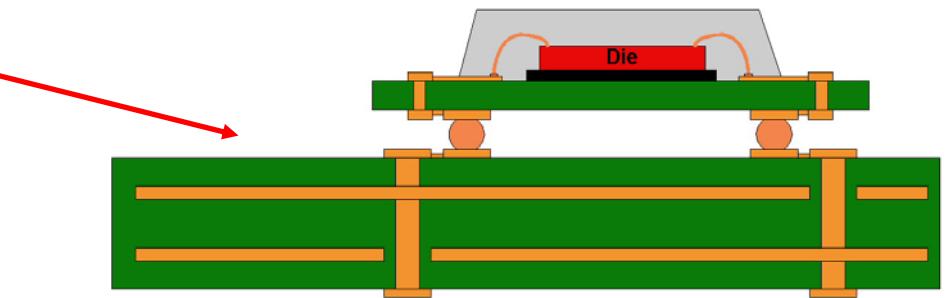

Current Solution to Reflections

- **Limitations of Approach**

1) Run the signals slow enough so that reflections are small

- **Limits System Performance**

2) Terminate Signals on the Mother board so that reflections are absorbed

- **This only eliminates primary reflections, the second still exists**



Proposed Solutions – Impedance Compensation

- **Add Capacitance Near Bond Wire to Reduce Impedance**


- Adding additional capacitance lowers the wire bond impedance
- Impedance can be matched to system, reducing reflections

$$Z_{WireBond} = \sqrt{\frac{L_{WireBond}}{C_{WireBond}}}$$

← Add Capacitance to lower Z

Proposed Solutions – Impedance Compensation

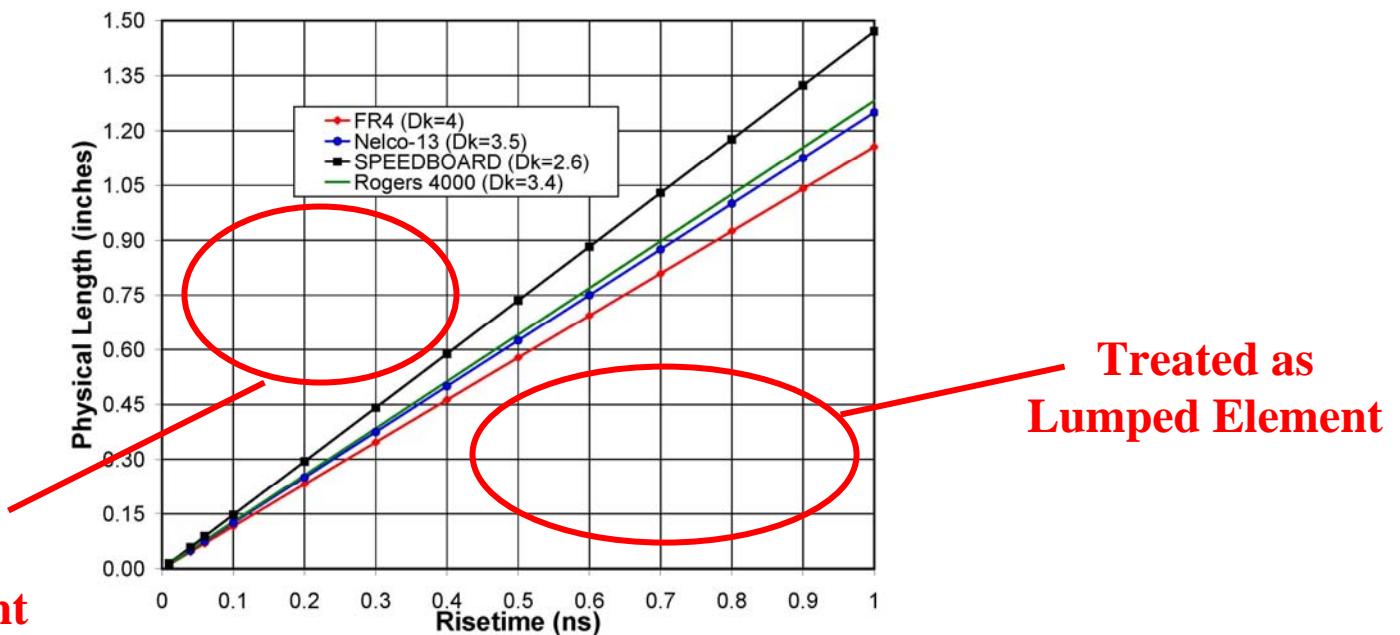- If the capacitance is close to the wire bond, it will alter its impedance
 - Electrical lengths less than 20% of risetime are treated as lumped elements
 - For modern dielectrics, anything within 0.15" of wire bond is lumped




Treated as
Distributed Element

Treated as
Lumped Element


Proposed Solutions – Impedance Compensation

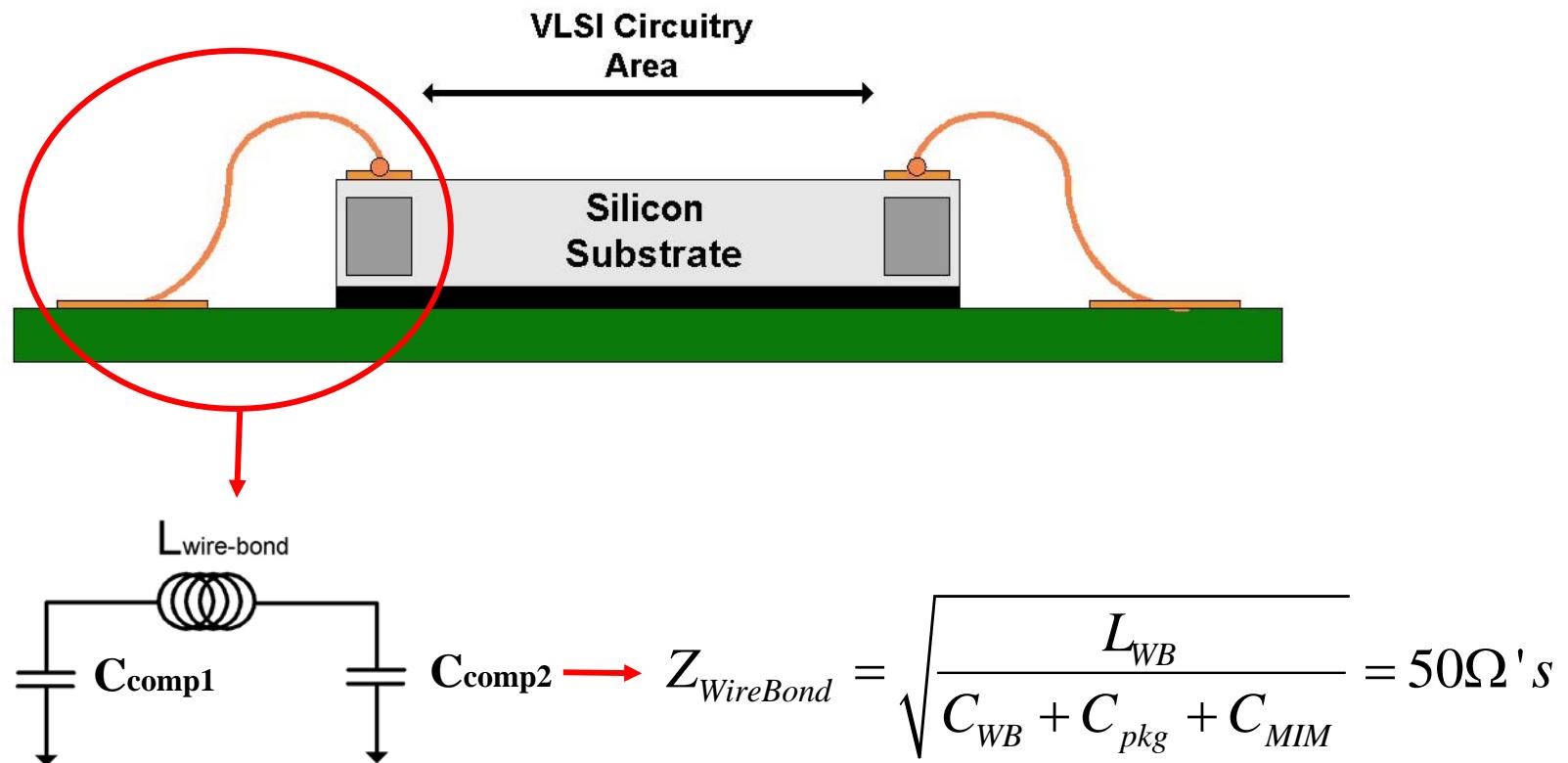- Capacitance on the IC or Package is close enough to alter impedance



Static Compensator

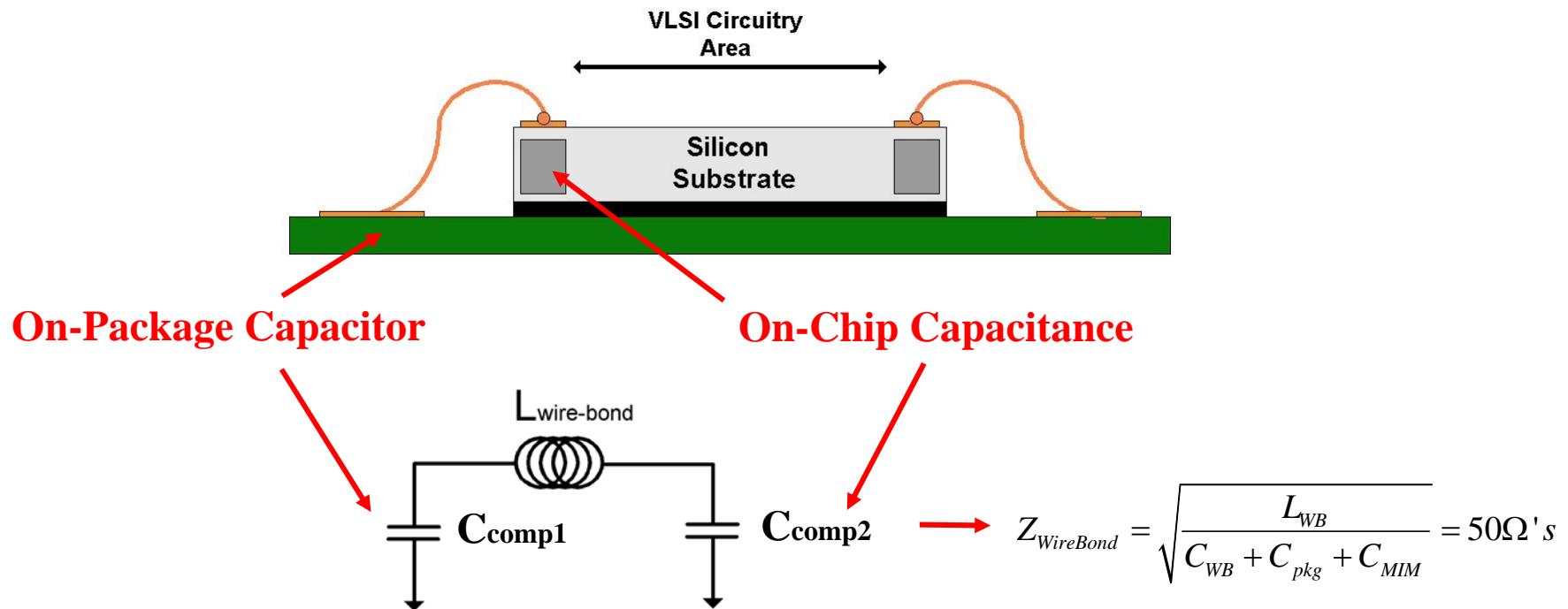
- Capacitor values chosen prior to fabrication
 - Equal amounts of capacitance are used on-chip and on-package



Static Compensator

- **On-Package Capacitors**

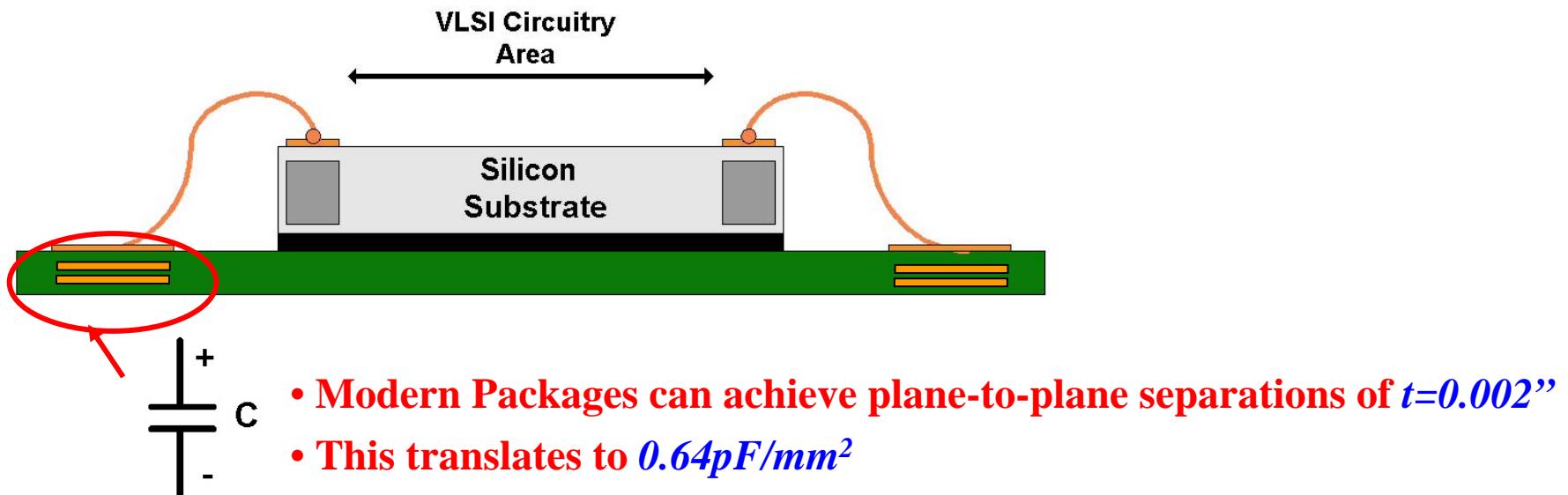
- Embedded capacitor construction is used
- No components are needed, reducing package cost
- Capacitance values needed can be implemented using this construction



Static Compensator

- **On-Chip Capacitors**

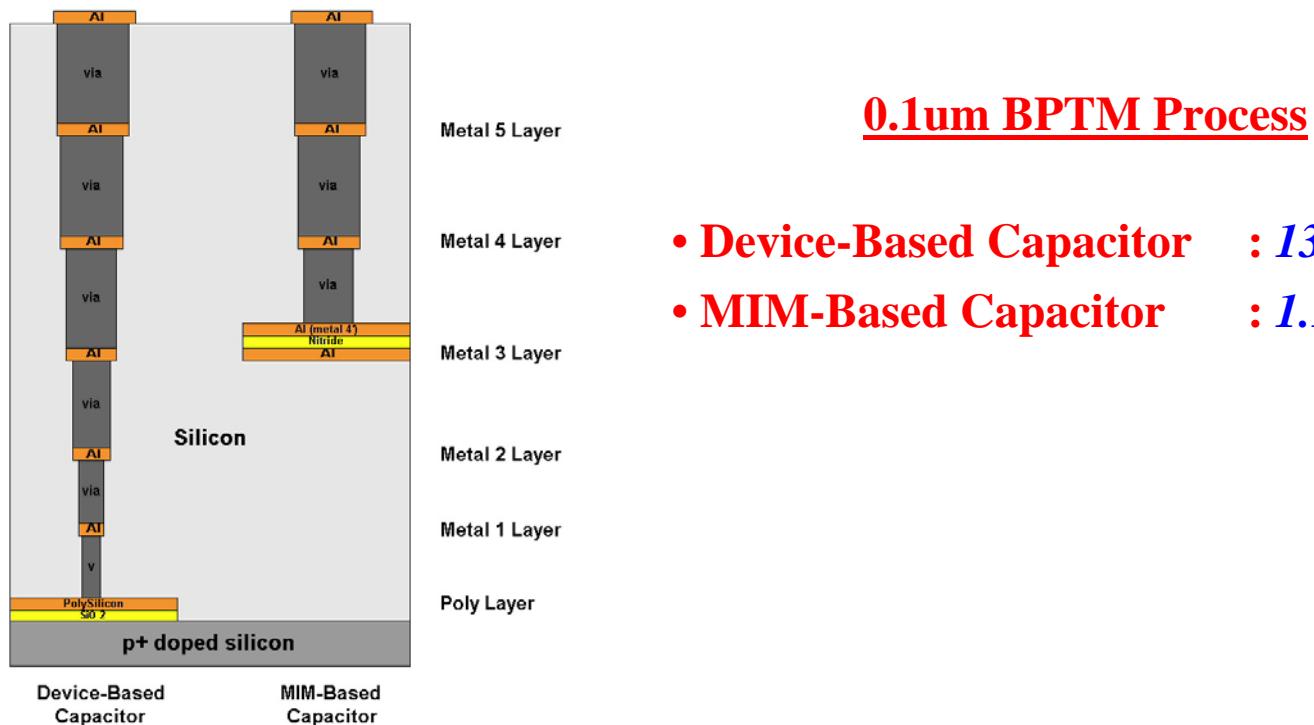- Device and MIM capacitors are evaluated
- Targeting area beneath wire bond pad, which is typically unused



Static Compensator

- **Wire Bond Modeling**

- Typical VLSI wire bond lengths range from 1mm to 5mm
- Electrical parameter extraction is used to find **L** and **C** or wire bond

<u>Length</u>	<u>L</u>	<u>C</u>	<u>Z₀</u>
1mm	0.569nH	26fF	148Ω
2mm	1.138nH	52fF	148Ω
3mm	1.707nH	78fF	148Ω
4mm	2.276nH	104fF	148Ω
5mm	2.845nH	130fF	148Ω

Static Compensator

• On-Package Capacitor Sizing

- Capacitor values are found to match wire bond to **50Ω**
- Area is evaluated for feasibility

<u>Length</u>	<u>C_{comp1}</u>		<u>C_{comp2}</u>		
<u>L</u>	<u>C</u>	<u>Area</u>	<u>C</u>	<u>Area_{MIM}</u>	<u>Area_{Device}</u>
1mm	102 fF	388 um ²	102 fF	10 um ²	2.7 um ²
2mm	208 fF	554 um ²	208 fF	14 um ²	3.9 um ²
3mm	325 fF	692 um ²	325 fF	18 um ²	4.9 um ²
4mm	450 fF	815 um ²	450 fF	21 um ²	5.8 um ²
5mm	575 fF	921 um ²	575 fF	24 um ²	6.5 um ²

Experimental Results: Static Compensator

- **Time Domain Analysis (TDR)**

- Simulation Performed using

Advanced Design System from Agilent




$Length_{wb}$	$\Gamma_{No-Comp}$	$\Gamma_{MIM-Comp}$	$\Gamma_{Device-Comp}$
1 mm	4.5%	0.05%	0.5%
2 mm	8.7%	0.4%	1.2%
3 mm	12.7%	1.3%	2.4%
4 mm	16.4%	2.7%	4.1%
5 mm	19.8%	4.8%	6.0%


Worst Case : 5mm

No Static Capacitance = **19.8%**

w/ Static Capacitance = **4.8%**

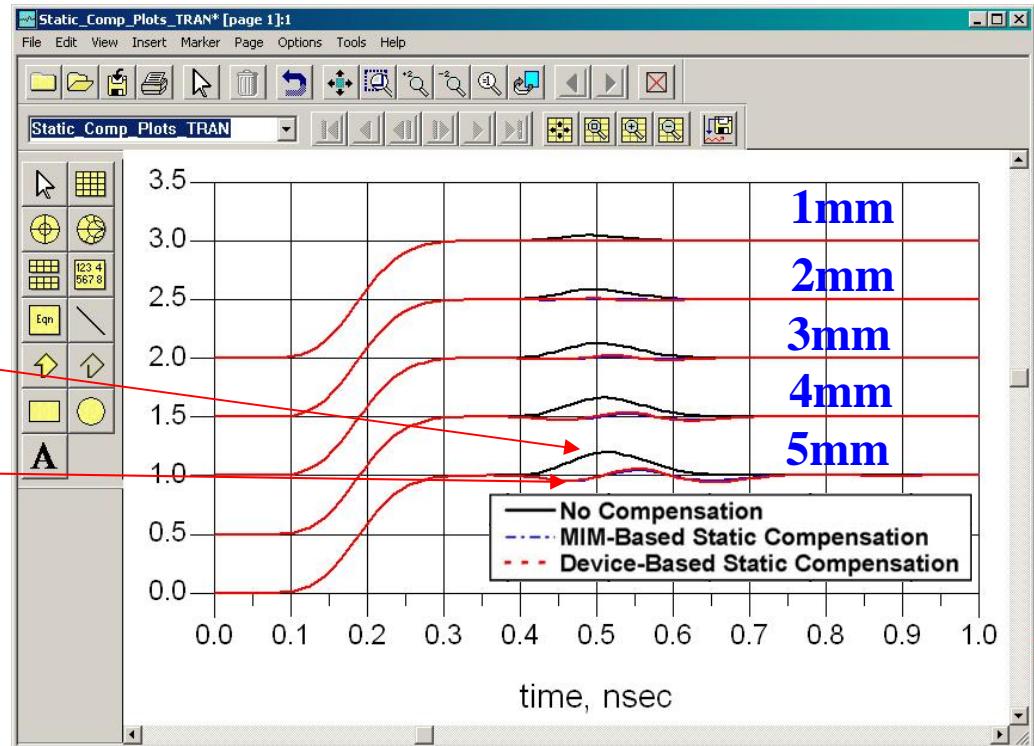


Frequency Domain Analysis (Z_{in})

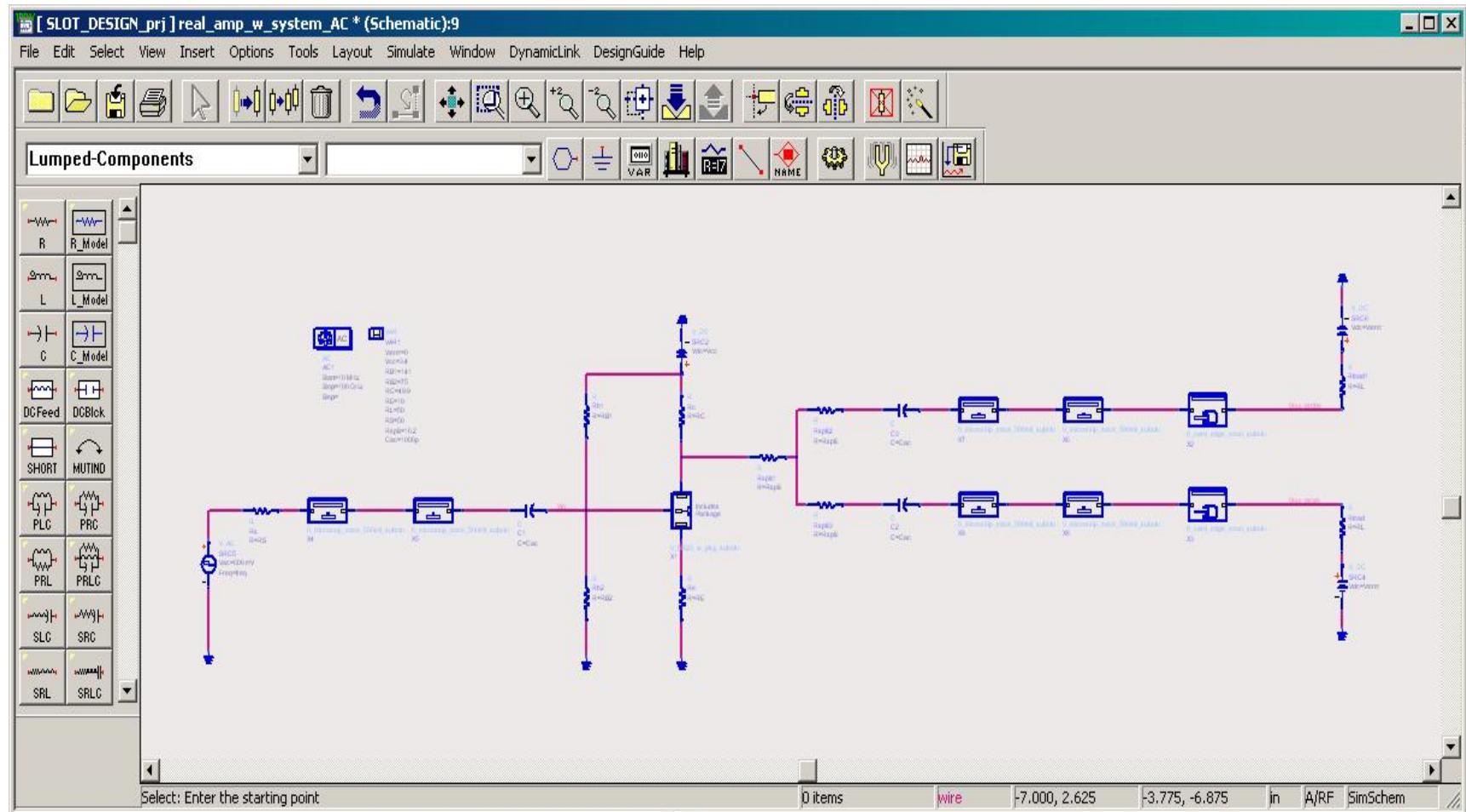

Experimental Results: Static Compensator

- Frequency Domain Analysis (Z_{in})

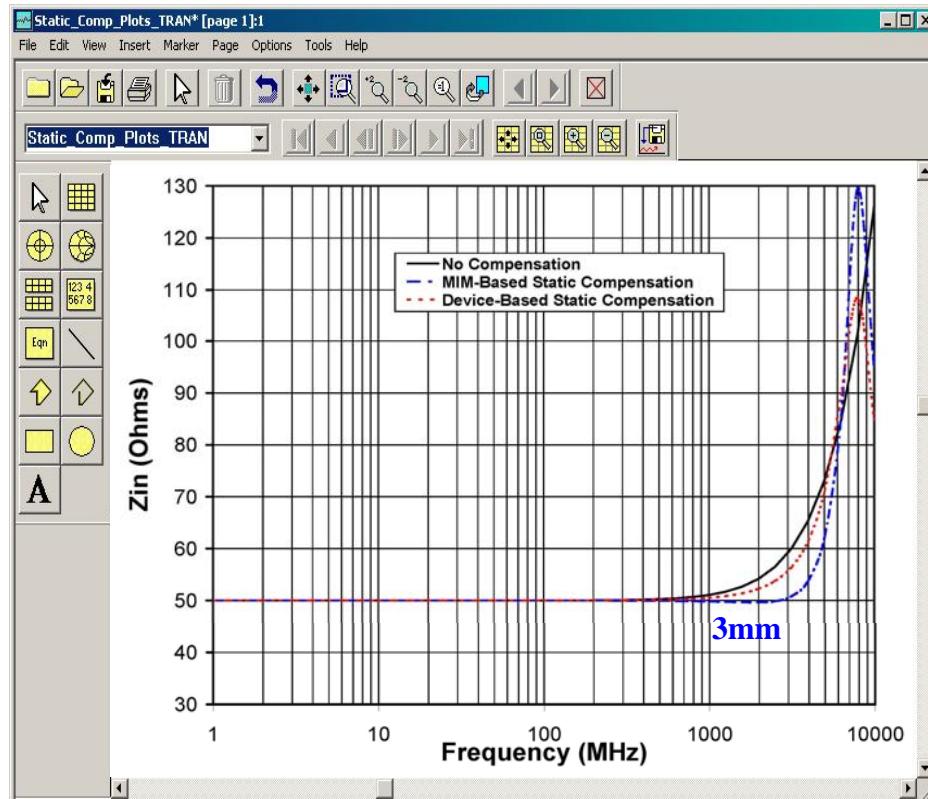

Worst Case : 5mm

$f_{+/-10\% \text{ No Static Capacitance}} = 1.9 \text{ GHz}$

$f_{+/-10\% \text{ w/ Static Capacitance}} = 3.0 \text{ GHz}$

$Length_{wb}$	$f_{No-Comp}$	$f_{MIM-Comp}$	$f_{Device-Comp}$
1 mm	9.3 GHz	14 GHz	12 GHz
2 mm	4.7 GHz	7.1 GHz	5.7 GHz
3 mm	3.1 GHz	4.8 GHz	3.8 GHz
4 mm	2.4 GHz	3.7 GHz	2.9 GHz
5 mm	1.9 GHz	3.0 GHz	2.5 GHz

Static Compensator

- **Limitations of Approach**

- Process/Design variation in wire bonds and capacitors lead to error
- Each wire bond must be evaluated for compensation requirements

- **Possible Enhancement**



- Altering compensation capacitance after fabrication
- i.e., *Dynamic Compensator*



Dynamic Compensator

- Programmable capacitance is placed on-chip
 - On-chip capacitance is close enough to alter wire bond impedance
 - Active circuitry on-chip can switch in different amounts of capacitance


On-Chip Programmable Compensation

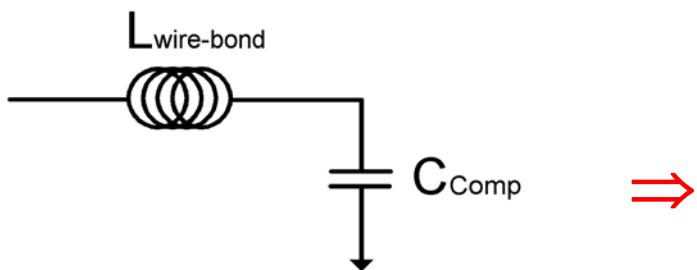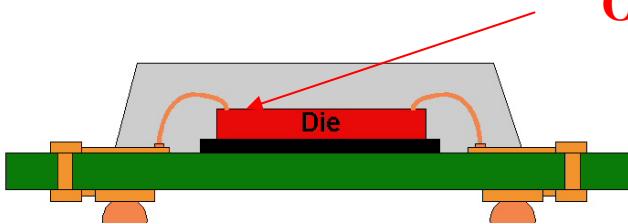

$$Z_{WireBond} = \sqrt{\frac{L_{WB}}{C_{WB} + C_{Comp}}} = 50\Omega \cdot s$$

Dynamic Compensator

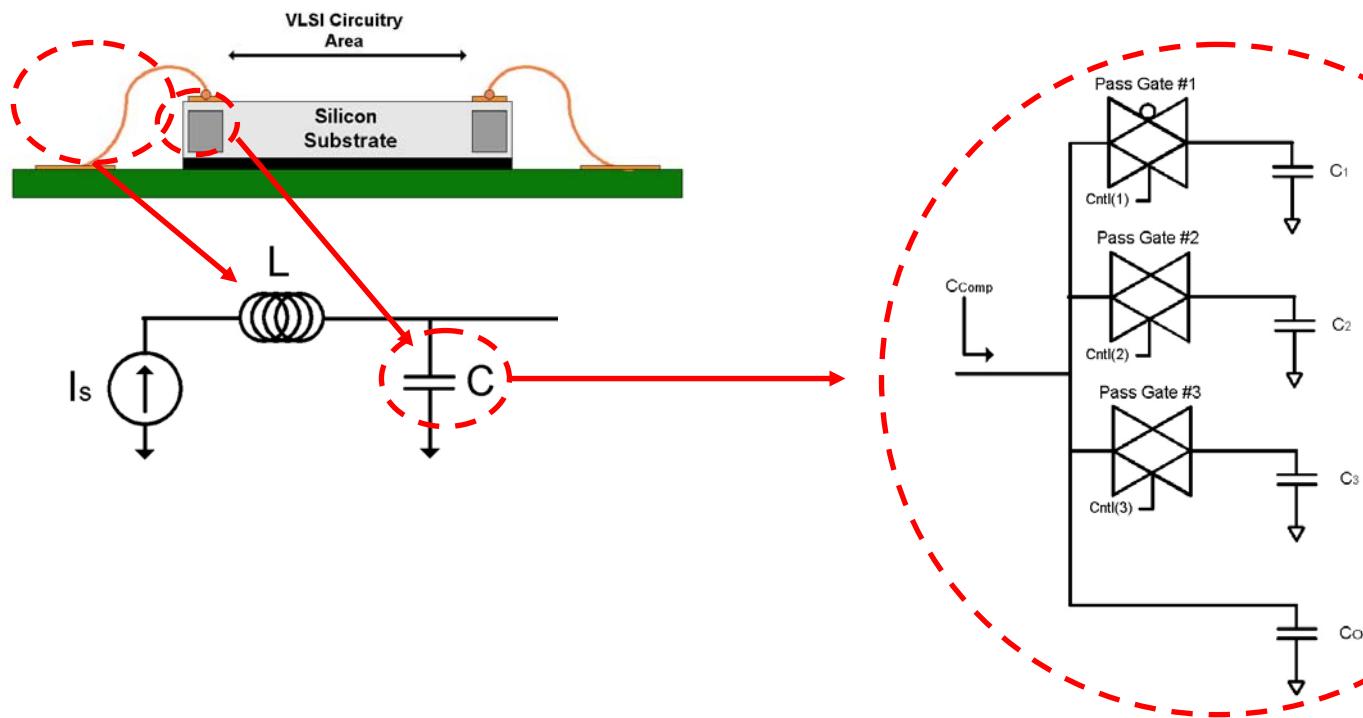
- Pass Gates are used to switch in on-chip capacitors
 - Pass gates connect on-chip capacitance to the wire bond inductance
 - Pass gates have control signals which can be programmed after fabrication



Dynamic Compensator

- **On-Chip circuitry is independent of package**
 - Compensation works across multiple package technologies
 - This decouples IC and Package design

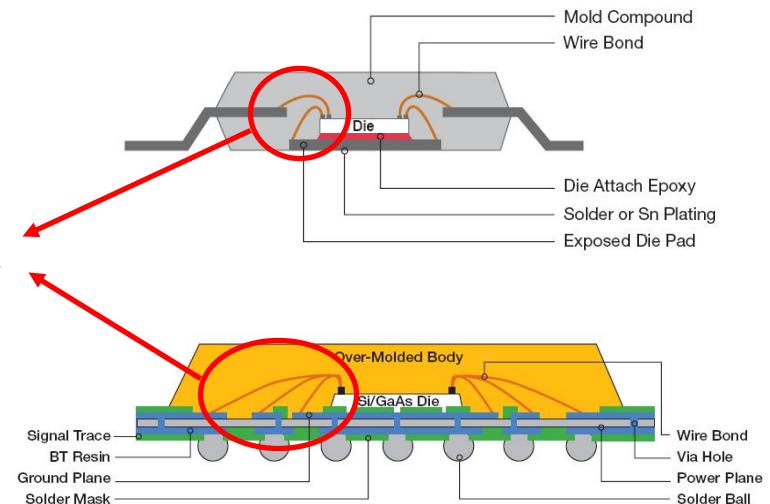Only IC technology is used for compensation



Dynamic Compensator

- **On-Chip capacitor sizing**

- The on-chip capacitance performs the compensation to **50Ω**
- The circuit must cover the entire range of wire bond inductances
- The diffusion capacitance of the pass gates must be included in the analysis

<u>Length</u>	<u>C_{comp}</u>	
<u>L</u>	<u>C</u>	
1mm	202 fF	
2mm	403 fF	
3mm	605 fF	
4mm	806 fF	
5mm	1008 fF	

200 fF \leq C_{comp} \leq 1010 fF


Dynamic Compensator

• Compensator Design

- The on-chip capacitance performs the compensation to 50Ω
- The diffusion capacitance of the pass gates must be included in the analysis

<u>Length</u>	<u>C_{comp}</u>
<u>L</u>	
1mm	202 fF
2mm	403 fF
3mm	605 fF
4mm	806 fF
5mm	1008 fF

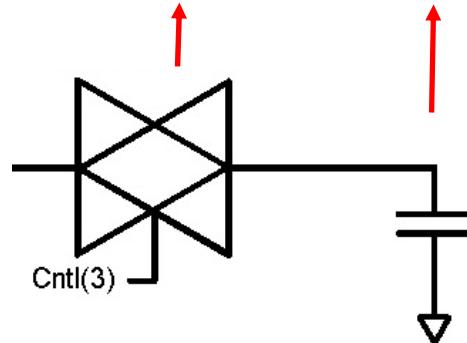
$$C_{\text{bank}} = \frac{1}{3}(C_{\text{bank}}) + \frac{2}{3}(C_{\text{bank}})$$



Dynamic Compensator

- **Capacitance Design**

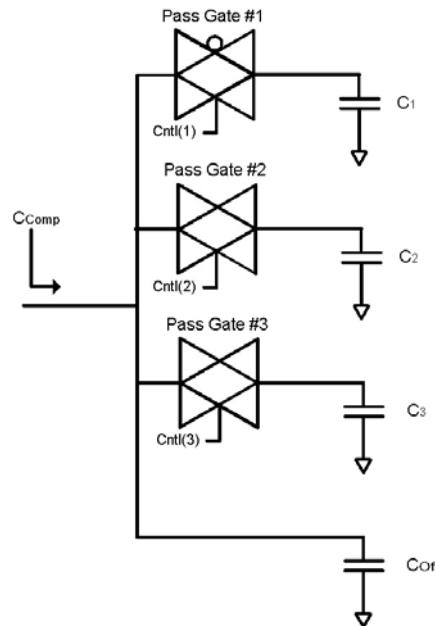- Pass Gates are sized to drive the on-chip capacitance
- Each *bank* of capacitance includes the pass gates



$$C_{bank1} = C_{pg1} + C_{int1}$$

$$C_{bank2} = C_{pg2} + C_{int2}$$

$$C_{bank3} = C_{pg3} + C_{int3}$$

$$C_{Off} = \text{Range Offset}$$



Dynamic Compensator

- **Capacitance Design**

- Again, both MIM and Device-based capacitors are evaluated for area

	MIM-Based	Device-Based
Component	Area (W × L)	Area (W × L)
Pass Gate #1	$32.4\mu\text{m} \times 0.1\mu\text{m}$	$32.4\mu\text{m} \times 0.1\mu\text{m}$
Pass Gate #2	$62.5\mu\text{m} \times 0.1\mu\text{m}$	$62.5\mu\text{m} \times 0.1\mu\text{m}$
Pass Gate #3	$129.6\mu\text{m} \times 0.1\mu\text{m}$	$129.6\mu\text{m} \times 0.1\mu\text{m}$
C_{off}	$8.5\mu\text{m} \times 8.5\mu\text{m}$	$2.5\mu\text{m} \times 2.5\mu\text{m}$
C_1	$11\mu\text{m} \times 11\mu\text{m}$	$3.3\mu\text{m} \times 3.3\mu\text{m}$
C_2	$15.5\mu\text{m} \times 15.5\mu\text{m}$	$4.6\mu\text{m} \times 4.6\mu\text{m}$
C_3	$22\mu\text{m} \times 22\mu\text{m}$	$6.6\mu\text{m} \times 6.6\mu\text{m}$
Total	$65\mu\text{m} \times 65\mu\text{m}$	$25\mu\text{m} \times 25\mu\text{m}$

Experimental Results: Dynamic Compensator


- **Time Domain Analysis (TDR)**

- Simulation Performed using

Advanced Design System from Agilent



$Length_{wb}$	$\Gamma_{No-Comp}$	$\Gamma_{MIM-Comp}$	$\Gamma_{Device-Comp}$	Setting
1 mm	4.5%	1.0%	1.0%	001
2 mm	8.7%	1.8%	1.3%	011
3 mm	12.7%	3.6%	3.0%	100
4 mm	16.4%	4.3%	3.3%	110
5 mm	19.8%	6.0%	5.0%	111

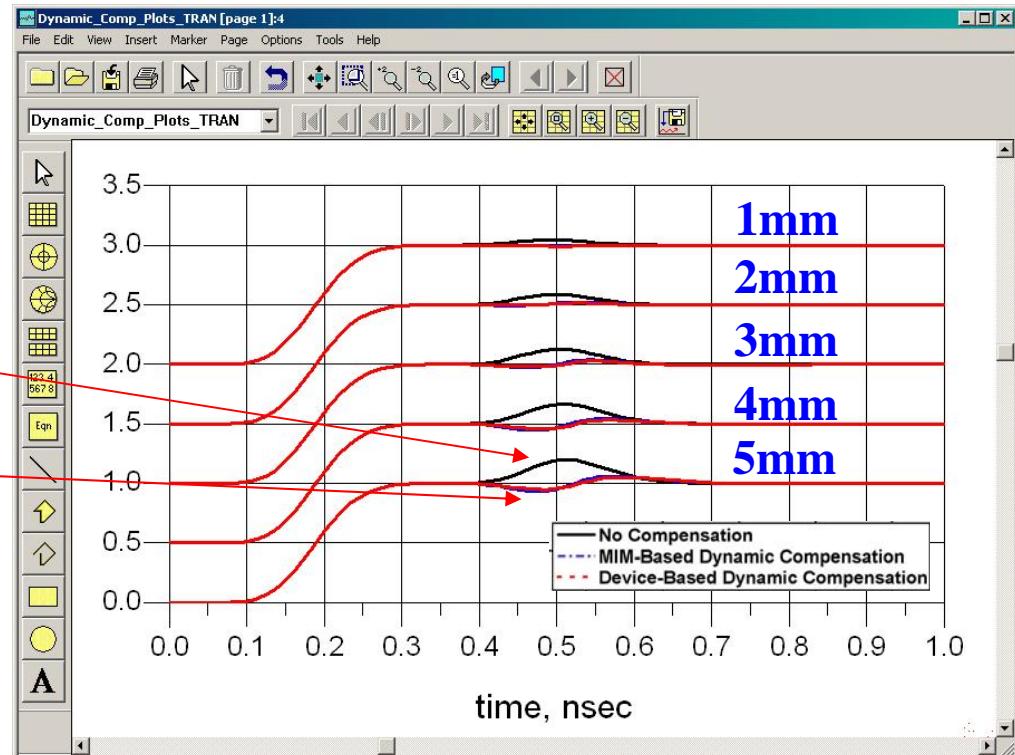


Worst Case : 5mm

No Dynamic Capacitance = **19.8%**


w/ Dynamic Capacitance = **5.0%**

Frequency Domain Analysis (Z_{in})

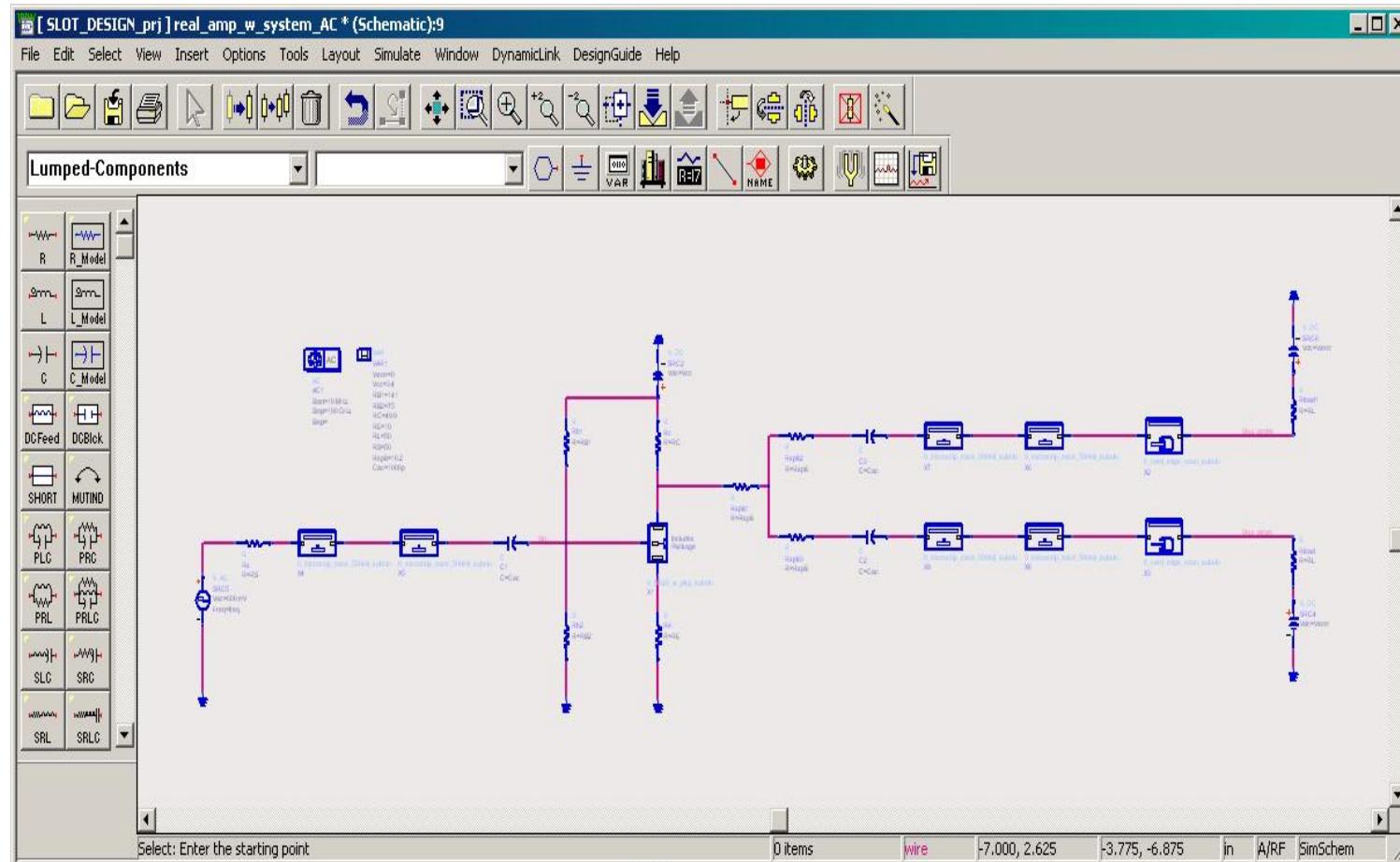

Experimental Results: Dynamic Compensator

- Frequency Domain Analysis (Z_{in})

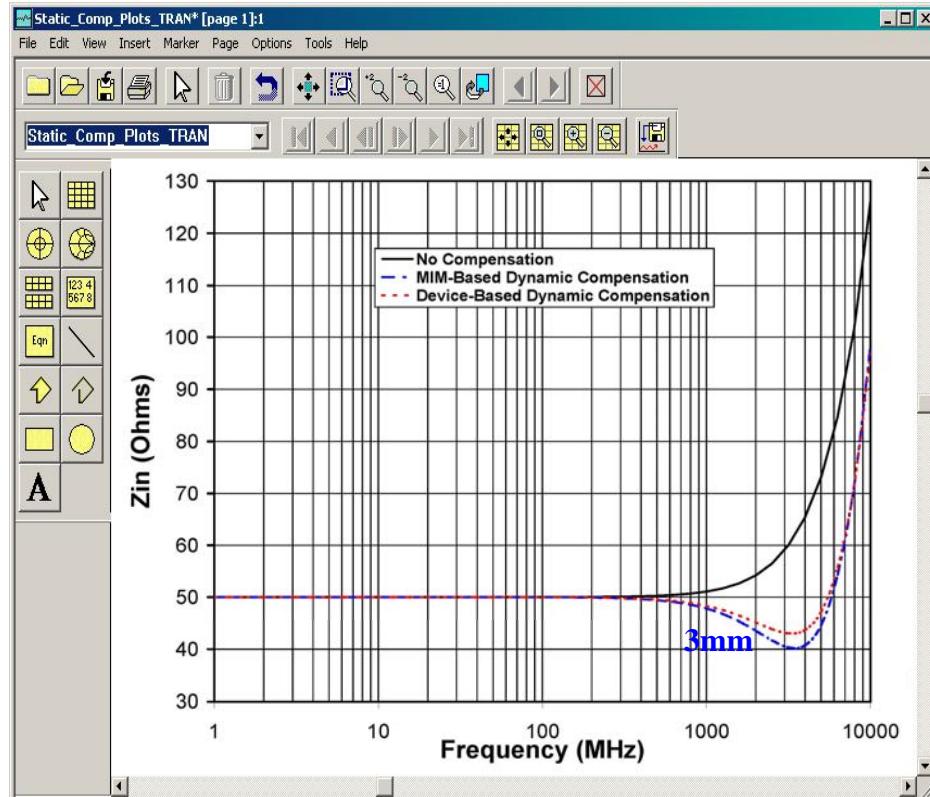

Worst Case : 5mm


$f_{+/-10\% \text{ No Dynamic Capacitance}} = 1.9 \text{ GHz}$

$f_{+/-10\% \text{ w/ Dynamic Capacitance}} = 4.1 \text{ GHz}$

$Length_{wb}$	$f_{No-Comp}$	$f_{MIM-Comp}$	$f_{Device-Comp}$
1 mm	9.3 GHz	20 GHz	20 GHz
2 mm	4.7 GHz	10.1 GHz	10 GHz
3 mm	3.1 GHz	6.8 GHz	6.7 GHz
4 mm	2.4 GHz	5.2 GHz	5.1 GHz
5 mm	1.9 GHz	4.2 GHz	4.1 GHz

Inductive Compensator

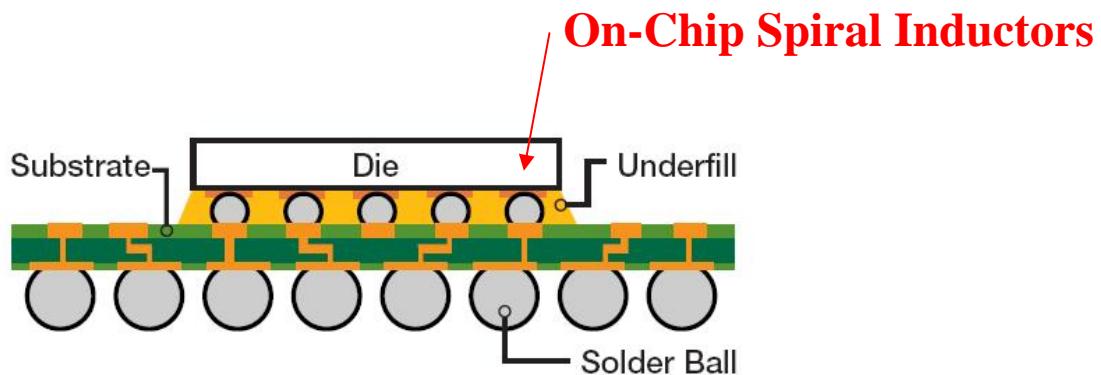- The same theory can be applied to capacitive interconnect
- Spiral Inductors can be added on-chip
 - On-chip inductance is close enough to alter capacitive interconnect impedance
 - Spiral inductors are a proven on-chip technology



$$\Rightarrow Z_{Flip-Chip} = \sqrt{\frac{L_{FC} + L_{Comp}}{C_{FC}}} = 125\Omega \cdot s$$

Experimental Results: Inductor Compensator

- **Time Domain Analysis (TDR)**

- Simulation Performed using

- Advanced Design System from Agilent*




Worst Case : 5mm

No Inductance

= **2%**


w/ Spiral Inductance

= **>0.1%**

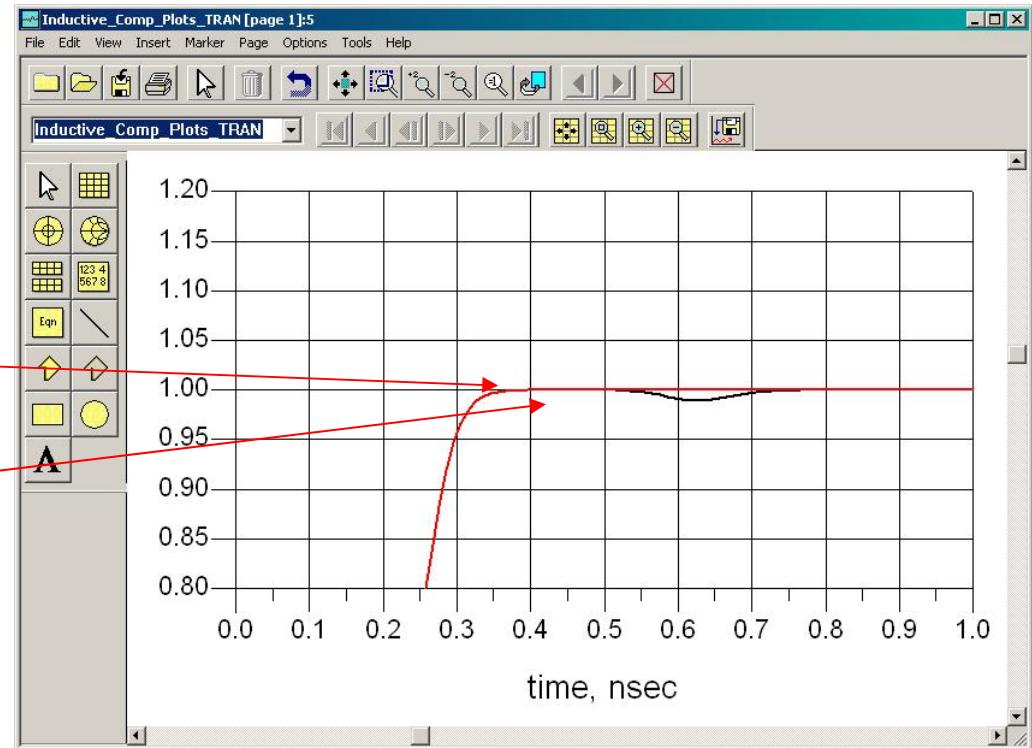

Experimental Results: Inductive Compensator

- Frequency Domain Analysis (Z_{in})

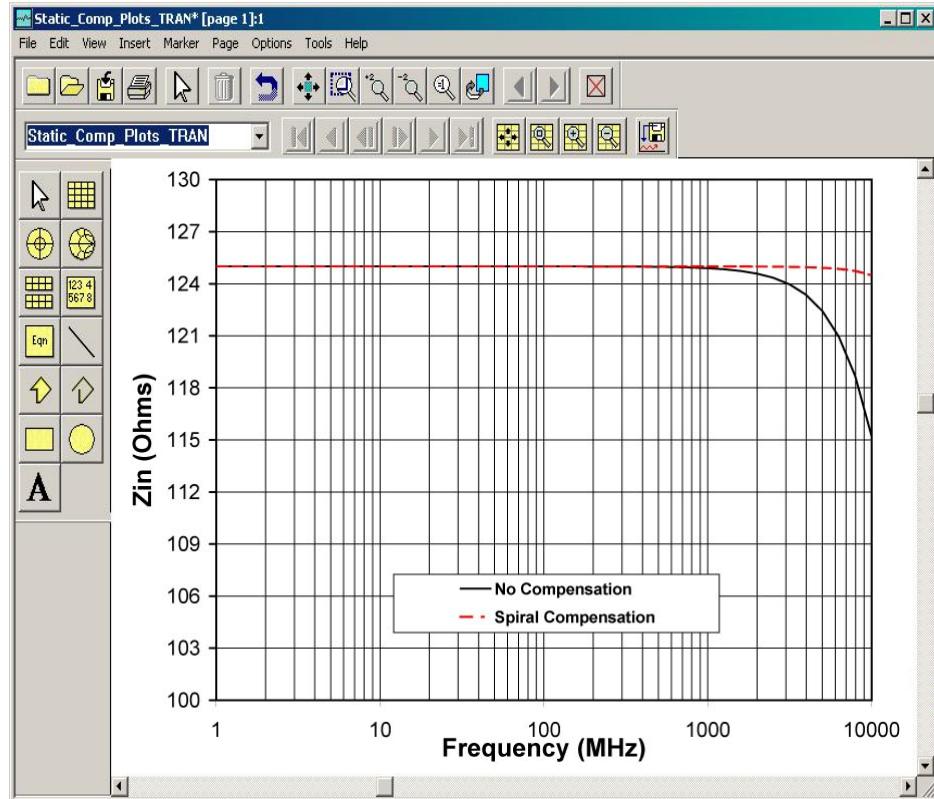

Flip-Chip Matching

$f_{+/-10\%}$ No Spiral Inductance =

10 GHz

$f_{+/-10\%}$ w/ Spiral Inductance >

15 GHz

Summary

- **Package Interconnect causes reflections which limits system performance**
- **The move toward Advanced Packaging is Resisted due to Cost**
- **Adding On-Chip & On-Package capacitors does **not** add cost**
- **A Static and Dynamic Compensation Approach can match the package interconnect impedance to the system**
- **The same approach can be applied to future interconnect structures which look capacitive**



Questions?



Agilent Technologies

Impedance Matching Techniques for VLSI Package

For more information about Agilent EEsof EDA, visit:

www.agilent.com/find/eesof

Agilent Email Updates

www.agilent.com/find/emailupdates
Get the latest information on the products and applications you select.

Agilent Direct

www.agilent.com/find/agilentdirect
Quickly choose and use your test equipment solutions with confidence.

www.agilent.com

For more information on Agilent Technologies' products, applications or services, please contact your local Agilent office. The complete list is available at:

www.agilent.com/find/contactus

Americas

Canada	(877) 894-4414
Latin America	305 269 7500
United States	(800) 829-4444

Asia Pacific

Australia	1 800 629 485
China	800 810 0189
Hong Kong	800 938 693
India	1 800 112 929
Japan	0120 (421) 345
Korea	080 769 0800
Malaysia	1 800 888 848
Singapore	1 800 375 8100
Taiwan	0800 047 866
Thailand	1 800 226 008

Europe & Middle East

Austria	0820 87 44 11
Belgium	32 (0) 2 404 93 40
Denmark	45 70 13 15 15
Finland	358 (0) 10 855 2100
France	0825 010 700*
	*0.125 €/minute
Germany	01805 24 6333**
	**0.14 €/minute
Ireland	1890 924 204
Israel	972-3-9288-504/544
Italy	39 02 92 60 8484
Netherlands	31 (0) 20 547 2111
Spain	34 (91) 631 3300
Sweden	0200-88 22 55
Switzerland	0800 80 53 53
United Kingdom	44 (0) 118 9276201
Other European Countries:	
	www.agilent.com/find/contactus

Revised: March 27, 2008

Product specifications and descriptions in this document subject to change without notice.

© Agilent Technologies, Inc. 2008

Printed in USA, May 26, 2006
5989-9452EN



Agilent Technologies